

73

December 1960

37¢

Amateur Radio

XMAS
1960

W6EXU ✓

K5JKX/6

W2NSD



3U7N ✓

7GU ✓

RS ✓

Y ✓

D ✓

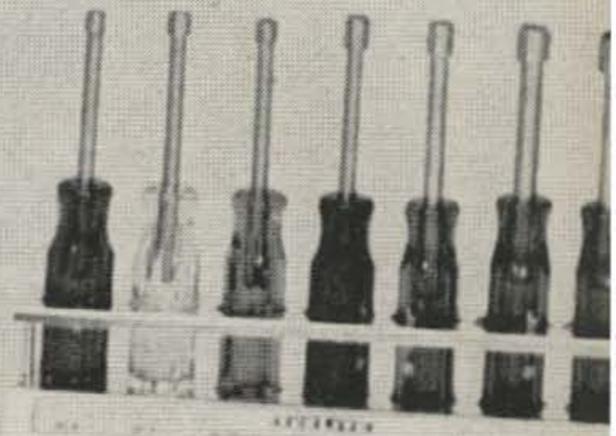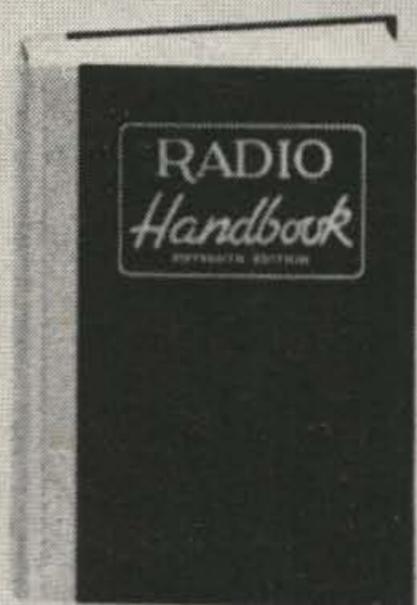

ON THE AIR

AMATEURS

CITIZEN LICENCEES

MOBILETTE 61



MOBILETTE 61, International's *new improved* all transistor, crystal controlled converter provides a "quick and easy" way to convert your car radio for short wave reception. MOBILETTE 61, units cover a specific band of frequencies providing a broad tuning range. Mobilette units are miniature size and quickly interchangeable.

Check these all New features . . . New and improved circuit for increased gain . . . New internal jumper for positive and negative grounds . . . New RF amplifier, mixer/oscillator . . . New separate input for broadcast and short wave antennas . . . Mounting bracket for under dash installation.

MOBILETTE 61, is available in a wide choice of frequencies covering the Amateur bands 75 through 6 meters, Citizens band, Civil Air Patrol

CIVIL AIR PATROL

AMATEURS

CITIZEN LICENCEES

...with improved circuit for mobile short wave reception

Write for International's complete catalog of precision radio crystals, and quality electronic equipment—yours for the asking.

**INTERNATIONAL
CRYSTAL MANUFACTURING CO., INC.**



18 NORTH LEE • OKLAHOMA CITY, OKLA.

low band frequencies, WWV time and frequency standards. Any frequency in the range 2 MC to 50 MC available on special order.*

Designed for 12 VDC, **MOBILETTE 61** will operate on 6 VDC at reduced output. Power connector plugs into cigarette lighter socket.

See the **MOBILETTE 61** at Your Dealer Today.

Mobilette 61 units cover these short wave frequencies.		
Catalog No.	Frequency	
630 - 110	6 meters (Amateur)	50 - 51 MC
630 - 111	10 meters (Amateur)	28.5 - 29.5 MC
630 - 112	11 meters (Citizens)	26.9 - 27.3 MC
630 - 113	15 meters (Amateur)	21 - 21.6 MC
630 - 114	20 meters (Amateur)	14 - 14.4 MC
	15 MC (WWV)	
630 - 115	40 meters (Amateur)	7 - 7.4 MC
630 - 116	75 meters (Amateur)	3.8-4 MC
630 - 117	10 MC (WWV)	
630 - 118	CAP (Low Band)	
630 - 119	Special Frequencies	2 MC - 50 MC

Complete, ready to plug in and operate only \$22.95

**Special frequencies 2 MC -50 MC.....only \$25.95*

from **EICO**® .. a completely new

CITIZENS BAND TRANSCEIVER

that meets
FCC regulations*

*EICO premounts, prewires, pretunes, and seals the ENTIRE transmitter oscillator circuit to conform with FCC regulations (Section 19.71 subdivision d). EICO thus gives you the transceiver in kit form that you can build and put on the air without the supervision of a Commercial Radio-Telephone Licensee!

#760:
117 VAC
Kit
\$59.95
Wired
\$89.95



Kit **\$69.95**
Wired **\$99.95**
#761: 117 VAC & 6 VDC
#762: 117 VAC & 12 VDC
incl. mtg. bracket (Pat. Pend.)

designed
by Hams...
for Hams...

to the highest
Ham standards

Highly sensitive, selective SUPERHET (not regenerative) receiver with 5½ dual function tubes and RF stage. Continuous tuning over all 23 bands. Exclusive Super-Hush® noise limiter. AVC. 3" x 5" PM speaker. Detachable ceramic mike. 5 Watt xtal-controlled transmitter. Variable "pi" network matches most popular antennas. 12-position Posi-Lock® mounting bracket. 7 tubes and 1 xtal (extra xtals available). Covers up to 20 miles. License available to any citizen over 18 — no exams or special skills required; application form supplied free. Antennas optional.

Additional crystals \$3.95 each.


Most EICO distributors offer budget terms.



NEW! 60-WATT CW TRANSMITTER #723
Kit \$49.95 Wired \$79.95
Ideal for novice or advanced ham needing low-power, stand-by rig. 60W CW, 50W external plate modulation. 80 through 10 meters.



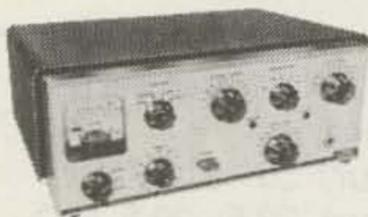COLOR & MONO DC-5MC LAB & TV 5" OSCILLOSCOPE #460
Kit \$79.95 Wired \$129.50
5" PUSH-PULL OSCILLOSCOPE #425 Kit \$44.95 Wired \$79.95



90-WATT CW TRANSMITTER* #720 Kit \$79.95 Wired \$119.95
*U. S. Pat. No. D-184,776
"Top quality" — ELECTRONIC KITS GUIDE. Ideal for veteran or novice. 90W CW, 65W external plate modulation. 80 through 10 meters.




PEAK-TO-PEAK VTVM #232 & *UNI-PROBE®
Kit \$29.95 Wired \$49.95
*U. S. Pat. No. 2,790,051
VACUUM TUBE VOLTMETER #221
Kit \$25.95 Wired \$39.95




HIGH-LEVEL UNIVERSAL MODULATOR-DRIVER #730
Kit \$49.95 Wired \$79.95
Delivers 50W undistorted audio. Modulates transmitters having RF inputs up to 100W. Unique over-modulation indicator. Cover E-5 \$4.50.



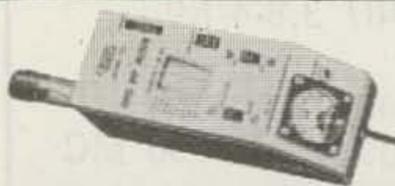RF SIGNAL GENERATOR #324 (150kc-435mc)
Kit \$26.95 Wired \$39.95
TV-FM SWEEP GENERATOR & MARKER #368
Kit \$69.95 Wired \$119.95



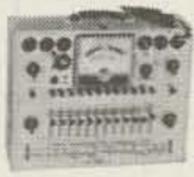GRID DIP METER #710
Kit \$29.95 Wired \$49.95
Includes complete set of coils for full band coverage. Continuous coverage 400 kc to 250 mc. 500 ua meter.



DYNAMIC CONDUCTANCE TUBE & TRANSISTOR TESTER #666
Kit \$69.95 Wired \$109.95
TUBE TESTER #625
Kit \$34.95 Wired \$49.95

EICO®

33-00 Northern Blvd.,
Long Island City 1, N. Y.

EICO, 33-00 N. Blvd., L.I.C. 1, N.Y. Show me how to save 50% on 72 models of top-quality: Ham Gear Test Instruments Hi-Fi Send free Short Course for Novice License. Send free catalog and name of neighborhood EICO distributor. Send 36-page Stereo - Hi-Fi Guidebook: 25¢ enclosed for postage & handling

Name.....
Address.....
City..... Zone..... State.....

73-11

Add 5% in the West.

Table of Contents

Transistorized 220 mc Converter Crystal controlled too.	J. Specialny W3HIX	8
R-F Sniffer Snooper sensitive RF detector which you will build.	Jim W. Kyle, Jr. K5JKX/6	11
SSB Dynamic Demonstrator Teaching SSB calls for some tricky stratagems.	Ed Summerfield W2UQB	12
Capacity Meter Two ranges: 0-40 mmfd (resolves 1 mmfd) and 0-900 mmfd.	Tom Lamb K8ERV	14
Station Control System Even if you don't build this one it will give you ideas.	David Cabaniss W1TUW	16
The Multivibrator in VOX Circuitry Technical article ending up with a corker of a VOX circuit.	Roy E. Paffenberg	18
The Fine Art of Transistorizing Changing your tube circuits to transistors.	Jim Kyle K5JKX/6	22
Simplify Your Log Keeping Just an idea which you probably won't like anyway.	Staff	25
Perfect Squelch Our big technical article for the month . . . all about squelching.	Staff	26
Low Noise Two Meter Converter The newest, the latest, the hottest 417A converter yet.	Lester Earnshaw ZL1AAX	32
Surplus Frequency Standard Simple conversion of the VO-4 oscillator. You'll like it.	R. Paffenberg	40
Simple Phone Patch This one is pretty simple and effective. Next month a simpler one.	Herb Brier W9EGQ	42
New Tube Base Coil Forms OC3W, 5R4WGA, etc., bases make splendid coil forms.	R. Paffenberg	44
Propagation Forecast What bands what time to where . . . probably.	Dave Brown K2IGY	50

Misc.:		Staff:
Editorial	4	editor-publisher Wayne Green W2NSD
Shopping List Cover Story	6	publications manager David Fish
New Products	25, 51	associate editor Jim Kyle K5JKX
Book Reviews	25, 44, 57	associate editor Don Smith W3UZN
Echo Echo	46	associate editor Jim Morrisett WA6EXU
Letters	49	contributing editor John Campbell W2ZGU
Vagabond Ham	52	subscriptions Virginia K2MNV
Most Important Item This Month	54	
Other Ham Publications	58	
Advertiser's Index	62	
Table of Contents	3	

The Cover: Virginia mulls over the shopping list we've assembled on page 6. All items are under \$20 and are needed in every ham shack. Photograph by Mort Weldon.

... de W2NSD

PLEASE forgive me for being still somewhat mesmerized with the sudden existence of 73 and with the myriad of problems that have attended the birth. Maybe in a month or so I will come out of my cocoon and have something significant to say. Maybe, but probably not.

Either a lot of people skipped over the list of the "policies" of 73 which were printed in the first two issues, or else they have to have things spelled out in words of fewer syllables. For instance I'm asked frequently when we're going to have a VHF column. Putting on an obviously condescending look and speaking with biting sarcasm I refer them to Policy #5 and explain that in the second issue we had, for the VHF men, the "Four Band Crystal Converter," the "FM VFO Exciter," an article on noise clipping, "Hard Facts about Echo," "Improving the Performance of the Communicator III," the "VHF Tri-Mode Receiver" and "Finding True North." If we had had a VHF column we would also have had to have a DX column, a Sideband column, a YL column, a Novice column, a Technician column, a transistor column, ad nauseum, and we wouldn't have had room for anything else, much less seven feature articles of interest to VHF'ers.

Further, if we use space for operating news of interest to only a small group we are robbing everyone else. Consider too that it takes about two months at least for such news to get into a monthly magazine like this and by this time everything is just a matter of record. If we don't run a VHF column we then encourage those fellows who are interested in reading operating news to subscribe to the VHF Amateur for \$3 a year and get the VHF news in extreme detail and get it considerably faster than they ever could through us. We'll still be specializing in the construction articles and things like that.

This same thing goes for the DX enthusiast. Why run a DX column in a monthly magazine when the news you get is much too old to help anyone. If you subscribe to the DX Bulletin

at \$5 a year you get a weekly detailed bulletin which lists just about every DX station on the air and tells you where and when to look for 'em and where to send the QSL. You can read about DXpeditions in time to work 'em instead of finding out about which ones you missed two months later.

Likewise the classified ads. As long as Ham Swap is around doing a better service cheaper and faster than we could do we are doing them harm and our readers a dis-service to compete with them. At \$1 a year you can afford to have it come and not even read it just on the chance that you will eventually want something. Then, when you do, you can pull out the paper and find it quickly. It comes out every two weeks which is a real good deal both for the seller and buyer. I've sent for things in classified columns only to find that they were sold over a month ago, before the ad ever appeared.

Conventions

Probably the biggest event locally in the hamisphere was the Hudson Amateur Radio Council Convention which was held at the Statler-Hilton Hotel. Multitudes of hams poured over some 34 exhibits by manufacturers and distributors. Two unusual events marked this Convention: the opening tape was cut by moonbounce signal (a photo of the apparatus involved appeared on page 6 of our November issue... unfortunately we left off that all important credit line to Leonard Victor W2DHN, who snapped the Picture... sorry LV, but you attached a subscription to your accompanying letter and our efficient subscription department confiscated it) and Jean Shepherd K2ORS was the Master of Ceremonies.


Too bad if you missed it this year. Jean was hilarious.

Another high spot was the illustrated talk on the western end of the Great Moonbounce Record by Bill Orr W6SAI. You also missed the mighty persuasive sales pitch I made to every one who ventured near the 73 booth.

More Worth

The survey results published last month were so interesting that it seemed only fair to run the survey again this month. I must admit that I was somewhat shaken to find myself trying to compare poor little 73 with two 184 page contemporaries, one selling for 50c and one for \$1.00! But, Never Say Die and let the chips fall where they may, etc. Here are the results of the fearless survey of actual pages devoted to technical or construction articles in November 1960.

73 Magazine	38 pages
Brand X	33 pages
Brand Y	35 pages

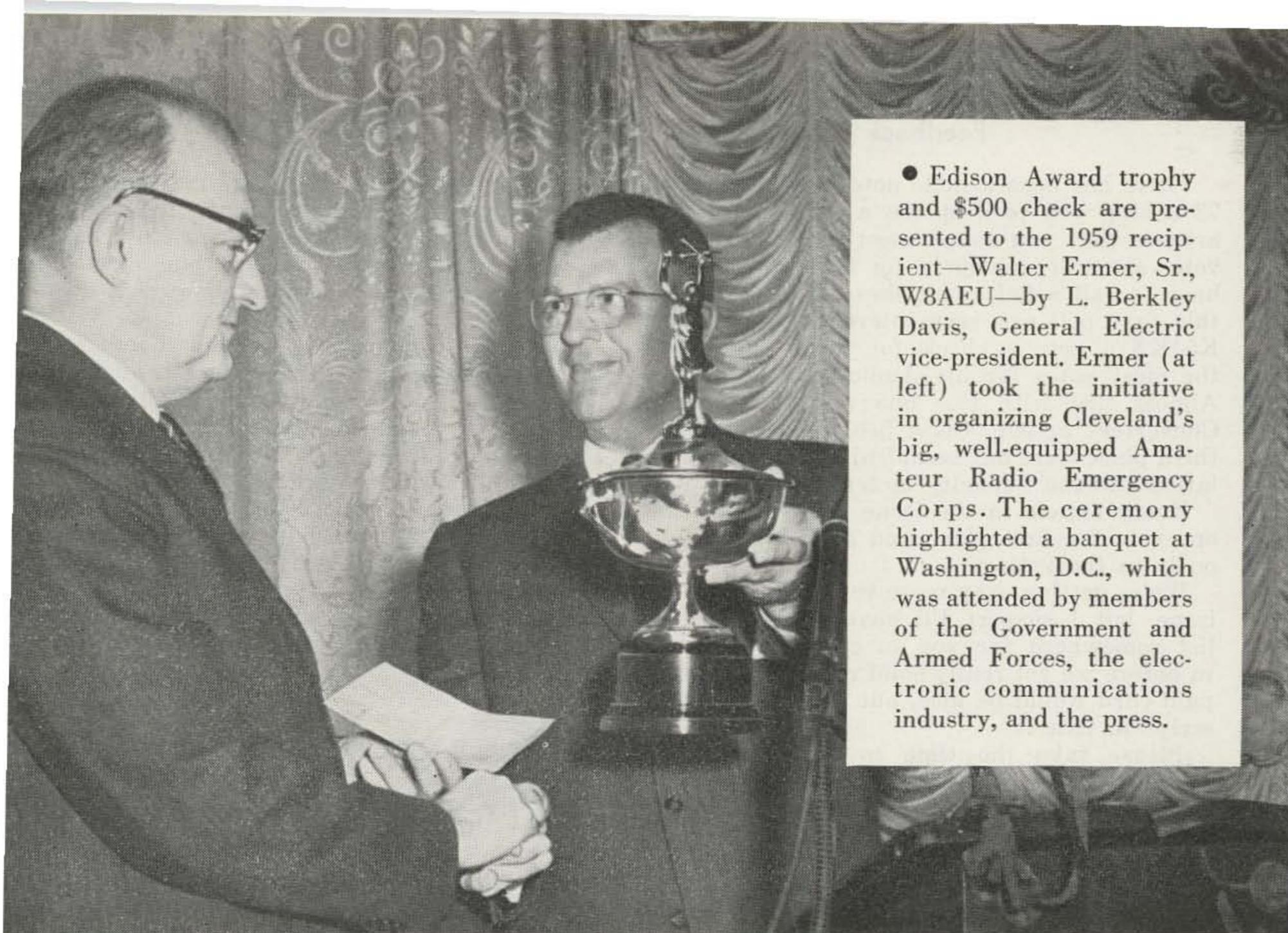

● Edison Award trophy and \$500 check are presented to the 1959 recipient—Walter Ermer, Sr., W8AEU—by L. Berkley Davis, General Electric vice-president. Ermer (at left) took the initiative in organizing Cleveland's big, well-equipped Amateur Radio Emergency Corps. The ceremony highlighted a banquet at Washington, D.C., which was attended by members of the Government and Armed Forces, the electronic communications industry, and the press.

JAN. 2 DEADLINE FOR EDISON AWARD NOMINATIONS

Nominating letters for the 1960 Edison Radio Amateur Award must be postmarked not later than January 2, 1961.

Please remember that the judges will consider only candidates whose names are submitted in writing by you and others. There is no other source for Edison Award nominations.

Therefore, between now and January 2, canvass in your mind the activities of amateurs you know, in order to make sure no deserving OM or YL fails to be represented. If you uncover such a candidate, by all means send in his name promptly.

For help with your nominating letter, and for rules of the Award, see the October issues of QST and CQ, or write to *Edison Award Committee, General Electric Co., Electronic Division, Cleveland, Ohio*.

HERE ARE TYPICAL ACTIVITIES THAT CAN QUALIFY FOR THE AWARD:

- Emergency communications work in a disaster, such as a flood, hurricane, tornado, or explosion.
- Helping amateurs and others with their specialized problems, through professional knowledge and experience.
- Community service in organizing mobile and fixed communications to promote the success of fund drives and other public events.
- Helping disabled or physically handicapped persons.
- Relaying messages from remote points for the benefit of isolated servicemen and civilians.
- Designing and constructing radio equipment for use by persons in remote parts of the world, who do not have access to regular commercial communication channels.
- Civil-defense organization work; weather reporting; radio assistance to state or local traffic and police authorities; cooperation in forest-fire prevention and control.
- Teaching basic electronics to young people.

GENERAL  ELECTRIC

Feedback

There has been a little note in each issue of 73 asking you to drop me a card listing the articles that you found most interesting. The votes are still coming in for issue #1, but we have to call a halt somewhere. The results of this first poll are very interesting. Jim Kyle K5JKX/6 gets a check for 50% extra with the most votes for his Audio Booster article. Almost tied with this one was the Bantam Converters article. Close behind and tied for third place were our technical article on Modulation and the Capacity Meter.

Every article in the issue received at least one vote for first place and none lagged seriously in the voting.

We're getting even more votes on the second issue, but I suspect I'll have to run a short list somewhere for you to cut out and mail in before we get really solid results. A postage paid card would be nice, but not at these subscription rates.

Please take the time to congratulate an author that has pleased you by dropping me a card with a vote for his article. I would prefer that you list the five most interesting articles in the order of your interest, but I'm not picky.

Advertisers

Several of the larger advertisers are still obviously missing from our pages. When you have occasion to write them on other business you might mention this oversight to them. Apparently some of you have already been plucking their coatsleeves for one of the largest mentioned that they had received a couple such letters. Unfortunately they pointed out that the company had no intention of advertising in 73 in the foreseeable future. We need all the advertisers we can get . . . but this is up to *you*. I would like to print a lot more pages of articles each month, but I can't run more than two pages of articles for every page of advertising without economic disaster overtaking me. If you'd just written to a few more of the November advertisers we'd have been able to run 80 pages in this issue!


Shopping List

If your family is anything like mine they start hounding you along about this time for a list of things you'd like for Christmas. It is wise to prepare one, for Christmas can turn into a day of horror if you find yourself opening box after box of sox and neckties.

With one eye on the pocketbook (limit \$20) and the other scanning magazine ads and catalog promises, a list of goodies has been prepared which should be welcomed by any ham. I've tried to list things which we all would like to have and which don't call for any knowledge of the part of the buyer as to what bands you operate or what equipment you may be using. A couple of these ideas are ostensibly for the junior op, but I suspect that he may have trouble getting you away from 'em long enough to break 'em.



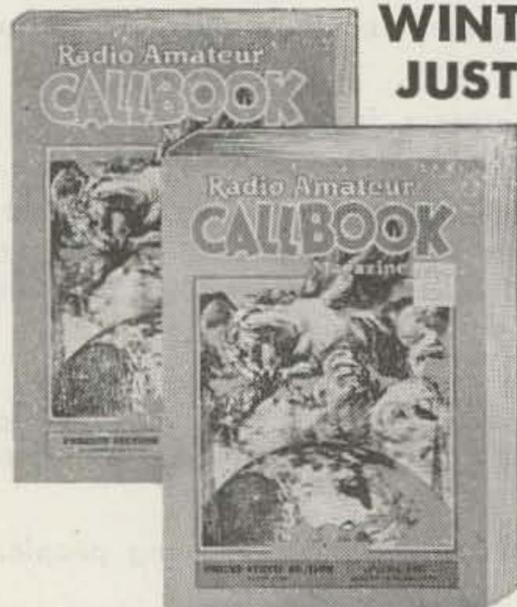A. The Key-municator, manufactured by Dow Key, costs \$9.95 and is available from almost any good parts distributor. This consists of a hand key with a transistorized audio oscillator built right into the base. A head-phone comes with it for copying. The key is mounted on a board which has the Morse code on it. This is one of the best deals I've seen yet to get the jr. op interested in CW. When you can get it away from him you can feed the tone into your vhf rig for ICW sending. Any number of these gadgets can be hooked



**WINTER ISSUE
JUST OUT**

ORDER YOUR CALLBOOKS NOW!

United States Section listing all K & W calls (over 225,000).
10,840 newly licensed radio amateurs added since the previous issue.

Single copy \$5.00 postpaid (add 25¢ per copy outside U.S.A.)


Foreign Section listing radio amateurs throughout the world (outside the 50 United States)—Fall-Winter 1960 issue.

Single copy \$3.00 postpaid (add 25¢ per copy outside U.S.A.)

On sale at your favorite radio parts distributor, or direct from the publisher.

RADIO AMATEUR CALLBOOK, Inc.
4844 Fullerton Avenue, Chicago 39, Illinois, Dept. ST-2

YOU ARE THERE!

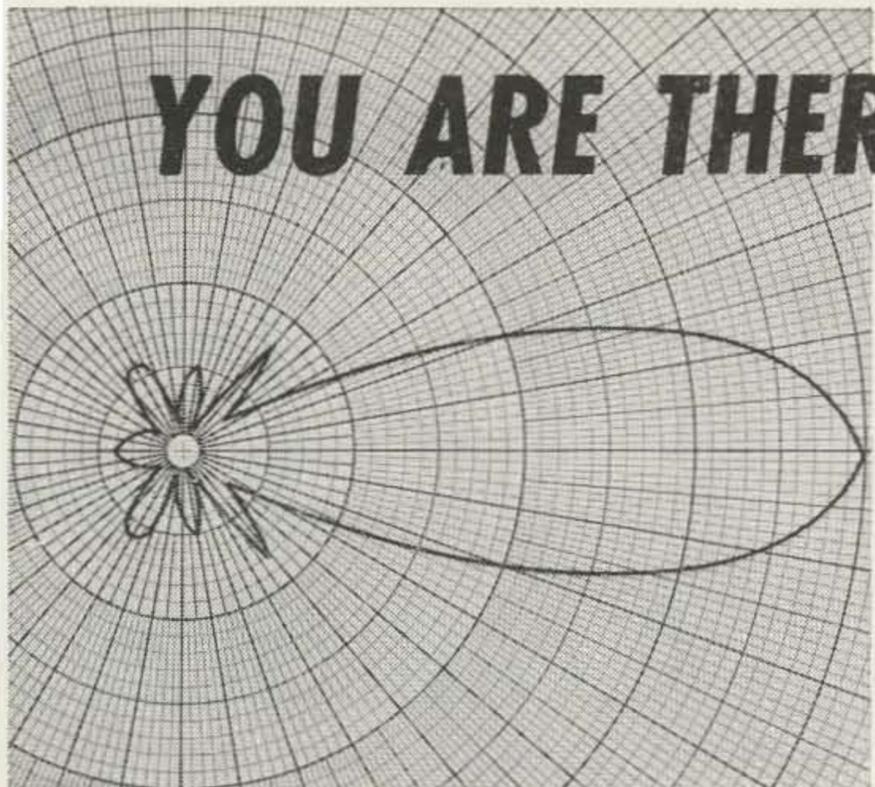

**For TOP-MAN-ON-
THE-FREQUENCY results...**

Install a Telrex antenna...dollar for dollar better in every way! Antenna systems from \$6.95 to \$12,000.00

with **telrex**
—“the-performance-line”—
with a “MATERIAL” difference!

Send for (or, at your distributor), PL 77 Technical Specifications and Performance Bulletin describing 106 Antennas from $\frac{3}{4}$ through 80 meters including “BALUN”—FED ROTATABLE DIPOLES, MONO, DUO, TRI, 4-BAND AND “SPIRALRAY” ANTENNAS, ROTATOR/INDICATOR SYSTEMS, TOWERS, BROAD-BAND “BALUNS,” ACCESSORIES AND “NICE-TO-HAVE-AROUND-YOUR-SHACK” INFO.

ANTENNAS

SINCE
1921

Communication and TV Antennas

telrex LABORATORIES

ASBURY PARK 40, NEW JERSEY, U.S.A.

together for code classes or sending from one house to another.

B. Another doohinky that the kids will get a big kick out of is this ten circuit transistor kit. This can be assembled in a few minutes and then, by means of changing the plug-in wires in the printed circuit board, you can make the circuit into a two stage AM radio, a light operated relay, a wireless broadcaster, a code practice oscillator, an electronic switch, a two stage audio amplifier, a body-capacity burglar alarm, a voice operated relay, or an electronic flasher. A card fits into the center of the board showing where to make the connections for each circuit. Costs \$15.75 from Allied Radio. Better order quickly and give the U.S. Mails time to deliver before Cringle is due.

C. This 15" wall clock by Scientific Industries costs \$19.80 (just under our \$20 wire) and has a 24 hour illuminated dial. This is fabulous for any shack. I seriously doubt if there is a ham alive who wouldn't be delighted to have one of these given to him. This is the kind of gadget that you seldom buy for yourself, but really appreciate getting from someone else.

D. Nut Drivers by Xcelite. The set of seven fit all common radio nuts from $\frac{1}{4}$ " to $\frac{1}{2}$ " and have long hollow handles so the nuts can be screwed on even when there are bolts sticking out. No ham shack is complete without a set of these. They're available at most parts distributors for \$7.47.

E. “ON THE AIR” sign which lights up when the rig is turned on. This unit is just like the ones used by commercial radio stations, only it costs but a fraction of the price: \$6.95 from Stellar Electronics. Besides being flashy (pun intended), this sign also puts visit-

ing loudmouths on notice to button up. Comes in grey or black case.

F. The Radio Handbook, latest edition, by Editors and Engineers. This is the best ham handbook ever printed and no hamshack should be without it. Cost is only \$7.50 from Radio Bookshop or your local parts distributor. This edition was written by Bill Orr W6SAI, so you know it's got to be good. There are dozens of interesting construction projects in it plus just about everything else you could ask for in a ham handbook.

G. Felt call letters that can be ironed on your jacket. Great for field day, picnics, ham-fests, club meetings, or just plain bragging. Washable, I understand. They cost 20c per letter or number from K9TVA Enterprises in the 3" size and 10c each for the 1" size.


H. 100 kc Crystal Callibrator kit by Heath. This \$14.95 kit comes complete with battery and transistor. It provides marker frequencies every 100 kc from 100 kc to 54 mc. Every ham shack must have some sort of frequency standard and this one certainly is the least expensive you're going to find for a while. This is model HD-20 and is available from Heath or from any Heath distributor.

I. Not available.

Manufacturers Please Note

When an amateur gets the bug to buy something the next step normally is for him to drag out the back issues of his ham magazines and look through them to try to find some information. Wouldn't it be clever if all manufacturers ran at least one ad on each of their current products during each three or four

(Continued on page 53)

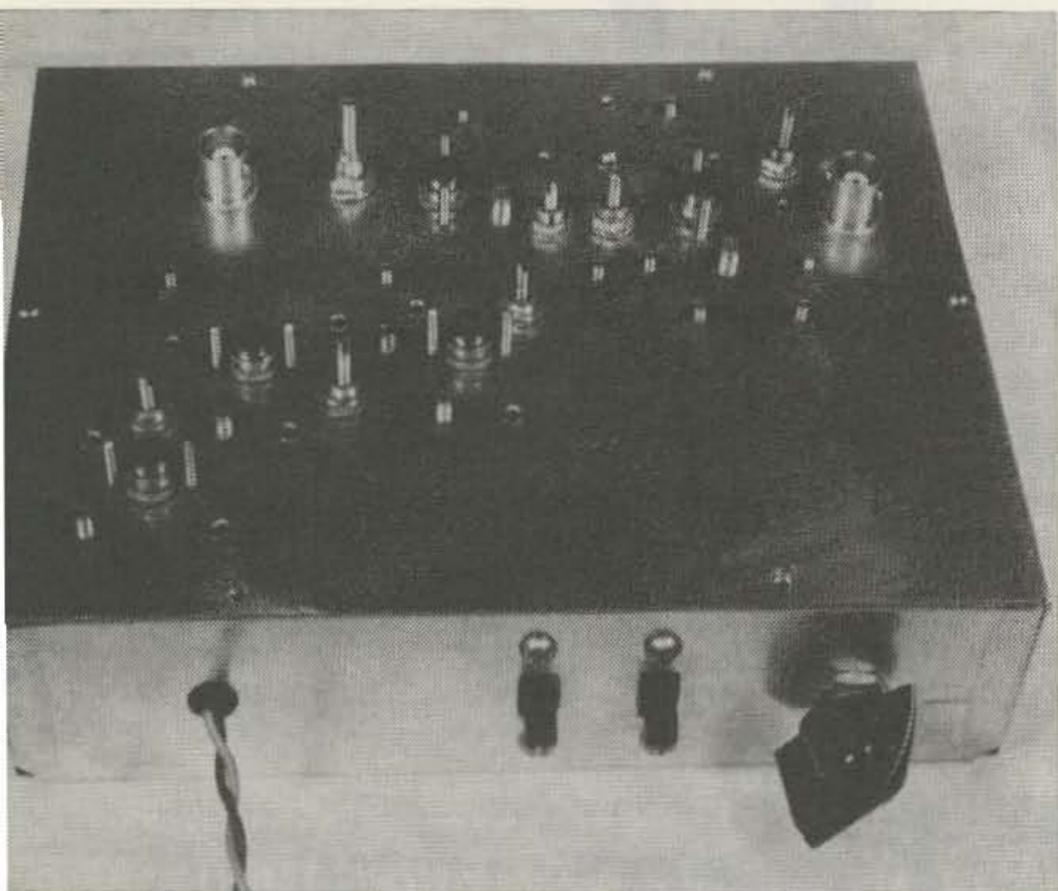

A Transistorized Crystal Controlled Converter

... for the 220 mc (1- $\frac{1}{4}$ meter) Amateur Band

J. Specialny W3HIX
Philco Corporation/Lansdale Division

This report describes a 1 $\frac{1}{4}$ meter converter for the 220-225 mc amateur band. It employs five Philco MADT VHF transistors and operates at a supply voltage of 12 volts. A communications receiver capable of tuning the 10 to 15 mc frequency range can be used as the *if* system.

THE unit employs five transistors, all operating in common emitter configuration. Transistor TR1, operating as a neutralized rf amplifier, is coupled to the mixer through a double tuned circuit. This method of interstage coupling is preferred because of its ability to reject signals outside the rf bandpass and to minimize feed through at the *if* frequency. The antenna is coupled to the amplifier through a tap on the input coil L1. Shunt capacitor C1 tunes the input circuit to the proper frequency. A series matching capacitor C2 applies the incoming signal to the low impedance base which typically is about 60 ohms. Neutralization is provided for by a capacitor network consisting of C3 and C6. Neutralization provides an increase in rf power gain of approximately 3 db as well as good circuit stability, although the amplifier would be quite stable if neutralization was not used.

The rf amplifier output circuit is tuned by inductor L2 and capacitors C4 and C5. A manual rf gain control is incorporated to reduce the gain on strong signals. The method used here is termed "forward gain control" and is noted for its excellent overload characteristics. The term "forward" is derived from the fact that the collector current is increased to reduce the stage gain rather than decreasing the collector

current as is done in the reverse method. A resistor R5 is inserted in series with output circuit and the negative terminal of the power supply. As the current increases by adjustment of gain control potentiometer R3 the voltage available between the collector and emitter of the rf stage decreases causing the gain to drop. This drop in power gain is nearly linear as the collector to emitter voltage is varied from eight volts to one half a volt. The MADT is the only VHF transistor suited for this type of gain control. Resistor R4 provides emitter stabilization and resistors R1, R2 and R3 determine the biasing level. The value of collector current varies from 2.5 to 6 ma depending on the setting of R3. The normal operating value is 2.5 ma for maximum gain. A stand by receiver switch is incorporated in the emitter lead.

Mixer

The output of the rf amp is coupled to the mixer transistor TR2 (Philco T1833) by loosely coupling mixer coil L3 to amplifier coil L2 (see coil data for details). Capacitor C7 tunes coil L3 and the value of capacitor C8 is selected to match the input resistance of the mixer. The local oscillator power is injected

into the emitter terminals by returning the bypass capacitor C13 to ground through a tap on coil L8. An *if* frequency of 10-15 mc was selected. Coil L4 and capacitor C9 tune the collector output to this frequency range and the output is coupled to the load through coil L5 which is wound over the cold end of coil L4. The 3 db *if* response of the converter is about 3 mc. Since most of the activity is centered around 221 mc, the *if* response was peaked to 11 mc. The rf response at the mixer

base is quite flat from 219.5 to 225.5 mc.

Emitter resistor R8 provides dc stabilization and resistors R6 and R7 determine the operating point.

Harmonic Generator


This section provides at least 180 millivolts rms of injection voltage to the emitter terminal of the mixer TR2 (Philco T1833). The local oscillator frequency is on the low side


PARTS LIST

C1=0.05 to 5.0 mmfd Piston Capacitor	C16=470 mmfd Ceramic
C2=1.5-7.0 mmfd Ceramic Trimmer. (A fixed capacitor of about 2.5 mmfd can be substituted.)	C17=68 mmfd Ceramic
C3=2.2 mmfd Ceramic	C18=68 mmfd Ceramic
C4=4.7 mmfd Ceramic	C19=0.0015 mfd Ceramic stand off type.
C5=0.5-8.0 mmfd Piston Capacitor	C20=2.0 mmfd Mica
C6=50 mmfd	C21=5.0 mmfd Ceramic
C7=0.5-8.0 mmfd Piston Capacitor	R1=8200 ohms 1/2w
C8=100 mmfd	R2=2700 ohms 1/2w
C9=3 mmfd	R3=10,000 ohms Potentiometer
C10=1.0-18 mmfd Piston Capacitor	R4=470 ohms 1/2w
C11=1.0-18 mmfd Piston Capacitor	R5=820 ohms 1/2w
C12=0.5-5.0 mmfd Piston Capacitor	R6=15 K 1/2w
C13=0.01 mfd Ceramic 75V	R7=4.7 K 1/2w
C14=0.0015 mfd Ceramic stand off type.	R8=1.5 K 1/2w
C15=0.01 mfd Ceramic 75V	R9=8.2 K 1/2w
	R10=3.3 K 1/2w
	R11=1.5 K 1/2w
	R12=39 K 1/2w
	R13=4.7 K 1/2w
	R14=470 ohms 1/2w
	R15=39 K 1/2w
	R16=4.7 K 1/2w
	R17=470 ohms 1/2w

COIL DATA

- L1—6 turns #20 tinned copper wire $\frac{3}{16}$ " l.d. $\frac{1}{2}$ " winding antenna tap 1 turn from ground end.
- L2— $3\frac{1}{2}$ turns #26 tinned copper $\frac{5}{32}$ " l.d. $\frac{1}{4}$ " winding length.
- L3— $4\frac{1}{2}$ turns #24 tinned copper $\frac{5}{32}$ " l.d. $\frac{1}{4}$ " winding length.
L2 and L3 form a double tuned circuit. Air wound in the same direction; spacing between coils as noted above.
- L4—72T #34 Nyclad copper wire close wound. W.L. about $\frac{5}{8}$ " on $\frac{3}{8}$ " ceramic form (Cambion type PLS-5 2C4L) powdered iron slug.
- L5—15 turns #34 Nyclad copper wire close wound over ground end of L4.
- L6—9 turns of #3003 Miniductor (B & W) or air dux #416T.
- L7—3 turns of #3003 Miniductor (B & W) or air dux #416T.
- L8—5 turns #18 tinned copper wire $\frac{1}{4}$ " l.d. W.L. = $\frac{1}{2}$ " tapped about $\frac{1}{4}$ turn from end.

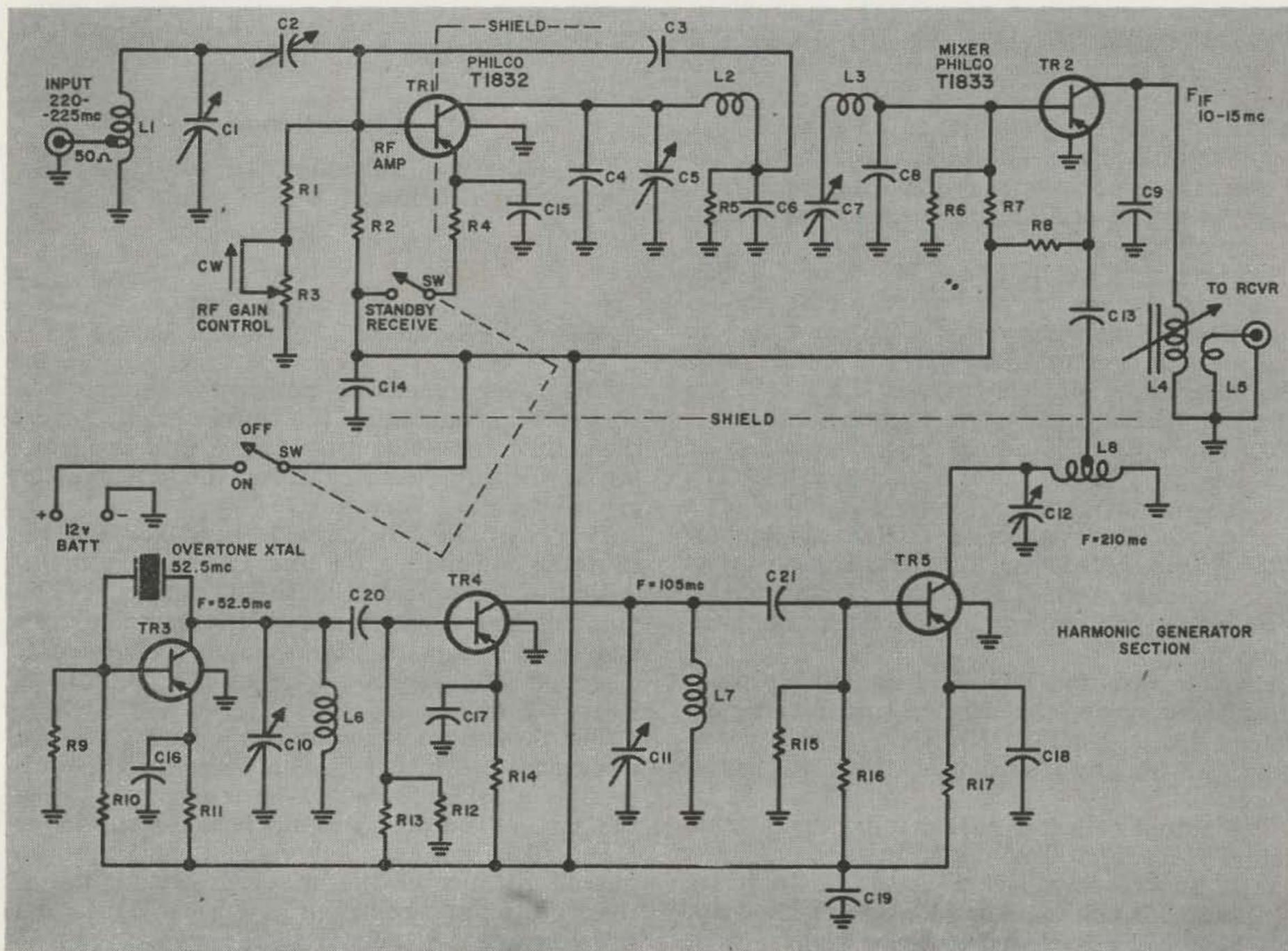

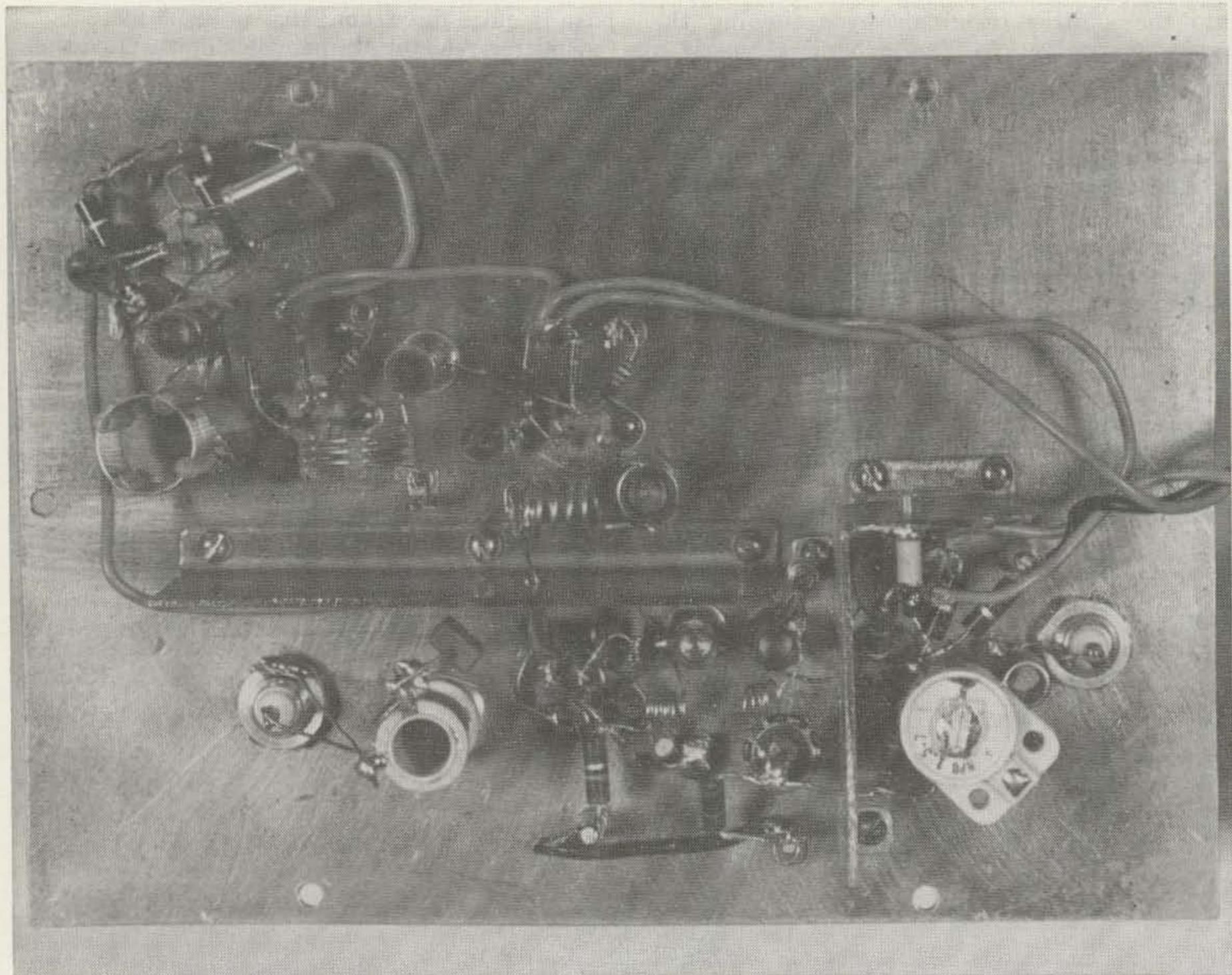

and the output frequency is 210 mc. This high frequency output is obtained through the use of two stages of frequency doubling and a one stage overtone oscillator operating on a frequency of 52.5 mc.

Transistor TR3 (Philco T1859 or T1695) is used in the crystal controlled oscillator circuit. Coil L6 and capacitor C10 are tuned to 52.5 mc, the overtone frequency of the crystal. The oscillator output drives TR4 (Philco T1859 or T1695) through coupling capacitor C20. The output is tuned to a frequency of 105 mc by coil L7 and capacitor C11. The 105 mc output from frequency doubler TR4 is used to drive another frequency doubler TR5 (Philco T1859 or T1695) through coupling capacitor C21. The output frequency of TR5 is tuned to 210 mc by coil L8 and capacitor C12.

Emitter resistors R11, R14 and R17 provide the necessary dc stabilization and biasing resistors R9, R10, R12, R13, R15 and R16 determine the biasing current of their respective stages.

The actual collector current flowing in transistors TR4 and TR5 is influenced to some extent by the level of rf excitation from the oscillator TR3 since a combination of fixed and self biasing is employed in these stages.

Operation

The individual collector and total currents are tabulated below:

TR1	TR2	TR3	TR4	TR5	Total IC with divider current
2.5 ma	1.8 ma	2.0 ma	2.0 ma	2.0 ma	14 ma

The sweep generator method of alignment is suggested in tuning up the converter. However, the unit can be tuned up fairly well by peaking it up on a carrier from the transmitter or an rf signal generator.

If a variable capacitor is used for C2, alternately adjusting C1 and C2 for maximum output should peak the input properly. The point of best noise figure should coincide very nearly to the point of maximum power gain. The noise figure should be in the vicinity of 5.5 to 6.5 db.

The overall power gain is about 22.0 db. An additional 1.5 to 2.0 db can be realized by inserting a series tuned 11-12 mc trap between the mixer base and ground because the input circuit does not completely short the 12 mc input admittance of the mixer. It was felt that the additional tuning procedure involved did not warrant the addition of the trap. 73

The RF Sniffer



Jim Kyle, K5JKX/6
1851 Stanford Ave.
Santa Susana, Calif.

EVERY now and then there's a need to know if any rf is present in a circuit. Frequency isn't so important—the question is simply, "Is there rf here?"

Your grid-dipper can frequently answer this, if used in the wavemeter mode, but occasionally it's not sensitive enough—particularly if you're working with a receiver oscillator where power is measured in microwatts.

Here's an rf Sniffer which will indicate the slightest trace of rf in a circuit. In addition to checking receiver oscillators, it's a perfect gadget to ensure perfect neutralization of a transmitter final.

Designed by W5JCB along classic lines, the Sniffer is built around a microammeter. While most 0-50 ma meters still bear price tags in the \$15 region, an import stocked by Arrow Sales Inc., North Hollywood, Calif., and listed as their catalog number 606PM1, sells for only \$5.95.

Using this meter, the total cost of the Sniffer should be less than \$6.75 complete—the only other parts are a 1N34A diode and a .001 mfd capacitor.

Connect the components as shown in the schematic and photograph. Use long-nosed pliers as a heat sink between the diode and the solder joint when wiring, to prevent diode damage. Note that the pickup loop of 14 gauge wire is insulated with a strip of spaghetti.

That's all there is to construction of the Sniffer. Here are some of its uses:

Amplifier Neutralization—Couple the Sniffer to the antenna terminal with a temporary two-turn link around the pickup loop. Remove plate and screen voltage from the final amplifier. Apply drive. Adjust neutralization for minimum indication on the Sniffer—but don't expect to be able to get it down to zero.

Oscillator Checking—Place the pickup loop near the oscillator coil. If the oscillator's working, the Sniffer will indicate rf. Touching either the grid or plate lead (use an *insulated* tool for this test, not your fingers) should reduce the Sniffer's indication.

Receiver Troubleshooting—Check the oscillator as described above. If it's okay, next check the mixer plate coil by placing the Sniffer pickup loop near it. If you get an indication here, move to the first if stage and place the pickup loop near the plate pin of the tube socket. Proceed through the receiver until you lose the indication. The trouble is somewhere between the last indication and the point at which it disappeared.


Field Strength Meter—Couple a short antenna to the pickup loop by two turns of wire around the loop. Field strength will be indicated in a comparative manner by the meter. It cannot be calibrated, but proves useful in tuning mobile or beam antennas, etc.

SWR Measurement—(Parallel lines only). Move the Sniffer long the line. Mark maximum reading and minimum reading over a half-wavelength. Divide minimum into maximum. The quotient is, roughly, your VSWR. This method is by no means exact, but will indicate whether the line is under or over a 2:1 SWR.

UHF Frequency Measurement—Set up Lecher wires. Couple the rf Sniffer lightly to the tank circuit instead of using a flashlight bulb. Use Lecher wires in normal fashion, reading Sniffer indications for maximum and minimum. This is much more exact than the normal methods.

Improved Grid-Dipper—If you have a signal generator available, it can be used with the rf Sniffer to serve as a "grid-dip" meter to locate resonance for any tank circuit. Couple both the generator and the Sniffer lightly to the unknown tank. Vary generator frequency. A sharp rise in Sniffer indication indicates the resonance point. 73

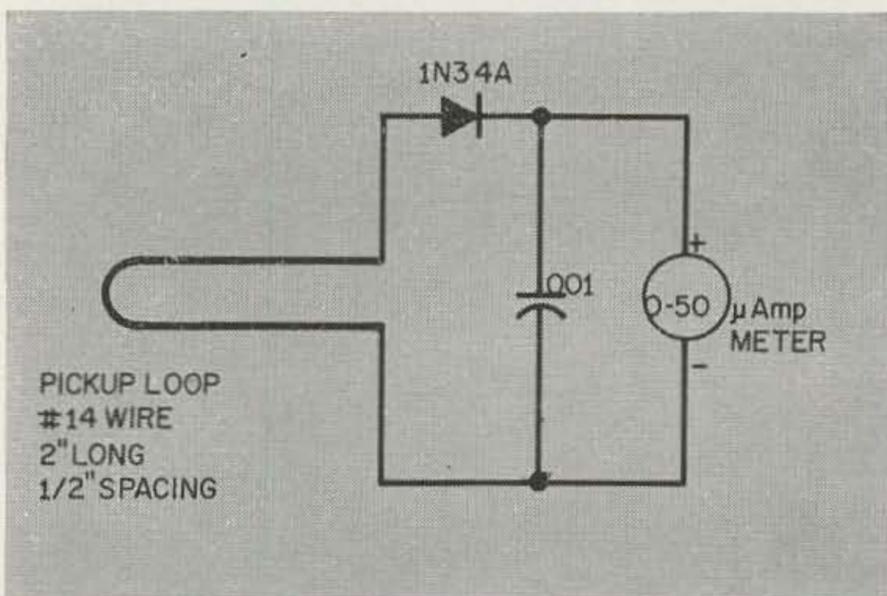Mount capacitor and diode on back of meter with shortest possible leads. Attach pickup loop directly to negative meter terminal; it's stiff enough to do without other mechanical support.



Balanced Modulator Dynamic Demonstrator

E. H. Sommerfield W2UQB
818 Wallace Street
Endicott, New York

HERE comes a time in every "ham's" life when he is called upon to impart to others his knowledge and experience on a given subject. This occurred to the writer recently when he was approached by "Doc"¹ W2JVZ, of the Greene Amateur Radio Society of Greene, New York, and invited to deliver a lecture on Balanced Modulators. Now one just does not get up before a group and point out a balanced modulator configuration and ask the listeners to accept the facts of carrier cancellation and sideband generation, neither does one go into a long series of vacuum tube equations. It's the correct mathematical procedure, but it's also a great cure for insomnia! No! The sensible approach is to analyze, via vectors, CW, AM, DSB and SSB, in that order, and demonstrate these forms of modulation on a dynamic demonstrator. This is the procedure the writer followed. After the talk the audience was invited to "twiddle knobs." As a result, an enjoyable and enlightening evening ensued.



The state-of-the-art of balanced modulators was examined to determine which circuit configuration would lend itself conveniently to the demonstration of all four of the aforementioned modes of modulation. It might be noted that CW is considered, by definition, a mode of modulation. The W2UNJ exciter was selected as a model for the following reasons:


1. Each tube, or generator, could be applied to the tank circuit, or rf summing network, independently, without upsetting the other generators.
2. All terminals, input, output, and modulation were isolated from each other

¹Dr. Centerwall—W2JVZ

(*Note that since the screens of the carrier tubes are operated at ground, very little RF output is obtained; therefore, under AM conditions very low modulation is applied.)

Fig. 1.

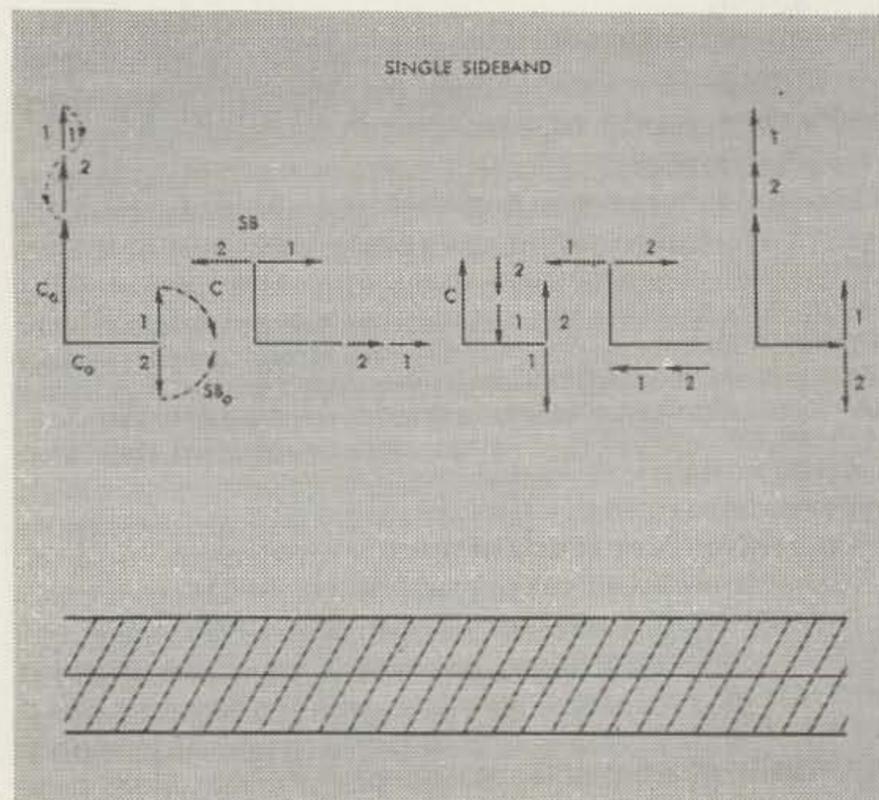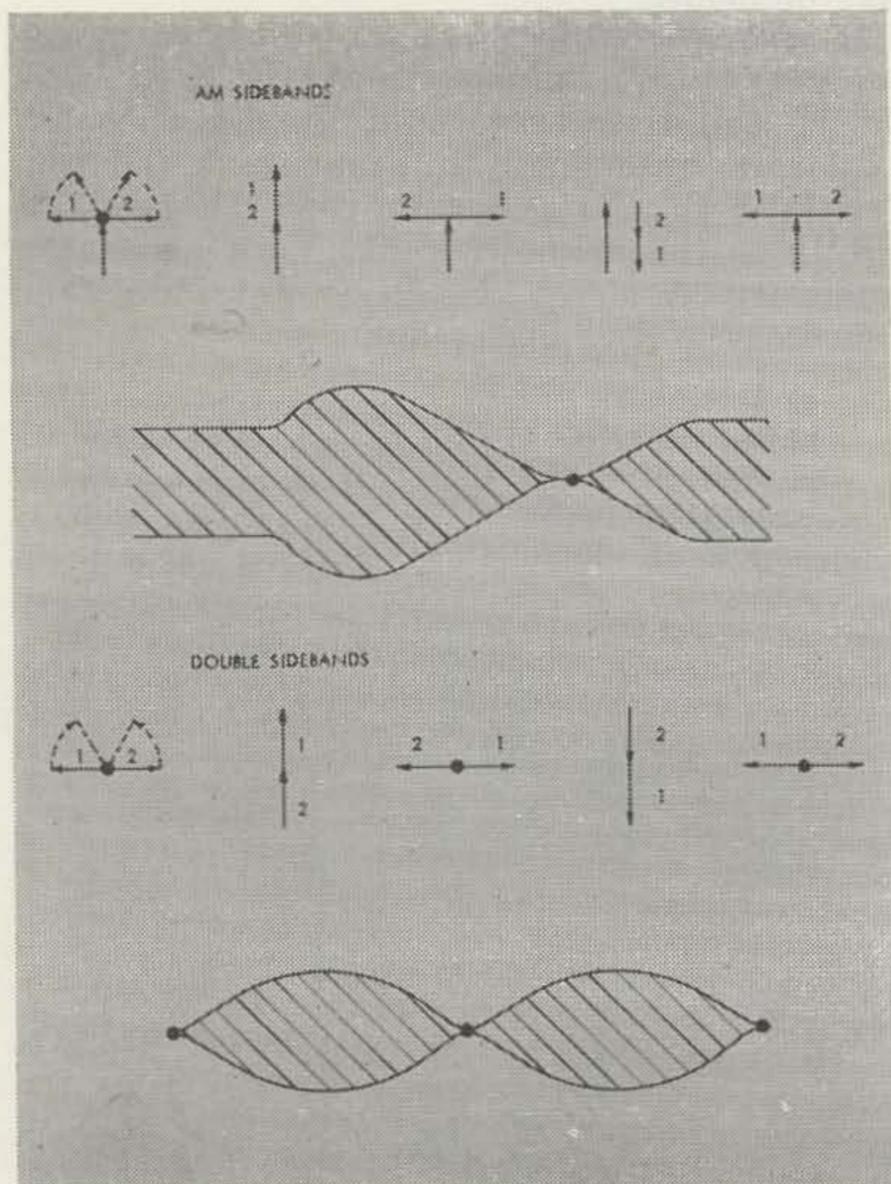

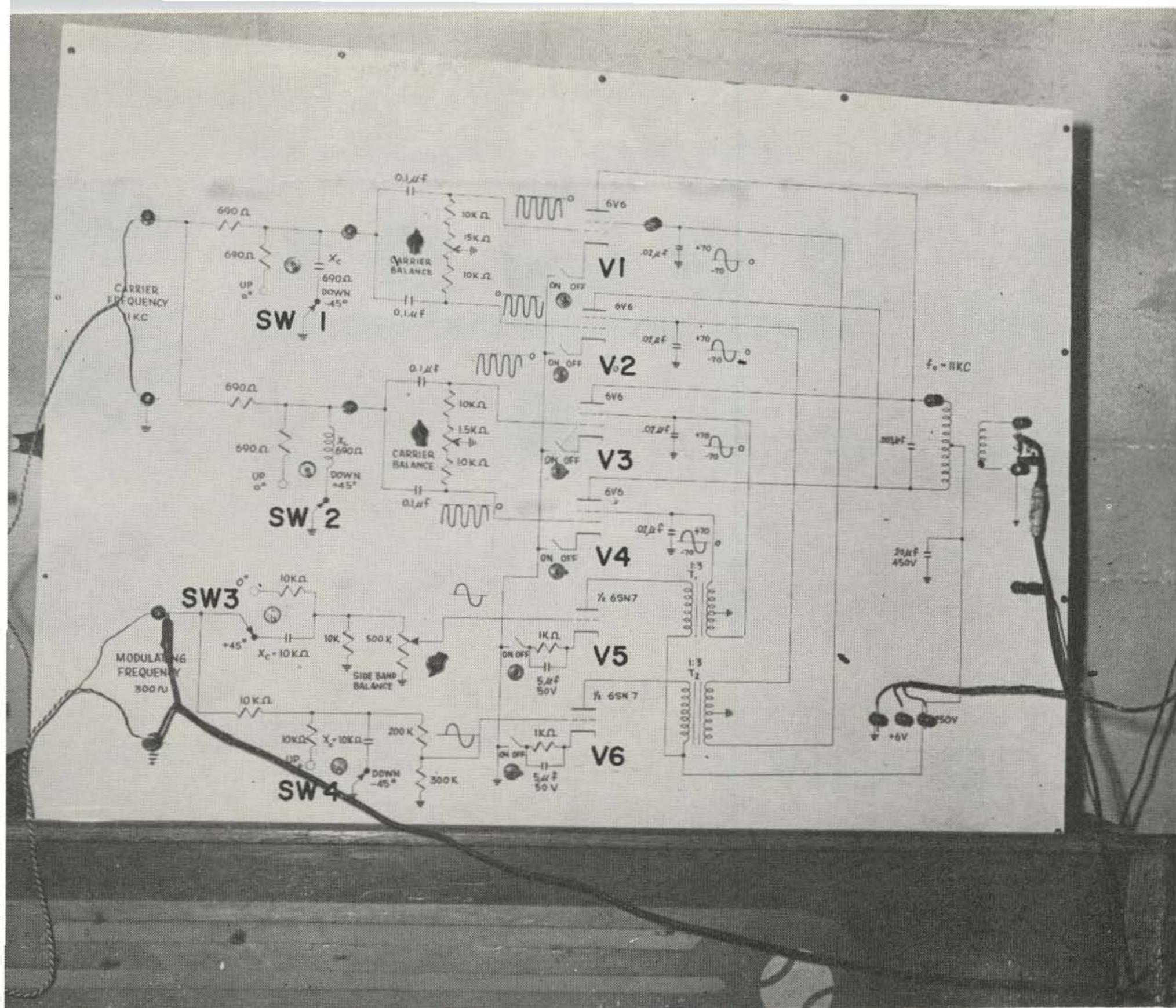

- preventing interaction between the different frequencies used.
3. Because of 1 & 2, audio frequencies could be used for both carrier and modulating signals. This permitted the use of long lead lengths necessary to physically mount controls and switches where the panel artwork directed.

If rf frequencies were used for the carrier, oscillation would have no doubt resulted. A single frequency was used for modulation with special emphasis being made that a phase shifting network, commercially available, would hold the phase difference, for the standard audio frequency range of 30-3000 cycles.

The circuit is shown in the attached photo. With the exception of the modulating phase shift networks, it is identical to the W2UNJ exciter described in many previous ARRL Handbooks. Although the overall circuit theory has been adequately covered in the previously mentioned handbooks, some circuit information was gained by noting the results obtained when the different generators were connected onto the tank circuit.

Abnormal operation can be displayed in SSB

by switching S_1 - S_4 (one at a time) to 0° and noting the increase in output ripple that occurs from the appearance of the unwanted sideband.


Before each mode was presented, Figure 1 displayed on large charts were referred to, to explain the theory.

An effort was made, at the conclusion, to point out the advantages of both DSB and SSB as a modes of modulation insofar as overall communications efficiency is concerned. Also, mention was made of the newer and more efficient balanced modulator configurations.

Although crude perhaps in its pedagogical approach, the effectiveness of this method of lecturing can be attested to by the number of additional invitations received to repeat it. [7] [3]

Table I describes the conditions of the various generators for the different modes of modulation.

Mode	V ₁	V ₂	V ₃	V ₄	V ₅	V ₆	SW ₁	SW ₂	SW ₃	SW ₄
CW	—	—	ON	—	—	—	0°	0°	0°	0°
AM	—	—	ON	—	ON*	—	0°	0°	0°	0°
DSB	—	—	ON	ON	ON	—	0°	0°	0°	0°
SSB	ON	ON	ON	ON	ON	ON	-45°	+45°	+45°	-45°

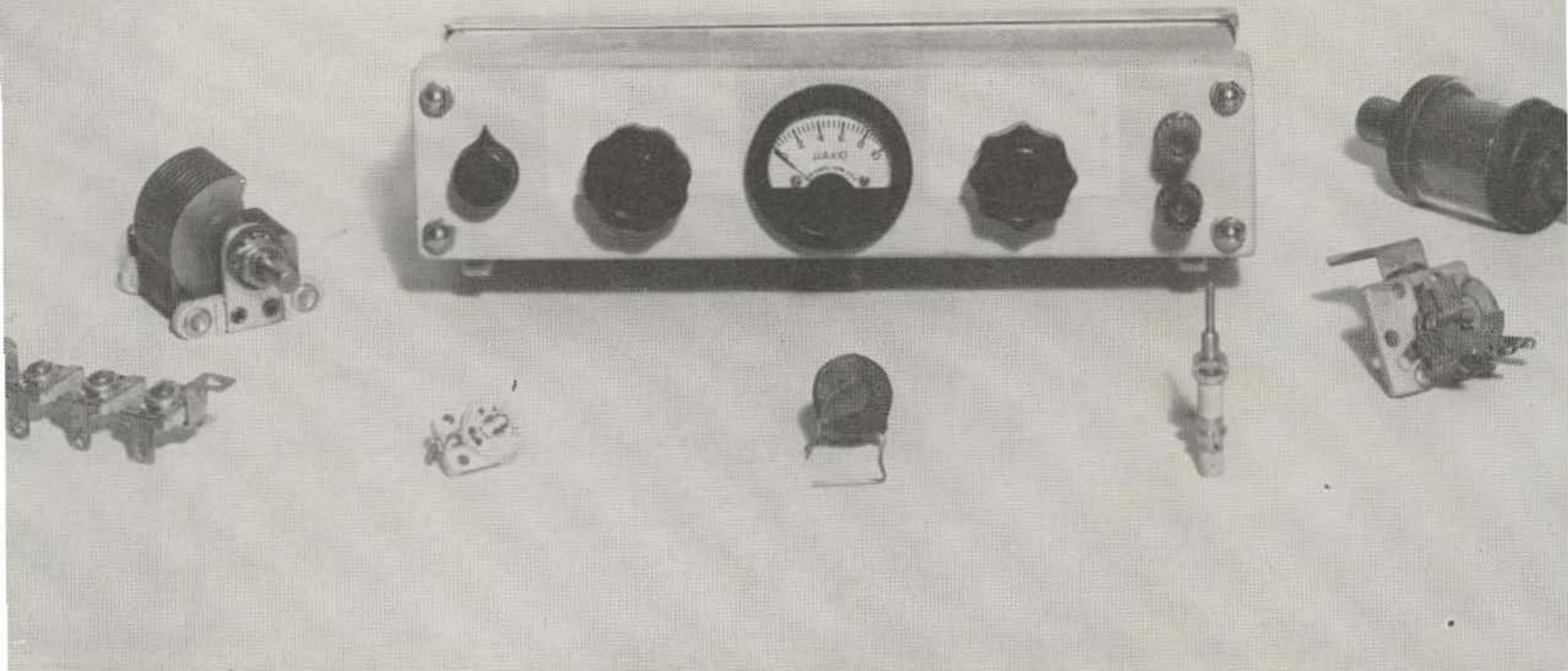

Tom Lamb K8ERV
1066 Larchwood Road
Mansfield, Ohio

Capacity Meter

... Second
only
in
usefulness
to
the
GDO


MEASURING variable or small unmarked capacitors is often a major problem. The Grid Dip Oscillator method is inconvenient and often more work than it is worth. The meter described will measure 0-40 mmfd and 0-900 mmfd in two ranges, and will resolve one mmfd on the low range.

The operation is shown in Fig. 1. A coil is tuned to resonate at one mc by two capacities, C1 and CX. An oscillator excites the circuit at one mc. and an rf voltmeter indicates resonance. Assume the circuit resonates with a total capacity of 50 mmfd. If there is no CX connected, then C1 must be 50 mmfd. to resonate. If an unknown capacity is now connected, C1 must be reduced exactly the amount of CX to bring the circuit back to resonance. If C1 is calibrated, the value of the unknown is indicated directly on the C1 dial.

This process is called capacity measurement by substitution. The unknown substitutes for an equal amount of capacity in the calibrated variable. This method has several important features. First, and most important, the accuracy and long time stability depend only on the calibrated variable condenser. Drifts in the battery, oscillator, and inductances will not affect the instrument. Second, the meter is unaffected by the hum pickup that often plagues homemade bridges. Third, condensers that are lossy at radio frequencies can be detected. Fourth, it is easy to measure capacities at the end of a long, high-capacity cable.

Fig. 2 shows the complete circuit. A simple transistor oscillator drives the tuned circuit

Fig. 1—Capacity measurement by the substitution method.

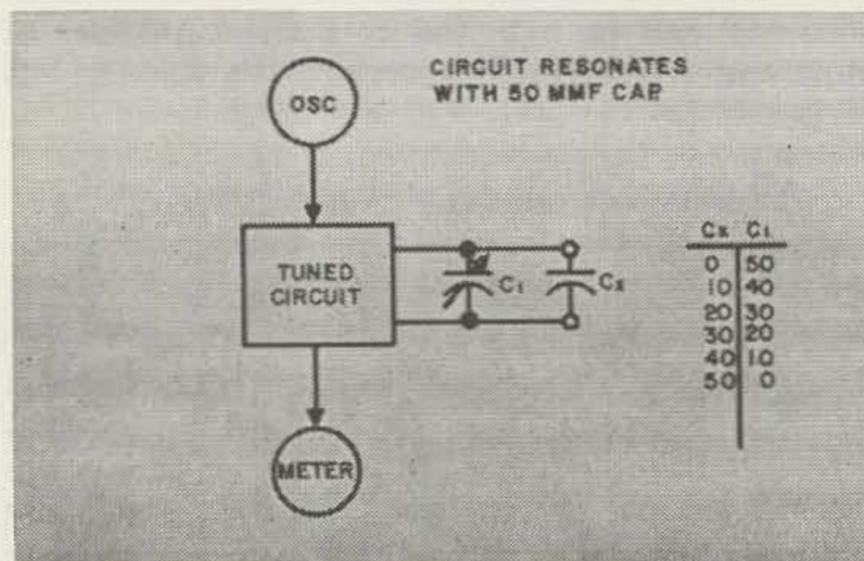

L2C2 through a small coupling condenser. A diode voltmeter indicates circuit resonance by a maximum reading. The operating frequency in my case was 1450 kc, but is not critical so long as the L1C1 and L2C2 circuits resonate at the same frequencies with C1 and C2 at maximum capacity. I suggest that L2 be duplicated and L1 be adjusted as described later. The leads to C3, S1, and the CX terminal should be short and spaced away from ground to reduce stray capacity in this part of the circuit.

Adjustment

Turn S1 to the "Hi-C" position and set C1 and C2 to maximum. Adjust the slug in L1 for a maximum meter reading. (If no read-

calibration or zero adjustment for the C2 dial. Now place known capacities across the CX terminals, and peak the meter with the C2 dial. Mark the known values on the C2 dial. The maximum capacity that can be measured is the value of the maximum capacity of C2.

Small capacities are substituted in the oscillator circuit which, because of its lower operating capacity, gives a more spread out scale. Set C2 at its zero mark and switch S1 to "Lo-C". Peak the meter with C1 and mark the C1 dial "0". Place small known capacities on the CX terminals and calibrate the C1 dial. The C2 dial now becomes the zero adjustment for the low capacity scale. The maximum capacity readable on the C1 dial will be less than 50 mmfd because of stray capacities.

Operation

To operate the capacity meter, simply set the scale in use on zero and peak the meter with the other dial. Add the unknown capacity and re-peak the dial in use and read the unknown capacity.

Capacities above the range of C2 may be measured by placing them in series with a known capacity of about 1000 mmfd and reading this combination. The unknown may then be calculated as shown in Fig. 3. If desired, a second scale could be calibrated on C2 for use with a particular series condenser.

At resonance the total capacity tuning L1 and L2 do not change between the zero and measure adjustments. Therefore the meter readings should be exactly the same. A high Q (low loss) condenser will not affect the meter

reading, but a low Q unit will decrease the reading. Generally, any condenser that affects the meter reading should not be used in a high Q or tuned circuit.

This meter has been in use for two years and is second only to the GDO in usefulness around the shack. 73

Fig. 2.


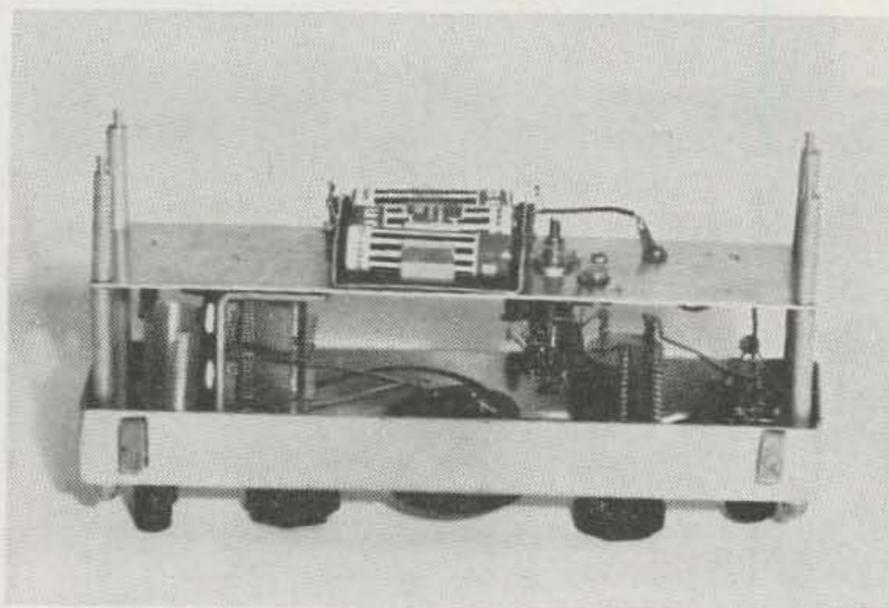
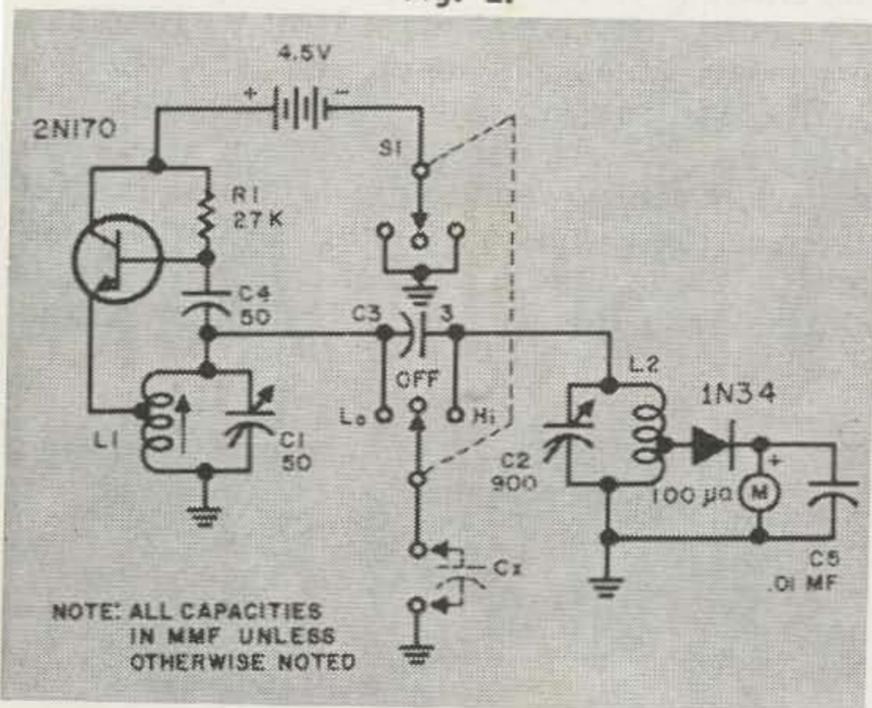


Fig. 3—A large capacity can be measured by placing a known capacity in series and measuring the combination.

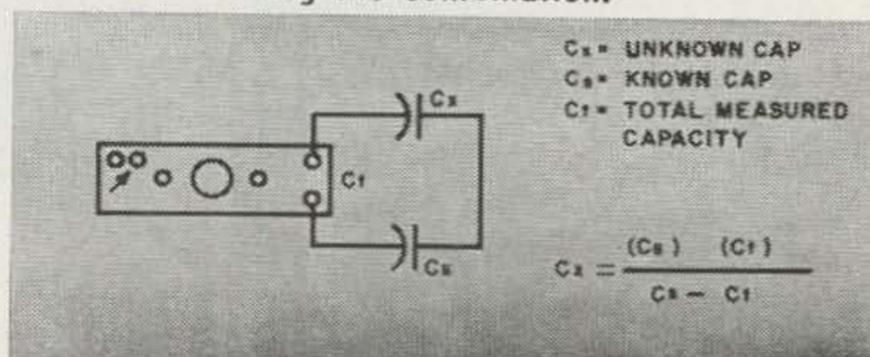

Calibration

Turn S1 to "Hi-C" and set C2 to very near its maximum capacity. Mark the C2 dial "0." Peak the meter with C1., which becomes the

ing is obtained, either the oscillator is not operating or it is not tuning to the frequency of L2C2.) The meter reading should be sharp but smooth as L1 is tuned. If C3 is too large, the meter will jump, due to the two tuned circuits interacting. If C3 is too small, the meter indication will be low. In my case the maximum reading was 20 μ a.

Now switch S1 to "Lo-C" and reduce C1 to again peak the meter. The difference in the two C1 settings is due to stray capacity in the instrument. The meter is now ready for calibration.

Station Control System



David L. Cabaniss, WITUW
113 George St.
Bristol, Conn.

THIS article is not directed at the amateur who has everything! It is, however, directed at those who like to tinker, etc., and find out just what can be done with all that extra junk hanging around the shack. The offspring of my junk box is shown in the photograph: a simple, cheap and easy way to convert your "push-to-talk" phone station into a "press-the-key-to-transmit" CW station, without the necessity of tearing apart all that gear that is operating so well at the moment."

All types of control systems have good and bad features. None of the systems described in the well known amateur publications depicted the type of system that I was looking for, so I decided to build my own, using a combination of many ideas that are well known in amateur circles. Of course, one of the prerequisites of the unit was that it had to be built entirely from the junk box.

The entire Station Control Unit was built on the chassis of an old ac-dc set. The panel is bakelite, and the cabinet is made of wood.

Referring to the circuit diagram it will be noted that the power supply is a standard $\frac{1}{2}$ wave rectifier type, providing 115 v dc, isolated from the line. I happened to have an old isolation transformer but two filament trans-

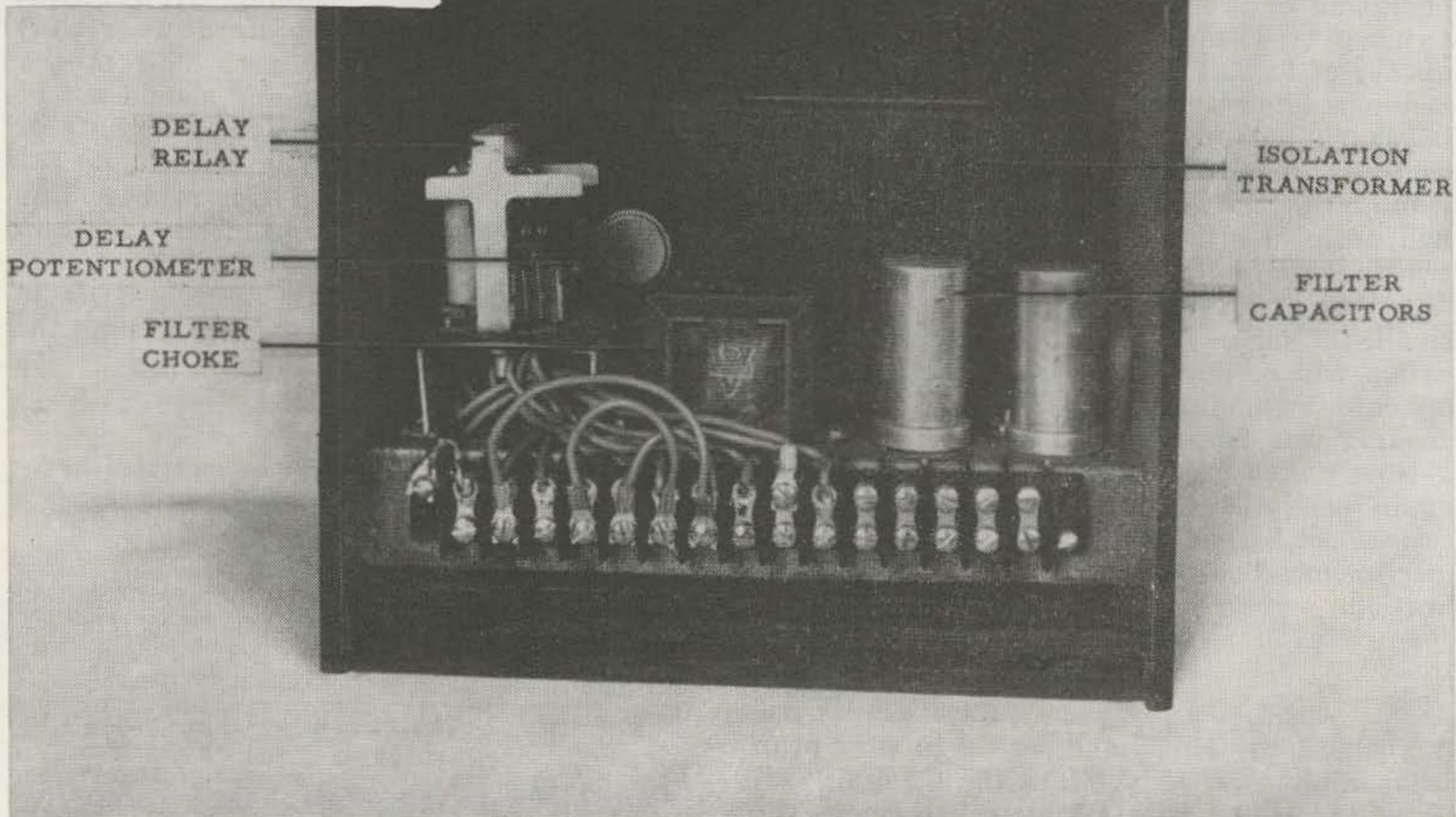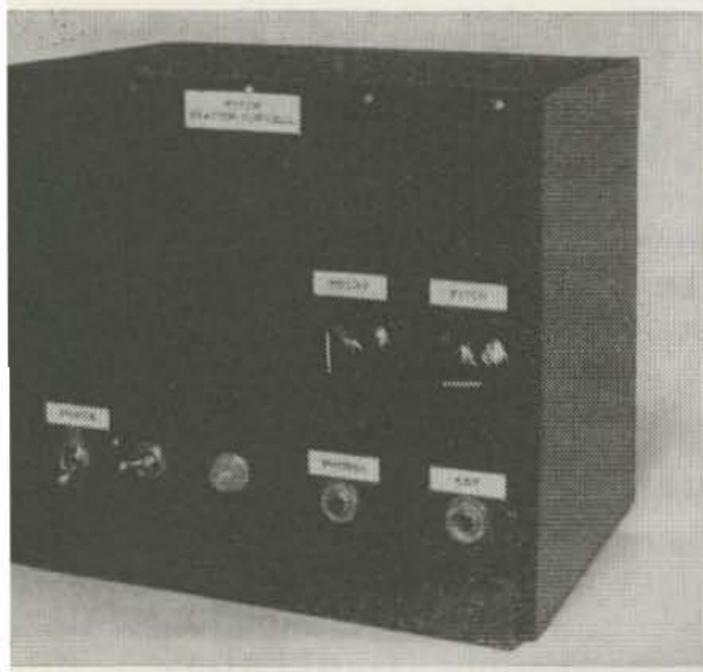

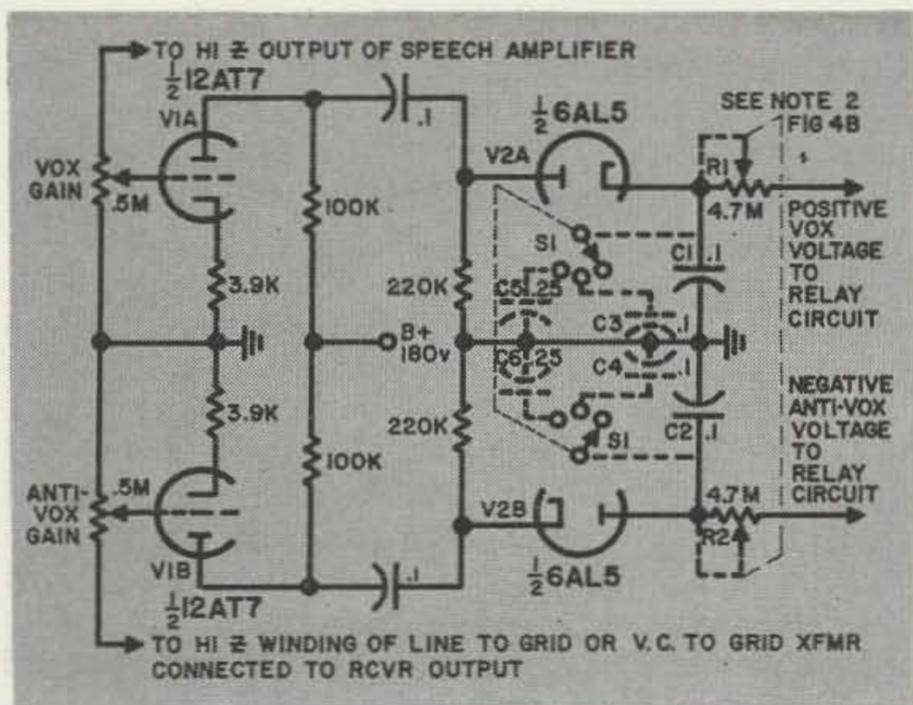


Fig. 1B. Suggested audio and detector circuit for the Schmitt trigger shown in Fig. 1A. Note 1: If variable C adjustable delay is desired, change C1 and C2 to .05 mfd and add C3, C4, C5, C6 and S1. Note 2: If variable R adjustable delay is desired, change R1 and R2 to 10 megohm dual potentiometer. The fixed values shown for C1, C2, R1, E2 provide optimum recovery delay.

While the basic circuit has many variations, the most suitable of these is the Schmitt trigger. The output of this circuit has two states, either cutoff or saturation, while the input possesses a selective or slicing characteristic. That is, when a signal or control voltage below a precisely determined trigger point is applied, there is no change in output. When the control voltage exceeds this point, the output stage triggers from cutoff to saturation. The circuit switches back to its quiescent condition when the control voltage falls slightly below the operate point. There is no appreciable in-between condition as the switching time is measured in microseconds. All of this is obtainable at no additional cost, since the component requirements of the Schmitt trigger are less than those of many dc amplifier circuits. Further, a very sensitive or high quality relay is not necessary. Almost any relay will do, so long as it has the required number of contacts and its operating current approximates the saturation current of the output stage.


Practical testing now appeared in order, so a speech amplifier and VOX assembly, using the circuit shown in Fig. 1A, was constructed for use in a surplus conversion project. With the configuration selected, the output stage is normally saturated and a positive control voltage is required to switch the Schmitt trigger circuit. The device functioned perfectly, switching reliably on 3 volts dc and switching back when the VOX voltage fell slightly below that point. A positive voltage applied to the grid of V1A causes a drop in the plate potential of that stage. This plate is coupled to the grid of V1B, which is normally clamped at cathode


potential. The plate current of V1B decreases, thus the cathode potential drops and the grid potential of V1A increases. The action is regenerative and V1B rapidly cuts off. Lowering the applied bias signal to a point slightly below the trigger voltage causes a reversal of this action. With the control voltages available, it was more convenient to return the input grid to a slightly negative point and to use a positive voltage to switch the stage. If the reversed relay operation is considered objectionable, simply add the bias resistor shown in dotted lines and a negative signal will saturate the output section of V1, although a slightly greater control voltage will be required. The improvement of this circuit over the conventional dc amplifier type of voice control is remarkable. No attempt was made to further optimize the circuit since operation, with values shown, was satisfactory in every respect.

Input and detector circuits suitable for use with this Schmitt trigger relay are shown in Fig. 1B and are typical of those normally used in this application. The VOX gain control is advanced until the unit is tripped by normal speech. Since the relay circuit operates on a "slicing" principle, considerable delay or recovery time adjustment may be obtained by varying the VOX gain between the points where normal speech trips the relay and ambient room noise causes operation. The theory of this is simply that the more the rectified control voltage exceeds that required to operate the relay, the longer it takes that voltage to decay to the point where the reverse operation occurs. After adjustment of the VOX gain, the Anti-VOX gain should be advanced to the point where normal speaker level will not trip the relay.

If the range of delay adjustment is not considered adequate, the values of R1 and R2 or C1 and C2 may be simultaneously changed to

Fig. 2. Transistorized multivibrator relay circuit provides reliable switching with very low level audio input.

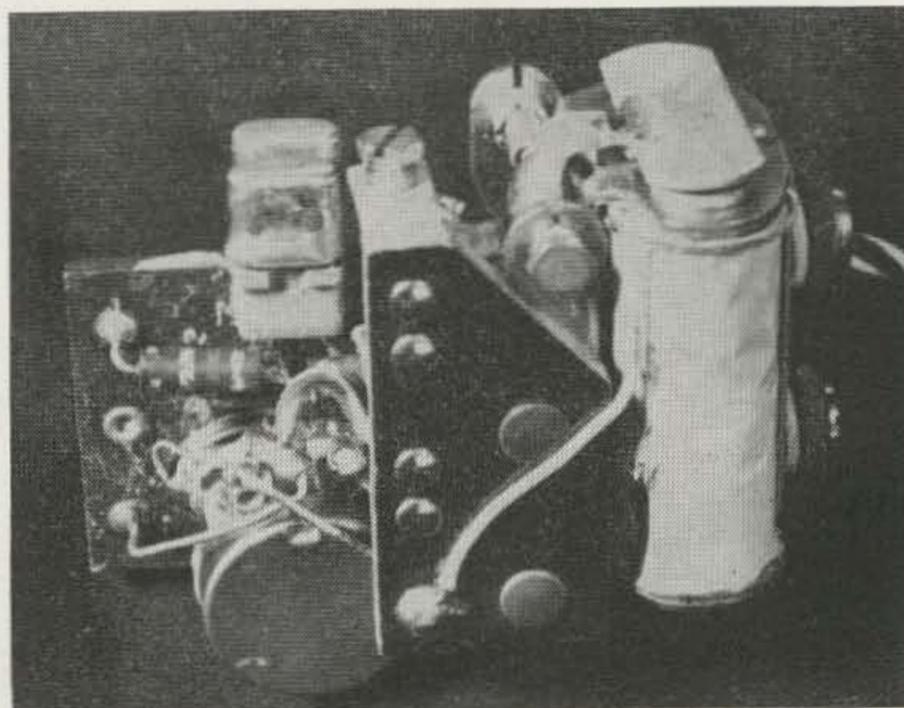

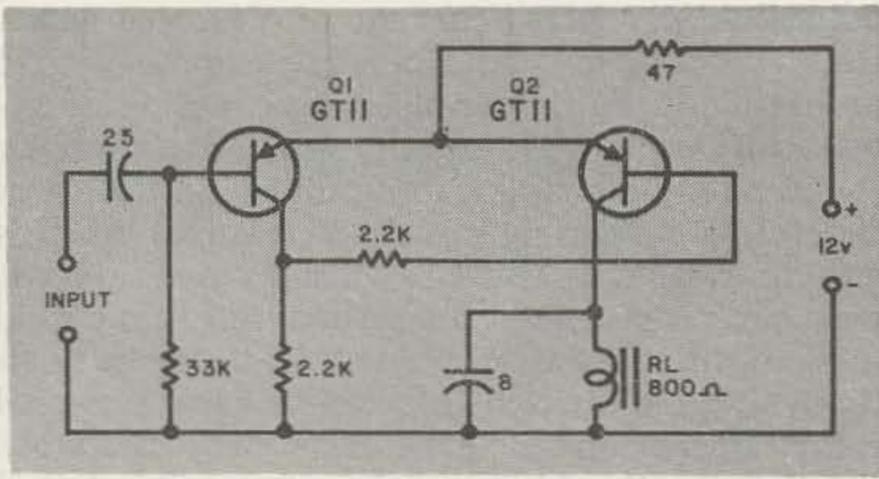

Compact, transistorized multivibrator controlled relay assembly. The complete switching circuit is shown here.

covery time is required, either the R or C option of Fig. 1B may be installed. Replace R1 and R2 with a 10 megohm dual potentiometer or install the capacitor switching network shown.


Transistorization

Having confirmed that use of the multivibrator in vacuum tube VOX circuits offered the apparent advantages, attention was turned to the use of transistors in this application. The writer desires to construct a fully tran-

sistorized SSB exciter with all of the operational features and performance characteristics of the better available commercial equipment. The following material was gathered for the preliminary design of the VOX circuit of this future project.

The use of a transistorized monostable multivibrator for relay control is not new. Such a circuit was featured in an article, "Multivibrator Operates Relay", by G. B. Miller, and published in the December 5, 1958 issue of "Electronics". While the circuit, reproduced in Fig. 2, was designed to function with an ac switching signal, the basic slicing action with the attendant advantages is present. While it might appear that an ac operated relay would be ideal for VOX switching, this is not necessarily true. While it functions perfectly in the VOX action, the integrating characteristic of the circuit makes the application of the Anti-VOX signal a difficult task. This emitter-coupled circuit is of interest in such applications and its performance is remarkable. If the Anti-VOX feature is not required, this circuit is a good, clean solution to the problem. Switching is obtained with an input signal of about 10 millivolts from a 10 ohm source and the circuit switches back when the signal drops slightly below this level. One additional advantage accrues in the use of multivibrators in

Fig. 3. Vox Anti-Vox module of the Collins Radio 786F-1 Sideband Generator. This portion of the 310F-6E Exciter illustrates a commercial application of transistorized voice control switching circuitry.

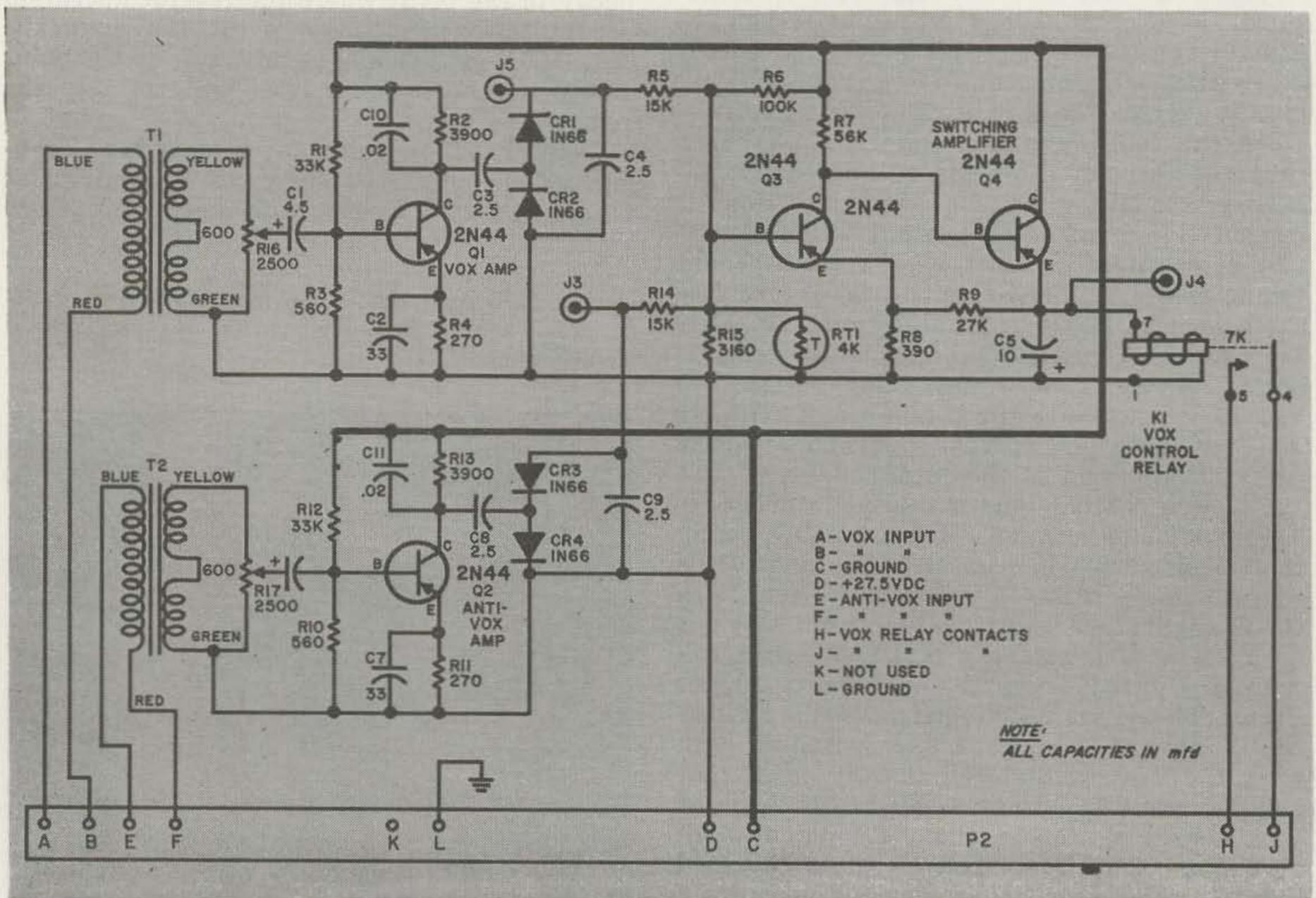

transistorized switching circuits. A transistor is capable of switching power far in excess of its Class A amplifier rating if the transition time between cutoff and saturation is very short. Therefore, any circuit that would permit the output stage current to dwell at some point between cutoff and saturation would greatly increase the output stage power handling requirement. If the relay recovery time is too short, the value of the capacitor shunting the relay may be increased in value up to several hundred percent without adverse effects.

Collins Radio in one of their "firsts" has used transistorized switching amplifiers in their military/commercial 310F-6E High Frequency Communications Exciter. The circuit, courtesy of Collins Radio Company, is shown in Fig. 3. Another feature contributing to the performance of his unit is the use of a voltage doubler configuration in the VOX and ANTI-VOX rectifier circuits. This technique is par-


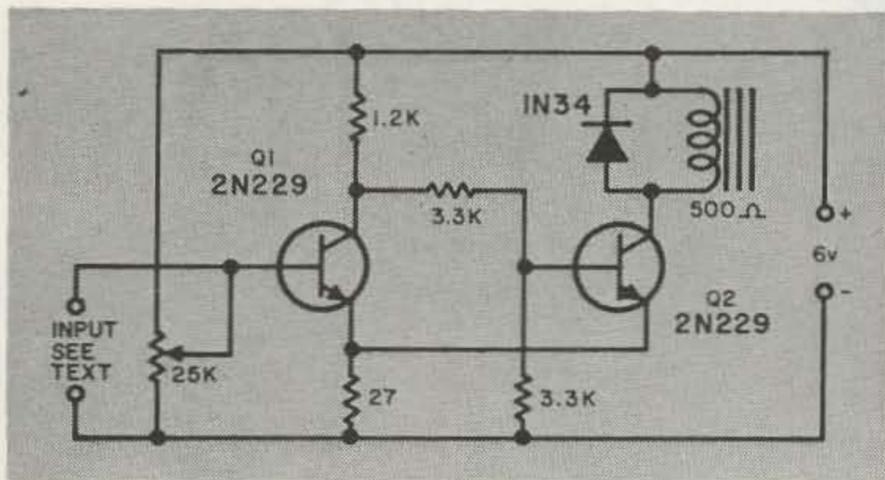


Fig. 4A. DC version of the transistorized multivibrator relay switching circuit.

ticularly valuable when using transistors, since the required voltage swing may be difficult to obtain without using special transformers. In any event, this circuit is seeing increasing use in receiver AGC and transmitter ALC applications.

The device shown in the photograph was constructed to test the ideas generated by this approach. The circuit, shown in Fig. 4A, was adapted from a circuit described in the Sylvania manual, "Performance Tested Transistor Circuits". The potentiometer in the input circuit is a change from the original bias network and permits setting the input stage bias for best operation. No real attempt was made to miniaturize the circuit, since the relay, the only one immediately available, was the limiting factor. Actually, the circuit is very non-critical and almost any general purpose NPN transistor may be used. If the battery and diode polarities are reversed, PNP transistors will serve equally well.

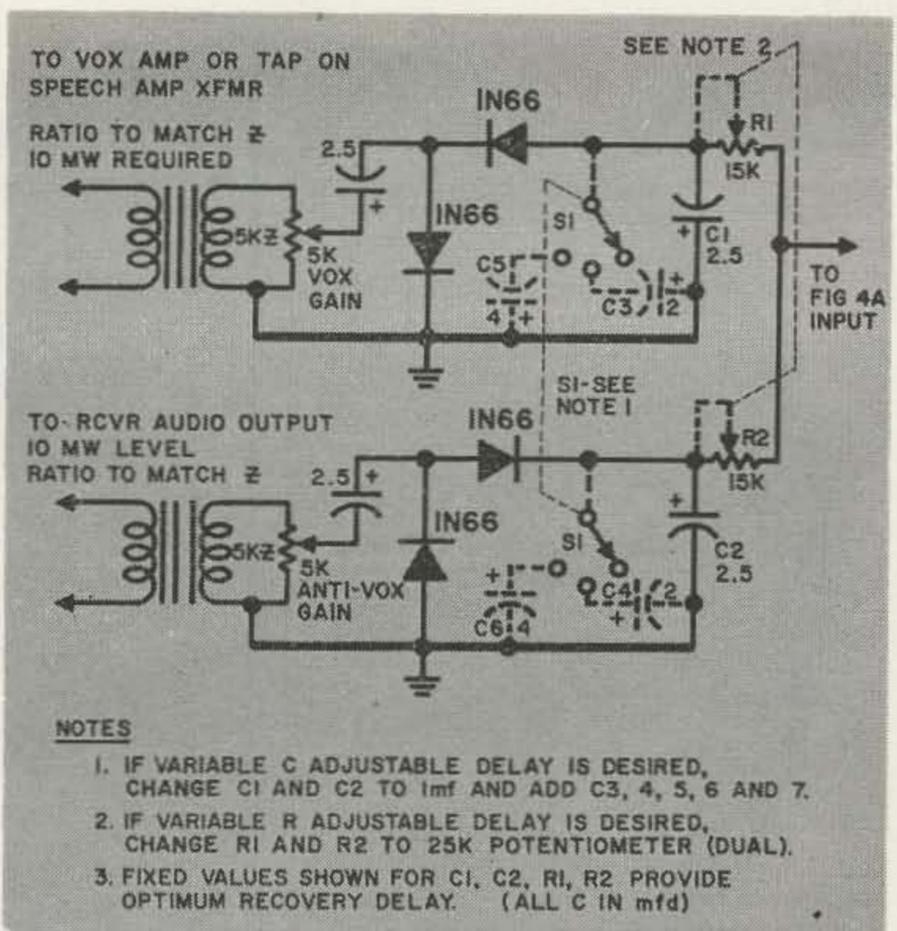Base bias of the input transistor is initially set slightly below the point where the relay operates. In this condition, Q1 conducts and Q2 is cutoff. As the base bias of Q1 is reduced by the rectified control signal, the collector



NOTES


1. IF VARIABLE C ADJUSTABLE DELAY IS DESIRED, CHANGE C1 AND C2 TO 1mf AND ADD C3, 4, 5, 6 AND 7.
2. IF VARIABLE R ADJUSTABLE DELAY IS DESIRED, CHANGE R1 AND R2 TO 25K POTENTIOMETER (DUAL).
3. FIXED VALUES SHOWN FOR C1, C2, R1, R2 PROVIDE OPTIMUM RECOVERY DELAY. (ALL C IN mfd)

Fig. 4B. Suggested input and detector circuit for the transistorized relay shown in Fig. 4A.

current is reduced and the collector voltage rises. This rise appears at the base of Q2 and when it reaches a critical value, Q2 conducts, switching the multivibrator. Relay current under these conditions is either negligibly small or, for all practical purposes, infinitely large. Therefore, positive, fast relay action is obtained with only a few millivolts variation in input signal. Desired operating delays in relay action may be achieved by altering the time constant of the RC network in the VOX and ANTI-VOX control signal rectifier circuits. Starting point values for this application may be found in Fig. 3. Since the detector circuits of Fig. 3 are designed for use with PNP switching transistors, the VOX and ANTI-VOX inputs of Fig. 3 must be reversed to permit use with the NPN switching circuit of Fig. 4A.

The information presented herein was developed to meet the previously described specific requirements and it is believed that the objectives have been realized. The results warrant more general application of this type control circuitry and, while certainly not in finished construction project form, this data should be of considerable value to anyone embarking on a similar project.

The same considerations, with respect to recovery time delay, that were described with reference to Fig. 1A and 1B apply to the transistorized version. Fig. 4B shows suitable input and detector circuits for use with the relay unit shown in Fig. 4A. If the recovery time delay of the circuit, using values specified, is not acceptable, alter R1 and R2 or C1 and C2 for the desired time constant. If adjustable recovery time is desired, replace R1 and R2 with a dual 25,000 ohm potentiometer or install the capacitor switching network shown.

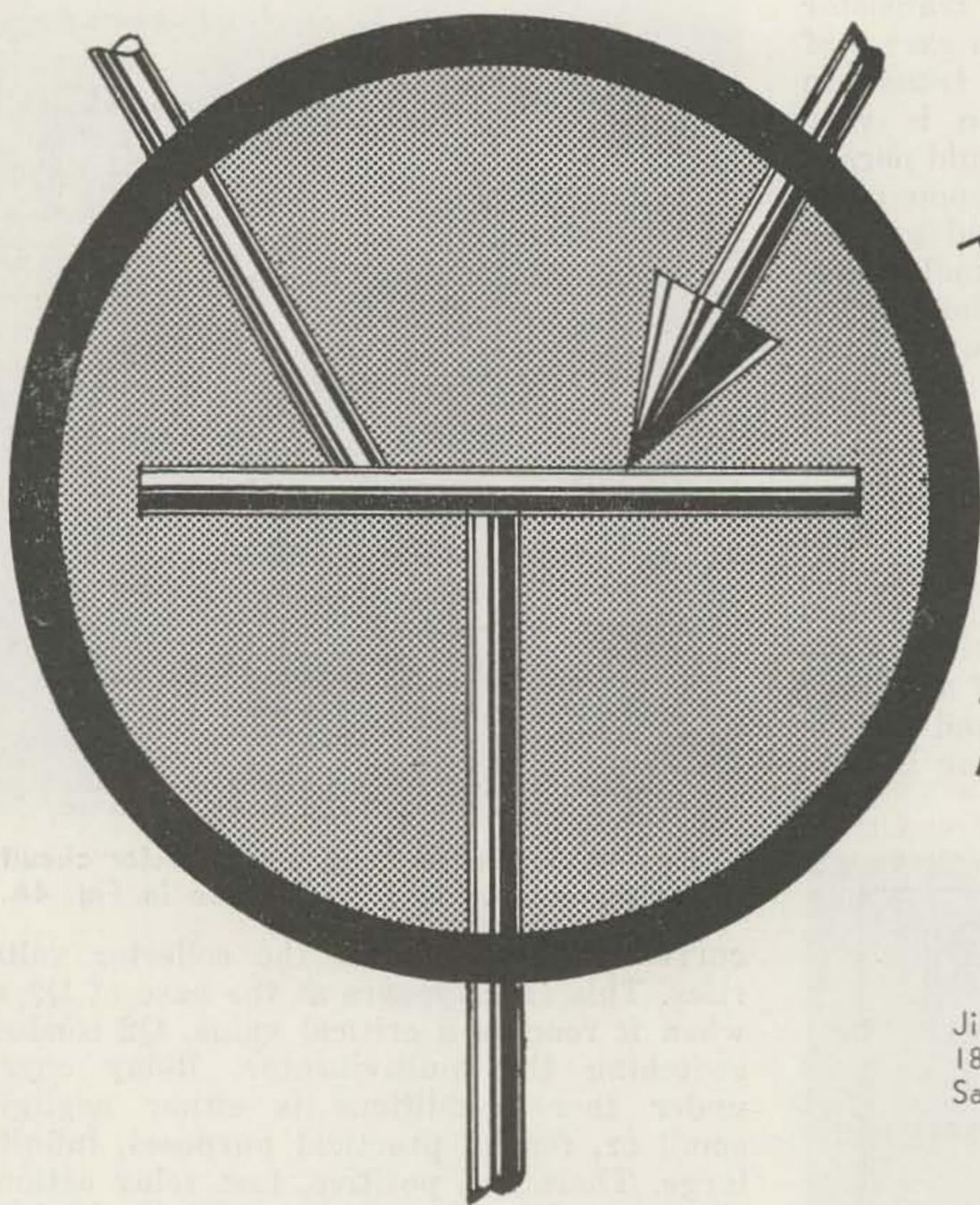

The Fine Art of Transistorizing

Jim Kyle K5JKX/6
1851 Stanford Ave.
Santa Susana, Calif.

SMALL, lightweight, low in power requirement . . . the transistor requires no sales talk to most hams. Dozens of amateur designers over the country are busily converting tried-and-true vacuum-tube circuits to use the super-duper semiconductor, while others are developing new circuits.

However, there are tricks to all trades—and the fine art of transistorization is no exception. The purpose of this article is to outline the general procedure for conversion of vacuum-tube circuits to employ transistors, and to point out some of the tricks along the way.

Many designers, faced with the problem of transistorizing a tube circuit, simply plug in semiconductors in place of tubes, change some parts values to take into account the differences of impedance involved, and hope for the best. They seldom achieve it, although their circuit will usually work.

As a matter of fact, this approach is just about the only starting point for conversion of a vacuum-tube circuit. The major thing to keep in mind is that it's just that—a starting point, not an end product.

To employ this technique (if I may repeat some hoary truths from the basic transistor books) all you have to do is remember that the base of the transistor corresponds to the

grid of a triode tube; the collector corresponds to the plate, and the emitter to the cathode.

Like tubes, transistors must be properly biased for the desired operating point. To continue using the "tube" analogy, the collector (plate) to emitter (cathode) circuit must be reverse-biased, while the base (grid) to emitter (cathode) circuit must have forward bias.

In the beginning, an easy way to remember what is forward bias is this: Consider "P" and "N" in the transistor type designation as the initials of "positive" and "negative" respectively. When a positive voltage is connected to a P element and the voltage is returned to the emitter, the element is forward biased. If a negative voltage is connected to a P element and returned to the emitter, the element is reverse-biased.

If you're using NPN transistors, polarity of the supply voltages will be the same as those used with vacuum tubes: the collector must be positive and the emitter negative. However, the base (grid) voltage will be opposite to that of a tube—it must also be positive.

Naturally, polarity of supply and bias voltages will be reversed with PNP transistors (the most common type).

Much has been said about the "extremely" low impedance of transistors as compared to

tubes. While semiconductor devices do have lower impedance than their tube equivalents, the difference is not so great as many may believe.

The reason behind the publicity about "extremely" low impedance is this: most early transistor work was done with the grounded-base circuit.

Looked at as a tube substitute, this makes it a bit more clear. The input impedance of a grounded-grid circuit is only about 75 to 100 ohms when a vacuum tube is used.

And in comparison, the 50-ohm average value of input impedance for a grounded-base transistor amplifier isn't so extreme, after all.

Actually, most transistor circuits exhibit impedances approximately 100 times less than their tube equivalents. If you used a 270,000-ohm plate load resistor in the tube circuit, try a 2,700-ohm unit in the transistor version. This rule is barnyard-broad, but will at least give you a starting point for experimentation.

One of the major differences between transistors and vacuum tubes is the fact that transistors are operated by current, not by voltage. Tubes, on the other hand, are primarily voltage amplifiers and any current gain is secondary.

This leads to the concept of "duality," which you'll find many words about in any semi-advanced transistor text. They won't be repeated here, except to say that the "dual" of any circuit element is some other circuit element which responds to current in the same manner that the original element responded to voltage. For instance, the series-resonant circuit is the dual of the parallel-resonant circuit, because current flow is high at resonance in the series circuit while voltage is high at resonance in the parallel case.

The amateur designer has little need for the "duality" concept, however. The time spent learning more about it will be put to better use discovering the circuits which are peculiar to transistors only and which have no vacuum-tube equivalents.

The most famous of these, of course, is the amplifier hookup which bears the lengthy title of the "complementary symmetry" amplifier. It provides push-pull amplification without any phase inverter, and has no equivalent in tube circuitry, since nobody yet has built a tube which operates with the plate negative and the cathode positive.

Basically, the amplifier consists of identical class B single-ended amplifiers connected with inputs in parallel and outputs in push-pull. The only difference between the amplifiers is that one uses a PNP transistor, and the other an NPN. Such a circuit is shown in Fig. 1.

Any signal which tends to increase forward bias on the transistor causes an increase in collector current. Therefore, the positive peaks of the input signal are amplified by the NPN transistor, and the negative peaks by the PNP.

Any signal which reverse-biases the base cuts the collector current off. Therefore, positive peaks cut off the PNP unit and negative peaks cut off the NPN. Bias conditions for the bases are chosen to minimize crossover distortion, and the result is a push-pull amplifier without phase inverters. The major disadvantage of the circuit is that it requires separate power supplies for each half of the amplifier.


The amplification property just mentioned—forward base bias resulting in greater collector current while reverse bias cuts the unit off—leads to another important circuit which is peculiar to transistors: the switch.

If a transistor is hooked up as shown in Fig. 2, with the base open-circuited and a load in the collector circuit, the transistor will appear to be an open switch so far as the load is concerned. No current can flow through the collector circuit.

However, application of forward bias to the transistor will reduce its collector-emitter resistance to less than 100 ohms (less than one ohm, in many cases) and it will then look to the load like a closed switch.

Since the collector current in the average experimenter-quality transistor can run as high as 50 ma, and rated current for more-expensive units runs into the amperes, the transistor is a simple substitute for the power relay. In addition, a current measured in microamperes is injected into the base to turn the unit on, while the load may take several amps.

Fig. 1—The complementary-symmetry amplifier shown here produces push-pull action without phase inverters. Values of resistors R are chosen from published data on the transistors chosen for the circuit. Input capacitor C must be chosen for best low-frequency response. Its value will be in the neighborhood of 25 mfd. in most cases. The transformer is chosen from power amplifier design charts such as those shown in the GE Transistor Manual. A 16-ohm speaker may be substituted for the transformer if desired.

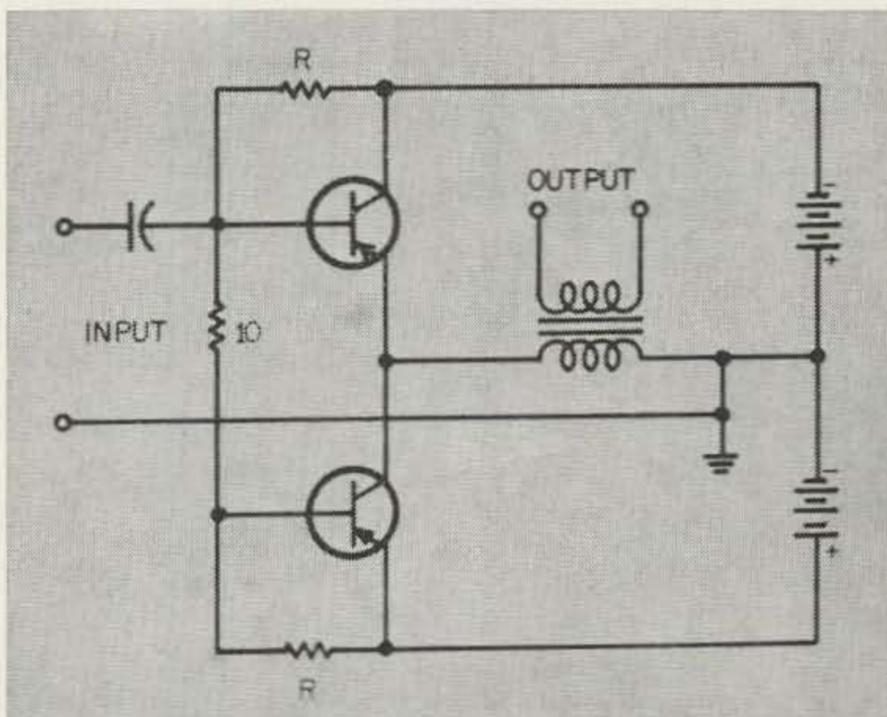


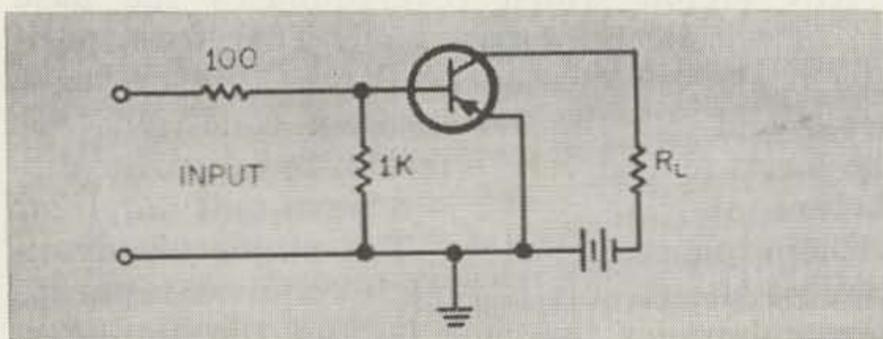


Fig. 2—The transistor switch circuit controls a load current which may range up to several amperes and requires only microwatts of input power. The 100-ohm series base resistor is to limit current to a safe value, while the 1000-ohm resistance from base to ground limits "off" current to a low value. Value of resistor R_L is determined by the power rating of the transistor. For a 2N107 operating from a 9-volt battery, R_L should be approximately 6,000 ohms.

The switching circuit, though, isn't confined to the handling of power. Take, for example, the FM limiter. If a sine wave is applied to the input of a transistor switch, a clipped sine-wave output will be obtained at the collector. This output will also be amplified. As the input frequency changes, so will the output frequency—but output amplitude will remain constant at the peak supply voltage so long as enough input signal is supplied. Presto, you have a four-component FM limiter!

If you need a source of square waves, the transistor switch will provide them. Simply

Fig. 3—The compound connection shown here provides a unit with gain ranging up to 250 million times. Though four transistors are shown, there is no theoretical limit to the number which may be used. Current gain of the total unit will be the product of each individual transistor's current gain. The individual transistors may be identical or of different characteristics, so long as all are either PNP or NPN. The compound unit is used as a single transistor (see dotted lines) in any standard circuit.

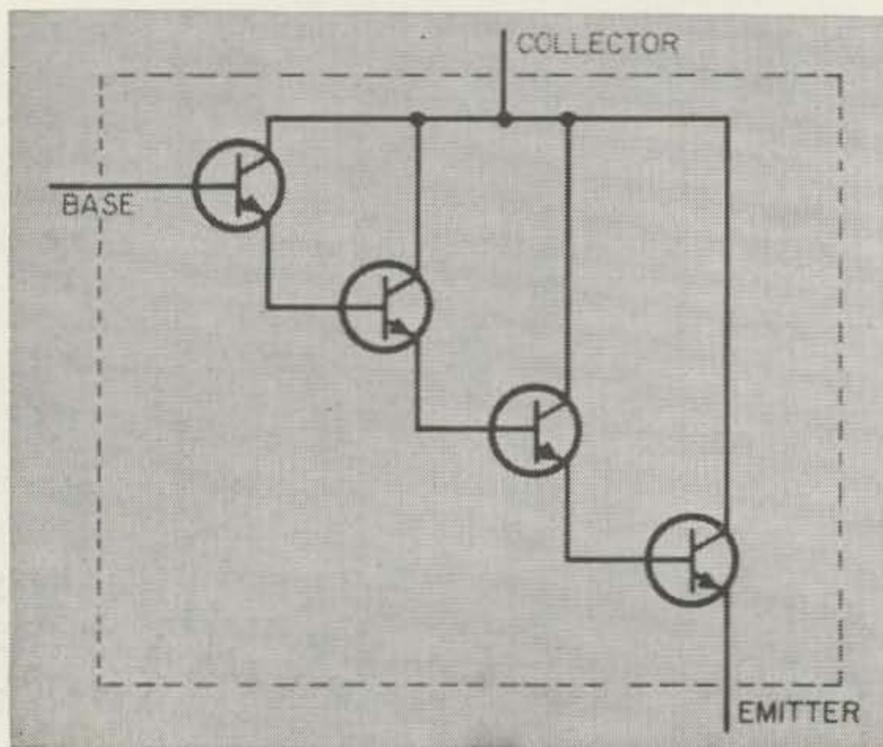

feed in a sine wave of the proper frequency, strong enough to drive the switch completely into saturation on each half-cycle, and pick off your square wave at the collector. In both of these "example" circuits, of course, a resistor is used for the switch load, as shown in Fig. 2.

Another transistor-only circuit can be used to obtain any gain you might desire in a single stage—up to a limit of some 250,000,000 times! Known variously as the Darlington and the compound connection, it combines two or more transistors into a single "compound transistor" which has a gain equal to the product of all the gains of each transistor involved.

The connection is shown in Fig. 3. Once the transistors have been connected together, think of them as a single unit with only three leads—base, emitter, and collector—and an overall gain equal to the product of the individual gains.

For an example, consider four type 2N508 transistors (an audio type selling for approximately \$2.00 which is unequalled gain-wise by anything else near that price), each of which has a current gain (or *beta*) of 125. When all four are connected in compound, the total gain is 125^4 or approximately 250,000,000—all in a single stage.

The practical limit to gain obtained in this manner is input noise. When leakage current from the first transistor in the compound becomes great enough to mask out the desired signal, you have too much gain. Remove one transistor and try it for size a second time.

Use of circuits such as these can frequently simplify a design when it is converted from tubes to transistors. A case in point is Jim Kyle's "Five-Dollar Frequency Meter."

The original tube-style frequency meter circuit used four vacuum tubes—two were in a squaring amplifier, one double-diode was in a counter circuit, and the fourth was the power-supply rectifier.

An earlier adaptation of that circuit to transistorized form used two transistors and four diodes to accomplish the same purpose. Two of the diodes squared the input signal, the transistors amplified it, and the other two diodes formed the frequency counter.

However, application of the basic switching circuit not once but twice brought the total unit down to two transistors. The input switching transistor converted the input signal to an amplified square wave, while the second transistor's base served as both counting diodes and its collector provided DC amplification, enabling use of a less expensive meter for indicating purposes.

You can do the same with your favorite tube circuit—if you just remember that straight substitution isn't the answer. Usually, if you take the time to figure out the differences, the fully-transistorized circuit proves simpler in the end.

Simplify Your Log-Keeping

ANY active ham knows that keeping his log accurate is simple—but checking back to verify a contact six months later can prove to be a nightmare. Here's a log-keeping trick (checked out and approved by the FCC) which can simplify QSL problems and bring order out of chaos.

Simply keep the log on 3x5 filing cards, one card per contact, rather than in the conventional log-book. Suitable cards are available commercially, already printed with blanks for the pertinent information, or you can make your own. Be sure to include the calls of both

stations, the time and date of the contact, the frequency, and your power input, if you prepare your own. A separate card can be used for TEST and CQ operating time.


Once filled out, the card is filed—not chronologically—but in alphabetical-numerical order. That is, DL4 cards would be filed ahead of DL5, and both would be ahead of K1's.

With this filing system, every contact can be quickly verified, given the call of the other station. All required information is still kept, and QSL bookkeeping becomes a pleasure rather than a chore. Try it and see! 73

New Product

Mobile Converters

International Crystal Mfg. Co. has a new line of mobile converters that may be just what you're looking for. These gadgets are quite small for simple mounting under the dashboard and operate either from 6 or 12 vdc, negative or positive ground. They are transistorized, have a peaking control, separate inputs for short-wave and broadcast antennas, and a switch which permits normal BC operation when not in use. The output range is 600-1600 kc and models are available for converting from all ham bands, from 75 thru 6 meters, the 27 mc citizens band, low band CAP, and the 10 or 15 mc WWV broadcasts. These sell for \$22.95 each. Special models will be made for

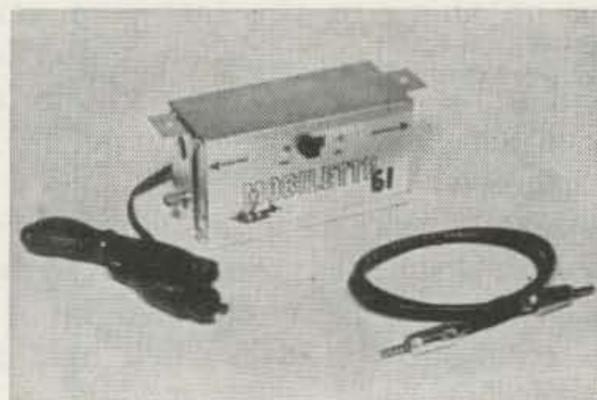

any band in the 2-50 mc range for \$25.95. Buy a bagfull. The 40 meter model pulls in the CHU time signals as well as letting your eavesdrop on 40 meter doings.

Book Review

Three books were received the other day for review in 73. All three have to do with radio service, which seems rather off the track for a ham magazine. For what little help it will be to them here they are:

1) **Practical TV Trouble-Shooting**, Gernsback Library #102. This 128 page paperbound book is a collection of reprints from Radio Electronics magazine and explains how to fix some of the "problem" sets a TV serviceman runs up against. \$2.35.

2) **Practical Auto Radio Service and Installation**, Gernsback Library #87. This one is 160 pages and costs \$2.95. The chapter on interference suppression may be worth the price of the book if you're having trouble with this misery.

3) **Radio, Television and Electrical Repairs**, Odhams Press. This British book (third edition) is chock full of pages (480 of them) tells you how to repair radios, record players, FM sets, vacuum cleaners, electric water heaters, refrigerators, washing machines, cookers, hot plates, and almost anything else you can think of. The British illustrations are fascinating. 21s,

which about \$3.00 over here . . . plus shipping and all that.

Tape Recorder Book

Rider (#251) has just published a new tape recorder book called "Getting The Most Out Of Your Tape Recorder." This 176 page soft cover book approaches the subject from the user viewpoint and will not strain the technical understanding of the Novice. It is profusely illustrated, as is usual with the Rider books. To give you an idea of the field covered, here are some of the chapters: What Kind of Tape Machine Do You Need?, How Many Heads Do You Need?, Types of Record Level Indicators, Adding a Tape Recorder to the Audio System, Microphones, Tape Accessories, Varieties of Tape, Frequency Response, Distortion, Signal to Noise Ratio, Equalization, Checking Frequency Response-Equalization - Azimuth - Head Height - Bias - Distortion - Noise, Stereo Considerations. Price is \$4.25.

The Perfect Squelch

Staff

ESPECIALLY in mobile or VHF operation, the background noise emitted by a receiver when no signal is coming in can become tiring in a hurry. Fortunately, it's not difficult to squelch out this noise with a muting circuit.

Such circuits are popular. This popularity is attested to by the number of different articles published on them in the last five years. The only trouble is this: with so many different circuits in print, how are you going to choose the one which best suits your needs . . . the perfect squelch?

To help you make this decision, we've gathered these circuits all in one place. Advantages and disadvantages of each are listed to help you choose which one will work best for your own installation.

Before going into details of the various squelch circuits, let's take a look at the basic purpose of such a system and the various ways in which this purpose may be accomplished.

The purpose is simple—to quiet audio output from a receiver when no signal is coming in. The ways of doing this, however, are legion . . . and each has its own set of pros and cons.

You can open the audio path with a carrier-controlled switch (the basic operation of most squelch circuits) or you can short-circuit this same audio path with a similar switch acting in reverse. You can use another carrier-operated switch to turn the whole receiver on or off—but this requires, in essence, two receivers, and so is not very practical in use.

Another approach is to use part of the audio signal itself to control a switching circuit. Squelches based on this principle are usable for sideband or CW as well as AM and FM. Any muting device which depends on the carrier for operation won't work so well with carrierless sideband.

You can see that all these techniques require some sort of switching circuit. However, this switch may be either a relay, a biased diode, a multi-grid vacuum tube, a combination of triodes, a transistor, or any other electronic device which allows one signal to control passage of another.

By the mathematical laws of permutation and combination, and considering only the items specifically listed above, this works out to a total of 20 possible different circuits. When you take into account differences in equipment, the number of possible practical circuits runs rapidly into the thousands.

We aren't going to talk about any thousand circuits here. We aren't even going to talk about 20 of them, since some of the possible combinations don't work out in practice. We *are* going to talk about all the practical squelch circuits which have appeared in the literature since 1945.

These circuits fall into six broad categories. The best-known of these is possibly the relay-squelch circuit, made famous by the SCR-522 and since adapted to many other receivers.

Other categories include shunt-tube squelch,


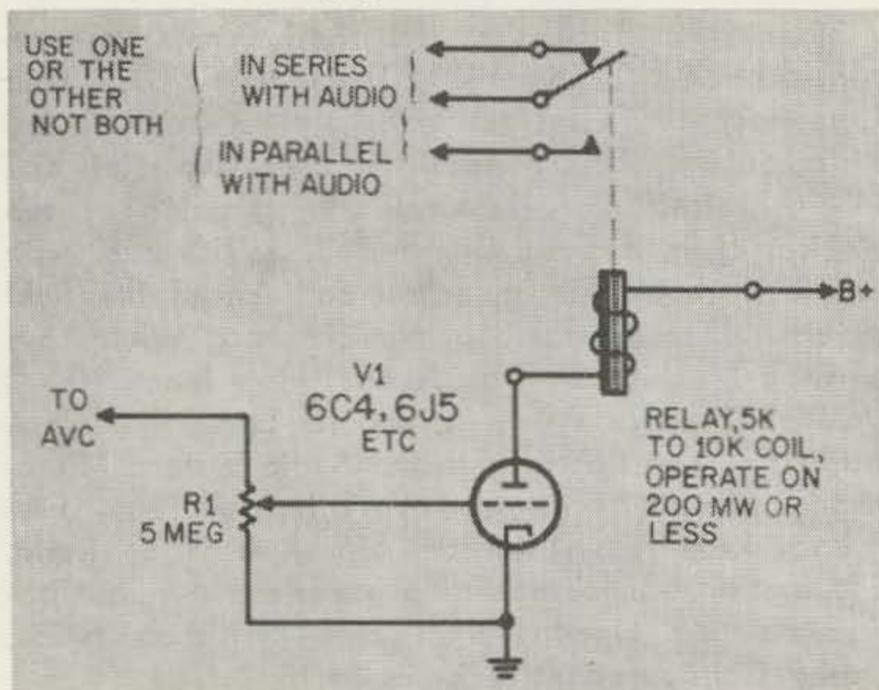


Fig. 1—Schematic Diagram of Relay-Squelch Circuit.

Fig. 2—Schematic Diagram of Shunt-Tube Squelch.

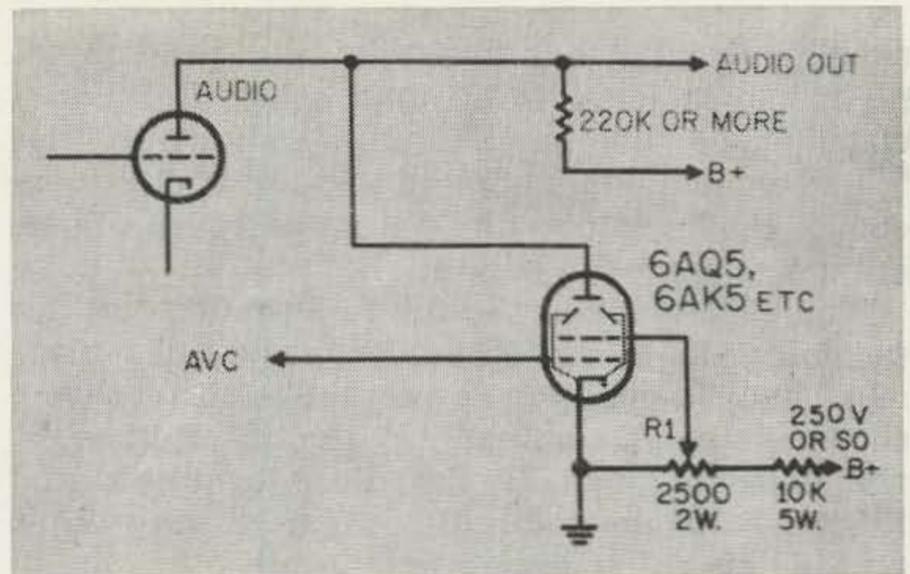

biased-detector muting, balanced-modulator quieting (the best example of which is the famed TNS), noise-operated circuits, and audio-cutoff (the basis of Western Electric's family of CODANs).

Since the relay-operated circuit is one of the best known, let's look at it first (Fig. 1). Component values shown on the schematic are all non-critical; almost any combination of junk-box parts should work well. The only requirement is that the relay operate when AVC voltage increases.

In operation, when no signal is tuned in the AVC level is at a minimum. The squelch tube (V1) draws plate current, holding the relay actuated. With arrival of a signal, AVC voltage rises. This voltage cuts V1 off, allowing the relay to drop out. The portion of AVC applied to the grid of V1 is selected by R1, the squelch-level control, allowing the operator to select the operating point of muting.

Contacts of the squelch relay can be connected to short an audio tube's grid to ground, or to open the speaker leads, as desired. Shorting the grid to ground usually results in quieter operation, but care must be taken to be sure you don't remove the tube's protective bias when you short it out.

Advantages of the relay squelch include ease of construction, inexpensiveness (when you have a well-stocked junkbox), and sureness of operation.

Disadvantages include the mechanical "plop" of the relay every time it operates, and the loading of the AVC line by R1. R1 will reduce the AVC time constant enough to prevent use of "hanging" AVC action on sideband signals. In addition, if you must purchase the relay and

can't find a suitable surplus unit, it will probably cost close to \$10 to build.

One of the least-known squelch circuits is the shunt-tube arrangement shown in Fig. 2. Like most other muting devices, it depends on AVC voltage for control—but unlike most other circuits, it requires almost no alteration of the receiver's existing circuitry. The only change necessary is substitution of a 220K ohm resistor in the first audio plate circuit if the existing resistor has a lesser value.

In operation, the squelch tube draws plate current if AVC is not present. By proper choice of tube—a 6AK5 or 6AQ5 is ideal—this drain may be made so heavy that voltage at the first-audio-tube plate drops nearly to zero. With almost no plate voltage, gain of the audio tube drops to nothing and the receiver is quiet.


When AVC arrives at the grid of the control tube, its plate current is reduced and voltage at the audio-tube plate rises because of less drop through the 220K resistor. When AVC is high enough—the amount of AVC necessary is determined by the control-tube screen voltage, set by R1—the control tube is cut off and the audio tube receives full plate voltage. Signals then pass through the audio stage.

Advantages of this circuit include the limited amount of receiver rework necessary and the low cost of parts.

Disadvantages include the necessity of providing filament power for another tube, and limited control of the squelching point (with a sharp-cutoff control tube, any AVC greater than about 5 volts will open the squelch regardless of control setting).

Biased-detector muting, one of the simpler

Fig. 3—Basic Biased-Diode Muting Circuit, Schematic Diagram.

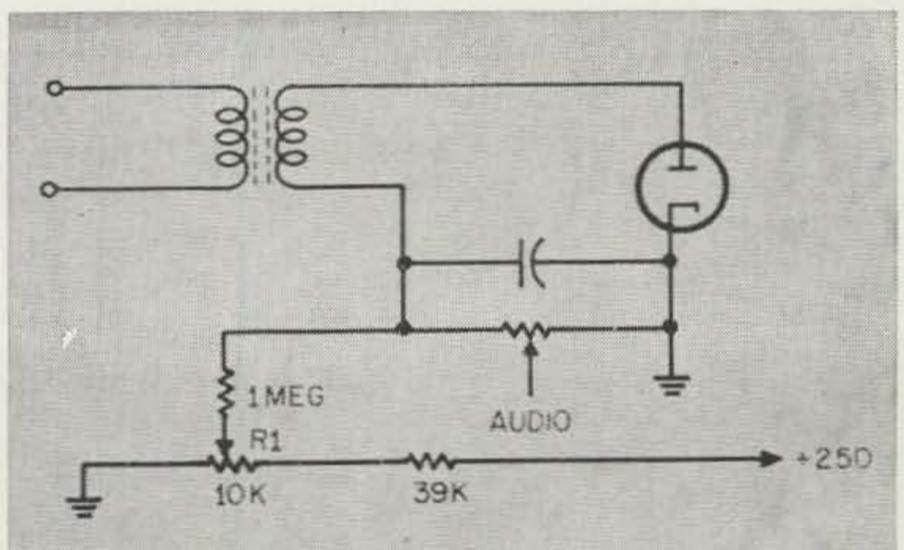

squelch circuits, has probably been the subject of more articles than any other individual circuit type. The basic circuit is shown in Fig. 3, and a more-sophisticated version which overcomes the greatest disadvantage of the basic circuit appears in Fig. 4.

The principle of operation of this circuit depends on diode switching. Whenever the plate of a diode is negative in respect to the cathode, the diode can't conduct. On the other hand, if the plate is positive the diode conducts and looks like a short circuit so far as any other applied signal is concerned.

By applying a positive voltage to the detector plate, the detector is effectively shorted and no audio (noise) can be fed to the receiver output. An incoming signal will also be shorted, until its amplitude is great enough to overcome the detector bias and drive the plate negative on peaks.

At that point, normal detector action resumes and the signal is heard. Adjustment of this critical bias point is made simply by varying the voltage applied to the detector plate with R1.

The basic circuit has only three added parts and requires only two connections to the receiver (aside from a grounding point). Cost is less than a dollar. Other advantages include an automatic delayed-AVC result (since the detector must overcome the squelch bias to develop AVC as well as audio) and a total lack of complicated adjustments.

However, the biased-diode basic circuit has a major disadvantage — distortion. Signals which are extremely strong compared to the noise will be relatively unaffected, but consider the case of a signal barely above the noise threshold. Only the peaks of the signal will open the squelch, and the resulting output signal will bear little resemblance to the original. In fact, it will be unreadable.

To overcome this disadvantage, the more-sophisticated biased-diode detector shown in Figure 4 was developed. It is adapted from a circuit described in 1943 by K. R. Sturley.

In operation, with no input signal, tubes V2 and V4 are conducting. The cathodes of V3,

V4, and V5 are all positive, and since V2's plate is positive and it is conducting, its cathode will also be positive to ground.

With V2's cathode positive, the cathode of V1 will be positive also, and the detector will be unable to operate for exactly the same reason as in the basic circuit. AVC voltage will be zero, as will audio output.

When a signal comes in, it is coupled through the capacitors to the plate of V3. V3, acting as a shunt detector rather than the conventional series type, rectifies the signal to produce a negative voltage at the top of the 25K load resistor. This voltage goes through the 470K isolation resistor to the grid of V4, increasing the tube's resistance and lowering the positive voltage on the cathode bus.

At a level determined by the setting of level control R1, the positive voltage on the cathode bus is cancelled by the fixed negative bias voltage. At any signal level greater than this, the negative bias overrides and changes the polarity of the cathode bus. At this time, V5 conducts and allows AVC voltage to pass. At the same time, V2 is cut off. With V2 cut off, the positive voltage is removed from the cathode of V1 and the detector resumes normal operation.

The distortion inherent in the basic circuit is overcome in this circuit by proper choice of RC time constants. Before all switching elements operate and allow the signal to pass, the signal must be far enough above the squelch level to be out of the distortion zone.

The relative freedom from distortion is the only advantage the circuit of Fig. 4 has over other squelches. Obvious disadvantages are the circuit complexity and the necessity for complete rebuilding of the audio detector-AVC portion of the receiver.

The balanced-modulator squelch used in the TNS circuit is shown in Fig. 5 in simplified form. For a detailed construction-type schematic of the TNS, see the references.

In operation, with no incoming signal, neither V1 nor V2 has any grid bias. Cathode bias provided by identical resistors keeps plate current within safe limits. Squelch control R1

Fig. 4—Advanced Biased-Diode Muting Circuit, Schematic Diagram.


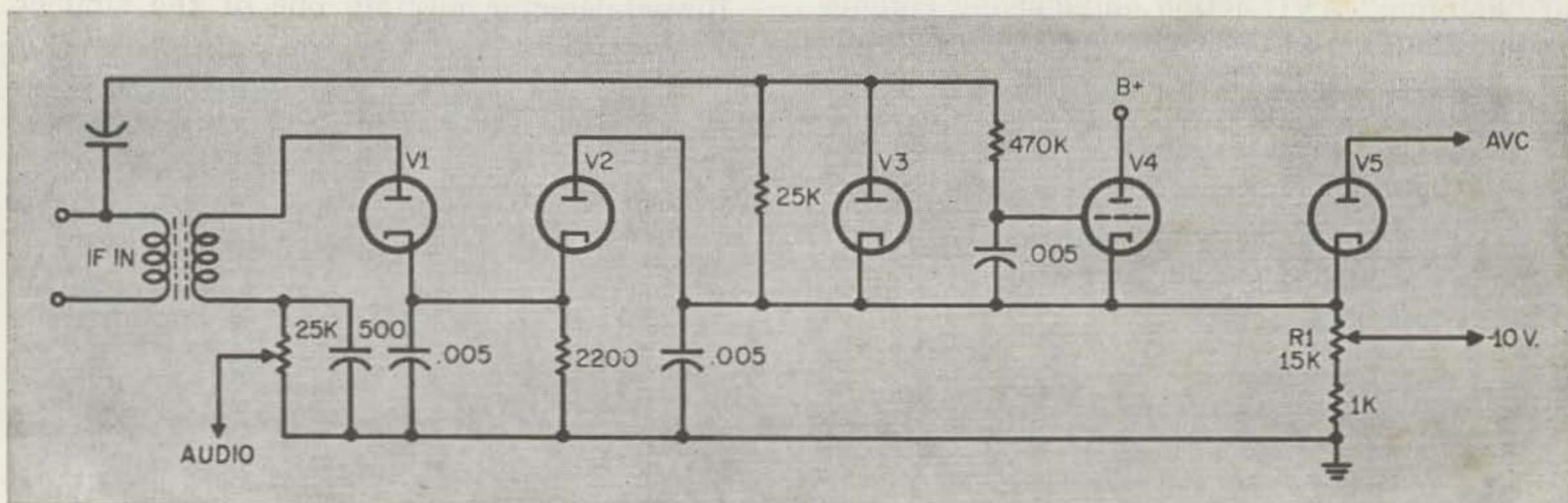


Fig. 5—Balanced-Modulator (TNS) Squelch, Simplified Schematic Diagram.

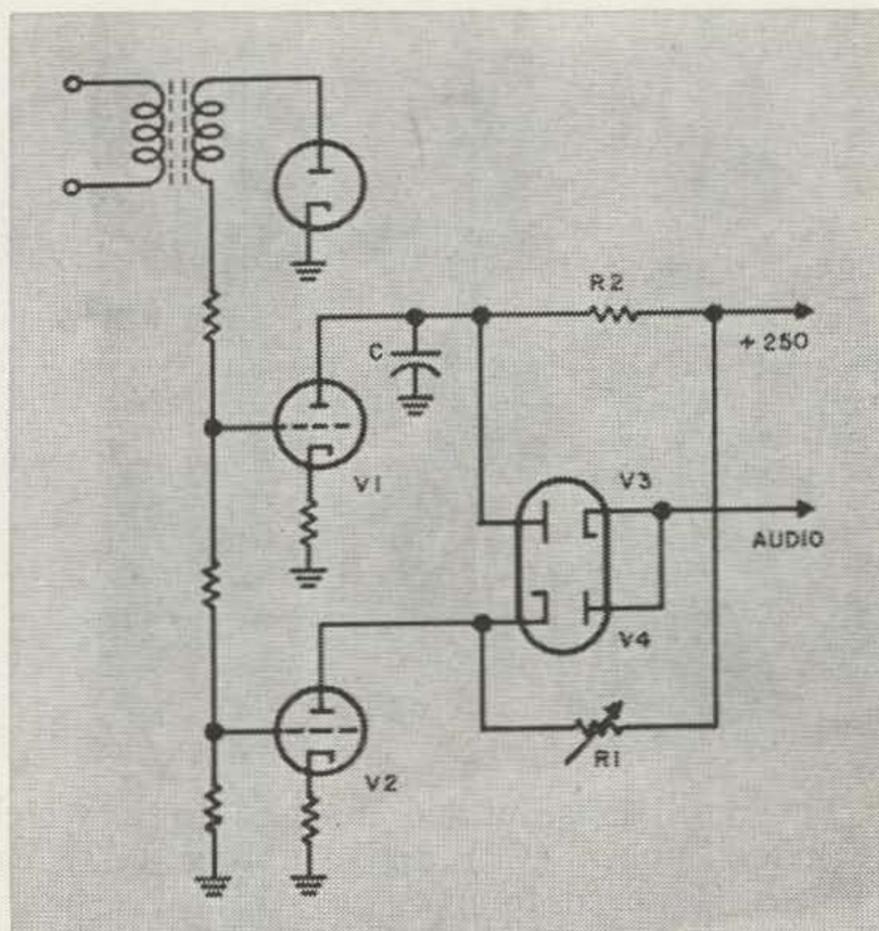

is set so that the voltage at the plate of V2 is slightly more than the voltage at the plate of V1.

Since the plates of both V1 and V2 are direct-coupled to diodes V3 and V4, this setting of the squelch control makes the cathodes of both diodes positive with respect to their plates. With the diodes not in conduction, no audio signal passes through.

With a signal coming in, the picture changes. The input voltage divider (which replaces the normal detector load resistor) is designed so that V1 receives half the AVC voltage as grid bias, while V2 gets only one-tenth.

This drives the plate of V1 positive as compared to the plate of V2, and biases V3 and V4 into conduction. Audio goes through.

Capacitor C, in conjunction with R2, perform the noise clipping. See Bill Orr's "Mobile Handbook" for a complete explanation of the TNS circuit—we're only concerned with its squelching action here.

Least-publicized of all squelch circuits, in ham literature at least, are those operated by noise. Most commercial two-way mobile gear

uses this type of squelch.


The distinguishing feature about the noise-operated squelch is the origin of its control signal. While other muting circuits depend primarily on AVC developed by an incoming carrier, the noise-operated version picks up AF noise from the detector, amplifies it, rectifies it, and uses the resulting DC as a control signal.

This works because most receivers exhibit a degree of "quieting" of background hiss with an incoming signal. With some high-quality VHF receivers, incoming signals produce an increase in background noise—and with these sets, a noise-operated squelch won't work.

Workings of the noise-operated muting circuits are explained in block-diagram form in Figure 6. A practical schematic, derived from the RCA Carfone series of commercial two-way sets, is shown in Fig. 7.

Looking at the two illustrations together, C1 and the 10-mh rf choke together comprise a 10-kc resonant circuit. This resonant circuit is the "high-pass filter" of the block diagram, picking off noise components of the detector output and feeding them to the triode section

Fig. 6—Noise - Operated Squelch, Block Diagram.

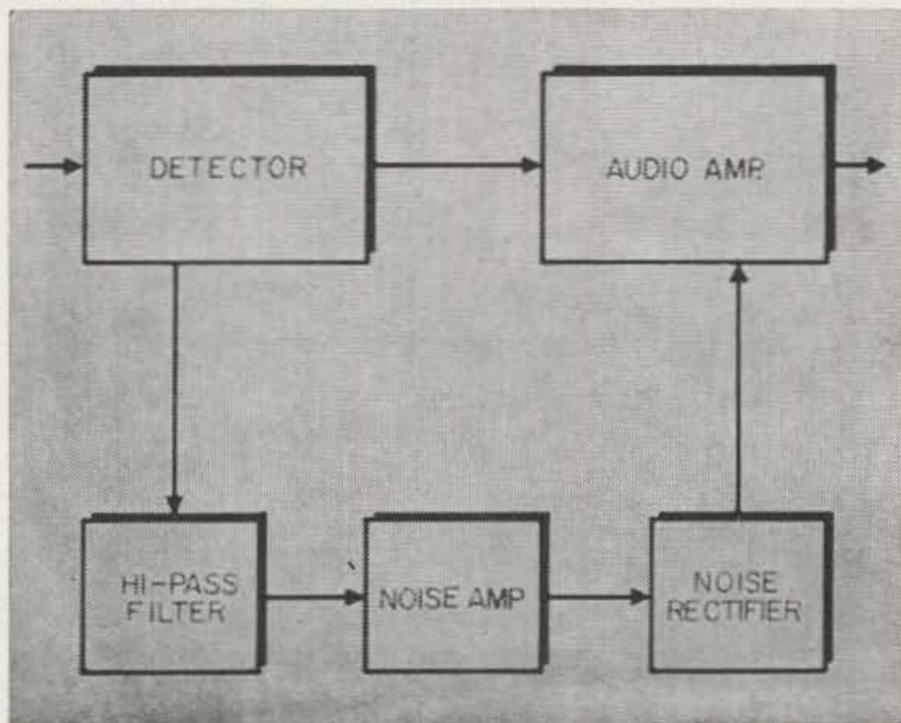

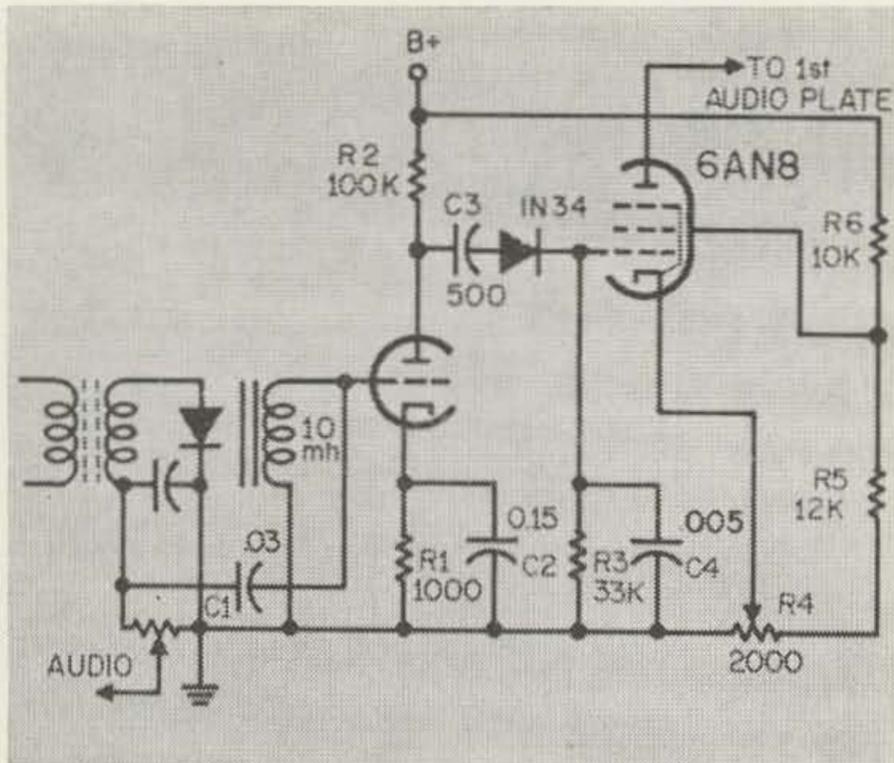


Fig. 7—Noise-Operated Squelch, Schematic Diagram.

of the 6AN8.

The noise is amplified in this stage, which includes bypass (C2) and coupling (C3) capacitors tailored to pass only high-frequency signals and to block voice-frequency output. The 1N34 rectifies this amplified noise voltage to produce a positive voltage at the top of R3, which is coupled directly to the 6AN8 pentode control grid.

This positive voltage on the grid doesn't hurt the tube, since a similar positive voltage is also applied to the cathode through R4, the squelch control (which may be remotely mounted since it carries only dc), and the voltage divider, R5 and R6.

The pentode half of the 6AN8 is the audio-control tube, operating in the same fashion as the shunt-tube squelch discussed earlier in this article.

In the absence of signal, noise is picked off and amplified. It reaches the grid of the 6AN8 pentode as previously explained. Cathode voltage on the 6AN8 will have been adjusted, via the control, to be slightly less than that on the grid. As a result, the tube conducts heavily, dropping plate voltage of the audio tube to less than a volt and cutting off all sound from the set.

When a signal appears, the noise level diminishes. This causes the voltage at the out-

put of the noise rectifier to decrease, leaving the 6AN8 pentode's control grid less positive than its cathode. The tube is cut off, plate voltage to the audio stage rises to the design value, and the set functions normally.

Advantages of this circuit which make it particularly attractive to the commercial manufacturers include its relative indifference to incoming signal strength. So long as the signal is above the noise level, it will operate the squelch—something not possible with any AVC-operated squelch. It also removes the squelch control from both high-voltage and signal-carrying circuits, allowing remote placement with no difficulty.

Disadvantages, naturally, include complexity and expense. While the entire circuit can be put together on a Vector turret socket and mounted in a small Minibox, it's still one of the most complicated of the six basic squelch circuits. With so many parts, it's more liable to failure due to the inherent perversity of inanimate objects. And troubleshooting this squelch circuit can drive the most patient technician mad, since any symptom can be caused by any component.

This brings us, naturally, to the audio-cut-off muting circuit. Developed for transoceanic telephone circuits by the Western Electric Company, it falls between the shunt-tube cir-


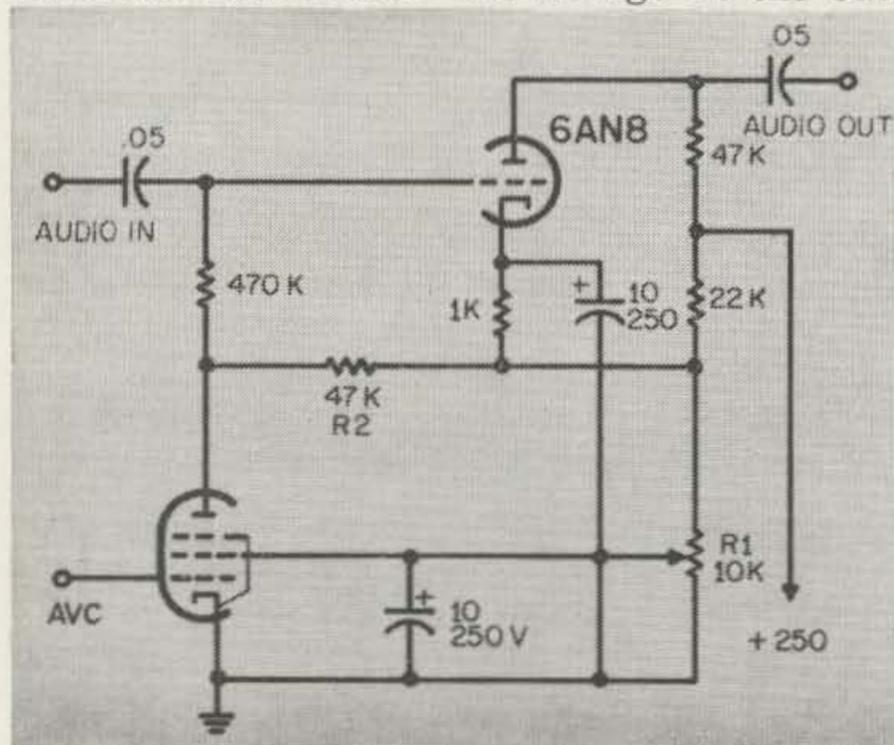


Fig. 8—Audio-Cutoff Squelch (CODAN), Schematic Diagram.

Fig. 9—Audio-Derived Control Voltage Adapter for Any Squelch Circuit, Schematic Diagram.

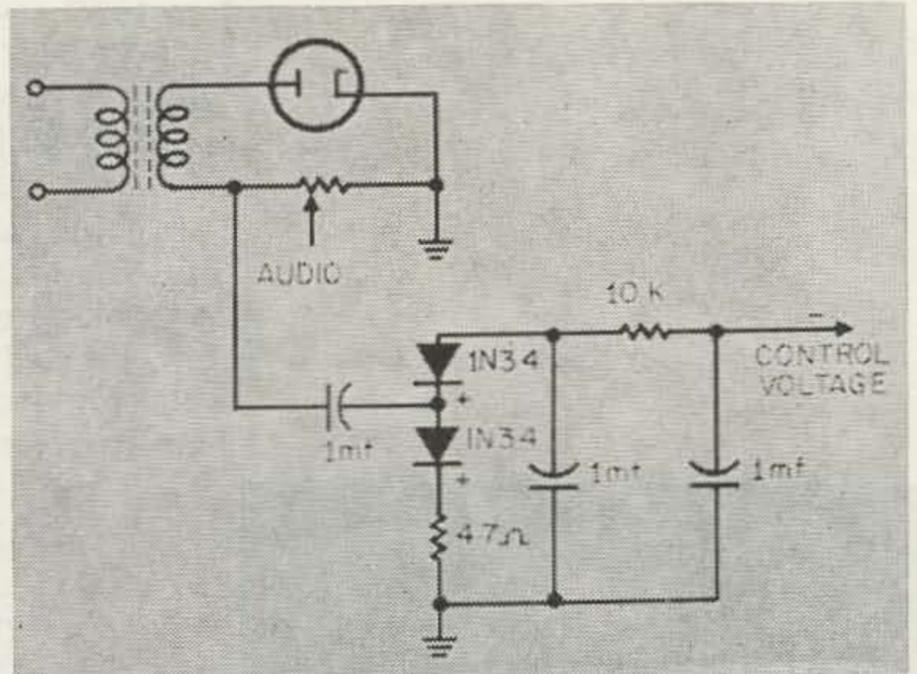

cuit and the noise-operated genre in complexity. A diagram appears in Fig. 8.

This circuit, like most others, is operated by AVC voltage. However, unlike some others it does not offer any load to the AVC bus.

In the absence of AVC, the pentode section of the 6AN8 conducts heavily. Just how heavily is determined by the setting of squelch control R1, which adjusts screen voltage and also determines the amount of negative voltage required to cut the tube off.

Plate current of the pentode section must pass through R2, which is also in the grid-cathode circuit of the triode section. The resulting voltage drop across this resistor is applied to the triode as negative grid bias, cutting the tube off and killing audio output.

When AVC is applied to the pentode, it is cut off and no plate current flows through R2. With no voltage drop, the audio tube functions normally.

Advantages of this circuit include a wider range of control in the squelching level (the CODAN can be set to operate for S7 signals but to reject those which are S6 or below) and additional audio gain, compared to other squelch circuits.

Disadvantages are its complexity as compared to shunt-tube, relay, or biased-diode muting circuits; the relatively high voltage applied to the squelch control; and the sensitivity to hum directly due to added audio gain. All parts of this circuit must be shielded, and especial care must be taken to keep the heater leads away from the audio signal path.

That completes the six basic squelch circuits—but there's still one more thing worth mentioning.

In all except the noise-operated circuit, the AVC line furnished the control signal which triggered the squelching switch. This works fine on AM or FM, but if your receiver is not equipped to use AVC on CW and sideband you won't be able to enjoy the advantages of squelch with these modes of communication.

A simple way to lick this difficulty is shown in Fig. 9. By picking audio voltage off the detector output at the top of the volume control, rectifying it in a voltage doubler, and using the negative output as control for the squelch, dependence on the AVC line is eliminated. Any audio developed at the detector will actuate the squelch, allowing it to be used with all communication modes. [7] [3]

References

Relay-Squelch Circuits:

- F. W. Mullings, W5BVF, *Squelch for any FM or AM receiver*, CQ Magazine, April, 1957, page 77.
 Sol Leise, W3LJV, *Squelch for the NC-300*, QST, March, 1958, page 31.
 D. L. Steinbach, W7FLC, *A Squelch—That Works!*, CQ, May, 1959, page 56.

Shunt-Tube Circuits:

- James Lanterman, K4GOM, *Real Easy Squelch*, CQ, April, 1958, page 33.

Biased-Diode Circuits:

- F. Langford-Smith, *Radiotron Designer's Handbook*, fourth edition, pages 1125 and 1126.
 K. R. Sturley, *Radio Receiver Design*, Chapman and Hall, London, 1943, Part 2, Chapter 12.
 H. Lukoff, W3HFT, *Squelch for 92¢*, CQ, June, 1958, page 51.

Bruce L. Mackey, *Squelch Circuit for Hallicrafters S-85*, QST, December, 1958, Hints and Kinks, page 69.

D. N. Shrader, K3CCC, *Squelch for Hallicrafters SX-99*, QST, May, 1959, Hints and Kinks, page 50.

Balanced-Modulator (TNS) (partial listing only):

- W. I. Orr, W6SAI, *Mobile Handbook*, pp. 85-91.
 W. I. Orr, W6SAI, *Radio Handbook*, 15th Edition, page 230.

Noise-Operated Squelch:

- Bob Eldridge, *2-Way Mobile Squelch Problems*, Radio & Television News, February, 1959, page 72.

Audio-Cutoff Circuit:

- American Radio Relay League, *The Radio Amateur's Handbook*.
 Langford-Smith, *op cit*, page 1127.
 F. E. Terman, *Electronic and Radio Engineering*, fourth edition.

IN 1957 two radio amateurs, John Chambers (W6NLZ) and Ralph Thomas (KH6UK), astounded the scientific world by doing the impossible. They communicated with each other over the 2500 mile path between Southern California and Hawaii on 144 mc, a line-of-sight band! Only a short decade ago, radio textbooks described this frequency as having very limited range, and actually gave a formula for computing distance. The answer was usually 25 miles, or so!

A Low Noise



You can be assured John and Ralph did not accomplish this tremendous feat using super-regen receiver or even superhets with a simple 6BQ7 cascode rf amplifier. The received signals were a small fraction of a millionth-volt (microvolt). At this level the rf amplifier stage, the antenna, and even the cosmos, gang up on the signal and try to push its head under a sea of noise. This noise is the hiss you hear on a television receiver between channels, and is the mating call of electrons in motion.

You can't do much about cosmic noise, or the antenna for that matter, but you can construct an rf amplifier which will contribute as little noise to the signal as possible. This converter incorporates such an rf amplifier. Its impressive performance is indicated by the signals received when it was tuned to the satellite frequency of 108 mc. Excellent recordings were made of the 10 milliwatt "Vanguard" transmissions when it was at the zenith of its orbit, some 23,000 miles away! Although no spectacular dx has been received on two meters, due to a poor location, the receiver noise increases considerably when the 10 element beam is turned toward the sun^{1, 2}.

Theory of Operation

The purpose of this type of converter is to *translate* signals from the transmitted frequency down to a more convenient range. Most amateurs possess a communications receiver covering 1.5 to 30.0 mc, but few have the time or inclination to construct a receiver for 2 meters. By building this low-noise converter, they can have a first class receiver with only a few hours work.

Fig. 1 is the schematic diagram of the low-noise converter. The antenna, connected to J1, is coupled to the rf amplifier grid coil (L1) through a 7-45 mmfd trimmer. This capacitor brings about an impedance match between the transmission line and tuned circuit and avoids experimenting with various tap points on L1.


The rf amplifier circuit is an offshoot of the common 6BQ7 cascode circuit found in most television tuners. However, this circuit, which was designed by W2AZL³, has many

innovations which combine to provide an extremely low noise figure (a figure of merit which determines how weak a signal can be detected). A 6BQ7 in a television tuner might have a noise figure of 7 or 8 db, when set to channel 13, since the response must be at least 6 mc wide. If the same tube and circuit was peaked on a small portion of the 2 meter band, the noise figure might drop to 5.5 db. Replacing the 6BQ7 with a lower noise tube (such as the 6AJ4 or 6AM4) would knock off another

Two Meter Converter

Lester Earnshaw ZLIAAX
Box 51
Warkworth, New Zealand

Fig. 1—Schematic diagram for the low noise two-meter converter.

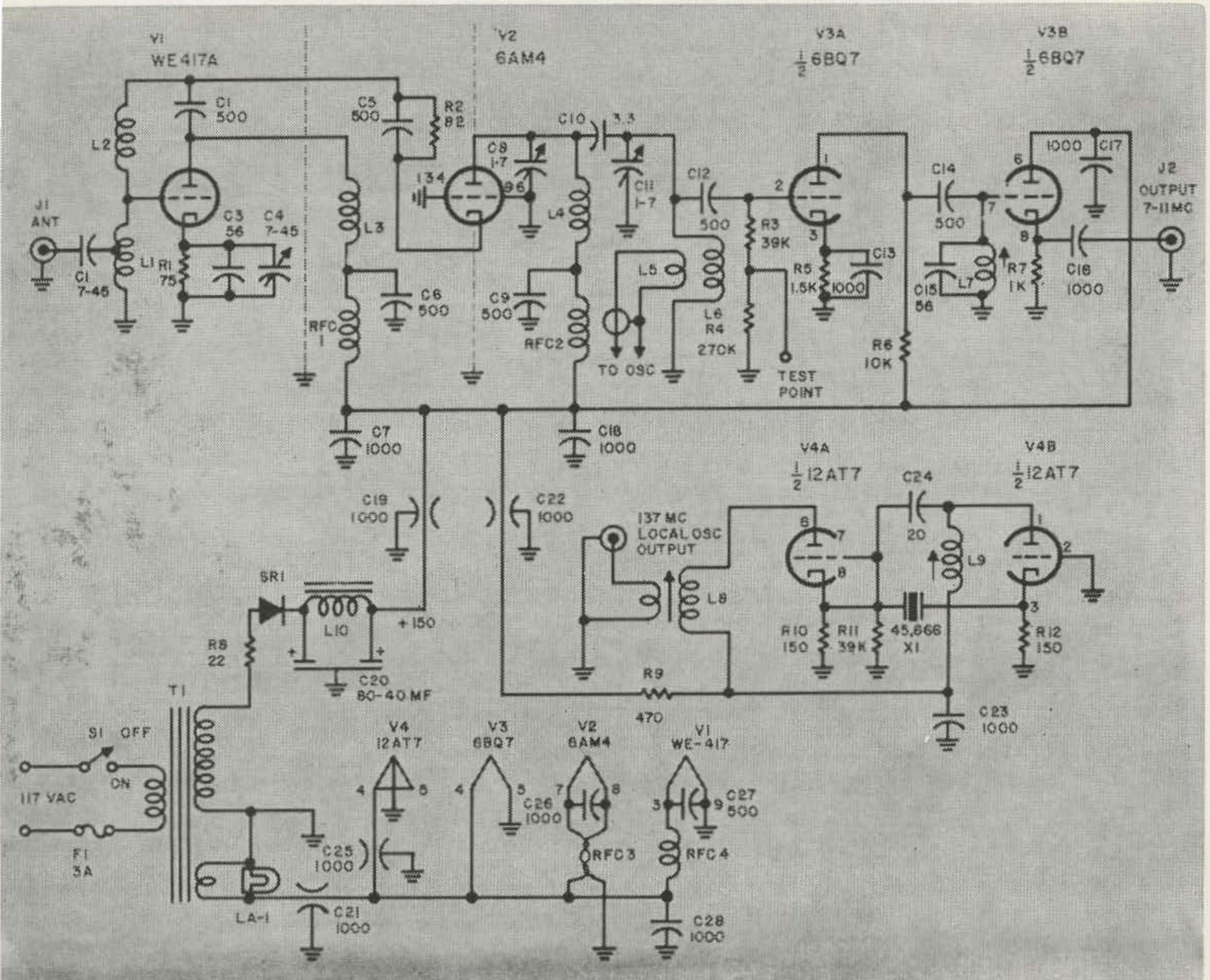

db. This circuit, incorporating a Western Electric WE417A, is capable of a noise figure which is less than 3 db! The value of reducing the noise figure below this point (with parametric amplifiers, masers, etc.) is subject to considerable debate since cosmic noise usually masks weak signals anyway.

The rf amplifier, V1, varies from the usual cascode configuration in that the anode circuit is resonated (L3) and capacitively coupled to the 2nd rf amplifier. This also permits a lower power supply voltage to be used. Ordinarily this circuit would oscillate due to the grid-plate capacity in V1. However, the addition of a neutralizing coil (L2) feeds back a small amount of out-of-phase energy to cancel the effects of tube capacity. Another "trick" which really soups up the rf amplifier is in the cathode circuit of V1, the use of a resonating capacitor (C4). Tilton has shown⁴ that series resonating the cathode inductance truly "grounds" the cathode and minimizes if degeneration. Resistor R1 biases the tube and prevents excessive plate current.

A second rf amplifier, which completes the cascode pair, is a 6AM4. Earlier it was pointed out that this tube is somewhat "noisier"

than the WE417A. However, this stage has very little effect on the noise figure and there is no advantage in using another WE417 for V2. Self bias is provided by R2 and the plate is resonant at 2 meters (L4 and C8).

The highly amplified signal is coupled to the mixer (V3a, a 6BQ7) where it combines with the oscillator energy that is link coupled to L6. A beat difference between the signals (the intermediate frequency) appears across R2 and is coupled to the cathode follower V3b. This stage has no amplification but simply provides an impedance match between the if coil (L7) and the receiver.

The Oscillator

The oscillator is a modified Butler circuit with feedback between the two low impedance cathodes. The crystal is a third overtone type and oscillates at 45.666 mc. Coil L9 is also resonant at this frequency and the energy is coupled to V4a, which triples to 137 mc. A small amount of 45 mc energy appears at the cathode of V4a (pin 8) and this rf is coupled back to the oscillator through the crystal to sustain oscillations. The local oscillator signal

Underside view of the converter showing the location of the compartments and shields. The layout in the rf amplifier section should be followed closely.

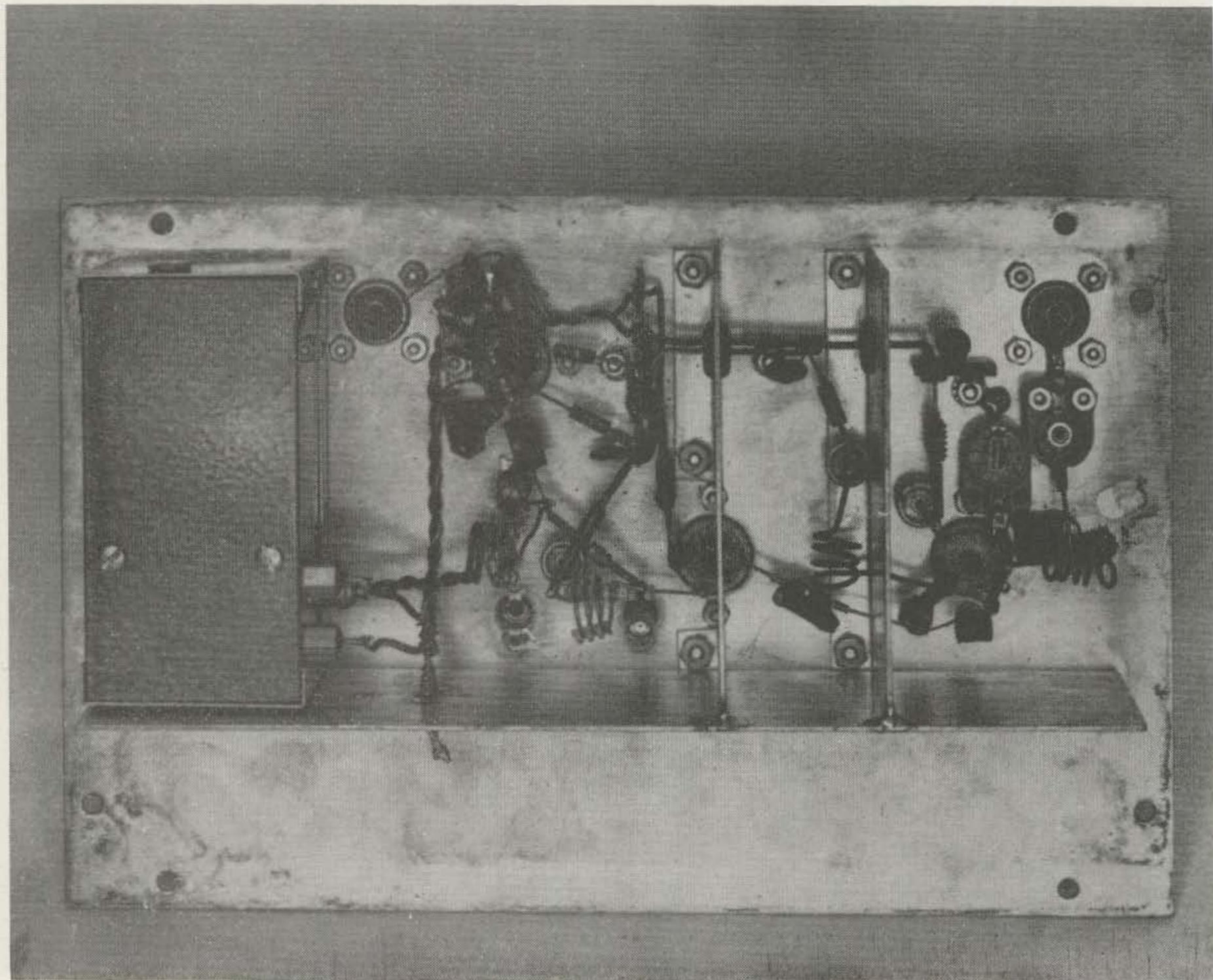


Fig. 2—Crystal and intermediate frequency chart. Note that the local oscillator injection frequency is always three times the crystal frequency and is below the signal frequency by the if.

CRYSTAL FREQUENCY	X3	PLUS IF =
45.667 mc	137.0 mc	144-148 mc
43.333 mc	130.0 mc	7-11 mc
39.333 mc	118.0 mc	14-18 mc
39.000 mc	117.0 mc	26-30 mc
38.833 mc	113.5 mc	27-31 mc
		30.5-34.5 mc

(137 mc) is coupled to the mixer from L8 to L6 through a short length of twisted hookup wire. The oscillator circuit is characterized by extremely stable operation. It either oscillates or it doesn't! There are no "half-way" oscillations where the crystal jumps frequency or pops from one mode to another. The frequency drift is also truly remarkable for such high frequency operation. The drift from a "cold start" is only a few hundred cycles. This is quite important when signals arrive intermittently due to temperature inversions. It is nice to know exactly where a station will appear when the band opens up.

The power supply is the most conventional part of the converter. It consists of a simple half-wave rectifier-filter system. An 80-40 mfd electrolytic and 5 hy filter choke provide near pure dc to the plates. An rf filter is included in the filament circuit of the WE417 to prevent undesired regeneration. A bifilar wound choke is used in the filament circuit of V2 since its cathode is at rf potential. Feedthrough capacitors (1000 mmfd) are used to feed filament voltage and B+ into the rf section and oscillator compartment. This complete shielding prevents reception of any spurious signals such as might occur if the 45.666 mc energy leaked out of the oscillator compartment. No if signals can force their way through the power supply either.

Choosing an IF

The choice of an if is not a haphazard thing. If the if is too low, images will become a problem. On the other hand, if it is too high, receiver stability may be the problem. In general, 7 to 11 mc, and 14 to 18 mc, are favored. The 14 to 18 mc range may be preferred for simply by inserting a "4" between the numbers, you can read the signal frequency (144- 148 mc) directly from the receiver dial.

Fig. 2 shows some of the common if's and how they are figured. Note that the local oscillator is always lower than the signal frequency by the amount of the if and the crystal is always one-third of the oscillator output. From this information you can easily determine a crystal frequency for any desired if. The 26- 30 mc range would be used by owners of Collins receivers which cover one and two mc bands. The 27- 31 and 30.5 - 34.5 range is useful for communications receivers which have a special calibrated scale for the two

meter band.

If the 14- 18 mc range is selected, rather than 7- 11 mc, capacitor C15 should be removed. If any of the other ranges are used, delete C15 and use only 20 turns on coil L7. The only other coils affected, in the oscillator compartment, will cover the full range and need not be modified.


Shielding

One of the success secrets of this converter is the careful use of shielding. When the circuits are isolated from each other by shields, each stage can have more gain without excessive regeneration.

A long shield bracket runs the length of the chassis to prevent stray signals in the power supply from coupling over to the rf circuits. Another shield is placed between V1 and V2. This shield also prevents coil L3 from "seeing" the input coil L1. The hot lead of L3 and the wire from C5 and R2 passes through holes in the shield. At the opposite end, the filament wire passes through a grommet in the shield. No feedthrough capacitor is required since this wire, and the B+ lead, is "stone cold".

Another shield passes through the center of the 6AM4 socket. The center post of this socket, along with pins 1, 3, 4, 6, and 9 are bent over and soldered to the shield. The remainder of the signal circuits are relatively uncritical and no shields are required. Note that all tubes are shielded except V4.

By way of contrast, the oscillator is really "buttoned up". Originally the oscillator was mounted on the chassis and capacitively coupled to the mixer. When the converter was tested, a 60 cycle buzz was heard near each end of the range (7- 11 mc). After many late hours watching the "modulated milk bottle", it was determined that these spurious signals were the picture carriers of channel 2 and 5. A little exploration with a high frequency receiver showed that the extremely strong television signals were bullying their way through the tuned circuits. In the mixer, the spurious signals were able to combine with a small amount of 45 mc (and 90 mc second harmonic) energy to produce a beat in the if range. Rewiring the oscillator and bottling it up in a box turned the trick. Even though the television signal may still force its way to the mixer, all it runs into is 137 mc. Thus any beats created are well outside the if.

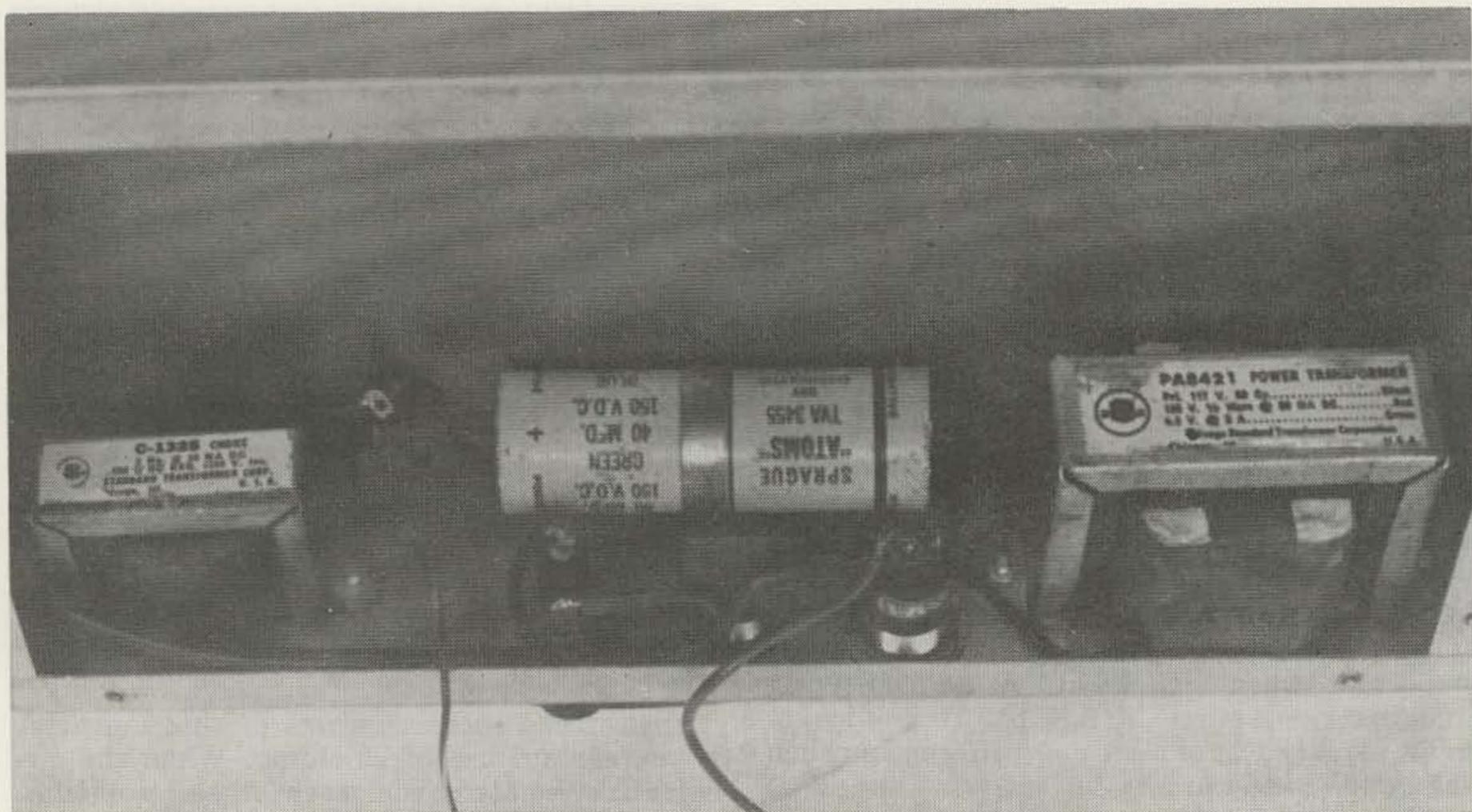

The converter power supply is built into the chassis base.

Layout

Other than the details just given, there are no particular precautions regarding layout. You may want to incorporate some ideas of your own and therefore no detailed layout drawing is included. However, a few basic facts are in order.

The converter is built on a 7" X 11" plate which is mounted on the 7" X 11" X 2" aluminum chassis. The chassis serves to enclose the rf circuits in addition to providing a foundation for the power supply. Although it may be "gilding the lily", the chassis and all shield plates were silver plated.

Some constructors may wish to include the power supply on the plate rather than the chassis. This would make the construction somewhat easier and should not create any particular problems other than layout of components.

In the 1st rf compartment (V1) you will find C1, C2, C3, C4, C27, and C28, coils L1, L2, and RFC 4, along with resistor R1. In between shield plates the following components are located: L3, RFC 1, C5, C6, C7, and R1. Note that C6, C9, and C27 are button stand-off capacitors and serve as tie points for the associated components. Coil L4 is supported by its leads between C8 and C9. One end of L6 is soldered to the chassis and the other end is supported by the terminal on C11. The test point jack serves as a tie point for R3 and R4. Resistors R6, R7, and capacitor C17 are located between the tube socket and the adjacent terminal strip.

The oscillator circuitry is contained in a 2 1/4" X 2 1/4" X 4" chassis box and includes the

following components; C22, C23, C24, L8, L9, R9, R10, R11, R12, crystal X1 and socket, and the tube. No terminal strips are required.


When wiring the converter be sure to keep the leads as short as possible, particularly around the rf amplifier. The same is true for the coils. Other than the slug-adjusted coils, they should be self-supporting with short leads. Two lug terminal strips are used in the rf compartments, and a five lug strip between the 2nd rf and mixer stages provides a tie point for the filament and B+ circuits in that area.

Alignment

If you do a good job of wiring the converter, and are lucky with the setting of the local oscillator coils, the converter will probably work without any tuning whatsoever. However, don't expect to obtain a noise figure less than 3 db without a certain amount of "fiddling". You should be able to obtain a noise figure around 5 db with an "ear alignment". To tune the converter for minimum noise you will need a noise generator to adjust the rf amplifier⁵.

Start the alignment by setting the oscillator coils to approximately 45 mc (L9) and 137 mc (L8). Have all circuits energized to load the power supply. The oscillator compartment should hang by its leads and be grounded to the chassis with a short wire. With a grid dip meter, preset the coils to their correct resonant frequency. Then turn the dip meter plate switch off (making an absorption wavemeter out of it) and adjust L9 for an indication of rf. Turn the power supply on and off a few

Fig. 3—Schematic diagram for a simple noise generator, useful in adjusting the low noise converter. The potentiometer is set so the noise approximately doubles when the switch is turned on. Then simply turn the generator on and off and adjust the converter turned circuits for the greatest increase in noise when the generator is switched on.

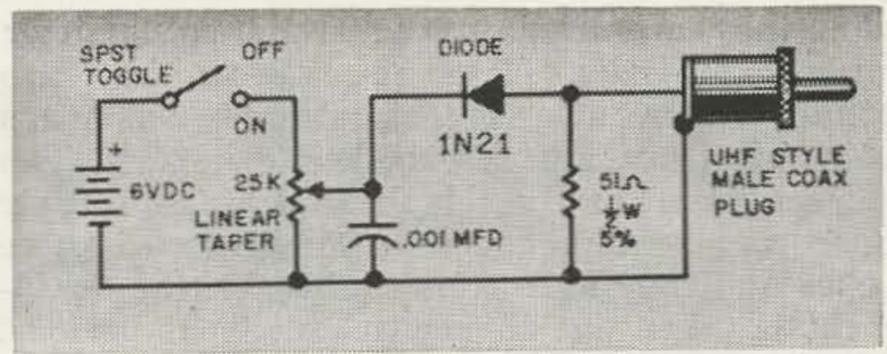

times to make sure the oscillator starts easily. Next move the dipper to the link (external to the box) and adjust both coils (L8 and L9) for maximum rf consistent with stable operation.

Now, install the oscillator box on the chassis plate and tightly couple the link to L6. If you like, you can again set the oscillator coils by adjusting them for maximum voltage at the test point jack. It is likely that enclosing the coils (by covering the box) may detune them slightly. Connect the converter to a receiver and 2 meter antenna. Peak coil L7 for maximum "hiss" at the center of the band. Then adjust C8 for maximum at the low end and the same for C11 at the high end.

The setting of C1, C4, and the inductance of L1, L2, and L3 will affect the noise figure and are given in the order of importance. Tune in a very weak unmodulated signal and adjust the above five components for the best signal, consistent with minimum noise. It should be stressed that the point of maximum signal strength will not be the proper setting for the best signal-to-noise ratio, or produce the lowest noise figure. By using a "tuning wand" (brass core at one end, powdered iron at the other) check the inductance of each coil. If the


brass core improves the noise figure, spread the turns. If the iron core brings about an improvement, compress the turns. The tap point on L1 probably will not require adjustment. However, if the noise figure seems to be best with maximum C1 capacity, move the tap one-half turn toward the "hot" end. Of course the opposite is true for minimum capacity.

To obtain a noise figure which is less than 3 db, you will require a noise generator such as the one shown in Fig. 3. Although this device cannot measure the noise figure, it will tell you when you have arrived at minimum. Its operation is just as simple as the circuit. Connect a dc voltmeter across the diode load in the receiver. Then adjust the noise figure determining components in the rf amplifier for a maximum increase in noise each time the generator is switched on. You will find that each adjustment goes through a minimum and this, of course, is the correct setting.

Obtaining the WE417A

The rf amplifier tube, a WE417A, is made by Western Electric and is not available through regular distribution channels. If you know someone who works at a television sta-

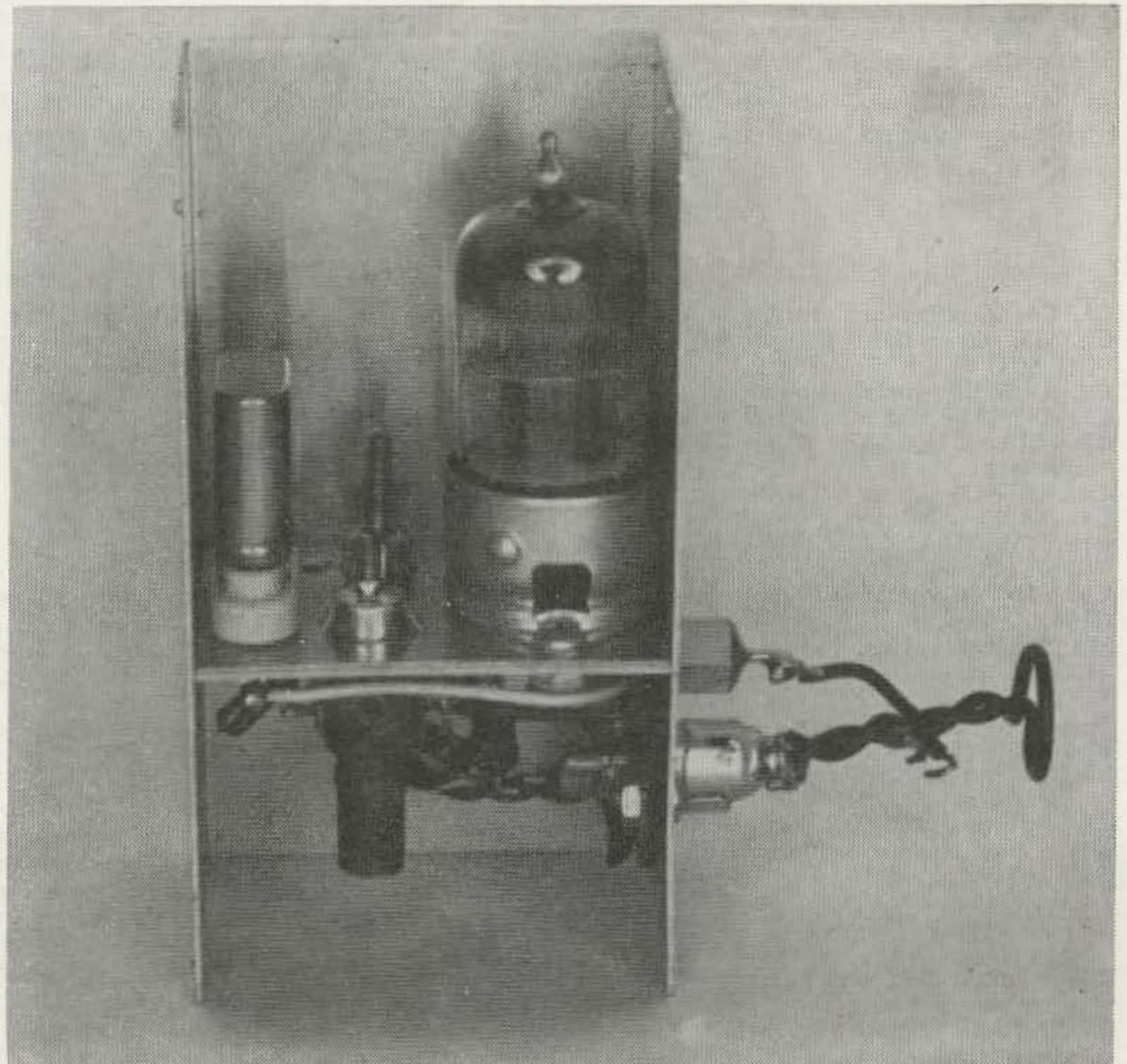Location of the components inside the oscillator compartment.



tion, they are used in the studio-transmitter microwave links. As a precaution they are usually retired after a certain number of hours of service, but are in excellent condition. The same is true for the telephone company. Their microwave equipment uses hundreds of these tubes and they are often "pulled" if the equipment is taken out of service for short periods. Wholesale tube suppliers, such as Barry, TAB, and JSH Sales, have the WE417A at very reasonable prices. If you prefer to purchase one directly from Western Electric they are available at Graybar Distributors (listed in the phone book) for approximately \$15.00. Don't shudder, fellows, this jug makes the difference between the men converters and the boy converters, so to speak.

Using the Converter

For best performance the converter should be used in conjunction with a very stable receiver. The sensitivity is not particularly important for the converter has a considerable amount of gain even without an if amplifier. On voice, a bandwidth of 2.5 kilocycles is optimum, while something less than 500 cycles is preferred on CW. An additional consideration is the tuning ratio. A station 3.5 kc wide does not take much room on a dial which covers 10 or more megacycles.

The WE417 is allergic to strong rf fields. The rf energy which leaks through an open antenna relay *could* wipe out the delicate grid in the twinkling of an eye, if the transmitter power is high enough. Some form of protection must be included in the converter connections. The most satisfactory system is to incorporate a second antenna relay in series with the converter input. When the main relay switches the antenna from the converter to the transmitter,

a second relay disconnects the converter input from the antenna relay and grounds it.

Earlier it was stated the converter was used on the 108 mc satellite frequency. An extra set of coils were wound up which can be interchanged with the two meter coils in about 5 minutes. Although bandchange switches are impractical at this frequency the conversion from one band to the other is quite simple. Builders who would like to use the converter on 108 mc, in addition to two meters, should make the following changes:

- L1—4 turns, #16, $\frac{3}{8}$ " diameter, center-tapped
- L2—20 turns, #24 enam., closewound, $\frac{1}{4}$ " diameter
- L3—6 turns, #16, $\frac{3}{8}$ " diameter
- L4—same as L3, but 5 turns
- L5—same as for 144 mc
- L6—same as L3, but 4 turns
- L7—same as for 144 mc, but remove C15
- L8, L9—same as for 144 mc
- X1—45.667 mc, if 29.0 mc

For simplicity, and ease of changing from 144 to 108 mc, the same 45.667 mc crystal is used on both bands. On two meters the local oscillator is 7 mc below the low end of the band. When the 108 mc coils are substituted, the oscillator is then 29 mc above the satellite frequency.

References

1. Cottony and Johler, "Cosmic Radio Noise Intensities in the VHF Band," Proc. IRE, Sept., 1952, p. 1053.
2. Bray and Kirchner, "Antenna Patterns from the Sun," QST, July, 1960, p. 11.
3. Southworth, "A Low-Noise 108/144 mc Converter," QST, Nov., 1956, p. 11.
4. Tilton, "Hints on Lowering Noise Figures," QST, Nov., 1953, p. 65.

Reference 3 lists additional reading for those interested in noise with respect to high frequency equipment.

PARTS LIST

C1, C4- 7- 45 mmfd. rotary trimmer (Centralab type 822)
 C2, C5, C12, C14- 500 mmfd tubular ceramic (Centralab D6-501)
 C3, C15- 56 mmfd tubular ceramic (Centralab D6-560)
 C6, C9, C27- 500 mmfd button standoff (Centralab type ZA)
 C7 C13, C16, C17, C18, C23, C26, C28- .001 mfd disc ceramic
 C8, C11- 1- 7 mmfd piston trimmer (Centralab 829-7)
 C10- 3.3 mmfd disc ceramic
 C19, C21, C22, C25- .001 mfd feedthrough capacitor (Centralab type FT)
 C20- 80- 40 mfd, 150 volt electrolytic (Sprague TVA 3455)
 C24- 20 mmfd disc ceramic
 F1- 3 ampere fuse (Littlefuse 3AG)
 J1, J2- UHF style antenna connector (amphenol 50-239)
 L1- 5 turns, #16, $\frac{1}{4}$ " diameter, spaced two-times wire size, centertapped.
 L2- 15 turns, #24 enam., $\frac{1}{4}$ " diameter, closewound
 L3- $3\frac{1}{2}$ turns, #16 enam., $\frac{3}{8}$ " diameter, spaced two-times wire size
 L4- 4 turns #18, $\frac{1}{2}$ " diameter, spaced two-times wire size
 L5- 1 turn hookup wire line, at cold end of L6 (see photo)
 L6- $2\frac{1}{2}$ turns, #18, $\frac{1}{2}$ " diameter, spaced two times wire size
 L7- 35 turns, #38 enam., scramble wound on $\frac{1}{4}$ " diameter slug tuned form (see text)
 L8- 4 turns, #28 enam., spaced two-times wire size on $\frac{1}{4}$ " slug tuned form. One turn link of #28 wire
 L9- 7 turns, #28 enam., closewound on $\frac{1}{4}$ " diameter slug tuned form

L10- Choke, 5 hy., 50 ma (Stancor C1325)
 LA1- #47 pilot lamp and holder
 R1- 75 ohms, 5%
 R2- 82 ohms, 5%
 R3, R11- 39K
 R4- 270K
 R5- 1.5K
 R6- 10K

All resistors $\frac{1}{2}$ watt, unless noted otherwise

R7- 1K
 R8- 22 ohms, 2 watts
 R9- 470 ohms
 R10, R12- 150 ohms
 RFC1, 2- 30 turns, #30 enam. closewound on 1 meg., $\frac{1}{2}$ watt resistor
 RFC3- 15 bifilar turns wound on two 1 meg., $\frac{1}{2}$ watt resistors
 RFC4- 7 turns, #16 wound on 1 meg., $\frac{1}{2}$ watt resistor, spaced diameter of wire
 S1- SPST toggle switch
 SRI- 50 ma. selenium rectifier
 T1- power transformer, 125 volts, 50 ma., and 6.3 volts at 2 amperes (Stancor PA8421)
 V1- WE417 (Western Electric)
 V2- 6AM4 (General Electric)
 V3- 6BQ7
 V4- 12AT7
 X1- Third overtone crystal (International FA-5, see text)

NOW ALL YOUR POWWOWS
CAN BE PRIVATE WHEN EVERYONE
IN THE WIGWAM KNOWS YOU'RE...



ON THE AIR

WITH A *COMANCHE*

CONTROLLED ILLUMINATION SIGN

- HEAVY GAUGE STEEL CASE
- BRIGHT RED LETTERS ON WHITE
- BLACK OR GRAY BAKED FINISH
- WALL OR TABLE MOUNTING
- AC-DC 6-12-120V (SPECIFY)

● JUST RIGHT FOR YOUR SHACK ●



TO INSTALL SIMPLY CONNECT LEADS TO THE
COIL OF YOUR ANTENNA CHANGEOVER RE-
LAY. WHEN YOU "FLIP" TO TRANSMIT YOU
ARE ON THE AIR.

ONLY
6⁹⁵
NET



AVAILABLE
IN OTHER
LANGUAGES

7.95
NET

COMANCHE PRODUCTS
STELLAR ELECTRONIC
BOX 82
GARLAND, TEXAS

WHO IS MY
NEAREST DISTRIBUTOR?

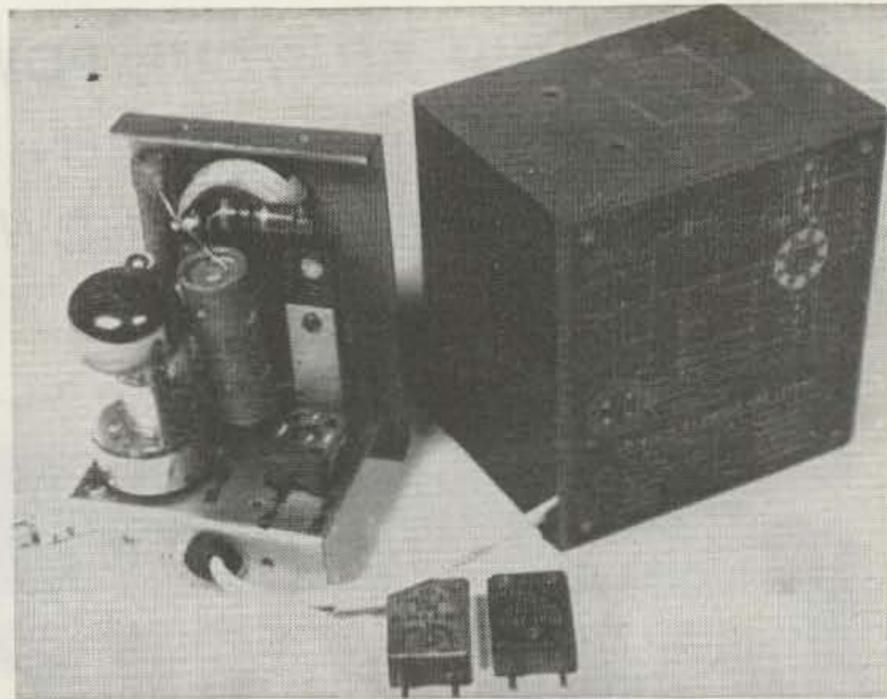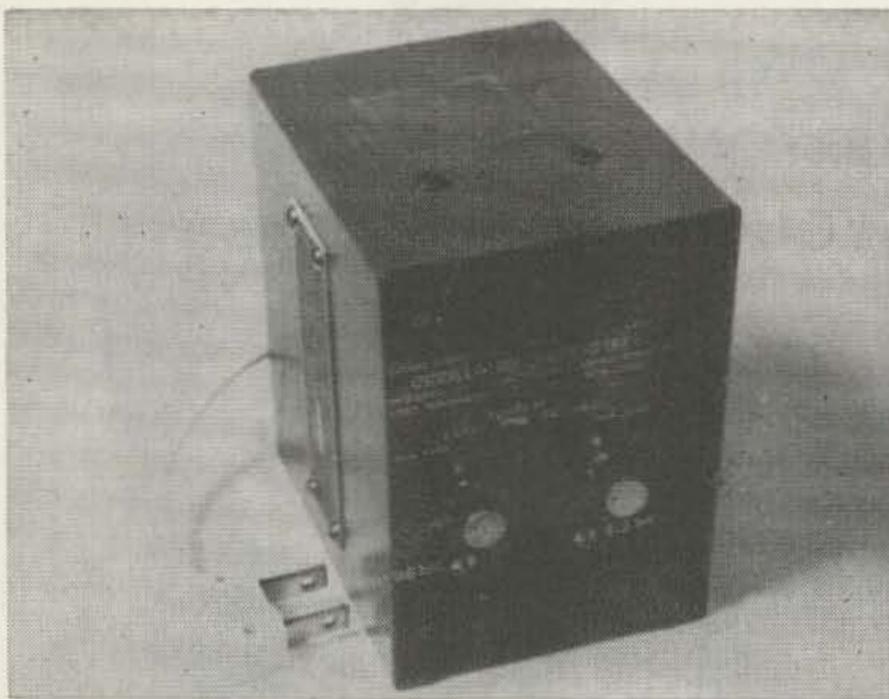NAME _____ CALL _____
ADDRESS _____ STATE _____



Surplus Frequency Standard

Roy E. Pafenberg
P.O. Box 844
Fort Clayton, Canal Zone


EXISTING PARTS

- R1—150 Ω Variable Resistor
- R2—1000 Ω $\frac{1}{2}$ Watt
- R3—5000 Ω $\frac{1}{2}$ Watt
- C1—.0025 mfd. Mica
- C2—.001 mfd. Mica
- C3—.001 mfd. Mica
- S1—D.P.D.T. Slide Switch
- S2—S.P.S.T. Switch, ganged to R1
- X1—4.3 mc. Crystal

- X2—2.88 mc. Crystal
- AFC—1.2 MH
- VT-185—3R6/1299

NEW PARTS

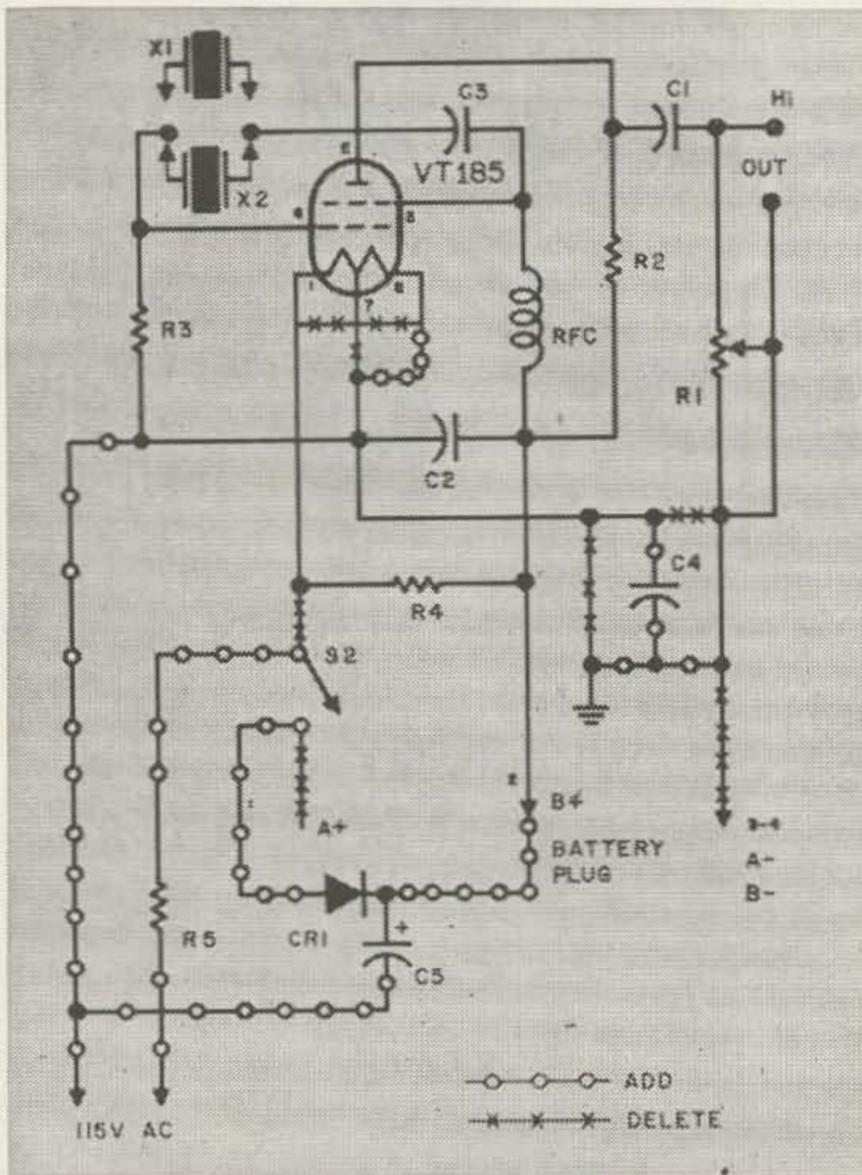- C4—.01 mfd. Mica
 - C5—20 mfd. 150V
 - CR1—Sarkes-Tarzian M-150 Silicon Rectifier
 - R4—10 Ω $\frac{1}{2}$ Watt
 - R5—1100 Ω 20 Watt.
- See text.



AN APPEALING little item of surplus, still in a fairly common supply, is the VO-4 Oscillator. The unit is a compact, battery operated, dual frequency, crystal controlled signal generator. The original application of the instrument was as a signal source for use in the alignment of the 2880 and 4300 kc if circuits of the SCR-510 and SCR-610 series of field radio sets.

While crystals for the above frequencies are supplied, the circuit works nicely with crystals from 1 to 12 mc. The simplicity and utility of the unit as a 1 mc standard or as a band edge marker, makes conversion to ac worthwhile.

Fig. 1 shows the schematic of the unit as supplied, with the necessary changes and ac power supply. The slightly unorthodox wiring of the power supply permits best utilization of component terminals as tie points. The other changes lift the circuit from chassis ground and series the filament sections of the 3D6/1299 tube.


The photographs show the mechanical details of the conversion. The crystals and the silicon rectifier were removed for clarity in the photograph. The battery cable is removed and the ac cord secured with a Heyco strain relief bushing. The bracket for the crystal retaining spring is drilled to mount the Sarkes-Tarzian M-500 or M-150 silicon rectifier. The required filament dropping resistor, in the authors version, consisted of a 1000 ohm, 10 watt adjustable resistor, mounted in an existing hole, in series with a 750 ohm, 10 watt, fixed resistor. Any combination that results in approximately 1100 ohms at between 15 and 20 watts will be satisfactory.

All in all, the compact construction and versatility of this crystal controlled signal source make it a desirable project for any ham shack.



NEW! A PRE-ENGINEERED HAM EQUIPMENT CENTER WITH BUILT-IN POWER & COMMUNICATION FACILITIES

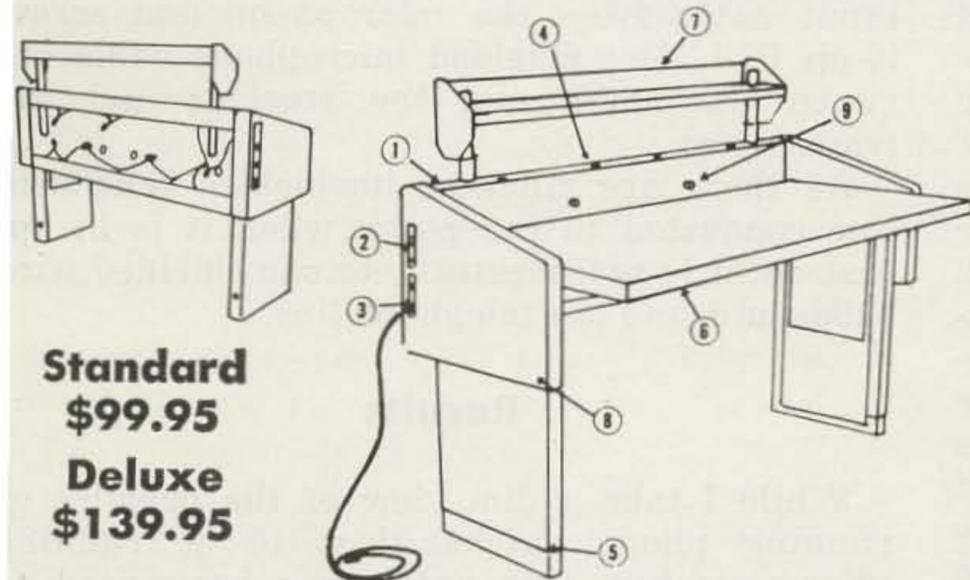Bring the ham center up out of the cellar—let the whole family share in the fascinating world opened up by global communications. The handsome styling of this functional unit fits well in any decor—neatly organizes equipment and cables.



Standard
\$99.95
Deluxe
\$139.95

DELUXE STATION FACILITY . . . complete with formica top, vinyl trimmed ends, shelf and all electrical and mechanical features listed above. Approx. shipping weight 190 lbs. F.O.B. BROCKTON, MASS.
Part number 5203-2DSFA AMATEUR NET only \$139.95.
STANDARD STATION FACILITY OR WORK BENCH . . . complete with standard steel ends, masonite top, and all applicable features as described above. Approx. shipping weight 160 lbs. F.O.B. BROCKTON, MASS.
Part number 5203-2SSFA AMATEUR NET only \$99.95.
Order direct from factory or write to customer department for additional information.

OUTSTANDING FEATURES—

1. **UNIQUE** power channel safely encloses all inter-connecting wiring, relays, etc. Eliminates "rat's-nest" behind equipment. Room for built-in power supply, filter network, etc.
2. **CONVENIENT** "big switch" with indicating fuse-holder and neon pilot light—additional individually controlled and fused circuit switches may be added.
3. **THREE** wire detachable line cord brings in all power—insures proper grounding.
4. **POWER** channel has eight 110-volt outlets—4 above top and 4 below top—with grounding contact—eliminates makeshift outlet strips or adapters.
5. **COMFORTABLE** operating position—legs are adjustable to suit your individual needs—casters may be added for portability.
6. **MASSIVE** 1 $\frac{3}{4}$ " thick top 26" x 60" provides ample room for transmitter, receiver, VFO, amplifier, etc. Deluxe top is white formica—standard is masonite.
7. **ADJUSTABLE** shelf, standard on deluxe model, holds test, monitoring or other equipment convenient to operator.
8. **END** panel covers removable—provide additional storage area for tools, tubes, etc.
9. **DELUXE** model equipped with 3 SO-239 RF antenna lead connectors.
10. **EASILY** assembled with $\frac{1}{2}$ " wrench and screwdriver—all screws removable with coin.
11. **PLEASING** appearance will appeal to XYL. Deluxe—two tone gray—gleaming white formica top—vinyl trimmed ends. Standard—gray with brown masonite top.
12. **HEAVY** gauge bonderized steel construction with baked enamel finish, will last a lifetime.

ALDEN PRODUCTS COMPANY
BROCKTON, MASS.

Additional accessories will be available soon—watch for advertisement. Specs. and prices subject to change without notice.




THE MULTIPHASE MODEL MM-2 RF ANALYZER

- Monitors the RECEIVED and TRANSMITTED signals. Shows flat-topping, overmodulation, parasitics, keyed wave shape etc. Silent electronic switching keyed by transmitted RF.
- No tuning required. Broadband response flat 1 MC to 55 MC at power levels of 5 watts to 5 KW.
- New variable sweep control for transmit and receive.
- RF attenuator controls height of pattern. Calibrated in 3 DB steps.
- Function selector for ENVELOPE, TRAPEZOID and BOW-TIE patterns on transmit. For SSB, DSB, AM and CW.
- Built-in 1 KC audio oscillator, less than 0.5% distortion. With 3" scope, is ideal for complete alignment of SSB excitors.
- For use in series with 52-72 ohm coax lines. A short pickup antenna may be used with other systems.
- Plug-in adaptors available to match 50 KC, 60 KC, 80 KC or 455 KC receiver IF systems. Only one simple connection to receiver.

MM-2 Kit ... (less IF adaptor). \$119.50
 Wired ... (less IF adaptor). \$149.50
 Plug-in IF adaptors (wired only)
 RM-50 (50 KC), RM-80 (60-80 KC),
 RM-455 (450-500 KC)... ea. ... \$12.50

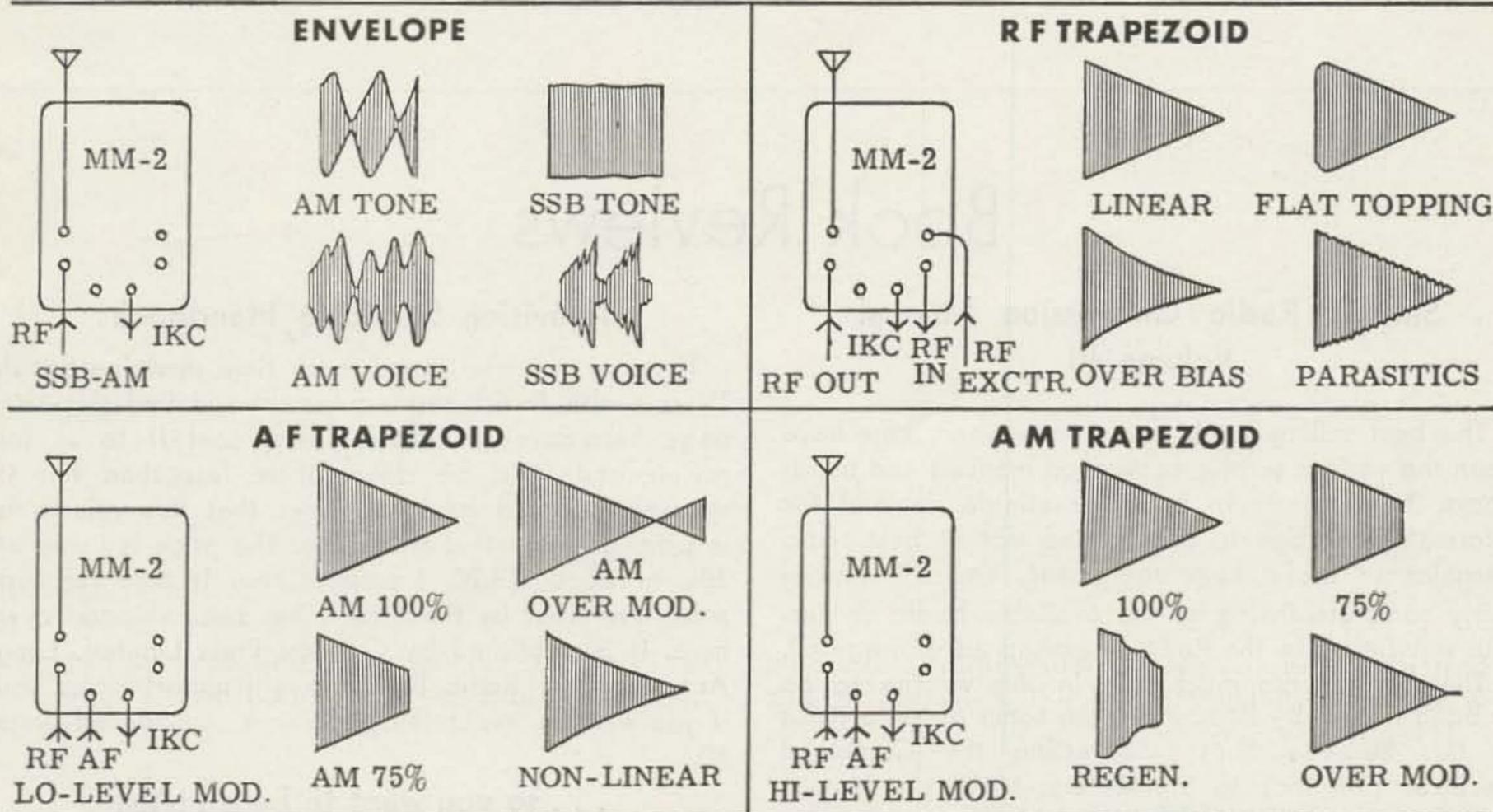THERE IS NO SUBSTITUTE FOR A SCOPE IF YOU WANT THE CLEANEST, MOST PERFECTLY MODULATED SIGNAL YOUR TRANSMITTER CAN PROVIDE. THE MM-2 IS BY FAR THE MOST DEPENDABLE and EASIEST TO USE, SINCE IT WAS DESIGNED STRICTLY FOR THIS PURPOSE.



OTHER FINE C.E. PRODUCTS

Model 100V....	New 100 Watt Broad-Band Exciter-Transmitter ..	\$795.00
Model 600L....	Broad-Band Linear Amplifier	\$495.00
* Model 20A	Bandswitching SSB Exciter	\$299.50
* Model 10B	Multiband SSB Exciter	\$193.50
* Model GC-1 ...	Gated-Compression Amplifier	\$ 66.50
* Model B	Sideband Slicer with Q Multiplier	\$104.50

* Also available in kit form
 AND MANY OTHERS ... WRITE FOR LITERATURE

**THE
SSB
PIONEER**



Central Electronics, Inc.

1247 W. Belmont Ave.

Chicago 13, Illinois

A subsidiary of Zenith Radio Corp.

New Tube Base Coil Forms

Fort Clayton



Photo credit: Jim Gardner

THE use of tube bases for plug-in coil forms is probably as old as the vacuum tube.

In an effort to make certain tube types more reliable in rough service applications, shock mounting tube bases have been developed. Shown are two representative tubes with bases that make excellent coil forms. The OC3W voltage regulator tube has a mica filled phenolic base $1\frac{1}{2}$ " in diameter and a usable winding length of $1\frac{3}{4}$ ". The 5R4WGA has a similar insulating base, slightly over 2" in diameter, with a winding area of $1\frac{3}{8}$ ".

While the use of these "no cost" coil forms will not obsolete band switching transmitters and receivers, they do add to the range of available coil form materials.

Book Reviews

Surplus Radio Conversion Manual Volume III

The best selling books for several years now have been the various surplus conversion manuals and handbooks. There seems to be an insatiable demand for information on how to convert the world's best radio bargains to useful ham equipment. You will find a fairly complete listing of the available books on surplus equipment in the Radio Bookshop ad on page 60.

There is far too much info in this volume to go through it item by item. Here are some of the articles in this 88-page book: Converting the Command Receiver (3-6 mc) to Six Meters; Making a Novice Receiver for 40 and 80 Meters from the 3-6 mc Command Receiver; A Plug-in Power Supply for Your Command Receiver; Converting the Q-5'er (BC-453) for Broadcast Reception; A Noise Limiter for Your Command Set; AVC for Your Command Set; Double-Conversion Command Receiver for SSB Reception; Converting the BC-455 for 20-15-10 Meters and Citizens Band; Hopping Up the Command Receiver; Converting the BC-603 to a 10-15-11 Meter AM/FM Receiver; Plus articles on the APN-1, CRC-7, URC-4, MD-7, RM-52/53, 701A tube, ARC-5 transmitters, BC-1253 transmitter, BC-1066, APN-4, MBF, R-28, ARC-4, SCR-522, BC-312, BC-342, BC-348, BC-375 & 191, ART-13, LM. There are schematics of many other surplus items in additions. The book is edited by Bill Orr W6SAI.

All this for only \$2.50. It's a good deal.

Television Servicing Handbook

Those of you who spend much time servicing British TV sets with British test equipment will find this 280-page hard-cover invaluable. They sent it to us for review and we'd be doing them less than fair if we were to hold back the news that this volume is in print and is rather well done. The price is listed at 30s, or about \$4.20. I suspect that it may run just a bit over that by the time it has been shipped over here. It is published by Odhams Press Limited, Long Acre, London. Radio Bookshop will import it for you if you want to avoid the paperwork . . . see ad page 60.

. . . so you want to be a HAM

This 188-page book by Robert Hertzberg W2DJJ is the second edition, completely revised and enlarged, of this successful idea. Chapter 1 tells all about our hobby, the various types of licenses, what we do, etc., complete with plenty of interesting pictures. Chapter 2 goes into methods for learning the code. From there on the book takes on the proportions of a giant catalog, showing pictures and giving brief complimentary descriptions of just about every possible piece of commercial ham gear. Bob is probably closer than the Handbook, with all its construction projects, to the present day spirit of our hobby. Old timers will remember when the problem was to decide what tube to use in the final . . . now we have to make the big decision about what brand of equipment we are going to buy. \$2.95.

6**10****15****20****meters**

With the *Exclusive*
MINI-PRODUCTS' 4-BANDER

Featuring --

4 BANDS Small size . . .
 Light enough for any
 TV Rotor

Model B-24
2 elements

Amateur Net
\$54.95*

Features

- Four Bands—6, 10, 15, 20
- Maximum element length 11'-6", boom 6'-10"
- Turning radius 7'
- Weight—11 lbs.
- Gain—comparable to any antenna of equivalent size
- SWR—Less than 2:1 on all bands
- 6061-T6 aluminum elements and boom
- 1" diameter elements for maximum band width
- Can be assembled in smallest garage

†Patent Pending

• For the ham with limited space and those desiring maximum efficiency in the smallest size, Mini-Products takes pride in introducing the *first* truly Miniaturized multiband antenna, using the new Multiple-Hat principle† a new concept in Multiband antennas which provides coverage of any number of bands within a two octave range with a single antenna.

End loading employed on all bands—universally accepted by antenna designers as the most efficient method of miniaturizing and maintaining the high radiation resistance and radiator current necessary for effective radiation.

Model M-4 MOBILE

Amateur Net

\$16.95*

Features

- Four Bands—6, 10, 15, 20
- Overall height—5'-8"
- Up to 5 db. gain over base loaded antenna's of equivalent height
- SWR—Less than 2:1 on all bands
- 1" diameter Radiator for maximum band width
- 3/8"-24 base stud—Fits all standard mobile mounts

*NOTE—Pennsylvania residents add 4% Sales Tax

Mini-Products, Inc.

Ask for them at your favorite distributor or order direct from:
 1001 WEST 18th ST., ERIE, PENNSYLVANIA

Echo Echo

Staff

This should be called Hard Facts About Echo, Part II, I suppose. The hard facts are that we ran an article last month by Don Goshay W6MMU which went on to prove that you can get a better bounce from the moon than you can from elusive "Echo" x and somewhere down in the print shop the chart which went with it became lost. Here is the chart. With this chart you can figure out ahead of time just how much signal you can expect to get back from what type of reflector. The next time some joker starts to tell you about the S-9 signals he got back on two meters when Echo was passing over you can whip out this chart and set him to looking for other phenomenon to explain his experience.

ECHO CHART

Band width	Add	Band	Add	Power	Add
5 mc	-30 db	144 mc	-19 db	12 1/2 watts	-16 db
50 kc	-10 db	220 mc	-15 1/2 db	125 watts	-6 db
5 kc	0 db	432 mc	-9 1/2 db	250 watts	-3 db
500 cps	10 db	1296 mc	0 db	500 watts	0 db
50 cps	20 db	2400 mc*	5 1/2 db	1 kw	3 db
10 cps	27 db			10 kw*	13 db
5 cps	30 db				

Dish Diameter	Add	Noise Figure	Add	Satellite Diameter	Add
2 feet	-6 db	2 db	0 db	100 feet	0 db
4 feet	0 db	4 db	-2 db	1000 feet	20 db
6 feet	7 db	6 db	-4 db	2000 feet	26 db
8 feet	12 db	8 db	-6 db	Moon at	0 to 6 db
10 feet	16 db	10 db	-8 db	239,000 mi	(see text)
12 feet	19 db	12 db	-10 db		
84 feet*	53 db				

Note: "Add" indicates plus valued corrections are to be applied in the direction of improved system performance.

Example: If a ten foot dish is used on 2400 mc with a transmitter output of 250 watts, a receiver bandwidth of 500 cps, and a receiver noise figure of 4 db, we would have a correction of $+16 + 5\frac{1}{2} - 3 + 10 - 2 = 26\frac{1}{2}$ db. Since we started with a reference of 20 db below the noise, our plus $26\frac{1}{2}$ db correction would give us an expected signal of $6\frac{1}{2}$ db over the noise!

*Asterisk indicates situation of JPL Tracking Facility at Goldstone, California.

SIX METER RECEIVER

MODEL 505A—50-54mc

Here's the ideal low-cost receiver to start your six or two meter station

- Excellent sensitivity with stable superregenerative detector
- Built-in 110 volt AC power supply
- Fully transformer operated, no voltage doubler
- Compact, fully enclosed in cabinet—only 3 inches high
- RF stage for increased sensitivity and isolation
- Send-receive switch for muting receiver
- Band set capacitor for full 4mc bandspread
- Features stable operation and dependability

Model 505A, 506A, KIT, complete as above: \$29.95 • WIRED: \$49.95

MOBILE OPERATORS: Model 505A, 506A are available with mobile power supply instead of AC supply at slight additional charge.

Send for data on the complete line of NEIL 2, 6 and 10 meter fixed station, mobile, and portable receivers, transmitters and transceivers.

SEE YOUR DEALER, OR ORDER FROM

THE NEIL COMPANY | 1336 Calkins Rd. • BAKER 5-6170 • PITTSFORD, N. Y.



ALVARADIO NEW HAM HEADQUARTERS GRAND OPENING SPECIALS



STORE HOURS:
Daily & Saturday—
9 a.m. to 9 p.m.
Sunday—11 a.m. to 6 p.m.

You have dealt with WOODY before. Well; he's at it again, wheeling and dealing. Xmas money waiting for you. Come in and visit our special Ham section.

CASH

for your old gear. . . . Get that buried money out of your garage, attic and basement. Clean out your old equipment. We buy used Ham gear, Commercial, Surplus. We're looking for all components of: GRC, I, PRC, SCR, BC, TS, IE radio and test equipment.



YOU ARE WELCOME TO COME IN AND BROWSE AND DISCUSS YOUR PROJECTS.



WOODY K6BXW



W6ATC HARRY



WA6NBM JIM

- Westinghouse 0-50 ma 3" square meter \$2.50
- WE tel. hand sets 1.49
- Speakers 1.39 and up
- Coiled cords 3 cond. 88¢
- Coiled cords 4 cond. 98¢

CHECK THESE PRICES COAX CABLE SPECIAL

- RG-8A/U 8¢ ft.
- RG-9A/U 10¢ ft.
- RG-7/U 9¢ ft.
- RG-59A/U 5¢ ft.

All in 500 foot spools.
Any length cut to order.

- SCR 625 Mine detectors \$19.95
- AN/PRS 3 Mine detectors, late models 33.50
- 100C crystal mike 3.88

- Gonset 10-11 converter 7.95
- Gonset Comm. II 2M. 149.50
- Gonset Comm III 2M 185.00
- Gonset Comm IV 294.50
- BC 620 new boxed extra tubes 12.95
- 30-40 mc mobile 25 watts 6v power supply, Xmitter - Revr exc. condition 34.95
- ART 13 Crystal calibrator 3 tubes, 200 kc xtal 3.95
- Magnetic bulletin board a must for ham shack 1.49
- New Silicon 750 MA rectifiers 27¢ ea.
- Ferris mod 22A 85kc to 25mc 6 bands Sig. Gen. microvolter. A lab inst. 88.88
- BC 683 27-39 mc FM-AM. Police, fire, paging. Extra set of tubes. New 34.50

Now: Gonset & Hallicrafters Distributor

- Volt-ohmmeter 1000 ohms per volt, pocket size AC-DC Ohms. \$6.88
- Keys 88¢
- 829B new boxed 3.95
- 4X125 pair 17.00
- 4X150 new 7.95
- Coax fittings 29¢

NEW WINTER CATALOG
Write for yours today.

- 2M Transmitter 100W input one package table-top size 115v 60cps power supply & ant relay built in. 829 final screen mod. Complete \$59.50

ALVARADIO INDUSTRIES
5205 LANKERSHIM BLVD. NORTH HOLLYWOOD, CALIF. TRiangle 7-2113

A DIVISION OF
STANDARD ELECTRONICS, INC.

All Over the World... DX-ing MERRY CHRISTMAS with

COSMOPHONE "1000"

Gledelig Jul

BUONE FESTE

NATALIZIE

GLAD JUL

Feliz Navidad

Poyeux Noël



- ▲ A Self-contained 1 KW Transmitter-Receiver
- ▲ A True Table-top Station with NO Sacrifice of Performance

SPECIFICATIONS

TRANSMITTER

INPUT: Full 1 kw on Voice Peaks (Meters Read 2500 V at 400 ma) into a pair of 4 x 300 A's
UNWANTED SIDEBAND: 42 db down
DISTORTION (SSB): Third order products approx. 32 db down
FREQUENCY STABILITY: Drift less than 100 cycles
CALIBRATION: Built-in 100 kc marker
AUDIO CHARACTERISTICS: 200-3100 cps
MIKE INPUT: High impedance
VOX: Built-in
LEVEL: Automatic level control
METERING: Screen, plate, and grid current, plus RF output
RF OUTPUT: 52 ohms
VFO's: Dual VFO's permit transmitting on the receive or any other frequency
CONTROLS: Vox, Qt, ALC, Grid Tuning, Plate Tuning, Antenna Loading, Audio Gain, Band Switch, Meter Switch

RECEIVER

SENSITIVITY: 1 microvolt for 6 db S/N
SELECTIVITY: 3.1 kc mechanical filter plus a T-notch filter
STABILITY: Drift less than 100 cycles from a cold start at room ambient
TUNING KNOBS: Coarse gear ratio of 20:1, fine gear ratio of 100:1 gives a 1 kc dial reading per division
CALIBRATION: Built-in 100 kc marker
IMAGE AND IF REJECTION: Better than 50 db
AUDIO DETECTOR: Balanced detector for SSB and CW, diode detector for AM
MODE SWITCH: Selects up or low SSB, or up low AM, or CW
DUAL RECEPTION: Two VFO's permit reception of any two frequencies on one band with the flick of a switch
BFO: Crystal controlled
METERING: S-meter
CONTROLS: T-notch filter, audio gain, RF gain, antenna trimming, tune selector, phone jack, tune A and B

"The COSMOPHONE 1000"—a complete Station, Receiver, and Transmitter. Dimensions: 17 inches wide, 12 inches high, and 15 inches deep. Power Supplies packaged separately, can be placed under operating desk. Price: "The COSMOPHONE 1000" with Power Supplies...\$1,550.00.

A Product of



For additional information and dealer nearest you, write Dept. 73-12

COSMOS INDUSTRIES, INC.

31-28 QUEENS BOULEVARD
 Long Island City, N. Y.

LETTERS

Arkansas VHF

Dear Wayne,

We've enjoyed your pearls of wisdom from time to time, but let us say that 73 is the Most . . . really have enjoyed my copies. We are looking forward to a real cool VHF section in your new sheet.

In working the various VHF bands we often hear this plaintive cry—"Why don't you guys in Arkansas get some activity on Six, Two or One and a quarter (as the case may be)." As the lawyers say, "I wish to refute this plea." We in Arkansas have activity plus on Six and Two and the beginnings of activity on 220 mc and 432 mc. Down in central Arkansas the VHF activity is very ably stirred by the Arkansas VHF Club and its associated nets, the Central Arkansas Emergency Net and its associated club.

The Arkansas VHF Club had its beginnings in the old Wonder State Net way back in 1956. The active president is Ike Roland K5GOW of Malvern. The club net on Six covers from Forrest City to Conway and from Searcy to Texarkana with relay coverage of the state. At present the net numbers 36 members on Six and 9 members on Two.

The Central Arkansas Emergency Net covers Pulaski County and the counties that touch it on Six and 75M. At present we have 26 mobile units on 6M narrow band FM with almost complete coverage of the area from six base stations.

Net	Frequency	Night	Time	NCS
Ark. VHF Net..	51.0	Tues.	2000	K5OZE/K5EZI
Cent. Ark. Emg. Net	51.0 NBFM 50.25	Thurs.	2000	K5CQP/W5TIE
Ark. VHF Net..	145.05	Thurs.	2100	W5TIE/K5EZI

In addition to the above we have two Air Force MARS nets operating in the area on Six. The 51.0 mc frequency in Arkansas is almost constantly monitored from 1700 until 2300 as is the NBFM frequency at 50.25 through the day from 0730 until 1700 and later. The 145.05 frequency on Two is sampled hourly from 2000 until 2300.

The Arkansas VHF Club is setting Spring 1961 as the target date for net operation on 220 mc and on 432 mc. Several of the fellows have gear that will operate on these frequencies now. We're in VHF up to our XYL's necks, just ask mine!

Jake K5EZI

I'll be listening for you and the gang with my ground plane pointed your way Jake . . . Wayne.

Decoding the Address Label

In addition to your name and address on your label you will find the usual hieroglyphics. Our system is deucedly simple since we didn't have anyone with enough experience to work out a complicated one. The first two numbers tell us when you first subscribed . . . 80: eighth month of 1960. The last two tell us which is the last issue to send . . . 92: September 1962. To get away from the nuisance of using extra numbers we use an "N" for November, and guess what for December. Code appears under the address.

TAPETONE'S NEW
WTC-1296
1/4 METER,
LOW-NOISE
CRYSTAL
MIXER
CONVERTER



NEWEST
CONVERTER
ON THE MARKET . . .

This advanced design approach, seldom used by amateurs but widely used in commercial UHF receivers, achieves outstanding performance. It consists of a double-tuned cavity preselector, followed by a crystal mixer and low-noise IF preamplifier.

SPECIFICATIONS:

NOISE FIGURE: 7.5 DB
GAIN: 20 DB
IMAGE REJECTION: GREATER THAN 40 DB
IF REJECTION: GREATER THAN 80 DB
ALL OTHER REJECTION: GREATER THAN 60 DB
TUBE COMPLEMENT: 1N21E, 6BC4, 6BC4,
12AT7, 6AK5, 1N295

STANDARD MODELS AVAILABLE:

WTC-1296B IF OUTPUT FREQUENCY 50-54 MC.
WTC-1296A IF OUTPUT FREQUENCY 51-55 MC.
WTC-1296N IF OUTPUT FREQUENCY 30.5-34.5 MC.
WTC-1296C IF OUTPUT FREQUENCY 28-32 MC.

PRICE \$134.50 (ANY MODEL)

ALSO AVAILABLE: WTC-432, PRICE \$119.50

TAPETONE, INC. 10 ARDLOCK PLACE,
WEBSTER, MASS.

VESTO TOWER

Survives 156 mph
HURRICANE "DONNA"

Vesto's famous
"Hurricane-Proof"
Construction is
the Reason!

NO GUY WIRES

EASY TO ERECT

Step-by-step
instructions given!
Can be taken down
and moved easily!


**HOT DIP
GALVANIZED**

to last a lifetime!

Prices start at

\$149⁰⁰

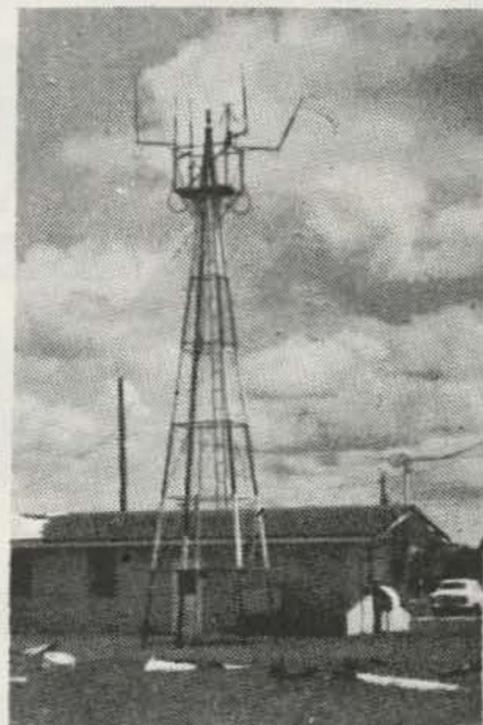EASY PAYMENT PLAN!
Write for new,
FREE Literature!




THIS VESTO TOWER
WITHSTOOD HURRICANE
"DONNA" IN FLORIDA


VESTO CO., INC.
20th and Clay St.
North Kansas City, Mo.

PROPAGATION CHART


EASTERN UNITED STATES TO:

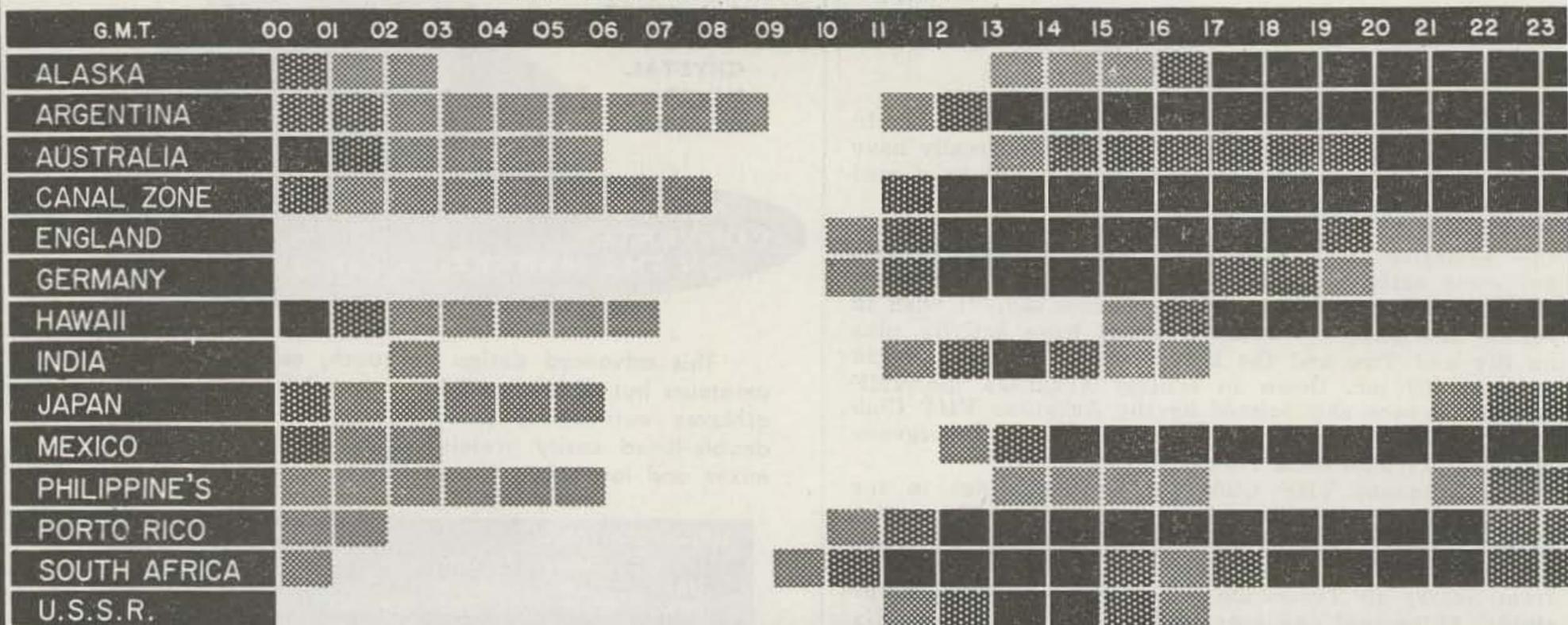

CENTRAL UNITED STATES TO:

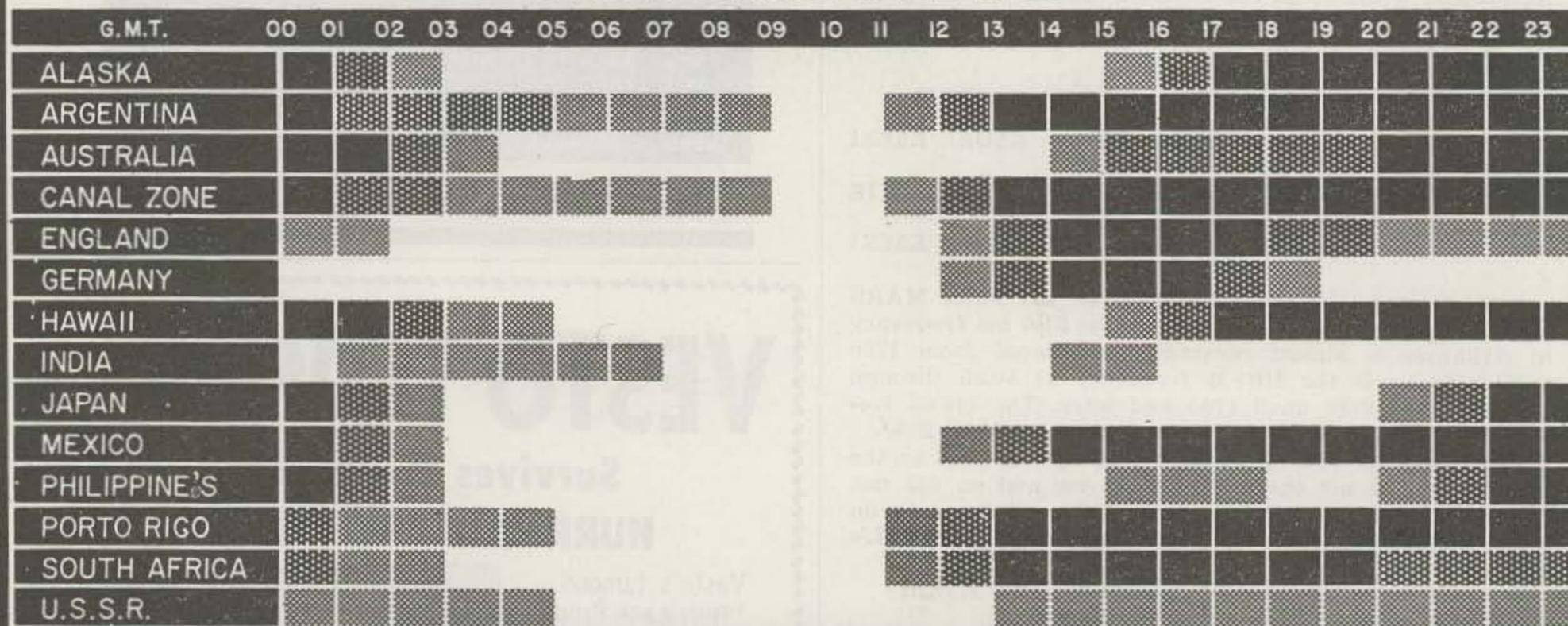

WESTERN UNITED STATES TO:

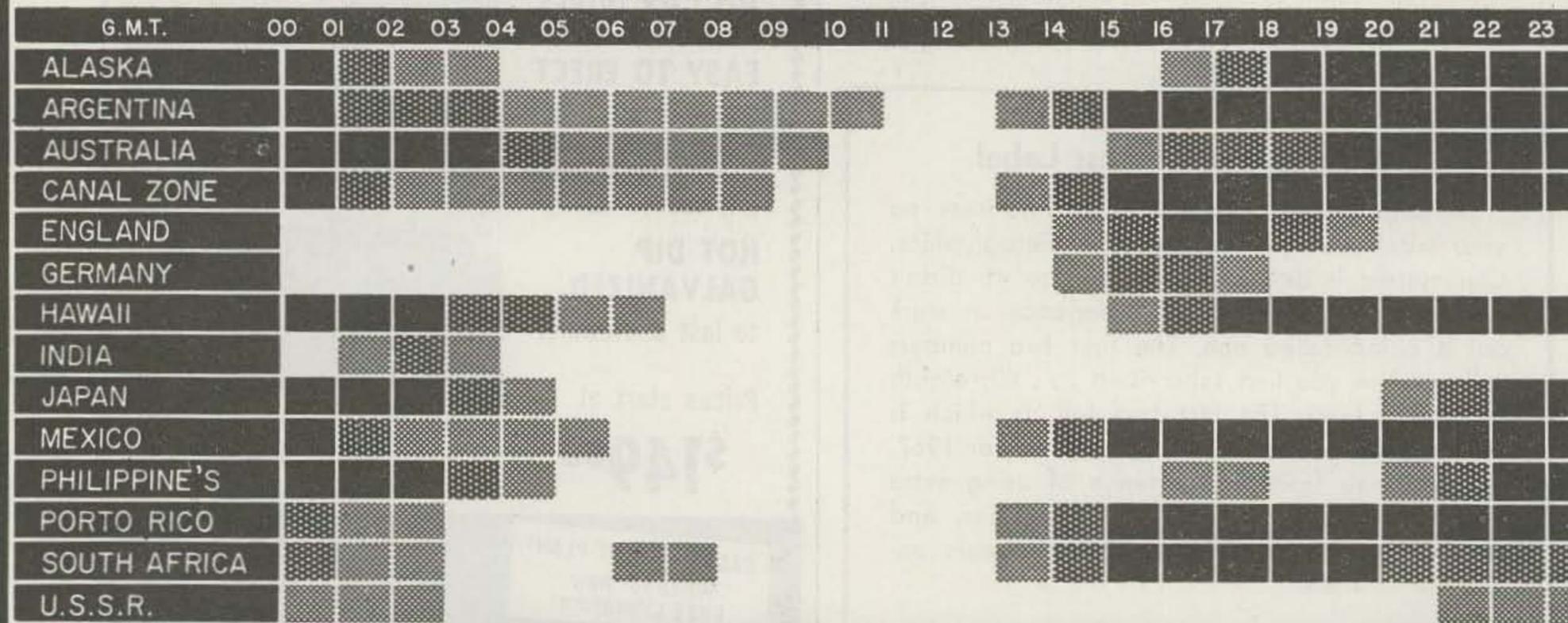

LEGEND

7 MC

14 MC

21 MC

28 MC

Technical Broadcasts

You really ought to listen to the interesting talks being given each Sunday from 2-4 p.m. (EST) on 3295-7540-15,715 kc.

Dec. 4—David P. Sarett: Principles of Guidance and Navigation, and Inertial Devices.

Dec. 11—G. W. Davidson: Analog and Digital Computers.

Dec. 18—J. Foster: Design and Application of Special Development Test Equipment.

Jan. 8—R. R. Darden: Exotic Applications of Semiconductors.

(All speakers are from the American Bosch Arma Corporation).

(There will be no broadcasts on the Christmas and New Year Sundays).

New Product

Gonset G-63

This new receiver by Gonset nets for a bit under \$250 and has a lot of interesting features. It is a ham-band only receiver and covers 80 thru 6 meters. It has separate second detectors for SSB/CW and AM, a peaking Q-multiplier and temperature and voltage compensated HF and BFO oscillators. Drop a card to Gonset Division, Young Spring & Wire Corp., Burbank, California for more details and a bigger picture. Tell 'em you saw it in 73, even if you didn't. Or tell 'em you didn't see it in 73. Just get 73 in there somewhere.



THE NEW P & H LA-400-C 800 WATTS PEP SSB LINEAR AMPLIFIER



**NOW 800 WATTS PEP
FOR ONLY \$164.95
THE "BEST BUY" YET**

NEW modern styling! NEW high efficiency 3 element band-switching pi net. Puts more power into any antenna or load from 50-70 ohms. For SSB, DSB, Linear AM, PM, CW and FSK. All bands 80-10 meters. May be driven to 800 WATTS PEP SSB with popular 100 watt SSB exciters. Uses four modified 1625's in grounded grid. On customers order, will be furnished with 837's. (note: 1625's and 837's are not directly interchangeable, since sockets are different.) Typical P&H Low Z untuned input. TVI suppressed. Parasitic Free. Meter reads grid drive, plate current, RF amps output. Heavy duty power supply using 816's. NEW modernistic grey cabinet measures approx. 9" x 15" x 10½". Panel is recessed. WANT TO SAVE MONEY? BUY IT IN KIT FORM. It's a breeze to assemble and wire. BEFORE YOU BUY — SEE THE NEW LA-400-C AT YOUR DEALERS.

LA-400-C Kit complete with tubes.....\$164.95

LA-400-C Wired and Tested.....\$219.95

P & H

ELECTRONICS INC.

424 Columbia Lafayette, Ind

Propagation Charts

The bands listed are MUFs and a higher band will not work for the time period listed. Lower bands will work, but not nearly as well. Times are GMT, not local time.

These charts are to be used as a guide to ham band openings for the month of December, 1960 to the various countries listed. I will be

David A. Brown K2IGY
60 New York Avenue
West Hempstead, N. Y.

interested to hear of your results in using these charts and to know what other areas you might wish included in future charts.

Advanced Forecast: December 1960

All days good except Fair on 5-6, 30-31. No bad days!

Vagabond Ham

*A vagabond's life is the life I live
Along with others, ready to give
A friendly laugh and a word of cheer
To each vagabond friend, both far and near.*

*I travel the air waves, day or night
To visit places I'll never sight
From the rail of a ship, or from a plane
Yet I'll visit them all again and 'again.*

*I never hear from a far off land
That my pulse doesn't quicken. With careful hand
I tune my receiver and VFO dial
To make a new friend and chat for awhile.*

*Africa, Asia, they're all quite near
In as easy reach as my radio gear
With the flip of a switch, the turn of a knob
I can work a ZL, a friend named Bob.*

*There's an LU4, a fellow that's grand
Who's described to me his native land
'Till I can hear the birds, and feel the breeze
As it blows from the slopes of the mighty Andes.*

*I learned of the surf, and a coral strand,
The smell of hibiscus where palm trees stand
'Neath a tropical moon, silver and bright
From an FO8 that I worked one night.*

*I've thrilled to the tales of night birds' screams
In the depths of the jungle where death-laden streams
Flow 'neath verdant growth of browns and greens
From a DU6 in the Philippines.*

*The moors of Scotland, a little French Shrine,
German castles on the River Rhine
Of these things I've learned, over the air
Without ever leaving my ham shack chair.*

*There's a KL7 on top of the world
To whom the Northern Lights are a banner unfurled
That sweeps across the Arctic night
Makes the frozen sky a thing of delight.*

*Tales of silver and gold and precious stones
Ancient temples and molding bones
Where the natives, I'm told, are tall and tan
By an XE3 down in Yucatan.*

*My vagabond trips over the air
Will take me, well, just anywhere
Where other vagabonds and I will meet
From a tropical isle, to a city street.*

*My vagabond's life will continue, I know
Through the fabulous hobby of ham radio
And one day from out at the world's end
We'll meet on the air, my Vagabond friend.*

Ken Johnson W6NKE

(... de W2NSD continued from page 7)

month period so we could find out specs and prices without having to send for that "further information" which takes from days to weeks to arrive? Even a brief listing would be helpful.

This could get to be pretty prohibitive if it weren't for the low advertising rates of 73. A quarter page ad is still only \$40.

Audio Booster Note

Jim Kyle points out that the value of R13 in the circuit may have to be changed to balance things if your rig has an input impedance which is different than his. If you've had any trouble in getting a balance this should help. For instance with a 1 megohm mike and a 1 megohm input R13 would have to be 2.2 megohms.

Chortle

Propagation forecasting, like weather forecasting, is divided into several schools of thought.

In comparing the Propagation Charts in the November 73 with those in other ham magazines I was surprised to notice that Dave Brown had forecast the period of November 12-15 as one of very bad conditions, while the other forecaster had promised that these dates would produce the best conditions of the month.

While visiting the Voice of America studios on November 16th to record a program for the VOA Ham show, Bill Leonard W2SKE and Gene Kern W2BAK discussed at length the worst radio blackout in recent years which struck from November 12-15.

Congratulations K2IGY and keep up the good work. I'll bet you were really worried when the National Bureau of Standards issued their November 9th advanced forecast for November 10-16th and predicted normal conditions.

News Clippings

Marvin Lipton VE3DQX, in addition to sending out a monthly bulletin to all editors of club bulletins to help them get news for their publications, will be excerpting news items which have made the newspapers for us to print in 73. Please scan your local paper carefully and send Marvin anything hammy that creeps in. Or send it to 73 and we'll forward it up to Marvin for condensing. Send it in, good or bad, to Marvin Lipton VE3DQX, 311 Rosemary Road, Toronto 10, Ontario, Canada.

Shorts

I hate to embroil you in editorial problems, somewhat. Bluntly put: we need more short items, stuff that obviously doesn't require full

(Continued on page 57)

"its here" CLIMASTER MERCURY CLIMASTER ZEUS

Three years of development and field testing were required to produce these worthy successors to the Climaster 62T10.

Note some of the advantages you get with these new units:

- Dual Band Coverage . . . 6 and 2 meters
- Self Contained STABLE VFO
- Compact, Modular Construction
- Automatic Modulation Control
- High Level Modulation
- High Efficiency Tank Circuits
- Ease and Convenience of Operation

CLIMASTER MERCURY . . . 200 Watts AM Carrier Output
CLIMASTER ZEUS . . . 90 Watts AM Carrier Output

Clegg

 LABORATORIES

DIVISION OF CLEGG, INC.

Rt. 53, Mt. Tabor, New Jersey • OAKwood 7-6800

CHECK* THESE ITEMS

Crystals, type CR27U, 28.5556 mc (in 10M phone band). Can be used with Johnson or Heathkit rigs. \$1.95

Time Delay Relay, 110vac motor operated type, adj. 2 sec-50 min. Size 5 1/2 x 5 1/2 x 5 1/2. Westinghouse. Sold for \$90.ur cost. \$6.50

Meter, O-500 μ a, 2 1/2" round type. \$2.65

Sigma Relay type 4-F 8000 ohms, pulls in at 1 ma. 5 prong can. \$4.75

Thordarson Plate Transformer, 220v pri, 3000 vct @ 300 ma sec. Shipping weight 69 lbs. . . . \$17.95

Open Frame Choke, 2 Hy, 0.650 amps, 15.8 ohms dc, 4 lbs. \$3.25

Par Metal Relay Rack type 2520, 24" x 21" x 12", 18 lbs. \$5.25

Astron Capacitor type MET-1.53M, 3 mfd 150v metalized paper type, non-polarized metal can. Orig. cost about \$5.ur cost. \$0.99

Capacitor, 4 mfd 10,000v Westinghouse Inerteen. . . . \$65.00

WE STOCK: Gonset, Solar, National, International Crystal, Johnson, UTC, Westinghouse, Cushcraft, B & W Coils, Dow-Key Relays, Mosley Antennas, Eico, and many others.

Write for our bargain list. If you're in the neighborhood stop in and say hello to Russ Spera, W2URU *from your check book, what else?

Spera Electronic Supply

37-10 33rd St., Long Island City I, N. Y.
STillwell 6-2199 STillwell 6-2190

Name Call \$3 yr.
Address \$5 2 yrs.
City Zone State \$4 yr. DX
..... years. Start: Oct.— Nov.— Dec.— Jan.— (Check one)
73 Magazine; 1379 East 15th St., Brooklyn 30, N. Y.

Name Call \$3 yr.
Address \$5 2 yrs.
City Zone State \$4 yr. DX
..... years. Start: Oct.— Nov.— Dec.— Jan.— (Check one)
73 Magazine; 1379 East 15th St., Brooklyn 30, N. Y.

Name Call \$3 yr.
Address \$5 2 yrs.
City Zone State \$4 yr. DX
..... years. Start: Oct.— Nov.— Dec.— Jan.— (Check one)
73 Magazine; 1379 East 15th St., Brooklyn 30, N. Y.

Name Call \$3 yr.
Address \$5 2 yrs.
City Zone State \$4 yr. DX
..... years. Start: Oct.— Nov.— Dec.— Jan.— (Check one)
73 Magazine; 1379 East 15th St., Brooklyn 30, N. Y.

Name Call \$3 yr.
Address \$5 2 yrs.
City Zone State \$4 yr. DX
..... years. Start: Oct.— Nov.— Dec.— Jan.— (Check one)
73 Magazine; 1379 East 15th St., Brooklyn 30, N. Y.

SOLAR SYSTEM VI

RECEIVER

Better than 1/5 microvolt selectivity.
10 kc selectivity (6 db down).
Double conversion for selectivity, image rejection and sensitivity.
Voltage regulated oscillators for stability.
Up to 5 watts audio output for external speaker.
Self contained speaker.
Large 6:1 vernier dial for easy tuning.
Jack for headset output.
Built-in noise limiter.
Spotting switch for zeroing receiver and transmitter.

MECHANICAL

Weight is only 15 pounds . . . you can carry it anywhere easily.
Size is 8"x12" deep to fit under dash or into a suitcase.
One piece double plated chassis for stability and long rust-proof life.
Removes from case easily for servicing.
Carrying handle easily removed for quick mobile installations or used as a mounting bracket.
Steel case with fine crackle finish.
All components are standard and replaceable (no

TRANSMITTER

12 Watts input to a 5763
High efficiency plate and screen modulation for maximum "punch"
Uses popular and inexpensive 8 mc crystals (FT-243 holders)
Provision for VFO operation
Press-to-talk
Metered
Microphone: crystal, ceramic or carbon
50-75 ohm output (will match standard auto receiving whip)

printed circuit boards).
Front panel is recessed and etched so lettering cannot wear off.
Mounting feet are instantly removable.

POWER SUPPLY


Self contained vibrator power supply for 6 vdc, 12 vdc and 110 vac.
Nothing else to buy. The change of power source can be made in seconds.
Separate power cords provided for dc and ac inputs.

SIX METER TRANSCEIVER

for . . .

- Mobile
- Fixed Station
- Emergency
- Aviation

Price **\$189.50**

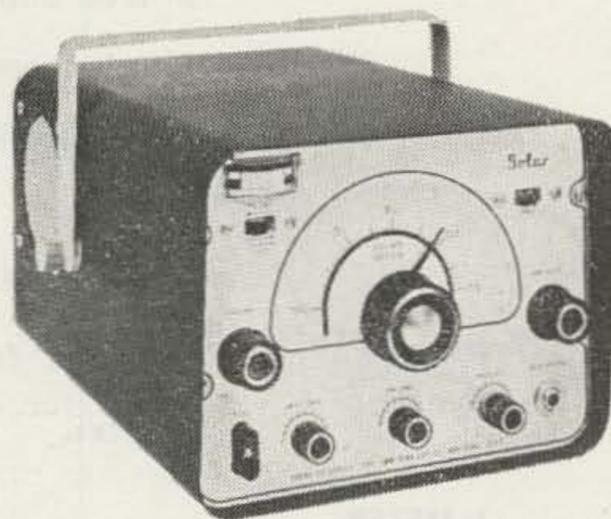

For information send to . . .

SOLAR ELECTRONICS

Corp. 149 Wooster Street
New York 12, New York

Subscription Department


If you like to build, you'll like 73

. . . and maybe you have some friends who would appreciate getting the next dozen issues of 73. We're guaranteeing you a continued supply of good construction articles, well written and easy to understand technical articles, and the usual guff from the editor. We'll be wasting no space on monthly columns. We'll continue to run more pages of articles than


any other ham magazine. Ham radio is the best hobby in the world . . . enjoy it with us. Rates: \$3 per year; \$5 for two years; \$4 per year for DX stations outside of the U.S. & Possessions, Canada and Mexico. Note that the sub blanks are cleverly designed so you can send 'em to friends. Make note if we are to send a gift card for you.

Name Call \$3 yr.
Address \$5 2 yrs.
City Zone State \$4 yr. DX
. years. Start: Oct.— Nov.— Dec.— Jan.— (Check one)

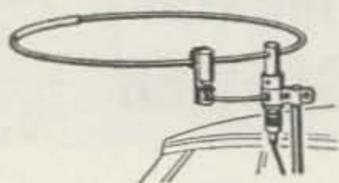73 Magazine; 1379 East 15th St., Brooklyn 30, N. Y.




2-METER

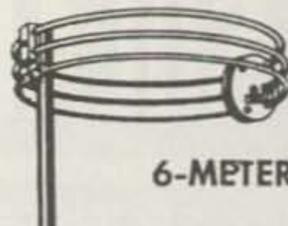

6-METER

HALO ANTENNAS

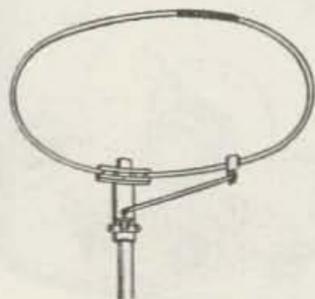Fixed and Mobile, for both 6 and 2 meters, by the pioneers in horizontal polarization for mobile communications.



6-METER


Hi-Par also manufactures a quality line of antennas for amateur, TV, FM and commercial services.

AT YOUR
DISTRIBUTORS
OR
WRITE DIRECT

HI-PAR PRODUCTS CO. ♦ FITCHBURG, MASS.

*the famous Bendix MRT-90 transceiver
is now available!*

only
\$39⁹⁵

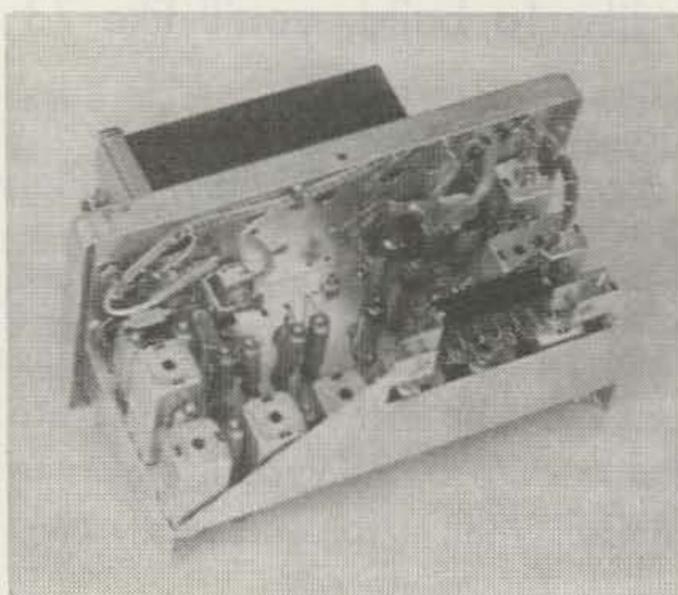

This transceiver was originally built for telemetering. Ideal for a mobile transceiver.

- model control
- telemetering
- home station transceiver

Complete with 19 tubes (at less than the cost of the tubes).
 0.8 uv sensitivity receiver.
 Double conversion, crystal controlled for extreme stability.
 1 watt push-pull output transmitter, crystal controlled, phase modulated.
 Built-in antenna relay, BNC connector for antenna.
 6 volt dc power supply on separate chassis, plugs into transceiver.
 Tuned to 138.06 mc, easily converted to 144 mc, instructions incl.
 Transmitter ideal for driving 6146 for higher power.

METRO ELECTRONICS CORP. 172 Washington Street
New York, N. Y.

(. . . de W2NSD from page 53)

article treatment. The object is to try to complete our articles without having to jump them to the back of the magazine. Readers get all clustered when we start an article in the middle of a page so the best solution is to use the R's D system and fill in the blanks with little spots.

How Are We Doing?

This is the question I get asked most. I assume that a lot of you would like to know. Well, we're not doing as well as I'd hoped, but we're doing better than I planned. we are just about breaking even on publishing expenses, with nothing yet left over for salaries. This, I believe, is considered to be a runaway success in the publishing field. Our circulation should be passing 20,000 with the January issue.

Wayne Green W2NSD


New Book

Repairing Transistor Radios

Now that transistor radios are turning up everywhere we find that we amateurs are frequently called upon for diagnosis and surgery. In all probability there are now one or more of these miniature frustraters in your household. Be ready when they gasp their last gasp, have a copy of Rider #270 at hand so you'll know where to find the patients' pulse. This \$3.50 book covers the subject with the usual Rider thoroughness, exhaustively illustrated. John F. Rider, Publisher, 116 West 14th Street, New York 11.

EVERY HAM NEEDS THIS FAMOUS

VIBROPLEX

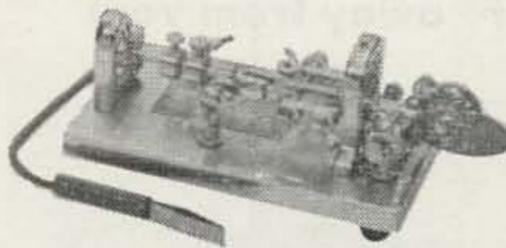


SEMI-AUTOMATIC

The Original Vibroplex features ease of operation, sharp clear signals, precision machining and is acclaimed by thousands of the finest operators. Adjustable to any speed and will not tire the arm or

upset the nerves. Good for 30 or more years even under rough usage. Comes in five models, standard or deluxe and is priced at only \$15.95 to \$29.95.

VIBRO-KEYER

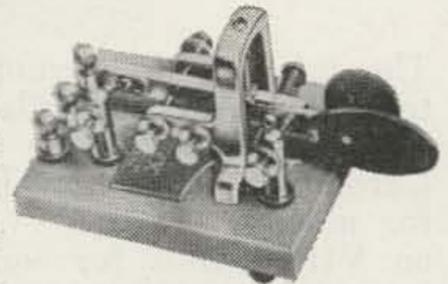A keying mechanism to be used in building electronic transmitting units. Features a beige colored base, 3 1/2" by 4 1/2" and weighing 2 3/4 lbs. A thing of beauty with the same large sized contacts, main frame and super finished parts as the Deluxe Vibroplex. Red finger and thumb pieces and trunion lever. Adjustable to suit your speed. Priced at \$15.95. Order today at your dealers or direct.



THE VIBROPLEX CO., INC.

833 Broadway • New York 3, N. Y.

FREE Folder

R-F WATTMETER

Model PCA-1

\$14.95

FEATURES

- Tuning Citizens Band Xmtrs
- Tuning Low Power Ham Rigs
- Tuning Mobile Xmtrs Police-Fire-Taxi-Bus-Ham
- Tuning Antennas
- Checking Modulation Quality



SPECIFICATIONS

- Reads Power to 10 Watts
- Field Strength Meter
- Modulation Monitor
- Built-in 10 Watt 52 Ohm Load

Manufacturers reps and distributors interested in a few extra pennies please write.

Order through your local parts distributor or send direct to:

PRECISION COMMUNICATIONS ACCESSORIES

674 Eighth Ave., New York 36, New York

CQ GHOST SHIP!



...by Walker A. Tompkins K6ATK

Thousands of hams and their Jr Ops enjoyed SOS AT MIDNIGHT. Now read the further adventures of Tommy Rockford in this new ham radio novel. Packed with action.

Only **\$2.95**


Order from

RADIO BOOKSHOP

1379 EAST 15TH STREET
Brooklyn 30, New York

YOUR KIDS WILL **idly**

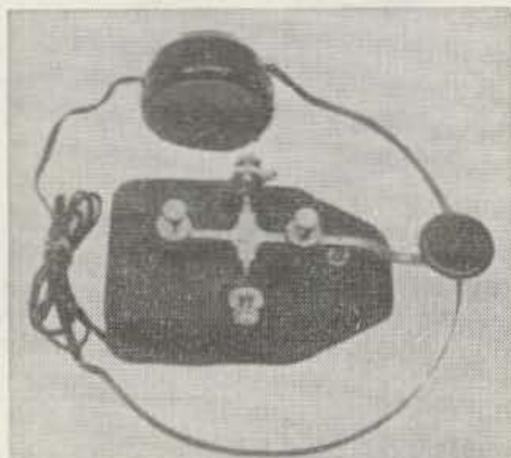(if they can get this Key-municator[®] away from you)



See
Cover

This is a hand key, complete with a built-in transistorized CW oscillator, long life battery (also built-in) and an earphone. Great for learning the code . . . will transmit over wires for miles to friends . . . or can be used on VHF bands for sending ICW. Comes mounted on a 9" x 12" base with the Morse code printed on it and a supply of message blanks. Ready to use. Any number may be connected together.

. . . at your distributor . . . **\$9.95**

DOW-KEY COMPANY

Thief River Falls, Minnesota

U.S. #1 ELECTRONICS

a division of AMBER INDUSTRIAL CORP.

1920 E. EDGAR ROAD (Right on Highway U.S. 1)
LINDEN, N. J.—across from ESSO RESEARCH LABS

PLENTY OF FREE PARKING!

30 minutes by Public Service from N. Y. C.

OPEN FOR RETAIL

after 15 years of wholesale only—now you can buy choice surplus electronics—from our enormous and varied stocks—material for the whole electromagnetic spectrum.

R8/ARN-8	75 mc RCVR 7 tubes.....	\$ 9.95
RT-86/APW-1	Exc. for conversion to 2 meters. New.....	19.95
GO-9	Brand new	69.50
SCR-522 XCVR	EXC W/Tubes	22.50
SCR-522 XCVR	L/New. W/Tubes	17.50
BC-603 RCVR	New. W/Tubes.....	15.00
BC-604 XMTR	Brand New. W/Tubes.....	8.50
BC-603 AS	1s, Less Tubes.....	5.00
DM-34 RCVR	DYN 12V. New	5.00
BC-458 XMTR	5.3-7mc. New	7.50
PE-117, 120	Power Supply, Vibrator....	3.45
Famous PE-103	Dyn. New	14.50
PE 103	Excell. Cond.	12.50
BC-312	New Cond.	72.50
T-26 Mobile Chest Mike	New \$1.00 ea.....	5/ 3.00
5F or 5G 60 Cycle Synchro	\$15.00 ea.....	2/ 25.00
10MFD 600v Oil Cond. New. G.E.....		1.00
15MFD 600v Oil Cond. New. G.E.....		1.50
.00025 MFD. 8000 volt Peak \$1.00 ea.....	6/	5.00
MP-22 Mast base, exc. mobile mt. New.....		1.95

THOUSANDS OF ITEMS—THOUSANDS OF BARGAINS!

Write for free listing—25% deposit on C.O.D. orders—
Minimum order \$5.00. All prices f.o.b. Linden, N. J.

Other Ham

RATHER than devote half or more of 73 to the printing of news of interest to specialized groups we believe that it is our function to do everything possible to encourage the publishers of bulletins which cater to these

HAM-SWAP. Published by Ham-Swap, Inc., 35 East Wacker Drive, Chicago 1, Illinois. Editor is Ed Shuey, K9BDK. Subs are \$1 per year by 3rd class mail, \$3 for 1st class, \$5 airmail, and \$7.20 special delivery. Published twice a month. Contains classified ads entirely. This is your best bet for an inexpensive way to sell or swap some gear in a hurry. Within two weeks people are answering your ad.

FLORIDA RTTY BULLETIN. Fred W. DeMotte W4RWM, P.O. Box 6047, Daytona Beach, Florida. \$3 per year including membership in Florida RTTY Society. Mostly operating news with a bit of technical info now and then. All TT men should be getting this.

SOUTHERN CALIFORNIA RTTY BULLETIN. Merrill L. Swan W6AEE, 372 West Warren Way, Arcadia, California. \$2.75 per year, not including membership in Society. Operating news and some technical articles. This is the oldest TT bulletin going. All TT men should also get this one. Monthly.

73 HAM CLUB BULLETIN. Marvin Lipton VE3DQX, 311 Rosemary Road, Toronto 10, Ontario, Canada. Sent free to all editors of ham club bulletins monthly to keep them abreast of what is going on with all the other ham clubs. This is an excellent source of news for putting together your club bulletins. To subscribe to this news bulletin just send a copy of your own club bulletin to Marvin.

WESTERN RADIO AMATEUR. Don Williamson W6JRE, 10517 Haverly Street, El Monte, California. Monthly. Subs are \$2 per year, \$3.50 for two years, \$5 for three years. Operating news of west coast activity, columns on DX, SSB, YL, and some articles. 48 pages.

Publications

interests. These bulletins bring you the news you want in far greater detail and in much less time than is possible in a monthly magazine where it usually takes two months for news to get into print.

SIDE BANDER. Official organ of the Single Sideband Amateur Radio Association, 12 Elm Street, Lynbrook, N. Y. Subs include membership to SSBARA: \$3 per year. Monthly. Primarily operating news and chit-chat for the SSB DX gang. Columns by W8YIN, K5MWU, K6EXT and occasional technical info.

THE MONITOR. Mar-Jax Publishers, 507 West Davis Street, Dallas 8, Texas. \$1 a year, 3 years for \$2.50. Monthly. Largely operating news. Columns: YL, Club Meetings, Arkansas News, Mississippi News, Florida News, DX, Missouri News, MARS, California News, Louisiana News, VHF News, Oklahoma News, Rio Grande Valley News, Novice News.

VHF AMATEUR. 67 Russell Avenue, Rahway, New Jersey. \$3 year. Monthly. Operating news for VHF men. Some technical info.

DX-QSL News Letter. Clif Evans, K6BX, Box 385, Bonita, California. Published quarterly. 40¢ each; Annual subscription \$1.25 (four copies) by first class mail (\$1.50 for DX stations). Lists all QSL Bureaus, managers for rare DX stations, etc.

DIRECTORY OF CERTIFICATES AND AWARDS. Clif Evans, K6BX, Box 385, Bonita, Cal. Complete Directory plus one year of revisions (quarterly) \$3.50. Add 75¢ for 1st class mail; \$1.25 for airmail; DX stations 1st class mail add \$1.00. Needless to say, this is the most complete collection of data on the hundreds of certificates and awards available.

MOBILE NEWS. Published monthly by the Amateur Radio Mobile Society, 79 Murchison Rd., Leyton, E. 10, England. Joining fee and 1 year sub. is \$2.50.

DX BULLETIN. Don Chesser W4KVX, RFD 1, Burlington, Kentucky. DX news in depth. Published weekly. 3rd Class mail \$5 year; 1st class \$6; Airmail \$7.50. DX rates on request.

THE *Only Complete Line* OF **V. H. F. ANTENNAS**

3/4 — 1 1/4 — 2 — 6 METERS

- BEAMS
- QUADS
- MOBILE HALOS
- DUAL STACKS
- COLINEAR ARRAYS

See your distributor or write for Free Catalog

CUSHCRAFT

621 HAYWARD ST.
MANCHESTER, N. H.

FREE Catalog

OF THE WORLD'S FINEST
**ELECTRONIC GOV'T
SURPLUS BARGAINS**



Receivers, Transmitters, Microphones, Meters, Headsets, Amplifiers, Generators, Test Equipment, Telephone Equipment, Motors, Dynamotors, Power Supplies, Antennas, Cable, Transformers, Inverters, Etc.-Etc.

Address Dept. 73

Fair Radio Sales


2133 ELIDA RD.

Box 1105 • LIMA, OHIO

MOBILE POWER SUPPLY

MODEL
A12/600/200

NOW
\$59.50

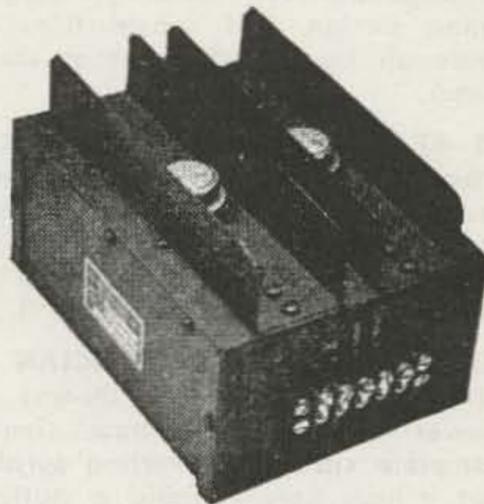

This 12V input dc to dc transistorized converter is conservatively rated for continuous output of 120 watts at 600V or 300V, or any combination of 600 and 300 volt loads totaling 120 watts.

High efficiency, small size, and light weight, plus freedom from maintenance, conserve your battery and increase the enjoyment of mobile operation.



ELECTRONICS DIVISION

GLOBE INDUSTRIES, INC.

525 MAIN STREET

BELLEVILLE, NEW JERSEY

Instructions for using Radio Bookshop:

- 1) Read list of books and mark those you **must** have.
- 2) Check off the same numbers on the order blank.
- 3) Total up the bill and enclose a check, money order or cash.
- 4) Put the whole works in an envelope, address and mail.
- 5) Don't forget the stamp.
- 6) Or your return address.

1—ELECTRONICS & RADIO ENGINEERING—Terman. One of the most complete text books ever printed. 1078 pages. Theory, but easy on the math. **\$14.50**

2—ELECTRICAL ENGINEERING HANDBOOK—McIlwain. Formulas, tables, circuits. A real handbook. 1618 pages. **\$10.00**

5—ANTENNAS—Kraus (W8JK). The most complete book on antennas in print, but largely design and theory, complete with math. **\$11.50**

10—I, LIBERTINE—Shepherd (K2ORS). Racy 35¢ book, a best-seller. Specially priced for you at . . . **50¢**

20—RTTY HANDBOOK—Kretzman (W2JTP). A-Z of ham Teletype. Very popular book, low supply. **\$3.00**

21—VHF HANDBOOK—Johnson (W6QKI). Types of VHF propagation, VHF circuitry, component limitations, antenna design and construction, test equipment. Very thorough book and one that should be in every VHF shack. **\$2.95**

22—BEAM ANTENNA HANDBOOK—Orr (W6SAI). Basics, theory and construction of beams, transmission lines, matching devices, and test equipment. Almost all ham stations need a beam of some sort . . . here is the only source of basic info to help you decide what beam to build or buy, how to install it, how to tune it. **\$2.70**

23—NOVICE & TECHNICIAN HANDBOOK—Stoner (W6TNS). Sugar coated theory: receivers, transmitters, power supplies, antennas; simple construction of a complete station, converting surplus equipment. How to get a ham license, build a station and get on the air. **\$2.85**

24—BETTER SHORT WAVE RECEPTION—Orr (W6SAI). How to buy a receiver, how to tune it, align it; building accessories; better antennas; QSL's, maps, aurora zones, CW reception, SSB reception, etc. Handbook for short wave listeners and radio amateurs. **\$2.85**

28—TELEVISION INTERFERENCE—Rand (W1DBM). This is the authoritative book on the subject of getting TVI out of your rigs and the neighbors sets. **\$1.75**

32—RCA RADIOTRON DESIGNERS HANDBOOK—1500 pages of design notes on every possible type of circuit. Fabulous. Every design engineer needs this one. **\$7.50**

40—RADIO HANDBOOK, 15th EDITION—Orr (W6SAI). This is far and away the best amateur radio handbook ever printed. Over 800 pages. **\$7.50**

45—CURTA COMPUTER. The world's smallest computer. Send for detailed information. Makes the slide rule look sick. Like a big Monroe computer only hand size. **\$125.00**

47—PRACTICAL ELECTRONICS—Hertzberg (W2DJJ). Almost solid with pictures. Touches lightly on many

aspects of electronics: ham radio, TV, transistor radios, hi-fi, microwaves, trouble-shooting, Novice station, antennas, test equipment, etc. **\$2.50**

48—BASIC ELECTRONICS—Covers subject completely. Written for use with RCA Institute training course. **\$9.25**

49—ELECTRONIC COMMUNICATION—Shrader. Huge book aimed at giving all information necessary for FCC commercial and amateur licenses. **\$13.00**

50—MICROMINIATURIZATION—This is the standard text on the subject. Don't see how a company library can be without this one. Everything is going to have to be built smaller, you know. **\$11.00**

52—HOW TO READ SCHEMATIC DIAGRAMS—Marks. Components & diagrams; electrical, electronic, ac, dc, audio, rf, TV. Starts with individual circuits and carries through complete equipments. **\$3.50**

53—BASIC ELECTRONIC TEST PROCEDURES—Turner. This book covers just about every possible type of electronic test equipment and explains in detail how to use it for every purpose. Testing: audio equipment, receivers, transmitters, transistors, photocells, distortion, tubes, power . . . etc. **\$8.00**

54—HAM RADIO HANDBOOK—Hertzberg (W2DJJ). This is a lavishly illustrated book to interest people in the hobby of ham radio. Tells how to get your ticket, select a receiver and transmitter, learn the code. Pictures and info on just about every commercial piece of ham equipment. Better than a catalog. **\$2.50**

55—TRANSISTOR CIRCUIT HANDBOOK—Simple, easy to understand explanation of transistor circuits. Dozens of interesting applications. **\$4.95**

56—RADIO TELEPHONE LICENSE MANUAL—Smith (W6BCX). Brand new question and answer study guide for FCC commercial licenses. **\$5.00**

57—QUAD ANTENNAS—Orr (W6SAI). Theory, design, construction and operation of cubical quads. Build-it yourself info. Feed systems, tuning. **\$2.85**

58—ANTENNAS FOR CITIZENS RADIO—Orr (W6SAI). General coverage, mobile and directional antennas for 27 mc. band. Build & tune 'em. **\$1.00**

69—S-9 SIGNALS—Orr (W6SAI). A manual of practical, detailed data covering design and construction of highly efficient, inexpensive antennas for the amateur bands that you can build yourself. **\$1.00**

70—CITIZENS RADIO CALL BOOK—Lists all calls issued until January 1960, plus lots of CB info. **\$3.95**

71—CITIZENS RADIO CALL BOOK SUPPLEMENT—Calls from January 1960 until July 1960. **\$3.95**

72—ABC'S OF HAM RADIO—Pyle (W7OE). Designed for the Novice ham. Includes all of the information needed to qualify for the Novice License. 112 pages. **\$1.50**

73—101 WAYS TO USE YOUR HAM TEST EQUIPMENT—Middleton. Grid-dip meters, antenna impedance meters, oscilloscopes, bridges, simple noise generators, and reflected power meters are covered. Tells how to chase trouble out of ham gear. 168 pages. **\$2.50**

74—HANDBOOK OF ELECTRONIC TABLES & FORMULAS—Formulas & laws, constants, standards, symbols and codes. Math tables, misc. data. **\$2.95**

75—BUILD-A-WARD QSL ALBUM—Mount your prize QSL's in this album. Room for 100 cards in each album plus labels for just about all possible operating awards. A fine way to show off your cards. **\$1.95**

76—MODERN OSCILLOSCOPES & THEIR USES—Ruiter. Second edition. Shows what a 'scope is, what it does and how to use it for radio, TV, transmitters, etc. 346 pages. **\$6.50**

77—BASIC ELECTRICAL MEASUREMENTS—Stout. Second edition. Covers aids to computation, measurement of resistance, galvanometers, shunts, standard cells, potentiometers, alternating current bridges, mutual inductance measurements, bridge accessories, instrument transformers, magnetic measurements . . . and lots more. **\$11.65**

78—INTRODUCTION TO ELECTRICAL CIRCUITS—Jackson. Deals with exactly what electronics and electrical engineering technicians need to know. Complete coverage of electrical circuit theory, from beginning level. Develops concepts of current, voltage, resistance, work, and power. Shows how to expand basic concepts to solve elaborate direct and alternating current networks used in modern electrical and electronic circuitry. **\$11.65**

79—TRANSISTOR PROJECTS—Skip the theory and start having fun. Radios: self powered, shirt pocket, regenerative, carrier-power, headphone. Instruments and accessories: sine-square wave generator, preamps for VTVM's, gain checker, shortwave calibrator, phase shifter, substitution box. Plus remote transistor ear, electronic compass, simple oscillator, lamp control, multi-impedance amplifier, electronic counter, portable power supply . . . etc. **\$2.90**

80—SURPLUS RADIO CONVERSION MANUAL VOLUME NO. I (second edition). This book gives circuit diagrams, photos of most equipment, and rather good and complete conversion instructions for the following: BC-221, BC-342, BC-312, BC-348, BC-412, BC-645, BC-946B, SCR-274N 453A series receivers conversion to 10 meter receivers, SCR-274N 457A series transmitters (conversion to VFO), SCR-522 (BC-624 and BC-625 conversion to 2 meters), TBY to 10 and 6 meters, PE-103A, BC-1068A/1161A receiver to 2 meters, Surplus tube index, cross index of A/N tubes vs. commercial types, TV & FM channels. **\$2.50**

81—SURPLUS RADIO CONVERSION MANUAL VOLUME NO. II. Original and conversion circuit diagrams, plus photos of most equipments and full conversion discussion of the following: BC-454/ARC-5 receivers to 10 meters, AN/APS-13 xmtr/rcvr to 420 mc, BC-457/ARC-5 xmtrs to 10 meters, Selenium rectifier power units, ARC-5 power and to include 10 meters, Coil data-simplified VHF, GO-9/TBW, BC-357, TA-12B, AN/ART-13 to ac winding charts, AVT-112A, AM-26/AIC, LM frequency meter, rotators, power chart, ARB diagram. **\$2.50**

82—SURPLUS RADIO CONVERSION MANUAL VOLUME NO. III—Original and conversion diagrams, plus some photo of these: 701A, AN/APN-1, AN/CRC-7, AN/URC-4, CBY-29125, 50083, 50141, 52208, 52232, 52302-09, FT-ARA, BC-442, 453-455, 456-459, BC-696, 950, 1066, 1253, 241A for xtal filter, MBF (COL-43065), MD-7/ARC-5, R-9/APN-4, R23-R-28/ARC-5, RAT, RAV, RM-52 (53), Rt-19/ARC-4, SCR-274N, SCR-522, T-15/ARC-5 to T-23/ARC-5, LM, ART-13, BC-312, 342, 348, 191, 375. Schematics of APT-5, ASB-5, BC-659, 1335A, ARR-2, APA10, APT-2. **\$2.50**

83—THE SURPLUS HANDBOOK, VOLUME I—Receivers and Transmitters. This book consists entirely of circuit diagrams of surplus equipment and photos of the gear.

One of the first things you really have to have to even start considering a conversion of surplus equipment is a good circuit diagram. This book has the following: APN-1, APS-13, ARB, ARC-4, ARC-5, ARC-5 VHF, ARN-5, ARR-2, ASB-7, BC-222, -312, -314, -342, -344, -348, -603, -611, -624 (SCR-522), BC-652, -654, -659, -669, -683, -728, -745, -764, -799, -794, BC-923, -1000, -1004, -1066, -1206, -1306, -1335, BC-AR-231, CRC-7, DAK-3, GF-11, Mark II, MN-26, RAK-5, RAL-5, RAX, Super Pro, TBY, TCS, Resistor Code, Capacitor Color Code, JAN/VT tube index. **\$3.00**

84—SURPLUS SCHEMATIC HANDBOOK—This, too, is a book of schematics . . . and just a hint of conversion strategy here and there. Contains: APA38, APN1, APR1, APR2, APS13, ARB, ARC1, ARC3, ARC4, ARC5, ARC5VHF, ARJ, ARK, ATJ, ARN7, ARR2, ART13, ASB7, ASB1GR, ATK, BCAR231, AC189, BC-191, 221, 312, 342, 314, 344, 348, 375, 438, 474A, 603, 610, 611, 620, 640, 645, 652, 653, 654, 659, 683, 684, 728, 733, 745, 779, 794, 906, 969, 1000, 1004, 1023, 1206, 1335, BN, BP, C3, F3, CRC7, CRO-208, CRT3, DAE, GF-11, GO9, GRR5, I122, I177, I208, JT350A, LM, MD7, MN26, PRC6, PRS3, R174, RAK, RAL, RAO, RAS, RAX, RBH, RBL, RBM, RBS, RC56, RC57, DC, DR, RDZ, SCR-274, 284, 288, 300, 506, 522, 578, 585, 593, 608, 610, 624, 628, SPR-1, SPR2, TBS99, TEW, TBY, TCK, TCS, TG34, TS34AP, TS251UP, VRC-8-9-10, VVX-1. **\$2.50**

85—SO YOU WANT TO BE A HAM—Hertzberg (W2DJJ). Second edition. Good introduction to the hobby. Has photos and brief descriptions of almost every commercially available transmitter and receiver, plus accessories. Lavishly illustrated and readable. **\$2.95**

R170—BASIC ELECTRONICS—Rider. Five volume set of really illustrated books. (1) Power supplies. (2) Amplifiers. (3) Oscillators. (4) Transmitters. (5) Receivers. Soft covers. **\$10.00**

R199—GETTING STARTED IN AMATEUR RADIO—Berens (W2PIK). Fundamentals for getting Novice License. **\$2.40**

R221—BUILDING THE AMATEUR RADIO STATION—Berens (W2PIK). Sequel to above. Everything you need to know to build your first ham station. **\$2.95**

R235—RADIO CONTROL FOR MODEL BUILDERS—Winter. One of the best and newest books available on RC. **\$4.25**

R245—HOW TO USE GRID-DIP OSCILLATORS—Turner (K6AI). Construction & uses, an important book. **\$2.50**

SNS8—SOUND-N-SIGHT CODE COURSE. Three 10" LP records and instructions for Novice code, 0-8 wpm. **\$9.50**

SNS20—SOUND-N-SIGHT CODE COURSE 20 WPM. Advanced course from 9-20 wpm, three 10" LP's. **\$8.95**

SNS28—SOUND-N-SIGHT CODE COURSE COMPLETE. All six LP records. 0-20 wpm and full instructions. **\$15.95**

Handy order form for people who don't mind ripping their magazines to pieces.

1	2	5	10	20	21	22	23	24	28	32	40
45	47	48	49	50	52	53	54	55	56	57	58
69	70	71	72	73	74	75	76	77	78	79	80
81	82	83	84	85	R170	R199	R221	R235	R245	SNS8	SNS20
SNS28											

Circle the book numbers you wish to order. Please include cash, check, money order . . . or something we can deposit in the bank.

Name: Call:

Address:

City: Zone: State:

Radio Bookshop, 1379 East 15th Street, Brooklyn 30, New York


EXCELLO ELECTRONICS PRESENTS

A New Low Price V. F. H. Six Meter Exciter wired and tested with tubes. The Excello SPC 6-6 Six Meter Transmitter Exciter is the lowest priced six meter transmitter on the market to-day. This is not a kit, but a complete unit, ready to put on the air with any power supply from an AC receiver.

PRICE

\$29.95

net to Amateurs
complete with
tubes.

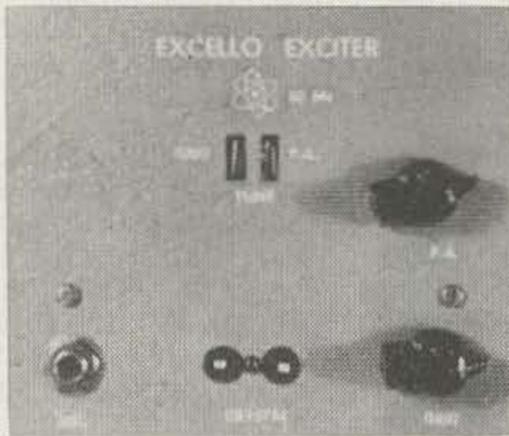

TRANSMITTER FEATURES

- Neon Indicators—Providing monitoring of B plus, Final Tuning, Grid Drive and Modulation, at a Glance.
- Tuning Controls—Tuning controls are all on the Front Panel.
- Access to Components—Removable Enclosure gives access to all Components.
- T. V. I. Suppression—T. V. I. Suppression is accomplished by shielding and design.
- Compact Size—Complete size of unit is 4" x 5" x 6" making it one of the Smallest Six Meter Xmitters available.
- Low Power Consumption—250-300 volts @ 60 MA, 6AQ5 Final Amplifier, 12AT7 Oscillator Multiplier, 6AQ5 Modulator, 6AU6 Speech Amplifier.

Send Money To

Excello Electronics Co., Inc.

196-10 116TH AVENUE . ST. ALBANS 12, N. Y.
Allow 1 to 2 Weeks Shipping

TELETYPEWRITER EQUIPMENT

Collins 51J Receivers .50-30.5 mc.

Model #14, 15, 19, 26 & 28 Teletype machines, Teletype Receiving Converter and others.
Kleinschmidt TT98-TT99-TT100

For general information & equipment list write:
Tom WIAFN, Alltronics-Howard Co.
BOX 19, BOSTON 1, MASS. Richmond 2-0048

PLEASE NOTE

Hams south of Boston, Mass. Bob Graham WIKTJ now has another exclusive amateur store at 1105 North Main Street, Randolph, on Route 28, one mile south of Route 128. Telephone: WO 3-5005.

SURPLUS BUYS

RG8U 2' jumper w. male coax plugs 69¢.....	3 for \$2.00
RG8U 50' w. male coax plugs	\$3.50
Headset H58U 10K ohms w./headband & PL55/new....	\$2.95
Headset HS30 lo imp, plug into ears, new.....	\$1.39
Relays: 12v coil, 2A cont. DPDT,	3 for \$2.00
11K ohms, small, sealed, DPDT.....	\$1.95
24vdc, Allied, sealed, DPDT.....	\$.95
5000 ohms, open frames, DPDT.....	\$1.89
6vdc coaxial, BNC fittings, SPDT, new.....	\$4.95
Variable Condensers: Dual 3-25 mmfd, small.....	\$.69
140 mmfd APC w./shaft	\$.89
100 mmfd APC screwdriver	\$.69
Dual 350 mmfd, 1kv Hammer, FB pi-net.....	\$2.25
Telephone Dial, newest type phone dial.....	\$3.95
Telephone Headset (Grey) new type w./coil cord.....	\$5.95
BC733 10 tube VHF rec. w./tubes dyna & conversion for 2 or 6 meters. 20 lbs, clean.....	\$5.95
BC-604 transmitter, new, conv. 10 meters.....	\$11.95
12vdc 2A supply, 115vac input, new, 35 lbs.....	\$8.95
Reed freq meter 57-63 cy 3" panel, new.....	\$9.97
Reed freq meter 380-420 cycles, new.....	\$10.95
Ground Plane ant, COA6689, 72.5 mc ¼ wave vert inst. bk & all fittings, uses 52 ohm cable, new.....	\$7.95
Vertical Antenna, collapsible, 25', spun alum. pulled by stainless steel cable on pulleys. Mtg clamps incl....	\$9.95
ARC-5; BC-458 new w./tubes, SSB conv.....	\$9.95

REX RADIO SUPPLY 84 Cortlandt St., N.Y. 7, N.Y.

Advertisers Index

Alden Co.	41
Allied Radio Corp.	64
Altronics-Howard	62
Alvaradio	47
Amber Industrial Corp.	58
Central Electronics, Inc.	43
Clegg Laboratories, Inc.	53
Cosmos Industries	48
Cushcraft	59
Dow-Key Co.	58
EICO	2
Excello	62
Fair Radio Sales.....	59
General Electric	5
Globe Industries, Inc.	59
Graham Co.	62
Ham-Swap	62
Hi-Par	56
International Crystal Mfg. Co. Cover 2, 1	
McRae-Smith	57
Metro Electronics Corp.	56
Mini-Products, Inc.	45
Neil Co., The	46
Peterson Radio Co., Inc.....	Cover 3
P & H Electronics, Inc.	51
Precision Communication Assoc... ..	57
Radio Amateur Callbook, Inc.	6
Radio Bookshop	60, 61
Rex Radio Supply Co.	62
R-F Wattmeter	57
Solar Electronics Corp.	55
Spera Electronics Supply	53
Standard Parts	47
Stellar	39
Subscription to 73.....	54
Tapetone, Inc.	49
Telrex	7
TMC	63
Vesto	49
Vibroplex Co., Inc.	57
73 Subscription	54

• HAM-SWAP •

The FASTEST way to buy, sell or swap Ham Gear!

\$1 a year brings you 24 issues of bargains galore—PLUS the "Fastest Way in the World" to profitably dispose of your old or excess parts and equipment. FREE ad certificate and latest edition returned immediately if you send \$1 NOW to:

HAM-SWAP, Inc., 35-F East Wacker Dr., Chicago 1, Ill.

A Merry Christmas

and Happy QSO's for 1961

Peace

God Jul

Zalig Kerstfest

Joyeux Noel

Fröhliche Weihnachten

Feliz Navidad

Ale Kalikimaka

Bum Natale

Feliz Natal

Peace on Earth

The Technical Materiel Corporation

MAMARONECK, NEW YORK
in Canada: TMC Canada Ltd.,
Ottawa, Ontario



Holiday Greetings

*to all our Ham Friends
the world over*

from the

ALLIED Ham Shack—



W8CZE
Jack Schneider



W9BHD
Joe Huffman



W9WHF
Jim Sommerville



W9HLA
Joe Gizzi



W9VOB
Burt Fischel

and from the rest of the gang at Allied

W9BUD Larry Blostein
K9BYD M. Fleischman
W9CCW Rudy Ackermann
K9CDJ Joel Bolker
W9DCB Milt Fojtik
W9ECC Bob Gumm
K9EIL Don Saxon
W9EXQ Chuck Stone
K9GSB Norman Eastman
K9GXK Jack Wolfson
K9HLV R. Archambeault

K9HOB Don Wisniewski
KN9IJO Mike Heinrich
K9KEF Leon Hearn
K9KVQ Rodger Nordlund
KN9KWT Bob Oatley
K9KWY Sherwin Berger
K9MDF Jack Marcus
W9MHB Goodwin Mills
W9QBB Tasker Day
KN9RID Lloyd Mast

W9RND Jack Matin
W9SFW Lou Dezettel
W9SIA Franklin Swan
W9THG Leo Borek
W9VHI Don Kobiljak
W9VHS Tony Marcello
W9WOV George Bercos
W9ZJU "Doc" Towler
HH2LR Louis Roumain
W9VES Phil Simmons
W9ZOA George Duffy



serving the Amateur since 1921

ALLIED RADIO

100 N. WESTERN AVE., CHICAGO 80, ILL.

*Unconditionally
Guaranteed*

... the Mark
of the Maker's
Confidence in
His Product



PRs are built to PERFORM . . . under good conditions and bad. They have that extra measure of stability and dependability BUILT-IN . . . that plus of rugged precision that guarantees years of unflinching service. Thousands of pre-war PRs are still performing . . . *still right on the kilocycle!* No wonder PRs can be UNCONDITIONALLY GUARANTEED.

40 and 80 Meters, PR Type Z-2, ± 500 Cycles.....	\$2.95 Net	6 Meters, PR Type Z-9A, 50 to 54 Mc., ± 15 Kc.....	\$6.95 Net
Third Overtone, PR Type Z-9A, 24,000 to 24,666 and 25,000 to 27,000 Kc., ± 3 Kc.....	\$4.95 Net	Citizens Band, PR Type Z-9R, .005%	\$2.95 Net



PR Crystals



USE **PR** AND KNOW WHERE YOU ARE

PETERSEN RADIO COMPANY, INC.
2800 W. BROADWAY • COUNCIL BLUFFS, IOWA

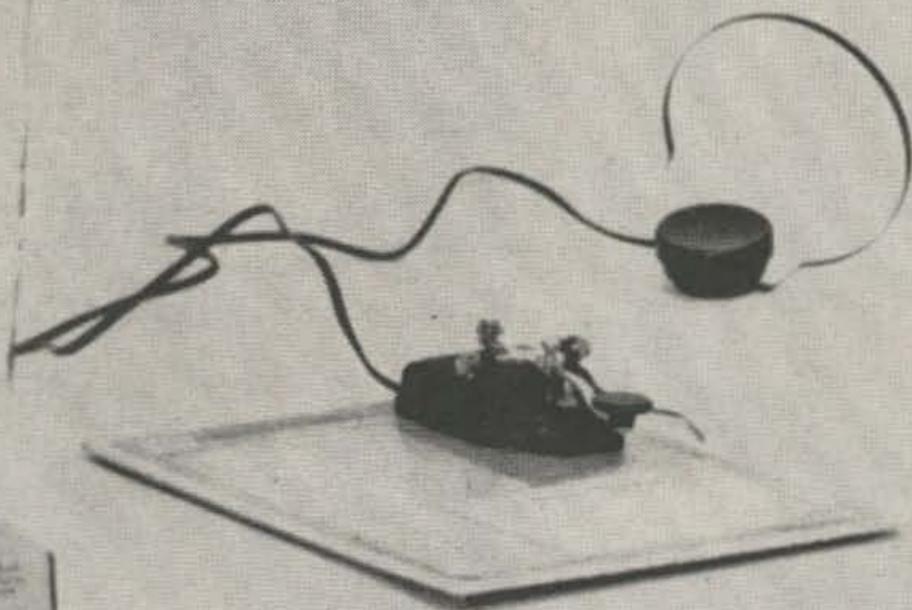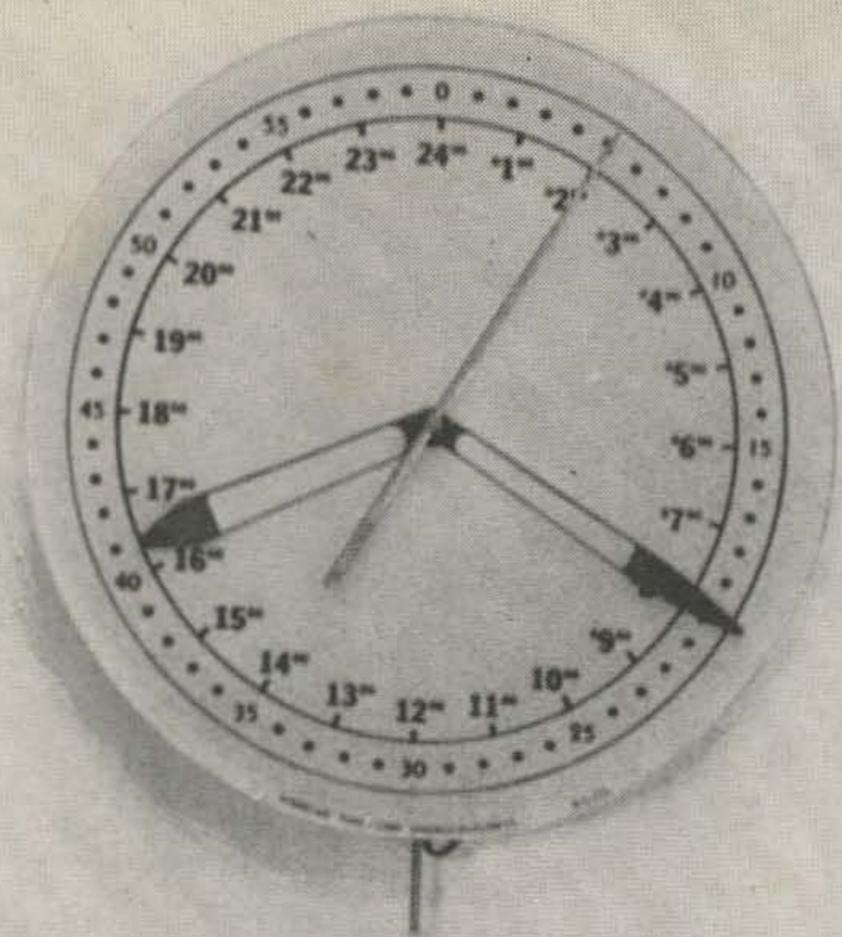EXPORT SALES: Royal National Corporation, 250 W. 57th Street, New York 19, N. Y., U. S. A.



12NSD

