


NEW!

RANGER II

NOW COVERS 6 METERS IN ADDITION TO 160, 80, 40, 20, 15, 10



*75 watts CW input
... 65 watts AM!*

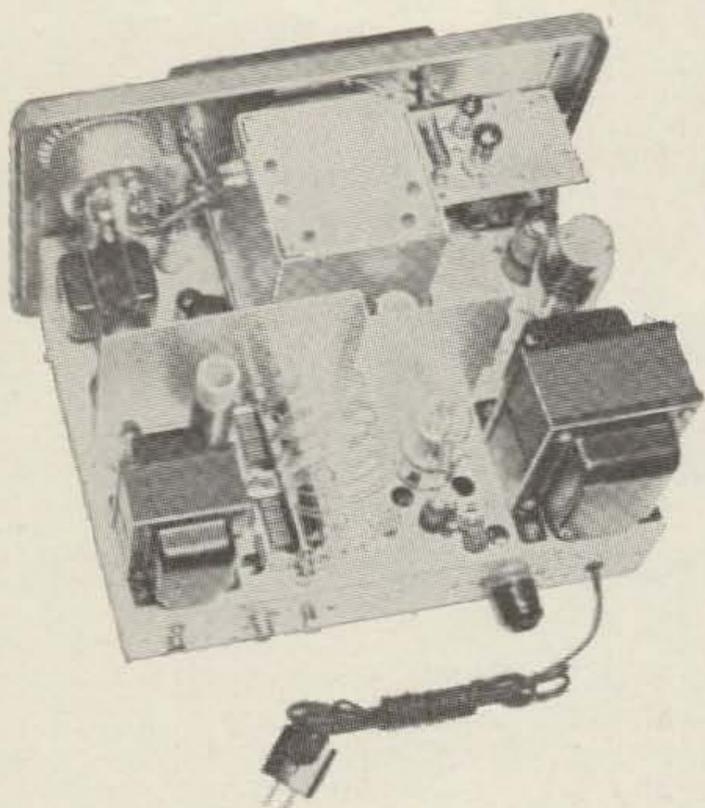

Now—a new version of the popular Viking “Ranger” . . . the “Ranger-II” Transmitter/Exciter! Completely self-contained in a handsome re-styled cabinet, the “Ranger II” now covers 6 meters! As a transmitter, the “Ranger II” is a rugged and compact 75 watt CW input or 65 watt phone unit. Pi-network coupling system will match antenna loads from 50 to 500 ohms and will tune out large amounts of reactance. Single-knob bandswitching on six amateur bands: 160, 80, 40, 20, 15, 10 and 6 meters—built-in VFO or crystal control. Timed sequence (grid block) keying provides ideal “make” or “break” on your keyed signal, yet the “break-in” advantages of a keyed VFO are retained.

As an exciter, the “Ranger II” will drive any of the popular kilowatt level tubes, provides a high quality speech driver system for high powered modulators. Control functions for the high powered stage may be handled right at the exciter—no modification required to shift from transmitter to exciter operation. Nine pin receptacle at the rear brings out TVI filtered control and audio leads for exciter operation. This receptacle also permits the “Ranger II” to be used as a filament and plate power source, and also as a modulator for auxiliary equipment such as the Viking “6N2” VHF transmitter. Unit is effectively TVI suppressed . . . extremely stable, temperature compensated built-in VFO gives you exceptional tuning accuracy and velvet smooth control. Complete with tubes, less crystals, key and microphone.

Cat. No. 240-162-1 Viking “Ranger II” Kit **Amateur Net \$249⁵⁰**

Cat. No. 240-162-2 Viking “Ranger II” wired and tested **Amateur Net \$359⁵⁰**

New Catalog

Write today for our newest Amateur Catalog! Available now—contains photos, schematics, and detailed specifications!



FIRST CHOICE AMONG
THE NATION'S
AMATEURS



Viking

E. F. JOHNSON COMPANY • WASECA, MINNESOTA

Silicon Rectifiers	Henry Cross WIOOP	6
How not to pop 'em, a lesson for hams and engineers alike.		
Tuning Bypass Condensers	Jim Kyle K5JKX/6	8
How to make a bypass bypass at the VHF's.		
Simplescope	Harvey Pierce WØOPA	10
Perchance the title may give this one away. You need one. Build it.		
VFO Chirp VS 6AU6	Al Brogdon K3KMO	20
Several VFO's use a 6AU6. Lousy choice, try a 6AH6 instead and see.		
Console	Beryl Dassow W9HKA	22
If you're going to be obstinate enough not to buy an Alden Hambench, then build this.		
Class B Modulators	Larry Levy WA2INM	28
We'll print anything.		
Eye for Resonance	Roy McCarthy K6EAW	30
How confounded simple can a GDO get? This is how simple, that's how.		
Break-in A la Transwitch	Ernest Austin W7AXJ	33
Complete station control unit, transistorized.		
Environmental Testing	Joseph Leeb W2WYM	36
Be nice to surplus gear, it has been through a lot.		
Band Edge Marker	Charles Berner WA2HRZ	37
A 3.5 mc crystal calibrates your receiver on all ham bands.		
Tell The World	J. Kyle K5JKX/6	39
Ham radio needs publicity, here's how to go about it.		
Zero Shift Keying	Kyle K5JKX/6	42
A new idea, presented first in 73. You'll be hearing more about this.		
Cross-Polarized Beam	George Messenger K6CT	48
A new approach to diversity transmission and reception.		
Crystal Oscillators	Staff	50
This is the Big Technical article. You'll find it interesting.		
Propagation Charts	Dave Brown K2IGY	64
Why a 73 Page Magazine Is Impossible	Wretched Coward K2PMM	72
or: further developments of the KW Transistor Transmitter.		

Misc.:

Editorial de W2NSD	2
Club Subscription Rates	4
Snap Bushings	20
Letters to Editor	29, 49, 63, 68, 69
Pi nets	38
Typical 73 Subscriber Shacks	46
SX-101A Note	49
MARS Technical Broadcasts	63
Ham Headlines	66
New Books	66

Staff:

editor-publisher	Wayne Green W2NSD
publications manager	David Fish
associate editor	Don Smith W3UZN
associate editor	Jim Kyle K5JKX/6
associate editor	Marvin Lipton VE3DQX
associate editor	Charles Spitz W4API
subscriptions	Mrs. Green
transportation	needs paint
printing	O'Brien Superban Pressers
Western Representative: Jim Morrisett WA6EXU	
Box 847, Reseda, California. Ph: DI 5-2077	

COVER: Mosaic.

73 Magazine is published monthly by Amateur Radio Publishing, Inc., 116 Main Street, Norwalk, Connecticut. Business Office, 1379 East 15th Street, Brooklyn 30, New York. Telephone: DE 6-8880. Subscription rates: U.S.A. and possessions, APO, FPO, Canada and Mexico; one year \$3.00; two years \$5.00; three years \$7.00. Foreign: one year \$4.00; two years \$7.00. Second-class postage paid at Norwalk, Connecticut. Printed in the U.S.A. Entire contents copyright 1961 by Amateur Radio Publishing, Inc. Postmaster: Please send form 3579 to 73 Magazine, 1379 East 15th Street, Brooklyn 30, New York.

... de W2NSD

(never say die)

Get Rich Quick

Nonsense, of course. Well, as mentioned an issue or so back, I'm anxious to make some information available at low cost that might not otherwise see print. We're getting set up to publish small booklets, between ten and twenty pages long, right at our 73 office. This will keep costs down, keep me out of trouble running the offset press and Varsityper, and make it possible to make these available at a low price.

This will also make it possible for us to pass along a good piece of the income from such a venture to the author of the booklet. I figure we can put out the booklets for 50¢ to 75¢ each and return 20% of this to the author. This means up to \$200 for every thousand booklets we sell. OK, stop fidgeting. I'm open for suggestions as to the subjects. One benefit of publishing small booklets is that they can cover one particular subject quite thoroughly and don't take the year or so of work that a regular book does.

Suggested subjects: Nuvistor circuits compendium and discussion; De-noising cars; Mobile antennas; Conversion of Motorola FM gear for ham use; Complete receiver construction articles; Antennas for 1296 mc; How RTTY Works; RTTY Converters; What TT printers to get and where to get 'em; How to keep a ham club alive and kicking; Roster of 432 mc stations; Who's Who on 1296; etc. If you can think of a subject that you think 1000 people will pay 50¢ to read about then check in to make sure that you aren't racing someone else on the same subject.

Once published, we'll keep the booklet in print as long as it continues to sell. We'll push it in 73, you may be sure, and we'll not only sell it directly but have it on sale in as many radio parts distributors as possible. Most booklets should sell well over 10,000 copies . . . none of the seven books I've produced in the field have sold less!

Bulletins

It is probably bad policy to tell everyone what we're planning for the future, but I'd like to see the reaction and a little discussion of it might just get someone thinking.

Reciprocation

Senator Barry Goldwater has just introduced a bill into Congress to permit reciprocal licensing of amateurs. It was referred to the Committee on Commerce. Please write immediately to your representative in Congress asking for support of Senate Bill S.2361. Here is your chance to be a hero, don't muffle it through laziness or disinterest. Sit down and write. This could have far reaching results toward preserving our frequencies in the long run.

Our policy, right from the start, has been not to have any monthly activity columns in 73. There is no notion of changing that. We've proven rather conclusively that there is no need for more columns. But there is a need for communications between fellows with similar interests. RTTY never got off the ground until there was a bulletin keeping everyone in touch with the happenings in the field and serving as a clearing house for operating news and technical discussions.

At present 73 is subsidizing the "73 News," put out by Marvin Lipton VE3DQX. This is a monthly paper which is sent out to all of the editors of ham club bulletins around the country (and the world) to give them news flashes of interest to help them with their bulletins. If the number of club bulletins coming in here with notes of credit to "73 News" is any indication, Marvin is doing a splendid job.

Undoubtedly there is a need in many other ham fields for a bulletin to exchange information. It is a lot of work to put out something like this. I've been through it myself, so I really know what it is all about. I started mine with a circulation of 50 on a hand mimeo and wound up with over 2500 three years later using offset printing. This was what got me into the publishing field originally and look what happened! With that warning I suppose I have discouraged you.

Though we have over two hundred thousand hams in the country, there are only a few who have the drive to take things into their own hands and do something about problems. We have a need for communications in many fields and a lot of good would be done if people were to suddenly decide to start a bulletin in that field. Note: most everyone will cooperate with you and send in information, but there will be a few who will fight you tooth and nail just on general principles. They want to know who the hell you are to set yourself up as the big cheese, etc.

Ditto and mimeo machines are quite inexpensive in used shape and are invaluable to the bulletin producer. It is amazing how these things grow. I now have a small mimeo, a large mimeo, a Ditto, five different types of typewriters and a Varsityper. Next comes an offset press, a stapler, and a large paper cut-

"Terrific!...Unbelievable... Best rig - ever"!

Here are a few unsolicited comments from owners of Clegg VHF equipment



Clegg Zeus VHF Transmitter FOR 6 AND 2 METERS

A highly efficient, 185 watt AM, high power VHF transmitter for full coverage of the amateur 6 and 2 meter bands and associated Mars frequencies.

Automatic modulation control with up to 18 db of speech clipping provides magnificent audio with "talk power" greater than many kilowatt rigs.

This beautiful unit with its ultra-stable VFO is the ultimate in VHF equipment for amateur and Mars operation.



99'er Transceiver FOR 6 METERS

This completely new transmitter-receiver is ideal for both fixed station and mobile operation. Small in size, low in cost, and tops in performance, the 99'er offers operating features unequalled in far more costly equipments. The double conversion superhet receiver provides extreme selectivity, sensitivity and freedom from images and cross modulation. The transmitter section employs an ultra-stable crystal oscillator which may also be controlled by external VFO. An efficient, fully modulated 8 watt final works into a flexible Pi network tank circuit. A large S meter also serves for transmitter tune-up procedure.

From Ohio:

"... I am a quality control supervisor with a leading electrical manufacturer and this Zeus transmitter is to me the finest piece of workmanship that I have ever purchased or inspected..."

From New Hampshire: Richard E. Hayes, K8UXU

"... We feel that our new Zeus is the best thing that ever happened to us since we have been in ham radio (5 years)..."

From Florida: Hazen & Beatrice Bean, K1JFQ

"... We are well satisfied with the results of this unit as we have worked forty DX contacts in little more than three hours on May 23, 1961, including six new states which we were unable to work in the past two years with a 120 watt, 6 & 2 transmitter of a different mfg...."

From California: Jack Edlow, K4YIW

"... Never before have I been more pleased with a piece of gear than I am with my Zeus. In two days I have worked 24 states with several contacts in each, (phone) on six meters. And the signal reports—yow! For the most part unbelievable..."

From Pennsylvania: Jeanne & John Walker, WA6GEE

"Words cannot express the pleasure and performance of ZEUS. I have worked 5 states 5-9, plus I have given you \$1,000,000 advertisement..."

From Puerto Rico: Dr. A. Schlecter, K30EC

"... I want to inform you of the excellent results obtained with the Zeus Transmitter I bought one month ago. Taking advantage of the band opening, I have been able to work up to the present thirty-eight states, including California..."

From New Jersey: Pedro Fullana, KP4AAN

"... I would like to tell you I am more than delighted with the operation of the Zeus. Have had nothing but good reports from other Ham's..."

From Georgia: Donald E. Gillmore, WA2QCQ

"... This set is terrific. I've had terrific results with it. It's the best rig—ever."

George E. Missback, K4QOE


K8CHE in Ohio tells about 99'er

"... with the 99'er haywired in from a four element beam, through 100 feet of coax, through a matching network, through a length of 72 ohm twinlead, and then through a length of 300 ohm twinlead to reach the 99'er, we could read the Michigan stations Q5! and back through the above haywire we were able to put 4.4 watts into the antenna as measured by a RF ammeter!..."

Ken Phillips, K8CHE

Clegg LABORATORIES

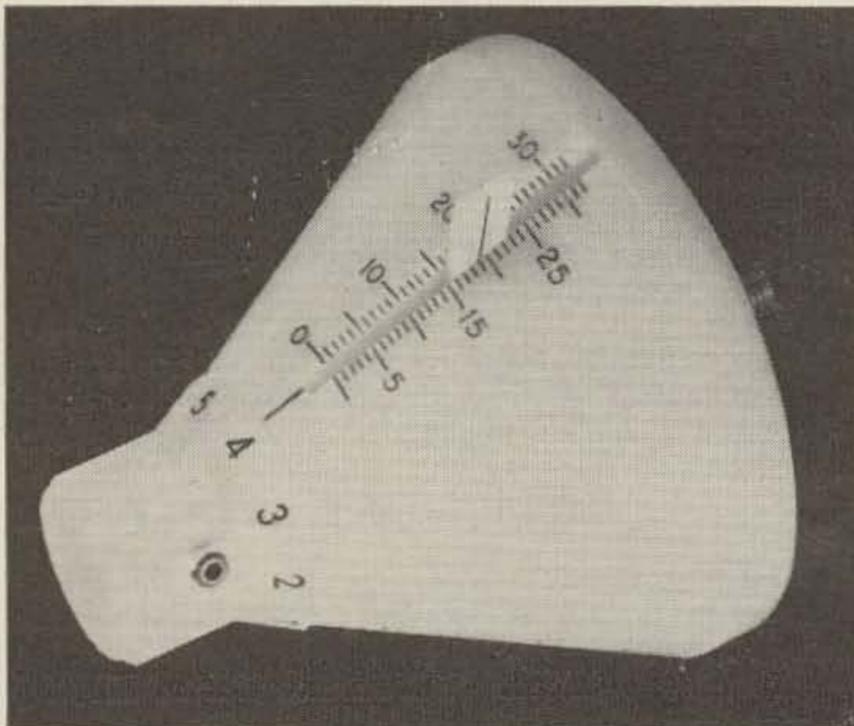504 ROUTE 53, MT. TABOR, NEW JERSEY • OAKWOOD 7-6800



Gentlemen:

To answer your request . . .
Here is our NEW COUNTER DIAL.

This dial was especially designed for panel mounting and manual operation of Jennings vacuum variable capacitors. It can be used with any Jennings variable capacitor requiring less than 32 turns of 1/4 28 NF adjusting screw to accomplish variations from minimum to maximum capacitance.

Constructed of shock resistant Delrin the dial is marked from zero to 32 for visual relative indication of capacitance. Since it replaces the standard turning head and mounts to the front of the panel a considerable saving of space is effected inside the chassis. In addition the translucent material of the dial permits rear lighting through the panel for easier reading of the dial markings.

Amateur net price \$14.00 each,
f.o.b. San Jose, California.

Descriptive literature is available
on request.

RELIABILITY MEANS VACUUM/VACUUM MEANS

Jennings®

970 McLaughlin Ave., San Jose, Calif. • Phone CY 2-4025

ter (I have a small one).

Once you have the machinery you can start by mailing your first thin bulletin to those few chaps you know who are interested in the field. Ask them all to recommend more readers. By the time you are putting out the third or fourth issue you will have most everyone on the list.

What fields are there? Lots come to mind right way. Ham TV, FAX, 220 mc, 432 mc, 1296 mc, contests, 2M SSB, 6M SSB, 75M DX, 160M DX, plus bulletins on VHF, SSB, awards, DX, etc., which would stress different aspects than are being covered by presently published bulletins. You can probably think of some that I have missed.

You'll never get rich putting out a bulletin, but you will have more fun than you've ever thought possible. I'll help anyone that wants to get started in any way I can (I'm short of money right now, but maybe by next year, if a few more advertisers will start using 73, we'll be in shape to even help that way). We'll give you every hand we can through the pages of 73 also as long as you don't tie up too firmly with other publications.

Changes

The result of the poll on our diagrams was in favor of the gray background. We'll try to get the engravers to make the gray lighter and the diagrams larger. I get just as distressed as as anyone when I see how small some of them come out. Absurd. We topped ourselves last month with the construction details on the Impedance Bridge. I'm having larger copies made of them for anyone interested in building the instrument. These should be available any day now for \$1. I'd like to send 'em out free, but we're constantly shying away from bankruptcy and I don't want to topple us. By next year we should be able to do things like that for the fun of it. We will if you'll keep needling those non-advertisers.

(Turn to page 69)

Club Subscriptions

As announced a few months ago, clubs may send in group subscriptions at the rate of \$2.50 per one year subscription in groups of five or more subscriptions. These subs must start with the next published issue and be for just one year. Orders for back issues should be sent in separately. By simplifying the procedure we can offer this reduced rate.

The regular subscription rate is \$3 per year; \$5 for two years; \$4 per year for DX operators outside North America. All back issues are 50¢ each. Send your name, call and address to 73 magazine, 1379 E. 15th St., Brooklyn 30, New York. Include money.

your choice of 2 GREAT **EICO**[®] TRANSMITTERS...

designed
by Hams...
for Hams...

to the highest
Ham standards



**90-WATT
CW TRANSMITTER* #720**
Kit \$79.95 Wired \$119.95
*U.S. Pat. #D-184,776
"Top quality"—ELECTRONIC
KITS GUIDE
Ideal for veteran or novice.
"Clean" 90W CW, 65W AM-
phone with EXT plate modu-
lation. 80 through 10 meters.

**60-WATT
CW TRANSMITTER #723**
Kit \$49.95 Wired \$79.95
"Compact; well-planned lay-
out. Clean-sounding, abso-
lutely hum-free carrier;
stable." — ELECTRONICS
WORLD.
Perfect for novice or ad-
vanced ham needing low-
power standby rig. "Clean"
60W CW, 50W AM-phone with
EXT plate modulation. 80
through 10 meters.



New!
**VARIABLE
FREQUENCY
OSCILLATOR
(SELF-POWERED)
#722**
Approaches
crystal stability.
80 through
10 meters.
Kit \$44.95
Wired \$59.95

**HIGH-LEVEL
UNIVERSAL
MODULATOR-
DRIVER #730**
Kit \$49.95 Wired \$79.95
Delivers 50W undistorted audio for
phone operation. Can plate-modu-
late transmitters having RF inputs
up to 100W. Unique over-modula-
tion indicator. Cover E-5 \$4.50.

**DC-5MC
LAB & TV 5"
OSCILLOSCOPE
#460**
Kit \$79.95
Wired \$129.50
5" PUSH-PULL OSCILLOSCOPE #425
Kit \$44.95 Wired \$79.95

New!
**CITIZENS BAND
WALKIE-TALKIE #740**
Complete with re-
chargeable battery
and charger. 9 tran-
sistors, 1 diode. Full
superhet. U.S. made.
Kit \$54.95
Wired \$79.95

**GRID
DIP
METER
#710**
Kit \$29.95 Wired \$49.95
Includes complete set of coils
for full band coverage. Continu-
ous coverage 400 kc to 250 mc.
500 ua meter.

**DYNAMIC
CONDUCTANCE
TUBE
& TRANSISTOR
TESTER #666**
Kit \$69.95 Wired \$109.95
TUBE TESTER #625
Kit \$34.95 Wired \$49.95

**CITIZENS
BAND
TRANSCIVERS**
Superhet; pre-
aligned xmitter
osc; match dif-
ferent antennas
by variable "pi" network. Single
& multi-channel models.
From Kit \$59.95 Wired \$89.95

**PEAK-TO-PEAK
VTVM #232**
& exclusive
***UNI-PROBE[®]**
Kit \$29.95
Wired \$49.95
VACUUM TUBE VOLTMETER #221
Kit \$25.95 Wired \$39.95

**RF SIGNAL
GENERATOR
#324**
(150kc-435mc)
Kit \$26.95
Wired \$39.95
**TV-FM SWEEP GENERATOR
& MARKER #368**
Kit \$69.95 Wired \$119.95

*U.S. Pat. No. 2,790,051



3300 Northern Boulevard,
Long Island City 1, New York
Export Dept., Roburn Agencies Inc.,
431 Greenwich St., N. Y. 13, N. Y.

EICO, 3300 N. Blvd., L.I.C. 1, N. Y.
 Send free Catalog & name of
neighborhood distributor.
 Send free "Short Course for
Novice License." Send
36-page STEREO HI-FI GUIDE:
25c enclosed for postage
& handling.

Name.....

Address.....

City..... Zone..... State.....

Add 5% in the West.

73-1

ENGINEERS: Excellent career opportunities in creative electronics design. Write to the Chief Engineer.

Silicon Rectifiers

and how not to blow them up

Hank Cross W100P
111 Birds Hill Avenue
Needham 92, Massachusetts

MANY hams and engineers that I know are mad at silicon power rectifier diodes. They tried them once and the results were disastrous. (The engineers are madder, because they thought they knew what they were doing). Nowadays the diodes are better and cheaper, and people are still popping them.

What Not to Do

If you own a slide-rule and a scope, plus lots of diodes, you can work out how to get away with almost anything in the way of a circuit. For the simple way out, avoid:

Choke Input Filters. When you open transformer primary, diodes get voltage surge, blow up.

Half Wave rectifiers, except direct off the line. That unloaded transformer is murder on

the backswing.

What to Be Sure to Include

A Series Resistor. For 115 volt rectifiers, ten ohms seems adequate for all commercial diodes. Transformer secondary dc resistance should be at least six ohms per hundred volts, add some if there isn't enough.


A Fuse. Secondary fusing (NOT a slo-blo) is smartest. Even 83's put out less into a short. And transformers cost money.


Enough peak inverse rating to do the job. Most small silicon diodes die of back voltage. My "115 volt" line went up to 138 without help from a variac one night: that's 200 peak or 400PIV for an ac-dc rectifier. My silicons didn't go, but a 500 volt electrolytic spread Reynolds Wrap all over the shack! (The power co. said it was a defective regulator). If you replace a 5Y3, 5U4 or 6X5 with silicon diodes, do not be surprised if the transformer runs hotter. Adding series resistance to replace the "plate resistance" (about 200 ohms in the case of a 5U4) will cool things down, if you want.

Ratings


Figure 1 shows the "plate characteristic" of a silicon diode—almost any diode. A volt in the right direction makes amperes flow; a good diode has a fraction of a microampere of leakage at room temperature in the reverse direction, up to the "avalanche" voltage, which depends on the diode and the temperature. Lower temperature gives less leakage and LOWER breakdown voltage; higher temperatures (up to that of melting solder at or near the junction) give greatly increased leakage, higher avalanche voltage, and slightly less forward drop (at least for low forward currents).

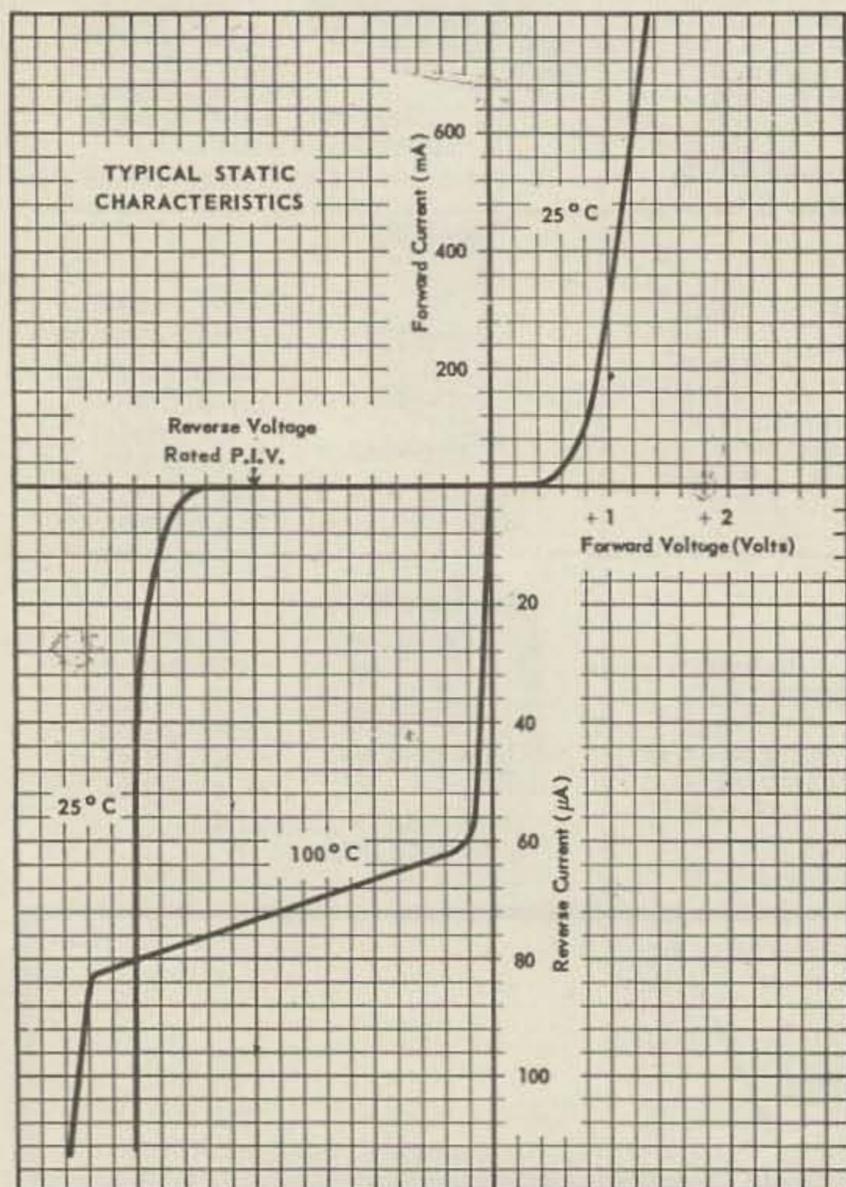The surge and forward current ratings are set so as not to melt the working parts; the rated PIV (peak inverse voltage) is picked so that it's below the avalanche voltage at minus 65C, even (a comforting thought). For some reason (such as fairly fancy testers) diode manufacturers don't put in a factor of




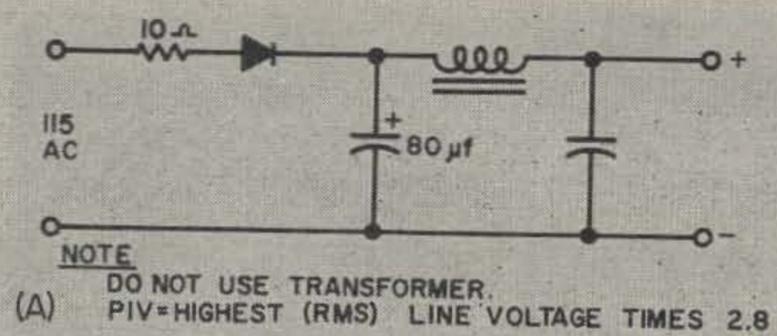

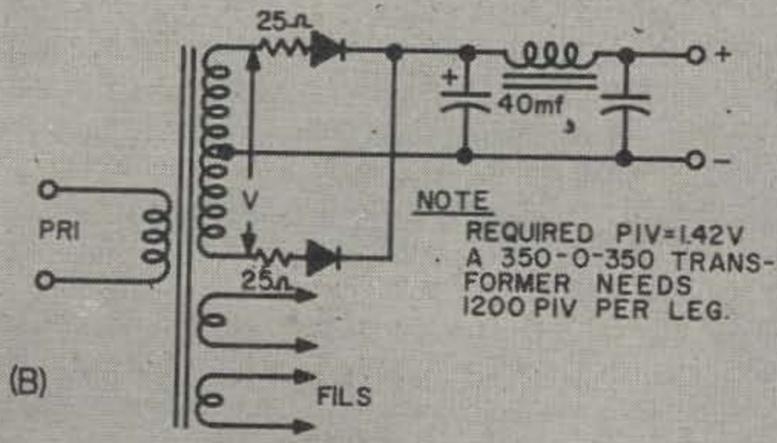
NOTE
DO NOT USE TRANSFORMER.
(A) PIV=HIGHEST (RMS) LINE VOLTAGE TIMES 2.8



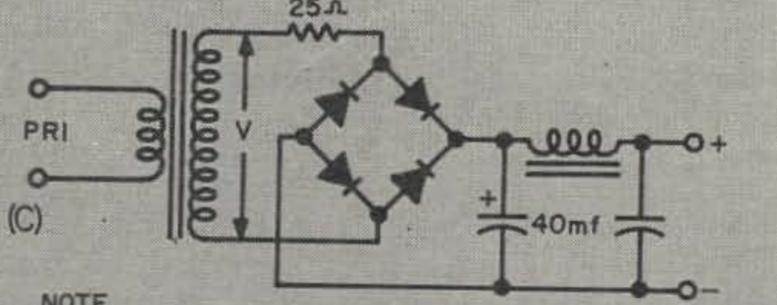
NOTE
REQUIRED PIV=142V
A 350-0-350 TRANSFORMER NEEDS 1200 PIV PER LEG.



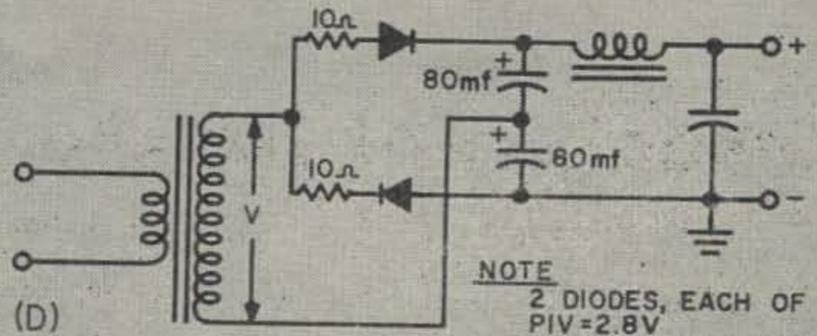NOTE
4 DIODES, EACH OF PIV TIMES 1.42
A 220 VOLT TRANSFORMER NEEDS 4-400 PIV DIODES, PUTS OUT ABOUT 280V.



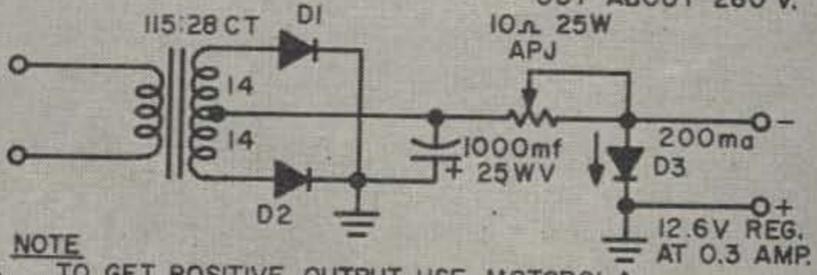NOTE
2 DIODES, EACH OF PIV=2.8V
A 115:115V ISOLATION TRANSFORMER NEEDS 2-400 PIV DIODES, PUTS OUT ABOUT 280 V.



NOTE
TO GET POSITIVE OUTPUT USE MOTOROLA IN 1353 REGULATION AND DIODES WITH ANODE TO BASE.

The bridge rectifier in 2-C could use a 110 to 220 volt isolation transformer (sold as a 220 to 110, most likely) to give 280 volts at 300 ma continuously with a 100 watt transformer, such as Stancor P-6383, and a 125 mfd input capacitor.

Figure 2-D shows how to get 280 volts dc from only two diodes and a 115 to 115 isolation transformer. A 50-watt unit is good for about 125 ma. Popular in modern TV sets.

In any of the above circuits, more output voltage than the example requires either higher PIV diodes or more in series. The price of diodes above 600v is quite high; at present it is cheapest to buy 400 or 500v units and put them in series.

Replacing Seleniums

The rules are simple: a six-plate selenium stack equals a 400 PIV silicon diode. An eight-plate stack should be replaced by a 500 or 600 PIV silicon. In choke-input circuits using seleniums, where the selenium rectifiers have "aged" but are not burnt, put the silicon diodes across the seleniums, and let the seleniums soak up voltage surges to protect the silicon junctions.

Heat Sinks

The bolt-on silicon diodes are used for higher average currents, but in many cases there is no need to bolt them to anything better than a solder lug. Rather than use mica washers and risk shorts, I prefer to bolt the diodes to individual plates of 1-16 in. aluminum and insulate these plates, such as with threaded ceramic standoffs. These cooling fins should usually be vertical. By picking circuits, it is often possible to run the diode cases at ground potential and avoid insulating, as in Fig. 2-E. The voltage regulator or "Zener" diode is what gets hot, so pick the polarity to go with your diode.

... W100P

safety—you have to do that. A term, "maximum allowable RMS voltage" shows up on some rating sheets: it usually means that you could test the diode into a resistor at that voltage, but in any real circuit half as much voltage would be excessive, so forget it.

- For a GE 1N1490 (to pick a type that I have used a lot of) the ratings read:
- Maximum allowable PIV 400 volts
 - Maximum allowable RMS voltage 280 (see remarks above!)
 - Maximum allowable continuous reverse dc voltage 400
 - Maximum allowable dc output at 125C ambient 250 ma
 - Maximum allowable dc output at 25C ambient 750 ma
 - Maximum allowable one-cycle surge current 15 amps
 - Max. full-load forward drop 0.55 volts
 - Max. leakage current, full-cycle av at 125C 0.3 ma

The power lost in leakage and in forward drop are about the same at 125C, which is hotter than I would run any silicon diode for any length of time beyond a few seconds.

What this means can be shown by some circuits. Figure 2 A using a 1N1490 will take 117 ac and give about 150 dc at up to 500 ma.

In circuit 2-B you'd need three of these diodes in series for each side of a 350-0-350 volt transformer, and get about 400 out under the transformer's rated load . . . six in all for 300 mils out of an old TV transformer.

Tuning Bypass Capacitors

Jim Kyle K5JKX/6
1851 Stanford Ave.
Santa Susana, Calif.

ESPECIALLY in the VHF regions and above, bypass capacitors can prove troublesome in both receivers and transmitters. Almost all commercially produced capacitors have some inductance too, and in addition the inductance of the capacitor leads becomes important at frequencies above 30 mc.

The purpose of a bypass capacitor is to be a short-circuit path for radio-frequency currents while isolating dc voltages from ground. Since inductance impedes the flow of ac, and the impedance of any given inductance increases with frequency, the inherent inductance of the leads and the capacitor itself produces an upper limit to the unit's effectiveness.

Conventional paper capacitors are almost useless for bypass purposes at any frequency higher than 500 kc; in the higher frequency ranges, disc ceramic capacitors are to be preferred since their flat-plate construction reduces inductance to a minimum. However, even these units are not usually recommended for use above 300 mc.

Normal construction practice for installing bypass capacitors is to make the leads as short

as possible to reduce any inductance contributed by them to an absolute minimum. As an example, a one-inch length of No. 20 wire has an impedance of 8 ohms at a frequency of 60 mc, and this 8-ohm impedance is enough to seriously upset the action of an otherwise-normal amplifier circuit.

Not so well known—although it was first described in 1948—is the fact that this lead inductance can be used to tune the capacitor to frequency, thus extending its use to frequencies higher than the normal limit and at the same time making its action more efficient than is otherwise possible.

For instance, a 470 mmfd capacitor with no inductance at all would have an impedance of approximately 6 ohms at a frequency of 50 mc. The same capacitor, if installed in a circuit with a total lead length of $\frac{3}{4}$ inch (say $\frac{3}{8}$ inch for each lead), would exhibit approximately 0.25 ohm impedance at the same frequency—a 25-fold reduction in impedance.


We said earlier that the upper limit for normal disc ceramic capacitors is in the neighborhood of 300 mc. By using the leads to tune the capacitor to series resonance, this limit can be extended upwards to more than 800 mc—enough to allow operation on another band.

Here's what happens: The inductance of the leads, and of the capacitor itself, is used to tune the capacitance to series resonance at the operating frequency. If circuit Q were infinite, the impedance at resonance would be zero; however, with circuit Q as low as 5 (and it's usually higher than this) the resonant impedance is still less than 0.25 ohm.

Inductance of the wire normally used for leads on disc ceramic capacitors is approximately 25 millimicrohenries per inch. If you like, you can plug this into the resonance formula and calculate length for yourself.

However, to save you the trouble, we've calculated the values for the range from 10 mc to 1000 mc, lead length from $\frac{1}{8}$ inch (the shortest usually found in practice) to 1 inch, and selected capacitor values from 5 mmfd to 0.01 mfd. The result is the graph shown in Fig. 1.

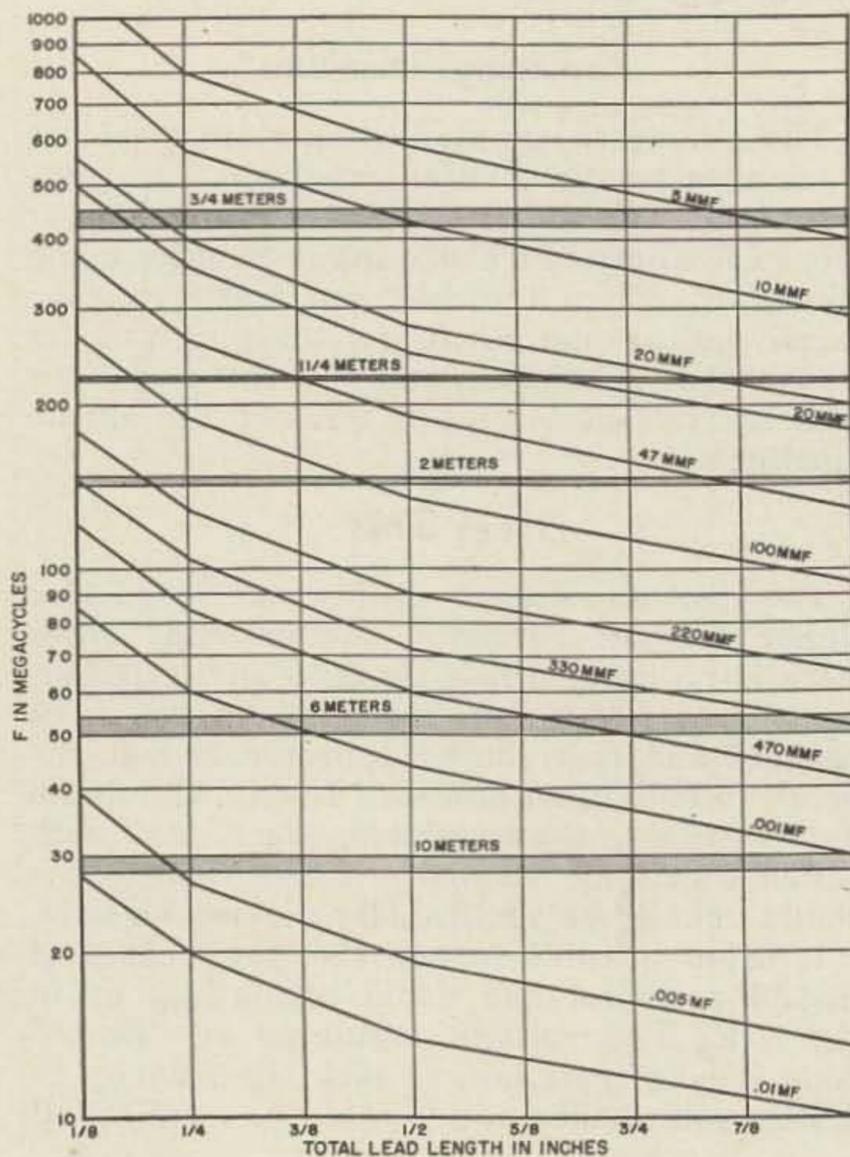To use the graph, first find your frequency on the left-hand scale. Reading across, you'll find several diagonal lines which intersect the frequency line. Each of these represents a usable value of capacitance. Read downward from the intersections to the lower scale to determine total lead length necessary for series resonance.



A couple of words of caution are indicated at this point. First, total lead length means the length of one lead added to the length of the other. If the graph says $\frac{5}{8}$ inch, one lead can be just $\frac{1}{16}$ inch long and the other $\frac{9}{16}$, or they can each be $\frac{5}{16}$ inch, or any other combination which totals $\frac{5}{8}$ inch. Secondly, since capacitance values are rarely more accurate than 20 percent, the best bet is to cut the leads a trifle longer than indicated and then to dip the unit to frequency with a GDO.

When possible, it's best to use the highest-value capacitor that can be resonated. The reason for this is that the effective bandwidth will be greater and the circuit will be more tolerant of errors.

For example, to quote directly from Volume 18 of the M.I.T. Radiation Laboratory Series, on page 326, if a 500-mmfd capacitor is resonated at 60 mc, the range over which its impedance is less than half an ohm extends from 57 to 63 mc. For a series-resonant 0.002 mfd capacitor, the corresponding range is from 50 to 72 mc.


This trick may also be used to help suppress harmonics and subharmonic feedthrough in transmitters, by deliberately using the smallest possible capacitor and resonating it very carefully to frequency. Because of the low capacitance and narrow series-resonant bandwidth, the capacitor will be effective only at operating frequency. At lower frequencies it will be a large capacitive impedance, and to harmonics it will look like an rf choke since a resonant circuit appears inductive at frequencies higher than resonance. In both cases, the result will be negative feedback to all signals except those at the chosen frequency, which will go through unhindered. This is especially applicable to screen bypasses, and can also be used for capacitance-coupling to pi-network output circuits. . . . K5JKX/6

RK34's

An excellent bargain in transmitting tubes is the RK34. These are low power dual triodes that make excellent exciters, drivers, multipliers, and finals. The plate dissipation is 10 watts, the maximum plate voltage is in the vicinity of 300 with a maximum plate current of about 80 ma. The full input power can be used up to 250 mc and it doesn't require too much drive. It is the ideal choice for a low power 6 or 2 meter final. The RK34 sometimes known as the VT-224 or 2C34 is available surplus for a few pennies. The probable reason for this is that it is an older type tube. I don't know the exact price that they sell for but I have seen them as low as 25¢ and once I have seen a few of them selling for 10¢. It would be hard to find a better bargain in transmitting tubes than this. . . .WA2INM

the MARK 2B SSB TRANSCEIVER

AVAILABLE NOW!
40 or 80 METERS

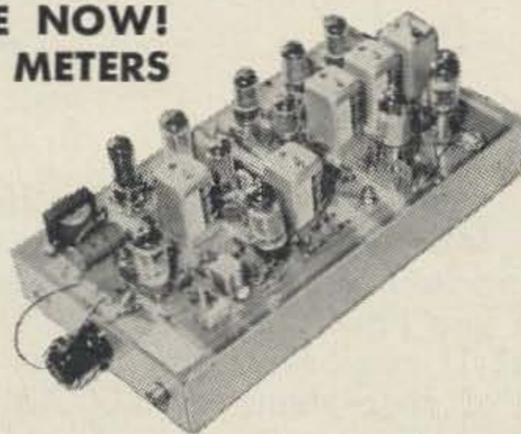

Originally described in the May, '61 issue of 73 Magazine (P. 57-58). This rugged filter type transceiver makes SSB available to all AT MODERATE COST. The Mark 2B is a single sideband transmitter and receiver delivering a conservative 2 watts output into a 50 ohm load. The basic unit is supplied on 40 or 80 meters, wired and tested. You may provide power supply, 455kc mechanical filter, tubes, carrier crystal and VFO or buy direct from us.

- NEW! Mark 2B basic unit wired and tested** \$97.50
- Kit of 11 premium tubes, including 4-12BA6, 1-12BE6, 1-12AU7A, 1-12AQ5, 1-12BY7A, 2-7360, 1-12AX7A (6V version available upon request)** \$19.75
- 455 KC Mechanical Filter (4.0 KC Bandwidth)** 44.00
- Carrier generating crystal (specify for USB or LSB)** 10.95
- NEW! Model 48 VFO operates 455 KC above desired output frequency. Includes 12AT7 dual triode as oscillator-cathode follower, 12BA6 buffer amplifier and OA2 regulator. Requires 260 to 325 VDC and 12/6V filaments. Specify 40 or 80 meters. Includes 4" calibrated dial.** \$39.50
- NEW! Model CM50 transistorized power supply. Supplies 300 VDC from 12-14 V battery. Plugs directly into transceiver. Plenty of Power for VFO also. Only 2 x 4 x 4 inches.** 29.50
- NEW! Model CM200 Transistorized power supply. Supplies 750 VDC at 200 MA from 12-14V input.** 49.50
- NEW! Model CM100A small and compact linear amplifier using 2-6146 tubes in parallel. Bandswitching for 40 or 80 meters. Conservative 100 watts output. Drives directly from Mark 2B, works into 50 ohm load. Less tubes. Requires 700-800 VDC for plates, 200 V screen and 45-50 bias. In rugged cabinet only 5 x 7 x 9 inches.** 57.95

All prices subject to change without notice.
Postage paid within the Continental U.S.

ORDER DIRECT FROM



CABRAL MOTORS INC.

Electro Mechanics Division

51 Victory Lane, Los Gatos, Calif.
Phone EL 4-8800

Harvey R. Pierce WØOPA
5372 E. Bald Eagle Blvd.
White Bear Lake 10, Minnesota

The Simplescope

Do you have to ask others "How's my modulation?" Do you have to wonder if you are modulating 100%? Do you know how much hum you have? If your speech clipper is clipping? If you have enough drive? If you aren't sure of your phone signals, AM or SSB, build the "Simplescope" and find out!

The name "Simplescope" comes because this is as simple as an oscilloscope circuit can get and still monitor AM, DSB, and SSB signals. I do not claim that this 'scope does a perfect job, or that it cannot be improved. My purpose is to present to you a proven, useable, simple, low-cost oscilloscope monitor. It works as well as many more expensive and more complicated instruments in telling you what your modulation is like, with a minimum of parts and expense.

The total cost shouldn't run over \$15.00, but I can't be very definite here, because prices vary so widely from catalogue to catalogue. And what do you have in your junk box? Many of the parts values are not critical, and substitutions can be made if you happen to have a substitute part hanging around. The most important item, perhaps, is the 'scope tube. The model illustrated used a 2AP1A. Latest prices I have for the 2AP1A is \$6.99. The 2AP1 will do equally well, and costs only \$3.50 from Barry Electronics. The rest of the parts show wide variations in price, too.

The simplification of this oscilloscope monitor lies in the elimination of all non-essential controls and features. This leaves four controls, two passive and two active. The two passive controls are the "Brilliance" and "Focus" controls that can be set once and then rarely touched. The two active controls are the "Function" switch and the "Width" control, that are changed occasionally. There are no vertical or horizontal centering controls because in my experience the undeflected spot of the average 2AP1 or 2AP1A is close enough to the center for average use. Vertical "Height" controls were left out because the ones that worked well were quite complicated. Amplifiers were left out because the sensitivity was more than adequate for the average ham transmitter of 60 watts or more. In fact, the model illustrated was used with great success on a 7½ watt AM transmitter on 10 meters.

This Simplescope is built in a standard 5 x

9½ x 3 chassis with an aluminum plate (not shown) to cover the "bottom" (now the side) of the cabinet. The power transformer is mounted outside at the rear to prevent its magnetic field from deflecting the spot. Don't try to mount it inside. The front end of the 2AP1 is held and framed by an old 2" meter case. Below it on the front panel are the "Function" switch and the "Width" potentiometer. The two knobs on the top rear are the "Brilliance" and "Focus" potentiometers. On the rear, above the power transformer is a terminal board for the audio input and the control circuit, protected by a perforated aluminum cage to prevent careless fingers from touching high-voltage circuits. Above this "cage" is the phono-type jack for the rf input.

Inside, the power supply components are on the bottom and most of the 'scope parts are at the top rear. The pictures do not give any detail here, as the details are obscured by the ten wires from the CRT base. The silicon diodes are mounted on a tie-point strip on the bottom rear. The two 8-mfd, 150-volt electrolytics are between two tie-point strips on the side, and two 1 mfd, 600 volt condensers on the bottom below them. The four bleeder resistors are mounted between them and a tie-point strip on the bottom, center, which also furnishes tie-points for the 117-volt leads for line cord, transformer, and switch. On top, under the handle, the hand-carved U-shaped saddle and aluminum strap that holds the rear of the 2AP1 can be seen. The CRT is wrapped with a strip of felt to protect it.

To save space and cost, no socket was used for the 2AP1. Instead, I used pin clips from two dismantled wafer sockets. Ten are needed. I soldered different colored wires to the lug part of each contact, slipping insulation tubing down over the wire, joint, and lug. These contacts were then pushed onto 2AP1 tube pins, with the lugs inward. Two wraps of ½" wide electrical tape keeps the wires in place and prevents twisting and shorting. Some octal sockets of the molded variety will give pin contacts that can be used with the lug in line with the contact part. Then the insulated sleeve can be pushed down over the tube pin too. While useable, these lugs take up a bit more room. In either case, the contacts and wires are put on CRT before it is installed. After the CRT is put in place, *with*


ONLY ONE KNOB TO TUNE THE 200V!

What's behind this knob? The Broadband Principle.

What is meant by a broadband transmitter? It is a transmitter with all stages designed to eliminate the need for manual tuning. Each stage has tuned circuits that are broadly resonant over a predetermined portion of the radio spectrum; for instance, 3.5 MC to 4.5 MC, 13.5 MC to 14.5 MC, etc. The signal is amplified in each broadband stage and is ultimately coupled from the plate of the final RF Amplifier to the antenna feed line through a broadband coupler.

WHAT'S IN A BROADBAND COUPLER? No copper sleeves, ferrites or any other "lossy" elements . . . just wire!

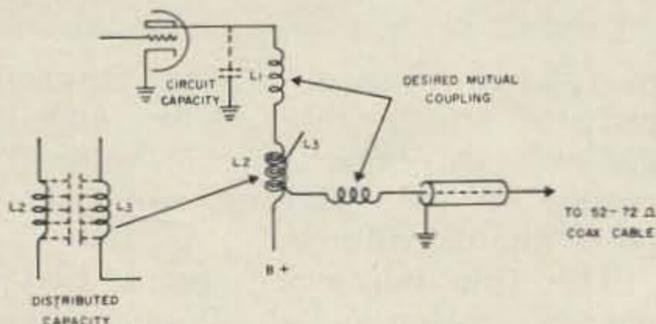There are no motors, servos or sensing circuits required to keep the 200V tuned up! The design of the broadband coupler does the job for you. It works like a transformer with a primary and secondary.



The primary L_1 L_2 is resonant at the high frequency end of the desired passband. Part of the secondary L_3 L_4 is wound bifilar with part of the primary. The bifilar winding has a distributed capacity between the wires. This capacity appears as a series resonant circuit with L_4 at the low frequency end of the desired passband. By controlling the size of the bifilar winding and the mutual coupling between L_1 and L_4 , it is possible to show the amplifier plate an essentially constant load impedance across the desired passband.

Write for 200V brochure for more detailed specifications.

EFFICIENCY? As long as the tube sees the proper plate load impedance, it will deliver power to that circuit. If this impedance is equal to that produced by a normally tuned and loaded circuit and the broadband coupler is not constructed with "lossy" elements, it follows that the RF power will be transferred to the load at essentially equal efficiency.

LOADING? Why do you normally tune and load an RF Amplifier? To make the tuned circuit show the proper load impedance to the plate of the tube at the desired frequency.

The output circuit of the 200V is designed to match 52 to 72 ohm coaxial transmission lines without dipping, loading, or tuning of any kind!

SWR? If the SWR is 2:1 or less, the reflected change in plate load impedance through the broadband coupler will be negligible.

HARMONICS? The broadband coupler could be designed wide enough to pass the 2nd Harmonic generated by the output tubes; however, since this is undesirable, the passband is restricted to one megacycle and a series trap circuit built-in to reduce 2nd and higher order Harmonics better than -50 db. The Harmonic rejection of the broadband coupler is equal to or better than a properly tuned Pi network.

The overall broadband circuit design makes possible a true single knob controlled transmitter. The *ONLY* tuning control is the VFO. In fact, the bands are so arranged that if you have the VFO set to 7280 KC and band switch to 20 meters, the transmitter is instantly ready to operate on 14280 KC; or switch it to 15 meters, and you are instantly on 21280 KC. The 200V is a Band Hopper's dream transmitter. It is the only transmitter that tunes like a receiver and yet provides the best sounding signal on the amateur bands!


73
Wes

Wes Schum, W9DYV

Central Electronics, Incorporated

A subsidiary of Zenith Radio Corporation

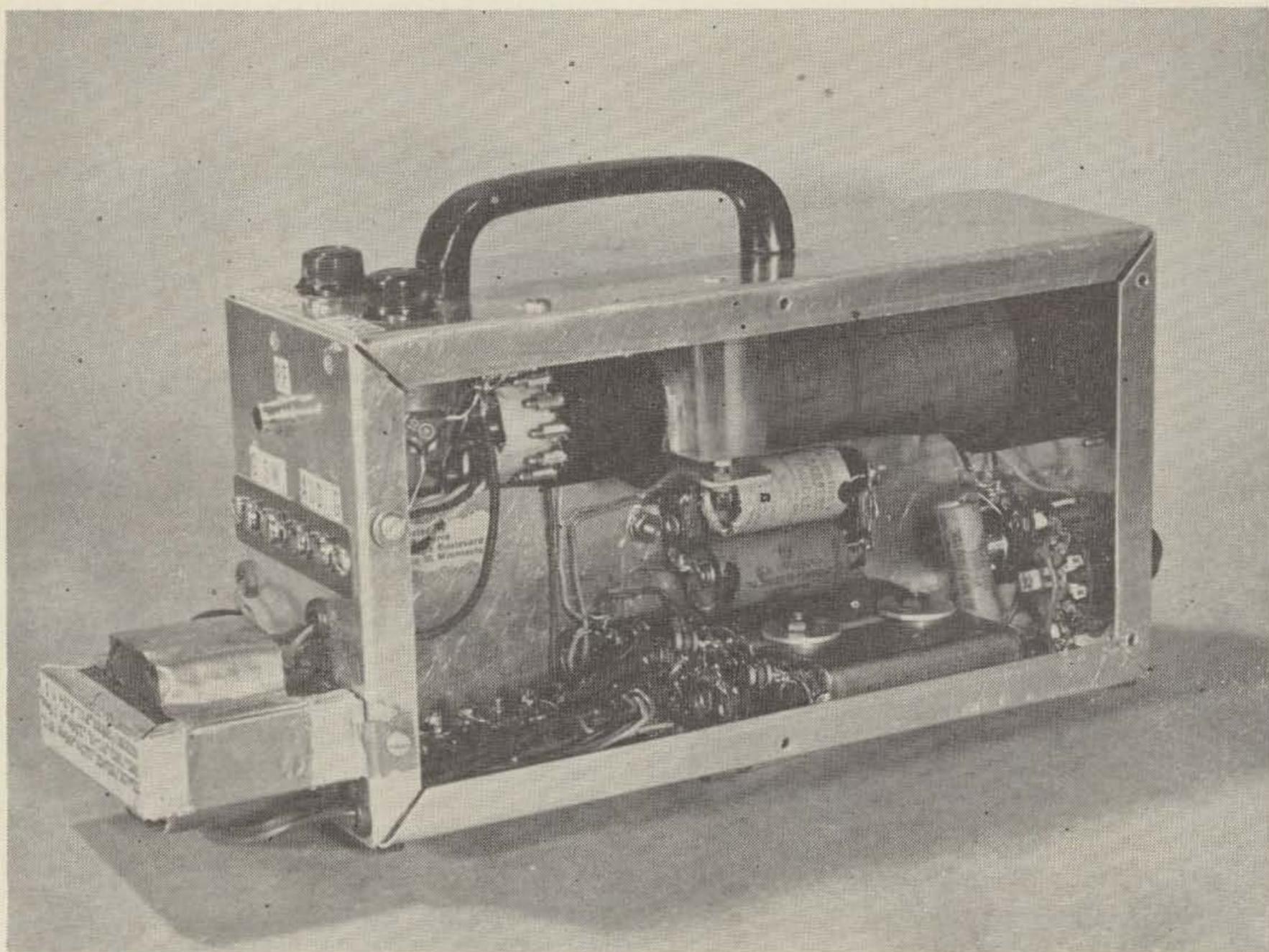1247 W. BELMONT AVENUE CHICAGO 13, ILLINOIS



the key of the locating pin on the bottom, the wires are cut to the proper lengths and soldered. Enough slack should be left in these wires to allow the 2AP1 CRT to be rotated 15 degrees either way to "level" the pattern later. While there are 10 wires coming from the CRT, only 7 colors are needed because pins 3, 7, and 9 are all ground and can be the same color, and pins 1 and 2 are connected together and can be the same color. Incidentally a likely source of both pin contacts and colored leads, already soldered, is a used TV picture-tube socket. Get a couple from your TV serviceman. Be sure to keep a record of the CRT pin numbers and colors, just in case. Write them on the inside of the side cover, where they won't get lost. This is also a good place to paste a schematic of the Simplescope, too.

Looking at the schematic diagram, Fig. 1, shows the rf input going direct to pin 6 of the 2AP1, with a $2\frac{1}{2}$ mh rf choke furnishing a dc and low-frequency ground. Vertical height is determined by the coupling to the transmitter. Various methods of coupling will be discussed under installation.

The horizontal circuit consists of a .01 mfd blocking capacitor and the 1 megohm "Width" control. The "Function" switch connects this to the "AUD" terminal for a trapezoid type pattern or to one side of the 117-volt line for the "envelope" type. More resistance must be added between the "AUD" terminal and the

modulated voltage in the transmitter in a ratio of one megohm, 1 w., added for every 200 volts in excess of 250 volts. The voltage rating of the blocking capacitor should be twice the dc voltage.

The function switch is a two-pole three-position wafer switch. It turns the power on to the Simplescope, and changes the pattern from the "Envelope" type with 60 cycle sweep to the "Trapezoid" type of display. This switch must be of the smaller size wafer to fit in the space allotted, but otherwise it is not particularly critical as to make or rating.

All three potentiometers shown should best be of the medium size, and have a linear taper, but here again there can be variations. If you have a pot of the right size, use it regardless of taper. And it won't make much difference if the value is up to 25% off. As to size, use them if they fit the space available. Because the "Brilliance" and the "Focus" pots operate at fairly high voltages above ground, they should preferably be mounted on an insulating board, and not the chassis, and their knobs should have recessed set screws.

All fixed resistors are one watt carbon. The .01 capacitor from pin #10 of the scope to ground is part of the power supply filter, in effect, and keeps stray voltages from intensity modulating the trace. It could be made a larger value, if you happen to have one, but for convenience in size a .01 mfd 1 k volt disc ceramic

be sure
you're on frequency . . .



with precision made *International Crystals*

International Crystals are designed for all types of communication service . . . Amateur — Commercial — Citizens. Thousands of transmitters, transceivers, and receivers this very moment are on frequency with International Crystals. From a quartz blank to the finished plated crystal, hermetically sealed in its can, International insists on the highest standard of manufacturing. You can be sure you're on frequency because International precision made crystals have built-in **DEPENDABILITY!**

For information on International's complete line of Amateur, Commercial and Citizens band crystals write International Crystal Manufacturing Company today.

International type FA-5 and FA-9 wire mounted crystals are for Amateurs and Experimenters where tolerances of .01% are permissible. Priced from \$3.30 to \$5.75 for fundamental frequencies, and from \$3.30 to \$9.35 for 3rd, 5th, and 7th overtones.

**INTERNATIONAL CRYSTAL MANUFACTURING CO., INC.**
18 NORTH LEE • OKLAHOMA CITY, OKLAHOMA

is best.

The power supply is a full wave voltage quadrupler and uses a small and inexpensive transformer (\$1.35 from Olson) and silicon diodes rated at 150 v RMS. These diodes range in price from 49¢ to \$3.75 each. Current ratings are not very important here as the current drain is low, only a few mils. The voltage ratings should be *at least* 150 volts RMS for the 130 volt transformer, higher voltage rat-

audio output transformers, etc.

The high voltage to the scope is turned on and off by a switch or relay contacts connected to "SW" and "G." This system was chosen over the "Blanking voltage" system because one of the leads is ground and as a result any accidental short circuit of these leads to each other or to ground, can do nothing more than turn on the scope spot or trace. The Simplescope should be turned on and off with the

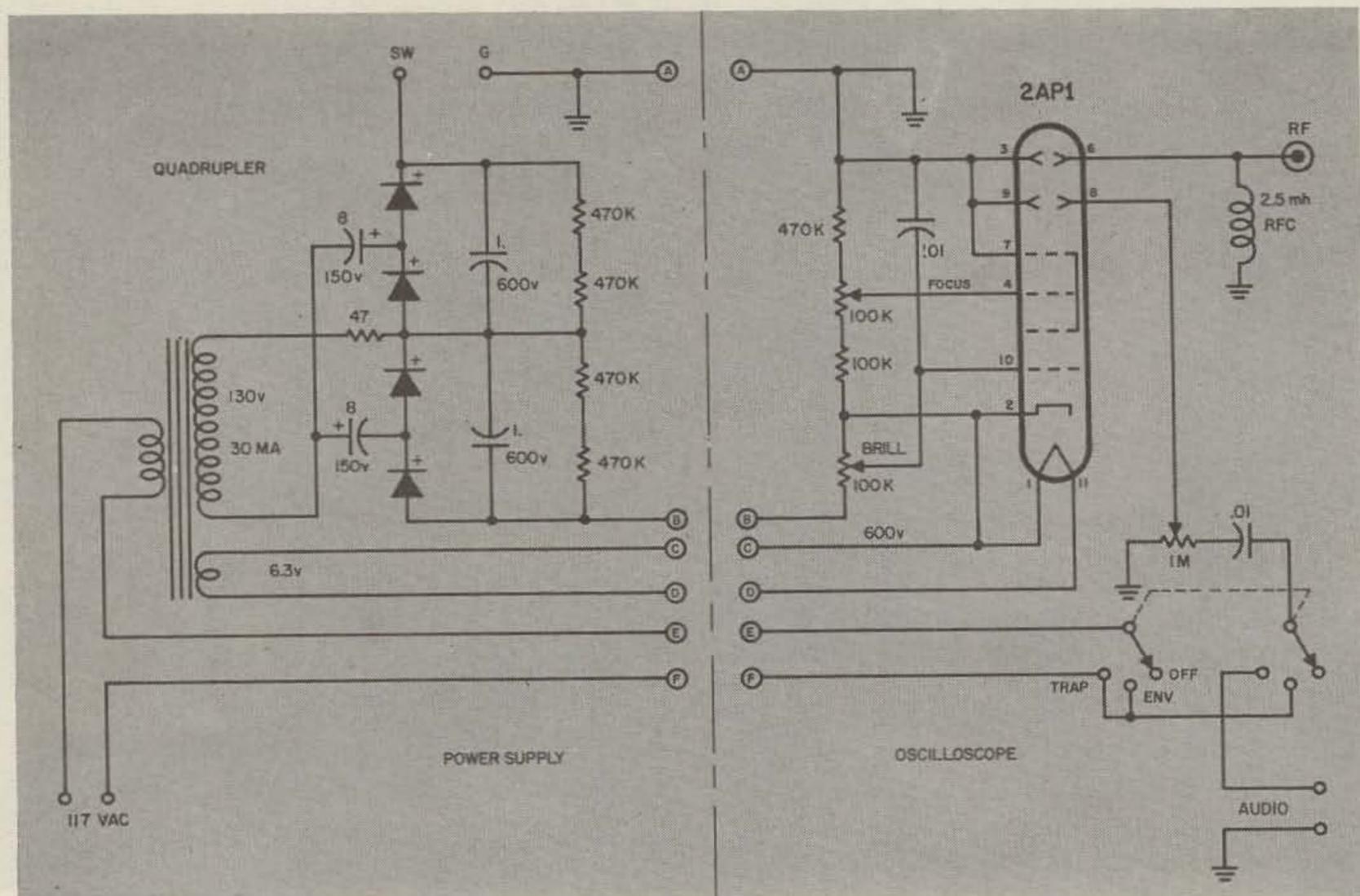


Fig. 1

ings are OK if you want. Selenium rectifiers can also be used, but they take up a lot more space, are harder to mount and give less output voltage. The capacitor values given are a compromise between various factors of size, cost, and availability. The builder can use higher values of both capacity and voltage here if he wants, if the capacitors will fit the space. The 47 ohm resistor in one lead of the transformer is the usual surge-limiting resistor to prevent damage to the diodes from the charging current into the capacitors. It can be increased in value to 100 or 150 ohms without harm. The four 470 K ohm resistors form the bleeder, and here, too, some variation can be allowed, but lower values reduce the output voltage, and higher values slow down the discharge rate.

With the values given for this quadrupler supply, the output voltage is 600 volts, plenty for the 2AP1 CRT tube which will work on as little as 300 volts. Lower voltages give greater deflection sensitivity but less margin in brilliance. With lower voltages the scope is much more susceptible to stray magnetic fields from adjacent power transformers and chokes,

transmitter, otherwise the undeflected spot will soon burn a dark spot in the screen, or a dark line if the 60-cycle sweep is used. For temporary testing purposes the two terminals may be connected together without harm, of course. If a relay, either ac or dc is used to turn the high voltage on and off simultaneously with the transmitter, it should *never, never* be mounted in, on, or near the scope since the magnetic field of its coil will distort the pattern on the Simplescope.

Fig. 2 shows two alternative power supply circuits that can be used to fit different power transformers that the builder may have in his junk box. Fig. 2A is a doubler circuit, suitable for transformers with a high voltage secondary of 225 to 300 volts. Be sure the rectifiers used will stand the transformer voltage. Fig. 2B is a half-wave circuit for transformers with a high voltage secondary giving from 500 to 750 volts. While the 5Y3 voltages ratings are exceeded, the current is very low, and the tube gives no trouble. There is plenty of room to mount it horizontally inside the chassis. Transformers less than three inches wide for mounting on the rear of the chassis

can be had for both the above circuits, but if yours is too big, it could be mounted separately, at the cost of reduced mobility, compactness, and utility of the scope.

In using junk box transformers be sure that the high voltage centertap is *not* internally grounded. (It is in a few types I have run across.) *Please note that in none of these power supplies is the negative grounded.* This is *one* case in which neither the negative high voltage, the cathode nor the heater circuit is connected to a ground. For simplicity and safety in the input and deflection circuits the *positive* end of the high voltage is the ground.

The same circuit and parts values shown in Fig. 1 may be used with the 3AP1 or 3BP1 scope tubes provided higher voltage power supplies are used. About 900 to 1000 volts are needed with these tubes. Of course a larger cabinet is needed, and the pin numbers will be different.

In figuring dc voltages from your power supply add 20% to the RMS ac rating of the high voltage winding and multiply by 4 for the quadrupler circuit or 2 for the doubler circuit. The half-wave circuit will give more than a 20% increase.

If you don't have an old 2-inch meter case to hold and frame the face of your CRT tube, there are other methods that can be used.


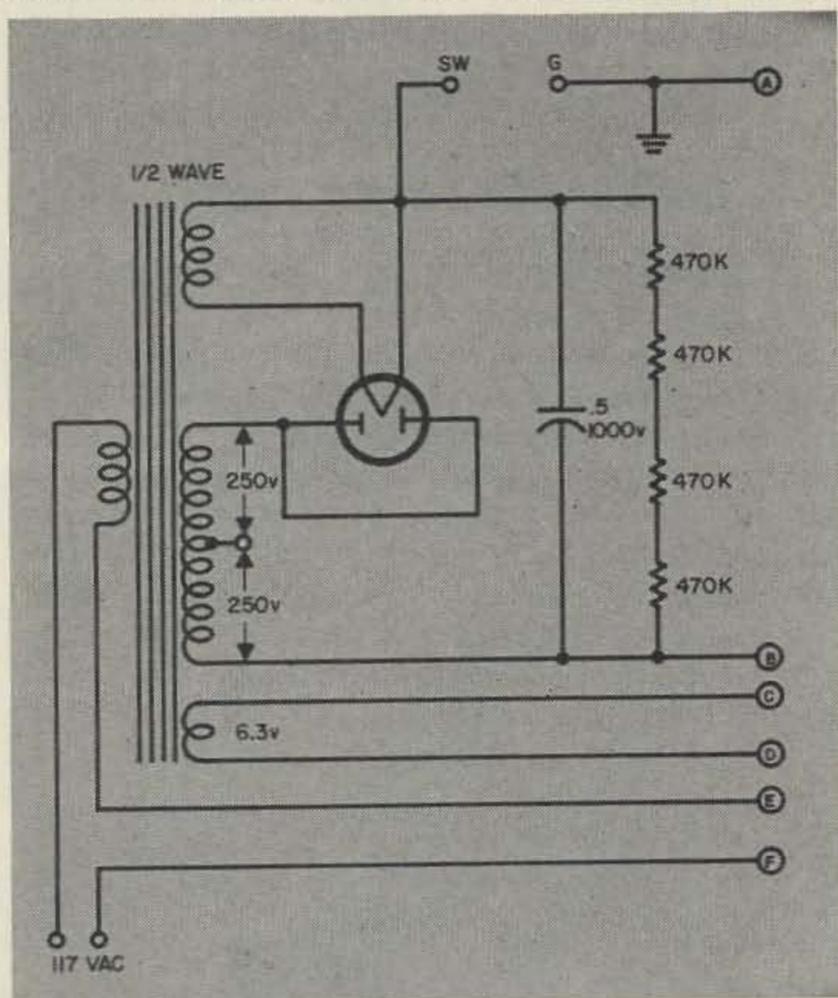


Fig. 2B

Probably the simplest is to make a grommet by slitting a length of rubber or plastic tubing of about $\frac{1}{4}$ " diameter and putting it around the opening. Or leaving the edge of the hole bare and supporting the end of the tube by three or four small rubber grommets bolted to the panel around the hole on the inside. A frozen orange juice can is a loose fit for the end of the CRT. With both ends cut out, and

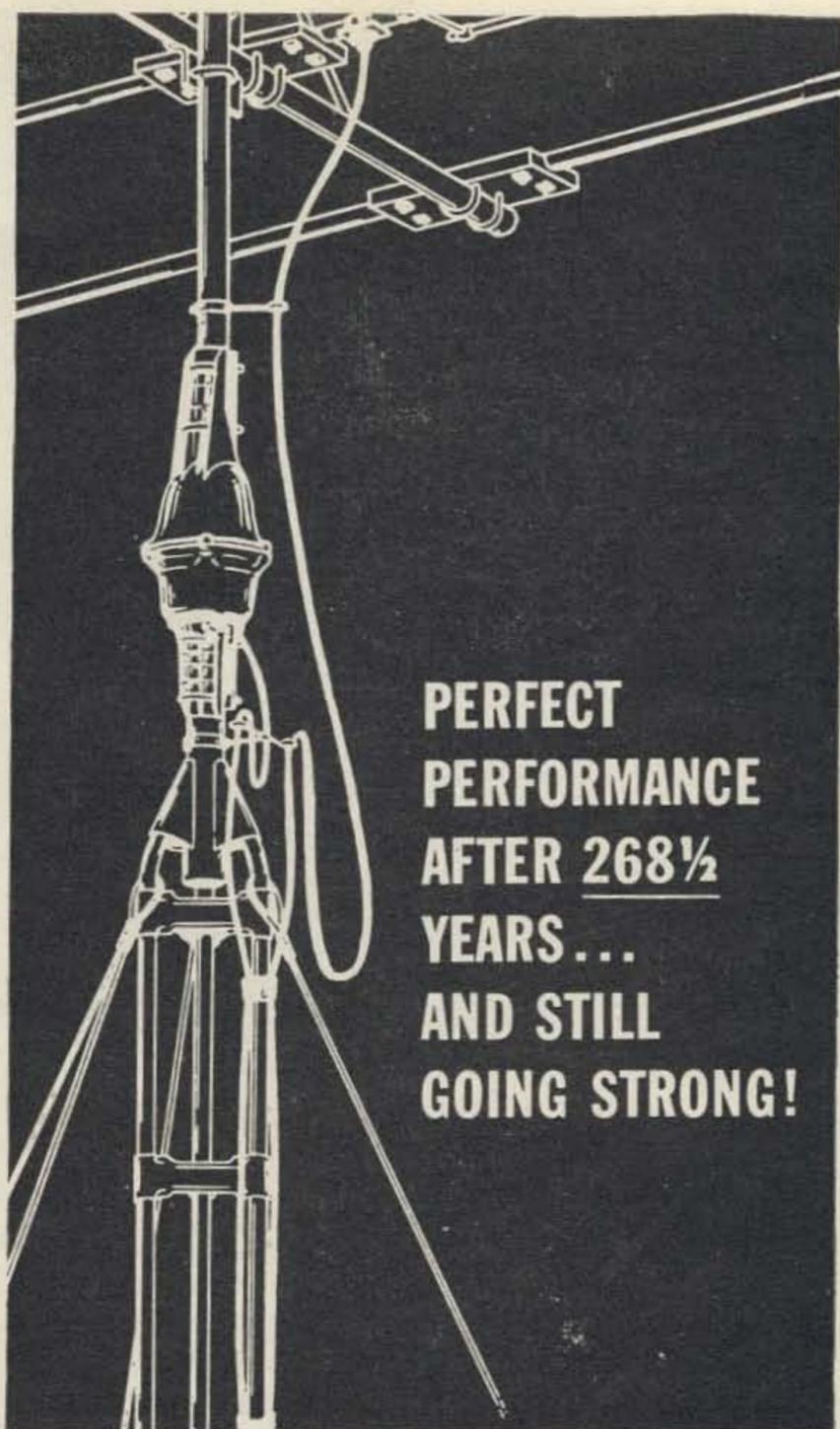

**PERFECT
PERFORMANCE
AFTER 268½
YEARS...
AND STILL
GOING STRONG!**

Some years ago, we installed several of our rugged, precision HAM-M antenna rotors on the roof of our plant and set them in motion. They've been going constantly ever since—under heavy antenna loading, through ice storms and hurricane-force winds—at the reversal rate of once every 1 min. 40 secs.

That's the equivalent service, per rotor, of over 268½ years. Now that's dependability, the kind of dependability you have the right to expect from Cornell-Dubilier! What's more, the HAM-M is backed by the famous CDE lifetime factory service warranty.

At \$119.50 amateur net, the HAM-M is the greatest rotor value around! For further information, contact Bill Ashby K2TKN, or your local CDE Radiart Distributor.



CORNELL-DUBILIER ELECTRONICS, DIV. OF FEDERAL PACIFIC ELECTRIC CO., 118 E. JONES ST., FUQUAY SPRINGS, N. C.

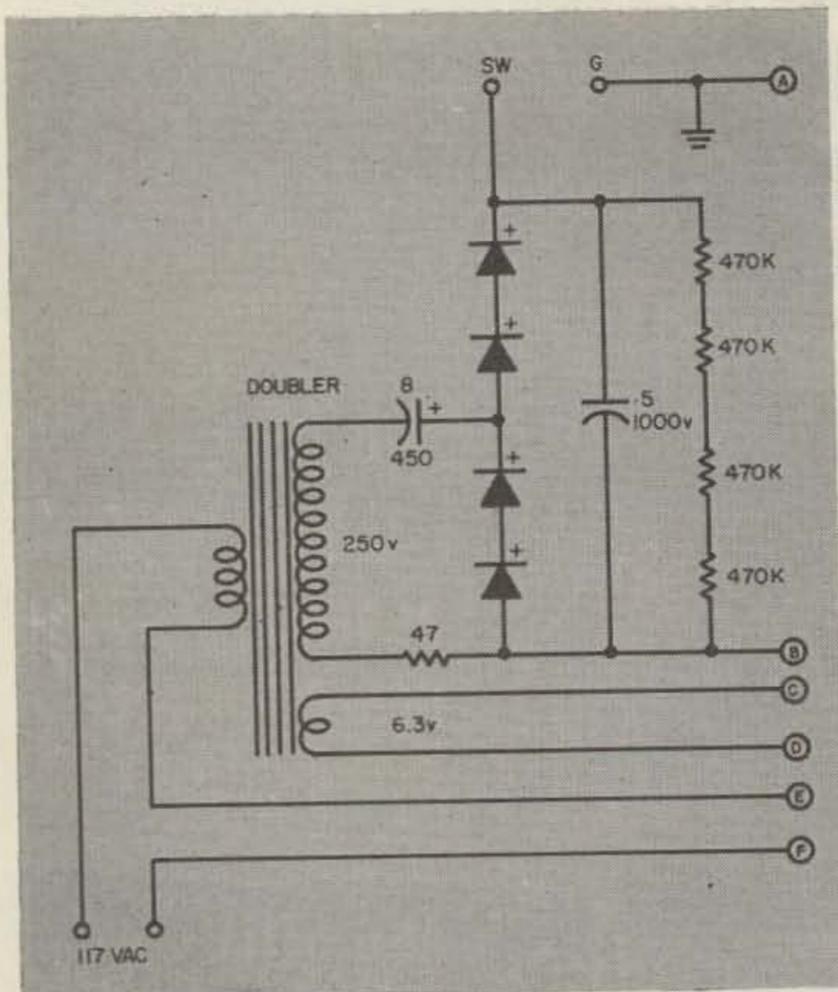


Fig. 2A

painted black, this makes an excellent light shield when slipped over the tube.

If an old 2-inch meter case is used, the glass is discarded and in most cases the support for the zero adjusting screw must be cut out to make the face opening round. Cutting this out is best accomplished with a coping saw using a metal-cutting or jewelers blade, and rounding the edges with medium or fine emery cloth. Clear nailpolish will shine the sanded surface beautifully.

In building and wiring the Simplescope there are few critical points. In the power supply polarity of the diodes and the capacitors must be carefully checked. Because no grounds are used in the rectifier-filter-bleeder circuit, be careful all parts are well insulated from ground. In the scope circuit, outside of the same insulation precautions, the only important thing is to keep the rf lead to pin #6 short and as far away as possible from everything else. All the other wires can run as convenient. And I might repeat again here that the builder should color-code the leads from the CRT tube and keep a record of them for future reference.


Testing is simple. With "SW" to "G" connections open, plug it in and turn it on. See if the CRT tube lights by looking for a glow in the base. OK? Now turn it off and hook a voltmeter from positive to negative. Any voltmeter that reads 1000 volts at more than 1000 ohms per volt will do. Turn on the power. Voltage OK? Turn off the power and connect "SW" to "G" temporarily, set the "Focus" control half on, and turn the power on and the function switch to the "Trapezoid" position. Adjust the "Brilliance" pot until a spot appears, then adjust the "Focus" control for

the finest spot. Readjust the brilliance if the spot is surrounded by a halo. Turn the function switch to the "Envelope" position and advance the width control. The spot should turn into a horizontal line. If the line can't be made long enough to go beyond the edges of the tube face, try reversing the ac plug in the socket, or ground the scope case, or both. If the line isn't exactly horizontal, loosen the CRT clamp and rotate the tube until it is. The brilliance and focus controls can now be touched up to get the best results. Failure to get proper results at any point of the above test should pin-point the trouble for you. If you have to check for voltages at any time, don't forget that the case is *positive*.

The undeflected spot should be fine and round. If it is a line, or "S" or "O" shaped there is some stray ac field that is affecting it. Pull the ac plug while observing the spot, and if it changes shape at the instant the plug is pulled, it is the scope transformer's field causing the trouble. The cure is to position the transformer differently. Sometimes a copper shorting band as shown in the picture will help. I put this band around this transformer while working on the problem of putting the transformer inside the case. It did help, but not enough. In the position shown for this type of transformer, the band was not needed, but was left on to protect the windings.

If the spot is not close enough to the center of the CRT tube face to suit you, and you are of an experimental nature, try putting a small (1" x 1/4" x 1/4") magnet different places around the cabinet. You'll probably find a place where the spot will center and the pattern won't distort.

Now that you have the scope built and tested, the next step is to install and use it. There are four different connections to be made for proper operation, but first you must find a place to put it. The Simplescope is small, requires little desk room, and all the wires come out the back, but you must bear in mind that the electron beam of the tube is very susceptible to magnetic fields, so it shouldn't be put anywhere in the field of a transformer, even an output or modulation

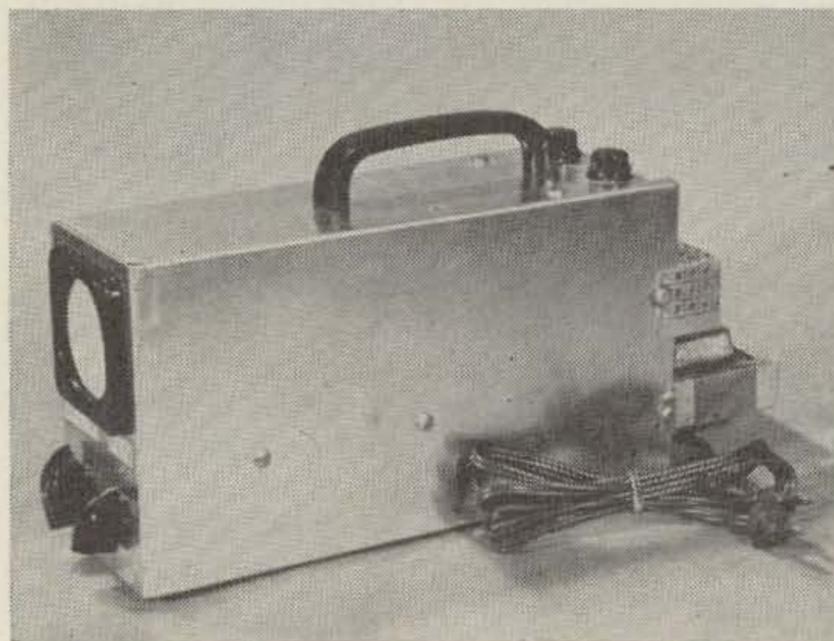

transformer. In general, this means six inches distance. Don't depend on a cabinet to "shield" the transformer, either. You may have to experiment a bit to see where it will work best. Turn the Simplescope on, get a fine spot on the face of the tube, and move the scope around, seeing where you can put it where, (A) you can see the tube face clearly without glare, and (B) where the spot is not moved by either 60 cycle or audio fields from transmitter or receiver.

The first connection to be considered is the power line. This 117 v. 60 cycle power should preferably come from the primary of the filament transformer of your transmitter. This connection assures you that the Simplescope will only be "on" when the transmitter is on. Other sources can be used, but at the risk of having the Simplescope left on accidentally, because it gives no light or sound to indicate the switch is on and the high voltage and heater active. Of course, if you habitually use a "Main Switch" that turns off everything in the station, it is OK to use such a controlled 117 v. outlet.

The second most important connection is the rf pickup. The simplest method is to connect an antenna to the rf jack thru a variable capacity of some sort. The antenna length and position and the amount of series capacity will control the vertical height, which should be about one inch. The best method is to run a short piece of RG58 or 59/U from the rf jack into the transmitter and couple it through a small capacitor to the antenna coax. The value of the coupling capacitor will depend on several factors, but in general the higher the transmitter power and the shorter the coax from the scope, the smaller the capacity that will be needed to produce a satisfactory pattern on the CRT face. With very low powers, a direct connection can be made. An advantage of this method is that if the transmitter output is into a very low SWR line on all bands, the scope pattern will be the same on all bands. Various other pickup methods for getting rf may also be used, such as from antenna tuners, etc. The point is to feed enough rf in to get a readable pattern.

The third connection is the control line "SW" and "G," the terminals that must be connected together at the same time that plate voltage is applied to the transmitter. They may be connected together by extra contacts on the send/receive switch, antenna relay or plate relay, or as mentioned previously by a separate relay activated by the send/receive switch.

The last connection to be made is for the audio. The "AUD" terminal is connected to the actual modulation voltage in the transmitter. It must NOT be connected to the speech amplifier, driver, modulator plates or primary of a modulation transformer. Any connections but to the actual modulated voltage will give a false picture because it will

NEIL

Designs and Manufacturers

- Printed Circuit Boards and Assemblies
- VHF Transmitters and Receivers
- Airborne Transceivers
- Mobile and Fixed Station Transceivers
- Special Instruments for Military and Industry plus Technical Writing for Manuals and Advertising

And now a new **6 METER** transceiver using 8mc crystals including a double-conversion crystal-controlled receiver for under \$120.

Write For Information

MAILING ADDRESS:

**NEIL ELECTRONIC
SYSTEMS CORP.**

1336 CALKINS ROAD
PITTSFORD, N.Y.


not contain all the phase shifts and distortions that may occur in the modulator. Thus the proper connection to a plate-modulator transmitter is to the terminal of the modulation transformer that connects to the rf plate circuit. For clamp- or screen-modulated transmitters (such as the DX40) the connection is to the screen terminal of the modulated tube. For DSB and SSB transmitters. The connection is to one terminal of the modulating voltage system. In this case the Simplescope may not be satisfactory because some DSB and SSB modulating systems operate at such a low level that there isn't enough audio voltage to give a satisfactory deflection horizontally. For the Simplescope illustrated it takes about 25 volts RMS or 70 volts peak-to-peak to produce a usable horizontal sweep (about 1/2 inch). Where the dc voltage being modulated is over 250 volts, additional resistance should be added in series with the "AUD" lead as previously mentioned, and this resistance is preferably installed in the transmitter to reduce the hazards of bringing the full voltage out of the transmitter. If more than one megohm is needed, use a series of 1 meg. one watt carbon resistors instead of a single larger value, to prevent possible arcing troubles. In cases where the modulation transformer terminals are available without digging inside the transmitter (the B&W 5100B, for one) these added resistors can be enclosed in a length of insulating tubing, or very thoroughly taped with a good electric tape for protection, and placed outside the transmitter. The "AUD" connection on the Simplescope can be made a high-voltage terminal and the resistors placed inside the case. Don't forget to ground the scope to the transmitter.

Of course the Simplescope can be used "as is" for temporary modulation checks with no connections to the transmitter, just using the "envelope" type of pattern to check modulation percentage, but this type of check doesn't tell all the story. For a temporary check it is only necessary to connect the "SW" terminal to "G" as when the Simplescope was tested, put the "Function" switch in the "Envelope" position and feed enough rf into the rf jack (from an antenna or pickup wire) to make the vertical height about 3/4 inch, and advance the width control until the envelope is the full width of the CRT face.

The unmodulated envelope pattern is a green ribbon, with top and bottom edges straight and parallel. When the carrier is modulated, ripples occur on these edges, the size of the ripples and waves depending on the modulation percentage. A wave on the top edge will be a mirror image of the wave on the bottom edge. "Perfect" 100% modulation occurs when the outer extremities of these waves double the width of the unmodulated ribbon or envelope, while the inner extremities just meet in the middle, making a bright dot. Over modulation is easily detected as the dots turn

into dashes. Clipping and limiting can be detected as a flattening of the peaks of these waves at a certain width of the pattern. Frequency response can be roughly judged by the proportion of high and low frequency waves under average modulation. Close observation is necessary for any wave-form distortion with the Simplescope because of the 60-cycle sine-wave sweep, but major troubles can usually be detected. Hum and noise show up well in the envelope pattern. Hum is seen as humps, dips, or loops in the top and bottom edges of the pattern. Two humps and two dips or two loops show 120 cycle hum, and a single loop or non-parallel edges show 60 cycle hum. Noise shows as irregular spikes or ripples.

The trapezoid pattern shows the unmodulated carrier as a vertical line that widens with modulation into a trapezoid. At 100% modulation the trapezoid becomes a triangle, and over-modulation is indicated by a line extending from the point of the triangle. The upper and lower edges should be perfectly straight. Any curvature indicates non-linear modulation of the carrier. The commonness cause is low excitation, or too heavy loading, or

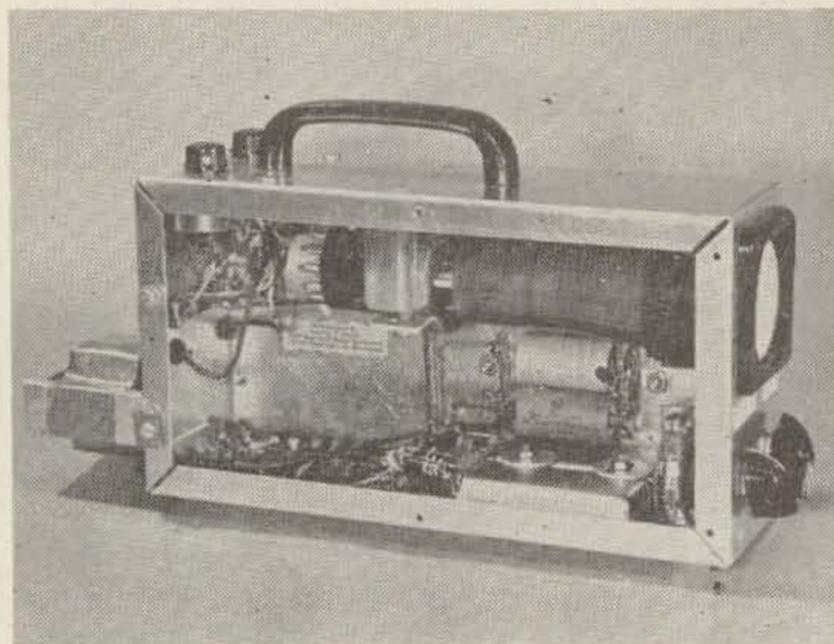


both. Poor design of the final is also a possibility. In efficiency-modulated finals (Grid, screen, cathode, or suppressor modulated) the correct adjustment shows up as the best-looking trapezoid.

In the trapezoid position SSB signals show as the "Bow-Tie" pattern. See the side-band handbooks and articles for interpretation. It is beyond the scope of this article to give instructions for interpreting scope patterns beyond the most common and simple effects. The Simplescope will monitor your modulation, hum, and excitation constantly and accurately. When you use it you'll never have to ask anybody, "How's my modulation?" Or, "Have I got any hum?" You'll know!

In conclusion I want to thank Bob Rode, W0BRE, for taking the excellent photographs as well as many useful suggestions for the design, and to Jim Borders, K0KMD, for building the preliminary model. Jim's worked the first time he plugged it in, and I hope yours does, too! Have Fun!


... W0OPA

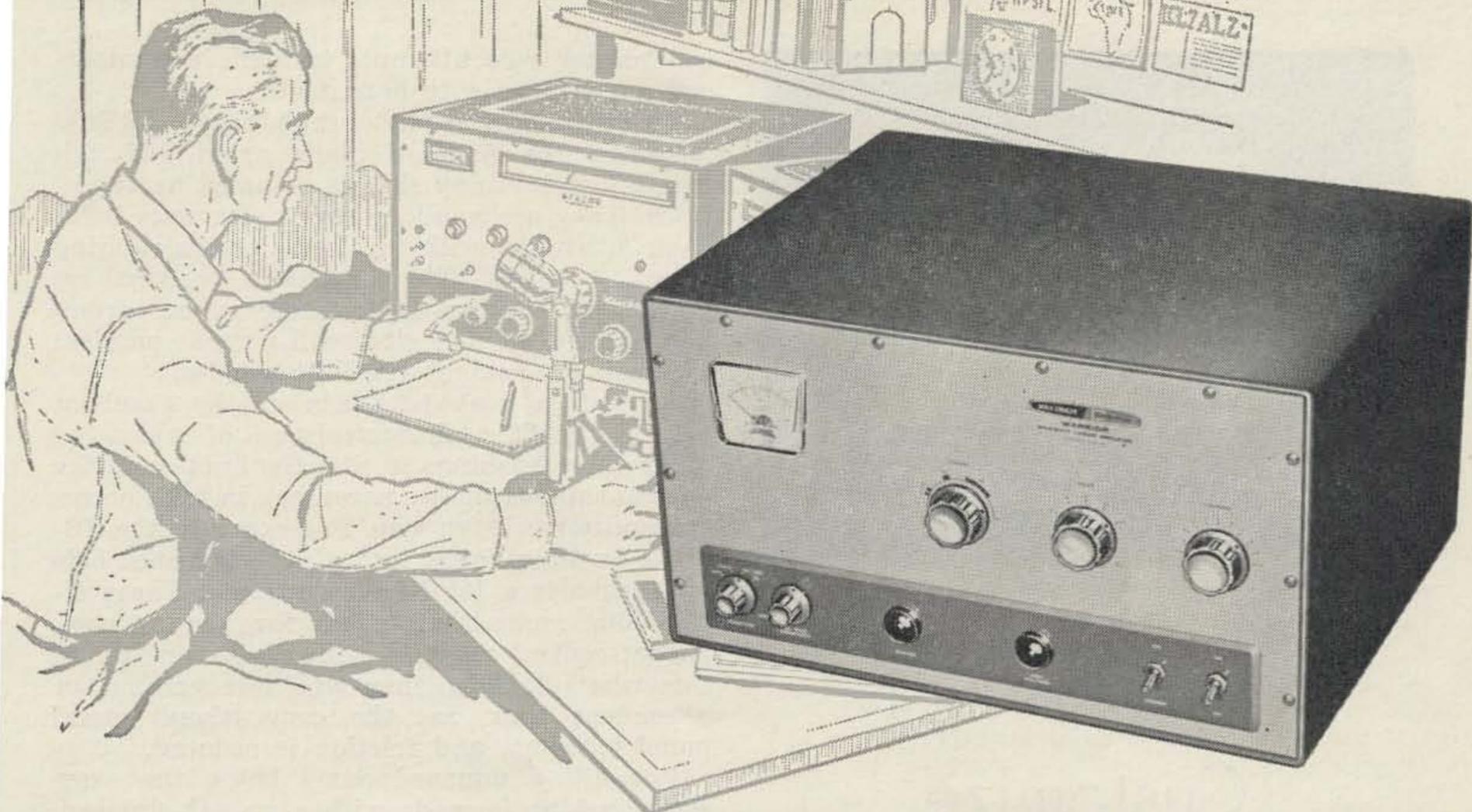

HERE'S A NEW HEATHKIT[®] GROUNDED GRID KW LINEAR...JUST \$229⁹⁵

The new Heathkit "Warrior" is a completely self-contained, desk-top kilowatt linear, loaded with special features, at half the cost of comparable units! Compare feature for feature, quality component for quality component, you'll find no shortcuts . . . only the finest watt-per-dollar value in a linear amplifier on the amateur market today!

Maximum power input: SSB—1000 watts P.E.P., CW—1000 watts, AM—400 watts (500 watts using carrier controlled modulation), RTTY—650 watts. **Driving power required:** 50 to 75 watts—depending on frequency. **Output circuit:** Variable pi-network (50 to 75 ohms). **Input circuit:** Broad banded—requires no tuning. **Input impedance:** Approx. 70 ohms. **Band coverage:** 80, 40, 20, 15, 10 meters. **Panel metering:** Switch-selected, grid current, plate current, high voltage and relative power output for ease of loading. **Tube complement:** 4-811A, 2-866A. **Size:** 19½" W x 11½" H x 16" D.

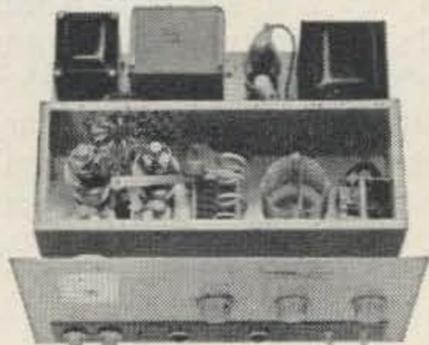

This inside view shows the neat circuit layout and husky components that emphasize quality. Note the internal shielding of plate circuit for maximum protection against TVI.

CHECK THESE FEATURES . . .

- Completely self-contained . . .* HV, Fil. and Bias supplies built in.
- Versatile . . .* May be driven by any 50 to 125 watt transmitter or exciter—no matching or swamping network required.
- Efficient . . .* Stable grounded grid circuitry allows most driving power to appear in output for up to 70% efficiency.
- Oil-filled capacitor . . .* And 5-50 henry swinging-choke provide the excellent dynamic regulation required for high peak power output with low distortion.
- Inexpensive tubes . . .* 4 paralleled 811A's and 2-866A's, forced-air cooled by silent built-in fan.
- Stable . . .* careful design provides a high degree of over-all stability in conjunction with the grounded grid circuit configuration.
- Exclusive . . .* Internal RF shielding of plate circuit for maximum TVI suppression.
- Interlocked switching . . .* prevents accidental application of HV before switching on filament and bias.
- Rugged construction . . .* 16 gauge steel chassis—¼" aluminum front panel—welded one-piece cabinet.

Kit Model HA-10 . . . 100 lbs. \$23 dn., \$20 mo. **\$229.95**

Assembled Model HAW-10 . . .
100 lbs. \$33 dn., \$28 mo. **\$329.95**

FREE CATALOG

Send today for our Free Catalog describing over 100 different Heathkit products in Hi-Fi, Test, Amateur Radio, Marine and General consumer fields.



HEATH COMPANY

Benton Harbor 11, Michigan

Please send my Free copy of the complete Heathkit Catalog.

NAME _____

ADDRESS _____

CITY _____

ZONE _____

STATE _____

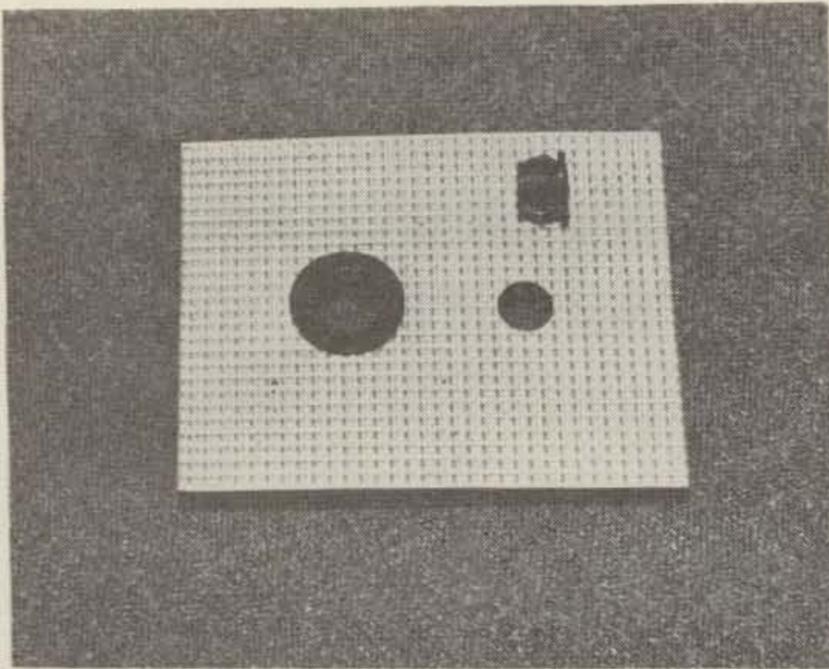


Photo Credit: Morgan S. Gassman Jr.

Snap Bushings Customize Equipment

Roy E. Pafenberg

THE appearance deficiencies of ventilation and clearance holes drilled in thin sheet aluminum are recognized and compounded if pre-finished enclosures are used. John Howard, K8MME, in a September, 1960 QST article, "Aluminum Eyelets Make Good Fever Medicine," proposes an answer to the problem. The solution is very effective, however there is work involved and the eyelets must be backed up for peening.

The use of plastic snap-in bushings came to mind and information was requested from the Heyman Manufacturing Company of Kenilworth, New Jersey on their line of HEYCO nylon bushings. The literature received by return mail provided the answer to this and other perplexities that plague the amateur

constructor who attempts to achieve commercial appearance with hand tools.

As shown in the photograph, these HEYCO bushings are made of black nylon and will firmly lock into any chassis or panel up to $\frac{1}{8}$ " thick. They are available to fit clearance holes from $\frac{3}{8}$ " to 2", with inside diameters ranging from $\frac{3}{16}$ " to $1\frac{5}{8}$ ". These bushings are ideal replacements for the conventional rubber grommet and the smaller sizes will provide painless eyewash for cabinet ventilation holes.

Advantage may be taken of the excellent bearing surface characteristics of nylon by using these bushings to ease the friction in the mechanical assemblies necessary in high power transmitter construction. For example, the SB-375-4 bushing snaps into a $\frac{3}{8}$ " clearance hole and provides a $\frac{1}{4}$ " bearing surface. These dimensions make them ideal for use as component control shaft feed-thru bushings. Being somewhat flexible, they are less critical of alignment than are the conventional metal panel bushings and friction is reduced.

For filling unused panel holes, the same style bushing is made with a smooth finished, closed top and sold as a hole plug. Aside from affording a welcome change from the usual chrome plated version, these provide an excellent means for the insulated mounting of a variety of components. The thin but strong nylon top is readily drilled to accommodate a jack or other part. Don't be concerned about the plugs pulling out. Though they are installed with finger pressure and are just as easily removable, the manufacturer claims they will withstand a 35 pound pull.

With all the advantages cited, there must be one fly in the ointment. These bushings and plugs are apparently available only through the manufacturer in minimum quantities of 100 each. Aside from the inconvenience of mail order buying, this is no real problem since the prices are low enough to make purchase in 100 lots attractive. For example, the smaller size bushing shown in the photograph sells at \$1.90 a hundred, less 1% on cash transactions. A letter to the company will bring catalog sheets and from that point you are on your own.

VFO Chirp vs. 6AU6

FOR some odd reason which has never been satisfactorily explained to me, several commercial equipment manufacturers have chosen the 6AU6 as a VFO tube. From my own experiences, and those of quite a few other hams, the 6AU6 is a mighty poor choice for this service. The case histories of two popular pieces of ham gear I have owned tell the story:

A number of years ago I bought a Heathkit

VF-1 VFO. After building the thing with extreme care in order to produce a stable unit, I was disappointed to learn it chirped like mad when I keyed it for break-in CW. The 6AU6 tested OK, and all other parts of the VFO seemed fine. On a hunch, I tried plugging in another 6AU6. All of a sudden—the chirp was gone! And still a third 6AU6 produced the chirp again. Obviously there is some feature of the 6AU6 such that, although it may

Al Brogdon, W4UWA/K3KMO
316 West Fairmount Ave.
State College, Penna.

with the great new

SHURE

440 SL HAM MICROPHONE

- Sharp Cutoff Below 300 and Above 3000 cps — Minimizes Splatter, Reduces Unwanted Sideband.
- Elimination of resonant peaks permits higher average power — more audio punch.
- Shaped frequency response — Superb Intelligibility — Naturalness of voice.
- Trouble-Free Controlled-Magnetic Design — Hi-Output — 52.5 db — Extraordinarily Rugged — No humidity problems.
- Complete with Grip-to-Talk Switch, Desk Stand, 2-Conductor Shielded Cable. Will operate VOX and Grip-to-Talk.

Complete with stand, grip-to-talk switch, 7 ft. highest quality 2 conductor shielded cable. Cable connector equivalent to Amphenol MC3M plug.

WRITE FOR LITERATURE: Dept. No. 52-H

Shure Brothers, Inc., 222 Hartrey Ave., Evanston, Ill.

MICROPHONES, HIGH FIDELITY AND ELECTRONIC COMPONENTS

minimize
splatter

ONLY
\$28.50*

*Amateur Net



test red hot on a tube checker, it may still chirp. And as long as I owned that VFO, the thing would key beautifully for break-in CW —the *only* way to work CW.

Recently, I bought and assembled a Viking Navigator. As most of you know, this transmitter and others in the Viking line feature grid-block time-sequence keying. The operation is simply this: When the key is closed, the keyer tube allows the VFO to start and go through any chirp inherent in the VFO circuit, then after the frequency is stabilized (a matter of a few milliseconds), the keyer tube turns on the buffer. Thus, the VFO may chirp, but it will do so at a time when the signal is not on the air. Well, when I started keying my Navigator, a V sounded like "yoop yoop yoooooooooop." Oh Lord here we go again. What was happening was that the 6AU6 was chirping over such a long time period that it was *still* settling down when the buffer came on.

Sure enough, it turned out to be the 6AU6. Another brand new tube that tested "jes fine" on a tube tester, but chirped away. So instead of plugging in another 6AU6 and taking the chance on it going soft and having to soon be replaced, I decided this is the time to try a more permanent cure. Besides, I was losing patience with those 6AU6's.

To state it simply, I checked the tube manuals and found that I could interchange a 6AH6

with the 6AU6, and plug it right into the VFO tube socket without making any wiring changes. Since I have been using the 6AH6, the Navigator has functioned perfectly with no chirp.

In the course of many CW contacts, I have run into several other fellows that have had the same chirp trouble with their VFO's, especially when cathode keying the Heath VF-1, with no time-sequence keying to take up the slop. A couple of these fellows have tried switching tubes and using 6AH6's with the same results I did. Now don't get the idea that switching to a 6AH6 will cure all your VFO chirp—please understand that this only applies to cases where the 6AU6 itself is the cause of the chirp. You may have chirp originating in any of a number of other sources in the VFO. Simply changing tubes won't cure all these sources.

But if you have a Clapp VFO circuit, such as the VF-1, the DX-100 VFO, Viking (Ranger, Navigator, etc.) VFO, or a homespun job, using a 6AU6—it's worth the try to get rid of an annoying chirp by plugging in a 6AH6 to see what happens.

As a closing note, calibration should be checked after switching tubes. The calibration will usually shift just a little bit due to the change from the 6AU6 to a 6AH6, and if you chase DX near the band edges, always play safe.

W4UWA/K3KMO

Beryl Dassow W9HKA
Clifton, Illinois



Console

DURING some period of a radio amateur's life there comes a time when he becomes conscious of the fact that the operating position leaves quite a bit to be desired. That is from the standpoint of orderliness, ease of operation and flexibility. Therefore, as can be seen in the photographs, an operating console was constructed.

The use of the standard relay rack panel spacing of 19 inches was used to provide the required orderliness. The grouping of the various pieces of gear as to the most active area on the console, gives us the ease of operation. The use of tempered hardboard cut to rack and panel size (or larger as in the case of the second photo), gives us the needed flexibility. Flexibility in that it makes it much easier to use either regular relay rack panel mounted equipment or the cabinet type as shown in both photos.

The unit as shown in the present dimensions may be a trifle large for the average amateur's allotted space. However it can be readily pared down to a three-panel width without adverse effects as to the overall usefulness.

This type of relay rack panel mounting was chosen over that of the semi-circular console design because of the simpler method of construction.

The entire rack may be constructed with hand tools with the exception of the vertical dividing and mounting pieces. For a four-panel width as shown, a total of five pieces, each about 5½ feet in length is necessary.

These can be usually cut at the lumber yard from a 2 by 3 or 2 by 6 fir stock at the time of purchase. See Photo 5 and Figures 3A and 3B.


Note also there are no special joints required. Since butt joints are used in most cases the unsightly joints are quite noticeable. To overcome this problem quite effectively, flexible wood trim tape is used. The type used is made by Weldwood in 8 foot lengths and the width varies from one inch to 1½ inches across the desk top front.

The desk top is covered with a piece of vinyl material. The material as shown was fastened with a pressure-sensitive adhesive and a great deal of care must be exercised when cementing the vinyl to the plywood desk top. The usual procedure is to place a newspaper between the two cemented pieces and gradually remove same as the vinyl is carefully rolled into position. To trim the vinyl edges, a beading strip is tacked into place. The wood tape as mentioned earlier will cover the front edge of the vinyl.

You will notice upon adding the various widths of wood strips and panel areas, an allowance of an extra half inch. This is to give a final ¼ of inch spacing on either side of each panel when mounted. The vertical spacing is sufficiently oversize as well.

Photograph number one shows the original console construction. However after the author traded equipment it was then necessary to make additional room for the newly acquired Valiant which is "over-size." This is easily ac-

MONOPOLE RHOMBICS AND SLOPING V's

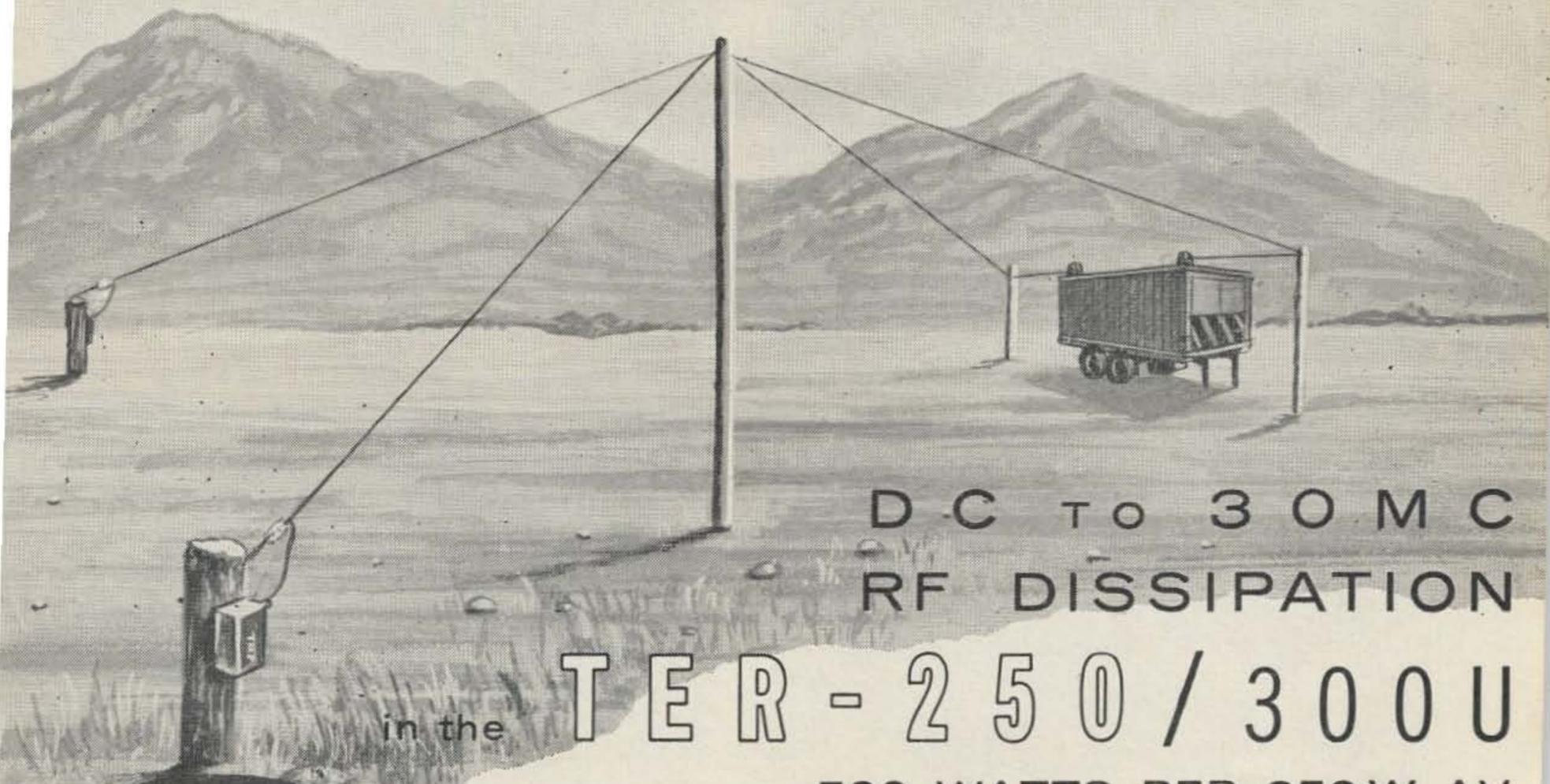

DC TO 30 MC
RF DISSIPATION

in the

TER - 250 / 300U

500 WATTS PEP 250W AV

and


TER - 1800 / 300U

3600 WATTS PEP 1800W AV

The TMC Models TER 250/300U and TER 1800/300U are unbalanced 300 ohm resistive terminations, usable at frequencies from DC to 30 megacycles.

These units were especially designed for use with portable systems. They are housed in convenient, rugged weather-proof cases, constructed for ease of installation and operation in any climatic condition.

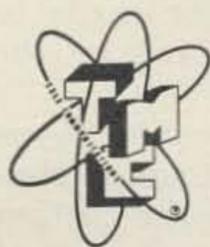TMC has specialized in the design and manufacture of RF termination, dissipators, and dummy loads. Standard impedances are available for Powers up to 50 kw PEP. Our Field Engineering Staff will be pleased to assist you with Standard or specialized RF distribution problems. We invite your inquiries.



Request
BULLETIN

THE TECHNICAL MATERIEL CORPORATION

World Wide Suppliers of Electronic Communication Equipment

MAMARONECK, NEW YORK

and Subsidiaries

OTTAWA, CANADA • ALEXANDRIA, VIRGINIA • GARLAND, TEXAS

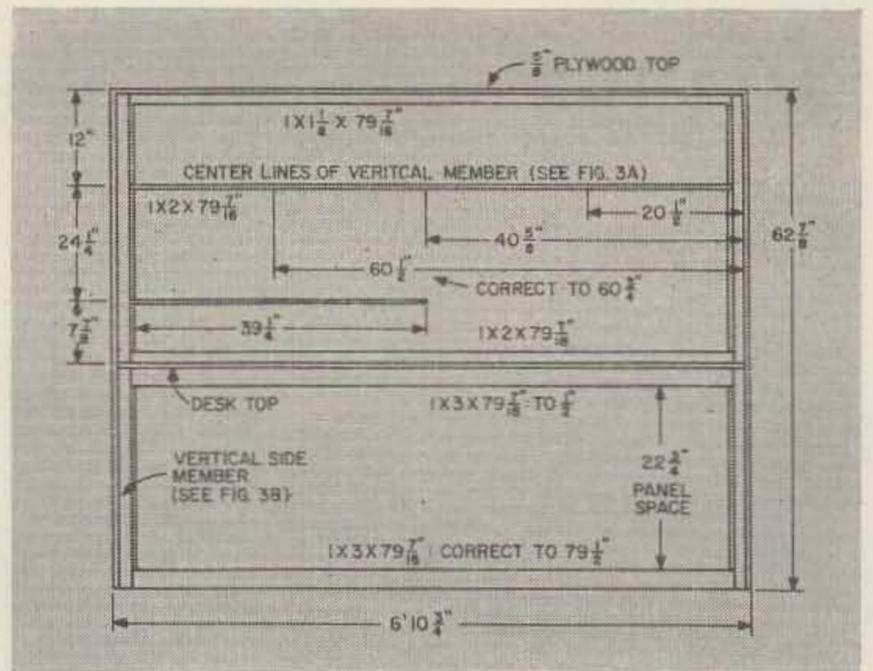
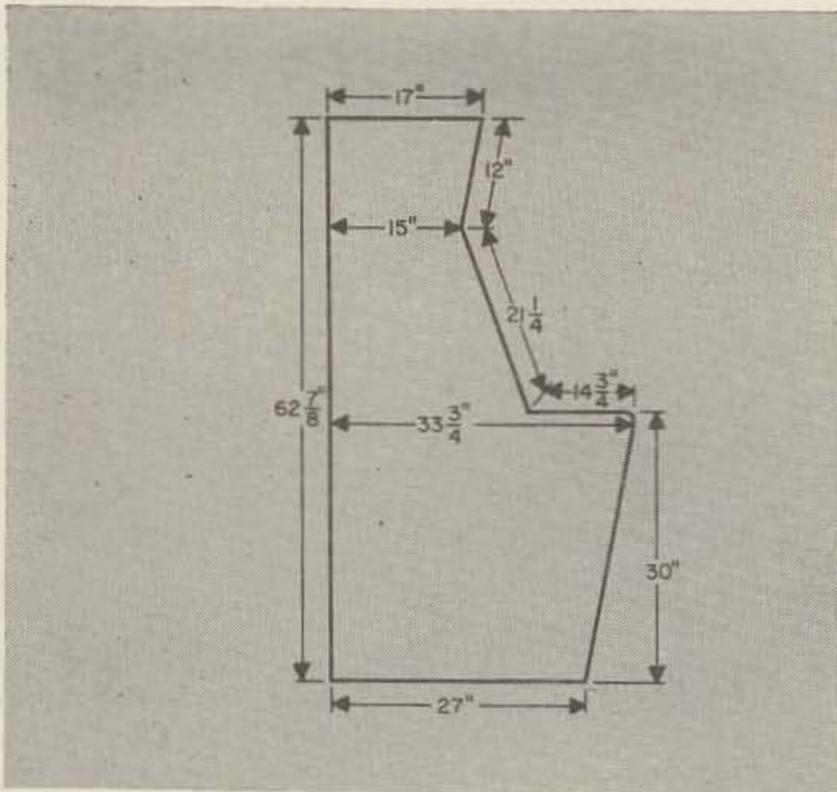


Fig. 2

Fig. 1

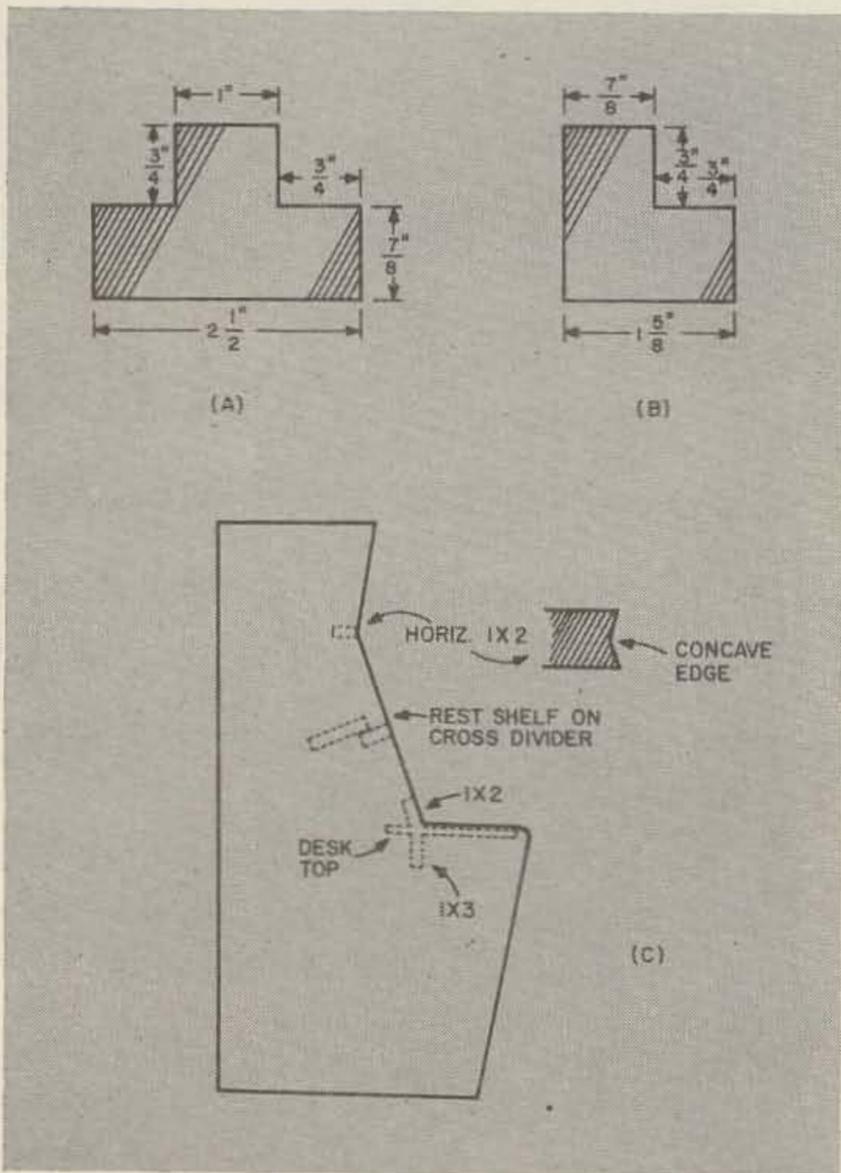


Fig. 3

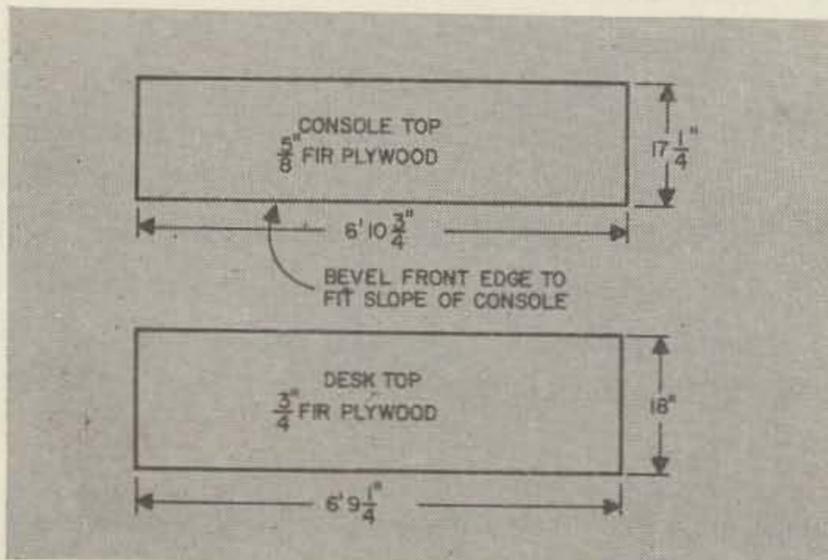



Fig. 4

completed by the removal of a vertical member. Note in Photo 4 the addition of a brace for added strengthening when this vertical piece is removed. Also added as per Photo 2, is a horizontal 1 by 2 for dividing the new panel across the bottom. This then leaves a space of 13 1/4 by 39 1/4 inches for use by the 6N2 and the Valiant. Other arrangements can be made to suit each individual station depending on the gear to be mounted.

As far as the mounting of the cabinet-type equipment, it is necessary to construct a simple shelf from the plywood left in the cutting of the sides or ends. It is best to run a vertical brace from the rear of this shelf down to the 2 by 4 tie at the bottom of the console. Note this 2 by 4 in Photo 3 across the bottom back

BULLSEYE BUYS at ARROW!

AMERICAN GELOSO V.F.O.'s

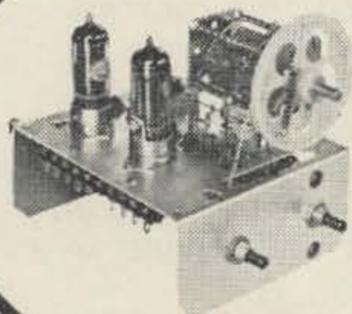


Wired, tested, calibrated, ready for use. Mod. 4/104 for driving one 807 or 6146 final in AM or CW under Class "C" conditions.

Mod. 4/102 for driving two 807's or 6146's final. Has 5 bands. Supplied with Mod. 1640 dial ass'y.

Mod. 4/103 for 144-148 mc bands. Combines VFO primary freq. of 18 mc with xtal fundamental freq. of 12 mc. Supplied with Mod. 1647 dial ass'y.

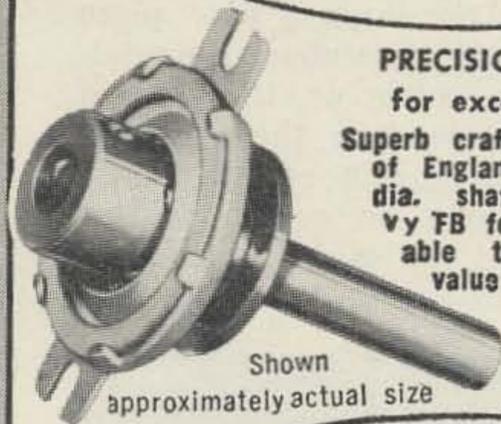Mod. 4/104, 4/102 or 4/103 less tubes and xtal, each \$29.95




PRECISION PLANETARY-VERNIER

for exceptionally fine tuning

Superb craftsmanship by Jackson Bros. of England. Ball bearing drive, 1/4" dia. shaft, 1 1/8" long, 6:1 ratio, V_y FB for fine tuning. Easily adaptable to any shaft. Comparable value — \$5.95.

Amateur Net \$1.50 ea.
10 for \$13.50

Shown approximately actual size

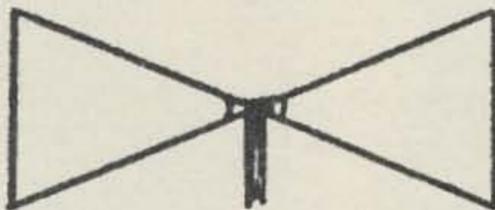

"Wonder Bar" 10 Meter Antenna

As featured in Nov. 1956 QST. Complete with B & W 3013 Miniductor. Only 8 ft. long for 10 meters. Wt. 5 lbs.

Amateur Net \$7.85



Versatile Miniature Transformer

Same as used in W2EWL SSB Rig — March 1956 QST. Three sets of CT windings for a combination of impedances: 600 ohms, 5200 ohms, 22000 ohms. (By using center-taps the impedances are quartered.) The ideal transformer for a SSB transmitter. Other uses: interstage, transistor, high impedance choke, line to grid or plate, etc. Size only 2" h. x 3/4" w. x 3/4" d. New and fully shielded.

Amateur Net \$1.39 10 for \$10.75

3 for \$3.49 ARROW Authorized distributor of HEATHKIT equipment

M. C. JONES Micromatch VSWR & RF POWER MEASURING EQUIPMENT

Mod. 261 COUPLER
0.5 to 225 mc. Power range to 1 KW. UHF type RF connectors. **\$22.50**

Mod. 262 INDICATOR
For use with Mod. 261 Coupler. Selector switch for direct reading of SWR or relative RF power. **\$14.50**

Mod. 690 RF LOAD RESISTOR
(not shown) Rated at 5-w. continuous, 10 w. intermittent duty. **\$2.95**



Mod. 261




Mod. 262

AGS-RT-101 CITIZENS BAND TWO WAY RADIO

No license required. Complies with part 15 of FCC rules on low power units. 1.5 mi. average range on land, up to 5 mi. on water. Xtal controlled XMTR, Rec. Sens. 1 μv. Each unit complete with transmitter-receiver, AM radio, leather carrying case, ear-phones, antenna, 6 penlight batteries.


\$70.00 ea. 2 for \$139.50

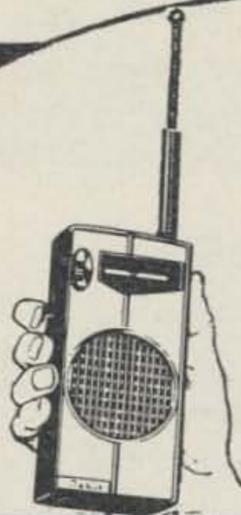

AMECO NUVISTOR PREAMPLIFIER

FOR 50, 144 or 220 mc. Over 20 db gain plus a lower noise figure, 2 tuned ckts, 6CW4 Nuvistor completely neutralized. Noise figure is 2.5 db @ 50 mc, 3.0 db @ 144 mc and 4.0 db @ 220 mc. Power requirements: 100-150 v. @ 8 ma, and 6.3 v. at .13 amps. Specify frequency desired.

Mod. PV, wired and tested **\$13.95**

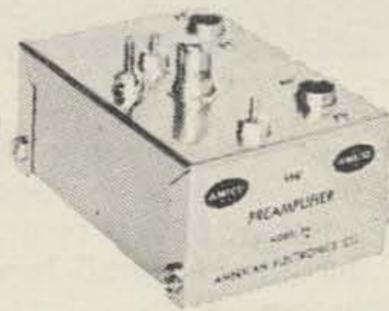

MAIL ORDERS PROMPTLY PROCESSED
SAME DAY SHIPMENT FROM STOCK

ARROW ELECTRONICS, INC.

65 Cortlandt Street, New York 7, N. Y. • Dlgy 9-4730
525 Jericho Turnpike, Mineola, N. Y. • Ploneer 6-8686

SAY! YOU SAW IT IN 73

TO SAVE C.O.D. CHARGES, PLEASE INCLUDE SUFFICIENT POSTAGE WITH YOUR ORDER. ANY EXTRA MONEY WILL BE RETURNED.

ALL PRICES F.O.B. N. Y. C.
Arrow's Export Dept. Ships To All Parts Of The World!
Prices Subject To Change Without Notice.

of the console. When cutting the hardboard to fit the cabinets, cut the round portions (corners) somewhat undersize and then file with a half-round file to fit. The straight edges can be cut with a coping saw as one will be working near enough to all four of the edges. The above may sound tedious but the hardboard saws and files very easily and the result gives a fair fit.

If one is careful in laying out the sides, one sheet of $\frac{3}{4}$ inch thick fir plywood in the 4 by 8 foot size will suffice. The plywood should have both sides good. See Figure 4. The few remaining pieces are then saved and used as angle braces, shelves etc. Perhaps it should be pointed out that the width of the console is such that it will clear a regular three foot door. If you have anything less it will be necessary of course to cut this dimension down to clear your opening.

While not discernible in Photo 4, two screen door turn-buckle type braces (connected in "series" for the required length) are used across the console directly in back of the upper horizontal $\frac{3}{4}$ by 2 inch strip. With reference to Photo 3 again, the 1 by $1\frac{1}{2}$ inch strip that is fastened to the bottom of the sides and to the bottom front of the unit can be seen. This is merely a trim, however it does eliminate

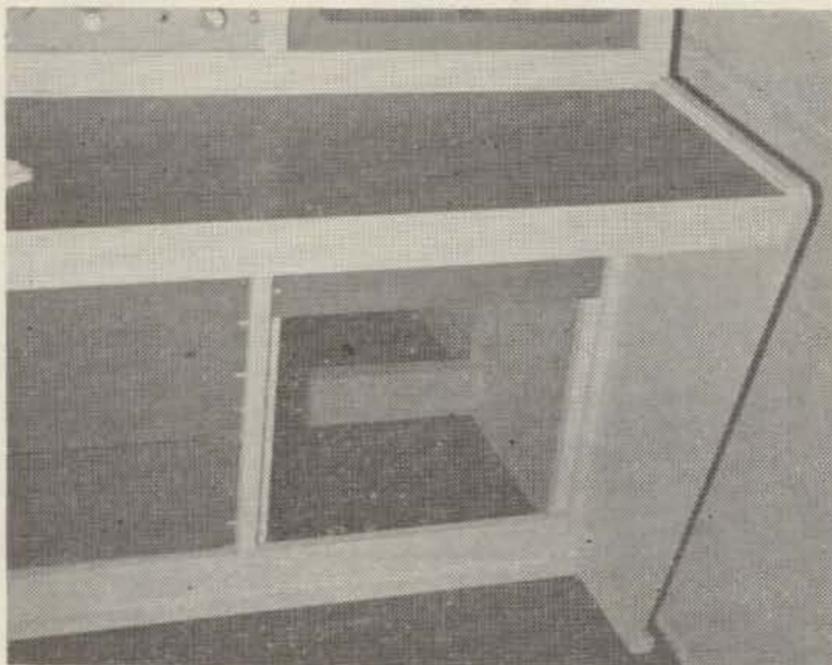


Photo 3

splitting the plywood edges when moving the console about during construction. The strip across the front edge of the desk top is used for rigidity and also conceals the small brace needed underneath in the center.

A reminder with regard to the horizontal 1 by $1\frac{1}{2}$, 1 by 2 and 1 by 3 inch strips; these should be as straight and free of knots as possible. The given dimension for the *width* is the exact size used. These pieces are cut from a board a size larger to secure the final widths and are not necessarily stock 1 by 2's, 1 by 3's etc.

The finished color of the unit itself is a light gray. Our supplier referred to it as French gray. This is a rather light color and is more contrasting to the darker blue gray panels. It



Photo 2

seems impossible to secure the same shade of gray when ordering panels, and this contrast has a tendency to make the various shades of rack panel gray less noticeable. If most of your panel gear will be home made, each panel may be given a light coat of paint from a pressurized paint can. Just a sufficient amount to change the shade of gray but not enough to eliminate the wrinkle finish.

As to the final cost of the described console; a figure of twenty-five dollars should cover practically everything that is required. The main item of course is the large 4 by 8 piece of plywood which in itself costs about nine dollars. If one desires to cover up the unused portions of the console pending the purchase of more equipment, it is less costly to use masonite board. This can be easily painted gray with a pressurized can of paint as mentioned before. Usually two coats are necessary.

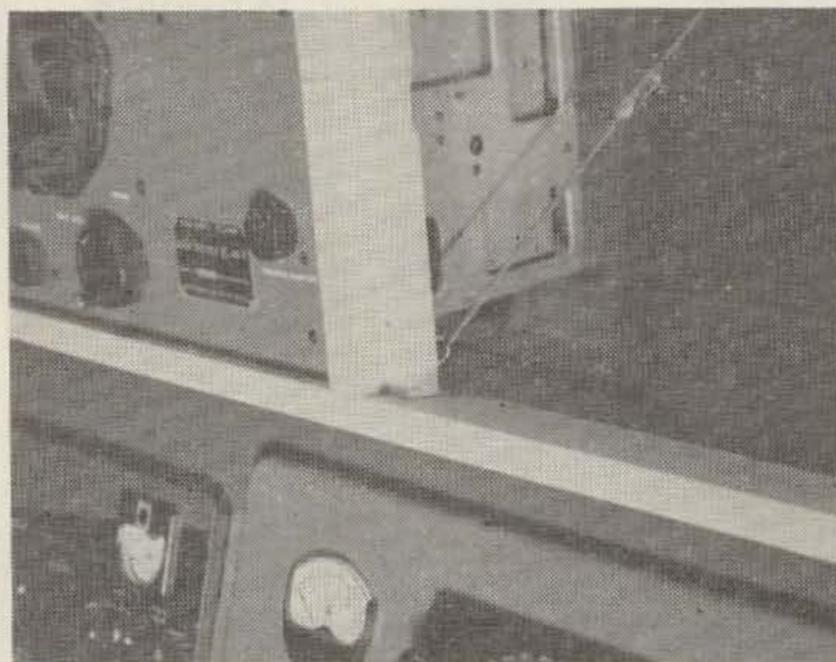


Photo 4

A brief description of the various pieces of gear as mounted by the author may be helpful. Besides the familiar BC-348, Valiant, 6N2, NC-300 etc. we have added at the lower left a $5\frac{1}{4}$ inch panel with several sockets mounted at the left. A cable with a matching plug then can be switched around to use either the Valiant alone, or the Valiant as an audio driver,

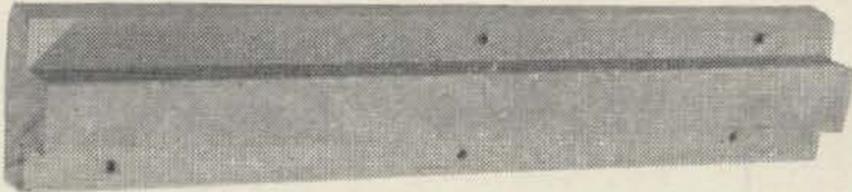


Photo 5

or to the 6N2.

To the right of this panel is the inter-com speaker so the operator will not fail to hear the dinner call. Underneath the National speaker is a 1 3/4 inch patch-panel strip for various audio inputs and outputs. The "eye" at the left is for monitoring RTTY signals. The 10 1/2 inch panel to the right of the speaker contains the National VHF converter units. Directly below this is an audio termination board similar to the one below the speaker. The push-buttons above the NC-300 are used for Conelrad monitoring and WWV and CHU time signals. Underneath the desk are two power supplies and an RTTY terminal unit.

After you have completed your console you are sure to enjoy many happy hours of operating pleasure with everything in order, at arms reach and you still may alter the unit at will. However, don't let your visitors go behind the scenes—its one big messy mass of wires and cables.

To ascertain quickly the main items required the following list can be used as a guide.


- 1—3/4" x 4' x 8' fir plywood (sides)
- 1—5/8" x 17 1/4" x 70 3/4" fir ply (top)
- 1—3/4" x 18 x 69 1/4" fir ply (desk top)
- 1—1 x 1 1/8" x 79 8/16" strip
- 2—1 x 2 x 79 8/16" strip
- 2—1 x 3 x 79 8/16" strip
- 1—1 x 2 x 39 1/4" strip
- 1—2 x 4 x 81 1/4"
- 18'—2 x 3 fir stock (for inside vert. members)
- 11'—2 x 2 fir stock (for outside vert. members)

The above is for the console as shown in photograph number 2. Add to the above list the necessary nails, screws, cup washers etc.


... W9HKA

Interstage Transformers

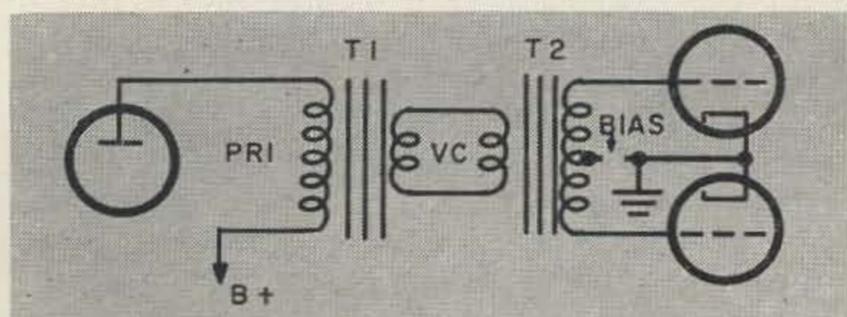It is possible to make an audio interstage transformer from two audio output transformers. The transformers are connected back to back with the voice coil windings together. While this doesn't always provide a theoretically perfect match, it will work perfectly most of the time. For details see diagram.



NINE SECRET FEATURES

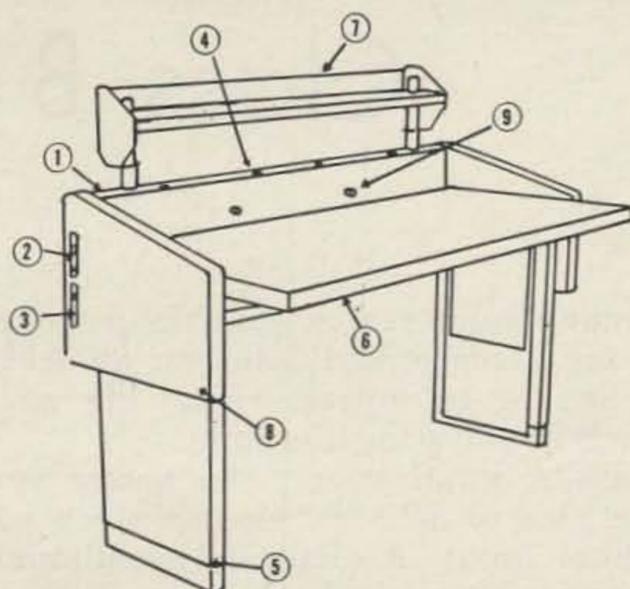

Once you find out about these nine secret features of the Alden Hambench you won't care any more that this is the finest operating bench ever built,* you will want one anyway. Oh, we'll send you complete information on these secret features in a plain wrapper if you write.

Two models: Super—\$99.95 (plus 5c for handling and shipping. Super Deluxe Model —\$139.95, including handling and shipping.

(If you can't wait to find out about those nine features you can look 'em up in our January ad in 73.)

ALDEN PRODUCTS

7373 North Main Street, Brockton, Mass.

(*Alden is the only manufacturer of Hambenches).

STURDY E-Z WAY TOWERS

Put your Tribander at 41' in 70 mph wind (125 mph cranked down to 24').

Tilts over for E-Z access to array.

Mounts Ham-M Rotor inside tower head. Top radial bushing - vertical thrust bearing.

Safety rest locks tower at desired height. No weight on cables.

E.I.A. RS-222 specs. Heavy wall structural steel tube legs, solid steel rod diagonal & horizontal bracing — arc welded. Sold by Top Flight Distributors

Everywhere!

Write for Catalog 22-1

MOUNTING KITS:

GPK-S40 \$75.00

Wonder Ground Post

BAK-S40 \$10.50

Wall Bracket

\$169⁵⁰

MODEL RBS-40P.

Dip painted

The MEDALIST Model RBS-40G \$209.50

E-Z WAY TOWERS, Inc.

P.O. BOX 5767

TAMPA 5, FLORIDA

Class B Modulators

Larry Levy WA2INM

NOT many hams realize that the power supply for a plate modulator on an AM rig usually has to be larger, or as big as, the power supply powering the final.

In Class A applications, the power supply has to be able to deliver twice as much power as the final input. A Class A modulator has the maximum theoretical efficiency of approximately 30%. Practical efficiencies average about 20-25%. In an application where a transmitter of 100 watts input is being modulated by a Class A modulator, the modulator input will be between 200 and 250 watts. It could be more, as these figures are not counting transformer losses or mismatch.

Class AB modulators draw lower standby currents and therefore require a smaller power supply than Class A. The size usually is about equal to the one used to power the final. The efficiency runs about 40-50%.


The most efficient form of modulator is Class B. Class B differs from Class A and AB in that driving power is required, whereas in Classes A and AB no driving power is required, only voltage. Considering the cost per watt, it cost far less to get an additional 5-10 watts of drive than to build the additional capacity in the power supply. Most Class B circuits require a fairly stiff bias supply capable of giving a few mils of current. Several other circuits use triodes and require a large amount of drive. The most practical (and the simplest, therefore the cheapest) circuit is one using zero bias and tetrodes. The efficiency runs between 70 and 75% and the power supply can be about $\frac{1}{2}$ (or even less) the size

of the power supply used to power the final. It must be capable of large current peaks and well-regulated.

In a tetrode, the screen voltage as well as the grid voltage, has a lot to do with the plate current. In a case where the screen as well as the control grid are at ground potential, the plate current is extremely low, usually in the order of a few mils. When the screen starts to become positive, the plate current starts to increase greatly, as long as the grid is not negative. In the circuit shown, a very high audio voltage is applied between the screens. Resistor "R" lowers the voltage on the grid in the proper ratio. Otherwise, the grid dissipation of the control grid would probably be exceeded, as well as the fact that so much positive voltage would drive the tube into saturation and cause severe distortion.

In a typical cycle, with no signal, the screens and control grids of both tubes are at ground potential and the plate current is extremely low (5 mils per tube with 807's). When an audio signal is applied, on the first half of the cycle, one of the tubes (call it V1 for convenience) starts to conduct because of a positive voltage on the screen and control grids. At the same time, Va is driven beyond cutoff by the negative voltage on both grids. At the end of the first half of the cycle, both grids are at ground potential, and on the second half of the cycle the same thing happens with V2 conducting and V1 cut off. About 100 to 400 volts of audio are required between the screens, or 50 to 200 volts from each screen to ground. This varies with the tubes and power level at which the tubes are run.

T1 is an input transformer, the impedance matching the driver and the modulators. One possibility is to use a small hi-fi or PA amplifier to drive the modulators with T1 being a PP plate to voice coil transformer wired in reverse. Usually one delivering about 5 watts will do fine. T2 should match the modulator plates to the final. Sometimes connecting a small capacitor across the secondary of the modulation transformer will improve the quality of the modulation. If you desire to experiment, C2, which is optional, can be between 500 mmfd and .01. Usually one about .005 works well. The voltage rating should be at least two or three times the plate voltage on the final. The purpose of this condenser is to reduce some of the higher order harmonics of the audio signal. This will help reduce the

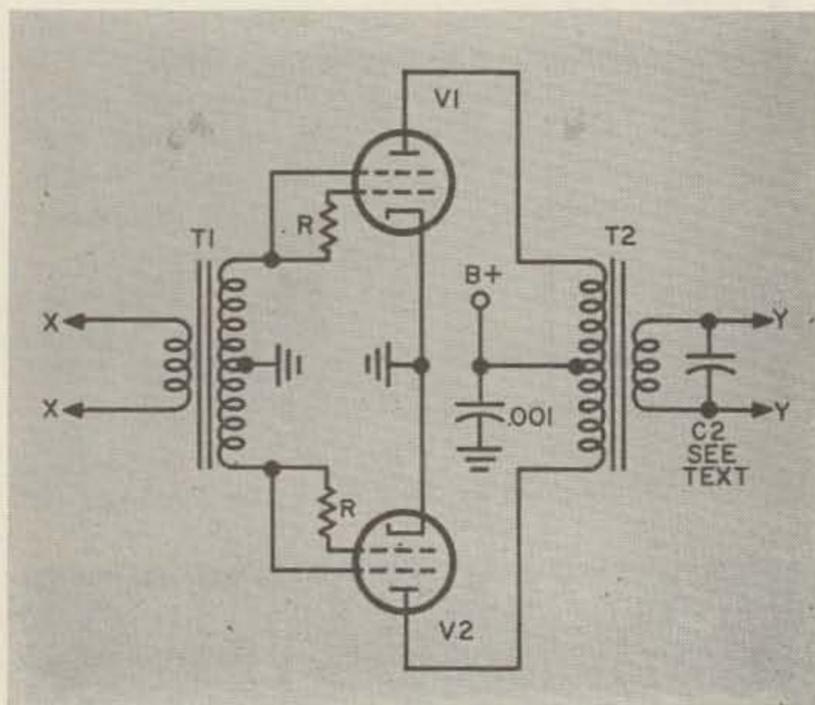

bandwidth of the signal. These harmonics, as well as higher frequency fundamental signals, may be present at the input of the modulator. There is also a possibility of the modulator itself generating some harmonics.

Using this basic circuit, modulators in almost any power class can be built. The one I am using uses 807's to modulate a 100 watt transmitter. The plate voltage is about 350 volts. The value of R is 27K. Approximately 3½ watts of drive are required. The standby current for two tubes is 8 ma. On modulation peaks this increases to about 220 mils. Using 750 volts and a little more drive, this same modulator can fully modulate a transmitter in the 200-250 watt power class. At 750 volts on the plate, the standby current is only about 15 or 20 mils. For lower power rigs, 6V6's will give about 18 or 20 watts output and will nicely modulate a 40 or 50 watt transmitter. 6L6's have more than enough modulation for a 6146, 807 or any transmitter up to about 80 or 90 watts.

The power transformer used in these modulators can be one taken from an old TV or radio. There is not much load on the power transformer as the peak currents are drawn for relatively short periods of time. Most of the time the standby current is only a few mils and this gives the transformer a chance to recover.

One possibility for a modulator tube is the 1625. The characteristics are identical to an 807 except that it has a 12 volt heater and a different socket. They are available for about 25¢ surplus and a pair of them are capable of modulating a 200 to 250 watt transmitter. They can be run at lower power levels, run quite cool, and are efficient. For lower power levels it is more practical to use lower plate voltages, as the efficiency (practical) increases when the tube draws lower standby current.

This modulator has been in use for over a year without any failures in tubes or components. The reason I mention this is that most of the parts come from the junkbox and some of them (especially in the power supply) are being subjected to overloads of 300-500 percent (on peaks). The results have been excellent and this modulator combined with speech-clipping in the driver completely modulates the transmitter at a cost lost lower than the power supply alone of a Class A modulator.

... WA2INM

Letter

Dear Sir:

This will acknowledge your letter of recent date regarding amateur radio call letters on registration plates. You are advised that no call letter plates are to be issued under the present plans for 1962.

William S. Hults
Commissioner of Motor Vehicles
State of New York

New York is a rotten state.

Swan Engineering Co. SSB Transceiver



- 130 watts PEP input to 6DQ5 Power Amplifier.
- High frequency crystal lattice filter; 3 Kc. nominal bandwidth, used for both transmit and receive.
- Unwanted sideband down approximately 40 db. Carrier suppression approximately 50 db.
- Transmits automatically on receiving frequency.
- Exceptional mechanical, electrical and thermal stability. Frequency is practically unaffected by voltage or temperature variations, or by vibration when driving over rough roads.
- Receiver sensitivity better than 1 microvolt at 50 ohm input.
- Smooth audio response from 300 to 3,000 cycles provides excellent voice quality for both transmitting and receiving.
- Control system designed for greatest ease of mobile operation. Front panel controls include: Main Tuning, Volume, Carrier Balance, Microphone Gain, Exciter Tune, P. A. Tune, P. A. Load, T-R Switch, Supply On-Off Switch, and Tune Switch.
- Main Tuning control is firm and smooth, with 16:1 tuning ratio. Calibrated in 2 Kc. increments.
- Transceiver produces approximately 25 watts carrier output on AM by simply adjusting the Carrier Balance control. Receives AM signals very satisfactorily.
- 3-Circuit microphone jack provides for Push-to-Talk operation.

POWER SUPPLY REQUIREMENTS:


- 275 volts DC, nominal, at 90 ma., receive and transmit.
- 650 volts DC, nominal, at 25-200 ma., transmit only.
- 80 volts DC, negative bias, at 6 ma., receive and transmit.
- 12.6 volts AC or DC at 3.45 amperes, for filaments.

A revolutionary new design by Swan Engineering provides single sideband communication at a surprisingly low cost. The one-band design gives exceptional high quality performance in all respects on the chosen band. The following models are available—

Freq. Range	Sideband
SW-175 3.8-4.0 mc.	Lower
SW-140 7.2-7.3 mc.	Lower
SW-120 14.2-14.35 mc.	Upper
SW-115 21.25-21.45 mc.	Upper

\$275
NET
PRICE

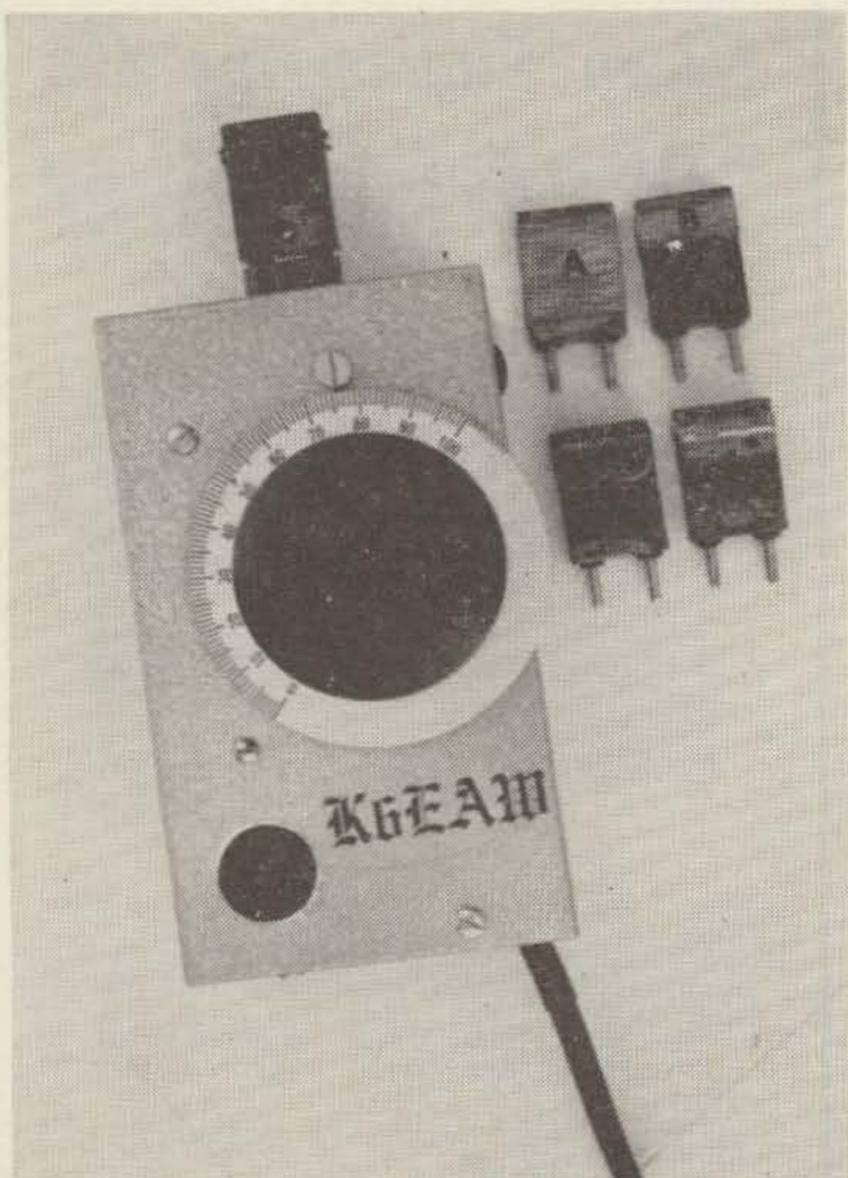ELLIOTT
ELECTRONICS, INC.
418 N. 4TH AVE.
TUCSON, ARIZ.



An "Eye" For Resonance

Roy A. McCarthy K6EAW
737 W. Maxxim Ave.
Fullerton, California

IF YOU don't have a grid dip oscillator you are probably missing out on a lot of the fun of ham radio. Simply knowing a new circuit is in tune before applying the power to it can change frustrating initial tune up procedures into pleasurable operating. Of course the GDO is far from being new, but the added expense is sometimes a bit too rough for hams on a limited budget. This one cuts the cost practically to the bone, especially if liberal use is made of junk-box parts rather than insisting on exact duplication. None of the components are critical in value.

Use of a tuning eye instead of a meter not only cuts down on the expense, but has a further advantage in that sharp dips can be detected which might be passed over with a meter. This is due to the instantaneous response of the eye. The major disadvantage of a tuning eye, namely the limited life of its brightness, was overcome by mounting it inside the case and using a simple optical system for viewing.

The instrument was intended mainly for use on the 6 to 80 meter bands. These are covered by four coils, each of which covers at least two ham bands. The inductance was adjusted so that a single calibration chart could be used for these ranges. A fifth range, covering approximately 50 to 100 mc was added, but no attempt was made to adjust it to the chart for the other ranges. This range acted a bit

peculiar, since it was approaching the upper frequency limit of the circuit.

The circuit uses the familiar Colpitts oscillator tuned by a two gang midget superhet type capacitor. The oscillator grid voltage is monitored by the miniature tuning eye. To allow for variations in the grid voltage developed in the oscillator a sensitivity control, R4, in conjunction with R2 acts as a voltage divider to set the eye's grid bias until the eye is nearly closed. A tuned circuit coupled to L1 absorbs power from the oscillator, reducing the grid bias, and causes the eye to open slightly, indicating the resonance frequency of the tuned circuit.

A filament transformer was used to furnish heater power for the two tubes, and a simple half wave rectifier and capacitor filter supply about 150 volts of B+. The only connections to the case are through the tuning capacitor frame and the rf bypass, C4. This prevents any possibility of getting a shock from the power line. The coil is isolated from any dc voltages present by C2 and C3. Use of over-rated capacitors will provide just about as much protection as the oil impregnated paper in most low cost transformers; however, for peace of mind a transformer using a 115 or 130 volt winding could be used to isolate the few milliamps used in the B+ supply.

The GDO was constructed in an LMB Tite-Fit Chassis Box #780, which is 5¼ x 3 x 2½

Order Now ^{from} **WRL's** Supermart of Values

Save \$38.00! Hurry! New WRL DesKit! IMMEDIATE DELIVERY

NEW WRL DesKit!

- Easy Assembly — Knockdown
- Mar-Proof Finish
- Beautiful Wood-Mosaic Appearance

complete
Only **\$29⁹⁵**
ONLY \$2.00 DOWN



EXCLUSIVE AT WRL!

- Functional Sloping Top
- Assemble in 1/2-hour
- No Glue or Nails Necessary
- Durable Nova-Ply
- Stable - Solid
- Slide-Out Writing Leaf

A functional, beautifully designed desk for the Ham and experimenter. Constructed of extremely durable Nova-Ply which is free from warp or shrinkage, the desk is easily assembled with only a screwdriver. Step-by-step instructions, rapid assembly, in only a few minutes. May be finished with commonly available kits. Takes an outstanding finish with smooth grainless Nova-Ply. Full sized, 49 1/2" x 29 3/4" x 31". . . . Shipping weight, 90 lbs. Order 6679007. WRL DesKit. Shipped Truck or Express.

SAVE 70%

Streamlined Cabinet with unpunched cadmium plated chassis and panel. For transmitters, receivers, amplifiers, etc. 15x7x9". Wt. 9 lbs. Was \$12.00. Order No. X79104

Only **\$3⁹⁵**

SAVE 60%

Carbon Hand Mike "Push-to-Talk"
\$2.99 BRAND NEW!

For PA, Mobile, and Citizens Band use. Internal resistance — 100 ohms, 70-7000 cps; sensitivity - 50 db. Brown plastic case; fits the hand, has loop for hanging. Supplied with 4 1/2' mike cord. Model 9979111

Lots of 6,
\$2.85 each

Exclusive Comet

VERTICAL ANTENNA KIT

Self-supported, Ground or Roof mounted, 10-80 Meter Vertical Antenna, handling up to 1 KW. No Guys. Easily installed. No Radials needed. 23 ft. overall height. 52 ohm Coax fed.

SAVE 50%

Model WVG of highest quality, heavy wall aluminum tubing with heavy duty base assembly and steel mast mounting bracket. Mounts at any convenient height. All hardware iridite treated. Order today! Order No. 6979053

ONLY \$14⁹⁵

Shipped Express

SAVE!

NUVISTOR PREAMP! (Model PV)

Uses the RCA 6CW4 Nuvistors for any one band; 6, 2, 1 1/4 meters. 2.4db Average Gain and at LOW noise figures. Requires 70-300VDC at 10ma and 6.3VAC at .13A. Fully wired and tested. Order by band. Model 79PV|(band)

Only **\$13⁹⁵**

SAVE \$7.17

NEW!

Only **\$1⁹⁹** **\$9.16 Value**
FRESH COAX

30 ft. RG8/AU 52 ohm coax with constant impedance 82-61 "N" plug each end. Coax alone worth \$5.40. Model X79037

TRADES - TERMS - BUY - NOW

LEO I. MEYERSON, WØGFQ

"We have the largest, cleanest Used Equipment Stock in the industry — more than 1000 units. Try us!"

EASY CREDIT
\$20 - \$50

ONLY \$2⁰⁰ Down

WE FINANCE OUR OWN PAPER!

WRITE FOR LATEST RECONDITIONED EQPT. LIST!

WRL WORLD RADIO LABORATORIES
3415 WEST BROADWAY • COUNCIL BLUFFS, IOWA 79S


LEO: Rush me the following bargains: _____

Enclosed is my check for: _____ plus postage
(All items F.O.B. WRL)

NAME _____ CALL _____

ADDRESS _____

CITY & STATE _____

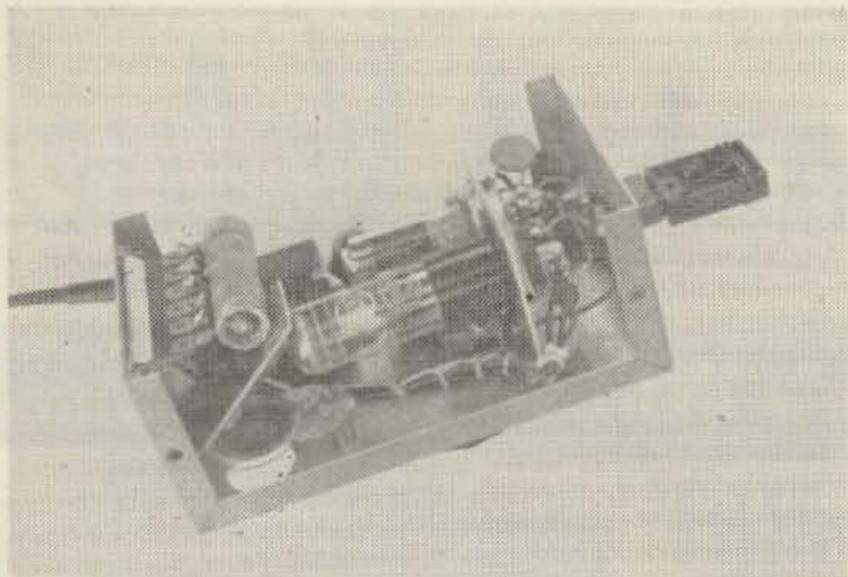

inches. All components used were standard radio parts except the tuning eye. The one used is a 7 pin miniature version made in Japan. These are made there by several manufacturers and are known interchangeably as the 6E5M and 6ME5. A regular 6E5/6U5 could be substituted if enough space is allowed for it in the layout. The tuning eye was mounted inside the case alongside the 6C4. A plain mirror is used to project the image through the hole in the top of the case. A small plastic lens is mounted just below the hole to provide magnification of the image. This provides easy viewing even in brilliant daylight. The mirror can generally be found in the xyl's discarded purse and cut down to size with a dime store cutter. The lens used was found in a box of Cracker-Jacks but similar ones are available in the Five & Tens.

Use of a crystal socket for the coil socket permits testing surplus crystals to check their activity and approximate frequency. The crystals which are defective can be dismantled and used for the coil forms. The cover is removed and discarded as are the various pieces of hardware inside. A piece of 1/16 inch plastic or similar insulating material is cut to fill in the space under the coil so that the turns wound on there will not be deformed by handling. The plastic should be cut a bit short so that the wires can be inserted into the cleaned out pins. Incidentally, cleaning out the pins (of the old solder) is simple if you merely heat them with the iron then give a mighty whoof of air into the xtal holder.

Wind the lowest frequency coil first and after checking its performance coat it with

Q coil dope quite liberally. Each higher frequency coil is then wound in turn, checking its tuning and adjusting the inductance as required by removing extra turns or folding back part of a turn. Adding the polystyrene Q dope has a negligible effect on the tuning. The higher frequency coils can also be adjusted slightly by spreading a turn or two away from the main winding.

A simple commercial dial calibrated from 0 to 100 was used in place of the usual hand calibrated dial. A graph was plotted showing frequency vs. dial reading and cemented to the bottom of the dipper, with a protective coating of plastic. The extra care used in trimming the coils paid off in an easy to read calibration chart, and 3.5, 7.0, 14.0 and 28.0 are at exactly the same spot on the dial.

Since the receiver in the shack only covers the ham bands it was used only for accurate spot checking of the frequency coverage. The remainder of the calibration was accomplished with the aid of an all band signal generator. Removing the cover of the signal generator exposed the coils & allowed using it as an accurate absorption wavemeter. The extra high band coil was calibrated by QRMing the TV set.


The construction and wiring are not particularly critical in view of the low frequency coverage intended. The best procedure is to get together the major component parts, then determine the layout and size of case needed. Individual calibration of the oscillator can be made a game rather than a chore by first winding a test coil to see what the circuit will do, then trying to wind the coils as close to the calculated numbers as possible.

... K6EAW

Coil Table

	Range	# turns	Wire size
A	3.2 to 7.4 mc.....	70	28
B	6.4 to 14.8 mc.....	24	28
C	12.8 to 29.6 mc.....	9 ³ / ₄	28
D	25.6 to 59.2 mc.....	3 ³ / ₄	28
E	50 to 100 (approx) mc.	1 ³ / ₄	18

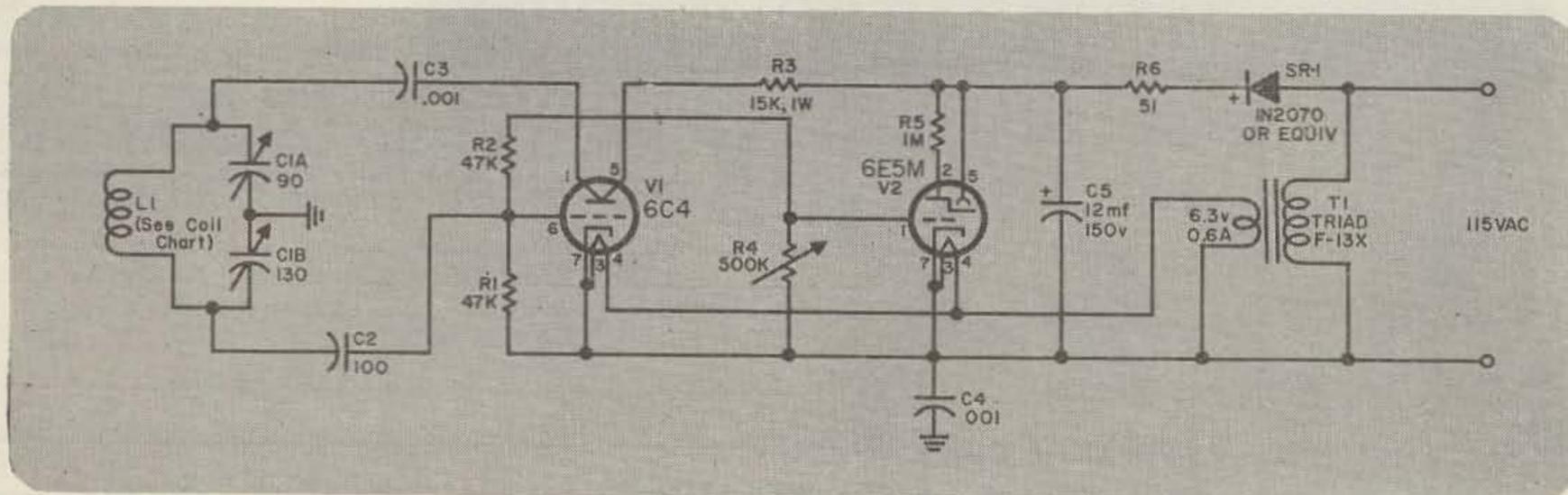All coils were close wound (except E) at the top of FT-243 crystal holders. Coil E had the turns spaced approximately 1/16 inch.



Break-In a la Transwitch

Ernie Austin W7AXJ
 Bob Austin K7DVB
 3211 S.E. Franklin St.,
 Portland 2, Oregon

4 transistors 22½ positive volts
 5 resistors 110 negative volts
 3 potentiometers Dash of capacitance

Mix judiciously. Connect to transmitter, receiver and TR switch. Adjust potentiometers for optimum operation. Place rig on air carefully. Relax and enjoy the finest and fastest CW break-in operation ever heard.

A transistor can readily be used to take the place of a relay in low current switching circuits such as grid-block transmitter keying arrangements. A typical circuit is shown in Fig. 1. The voltage applied to the emitter of the transistor can be as shown or may be obtained from sources such as the collector of the output transistor in the W5LAN version of the popular "TO" keyer. (Marland M. Old, W5LAN, "Transistorized Electronic Key and Monitor," QST, May, 1959.)

Break-in operation requires some form of control of the receiver gain. This, too, can be accomplished with a transistor. There are so many different circuits in use for receiver muting, however, that it would be impractical to attempt to describe how transistors could be applied to all of them. Therefore, this article will be confined to one arrangement which has been used successfully with the hope that it will inspire other circuit designers to develop units with broader application for presentation to the communications fraternity.

A particularly effective form of receiver muting is shown in Fig. 2. It will be recognized as the circuit used in some of the

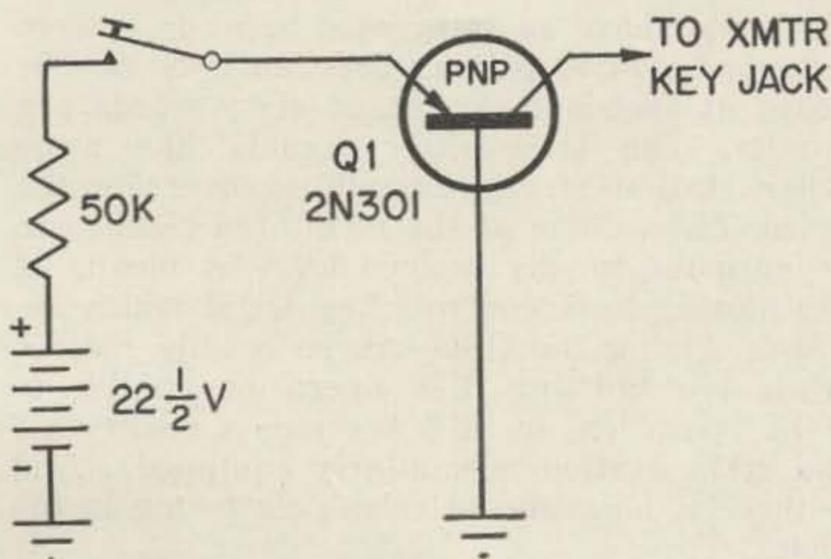


Fig. 1—Using a transistor in a transmitter grid-block keying circuit.

Hallicrafters receivers in which the sensitivity is controlled by varying the cathode resistance of several tubes. The "Monitor" potentiometer controls the receiver gain on "Standby" so that the receiver can be used to monitor the transmitted signal.

The transistor in the upper half of Fig. 2 has been added to the original circuit to reduce the sensitivity of the receiver when the key is closed and restore the receiver to normal sensitivity when the key is opened. The "Rec-Stby" switch is left in the "Stby" position when the transistor is used. Also the condenser which shunts the sensitivity control in the original circuit has been rewired so that it, too, is lifted from ground when the receiver is muted. This makes the receiver recover its sensitivity more rapidly so that breaks between dots can be heard at high keying speeds.

A "Muting Level Control" may be connected as shown in Fig. 2 and extended to some convenient location on the operating desk. This

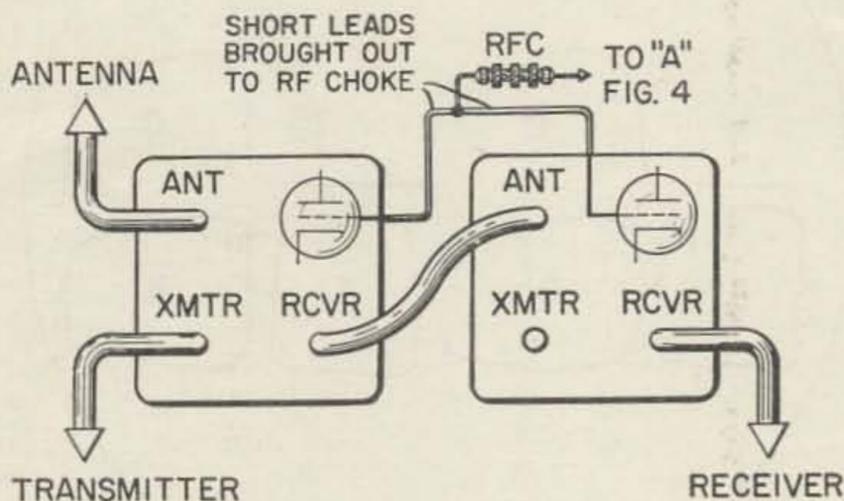


Fig. 5—Using two TR switches to increase isolation between transmitter and receiver.

makes it possible to adjust the monitoring volume level while transmitting. This control is labelled R1 on the diagram. When it is used the "Monitor" control is set at minimum gain.

It will be seen that two of the basic requirements of break-in operation have been met. However, these two circuits cannot readily be operated from the same keying source without too much interaction. It is advisable to introduce a third transistor.

Fig. 3 combines the circuits of Fig. 1 and 2 and adds the third transistor. Note that the first two transistors were PNP types while the third one is an NPN type. The base

of Q2 is now keyed by Q3 which, with its associated resistors and the negative potential source, take the place of the 15 volt battery and 15K resistor used in Fig. 2. The voltage divider potentiometer R3 determines the operating point of Q2 through Q3. It is adjusted for maximum receiver gain with the key open. The 0.5 mfd capacitor from the base of Q2 to ground and the 150K resistor, R4, from the collector of Q1 to ground, improve the timing characteristic of the circuit which is controlled by the 100K resistor R2.

The timing action of the circuit is shown in Fig. 6. The receiver gain is reduced to a very low level before the transmitter is turned on and the transmitter is turned off before the receiver gain is restored to normal. The amount of time between "receiver off" and "transmitter on" is the timing characteristic which is controlled by R2. R2 also affects the leading edge of the transmitted signal at some settings.

If the transmitter comes on before the receiver gain is reduced keying thumps will be heard in the monitored signal. These thumps will be generated in the receiver, giving a false indication of the signal transmitted on the air.

With some transmitter-receiver combinations using a TR switch this combined circuit may be adequate. However, if it is necessary

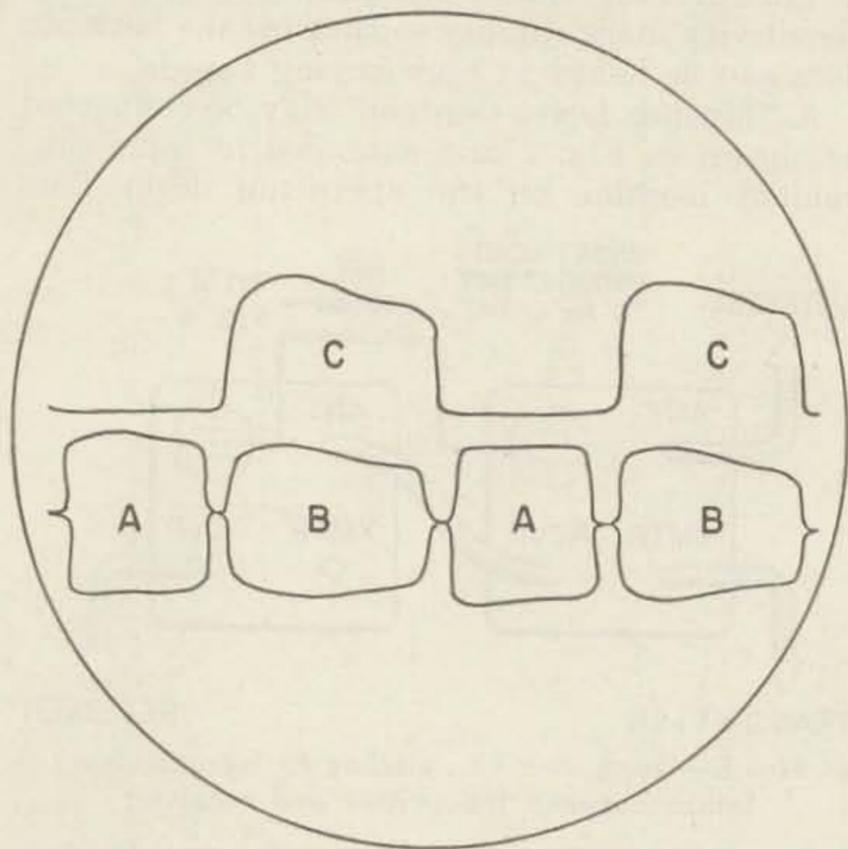


Fig. 6—Tracing of oscilloscope presentation of waveforms in antenna and in receiver if using the deluxe transistor break-in circuit. An electronic switch was used. The upper trace is from a demodulator probe at the transmitter output. The lower trace is from the receiver if with the receiver tuned to a steady carrier. The transmitter was keyed with steady dots at 18 dots per second (45 words per minute). The incoming carrier heard in the receiver is marked "A". The monitored signal in the receiver is marked "B". The transmitted dot in the antenna is marked "C". Note that the signal in the if drops to zero then returns to full sensitivity between dots.

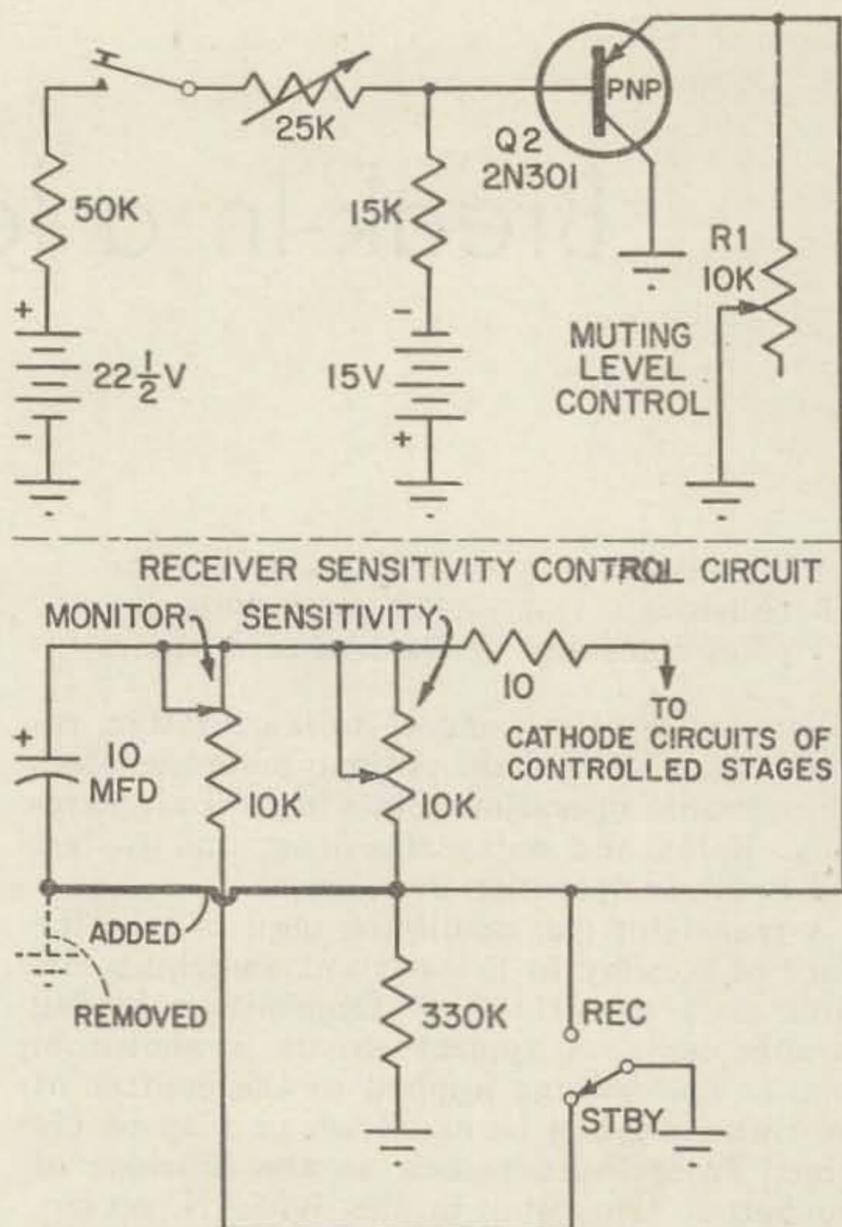


Fig. 2—Receiver muting with a transistor.

to reduce the level of the signal reaching the receiver from the transmitter through the TR switch, this can be accomplished with another transistor and use of the negative potential supply as a source of cut-off bias for the TR switch. See Fig. 4 and 5. The key-down bias may be insufficient to adequately cut off the TR switch and help reduce keying thumps. If this is the case the bias voltage at the TR switch grid can be increased by adding a second transistor as in Fig. 4a.

With high power it may be necessary to introduce more attenuation between the transmitter and receiver. In this case, two TR switches can be used. They should be connected in series and blocked simultaneously as in Fig. 5.

We now have an integrated break-in system using no relays. Breaks between dots can be heard at speeds in excess of sixty words per minute. The transmitter sounds like some other station strong enough to override the noise. The volume of the monitored signal can be adjusted to any desired level by means of the muting level control. Any QRM which develops during the QSO can be readily noticed while transmitting. CW operation similar to VOX operation on SSB becomes a reality (if the other station is similarly equipped). And—there is no sound of relays clattering in the shack.

Adjustment: R1 is the muting level or monitoring volume control. R2 is adjusted for

minimum clicks in the receiver when transmitting, consistent with good transmitter keying. R3 is adjusted to the lowest value which will give maximum receiver sensitivity with the key up.

Construction: All resistors shown in the diagrams are 1/2 watt. The potentiometers are volume control types and the capacitor can be rated at any value above 110 volts. The transistors may be placed in the circuits which they control or they may be mounted together with extension leads to the various circuits. At W7AXJ they are mounted in a small chassis with the electronic bug. There is no need for special construction practices except where there is excessive rf in the shack. In this case it will probably be necessary to shield the leads to the transistor bases where they are remote from ground. A better solution would be to shield the transmitter!

Use of transistors: Many words have been written on the theory and application of transistors. No attempt is made here to improve on the literature. Two simple precautions are recommended while experimenting with transistors in switching circuits. (1) Use a fairly high resistance in the base lead and (2) Limit the total current through the transistor to the amount specified by the manufacturer under "Characteristics for Switching Applications." Do this with suitable resistors in the emitter

Fig. 3—Break-in circuit using transistors in place of relays.


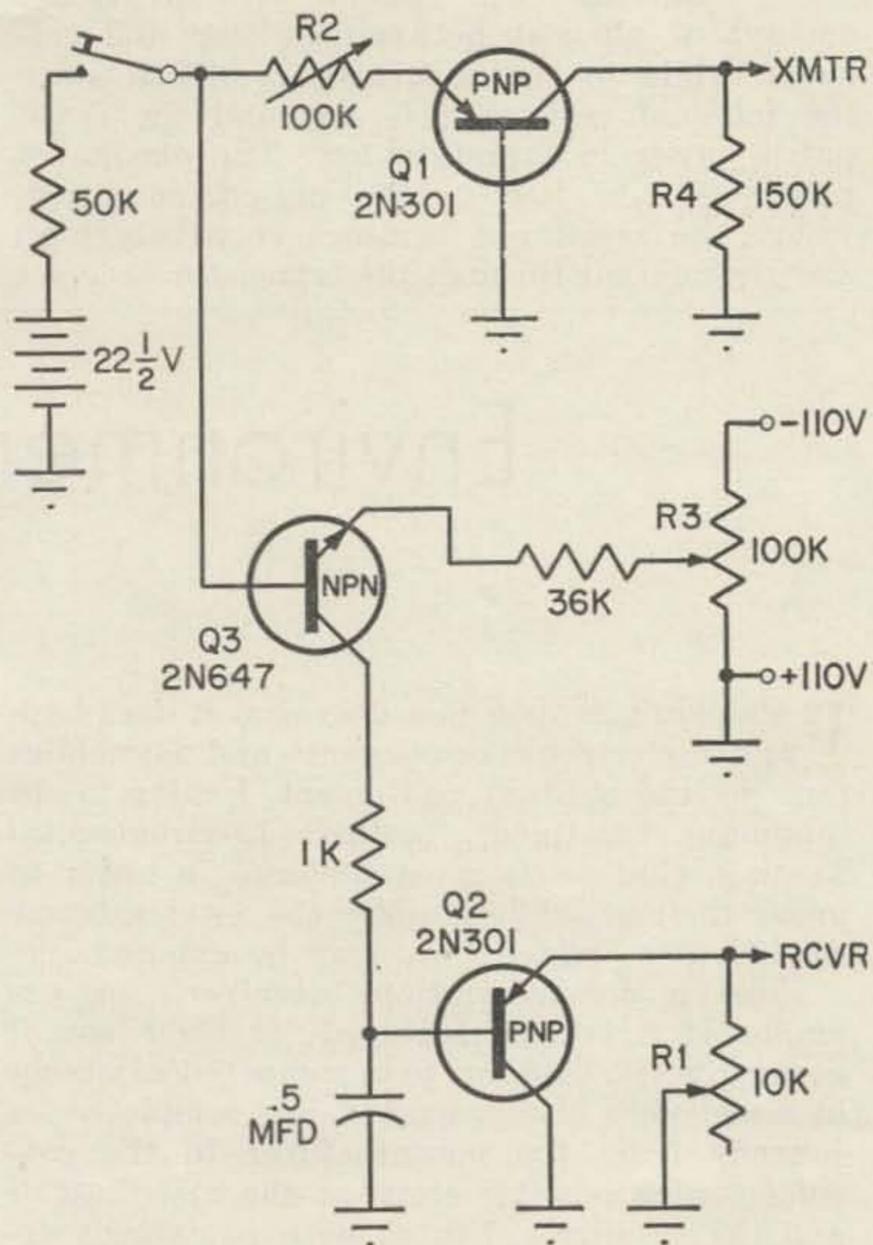


Fig. 4—DeLuxe transistor break-in circuit with blocking bias circuit for TR switch.

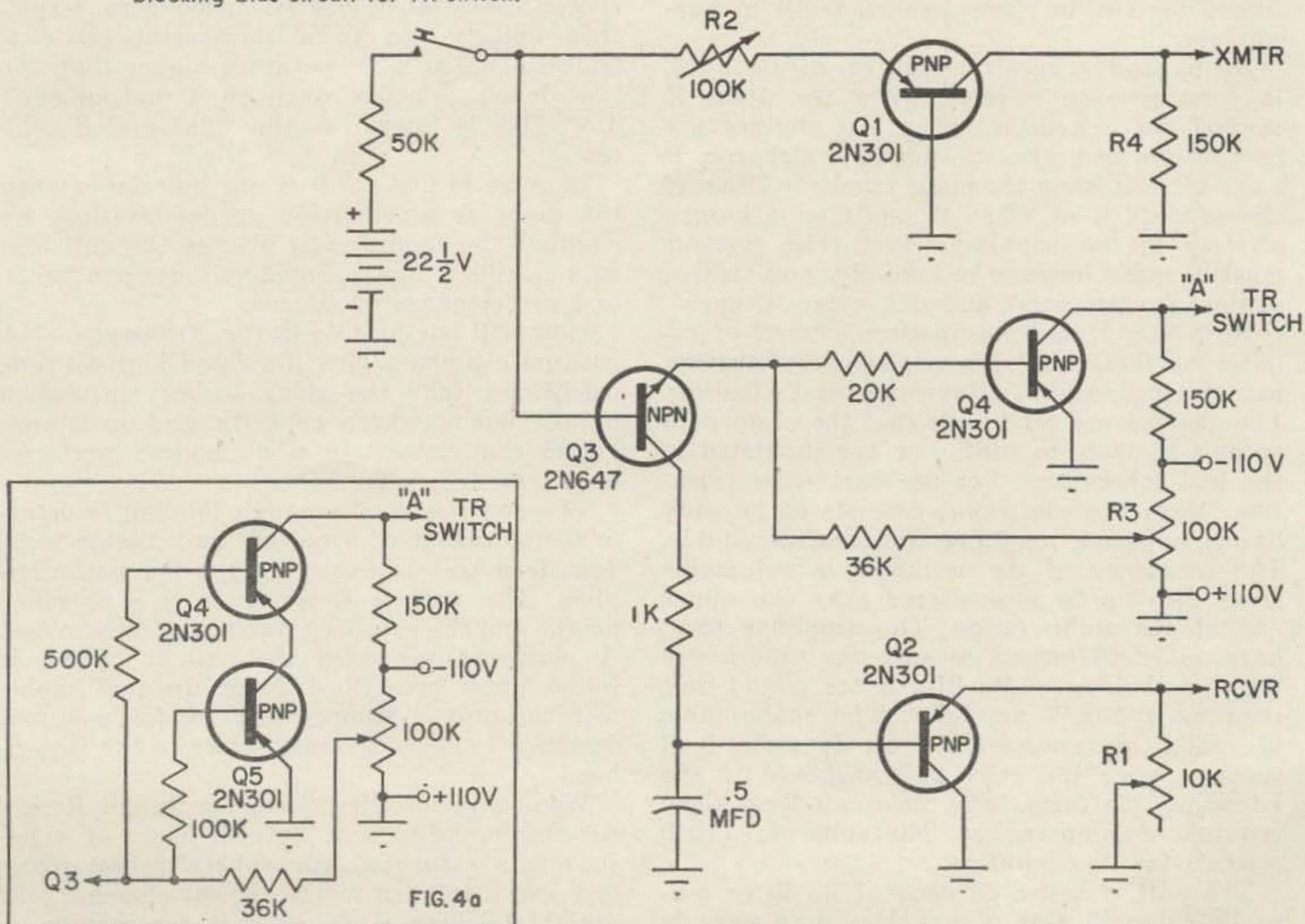

and collector leads.

A transistor will handle a surprising amount of current between emitter and collector while in the saturated condition since the internal resistance is low and the dissipated power is therefore low. The dissipated power is also low in the cut-off condition, where the resistance becomes relatively high and the current through the transistor becomes

very small. In this condition it is necessary to be careful that the voltage across the transistor is not excessive.

The transistor types shown in the diagrams need not be used. Any similar type should be satisfactory. Buy yourself a handful and hook them up. You will be pleased with the results—but watch that base current!

... W7AXJ-K7DVB

Environmental Testing

Joseph Leeb, W2WYM
549 Green Valley Road
Paramus, New Jersey

IT shouldn't happen to a dog—but it *does* happen to electronic components and assemblies that go into military equipment. I refer to the inhuman treatment, called Environmental Testing, that parts must undergo in order to prove their reliability under the most extreme conditions to which they may be exposed.

Take a communications receiver, for example. If it is manufactured for home use, it generally settles down to a pampered existence in somebody's shack, once it has completed its journey from the manufacturer to the consumer, with possible stops at the distributor's and the retailer's. Not so with equipment designed for use in planes, ships, tanks or submarines.

Let us study a receiver built for aircraft use. It must operate reliably when the plane is taxiing for a takeoff, when the engines are revving up, and when the plane is airborne. It must not fail when the plane climbs to 30 or 40 thousand feet, or when it lands on a bumpy airstrip in the burning desert. The receiver must be made immune to humidity and treated against fungus, sand, and salt water spray.

How does Uncle Sam assure himself of reliable performance? By means of exhaustive, painstaking, brutal Environmental Testing. The most severe conditions that the component or unit is likely to encounter are simulated in the test laboratory. Let us start with vibration. Here the equipment consists of an oscillator, a power amplifier and a shake table. The frequency of the oscillator is adjustable from zero up to somewhere near the upper end of the audio range. The amplifier must have sufficient output to give the unit under test the shaking of its life. A ten pound unit requires a 5 KW amplifier. The shake table is really an enormous electrodynamic loud speaker, with the voice coil anchored to the vibrating platform. The field winding alone requires 5 amperes at 200 volts dc (1000 watts!) for its excitation.

The unit is tested in each of its three mutually-perpendicular planes. If a man were to

be given a vibration test (let's hope it will never come to that!) he would be shaken first standing up, then on his back, and, finally, lying on his side. In each position he would be securely anchored to the shake table.

Now comes the "search". The oscillator dial is swung slowly back and forth to determine the resonant frequency, or frequencies, of the test unit; in other words, the point or points on the dial where it vibrates most violently. While vibrating thus, the unit is fed rated voltages and its performance is monitored.

To make sure our unit will not conk out it taken to a place like the DEW line, it is put in a deep freeze at 65 degrees below zero, tested, then quickly put in a thermostatically-controlled oven, at a temperature higher than the heat inside a boiler room on a midsummer's day. This is known as the "Thermal Shock" test.

In order to find out how our unit fares when the plane is accelerating or decelerating, we simulate the condition by placing the unit in a spin chamber. Again, rated voltages are fed in and performance monitored.

How will our unit do in the stratosphere? A vacuum chamber, with simulated high-altitude conditions, tells the story,—where insulation breaks down, where capacity and resistance values change, and in what manner performance may drop off.

The end result of a rough landing is determined by means of drop, jolt and jumble tests. The drop test is exactly what the name implies. The unit is dropped from a specified height and the resulting damage, if any, noted. A platform, to which the unit is bolted, is jolted by a prescribed force. In the jumble test, the unit is bumped in a random manner, designed to show up weaknesses in the fastenings.

We now go into the "Steaming Jungle Room" for the humidity test. Several hours of exposure to a saturated atmosphere, a salt spray test and a sojourn in the fungus chamber will decide the fitness of our unit for service on

a tropical isle.

Before the unit is subjected to the aforementioned treatment, the individual components must prove their worth. Capacitors are carefully checked for leakage, breakdown voltage, power factor and dissipation factor, under various environmental conditions. Resistors must prove themselves within specified limits of ohmage, and current-carrying capacity under extreme heat and cold. Fuses must blow within the specified number of milliseconds after application of current, as measured by an electronic counter. The hermetic seal on the ferrules must permit no moisture to leak in at high altitude or pressure. How do we detect the presence of a droplet of moisture hardly bigger than a molecule? Test fuses are dropped into a beaker of fluorescense solution, and the beaker placed in a vacuum chamber. After taking the fuses up to the required altitude or pressure and back to sea level pressure, the components are rinsed in running water and examined under ultraviolet, or "black" light. The most minute particle of fluorescense will glow brightly under this influence.

Hookup wire is checked for insulation resistance and breakdown voltage, in addition to resistance per foot and mechanical dimensions.

Connectors are checked for insulation resist-


ance, voltage breakdown at high altitude, and contact resistance, among other things. In the contact resistance test, rated current is passed through each pair of mating contacts and the millivolt drop is recorded. This calls for a 4-wire hookup—two wires for feeding the current into the connectors, and two wires from the millivoltmeter to specified points on the connector contacts.

If the unit is to operate near combustible gases, it must be made explosion-proof. Every pair of make-and-break contacts must be bypassed with capacitors or Zener diodes, to completely eliminate arcing. Elaborate grounding must be employed if the unit contains moving parts that might generate static electricity. Connectors must have hermetic seals.

A sufficiently large random sampling of a production run is made for environmental test purposes to ensure reliability of the end product. For example, the specification may call for the testing of 10%, or a minimum of 50 pieces, out of each lot, regardless of how small the lot may be. It frequently happens that the entire lot must be destructively tested, if the lot happens to be a small one.

So—next time you buy a piece of surplus equipment, treat it with respect—it has been through fire and was not found wanting.

... W2WYM

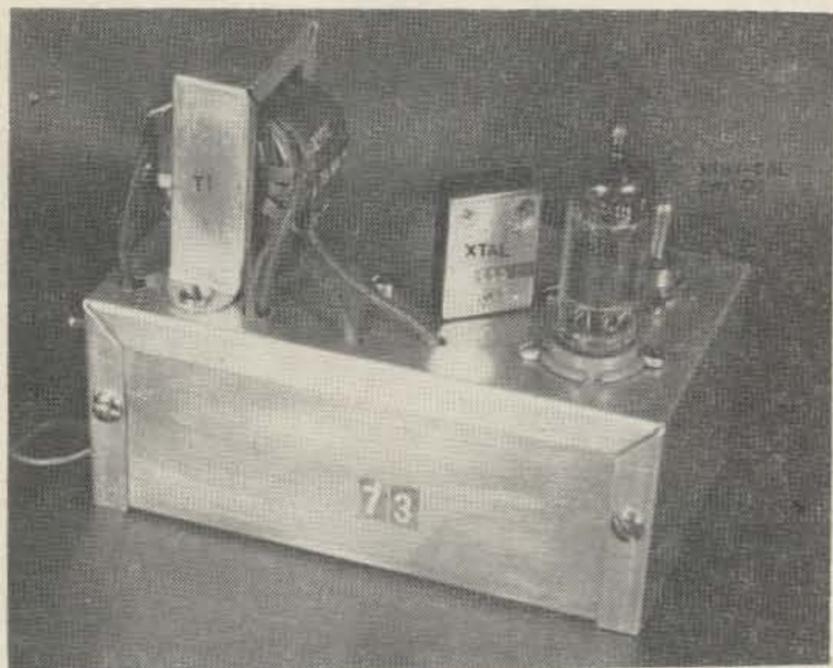

All Band Band Edge Marker

Charles Berner WA2HRZ
125 Navy Walk
Brooklyn 1, New York

Photo taken by S. Blechman


A while ago, the editor of this magazine gave some advice to teenaged hams concerning the writing of articles for 73. I took this advice and, after hocking my switchblade, bought the necessary parts for this undertaking with the money raised from this sale.

I had a commercially made 100 kc xtal calibrator whose performance didn't satisfy me at all. I reasoned that since the ham bands are harmonically related, why not use a 3.5 mc xtal to obtain the marker signals. Table 1 shows that the higher you go in frequency, the higher the multiple of the fundamental. As the multiple increases, the signal strength decreases, and by the time you get up to 10 meters you have practically nothing. Not so

with a 3.5 mc marker; the eighth harmonic will place you right on 28.0 mc, while the 280th harmonic is needed with a standard calibrator. This makes some difference in signal strength! This unit has been tested on 1 1/4 meters and works quite well.

Believe it or not, the total cost of this gem is only about \$11. In fact it cost me exactly \$11.79, including the confounded 3% city sales tax. This nominal investment shows that by homebrewing your equipment, you can double the performance of a commercial unit at half the cost.

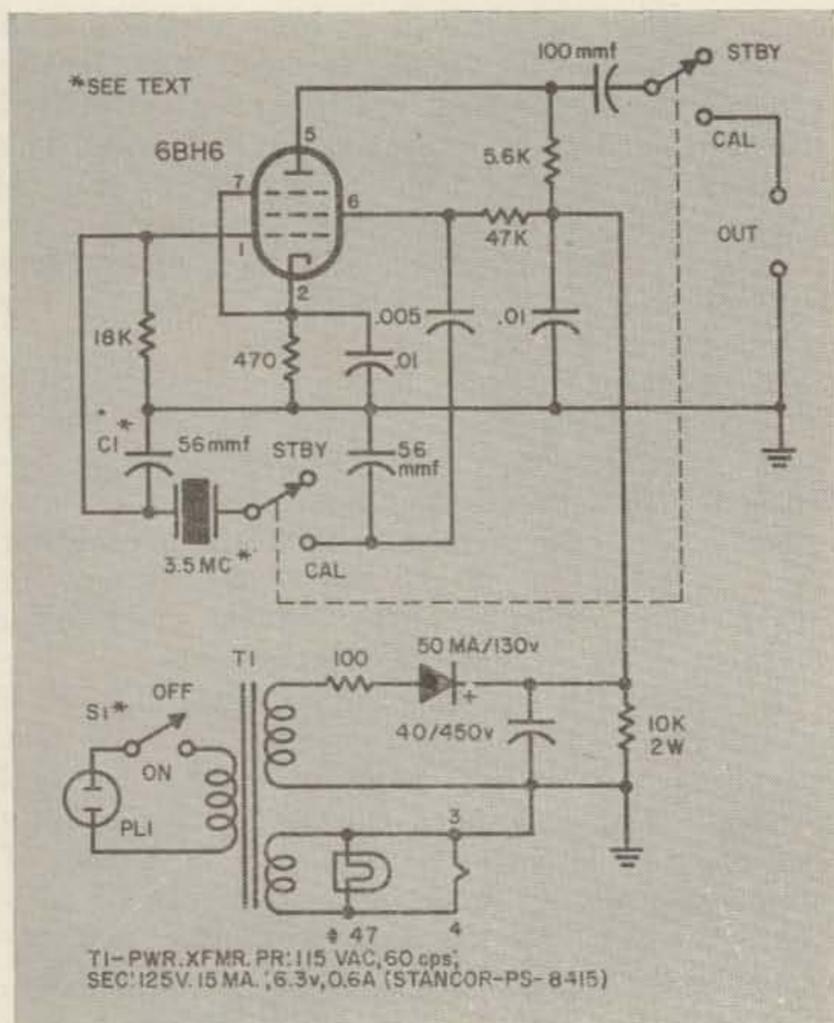This calibrator is complete with its own ac supply, eliminating the need for taking power from the receiver. If ac outlets are at a premi-



um at your shack, the on-off switch and the line plug can be eliminated and the ac line connected across the receiver's ac input so that the calibrator comes on whenever the receiver is turned on. A high density selenium rectifier was used and this contributes greatly to the compactness of the unit. The whole thing runs very cool and even after 24 hours operation, still isn't hot.

Wiring isn't too critical, but keep all leads short and direct. Using an octal socket for a

xtal holder lets you use the unused pins as tiepoints and is recommended.

A Petersen type Z-2 xtal was used because it has a tolerance of .002%. This is one reason why no provision is made for "zeroing" the calibrator against a standard. The other is that there isn't any such standard as WWV for use. However, if this provision is desired, C1, the 56 mmfd capacitor, connected to pin 1 of the 6BH6 thru the 18K resistor, can be made variable. Also, if band edge markers are wanted for 50 mc and up, a 5 mc xtal may be substituted when this function is wanted and C1 made variable for "zeroing" against WWV.

This gadget can also be used as a xtal activity checker by simply replacing the marker xtal with the xtal to be tested. Tuning your receiver should get you a strong signal at the xtal's fundamental if it is OK.

I would appreciate hearing from anyone who has come up with additional uses for this unit. Please send all letters to my home QTH as Wayne may think that they are bills and burn them.

WA2HRZ



Table 1:

Band	Harmonic		Marker Frequency
	3.5 mc	100 kc	
80 meters	1	35	3.5 mc
40 "	2	70	7.0 mc
20 "	4	140	14.0 mc
15 "	6	210	21.0 mc
10 "	8	280	28.0 mc
6 "	15	525	52.5 mc
2 "	42	1470	147.0 mc
1 1/4 "	63	2205	220.5 mc
1 1/4 "	64	2240	224.0 mc

Pi

The Pi output circuit (A, above) has practically supplanted its predecessor the parallel tuned circuit in modern day ham transmitters, and is so-called because of its resemblance to the 16th letter of the Greek alphabet, π . The Collins Radio Company is generally given credit for first making extensive use of it and indeed it is still referred to in some quarters as the Collins coupler. The circuit can be redrawn as in B, above, to permit comparison with the more familiar parallel tuned circuit. "A" is the tuning capacitor and "B" the loading capacitor. With "B" at full capacity (minimum loading) the antenna connection point is practically at ground potential. With "B" toward minimum and "A" retuned to maintain resonance more and more power flows out

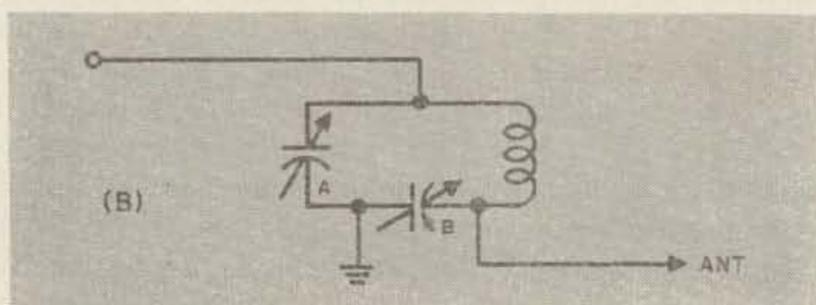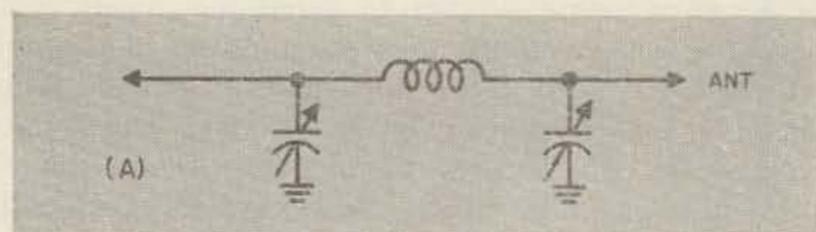the antenna as it is in effect disconnected from ground. . . . W₀HKF



Tell The World

How to Get Free Publicity

Jim Kyle K5JKX/6
1851 Stamford Ave.
Santa Susana, Calif.

IF MY boss ever reads this article, I'm liable to find myself fired. Because by trade, I'm a newspaper reporter—and we're supposed to foil publicity attempts, not encourage them.

But if you follow the instructions I'm about to give you and come to see my boss, I'm not worried about the job coming to an abrupt end. If you do this, what you have to offer will be news, not publicity—and news is what we're paid to find.

Let's back off a little and start at the beginning. Why do we, as hams, want publicity?

That's not so easy to answer as it sounds. Too many of us just want to see our names in print, to have something to show off.

But the major reason, I hope—and the reason I'm writing this article—is that without good publicity, our hobby stands in serious danger.

Frequency allocations are valuable. As Wayne has been telling you repeatedly, while commercial interests are aware of the value of amateur radio in providing tomorrow's engineers, they forget about our value when they see all that space we take up—space that they want!

So far, we've done fairly well in keeping ourselves in existence. We've lost only two bands in as many years. But we have to keep at this business, and one of the best tools for doing so is publicity.

A former governor of the state of Oklahoma had a famous saying: "There ain't no such thing as bad publicity."

He wasn't completely right, but too many of us are shrinking violets when it comes to telling the world of our services and accomplishments as hams. And we're so afraid of bad publicity at times that we forget that any subject can be handled at least two ways. Even TVI can be made palatable with proper treatment.

So now you know that the aim of publicity is to promote the good name of ham radio rather than to blow the horn of any particular amateur. How do we go about doing this?

There's a simple two-part formula that will get you space in almost any publication or air time on radio and TV. It's this: 1—Do something worth while, and 2—Let the news media know about it.

Let's take a closer look at this. It may sound a little bit too simple to work out, but it's not.

By "doing something worth while," I mean something that John Q. Televisionviewer will

think is worthwhile. You know and I know that it takes a tremendous amount of skill to work all states on 144 mc or to snag some rare DX. But is it worthwhile?

Not to old John Q., who thinks 144 megacycles means a gross of those things traffic cops ride on.

But any of your public service activities are horses of significantly different hues.

For example, in Oklahoma there's a storm warning net which operates on 3850 kc. These boys track tornadoes, and it's easy to show that their activity has saved a number of lives.

That's something worthwhile.

As a matter of fact, in the last two years I've written four feature stories about this same bunch of hams. Every one of these stories has proved to some 300,000 readers that hams are public-spirited citizens.

Or civil defense work. There's something worth plugging. There are all sorts of photo possibilities in the workings of a CD net, possibilities that any photo editor in his right mind, with a view to local news, will jump at.

You don't have to do anything big and ambitious, though. Nearly every one of us has, at some time or another, helped a fellow ham do something. Maybe the other fellow is paralyzed and can only communicate with the world via radio, and you've helped him get a new rig in place.

That's human interest, friend, and that's what the editors go into ecstasy over.

Or if you like to handle traffic, possibly you have taken messages from servicemen overseas on holidays or birthdays.

Actually, the list is nearly endless. Just remember, look at your accomplishment through the eyes of someone who knows nothing about the technical end of radio and cares less, and evaluate it from his viewpoint.

If it still seems interesting, brother, you've got a story. But if it only appeals to another ham, put it on the shelf and try again.

So you've decided you have a story; what do you do next?

First, here's what *not* to do. Don't, under any circumstances, call the editor just at deadline time and ask him, "How about some publicity for ham radio?" Not only will you get turned down flat, but hams' names will be mud with that particular editor from then on.

Instead, call him at a lull hour—for a morning paper, that's about 2 p.m., and in the case of an evening paper, about 3:30 to 4 p.m.—

and tell him you think you have a human-interest (or public-service) story possibility.

You might present it this way: "Mr. Smith, my name is Joe A. Hamm. I'm a member of a group of people here in Anytown which has organized to provide emergency communications for disasters or civil defense. There are 17 of us in the group—all local people—and we're working with the sheriff's office to help out whenever they need us. We're having a meeting Friday night, and I thought you might like to get a story about our public-service activity."

With that kind of presentation, he's not going to turn you down cold. Even if he can't get a reporter out to cover your meeting, he'll be interested in hearing more about your activities.

And you've got the foot in the door toward good relations with the press.

An even better approach, actually, is to locate a friend who's a friend of the editor. Through the mutual friend, get acquainted with the editor on a personal basis. If you can't work it with the editor, get a reporter instead. The idea is to know somebody in the news room.

Then, when you have the editor or reporter hooked, get him interested in what you're doing. Follow the ancient secret of the female race and let him chase you until you have him where you want him.

Plant your human-interest or public-service possibilities in his path, but let him think he's discovered them for himself. He'll be a lot more enthusiastic about them if you do.

And don't ever expect friendship to keep him from printing any bad publicity. That seldom happens. The way to avoid bad publicity is to prevent unpleasant incidents from ever happening in the first place. If it happens, and the newsman is worth his pay, he's going to print it.

An important point in this business is to let the media know in advance, wherever possible, what you're doing.

If you have a CD drill, for instance, and wait until it's all over before telling about it, you'll be lucky to get a two-paragraph item listing the names of those present.

But if you plant it in advance, then the editor can send out a writer and a photographer and make a major feature out of it. And in the newspaper or TV news business, good local features are worth their weight in gold. They're rare.

Be prepared for what seem like stupid questions. Chances are the reporter who handles the story will know from nothing about radio. He's going to ask some foolish questions. If he doesn't, he's not getting your complete story. You just be ready to answer them in language he—and his readers—can understand.

Ham talk is full of abbreviations. U cn see

hw odd it is at times, but when ur in QSO both you and the guy on the far end are talking the same lingo.

The reporter won't know the language, unless you're lucky and find another newspaper office with a ham in it.

Don't think he's stupid just because his questions sound that way. Would you know what to do if someone told you to: "Put a set of dingbat lines on that four-column and rush it up, I need it for the first!"?

If you take a little time to make sure the reporter understands exactly what you're up to, you'll get a better story out of him, and the publicity will achieve its purpose.

But don't go too far and try to tell him how to write the story, or ask him to let you go over it after he's through.

Any newsman worth his pay is a specialist. He knows at least one thing well, and that's how to write. Most of them spend most of their time writing about things which are foreign to them, and they're pretty good, as a rule, in this matter of getting the details correct.

He'll be touchy about you going over the story. To him, that means you want to censor his work. As a matter of fact, he even hates for the editor to check his writing when he turns it in!

But if he seems completely confused, it won't hurt to offer—not ask—to go over the piece with him when it's finished to catch any possible errors or mistakes in detail. If he's really mixed up about what you're doing, he'll appreciate the help.

If this happens, be careful. Don't say a thing about his writing or his approach to the story. Just watch out for technical goofs such as a transmitter on the "one-kilowatt band" and leave the writing style alone. That way, you'll get along fine with the writer.

And as a final word, don't try to work the newsmen to death. About one good story every three months or so is all any one medium can take on any subject. Editors have long memories, and if you call much oftener than that you'll get the reputation of being a publicity hound—and that will be the end of your efforts.


Of course, he can take a public service story now, and a human interest yarn then, if they involve different hams. And any activity that ties in with other news stories—March of Dimes telethons, floods, brush fires, missing-persons searchers, etc.—is nearly always good for a news story on the ham angle alone. Just be sure to let him know right then—not a week later.

For in the news business, there's a saying: "There's nothing deader than yesterday's story." When you're involved in something timely, take a minute to call the editor and let him know. Otherwise, let him know in advance. That way, you'll tell the world.

K5JKX/6

NEW from

Space-Raider

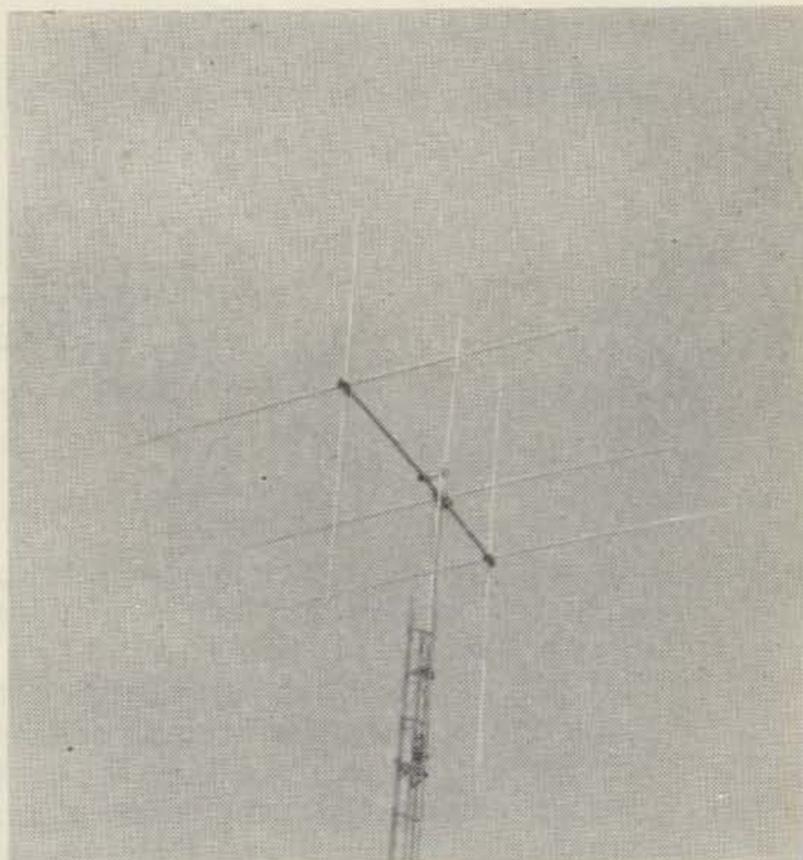

Hailed by HF men as a major break through in antenna design and performance, the famous K6CT polarized diversity beam, based on the proven principles of the Yagi parasitic array and Brown turnstile antennas, and using the rugged plumbers delight construction.

Minimizes QSB due to polarization shift, increases forward gain 50%, F/B ratio by 70% and side rejection to a level heretofore considered impossible.

After one year of rigorous tests under all conditions, proving the validity of design concept, its superior performance is now well known to the DX fraternity on 10 meters.

Space-Raider is pleased to announce the first of a new family of beam antennas, which was the DX contest winner in W6 land in October of 1960 and also is consistently reported as the first in and last out and many times the only U.S.A. signal readable. For comments at the other end; ask about this antenna of VK6QL (78 QSO's), ZL2UD (44 QSO's), LUTDAB (15 QSO's) and KA2EB.

The new Space-Raider Polarized Diversity Beams are all-aluminum construction of course, including all elements, boom, support mast, hardware and matching section.

Boom and mast material used in Space-Raider beams is of 6063-T-6 alloy which together with the elements carries the A rating in the standard scale of corrosion resistance thereby insuring maximum resistance to corrosion. Aluminum hardware is of high strength Aircraft Alloy. Bolts and nuts are steel 5/16 Standard hex and are especially plated to resist corrosion.

NO COMPROMISE has been made with quality and ruggedness in producing these fine light weight heavy-duty antennas.

10 METER BAND

Model	Specifications	Amateur Net	Weight
B-10-66	K6CT Polarized Diversity Beam, 6 element. 1 1/4" O.D. Center Sections; 1" O.D. & 3/4" O.D. adjustable end sections. Boom: 2" O.D. 15" long. .125 .19 Spacing Forward gain 12 D.B. Front/Back ratio; 44 D.B.	\$70.00	32 lbs.

15 METER BAND

B-15-6	K6CT Polarized Diversity Beam, 6 element. 1 1/4" O.D. Center Sections; 1" O.D. & 3/4" O.D. adjustable end sections. Boom: 2" O.D. 15" long. .125 .19 Spacing. Forward gain 12 D.B. Front/Back ratio; 44 D.B.	\$70.00	32 lbs.
--------	--	---------	---------

20 METER BAND

B-20-6	K6CT Polarized Diversity Beam, 6 element. 1 1/4" O.D. Center Sections; 1" O.D. & 3/4" O.D. adjustable end sections. Boom: 2" O.D. 24' long. .125 .19 Spacing. Forward gain 12 D.B. Front/Back ratio; 44 D.B.	\$114.50	44 lbs.
--------	--	----------	---------

6 METER BAND

B-6-12 COMING SOON

Direct inquiries to:

Space-Raider
ANTENNAS & CRANK-UP ANTENNAS

PREPAID SHIPMENT U.S.A.—DIRECT INQUIRIES TO
1076 E. WALNUT ST., PASADENA, CALIFORNIA

Zero-Shift Keying

Jim Kyle K5JKX/6

ARE you an experimenter, looking for the opportunity to pioneer new fields? Then maybe this article is for you.

Let's admit right off that it's theoretical; although it includes several schematics, none of the equipment has been built or tested—which means that the system may have a number of hidden bugs. However, all the component parts of the system have been used in other branches of electronics with success—and there's no apparent reason why they won't do as well here.

Even if the entire system had been built, it couldn't be tested on the air (except at microwave frequencies, which offer their own problems) under present regulations—which means that if it works for us in our bench test, we'll have to petition the FCC for permission to use this type of modulation on the more-popular ham bands.

But, if it works, getting permission to use it should pose no problem, because the gadget is a high-speed RTTY system requiring virtually zero bandwidth. It's also almost impervious to interference, noise, or other disturbances, and utilizes present equipment with less modification than is necessary with present-day RTTY gear. Only one attachment is necessary at the transmitter, containing a single stage, and another at the receiver.

The entire system is based on the fact that RTTY is basically a binary pulse-code modulation system, in which groups of five pulses convey each letter. Most RTTY activity today uses frequency-shift keying, in which one frequency is transmitted to indicate the presence of a pulse and another frequency is sent to indicate pulse absence. These are known as the "mark" and "space" frequencies.

Commonly, mark and space frequencies are separated by 850 cycles (the value is a carry-over from landline teletype operation) although regulations allow us to use any shift between 0 and 850 cycles.

Now, let's back off a minute and look at the situation from the viewpoint of a digital computer engineer. His hardware operates with strings of binary pulses which are either there or aren't there, too. Instead of mark and space, he calls them "one" and "zero", but it's the same situation. To him, a teletype transmission is simply a chain of 5-bit pulse trains.

One of the larger problems facing computer men today is that of transmitting data from one computer to another cross country, and they've put a lot of study into it. They've analyzed almost every possible form of modulation from the standpoint of easy separation of "ones" and "zeroes", and the system we're describing is based on this study.

Take a flow of direct current. Its polarity may be either positive or negative. This provides a binary representation, which in fact has been used in the trans-Atlantic cable.

However, it's difficult to transmit dc over the air, so let's turn our attention to a sine wave. It, also, may be either positive or negative. That is, the sine wave may be either in phase with a known reference, or 180 degrees out of phase with the reference. This, too, provides a binary representation.

In other words, "mark" can be represented by an rf sine wave of any desired frequency and "space" would then be a sine wave of the same frequency but 180 degrees opposed in phase. Since frequency would remain unchanged, bandwidth of the system would approach zero (actually, in FM terms the signal would have infinite bandwidth every time the phase changed and zero bandwidth in between. However, energy content at any one frequency of a signal of finite power spread over an infinite band is infinitesimal and can be ignored).

To accomplish this in an actual transmitter,


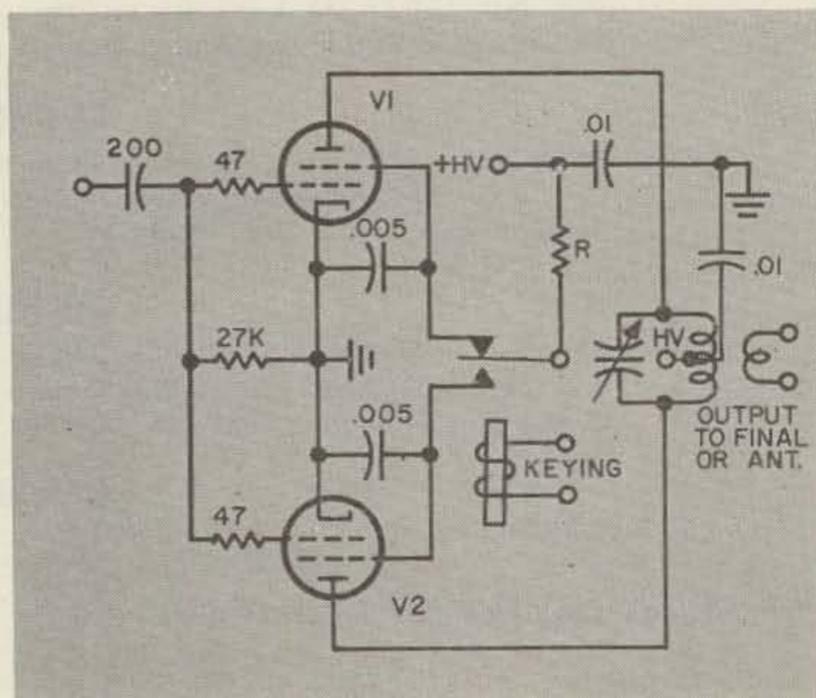


Fig. 1

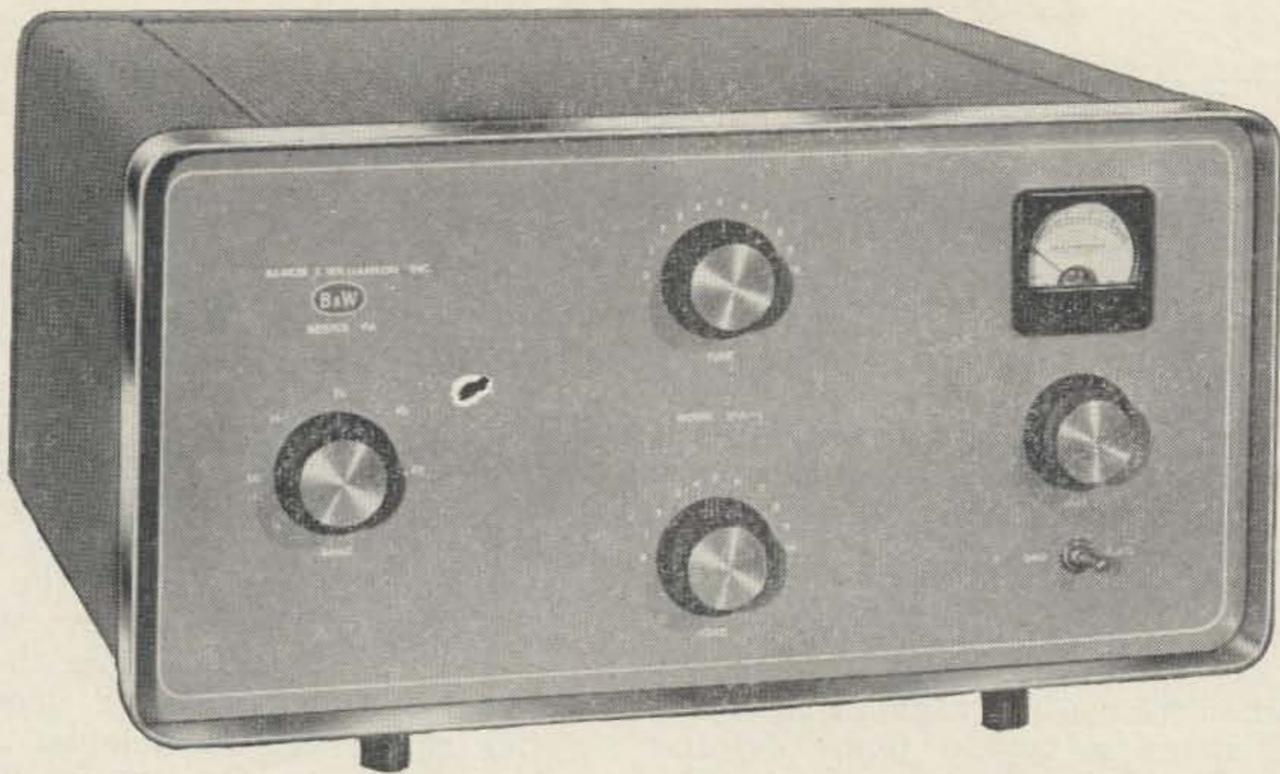

NOW

LPA-1 AVAILABLE IN KIT FORM

The most copied grounded-grid 1-KW linear amplifier by those who build their own.

AMPLIFIER KIT

LPA-1 Kit—(less tubes, cabinet and blower).....	\$269.50
Blower—(optional for warm climate use)	19.95
Cabinet—	48.75
LPA-1 Amplifier—Factory wired and tested Complete with cabinet, blower and tubes	375.00

POWER SUPPLY KIT TOO


LPS-1 Kit—(complete with cabinet but less tubes) .	\$169.50
LPS-1 Power Supply—Factory wired and tested Complete with cabinet and tubes	205.00

(See Nov. QST, page 115 and Nov. CQ, page 21, for outstanding features)



LPA-MU Matching Unit Price \$36.00
LPA-MU-2 Matching Unit Price \$36.50
Factory wired and tested

LPS-1 Power Supply for LPA-1

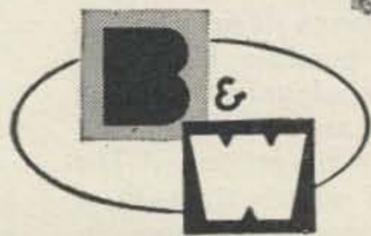

Barker & Williamson, Inc.

Canal and Beaver • Bristol, Penna.

Foreign Sales—Royal National Corp., 250 West 57th St., New York 19, N.Y.

OTHER B&W EQUIPMENT: Transmitters AM-CW-SSB • Transistorized Power Converters and Inverters • Dip Meters • Matchmasters • Frequency Multipliers • Low Pass Filters • T-R Switches • R. F. Filament Chokes • Transmitting R. F. Plate Chokes • Band-Switching Pi-Network Inductors • Cyclometers • Antenna Coaxial Connectors Baluns • Variable Capacitors • Toroidal Transformers • Coaxial Switches • Fixed and Rotary edgewound Inductors • Plug-in Coils with fixed and variable links • Straight type air wound coils in a variety of dimensions.

the keying unit shown in Fig. 1 could be inserted at any stage operating at the output frequency, preferably just before the final.

This unit is a balanced modulator such as is used in sideband, but it's fed from a dc source. The tubes conduct only if their screens are connected to positive voltage. Relay K1 assures that only one conducts at a time. If V1 is conducting, the output phase will be 180 degrees away from that of the input, while if V2 is conducting, the phase will be unchanged. Thus keying the relay changes phase of the output signal by 180 degrees.

At this point, we have a signal going out which contains all our information in zero bandwidth, but we have no way of detecting it. That's what we need to examine next.

Figure 2 shows a typical phase detector which compares the incoming signal to a reference and gives one polarity output if incoming and reference signals are in phase and the opposite polarity if they are 180 degrees opposed. With such a detector at the end of the receiver's *if* strip, we could use the polarity changes to operate either a sensitive

polarized relay or a dc amplifier circuit to key the printer—if we had a stable reference source.

The best reference source is the incoming signal itself. If we double its frequency in a multiplier, the phase shifts will disappear. We can then use this as a reference voltage to phase-lock a frequency divider, ending up with a phase-stable reference voltage which is either in phase with the original reference or 180 degrees out. If it's 180 degrees out, the result will be the same as being tuned to the wrong side of zero-beat in a present FSK system, and the cure is also the same—switch to the other side using a reversing switch.

A complete unit fed from the grid of the receiver's final *if* stage is shown in Fig. 3. Power supply for the adapter is not shown, but a separate power supply should be built for it since most receivers can't stand being robbed of so much filament current as the adapter would require.

In addition to the saving in spectrum space achieved by going to zero bandwidth, this system would be much easier to tune than the

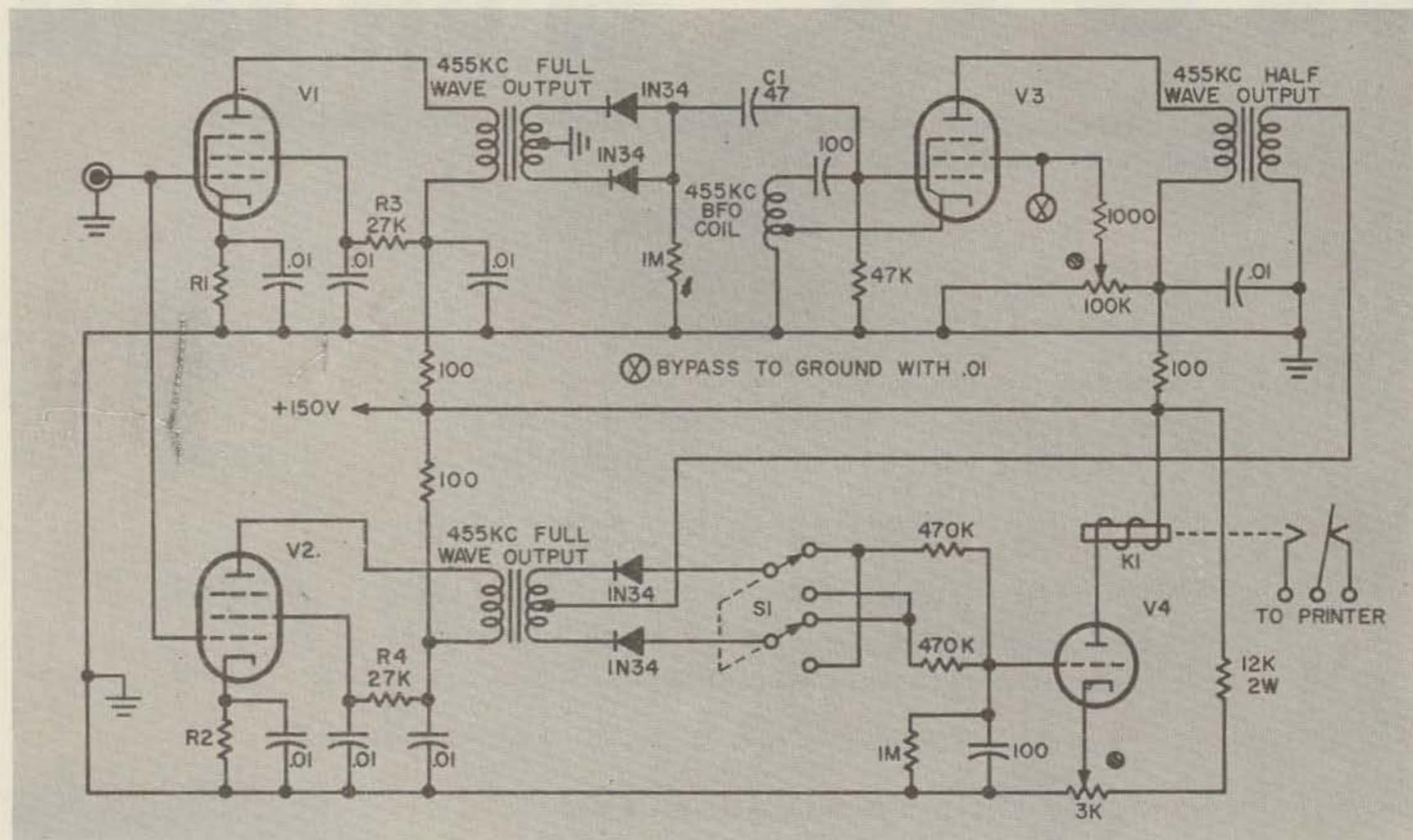


Figure 3. Zero-shift RTTY Receiving Adapter, Schematic Diagram. All transformers are replacement-grade 455-kc *if* transformers. Suitable units are made by Miller and by Stancor, among others. V1 and V2 are isolation amplifiers; the input connection is to be taken from the grid of the receiver's final *if* tube. V1 feeds a full-wave frequency doubler, which removes phase information from the incoming signal and then, through C1, synchronizes reference oscillator V3 in perfect phase with the incoming carrier. If the value of C1, R1, and R3 is correct, when the receiver is tuned to an AM station and the output of V3 temporarily coupled back to the regular detector, the beat note will jump to an

absolute lock (thereby disappearing) as it reaches 2 to 3 kc. V2 feeds the incoming signal directly to the phase detector, where it is compared in phase with the reference derived in V3. Switch S1 corrects for the possible 180° misphased condition which is analogous to being tuned to the wrong side of zero beat in conventional FSK. V4 is a relay-driver stage. The 100K pot in the screen of V3 adjusts strength of the reference voltage with respect to incoming-signal voltage at the phase detector. The 3000-ohm pot in the cathode of V4 adjusts bias on V4 for proper on-time-off-time conditions at the relay while receiving an "RY" series.

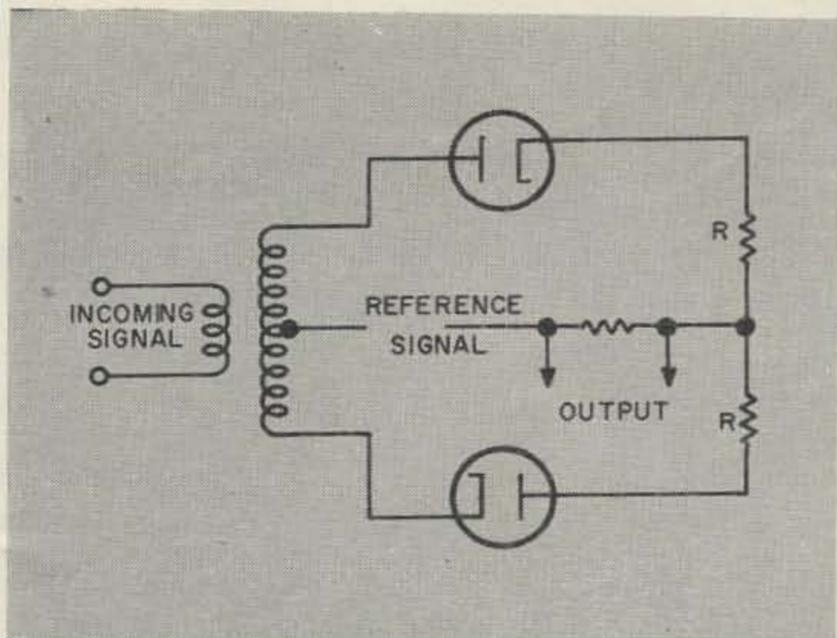


Fig. 2

present FSK technique. In the absence of a strong interference which might capture the phase-reference generator, the only requirement for a solid copy would be that the incoming signal be somewhere in the receiver passband. By using only the polarity of the received and detected signal as the indicator of information, slight phase shifts and beats caused by interference are made insignificant. Computermen report an average increase of 3 db in usable-signal-noise ratio as compared to FSK for this system; this means that the signal can be 3 db lower in the noise level for the same accuracy of copy.

The advantages have been listed, but there are a few disadvantages too. The largest is that this system is incompatible with present FSK RTTY. A station equipped only for zero-shift could not communicate with an FSK station, and vice versa. The situation is somewhat analogous with the wideband FM vs. AM, or AM vs. SSB, dilemma on the phone bands. In addition, as mentioned at the start, this is only a theoretical system in its application to RTTY and has not been tested at all. Hidden bugs might appear in widespread tryouts.

However, if you're an experimenter, looking for the opportunity to pioneer new fields, then maybe here's one for you. What do you think?

Diagram Clarification

Those little buttons near the pots in Fig. 3 are our cryptic way of indicating that they should be the screw-driver adjustable type and need not protrude from the panel for use. The top 1N34 in the V4 grid circuit is shown connected backward. This probably won't affect you since the likelihood of your building this circuit is rather remote. . . . K5JKX/6

Bibliography


- Weir, J. N., "Digital Data Communication Techniques," Proceedings of the IRE, Special Computer Issue, January 1961, pages 200 and 201.
Green, W. and B. Kretzman, The RTTY Handbook, Privately Published.

TAPETONE

Designers and Manufacturers of
**Ultra quality low noise VHF-
UHF receiving equipment for
commercial and military
applications**

Custom Front Ends
Parametric Devices
Ham Converters, custom tuned for:
50 mc 144 mc 220 mc 440 mc 1296 mc

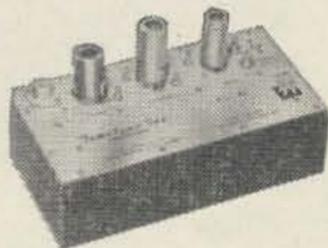These converters are for the DX-minded ham who wants the very best that can be turned out. They are available on an individually tested and tuned basis directly from our laboratory. Write for specifications and prices. Club secretaries should write for details of our new club sales program.



LOOK!




Sam Harris, Chief Op at WIBU

**SAM HARRIS W1FZJ is
working with us now!
Wait'll you see what Sam
has up his sleeve for you!**

TAPETONE

10 Ardlock Place • Webster, Mass.

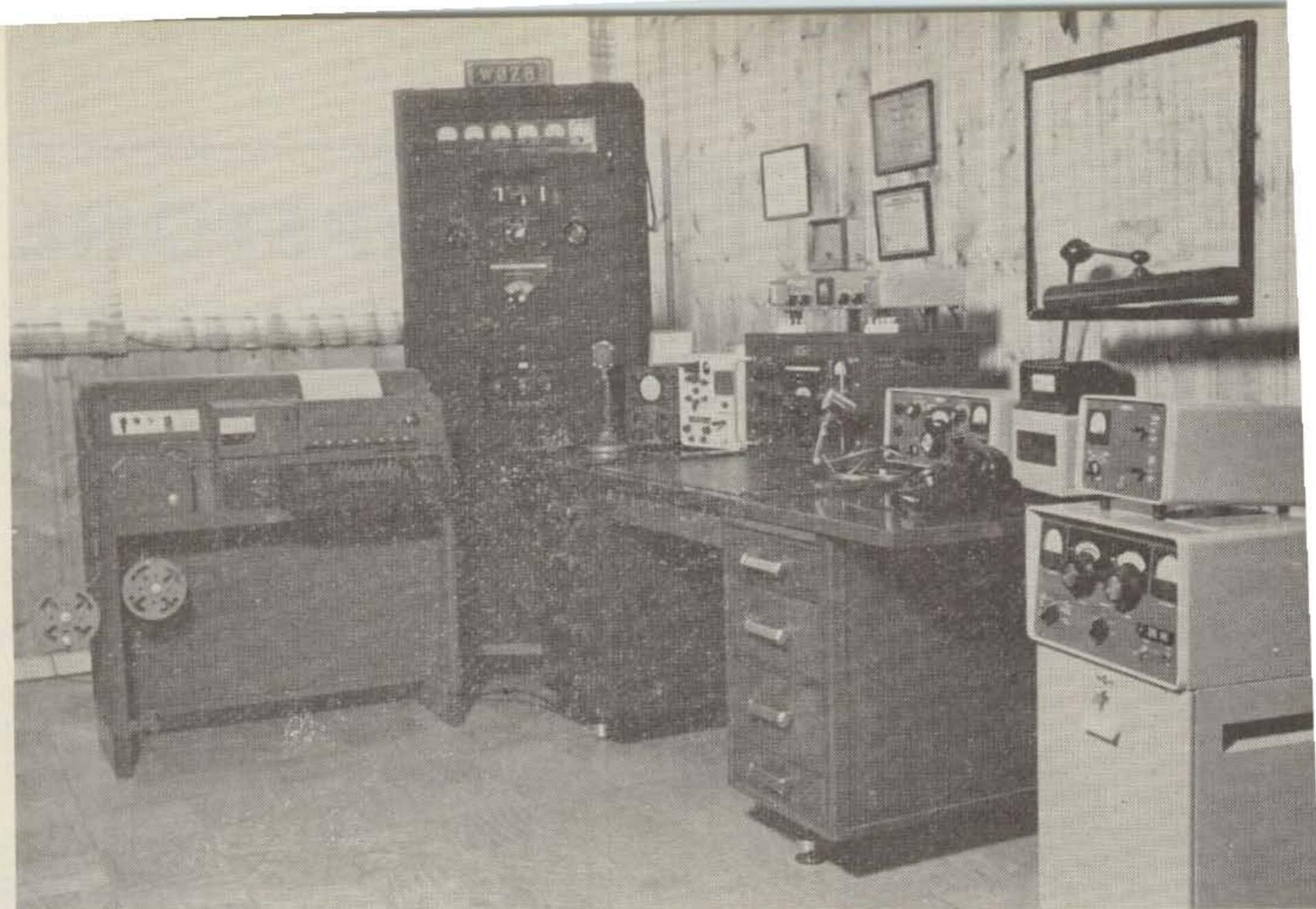

Typical 73 Subscriber Ham Shacks

Two of our RTTY ops sent in photos of their shacks, which you can see are quite normal. Les Benson, WØZB of St. Louis has a Model 28 Teletype, a KW-1, and a few minor items of Collins lineage. Ray Nuss W8KDW of Doylestown, Ohio has a couple Model 15's and a Model 14 Teletype, plus the Collins 51J4 and 32V3 into a **HOMEMADE** linear.




free

send for the

ALLIED

VALUE-PACKED 1962 ELECTRONICS CATALOG

444 PAGES • WORLD'S BIGGEST

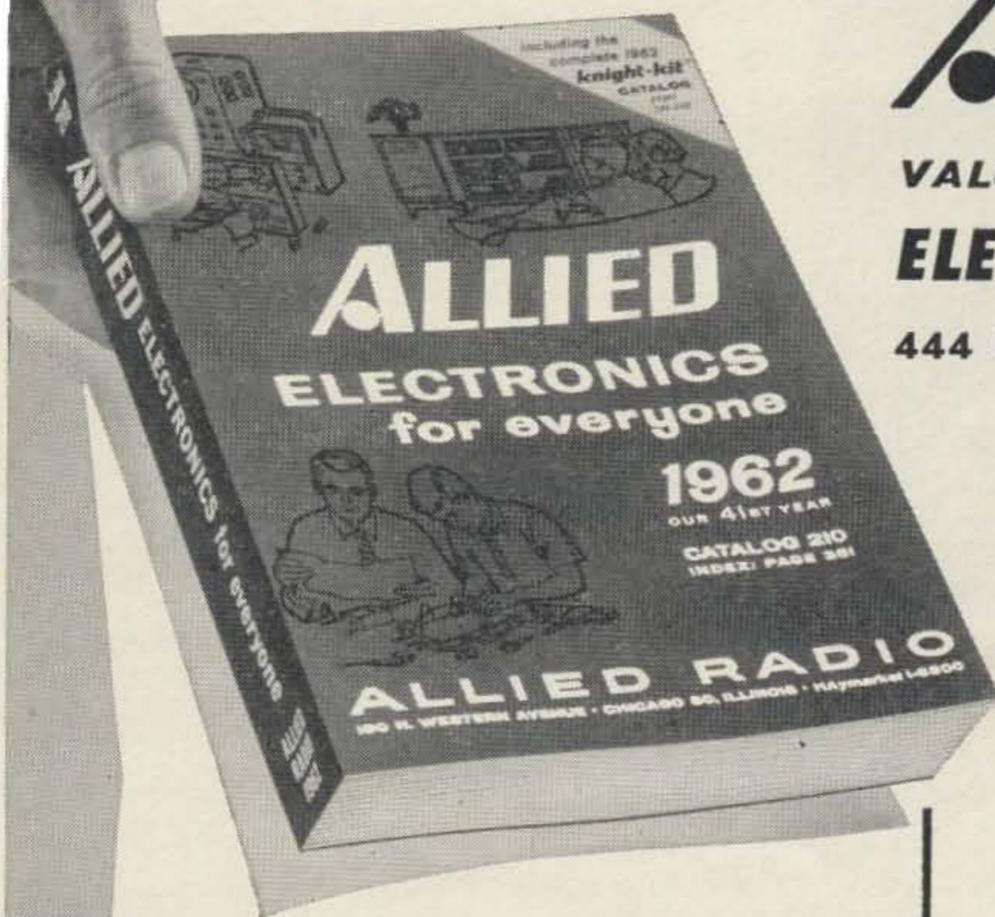

get every
buying advantage


FOR THAT BEST DEAL on all the new equipment you want, write or call Jim Sommerville, W9WHF, c/o Allied, or stop in at our Ham Shack and meet Joe Huffman, W9BHD; Joe Gizzi, W9HLA; Lowell Warshawsky, W9NGV; John Chass, K9LOK...

HAM-TO-HAM HELP—Our staff of more than 30 Hams goes all-out to give you the help you want, whether you write, call or visit us in person. You'll like the friendly attention and interest you get *all-ways* at ALLIED.

NO MONEY DOWN
now you can buy on
the easiest terms ever

one order to Allied
fills the whole bill

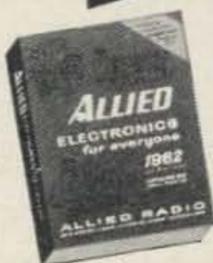Save time, trouble and money—fill all your electronic supply needs from your 1962 Allied Catalog



send for
FREE
CATALOG

Everything IN ELECTRONICS FOR THE AMATEUR

Send today for the 1962 ALLIED Catalog—most widely used by Amateurs for *complete* electronic supply. You'll want it handy always—to fill all your station equipment needs—to supply you with *everything* in electronics at lowest, money-saving prices. Features the largest and latest selection of:

- Ham Receivers
- Ham Transmitters
- Station Supplies
- Electron Tubes
- Semiconductors
- Test Instruments, Meters
- Build-Your-Own Knight-Kits®
- Everything in Stereo Hi-Fi
- Recorders & Accessories
- Everything in Electronic Parts, Tools & Tech Books

For *everything* in electronics, get the 444-page 1962 ALLIED Catalog now!

ALLIED RADIO

serving the Amateur for 41 years

ALLIED RADIO, Dept. 150-J1
100 N. Western Ave., Chicago 80, Ill.


Send me the FREE 1962 ALLIED Catalog

Name _____
PLEASE PRINT

Address _____

City _____ Zone _____ State _____

*A new
antenna design
concept*

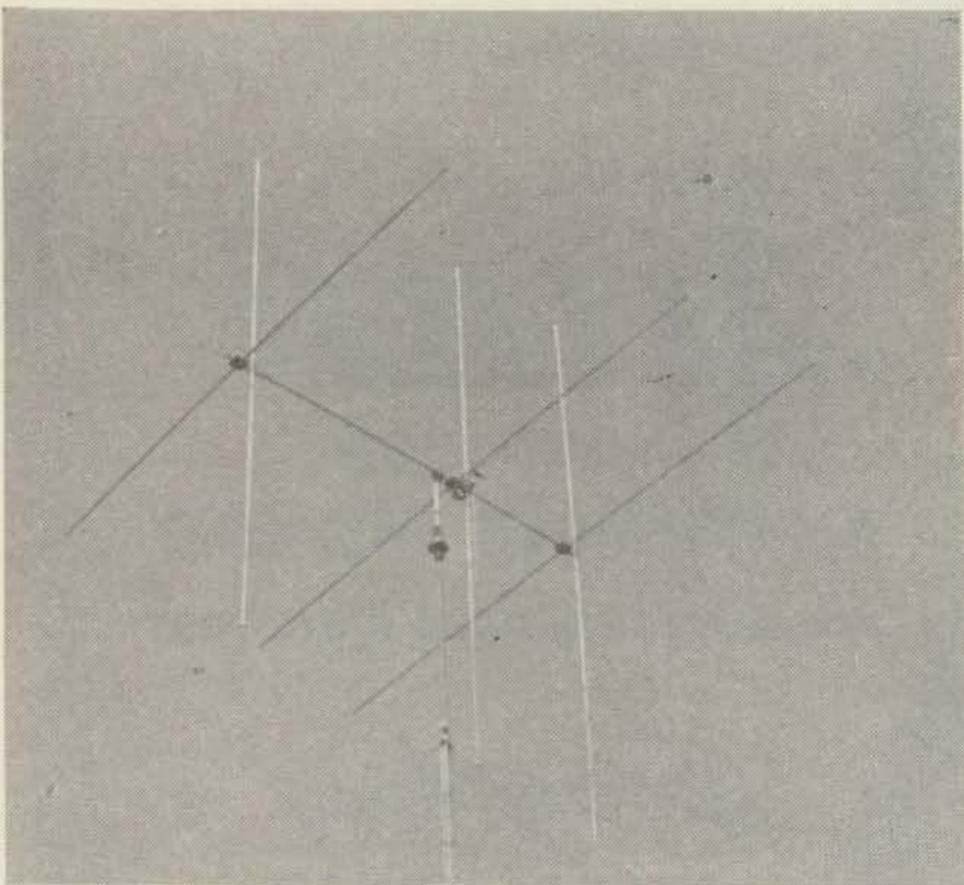

George Messenger K6CT
603 S. Lark Ellen
West Covina, California

Polarization Diversity

QSB appears to be one of the worst factors in reducing the readability of signals. W6ZGC and I checked the 10 meter band for a 12-month period during 1958 and 1959. Using dual installations, one having a horizontally polarized antenna and the other vertical, and found that *QSB due to polarization shift caused about 80 percent of the total of QSB present in received signals.* The 20 percent balance consisted of QSB caused by the signal swinging in azimuth, over or under jumping, and polar flutter. An antenna system capable of receiving in both planes simultaneously was obviously worth working on.

The usual method of getting diversity reception is to use two separate antennas, spaced well apart, and feed them into two receivers. Obviously this arrangement was not for ham radio. We wanted to work up something that was simpler and generally usable without a lot of expense or dither. We wanted to solve the problem the "ham" way, not the commercial way.

I will gloss quickly over all of the mistakes we made along the way and cut short the suspense. Since you are reading an article you will not be surprised to know that we solved the problem rather neatly. The result is a six element Yagi, with three elements vertically polarized and three horizontally polarized. It is fed with 52 ohm coax, permitting me to keep the low-pass filter in the line (and me in the neighborhood). The Brown Turnstile feed system was chosen, being real simple.

The project evolved along normal ham lines.

Lacking a tower for preliminary tests we put it up as best we could and rigged up horizontal and vertical field strength meters. Even though it was so low that passing cars made the SWR meter jump like a radar speed meter we found that signal reports were already unbelievable. This tempered the home climate a bit and I "gave" my wife a tower for her birthday, pointing out that this was a small enough sacrifice for science and besides that was the only money I had.

Once we had it up on her tower the signal reports were even more incredible. Running only 135 watts to a Viking II I polished off the following Q5-S9 contacts consecutively: CX1VD, LU1NH, ZS3L, ZS6AST, ZE7JV, JA3AVD, JA1BYM, LU3ACA, W1NCX, ZL1LY, VKØWH, and ZL3BL. On all contacts I checked the new beam against my quad, operating at the same height above ground, and found that the signal was always much higher on the new beam. The average difference ran from 3 to 5 db above the quad! Stations, one after the other, reported that my signals didn't have the QSB they were hearing on all other signals.

Many an operator has thought his station to be outstanding, only to be crushed during a DX contest. I battled through the 1960 CQ WW DX test and racked up 8190 points on 10 phone. The next highest score was old contester W6NAT with 4026 points. I had more than doubled the score of the runner-up in the sixth district, which you'll have to admit is the toughest there is. The final results aren't in

for the 1961 ARRL DX test, but I managed 8280 points on 10 phone.

In normal operating you notice the difference in that stations almost invariably come back to you when you call. They all report a lack of QSB on the signal. They usually mention that I have the loudest signal from my area and that my signals are the first in and the last out. Many report calling me for an hour or so before their signals were able to come through in the opposite direction.

After much testing we have measured the front-to-back ratio as 46 db and the front-to-side as 66 db. Since this is regardless of incoming polarization it is phenomenal to use.

As more and more stations became aware of what was going on I got more insistently peppered with questions about the beam. As KR6CR said, "Please send the dope . . . all the talk out here is about your antenna. You come through from Stateside when we don't hear anyone else."

Though you can probably duplicate my beam pretty well from a look at the not too clear photo in this article, I'll be along with the details for you in Part II next month. If you can't wait (ahem, here comes the commercial) then you might check the obscure little ad on page 41. . . . K6CT

Letter

Dear Wayne:

Just mailed in my renewal to "73." That ought to shake u up. I was looking for a low powered 2 meter transmitter. I read your article on page 34 of April "73," and bought the Heath Twoer. I had no trouble with the construction or alignment. I made a simple modification and now I have a 4 watt 2 meter base transmitter and a 2 meter portable rig.

Parts required: 1 phono plug; 6 inches of wire. Install the phono plug on the rear apron between the fuse holder and the regeneration control, run the six inch wire from the phono plug to contact number 10 of the rotary switch (Z). This brings the antenna out to the newly installed phono plug. I feed this into my "International 2 Meter Crystal Converter" and into my Hallcrafters SX101. The 6BSS preamp. detector must be removed from the Twoer or the radiation from the oscillating detector will block the receiver.

Martin Rexsen W2FEI

SX-101A

In the S meter circuit of the SX-101A the 6BA6 tube can be replaced by a 5749, which proves to be much better. This will add up to 10 or 15 DB's more on each S meter reading. Nothing has to be done to the receiver since these tubes are interchangeable. Since this tube makes the meter more sensitive, the S meter must be re-adjusted a little. This tube will make for truer signal reports.

Jeff Gilbert WA2NYO



CITIZEN BAND All 22 Frequencies in Stock CLASS "D" CRYSTALS

3rd overtone. .005% tolerance—to meet all FCC requirements. Hermetically sealed HC6/U holders. 1/2" pin spacing—.050 pins. (.093 pins available, add 15¢ per crystal).

\$2.95
EACH

The following Class "D" Citizen Band frequencies in stock (frequencies listed in megacycles): 26.965, 26.975, 26.985, 27.005, 27.015, 27.025, 27.035, 27.055, 27.065, 27.075, 27.085, 27.105, 27.115, 27.125, 27.135, 27.155, 27.165, 27.175, 27.185, 27.205, 27.215, 27.225.

Matched crystal sets for all CB units. . . . \$5.90 per set. Specify equipment make and model numbers.

RADIO CONTROL CRYSTALS IN HC6/U HOLDERS

Specify frequency, 1/2" pin spacing . . . pin diameter .05 (.093 pin diameter, add 15¢) . . . \$2.95 ea.

FUNDAMENTAL FREQ. SEALED CRYSTALS

In HC6/U holders
From 1400 KC to 2000 KC .005% Tolerance . . . \$4.95 ea.
From 2000 KC to 10,000 KC any frequency
.005% Tolerance . . . \$3.50 ea.

SEALED OVERTONE CRYSTALS

Supplied in metal HC6/U holders
Pin spacing .486, diameter .050
15 to 30 MC .005 Tolerance . . . \$3.85 ea.
30 to 45 MC .005 Tolerance . . . \$4.10 ea.
45 to 60 MC .005 Tolerance . . . \$4.50 ea.



QUARTZ CRYSTALS FOR EVERY SERVICE

All crystals made from Grade "A" imported quartz—ground and etched to exact frequencies. Unconditionally guaranteed! Supplied in:

FT-243 holders Pin spacing 1/2" Pin diameter .093
MC-7 holders Pin spacing 3/4" Pin diameter .125

CR1A/AR holders Pin spacing 1/2" Pin diameter .125
FT-171 holders Pin spacing 3/4" Banana pins

MADE TO ORDER CRYSTALS . . . Specify holder wanted

1001 KC to 2600 KC:
.005% tolerance . . . \$1.50 ea.
2601 KC to 9000 KC:
.005% tolerance . . . \$2.50 ea.
9001 KC to 11,000 KC
.005% tolerance . . . \$3.00 ea.

Amateur, Novice, Technician Band Crystals

.01% Tolerance . . . \$1.50 ea.—80 meters (3701-3749 KC), 40 meters (7152-7198 KC), 15 meters (7034-7082 KC), 6 meters (8335-8650 KC) within 1 KC
FT-241 Lattice Crystals in all frequencies from 370 KC to 540 KC (all except 455 KC and 500 KC) . . . 50¢ ea.
Pin spacing 1/2" Pin diameter .093
Matched pairs + 15 cycles \$2.50 per pair
200 KC Crystals, \$2.00 ea.; 455 KC Crystals, \$1.25 ea.; 500 KC Crystals, \$1.50 ea.; 100 KC Frequency Standard Crystals in HC6/U holders \$4.50 ea.; Socket for FT-243 crystal 15¢ ea.; Dual socket for FT-243 crystals, 15¢ ea.; Sockets for MC-7 and FT-171 crystals 25¢ ea.; Ceramic socket for HC6/U crystals 20¢ ea.

Write for new free catalog #961 complete with oscillator circuits

ASK YOUR PARTS DEALER FOR TEXAS CRYSTALS
See big red display . . . If he doesn't stock them, send us his name and order direct from our Florida factory.

NOW! Engineering samples and small quantities for prototypes now made either at Chicago or Ft. Myers Plant. 24 Hour Service!

IN CHICAGO, PHONE GLadstone 3-3555

RUSH YOUR ORDER TO OUR NEW PLANT

Use coupon below for 1st Class shipment.

TEXAS CRYSTALS

Dept. G-91, 1000 CRYSTAL DRIVE, FORT MYERS,
For extra fast service, Phone WE 6-2100

ATTACH THIS COUPON TO YOUR ORDER FOR SHIPMENT
VIA 1ST CLASS MAIL AT NO EXTRA COST

TERMS: All items subject to prior sale and change of price without notice. All crystal orders must be accompanied by check, cash or M.O. with PAYMENT IN FULL.
Dept. G-91.

Crystal Oscillators

OSCILLATORS are important gadgets to us hams. Even aside from their uses in receivers, the ever-present oscillator is a necessity for any transmitter. For CW use, the entire transmitter might be made up of an oscillator and a power supply—and in any other rig, at least one oscillator must be included to generate the carrier frequency.

Since the oscillator is such an important device, it has undergone thorough study by many researchers. As a result, literally hundreds of oscillator circuits have been published. Choosing the best circuit for your own use from this mass of material becomes difficult, and many otherwise worthwhile circuits have become almost lost simply because not enough people have learned about them.

We're going to explore the entire subject of vacuum-tube oscillators, including several circuits which haven't seen much use as well as some of the old standards of the field.

Since there are so many different circuits, though, we're going to divide the field between crystal-controlled oscillators and those oscillators whose frequency is continually adjustable (or, in other words, VFOs) and cover each part in a separate article. This article deals strictly with crystal oscillators.

The crystal of a crystal oscillator is a small plate of Brazilian quartz, ground to precise size and thickness. The physical dimensions of the rock determine its natural resonant frequencies. In the proper circuit, these natural resonance frequencies determine the frequency of operation of an electronic oscillator—and

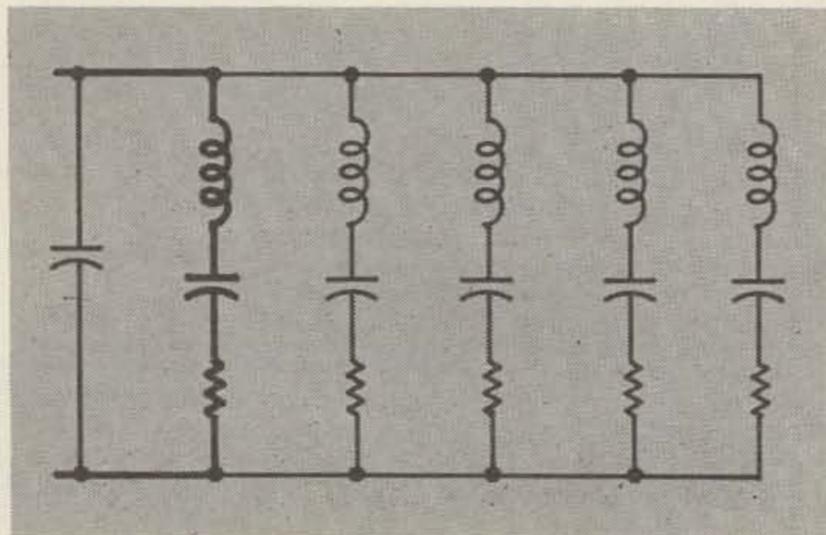


Fig. 1

since the crystal's resonances are determined by physical means rather than electronic elements, the frequency remains much more stable than would otherwise be possible. Frequency stability as great as one part in ten billion (that's 0.00000001 percent) is possible with the proper crystal circuit and construction.

You may have noticed that all through that last paragraph we were talking about the crystal's resonant frequencies, although only one frequency is marked on any commercial crystal. That was no mistake; all quartz crys-

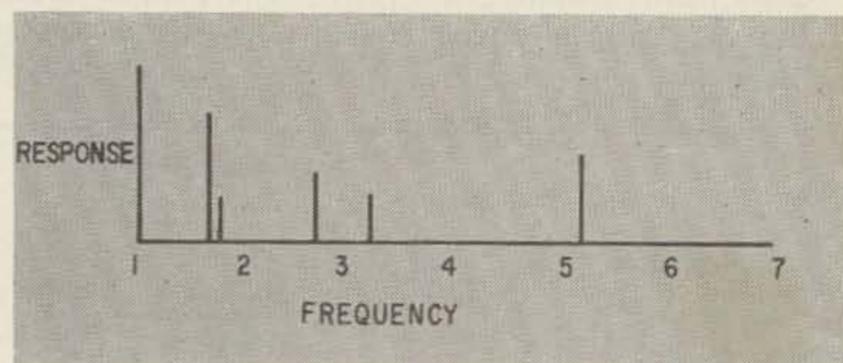


Fig. 2

tals exhibit multiple resonance. The marked frequency is the one at which the rock is intended to operate, but operation at any of the other resonances is usually possible. One of the best examples of multiple-resonance operation is the conventional overtone crystal, which operates at the third harmonic of the basic fundamental frequency through proper circuit design. Frequently, these crystals, may be coaxed into operation at other overtones as well.

One way of grasping the idea of a crystal's operation is to examine its equivalent circuit, shown in Fig. 1. This is what a crystal looks like, electrically, to the circuit. You can see that the several series-resonant circuits also form parallel-resonant circuits at other frequencies. This multiple-resonance quality of a crystal is shown in Fig. 2 as a frequency spectrum for a typical unit.

At this point, let's concentrate on just one of the series circuits shown in Fig. 1—the one shown in heavier lines. This is the primary resonance of the crystal, the one at which it will oscillate or transmit most readily. It's drawn separately in Fig. 3, along with the shunt capacitance of the electrodes which make

contact with the two sides of the rock itself.

You can easily see that at one frequency, C_1 will be almost a short-circuit which leaves only a parallel-resonant tank circuit, while at some other frequency C_h will be almost an open circuit which leaves only a series-resonant arrangement. In practice, these two frequencies are usually within a very few kc of each other, which leads to the crystal impedance curve shown in Fig. 4.

It's important to remember that every crystal has both series-and parallel-resonance at its primary frequency; at its other resonant frequencies this way not be so, since the effective values of inductance and capacitance may be so far different. However, in fundamental-frequency operation some circuits use series resonance and others employ the parallel or antiresonant condition. This makes the same rock operate at two slightly different frequencies, depending on which type of circuit it's used in.

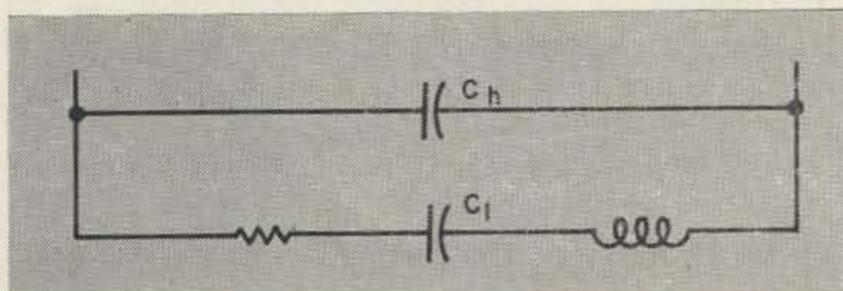


Fig. 3

In addition, external circuit capacitance or inductance will also reflect back into the equivalent circuit of Fig. 3, which causes slight changes of frequency with changes of external elements.

This can be used as an aid to getting precise spot-frequency results, especially at VHF, by connecting a trimmer capacitor across a crystal which is operating in parallel mode or in series with a series-mode crystal; however, it can also be a hindrance if you don't make allowance for it in building any equipment which will use a crystal oscillator.

Enough about the crystal itself; let's look at some practical circuits.

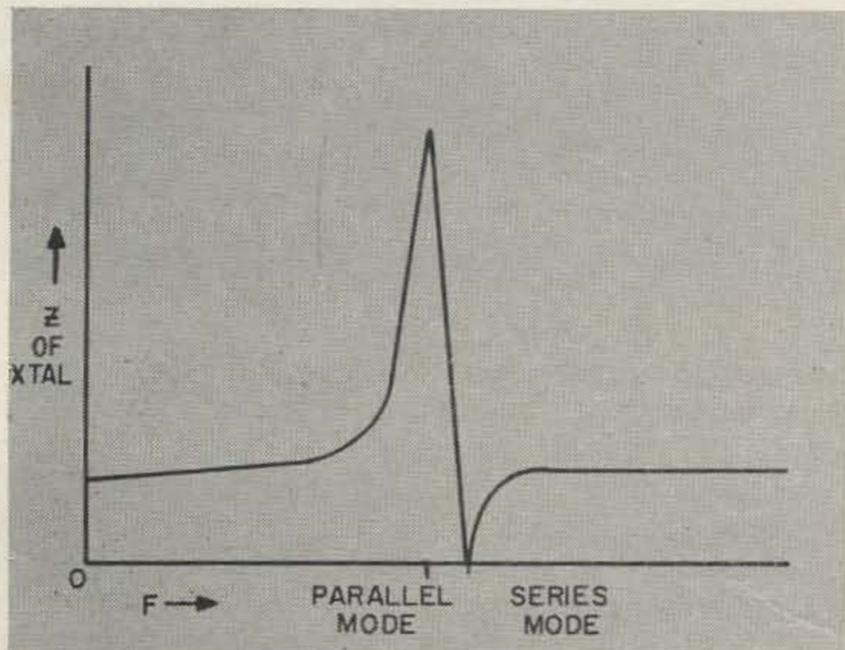


Fig. 4

NEW P & H LA-400-C LINEAR AMPLIFIER NOW 800 WATTS PEP FOR ONLY \$164.95



PANORAMIC SPECTRUM ANALYSIS

Odd order distortion products (1kc, separation) using popular 100 watt SSB exciter and LA-400C.

	3rd order	5th order
EXCITER ONLY	-37 db.	-47 db.
EXCITER AND LA-400C	-37 to -40 db.	-47 to -50 db.

Certified by ITT FEDERAL LABORATORIES

The 80 thru 10 meter band-switching pi network is designed for 800 watts PEP SSB, 400 watts CW, FM or FSK and 230 watts Linear AM (controlled carrier) or 185 watts (constant carrier) with 50-70 ohm output. Popular 100 watt SSB exciters require no swamping or matching networks to drive the low Z untuned input. Grounded grid circuit uses four 1625's or 837's on customers request. Meter reads RF drive, plate current, RF amps output. New modern compact 9" X 15" X 10 1/2" gray cabinet also contains power supply using 816's. TVI suppressed, Parasitic Free.

One-Year Warranty on all Parts and Tubes
SEE THE NEW LA-400C AT YOUR DEALERS

LA-400C Kit Complete with tubes\$164.95
LA-400-C Wired and tested\$219.95

P & H ELECTRONICS INC.
424 Columbia Lafayette, Ind.

Act-WRITE NOW!

Better Yet — WIRE OR CALL TODAY FOR

1. Burghardt's "Deal of the Month" For September.
2. Our September Listing of Reconditioned Equipment Carrying Burghardt's "Seal of Satisfaction."

YOU'LL BE GLAD YOU DID!

* Featuring . . .
Central Electronics, Collins, Drake, Gonset, Hallcrafters, Hammarlund, Hy-Gain, Johnson, Mosley, National.

* Your Direct Line to Every Manufacturer.

Burghardt
RADIO SUPPLY

Phone TU 6-5749
Box 746B
Watertown, So. Dakota

CRYSTALS BY QUAKER

Third overtone crystals in HC-6/U type holders. .005% Tol. Crystals sell \$1.00 postpaid U.S.A. Frequency listed in megacycles. Give 2nd choice.

10.5	10.666	11.618	12.0	12.027
12.127	15.777	17.055	17.255	17.855
20.006	20.533	21.006	22.155	26.12
26.162	26.666	27.725	31.111	31.666
32.222	33.0	33.333	34.0	34.444
35.0	35.555	36.0	37.0	37.407
38.0	38.14	38.888	39.0	40.0
40.111	42.333	42.592	42.7	42.962
45.0	49.012	49.762	50.1	50.663
50.570	51.052	51.262	51.1	51.364
53.737	54.850	57.275	82.833	83.333

THOUSANDS OF OTHER CRYSTALS IN STOCK from 1900 thru 8716 Kcs. 4¢ stamp brings you 12 page catalog. All crystals fully guaranteed.

SPECIAL—HF-15-X Variables 60¢. HF-35 Variables 40¢. JOHNSON miniatures 1.8 to 8.7 mmf 40¢. 80 Watt Dummy load for 80-75 meters \$1.50 postpaid.

QUAKER ELECTRONICS

MT. TOP, PENNA.

R-F WATTMETER

Model PCA-1

\$14.95

FEATURES

- Tuning Citizens Band Xmtrs
- Tuning Low Power Ham Rigs
- Tuning Mobile Xmtrs Police-Fire-Taxi-Bus-Ham
- Tuning Antennas
- Checking Modulation Quality



SPECIFICATIONS

- Reads Power to 10 Watts
- Field Strength Meter
- Modulation Monitor
- Built-in 10 Watt 52 Ohm Load

Manufacturers reps and distributors interested in a few extra pennies please write.

Order through your local parts distributor or send direct to:

PRECISION COMMUNICATIONS ACCESSORIES

674 Eighth Ave., New York 36, New York

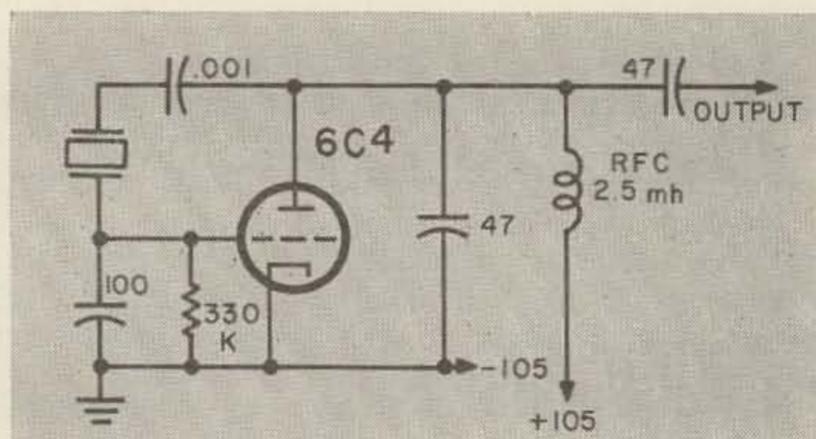


Fig. 5

One of the simplest of all crystal oscillator circuits is the Pierce, shown in Fig. 5. While this circuit, at first glance, looks as if it would use series-resonance to feed back energy from the plate circuit to the grid and cause oscillation, such is not the case. It actually uses the parallel resonance of the crystal to establish a rather complicated network from plate to grid circuits.

Because of its simplicity, many hams appear to have the feeling that the ancient Pierce oscillator can't be very good. Actually, it is as stable as any other crystal oscillator circuit in general use. Its only major disadvantage (shared by many other circuits) is that it's easy to overdrive the crystal and damage it. For best results, any crystal oscillator should be run at minimum power input. Its purpose is strictly to establish the frequency; power buildup should be reserved to later stages. If the Pierce is used in this manner, its performance is equal to any normal crystal oscillator.

Advantages of the circuit are its simplicity and its versatility; this is the only common oscillator circuit which requires no readjustment at all when changing frequency, regardless of the difference in frequencies. It will oscillate at the primary parallel resonance of any crystal put in the socket.

Another well-known fundamental-frequency oscillator is the Miller circuit of Fig. 6. It's

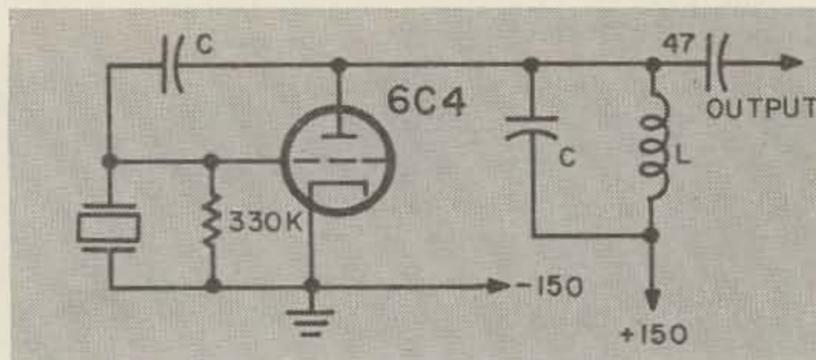


Fig. 6

almost as simple as the Pierce, especially since capacitance C is usually furnished by the tube's internal capacity. Like the Pierce, it provides output only if a crystal is present, but unlike the Pierce it requires a fairly critical adjustment of the plate inductance whenever frequency is changed.

If you don't mind an additional knob to twist at tuneup time, this is no disadvantage, but

it does introduce some slight shift of frequency from that stamped on the crystal holder. If you're not multiplying you'll never notice it, but if the Miller circuit is used at the fundamental for multiplication to VHF, you can almost use the plate tuning adjustment to make the oscillator's frequency variable over an effective 100-kc range!

Crystal dissipation in the Miller circuit is considerably lower than in the Pierce, since the rock gets only the grid voltage across it (in the Pierce, full output voltage was impressed across the crystal terminals). In practice, this means that a Miller circuit can be used to develop enough power to drive the next stage without harming the crystal—an important point when building portable or mobile equipment. However, frequency stability is not as good as that of the Pierce circuit, because any changes in tube characteristics during use are reflected back to the crystal.

Both the Miller and the Pierce circuits make use of parallel resonance; let's look at some of the series-resonance circuits. Before we do, though, let's investigate this business of overtone oscillators a bit.

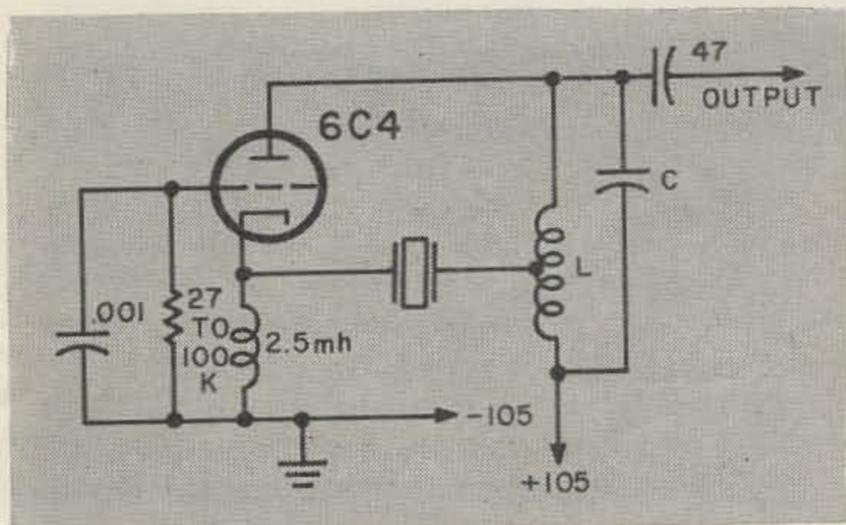


Fig. 7

Earlier, we pointed out that every crystal has a number of resonances. Some of these resonances are located near the third, fifth, seventh, and higher odd-order harmonics of the primary resonance. Notice that we said *near*, not *at*, because they're never located at exact multiples of the primary resonance. The most active of these resonances are the parallel mode at the third harmonic and the series modes at the fifth and seventh overtones.

Since the growth of interest in VHF, there's been considerable interest in "overtone oscillator" circuits. A number of circuits have been developed primarily for this use—but there's nothing about these circuits which would stamp them overtone circuits. Most of them are merely series-mode circuits with the resonant circuits tuned to the appropriate overtone.

"Overtone crystals" are especially processed to yield higher output on a selected higher-order resonance, but the greatest advantage to the use of special overtone crystals is that they are calibrated at the operating overtone frequency. For example, a 10-mc rock may be operated at its fifth overtone, and the out-

KEEP CANDEE HANDEE!

COMMAND GEAR

Famous Q-5'er. 190-550 kc. The receiver you've been looking for at only	\$9.73
BC-454/R-26: 3-6 Mc.	7.73
BC-455/R-27: 6-9.1 Mc.	7.73
MD-7 MODULATOR: Special	3.73
T-18/ARC-5 XMTR. 2.1-3 MC excellent condition...	\$4.73
T-19/ARC-5 XMTR. 3-4 MC excellent condition....	7.73
T-20/ARC-5 XMTR 4-5.3 MC excellent condition...	4.73
T-21/ARC-5 XMTR 5.3-7 MC excellent condition...	4.73

A TRIO OF HEADSET BARGAINS!

HS-23: Hi impedance. Leather covered headband. Brand new. Great buy. Only	\$4.73
HS-33: Low impedance. Leather covered headband. Brand new. A. J. J. Candee Special.....	5.73
Hi Fi Headset: 15,000 cycles! Brand new with chamois cushions. Ia's terrific! Only.....	8.73
CD-307A Headset Extension Cord: Brand new. Approximately 5 ft. length. Only37

APN-1 FM TRANSCEIVER

420-460 Mc. Complete with tubes. Exc. Ea.	\$2.73
Approx. shp. wt. per unit 25 lbs.	TWO for 5.00

YOU GOT IT! WE WANT IT! LET'S DEAL?

We're paying top \$\$\$ for GRC-9; PRC-6, -8, -9, -10; GN-58A; All electronic test equip.

R-4A/ARR-2 RECEIVER

234-258 Mc. 11 tubes. UHF, tunable receiver. See Aug./59 C.Q. Magazine for conversion. Excellent cond.	
TWO for \$5.00. Each	\$2.73

APX-6 TRANSPONDER

A midget warehouse of parts! Blowers, three Veeder-Root counters, I. F. strips, cavity, over 30 tubes, etc. Includes 3E29 tube. Good cond. A STEAL AT ONLY	\$9.73
APX-6 Manual	\$1.37

T-67/ARC-3 TRANSMITTER—

100 to 156 MC.	Used: \$14.73
---------------------	---------------

R-77/ARC-3 RECEIVER—

100 to 156 MC.	Used: \$14.73
---------------------	---------------

ADF AN/ARN-7

Receiver R5/ARN-7	\$29.73
Loop LP21LM	7.73
Inverter MG-149F	9.73
Control Box C-4/ARN-7	5.00
Mount FT-213	3.00

APN-4 LORAN EQUIPMENT

Marine or airborne. Long range navigational gear to determine exact position of ship or plane up to 1200 miles from base. Complete with tubes, crystals. Ex.	Only \$19.73
---	--------------

ART-13 COLLINS

Transmitter, removed from aircraft, 10-channel auto-tune or manual. 2-18.1 Mc. for Ham Rig with 813 final. Output 60-100 W. CW or modulated. Crystal-calibrated for VFO. Excellent Condition.....	Only \$33.37
---	--------------

RT91/ARC-2 TRANSCEIVER

Airborne; AM, CW, MCW, Output 40 W. Input 500MW Freq. Range 2000 to 9050 KC in eight channels; Input 26.5 volt DC, excl. cond. ship. wt. 100 lbs., w/control box.....	\$39.73
---	---------

All items FOB Burbank, Calif., subject to prior sale. In Calif. add 4%. Min. order \$3.73.

J. J. CANDEE CO.

Dept. MS

509 No. Victory Blvd., Burbank, Calif.
Phone: Victoria 9-2411

MODEL
HP-34 NEW FROM
E-Z WAY

**THE TOWER
THAT "MEASURES UP"**

Here is the tower that will be the choice of "Hams in the know". E-Z Way has made a giant step forward in tower construction, incorporating our tried and proven design with high tensile steel (55,000 PSI). The result... a low cost, light weight, super strength tower... designed to please the most discriminating Hams!

- Self-supporting to 34 ft.
- Famous E-Z Way Rotor Head.
- Light weight 10 ft. section weighs only 29 lbs.
- Climbable ladder on three sides.
- Heavy hot dipped galvanized X-type and horizontal bracing

AM. NET.
\$84.95

Other HP models available. See your nearest dealer or write for free literature!

E-Z WAY TOWERS, Inc.

P.O. BOX 5767

TAMPA 5, FLORIDA

J BEAM "SKELETON SLOT"
REVOLUTIONARY ADD-A-LINE
CONSTRUCTION

THE "J" IS NEVER OBSOLETE
ENDLESS — COMBINATIONS

BUY COMPLETE ARRAYS OR
GET BASIC UNIT & ADD UNITS LATER

2/2 (4 Ele.)	144 MC, GAIN 10.0 DB..	\$18.95
4/4 (8 Ele.)	144 MC, GAIN 13.8 DB..	\$23.50
6/6 (12 Ele.)	144 MC, GAIN 15.8 DB..	\$29.95
8/8 (16 Ele.)	144 MC, GAIN 16.8 DB..	\$36.50
300 ohm feed for Low Loss Lines		
WATER TIGHT—HEAVY DUTY BALUN		
300 to 52 ohm		\$8.60
MATCHING HARNESS—TWO 144 MC		
ARRAY		3.80
2—8/8, 144 MC, 19.8 DB GAIN WITH		
HARNESS		81.60

CONSTANT IMPEDANCE OVER "8%"
OF THE CENTER FREQ.

GET THIS ASTOUNDING ANTENNA
— NOW! —

WILLIAM H. ROBERTS

7921 Woodlawn

Chicago 19, Ill.

put will be somewhere near 50 mc. A fifth-overtone 50-mc crystal, on the other hand, will give output right at 50 mc but if operated at its fundamental will only be somewhere near 10 mc.

Now, back to the series-mode circuits. Remember, they operate at the fundamental or the fifth or seventh overtones equally well, depending entirely on circuit constants.

One of the simplest series-mode circuits was developed by Butler and is described in Edson's "Vacuum Tube Oscillators" as "The Grounded-Grid Circuit." It's shown in Fig. 7.

In operation, output of the tube is fed from the plate back to the cathode at the crystal's series-resonant frequencies. Just which frequency is effective is determined by the tuning of the LC circuit.

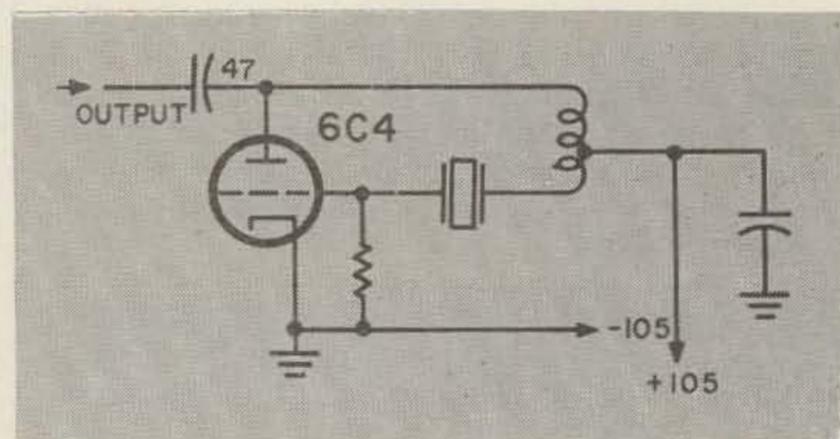


Fig. 8

This circuit will work well with most any crystal, since the input impedance of the tube's cathode is low. This means any current which gets through the crystal will go into the cathode circuit rather than to ground. If tube gain is great enough, the crystal can be extremely sluggish yet still provide good input.

A similar circuit was described several years ago by W8CBM, who called it a "grounded cathode Hartley." His version is shown in Fig. 8. The major difference is that the tube is fed at the grid rather than at the cathode, and consequently fewer parts are required.

Either of these circuits will oscillate on its own if the tap is too high on the coil; to determine if the circuit is under control of the crystal, touch the crystal terminal with a screwdriver while listening to the output signal on a receiver. If the crystal is controlling the signal, frequency shift will be extremely small—possibly even so little that you can't tell it. If the oscillator is taking off on its

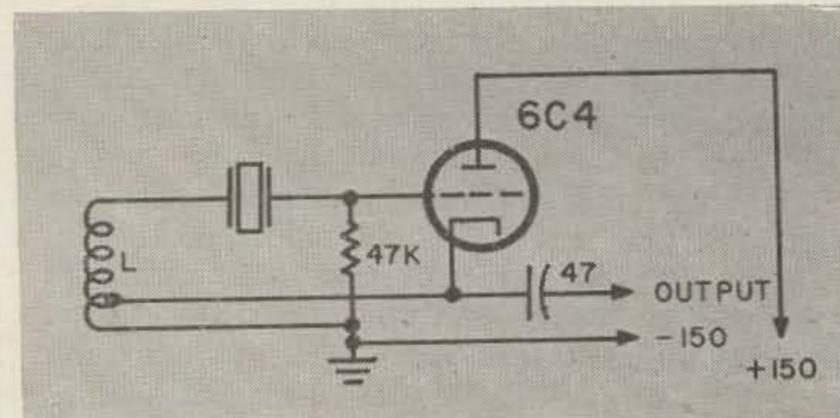


Fig. 9

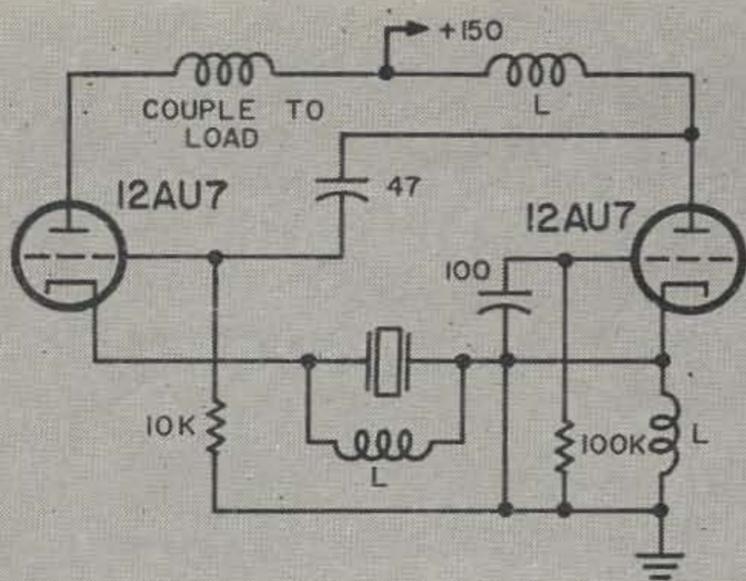


Fig. 10

own, the signal will jump out of the receiver passband with this test.

Still a third version of this circuit has been developed in the 73 labs in connection with a low-plate-voltage converter which refused to operate properly with conventional crystal oscillator circuits. It's shown in Fig. 9. The difference here is simply in the cathode return circuit; frequency is still determined by the crystal's series resonance.

If you're familiar with the Hartley VFO, you'll recognize the preceding three circuits as the Hartley, with ground returns for rf made at the grid, cathode, and plate respectively. Each has its own advantages and disadvantages for specific applications, but in general there's little to choose from between the three. For instance, only the circuit of Fig. 9 is suitable for mixer use, since it's the only one having the plate at rf ground. On the other hand, the circuit in Fig. 8 is least susceptible to hum modulation from the tube's heater, since the cathode is grounded for both rf and dc.

Another series-mode circuit widely used for
(Turn page)

you haven't heard?

EVANS OFFERS

COMPLETE SERVICE

- To HAMS - - - By HAMS (12 licensed employees)
- EQUIPMENT and COMPONENTS (Ham - Electronic - Electrical)
- TRADE-INS (on new or used units)
- TIME PAYMENTS (flexible, financed ourselves)
- ENGINEERING DEPARTMENT (backing all equipment sales)
- RECONDITIONED EQUIPMENT (Largest inventory in the Northeast)
- EXPERIENCE - - - 26 years as:

"YOUR FRIENDLY SUPPLIER"


Evans RADIO

CA 5-3358 • ROUTE 3A • BOW JCT.
BOX 312 • CONCORD, N. H.

TELETYPEWRITER EQUIPMENT

COLLINS 51J2, 51J3, R-390A/URR Receivers (.50-30.5 MC)
TELETYPE Printers #14, #15, #19, #20, #26, #28.
KLEINSCHMIDT Printers #TT-4A, TT-76, TT-98, TT-99
TT-100, GGC-3.
TELEWRITER Frequency Shift Converter.
For general information & equipment list write: Tom WEA FN

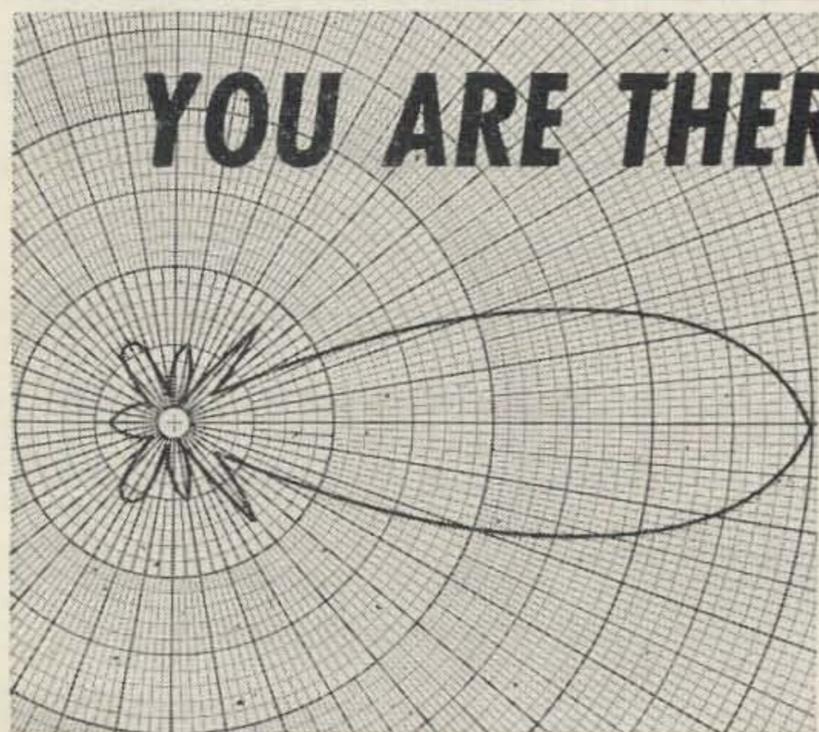ALLTRONICS-HOWARD CO.
Box 19, Boston 1, Mass. Richmond 2-0048



YOU ARE THERE!

For TOP-MAN-ON-THE-FREQUENCY results...
Install a Telrex antenna...dollar for dollar better in every way! Antenna systems from \$6.95 to \$12,000.00

with telrex
— "the-performance-line" —
with a "MATERIAL" difference!


NOW! Precision tuned and matched "Balun" fed (supplied) 8 element 2 Meter Yagi...Model 2M814

\$16⁵⁰

Send For PL77— Tech info on 107 Antennas

ANTENNAS SINCE 1921 **telrex** LABORATORIES
Communication and TV Antennas
ASBURY PARK 40, NEW JERSEY, U.S.A.

VHF Colinear Arrays

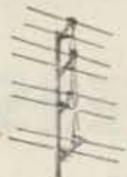

FEATURES

- LIGHT WEIGHT
- MECHANICALLY BALANCED
- HIGH FORWARD GAIN
- HIGH FRONT TO BACK RATIO
- LARGE CAPTURE AREA

32 AND 64
ELEMENT
STACKING
KITS
AVAILABLE

430 MC. 16 Element	\$ 9.85
220 MC. 16 Element	\$12.95
144 MC. 16 Element	\$16.00
See your distributor or write for FREE CATALOG	

CUSHCRAFT

621 HAYWARD ST.
MANCHESTER N. H.

ANYONE FOR HAM TV?

Ham TV is no longer a complicated or expensive hobby. It is quite simple to put a signal on the air when you know what you are doing. This book tells you how. Used TV receivers are available very reasonable these days . . . find out how to convert these old sets for Ham TV. This book is light on theory, presenting just enough so you'll have a good idea of what you are doing. Ham TV is inexpensive and just about the most fun you can have in ham radio. Get this book and get on the air.

Here are some of the contents of this book: Introduction to Ham TV; Image converters; video amplifiers; the TV receiver; the station; flying spot scanner; the camera scanning unit, pickup unit, mixer unit; monitor receiver; slides for the camera; video transmitter; video modulator; transmitter test equipment; transmitter adjustments; audio; antennas; converters; station operation suggestions.

This is the first Ham TV Manual ever published. Order one now!

\$3.00 per copy.

Name..... Call.....

Address

City..... Zone..... State.....

Order for..... copies of the Ham TV Manual
@ \$3.00 each.

ORDER FROM "73" MAGAZINE

1379 East 15th Street, Brooklyn 30, New York

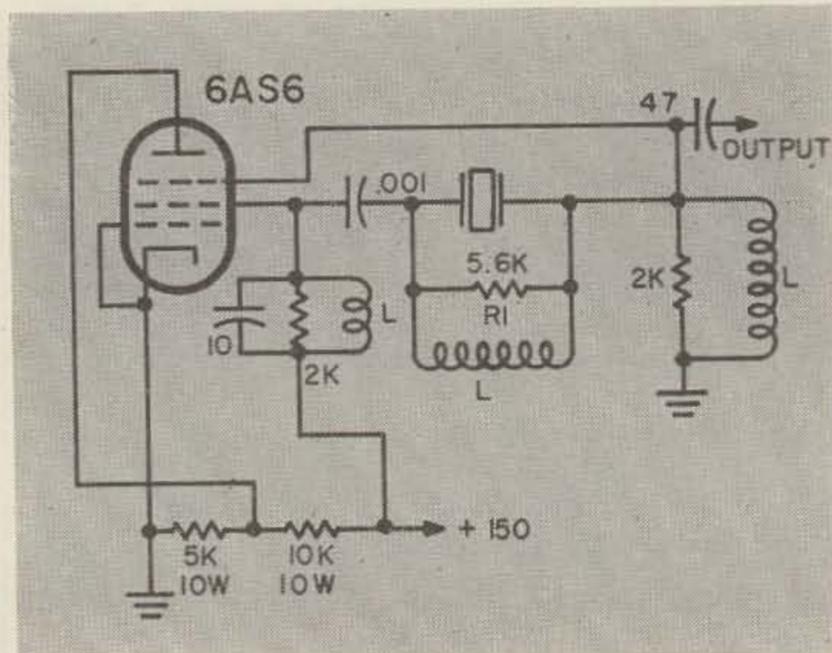


Fig. 11

overtone applications is that shown in Fig. 10. It's known as the cathode-coupled oscillator.

This circuit, though it uses two tubes instead of one, offers almost complete isolation between the crystal itself and the load circuit. In addition, it is capable of considerably more power output than other series-mode circuits.

However, the circuit does not perform well with low-resistance crystals, and in most situations a single-tube oscillator followed by a buffer amplifier will outperform the cathode-coupled circuit in both the power-output and frequency stability departments, according to Edson.

A series-mode circuit especially suited for use with high-impedance (or sluggish) crystals is shown in Fig. 11. Originally described in a 1938 German publication by K. Heegner, it is also shown in Edson's book (which is the virtually complete work on all types of oscillators).

Edson calls the circuit the Transitron, because it operates in a manner similar to the Transitron VFO. If you remove the crystal from the circuit and replace it with a capacitor of value equal to the crystal's shunt capacity, you'll have a Transitron. However, because the resistances are chosen for crystal-only operation, the circuit won't oscillate.

When the crystal is replaced, the circuit is unchanged except at the crystal's series-mode resonant frequencies. At one of the frequencies (which one is determined by tuning of the LC circuits, which are not critical) R1 will be shunted by the crystal's internal resistance, which is much lower. This upsets the non-oscillation balance originally established without the crystal, and the circuit takes off at the crystal frequency.

The Transitron is good up to 160 mc, allowing direct crystal control on 144 mc. No other widely known crystal circuit is capable of operation at such high overtones.

However, a relatively unknown circuit called the capacitance-bridge oscillator can go as high as 219 mc, using the 73rd (no pun intended!) overtone of a 3 mc crystal.

You have to pay a price for this extra-high

operating frequency; the version of the capacitance-bridge oscillator which gets to this astronomical (for crystals) frequency requires not one but three tubes for operation. However, it should be a natural for 220-mc converter use to avoid birdies. The circuit is shown in Fig. 12.

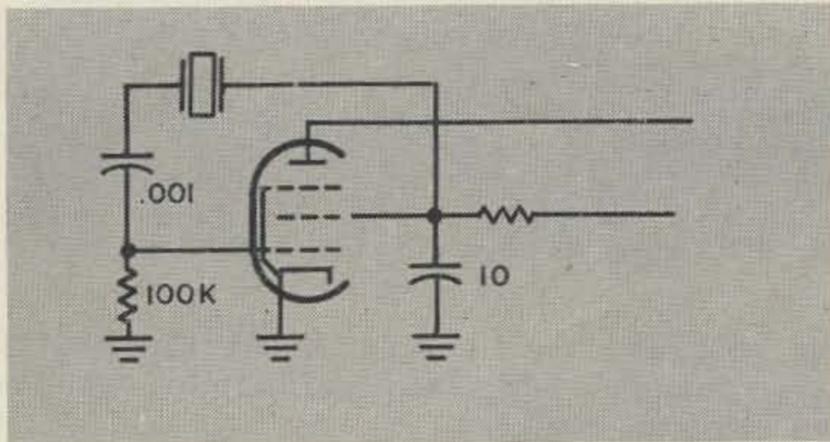


Fig. 12

Here's how it works: The bridge containing the crystal is initially balanced by adjusting C3, with C2 and C1 tuned well away from the desired operating frequency. This eliminates all feedback through the crystal shunt capacity. Then, C1 and C2 are tuned to the approximate frequency desired. The two-stage amplifier circuit then has high gain at this frequency, and since phase shift around the complete loop is 360 degrees the circuit will oscillate if any energy is fed back.

However, the only route through which feedback energy can travel is through the crystal, and this route is open only at a series-resonant frequency. As a result, the circuit oscillates at the nearest series resonance of the crystal. With a high enough fundamental-frequency crystal, the series resonances will be spaced widely enough that you will have no doubt as to the operating frequency.

This circuit requires complete shielding between stages, and long insulated shafts on all capacitors to eliminate unbalance caused by hand capacity. To achieve operation in the

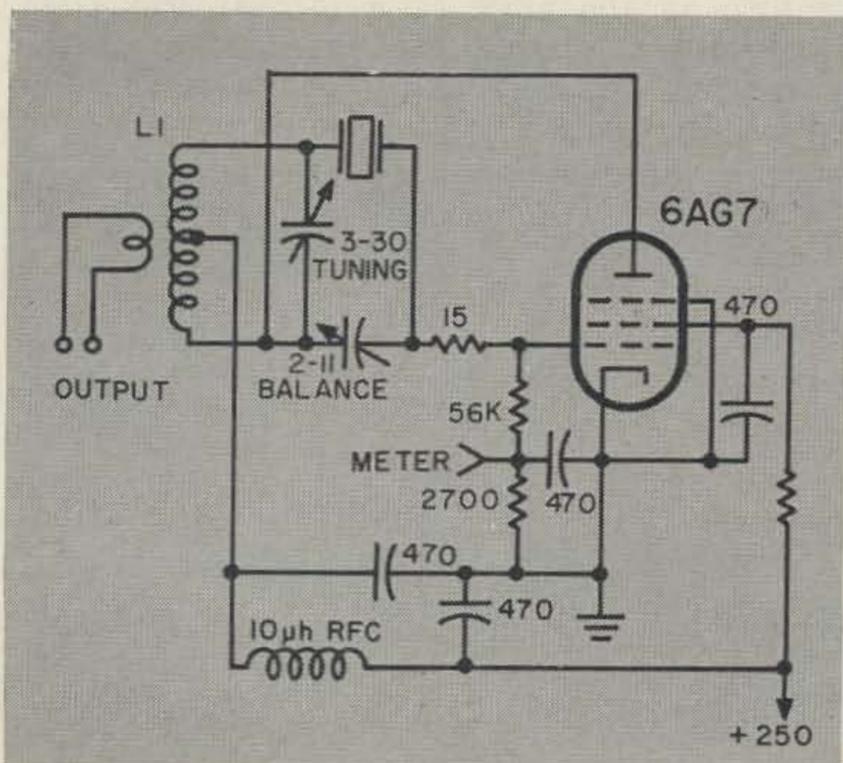


Fig. 13

RADIO HANDBOOK

- the comprehensive reference source
- a problem solver for designers and builders of radio equipment

Gives simplified theory on practically every phase of radio. Tells how to design, build, and operate the latest standard types of radio transmitting and receiving equipment. More "How-To-Build" articles than any book in the field.

All information is original, up-to-date, and complete. 800 pages of data, clearly indexed, between hard covers—the largest RADIO HANDBOOK ever published.



\$8.50 —at your distributor

*Order from your favorite electronic parts distributor.

If he cannot supply, send us his name and your remittance, and we will supply; foreign, add 10%.

EDITORS and ENGINEERS, Ltd.



Summerland 8, California

Dealers: Electronic distributors, order from us. Bookstores, libraries, newsdealers order from Baker & Taylor, Hillside, N. J. Export (exc. Canada), order from H. J. Snyder Co., 440 Park Ave. So., N.Y. 16.

HAM SHACK NOVELTY

Authentic-looking, two-color certificate claiming tongue-in-cheek ownership of an acre on the Moon's surface. Ideal gift or conversation piece for shack, bar, den or office. (See Pg. 119—Jan. 61, CQ.) With gold seal and name and call inscribed only \$1.00 each. Six for \$5.00. Send check or M.O. to—

BOX DXG, 1738 — 201 St., Bayside 60, N. Y.

EXCLUSIVE

Did you know Bob Graham deals only in Amateur Radio Equipment? Did you know he has two stores handling only equipment such as Collins, National, Hallicrafters, Hammarlund, Gonset, Johnson, Central Electronics, Clegg, Globe, etc.? Did you know he services all types of ham gear as well as buys, trades, swaps, rents, and installs equipment? Did you know he has a large selection of reconditioned and guaranteed used gear? You didn't! Well now you do.

GRAHAM RADIO INC.

505 Main St., Reading, Mass. ● Tel. 944-4000
1105 No. Main St., Randolph, Mass. ● Tel. WO 3-5005

200-mc region, the push-pull portion must be accurately balanced both in the bridge and in the amplifier, and leads must be short. The oscillator is also rather more voltage-sensitive than most, so plate supply voltages should be regulated with VR tubes.

At lower frequencies, the capacitance-bridge circuit makes possible construction of an overtone power oscillator which is crystal controlled. Stability is poorer than in other circuits, but for compact portable or mobile equipment operating on 6 or 2 meters the advantages of getting a full watt output from a single-tube oscillator stage more than outweigh lowered frequency stability—particularly when the stability is still greater than most VFO circuits achieve.

The circuit for the high-output oscillator is shown in Fig. 13. Measured output from this one is one watt of rf at 50 mc, operating on the 5th overtone of a 10-mc crystal, and $\frac{1}{2}$ watt output at 80 mc. The circuit output falls off rapidly above 80 mc, primarily because of the large physical size of the 6AG7 tube. Substitution of a 6CL6 or a 6AH6, possibly with some change in circuit constants, would probably raise its upper frequency limit nearer the 2-meter band.

This oscillator drives the crystal too far beyond its rated limit, but researchers work-

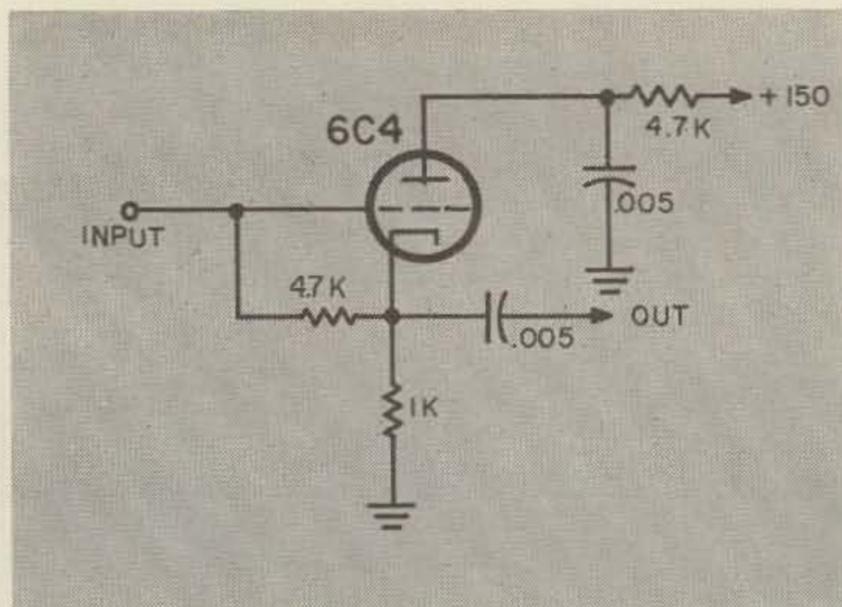


Fig. 14

ing with the circuit report that they have never damaged a crystal in this circuit despite the overload condition.

Both these capacitance-bridge circuits are described more fully in a little-known government publication, "Handbook of Piezoelectric Crystals for Radio Equipment Designers," which is the result of an extensive Air Force-sponsored study of all possible crystal circuits. It's available from the Department of Commerce (see bibliography).

So far, we've been talking primarily about basic oscillators, in which output is taken directly from the oscillator circuit.

Usually, this isn't a good way to get the output, since it means that any variation in loading will be reflected back directly into the oscillating loop and may change the frequency. One way to isolate the oscillator from the load is to add a cathode-follower buffer amplifier, such as the circuit shown in Fig. 14. It connects directly to the point marked "output" in any of the other diagrams.

However, a simpler way of doing it if your oscillator circuit has its plate grounded for rf is to use an electron-coupled oscillator.

This circuit, which is applicable to any of the diagrams in which the plate is at rf ground, makes use of the screen grid of a pentode as the plate of a virtual triode. In other words, simply use the screen as the plate of the triode which is shown in the diagrams. Suppressor connection is normal, and

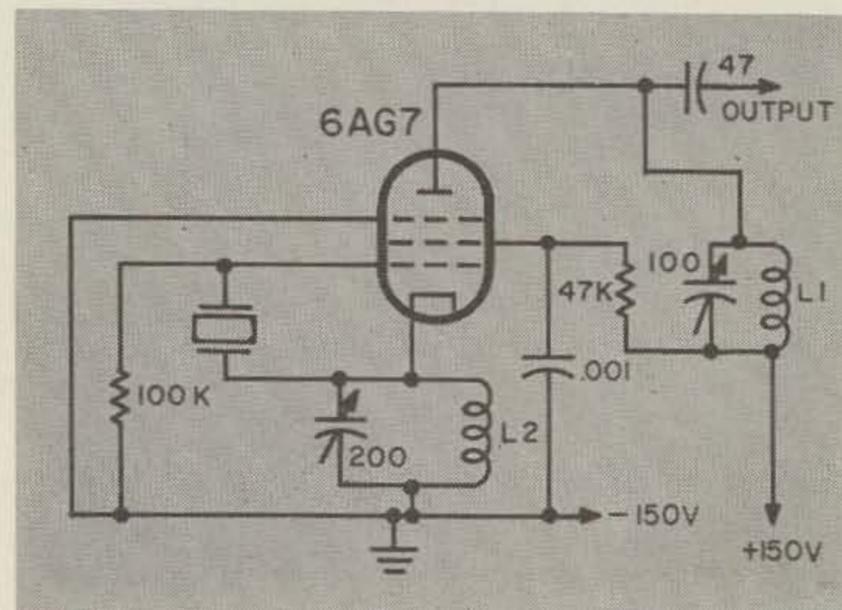


Fig. 15

**from the House of Glass—
a TRUCKLOAD of 73 SPECIALS!
COMPLETE 2-METER STATION
UNDER \$25!**

ARC-3 2-Meter Transmitter, uses 2 832A's in final. Automatic tuning assembly, aligns itself automatically—both transmitter and ARC-3 Receiver can be used on 2 Meters with hardly any changes. Complete with tubes. Just unpacked!

Transmitter	\$14.73
Receiver	\$14.73
Both for	\$24.73

SCOPE SCOOP!

5" Scope with 22 tubes such as 6SN7, 6SL7, 6H6, etc. Compact; easily converted for oscilloscope use or panadapter. Complete with all tubes—don't faint! —a smashing 73 Special at only..... \$5.73
(Designate APN-4 SCOPE BASIC)

**POWER SUPPLY, TRANSMITTER +
RECEIVER**

The 12V TCS Dual Supply, fully filtered, which we used to buy for more than twice this 73 Special price! Brand new, mounted on single base, 2 dynamos, 440V @ 200 MA for transmitter, 220V @ 100 MA for rcvr. We drove a fabulous bargain on these, we're passing it on to you. Only..... \$9.75

100 WATTS ON 80, 40 & 20 — 813 FINAL!

The famous Collins ART-13 Transmitter at a 73 Special price designed to extrude the orbital members to the utmost! 2 to 18.1 MC, VFO and high-level AM Modulator built in, all you need is power. EASILY CONVERTED TO 10 METERS, TOO! Good Condition

..... \$29.73

"TWOFR" 73 SPECIALS

1000 KC Crystal, mounted in metal sealed holder, $\frac{1}{2}$ " pin spacing.....\$1.37 each, two for \$2.73

BC 604 TRANSMITTER

Brand new with all tubes and crystal storage box. Covers 20 to 28 MC. Wow-type 73 Special, only \$4.37 Buy one for a buddy, be sociable. Pair..... \$8.73

J. J. GLASS CO.

1624 S. MAIN STREET LOS ANGELES 15, CALIF.

Output is taken from the plate circuit by either inductor or capacitor coupling.

In operation, the electron stream from cathode to the screen grid is carrying the oscillating current, but the screen doesn't intercept the oscillation current. What misses the screen flows on to the plate and from there to the external load.

Since the load circuit and the oscillating circuit are coupled only by the electron beam from plate to cathode, the circuit is called electron-coupled.

In addition to the oscillators already discussed, several types of circuits are possible only with the electron-coupled arrangement. Such a circuit is the "Tri-Tet" or electron-coupled Miller circuit, shown in Fig. 15. This

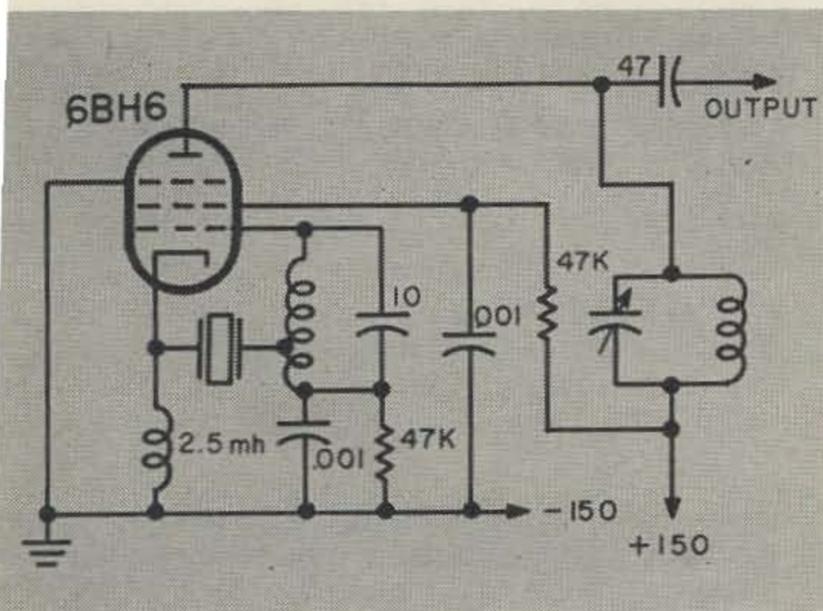


Fig. 16

circuit is capable of delivering a large power output with good frequency stability; its major drawbacks are that the plate circuit must never be tuned to the fundamental frequency of the crystal (too much feedback might damage the crystal) and that there are two controls instead of one to adjust when changing crystals.

Another electron-coupled circuit, described by Edson, is the series-mode grounded-plate oscillator shown in Fig. 16. Good operation is claimed, with "relatively large" power output at either fundamental or harmonic frequencies.

An excellent electron-coupled circuit which operates equally well at fundamental or harmonic frequencies is shown in Fig. 17. Originally described several years ago in a P-R Crystal advertisement, where it was dubbed the "grid-plate" oscillator, the circuit is also known as the Colpitts crystal oscillator.

The crystal is used in its parallel mode, at primary resonance. Feedback is established by capacitors C1 and C2. While either of them may be made adjustable, values shown in the diagram have proven satisfactory in practice. Almost any tube may be used; good results have been obtained with the 5763, the 6CL6, the 6AG7, and (in the non-electron-coupled version) the 12AU7, despite warnings that only the 6CL6 and 6AG7 were suitable for the

(Turn to page 61)

NOW!

GAIN ANTENNAS

**BUSINESS MEN'S
FREQUENCY
or TWO METERS**

(144-170 Mc)

**FIXED STATION
and MOBILE**

ALSO UHF & VHF MODELS UP TO 10.5 DB
Engineers in the Communication Field have tried and proven GAM VHF antennas to give users the ultimate in performance. GAM antennas will give you the "marginal" signal, in most cases eliminate the "dead" spots and cut down on "picket fence" effect. These antennas are end fed through an efficient hermetically sealed matching transformer that is part of the antenna. All models are light in weight and of heavy duty construction.

MODEL TG-3-S

**FIXED STATION;
2 STACKED
9 db gain for \$45.00
Net**

- Gain of 9 db over coaxial antenna
- Heavy duty construction
- Two half wave elements
- Can be cut to frequency
- Mounts on standard 1 1/4" pipe
- 52 Ohm Impedance
- SWR less than 1.5-1

MODEL TG-2

**MOBILE ANTENNA
6 db gain for \$14.10
Net**

- Half wave resonant antenna
- 6 db gain over coaxial antenna
- 52 Ohm Impedance
- SWR less than 1.5-1
- Functions without additional elements
- Reduces flutter effect and extends coverage

CONTACT YOUR DISTRIBUTOR OR GAM DIRECT

GAM Electronics Inc.

138 LINCOLN ST. MANCHESTER, N. H.

Radio Bookshop

Look over this list of books you should have and pick out one or two that you've been wanting. The way to have a good reference library is to build it up a little at a time. We pick over all the latest books carefully and list only those which are of real interest to amateurs. They're on hand ready to ship, postage paid.

2—ELECTRICAL ENGINEERING HANDBOOK—McIlwain. Formulas, tables, circuits. A real handbook. 1618 pages. **\$10.00**

6—VACUUM - TUBE CIRCUITS AND TRANSISTORS—Arguimbau. Designed for both beginners and engineers. Math kept to a minimum. Simple explanations of complex ideas. You'll know a lot more about radio after you read this book. 646 pages. **\$10.25**

8—RADIO-TELEVISION & BASIC ELECTRONICS—Oldfield. Logical presentation and descriptive illustration make this an ideal book for the beginner. 342 pages. **\$4.95**

9—LICENSE Q & A MANUAL—All the dope for commercial FCC licenses, 720 pages, become a professional for **\$6.00**

13—REFERENCE DATA FOR RADIO ENGINEERS. Tables, formulas, graphs. You will find this reference book on the desk of almost every electronic engineer in the country. Published by International Telephone and Telegraph. **\$6.00**

SPECIAL! NOW \$2.50

16—HAM REGISTER—Lewis (W3VKD). Thumbnail sketches of 10,000 of the most active and well known hams on the air today. This is the Who's Who of ham radio. Fascinating reading.

21—VHF HANDBOOK—Johnson (W6QKI). Types of VHF propagation, VHF circuitry, component limitations, antenna design and construction, test equipment. Very thorough book and one that should be in every VHF shack. **\$2.95**

22—BEAM ANTENNA HANDBOOK—Orr (W6SAI). Basics, theory and construction of beams, transmission lines, matching devices, and test equipment. Almost all ham stations need a beam of some sort . . . here is the only source of basic info to help you decide what beam to build or buy, how to install it, how to tune it. **\$2.70**

23—NOVICE & TECHNICIAN HANDBOOK—Stoner (W6TNS). Sugar coated theory: receivers, transmitters, power supplies, antennas; simple construction of a complete station, converting surplus equipment. How to get a ham license and build a station. **\$2.85**

24—BETTER SHORT WAVE RECEPTION—Orr (W6SAI). How to buy a receiver, how to tune it, align it; building accessories; better antennas; QSL's, maps, aurora zones, CW reception, SSB reception, etc. Handbook for short wave listeners and radio amateurs. **\$2.85**

28—TELEVISION INTERFERENCE—Rand (W1DBM). This is the authoritative book on the subject of getting TVI out of your rigs and the neighbors sets. **\$1.75**

32—RCA RADIOTRON DESIGNERS HANDBOOK—1500 pages of design notes on every possible type of circuit. Fabulous. Every design engineer needs this one. **\$7.50**

33—WAVE PROPAGATION & ANTENNAS—Welch. Highly recommended by the propagation experts as the best Book on the subject. **\$5.75**

37—101 WAYS TO USE YOUR HAM TEST EQUIPMENT—Middleton. Grid-dip meters, antenna impedance meters, oscilloscopes, bridges, simple noise generators, and reflected power meters are covered. Tells how to chase trouble out of ham gear. 168 pages. **\$2.50**

40—RADIO HANDBOOK, 15th EDITION—Orr (W6SAI) This is far and away the best amateur radio handbook ever printed. Over 800 pages. **\$8.50**

47—PRACTICAL ELECTRONICS—Hertzberg (W2DJJ). Almost solid with pictures. Touches lightly on many aspects of electronics: ham radio, TV, transistor radios, hi-fi, microwaves, trouble-shooting, Novice station, antennas, test equipment, etc. **\$2.50**

50—MICROMINIATURIZATION—This is the standard text on the subject. Don't see how a company library can be without this one. Everything is going to have to be built smaller, you know. **\$11.00**

52—HOW TO READ SCHEMATIC DIAGRAMS—Marks. Components & diagrams; electrical, electronic, ac, dc, audio, rf, TV. Starts with individual circuits and carries through complete equipments. **\$3.50**

53—BASIC ELECTRONIC TEST PROCEDURES—Turner. This book covers just about every possible type of electronic test equipment and explains in detail how to use it for every purpose. Testing: audio equipment, receivers, transmitters, transistors, photocells, distortion, tubes, power . . . etc. **\$8.00**

R235—RADIO CONTROL FOR MODEL BUILDERS—Winter. One of the best and newest books available on RC. **\$4.25**

R245—HOW TO USE GRID-DIP OSCILLATORS—Turner (K6AI). Construction & uses, an important book. **\$2.50**

MMD—ELIMINATING MAN MADE INTERFERENCE. What makes it, how to find it, how to cure it in homes, factories, automobiles, aircraft, boats, etc. Or maybe you haven't been plagued lately. 160 pages. **\$2.95**

G-83—FUN WITH ELECTRICITY. This book ought to fire the imagination of the teenager. Build a galvanometer, a dc motor, an ac generator, a solenoid, a spark coil, a Tesla coil, etc. Helps teach the basics of electricity while having fun with simple projects. 128 pages. **\$2.65**

QAN — SECOND CLASS RADIOTELEPHONE HANDBOOK—Noll (W3FQJ). Everything you need to know to pass the FCC exam and get started servicing two-way equipment. Much more than just a Q & A manual. **\$3.95**

86—CONVERTING BC453 TO SSB **\$3.00**

SEE AUG. ISSUE FOR LIST OF CONVERSION MANUALS

Order Form

2 6 8 9 13 16 21 22 23 24 28 32
33 37 40 47 50 52 53 R235 R245 MMD
G83 QAN 86

Circle the book numbers you wish to order.
Please include cash, check, money order . . .
or something we can deposit in the bank.

Name Call

Address

City State

RADIO BOOKSHOP

1379 East 15th Street, Brooklyn 30, N. Y.
(N.Y.C. add 3% tax)

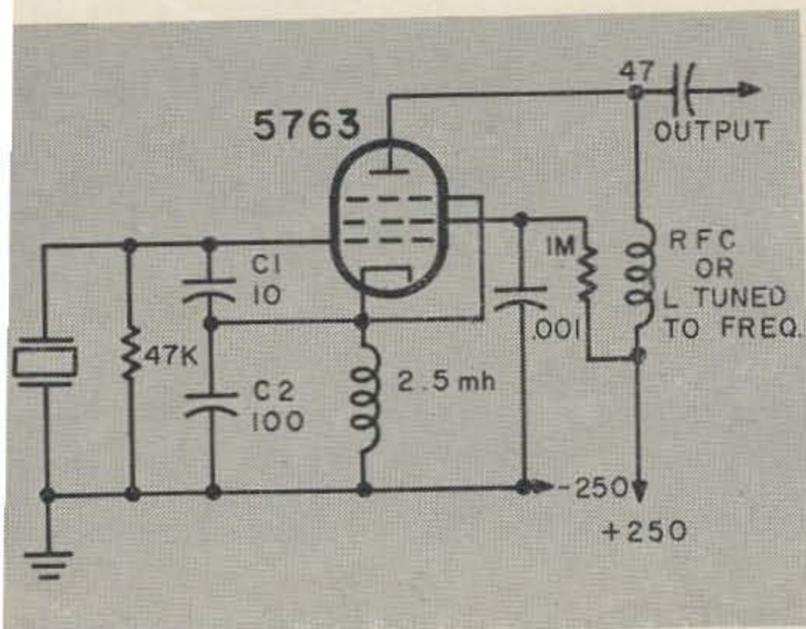


Fig. 17

rcuit.

Tuning of the output circuit is relatively broad; it needs only to be peaked at the center of the operating range. Since the output and oscillating circuits are separated, output tuning has almost no effect on frequency. This means that, like the Pierce, no adjustment of the oscillator is necessary when changing crystals. In practice, this circuit has been found to deliver approximately the same output as a Tri-Tet when used with the same tubes and crystals, at a net saving of two adjustments per crystal change, as well as allowing fundamental operation when desired.

Some circuits recommended by crystal manufacturers haven't been discussed yet; these are all variations of circuits already shown. For instance, International Crystal recommends the circuit shown in Fig. 18 for use with its fundamental-type crystals. This is a Pierce electron-coupled circuit, with capacitors added from each side of the crystal to ground to maintain circuit capacitance at 32 mmfd (International's design value).

The same manufacturer recommends the circuits of Fig. 19 and 20 for overtone use with third- and higher-order crystals, respectively. The third-order circuit is simply a basic Miller, while the higher-order oscillator is a very slight modification of the Butler grounded-grid circuit.

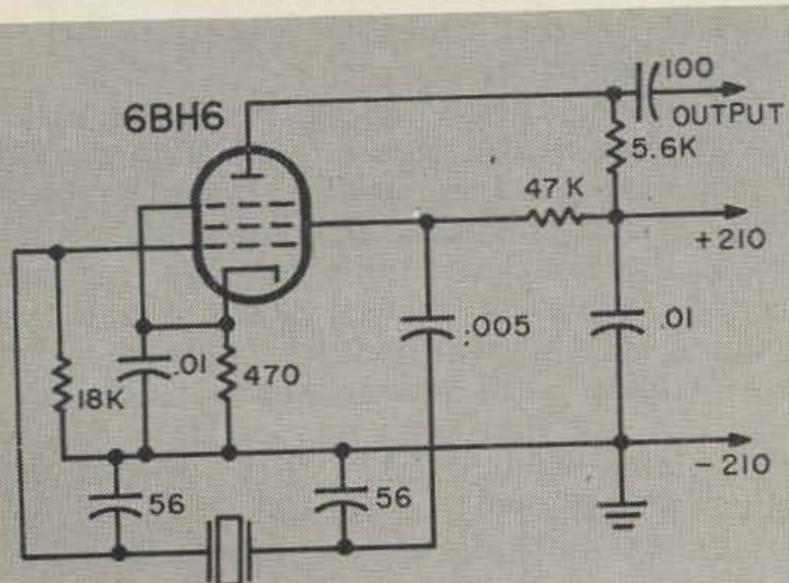


Fig. 18

COLUMBIA GEMS!

WE BUY! BC-610, GRC, VRC, TS Equip. & parts! TUBES, etc. **TOP PRICES PAID!** What do you have?

RT-91/ARC-2 COLLINS TRANSCEIVER

2-9 Mc. 50 W. Xmtr. and Recv'r. Uses Collins PTO oscillator. Includes 22 tubes and 100 kc crystal. Built-in 24 V. dynamotor. Compact table-top unit. F.B. for marine, amateur and mobile use. With Schematic. **\$39.95**
Good Cond. **49.95**
Like new

TDQ 50 WATT 2-METER TRANSMITTER

At last, we got 'em! The ones the VHF boys have been crying for for two years, and at 1/2 the price many have been sold for! Complete— One of the most versatile high power AM transmitters available. No conversion required. Manufactured by RCA. Separate modular Power Supply, RF and Modulator sections. Excellent condition. Final uses 829B driven by 829B. 110V 60 cycles. Like Wow? **THIS IS IT.** Rob us at only..... **\$89.50**

MOBILE RADIOTELEPHONE 150-170 mc FM. 6v input. Output 25 watts. Consists of Transmitter, Receiver, Antenna & connecting cable. Good Condition **\$24.95**

APX-6 TRANSMITTER-RECEIVER SPECTACULAR!
1215 Mc. **LESS TUBES** **\$3.95**
Complete conversion data **\$1.50**

COMMAND SETS!

Q-5'er RECEIVER: 190-555 kc. Excellent.... **\$9.95**
3-6 MC RECEIVER: Excellent..... **7.95**
6-9 MC RECEIVER: Excellent..... **7.95**
2.1-3 MC TRANSMITTER: Excellent....NEW **5.95**
3-4 MC TRANSMITTER: Excellent..... **9.95**
4-5.3 MC TRANSMITTER: Excellent..... **4.95**
5.3-7 AC TRANSMITTER: Excellent..... **4.95**
7-9 MC TRANSMITTER: Excellent. Like New **14.95**
MD-7/ARC-5 PLATE MODULATOR: For all of the above Transmitters. Excellent...Only **4.95**

RA-105 POWER SUPPLY

115 vac, 60 cyc input, multiple outputs: 2400 @ 10 ma., 540 v @ 175 ma., 295 v @ 100 ma., 6.3 vac @ 12 a, 6.3 vac @ 10 a. Tubes: 3-504, 3-2X2, & 1-6X5. **\$9.95**
With tubesExc. Cond.

NEW TRANSMITTING TUBES

4-65A\$ 7.50	4CX250B\$22.50
4-125A 19.95	4-400A 25.00
829B/3E29 ... 4.95	2C39WA 12.95

WRITE IN for new Bargain Bulletin!
All orders FOB Los Angeles. 25% deposit required. All items subject to prior sale. **NOTE MINIMUM ORDER, \$3.00. WRITE TO DEPT. 73**

COLUMBIA ELECTRONICS

4365 WEST PICO BLVD. LOS ANGELES 19, CALIF.

DIRECTIONAL POWER COUPLER

50 TO 500 MCS — 10 TO 1000 WATTS

4 INSTRUMENTS IN ONE



STANDING WAVE RATIO
MODULATION MONITOR
FIELD STRENGTH METER
LINE LOSS
52 ohm model: L52
75 ohm model: L75
BULLETIN E-5275

\$24.50 Each unit individually aligned to insure perfect meter calibration.

NUVISTOR PRE-AMPLIFIER

EXCELLENCE IN PERFORMANCE

MODELS TO COVER:



48-60 MCS—
MODEL G-50
140-150 MCS—
MODEL G-144
210-240 MCS—
MODEL G-220
410-450 MCS—
MODEL G-432
BULLETIN E-5124

\$19.95 Each unit individually aligned for optimum noise figure.

417-A GROUNDED GRID PRE-AMPLIFIER
\$21.95 LESS TUBE \$39.90 WITH TUBE

Eliminate the guesswork from your matching problems. Quarter wave linear balun transformer. Any frequency from 100-500. Any impedance ratio between 50 and 600 ohms. Write for bulletin E50-600

VHF-UHF ASSOCIATES
P. O. BOX 1068
FAIRFIELD, CONN.

Give Your Shack
That Professional
Look



Really dresses up the shack. Wall or table mount. Steel case in black or grey, bright red letters on white background. 10 1/2" x 3 1/2" x 3". Available in other languages, with your call letters, or what do you want it to say? . . . a dollar extra. AC/DC 6-12-120v (specify). Can shine out back window of your car at night, mount on your rig, outside shack door, or where have you.

\$6.95 at your distributor

Distributors write:

STELLAR ELECTRONICS, Box 82, Garland, Tex.

AUTRONIC KEY AND KEYS

For Perfect, Faster CW

Send QSL or Postcard for full data.



FREE TRIAL

Fully transistorized, digital circuitry keyer eliminates erratic sending. Precision-made key will not walk; is fully adjustable.

Electrophysics Corp.
2500 West Coast Hwy.
Newport Beach, Calif.

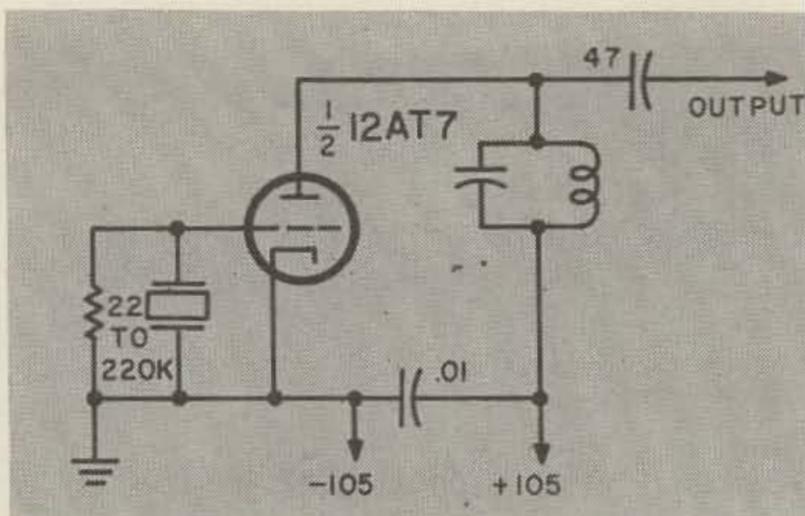


Fig. 19

All the crystal oscillator circuits described so far have one thing in common—they're single-frequency affairs. That is, they provide spot frequencies determined by the individual crystal in use rather than continuous coverage over a ham band. Continuous coverage, most people feel, is the province of the VFO; they reserve the crystal for spot frequencies where stability is important. However, the crystal oscillator *can* provide much of the flexibility of the VFO if properly used. One method has already been mentioned; this is the method of attaching a trimmer capacitor to the circuit to "bend" the crystal's frequency a little. The amount of variation obtainable depends both on the individual crystal and on the amount of frequency multiplication which follows the oscillator. For instance, W9KLR has used this trick to obtain 30 kc adjustable range on 2 meters, starting from a 4 mc crystal. A more extreme case is reported by W4KXI, who uses a special 8-mc crystal in a unique circuit to obtain a full megacycle of frequency swing on 144 mc. Details of the circuit are given in his article; it's too long to reproduce here.

Another approach to variable-frequency operation with crystals is the "frequency synthesizer," a device which uses a number of crystals (sometimes as many as 30) to obtain spot frequencies one kilocycle apart over all ham bands up to 50 or 144 mc. These devices work by mixing two crystal-controlled frequencies together, then selecting either the sum or difference as desired. Often the process is repeated several times to come up with the proper output frequency.

Like all multiple-mixing processes, use of a frequency synthesizer is subject to the bugs of spurious mixing products; they show up here as outputs at undesired frequencies in addition to the desired output. However, when properly designed, one of these gadgets can combine all the best features of both crystal and variable oscillators in a single unit.

Such a unit has been described by W2JKH (see bibliography) and others are also in print. All share the disadvantage of complexity; that's the price you pay for flexibility plus extreme stability and reset accuracy.

By combining both the frequency synthesizer and the "rubber crystal" trick, you can achieve

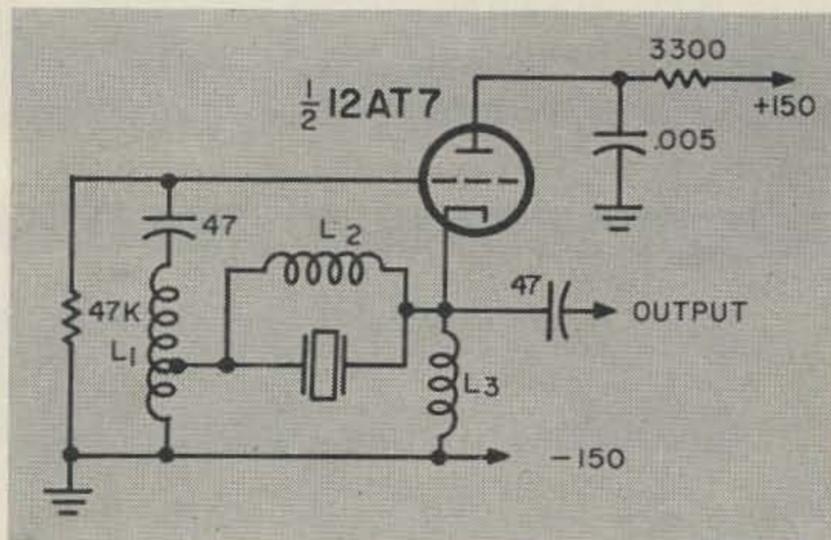


Fig. 20

complete coverage with no blind spots, on every ham band. However, at a slight sacrifice in stability and reset accuracy and an enormous gain in construction simplicity, you can do the same thing with a VFO—and that's the subject of our next technical article.

BIBLIOGRAPHY

- American Radio Relay League, *The Radio Amateur's Handbook*.
- E. B. Blett, W8CBM, FM and TV Interference on the VHF bands, *CQ*, December, 1957, page 46.
- Warren H. Clark, W6COK, Crystal Frequency Comparator, *QST*, December, 1959, page 53.
- Buchanan, John P., *Handbook of Piezoelectric Crystals for Radio Equipment Designers*, WADC Technical Report 56-156, October, 1956 (available through the Office of Technical Services, U. S. Department of Commerce, Washington 25, D. C., for \$7.00).
- William A. Edson, *Vacuum Tube Oscillators*, John Wiley & Sons, Inc., New York, 1953, pages 113, 205, 208-218, and 224.
- Henry G. Elwell, Jr., W2JKH, A Crystal Synthesizer, *CQ*, November, 1959, page 34.
- Jim Kyle, K5JKX, Crystals, *Popular Electronics*, April, 1960, page 83.
- Henry J. Saborsky, W4KXI, A VHF Variable Frequency Crystal Exciter, *QST*, November, 1960, page 27.
- Herman Shall, W3BWK, VXO—A Variable Crystal Oscillator, *QST*, January, 1958, page 11.
- F. E. Terman, *Electronic and Radio Engineering*, Fourth Edition, McGraw-Hill, New York, 1955, chapter 14.
- Edward P. Tilton, W1HDQ, Shifting Frequency With Crystal Control World Above 50 Megacycles, *QST*, August, 1956, page 61.

Letter

Hi! Wayne:

Allright wise guy, what did you do with page 72 of the August issue? I desperately need that K2PMM KW to complete the portable rig I have in mind. It includes a minibox sized 75A4, 50 foot portable collapsible tower and new solar/terra (combining solar power with the plentiful ground currents) transistorized power supply. Publish it right away or I'll tell everyone that you secretly write articles for and subscribe to *QST*.

Wm Magee W2CDJ

Air Force Mars Eastern Technical Net

Sundays 2-4 PM EDST 3295kc 7540kc 15715kc
 Sept. 10—Business Meeting
 Sept. 17—Doing the job with photoelectrics.
 Sept. 24—Communications receiver design.
 Oct. 1—Power generation in the atomic age.

**GRADUATE—
 TO MOBILE ANTENNA PERFECTION!**

**WITH THE EBCO
 SKYSWEEPER SPECIAL**



**4 ELEMENTS — BECAUSE
 THEY WORK SO MUCH BETTER!**

- 2-1/2" diam. parasitic elements
- 1-3/8" diam. driven element
- 1-5/8" diam. element

WORKS LIKE A BEAM! — —

**BUT — IN ALL DIRECTIONS AT ONCE
 EXTREME LOW ANGLE RADIATION
 NO MATCH REQUIRED — 52 OHMS**

EBCO MANUFACTURING CO.

Box 895, Los Amigos Station, Downey, California
 Box 416, Village Station, Warren, Michigan
 Box 23, Stoneham 80, Massachusetts



**THE NEW, COMPACT
 Loudenboomer
 MARK III
 ANTENNA ROTATOR**

\$225⁰⁰

**Complete with brackets for "in-tower" mounting
 and direction indicator.**

- **Worm cut into large, one-piece steel jack shaft.** 3/4" thick gear welded to main shaft and specially hobbled. No keys, no screws, no pins to work loose.
- **High strength rotor** withstands 12,000 inch pounds. Absolutely will not drift or pinwheel in high wind.
- **High torque,** 1/8 H. P. custom built G. E. motor. 1 1/2 R. P. M. turning speed.
- **Continuous rotation** in either direction with 50 ohm coax feed system through rotor. SO-239 connectors.

Radio Industries Inc. unconditionally guarantees all products against any defect in material or workmanship for a period of 90 days.



**SEE YOUR DISTRIBUTOR
 RADIO INDUSTRIES INC
 1307 CENTRAL AVENUE
 KANSAS CITY, KANSAS**

(3054)

PROPAGATION CHART

EASTERN UNITED STATES TO:

G.M.T.	00	01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24
ALASKA																									
ARGENTINA																									
AUSTRALIA																									
CANAL ZONE																									
ENGLAND																									
GERMANY																									
HAWAII																									
INDIA																									
JAPAN																									
MEXICO																									
PHILIPPINE'S																									
PUERTO RICO																									
SOUTH AFRICA																									
U.S.S.R.																									

CENTRAL UNITED STATES TO:

G.M.T.	00	01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24
ALASKA																									
ARGENTINA																									
AUSTRALIA																									
CANAL ZONE																									
ENGLAND																									
GERMANY																									
HAWAII																									
INDIA																									
JAPAN																									
MEXICO																									
PHILIPPINE'S																									
PUERTO RICO																									
SOUTH AFRICA																									
U.S.S.R.																									

WESTERN UNITED STATES TO:

G.M.T.	00	01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24
ALASKA																									
ARGENTINA																									
AUSTRALIA																									
CANAL ZONE																									
ENGLAND																									
GERMANY																									
HAWAII																									
INDIA																									
JAPAN																									
MEXICO																									
PHILIPPINE'S																									
PUERTO RICO																									
SOUTH AFRICA																									
U.S.S.R.																									

LEGEND

7 MC

14 MC

21 MC

28 MC

Propagation Charts

David A. Brown K2IGY
30 Lambert Avenue
Farmingdale, N. Y.

For the DX propagation chart, I have listed the HBF which is the best Ham Band Frequency to be used for the time periods given. A higher HBF will not work and a lower HBF sometimes will work, but not nearly as well. The time is in GMT, not local time.

Advanced Forecast: September 1961

Good: 6-20

Fair: 4-5, 21-24, 27-29

Bad: 1-3, 25-26, 30

The Short Path propagation chart has been set up to show what HBF to use for coverage between the 48 states. Alaska and Hawaii are covered in the DX chart. The use of this chart is somewhat different than the DX chart. First, the time is the local time centered on the mid-point of the path. Second, the distance given in miles is the Great Circle path distance because of the Earth's curvature. Here are a couple of examples of how to use the chart. A.) To work the path Boston to Miami (1250 miles), the local time centered on the mid-point of the path is the same in Boston as in Miami. Looking up the HGF's next to the 1250 mile listings will give the HBF to use and the time periods given will be the same at each end of the circuit. B.) To work the

WATT FOR WATT —UNBEATABLE!

\$44.50 for 125
WATTS at 85%
efficiency!



Dual Output:
500V @ 200 MA.*
250V @ 100 MA.*
ripple less than 1%

*or any combination of currents totalling 125 watts.

Input: 12VDC positive or negative ground.
FOOLPROOF — No loss of expensive power transistors thru wrong connection — completely protected from wrong polarity or HV short.

Small, but mighty! 4 x 4 x 5!

AIR ELECTRONICS
MODEL PS-12-125

\$44.50

AMATEUR NET

Postage Paid
MONEY BACK GUARANTEE—1-YR. PARTS WARRANTY
SAVE MONEY, SPACE, WEIGHT — CONVERT YOUR SHACK OR CAR TO AIR ELECTRONICS TRANSISTORIZED POWER SUPPLIES!

AIR ELECTRONICS CO.

7250 Hinds Avenue N. Hollywood, Calif.

path New York to San Francisco (2,600 miles), the local time centered on the mid-point of the path will be 1½ hours later than at San Francisco and 1½ hours earlier than in New York (the time difference between New York and San Francisco is 3 hours). Looking up the HBF's next to the 2,500 mile listings will give the HBF to use. In San Francisco subtract 1½ hours from the time periods listed for local time and in New York add 1½ hours to the time periods listed for local time.

UNITED STATES SHORT PATH PROPAGATION CHART

SEPTEMBER 1961

G.M.T.	00	01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24
2500 MILES																									
2,250 MILES																									
2,000 MILES																									
1,750 MILES																									
1,500 MILES																									
1,250 MILES																									
1,000 MILES																									
750 MILES																									
500 MILES																									
250 MILES																									

LEGEND

3.5 MC

7 MC

14 MC

21 MC

Ham Headlines

If ham radio makes the newspapers in your town please send a clipping to Marvin Lipton VE3DQX, 311 Rosemary Road, Toronto 10, Ontario, Canada. Marvin runs the 73 News Service, a monthly publication sent to all editors of club bulletins. He will digest the most important stories that are submitted each month for us to print in 73.

HAMS HELP BLIND PEOPLE

(Toronto Daily Star.) When a group of 30 blind people began to look farther afield for more chess competition, VE3TC and VE3AEO came to the rescue. Both hams provided communications for the sightless players who are members of the Canadian Institute For The Blind Chess Club. It was hoped that the first 73 move game would provide inspiration for other hams to take up the call and lend their radio time to other CNIB players.

(Philadelphia Inquirer, submitted by J. Rosewald Jr.) A photographic description of a series of earthquakes in San Jose, Costa Rica, was given to a Philadelphia radio ham recently. William Weisbord, 57, was talking to a fellow ham in Costa Rica when the quake hit and forced the station to go off the air.

Weisbord learned from another station in Costa Rica that no serious injuries had occurred although considerable property damage resulted. The same night other stations were monitored and they also reported earthquakes in their areas.

New Books

You know, you could do a lot worse than keep up with the Rider Electronic Technology Series of publications. The latest in this series are two books by Dr. Alexander Schure, one on Transformers (#166-37 @ \$2.00) and one on Filters and Attenuators (#166-36 @ \$2.25). The books give you a thorough treatment of the theoretical and practical aspects of these circuit elements. These books cover each element of electronics with care that could never be used in a single book.

Locate and Eliminate Interference

How To Locate and Eliminate Radio & TV Interference, Rider #158, \$2.90, is the second edition of this book—covers the subject quite well. It explains what makes noises, what you use to track them down, how you go about finding some of the more difficult ones, and what you do about them after you've located the misery.

Citizens Band Radio

Citizens Band Radio, Rider #273, \$3.90, is more handbook than anything. It gives all the rules, covers just about every piece of available equipment and its application, the antennas, power supplies, kits, servicing, etc. Hams, whether they themselves like CB or not, are expected to be experts on the subject. This book will make you an expert.

Transistor Substitution Guidebook

The new Rider (#276, \$1.50) International Transistor Substitution Guidebook for direct transistor substitutions has been badly needed. It lists over 4500 direct substitutions of American, Japanese, British, Dutch, French, Italian and German transistors.

Basic Mathematics

A lot of fellows, as a result of the terrible teaching methods being used in many schools, have gotten the idea that math is not for them. Since math is so fundamental in our hobby it stands to reason that this trauma should be repaired if possible. This book (Rider #268-1, \$3.90) certainly should get almost anyone over the idea that math is hard to understand.

IN THE --- - WEST - it's

WESTERN RADIO

and TELEVISION
SUPPLY
CO.




FOR OVER 25 YEARS ONE OF THE WEST'S OLDEST AND LARGEST FIRMS
DEVOTED EXCLUSIVELY TO AMATEUR AND ELECTRONIC EQUIPMENT.

**1331 India St.
P. O. Box 1728**

**San Diego 1, Calif.
BElmont 9-0361**

NEW FEATURE-PACKED TRANSMITTER

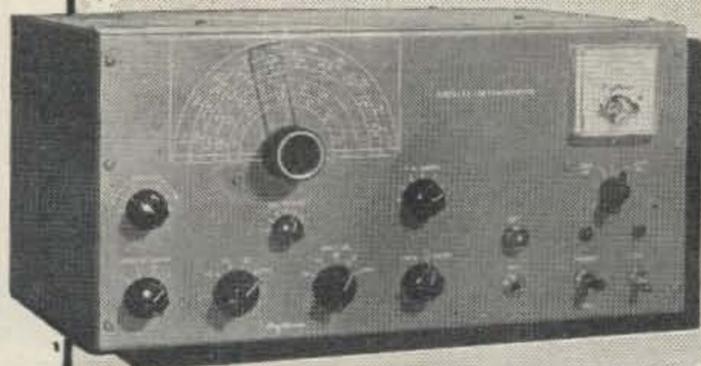

CT-120

combines real operating convenience and dependability with the high performance usually associated with more costly equipment.

Expressly designed for the amateur who wants a **complete** general-purpose transmitter in a single, easy-to-operate package, the CT-120 provides all the most important features at a truly economical price.

FEATURES

- Completely self-contained, including VFO and power supply (115 vac)
- Single-knob band-switching on 10-15-20-40-80 meter bands
- Plate power input: 120 watts CW; 80 watts Phone (AM)
- Time-proven reliable 807's parallel final amplifier
- High-efficiency screen modulation
- Oscillator cathode keying with clamp-tube key-up protection
- Temperature-compensated VFO accurately calibrated on all five bands. VFO/three-crystal selector switch
- Pi-network output matches 30- to 1000-ohm loads
- Built with high-quality, conservatively-rated components
- Functional panel layout provides maximum operating convenience
- Cabinet Dimensions: 15 $\frac{3}{4}$ " W x 8" H x 9 $\frac{3}{4}$ " D.

ORDER DIRECT FROM FACTORY:

Amateur net price: \$187.50 f. o. b. Santa Clara, Calif., completely wired and tested, with tubes, less crystals, key, microphone. Shipping weight: 40 lbs. Complete descriptive literature available on request.

CRAFTRONICS

920 Shulman Ave. • Santa Clara, California



SATURN 6

the original

HALO

How come thousands of these little gadgets are riding around on the backs of cars all over the country? And how come so many are in use at fixed locations?

WELL

Verticals were tried first for mobile work. Most fixed stations used horizontal polarization and could hardly hear the mobiles. Flutter was a serious problem. When Hi-Par introduced the Saturn 6, mobiles found they could work fixed stations over amazing distances and that flutter was a thing of the past. Ignition noise was greatly reduced too. The antenna became very popular for fixed stations too since it was omnidirectional and horizontally polarized. Beams are great, but much of the time you want to talk to stations in more than one direction at a time.

Saturn 6 Antenna only... **\$11.95**


Saturn 6 plus mast &
bumper mount... **\$16.95**

We make a lot of other antennas, but this is our best seller. Write for info on this and other antennas. Order through your local parts distributor or direct.

HI-PAR

Products Co.

FITCHBURG, MASSACHUSETTS

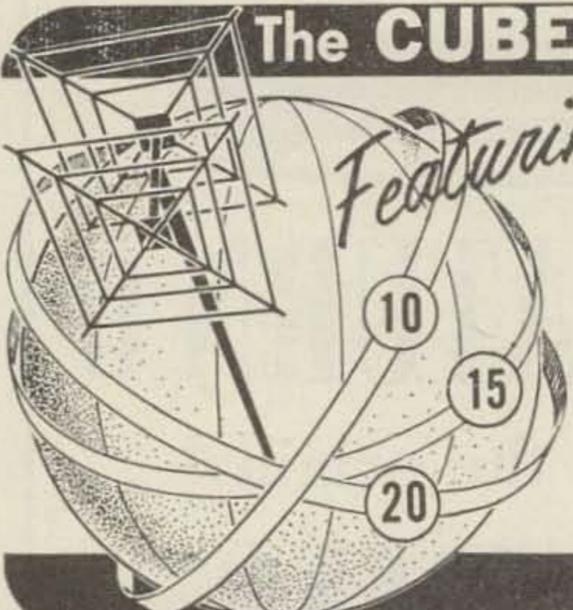

The CUBEX MK III De Luxe 3 BAND QUAD

FOR 10 — 15 — 20 METERS

- SINGLE FEEDLINE—3 BANDS (optional)
- HIGH GAIN ● HIGH FBR ● LOW RADIATION ANGLE
- HEAT TREATED ALUMINUM END SPIDERS
- HUSKY FORMED ALUMINUM BOOM-TO-MAST FITTING
- RUGGED 2" DIAMETER TUBULAR ALUMINUM BOOM

Gain: 10 db on 10 and 15 — 8 db on 20. F/B Ratio 24 db.

Low Wind Resistance — Light Weight, only 27 lbs. — TV Rotor Handles — Low SWR — Pre-tuned Reflector Coils — No Stubs

The CUBEX MK III gives you 3 FULL SIZE, FULL EFFICIENCY, beam antennas with separate FULL WAVE driven elements on each band. All this in half the horizontal space required by a 3 el, 20 mtr. beam.

Only
\$67.50
F.O.B. Factory
Other Models
from \$49.50

WRITE FOR FREE BROCHURE "M"

CUBEX COMPANY

3322 TONIA AVENUE • ALTADENA • CALIFORNIA

THE VHF AMATEUR

This magazine was begun several years ago in an effort to provide the VHF man with his own publication devoted entirely to the world above 50 mc. Since its beginning, **The VHF Amateur** has grown to the point where we now enjoy readership in all fifty states and over twenty foreign countries—for a total of more than 3,000 circulation (all VHF men). We are proud of our little endeavor, and would like you to become a part of it. We are now bringing our select group of readers forty pages a month of all we can get our hands on that pertains to VHF. In the past few issues of **QST** we have mentioned the names of articles in our current issue. But our July issue was such a great success that we'll just surprise you with it except to say that we have regular columns on Moonbounce, Propagation Forecast for 6 and 2, Free Trading Post, S.S.B., and much more. In addition, we are giving away converters, transmitters, and a Clegg 99'er transceiver! Read how to win hundreds of dollars worth of gear! Ask to start your subscription with the July issue. Subscriptions: \$2.00 for one year, \$5.00 for three years. (Send quarter for sample). Editor-Publisher: Bob Brown, K2ZSQ.

THE VHF AMATEUR, 67 Russell Ave. Dept. EX, Rahway, N.J.

Give A Look

KTV Hy-Track towers are now located in the following areas:

Boston	Richmond, Mich.
Stamford	Chicago
Passaic	Shelbyville, Ill.
Troy, N. Y.	Lincoln, Neb.
Cleveland	Ogden
Toledo	Albany, Ga.
	Jacksonville

If you'd like to see what they look like just drop a card and we'll send the call and QTH where you can see it.

KTV TOWERS

P.O. Box 294 • Sullivan, Ill.
(See our ad on page 6, March, 73 Mag.)

Letters

Dear Wayne:

Just flipped the back cover of August 73 closed with my usual smug grin of satisfaction, but this time you have hit an article that really takes my fancy. I refer to the article about the KW transistor mobile transmitter on page 72. You have finally hit on what I've been looking for for years and I am starting to build it immediately; that is just as soon as I can find the parts in the catalogue. Can't seem to find some of them. Had the same trouble finding the parts list in the article. You really have to look this one over close as it tends to elude you. Hope I don't have too much trouble identifying the parts when they come.

For years I've wanted to put a mobile rig in the family bus, but the XYL always complained that it got in the way of her knee's. Now I can have a gallon right under her nose and she won't even know it's there. She may think I've finally blown my gasket when I start talking to someone but that's alright because she thinks I'm nut's anyway, so that won't be anything new. My one big hope is that it will be as inconspicuous in the car as it is in the magazine. I wonder if you have any idea's for an invisible whip to go along with the rig? The regular whip may give me away. I thought I might be able to use a throat mike instead of a hand mike, then I could crank up the gain and just mumble, my wife says I mumble all the time any way so she will be used to this and may never catch on. I can hardly wait.

So listen close on 20 meters in the near future Wayne and when you hear a large clear spot of beautiful dead silence you will know I'm on the air. By the way I have heard a lot of guy's around town grumbling; seems the printer's left this article out of their magazine. Well I'll loan them mine when I finish the rig. Wonder what you have for next month. . . .

Earl Spencer K4FQU

Dear Wayne:

I just finished reading Frank Merritt, Jr's fine article "The Drake Receiver" in your August issue. There are a few points however, which I feel require some clarification. First, all 2-Bs have a fast AVC decay time of .025 seconds rather than the .05 second figure mentioned in the article. While it was true that the 2-A has a .05 second decay time, this figure was reduced in the 2-B to permit greater ease in operating break-in CW. The first audio amplifier stage consists of the triode section of an 8BN8 tube. The two diode sections in this tube are used as bias rectifier and AM noise clipper respectively. This arrangement is common to all 2-Bs as well as many 2-As.

There have been no significant modifications in the 2-B since production began, so a modification service on it is not available nor necessary. Because of the expense involved and the chassis alterations which would be required, we do not feel that it would be practical to modify earlier 2-A receivers to include noise limiter circuits and are not offering such a service.

It is also worth noting that the 2-B combines the advantages of a "ham band only" receiver with the capabilities of extended coverage. It is equipped with five accessory bandwidth positions which permit the addition of five 600 KC tuning ranges between 3.5 and 30 mc by merely adding the appropriate crystals to the respective socket. This feature is particularly useful for "MARS" coverage and would prevent it from becoming obsolete in case changes were made in amateur band frequency allocations.

All of us here at the R. L. Drake Company were well pleased with the article and we would like very much to congratulate Mr. Merritt on a job well done.

James F. Waits, Engr. Dept.
R. L. Drake Company

Dear Wayne:

Oops! is doubly appropriate for your July issue. Don't you know a dipole from a vertical ground plane either?

Hi. (Page 8.)

Would you please inform our readers that they should cross out "18 inch elements and two of the" in the eighth sentence below the picture of the "Tinker Toy Tree Element Beam" on page 10. Otherwise they would end up with six quarter wave segments in the driven element. Thought I marked that "delete" on the photo.

My only other complaint, Wayne, is that you really let your readers on the spot in asking them to vote for the best articles each month. There are so many good ones in this month that a fellow could develop some sort of complex in attempting to make such a weighty decision. Keep up the good work.

Bill K8LFI

(W2NSD from page 4)

July Votes

July was the nip and tuckiest month yet, noteworthily. The Two Meter Nuvistor Line Amplifier nudged out Tinker-Toy for Two by only twelve votes out of over 1500 for each! We'll continue to run Nuvistor articles in spite of RCA's complete indifference to 73 as an advertising medium. We have several more good Nuvistor articles being prepared for publication, including a fine 220 mc converter.

Our big Pandaptor was in third place by only seventeen more votes. Nine votes behind was our Big Technical Article on power supplies, and tied with it was W7CSJ's article on AM systems. That was quite an issue. Be sure to send in your vote for articles you like best in this issue as this helps me to decide what to publish in the future and pays off the winning authors with an extra 50% pay.

August should be a light month for votes, but they are coming in hot and heavy. The Nuvistor converter seems to have a strong lead so far, but a sudden surge of votes for the Impedance Bridge or the Deviation Meter could change the order. You may have noticed that there was a place to vote for the most interesting ad on the card too. I had in mind giving maybe a 50% rebate for the ad which wins this vote each month. The purpose of this would be to encourage companies to put a little more effort into their advertising and eventually make the magazine more interesting to read. The Drake ad is leading so far, with Clegg Laboratories not far behind.

Renewals

With several thousand subscription renewals all coming due this month I was a bit worried about how hard a time we would have in getting the fellows to re-subscribe. I needn't have worried. With still one more issue to go there are now less than 500 who have not renewed! If your stencil ends in 91-01-N1-D1 then your subscription is running out. Send money.

BC-221 FREQUENCY METER.	\$69.50
Like New	
85kc IF Transformers	2.25
ARC-12, New. 79¢ ea. 3 for.....	
BC-603 FM Receiver	14.95
20-27.9 Mc. Exc. cond.	
B-603 FM Receiver	18.95
20-27.9 Mc. Brand New	
BC-923 A FM Receiver	29.95
27-38.9 Mc. Brand New	
ART-13 Transmitter	39.50
with tubes & meters, used.....	
BC-604 MF Transmitter	4.95
with tubes. Brand New	
Antenna Mast Base	2.95
& 3-39" Mast Sections.....	
ARC-2 Transceiver, Collins	29.50
Permeability Tuned Oscillator Excellent....	
APS-19 "X" Band Rec-Trans.	P.U.R.
with 2J55 Magnetron	
APS-20 "S" Band Synchronizers	19.95
with 34 tubes	
ID-6/APN-4 Indicator	2.95
less tubes	
B-442 Antenna Relay	1.95
with Meter & Vac. Cap.	
ARR-2 Receiver,	4.95
11 tubes with CB conversion.....	
ARC-3 AM Receiver	12.95
100-156 Mc. Excellent	
ARC-3 AM Transmitter	14.95
100-156 Mc. Excellent	
I-130A Signal Generator,	7.95
100-156 Mc.	
I-95B Field Strength Meter,	7.95
100-156 Mc.	
DM-34 Dynamotor,	2.95
brand new	
DM-35 Dynamotor,	9.95
brand new	
KY65/ARA-26 Automatic Keyer	2.95
as converted in this issue of "73".....	

Send Money Order or Check with Order

Write for Bulletin No. 33 — LOADS OF BARGAINS!


R W ELECTRONICS

2430 S. Michigan Avenue
Phone: CAIumet 5-1281

Dept. 73
Chicago 16, Illinois

THINKING SIX

(OR TWO)

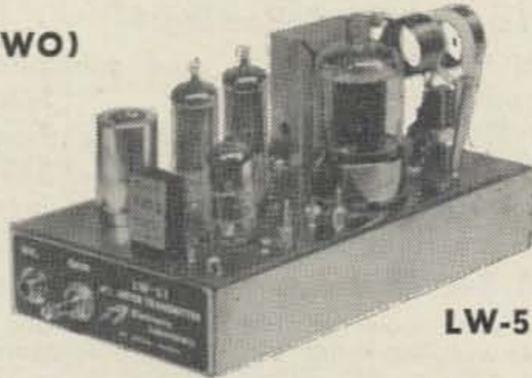

LW-51

	6M 50 watt	2M 45 watt
Kit price	\$37.50	\$39.95
W/tubes & xtal.	49.50	54.95

Both models in kit form have over 85 chassis parts mounted and all difficult soldering completed with explicit wiring instructions and photo-diagrams. Xtal osc, using low priced 8 mc xtals, multiplier(s), straight-thru final, two stage speech amp, push-pull modulators.

May be converted to LW-51 DELUXE for \$25

Other products:


LW-61 VHF Converters	\$18.50
LW-80 Pre-Amplifiers	12.50
LW-72A Transmitter Power Supply	49.95

LW ELECTRONIC LABORATORY
ROUTE 2 JACKSON, MICHIGAN

Amateur & CB Crystals

\$3.00 2500 kc to 15,000 kc, fundamental frequencies 15 mc to 30 mc, third mode

\$3.50 30 mc to 50 mc

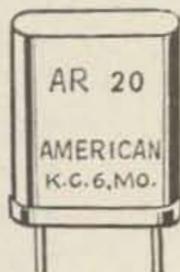

All crystals for amateurs are set at 20 mmfd, hermetically sealed with pins optional: .050" (CR-1); .093" (FT-241/3); .125" (HC-6); 1/2" centers.

Citizens Band transmitter crystals in stock for the following equipment: JR-800, 761A, CD1, GW10, CD5, CD100, CD100A, TR330, C27, AT20, Messenger, MK7, R2700, TR910, 27C2, ED27, CR117, CDD5, CT1, RP115, CD27, TECT. Guaranteed .004% of nominal: \$3.00.

AMERICAN CRYSTAL CO.
P.O. BOX 2366 • KANSAS CITY 42, MO.

6 METER "PACKAGE DEAL"

only \$19.98 postpaid

Consisting of the following:

- I—VANGUARD 5 watt, crystal controlled R.F. transmitter\$14.99 list
- I—VANGUARD modulator for carbon and crystal mikes\$15.99 list
- I—VANGUARD crystal controlled converter with broadcast band output.....\$15.99 list

A \$46.97 value for only \$19.98

All units are new printed circuit modules, tested and complete with all tubes and crystals. Requires 150 to 300 volts d.c. and 6 or 12 volts.

VANGUARD ELECTRONIC LABS

Dept. H-9 190-48 99th Ave., Hollis 23, N. Y.

JIM CLARK * WIULU

KIT WIRING & TESTING LABS

REPAIRS & SERVICE ON ALL MAKES OF HAM GEAR AND

TEST EQUIPMENT, CITIZENS BAND GEAR & HI-FI

2 Aiken St. Tel. HEmlock 2-3600 Derry, N. H.
ALL WORK GUARANTEED

Reyco Multiband Antenna Coils

Traps for dipoles . . . high strength . . . moisture proof guaranteed to handle a full KW. Model KW-40 coils will, with a 108 foot antenna, provide operation on 10-15-20-40-80. \$12.50 set.

For information on other models write:

FRED L. REYNOLDS W2VS, 492 Ravenswood Ave., Rochester 19, New York

Advertisers

Air	65
Alden	27
Allied	47
Alltronics-Howard	55
American Crystal	70
Arrow Electronics	25
Burghardt	51
B & W	43
Cabral Motors	9
Candee	53
Central Electronics	11
Clark	70
Clegg	3
Columbia	61
Cornell-Dubilier	15
Craftonics	67
Cubex	68
Cushcraft	56
Ebco	63
Editors and Engineers	57
EICO	5
Electro-Physics	62
Elliott	29
Evans	55
E-Z Way Towers	27, 54
GAM	59
Glass	58
Graham	57
Ham TV Book	56
Heath	19
Hi-Par	67
International Crystal	13
Jennings	4
Johnson	Cover II
KTV	68
Lafayette Radio	73
L-W Electronics	69
National Radio	Cover IV
Neil	17
Novelties	57
Petersen	Cover III
P & H	51
Quaker	52
Radio Bookshop	60
Radio Industries	63
Reyco	70
Roberts (J-Beams)	54
R-W	69
Shure	21
Space Raider	41
Springfield	70
Stellar	62
Subscriptions	4
TAB	71
Tapetone	45
Technical Material Corp.	23
Telrex	55
Texas Crystals	49
VHF Amateur	68
VHF-UHF Associates	62
Wattmeter	52
Western Radio	66
World Radio Labs	31

For Superb Performance, Quality & Value

LOOK TO LAFAYETTE FOR THE BEST BUYS IN AMATEUR GEAR

THE LAFAYETTE HE-30 Professional Quality Communications Receiver



99.50

- TUNES 550 KCS TO 30 MCS IN FOUR BANDS
- BUILT-IN Q-MULTIPLIER FOR CROWDED PHONE OPERATION
- CALIBRATED ELECTRICAL BANDSPREAD ON AMATEUR BANDS 80 THRU 10 METERS • STABLE OSCILLATOR AND BFO FOR CLEAR CW AND SSB RECEPTION • BUILT-IN EDGEWISE S-METER

Sensitivity is 1.0 microvolt for 10 db, Signal to Noise ratio. Selectivity is ± 0.8 KCS at -6db with Q-MULTIPLIER. TUBES: 6BA6—RF Amp, 6BE6 Mixer, 6BE6 OSC., 6AV6 Q-Multiplier—BFO, 2-6BA6 IF Amp., 6AV6 Det-AF Amp. ANL, 6AQ5-Audio output, 5Y3 Rectifier.


New! LAFAYETTE HE-50 10 METER AMATEUR TRANSCEIVER



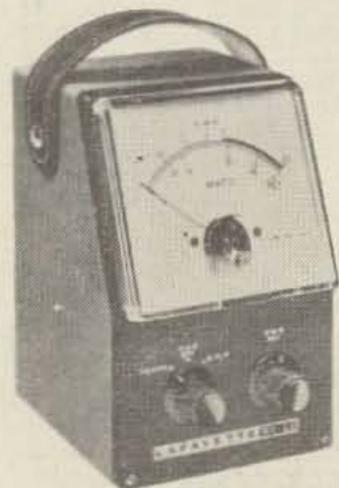109.50 Made in U.S.A.

A significant step forward in 10-meter communications. The Lafayette HE-50 transceiver sets new standards of flexibility and performance in the 10-meter band.

- Superhet Receiver Section • Sensitivity $1\mu\text{V}$ • Image Rejection 45db • 12 Watts. Input To Final • Use on both 117 VAC & 12 VDC • Built-in Mobile Power Supply • Uses Standard 7 MC Fundamental Crystals with Sockets on Front Panel • Provision for External VFO on Front Panel • Adjustable Pi-Network • Contains Spotting Switch • Built-In Illuminated S Meter • Variable Tuning • Extremely Effective adjustable Noise Limiter • Complete with Rugged Push-To-Talk Ceramic Mike • Tubes: 1—6BA6 RF, 1—6BA6 IF, 1—6U8/6EA8 IF, 1—6U8/6EA8 IF, 1—6U8/6EA8 Transmit Osc. & Buffer, 1—2E26 Transmitter Output, 1—6AQ5 Audio Output, 1—6CN7 Det. & Noise Limiter.



HE-28 RF WATTMETER AND SWR BRIDGE **36.95**

Measures SWR & Relative Power up to 1 KW. 150 watts full scale—built in dummy load—Wattmeter $\pm 5\%$ to 50 mcs. SWR $\pm 5\%$ for in line use.

TOP VALUE COMMUNICATIONS RECEIVER

KT-200WX in Kit Form

64.50

HE-10 WIRED AND TESTED

79.95



- SUPERHET CIRCUIT UTILIZING 8 TUBES AND RECTIFIER TUBE • BUILT-IN "S" METER WITH ADJUSTMENT CONTROL
- FULL COVERAGE 80-10 METERS • COVERS 455KC TO 31 MC
- VARIABLE BFO AND RF GAIN CONTROLS • SWITCHABLE AVC AND AUTOMATIC NOISE LIMITER

The Communications Receiver that meets every amateur need—available in easy-to-assemble kit form. Signal to noise ratio is 10 db at 3.5 MC with 1.25 microvolt signal. Selectivity is -60 db at 10 kc, image reflection is -40 db at 3 MC. Tubes: 3—6BD6, 2—6BE6, 2—6AV6, 1—6AR5, 1—5Y3.

SEND FOR LAFAYETTE'S NEW 1962 CATALOG

LAFAYETTE RADIO, Dept. 731-1
P. O. Box 10
Syosset 10, N. Y.

FREE!



Send FREE 1962 Catalog 620 featuring the full line of Lafayette Ham Equipment
Catalog 620 340 Giant Size Pages
\$ _____ Enclosed for Stock No. _____

Name _____

Address _____

City _____ Zone _____ State _____

25 YEARS with PR!



■ Adolph Schwartz, W2CN, is celebrating his 25th year as sales representative for PR Crystals. But W2CN was a ham operator long before that. His original ham license was dated April 12, 1916 . . . Commercial First Class License dated 1917. Before and after World War I, Adolph had call letters 2AFT and 2ASK. He has always been an active amateur, and his present license is Amateur Extra First Grade.

■ Here is W2CN at his rig. Rx-Collins 75A4. Tx-Johnson KW Final. Driver Johnson Pacemaker. Antennas: 40M, inverted vee dipole. 20, 15, 10 M, 3 separate 3-elem. beams. W2CN is active on SSB, AM, and CW, on 40, 20, 15 and 10 meters. He likes to chase DX and has over two hundred confirmations. Give him a call sometime.



■ Top Row: 1916 Ham license; renewal 1917 Commercial License; Bill Eitel and W2CN. Lower Row: First Class Commercial License, 1921; 1919 Ham License 2AFT; U.S. Army Discharge; W2CN tied to ball and chain.

■ PR Crystals have been the standard of quality since 1934. It was their outstanding performance and dependability that first interested Adolph Schwartz. In March 1936 he started using PRs in his rig at W2CN. He was so impressed by PR Crystals that he immediately asked to be their sales representative in the New York territory. Says W2CN: "It is a pleasure to sell PR Crystals because they are quality products that operate without trouble to their owners."

Yes, it is a pleasure to sell PR Crystals, but the most pleasure comes in using them in your rig. Many thousands of hams have used PRs for years with complete satisfaction. Every PR Crystal is UNCONDITIONALLY GUARANTEED. Get them from your jobber.


PR


Crystals

Since  1934

USE  AND KNOW WHERE YOU ARE

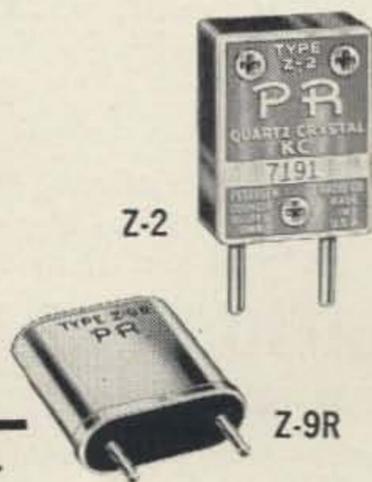PETERSEN RADIO COMPANY, INC.
2800 W. BROADWAY • COUNCIL BLUFFS, IOWA



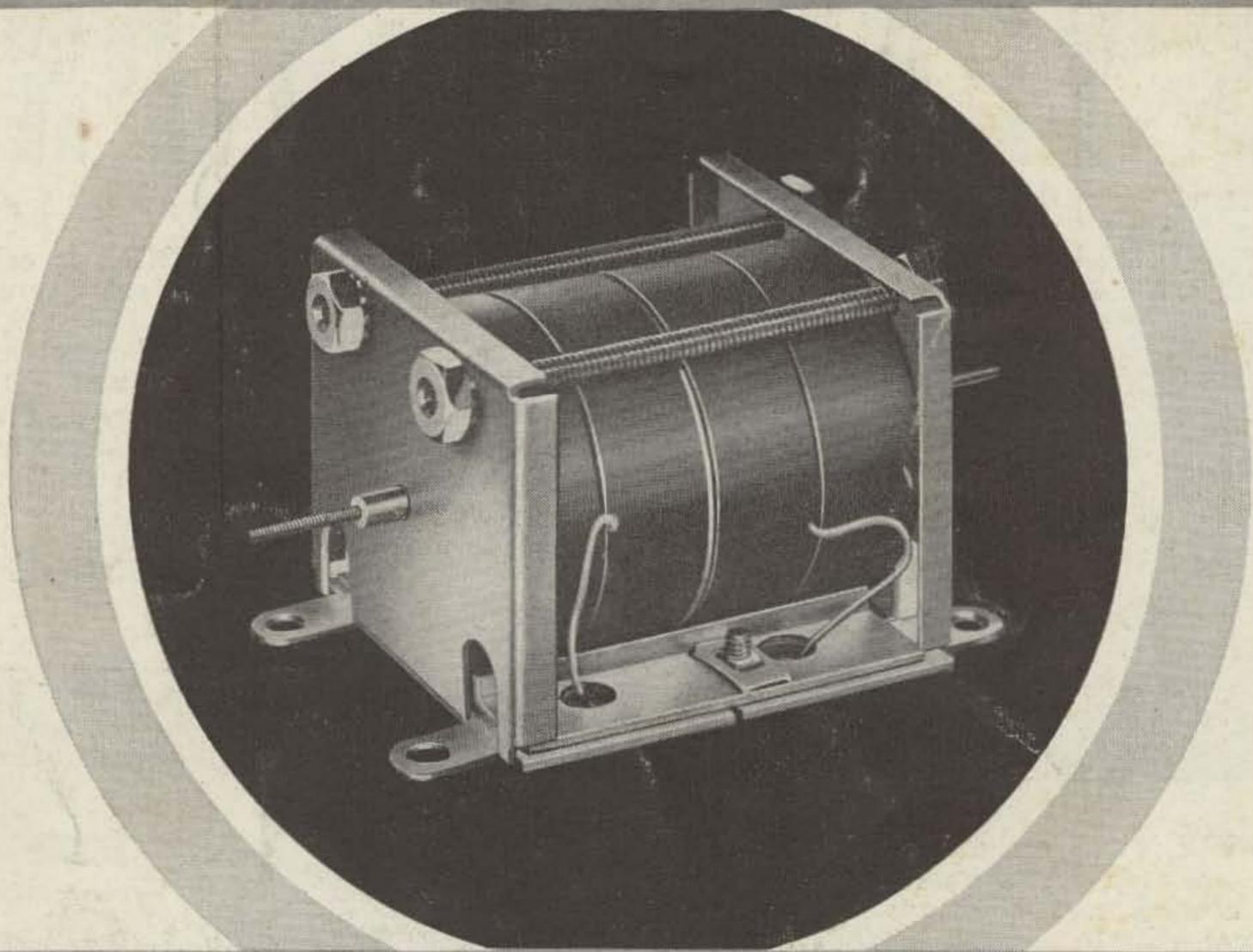

INSTANT SSB-CW-AM-SELECTION WITH NATIONAL'S FERRITE FILTER* IN THE NEW NC-270

National's patented Ferrite Filter provides instantaneous selection of 5 kc, 3 kc, and 0.6 kc bandwidths *plus* 2.5 kc selectable sideband with no extra filters to buy! It's available only in National's new "Cosmic Blue" NC-270!

The compact high permeability construction of the Ferrite Filter provides an average "Q" of 500 at 230 kc. The higher filter frequency in the NC-270 means superior secondary image rejection—none of the blocking problems or spurious signals characteristic of receivers using very low intermediate frequencies. And—*stable* "IF Shift" selectable sideband means . . . the NC-270 does not rely on mixing oscillators to maintain zero-beat.

Make Sure You Check These Features Of The NC-270: 6 meter band included, (no converters to buy); sensitivity—1.5 uV for 10 db signal to noise ratio; product detector for SSB and CW; Bi-Filar T-Notch Filter with external depth control; built-in 100 kc calibrator; extreme mechanical and electrical stability; compact, modern styling—the NC-270 includes National's "Flip Foot" for maximum operating convenience . . . plus many other features.

Only \$24.99 down**

Suggested cash price: \$249.95. NTS-3 Matching Speaker: \$19.95 (slightly higher west of the Rockies and outside the U.S.A.). **Most National distributors offer budget terms and trade-in allowances.


NATIONAL RADIO COMPANY, INC.



MELROSE 76. MASS.

A WHOLLY OWNED SUBSIDIARY OF NATIONAL CO., INC.

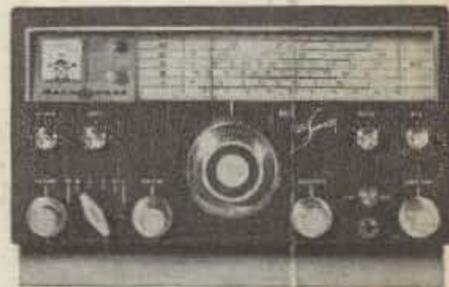Export: AD AURIEMA, INC., 85 Broad St., New York, N. Y.
Canada: TRI-TEL ASSOCIATES LTD., 81 Sheppard Avenue W., Willowdale, Ont.



*PATENT PENDING

SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE