

AMATEUR RADIO


73

November 1962
a miniscule 40¢



"S" SERIES

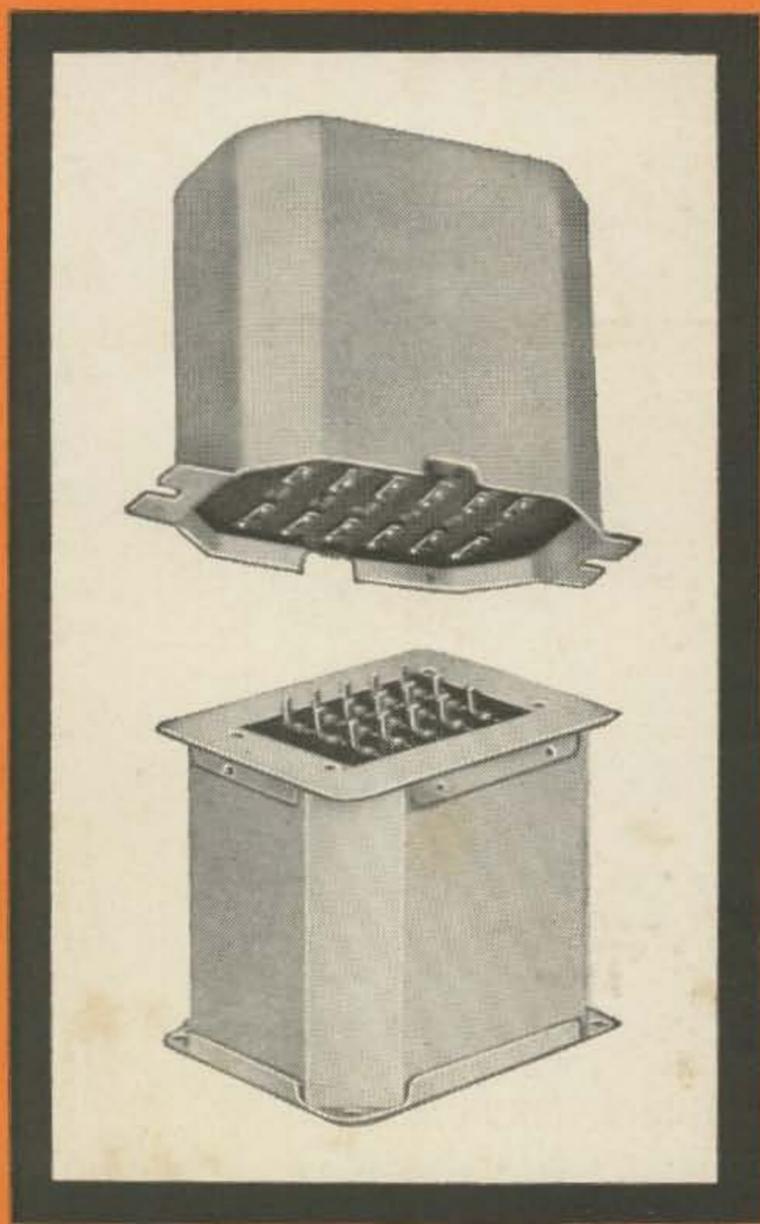AUDIO & POWER TRANSFORMERS & REACTORS For Complete Ham Systems



**Popular Priced
Matched Components
for
Power Supplies
Modulation
Pre-Amp &
Power Amplifiers
... for entire ham rigs**

Thirty years of attention to ham requirements have resulted in a complete line of reliable, high quality components geared especially to your needs. The "S" series of audio and power transformers and reactors, designed specifically for ham and PA service, are completely matched for compatibility in constructing a rig. These are popular priced units which afford the ham the full benefits of UTC's established excellence for quality components coupled with high reliability.

Write for catalog of over
1,000 STOCK ITEMS



UNITED TRANSFORMER CORP.

150 VARICK STREET, NEW YORK 13, N. Y.

PACIFIC MFG. DIVISION: 3630 EASTHAM DRIVE, CULVER CITY, CALIF.
EXPORT DIVISION: 13 EAST 40th STREET, NEW YORK 16, N. Y.

CABLES: "ARLAB"

Solid State 1296 mc Converter	W3HIX	6
Transistors on 1296? Good grief, what next? Sensitive too!		
Deluxe Your Transceiver	K6UGT	10
The Lafayette HE-35A, for example. S-meter, spotting switch, etc.		
Junction Checks	K2OPI	16
Quick way of making sure the junctions are still good on your transistors.		
The Continental Six	WIPYM	18
Six meters SSB with this low cost high performance transmitting converter.		
Build Your Own Mobile Mike	K5JKX	20
Transistorized mike preamplifier for more mobile punch.		
73 tests the Gonset 220 mc Communicator	W4API	24
Commercial equipment comes to the 220 mc band!		
In Defense of the Operator	W ϕ OBF/2	26
A weak defense is better than no defense at all.		
Catch All	Rodgers	28
Ha, ha.		
Of RTTY and Filters	W3TUZ	32
Book length feature.		
Premium Tube Replacement Guide	W4WKM	46
Equating all those four numbered tubes to better known tube numbers.		
73 tests the Lafayette Starflite	WIMEL	50
Inexpensive all-band rig. Eighty dollars, ninety watts.		
Complicating the Simplescope	W ϕ OPA	52
Modifications and improvements of the Sept. 1961 article.		
73 tests the Heath IM-30	W5SJN	58
Transistor analyzer kit for \$54.88 really does a good job.		
Simple Squelch	K4UWX	60
Squelching that communications receiver used with a VHF converter.		
Good Old Charlie Queen	WIQUE	64
Can this be fiction?		
Spotting Simplified	W4MLE	66
Getting those "spot" switches to really do the whole job.		
Coax vs Open Line	W9HOV	67
Coax doesn't fare so well, we'll warn you.		
Inverted Vee-Beam	W8DLU	70
Works out like a bandit. Replace guy wires with a very effective antenna.		
Choke Evaluator	Ives	72
Test equipment for the shack, not the car.		
Those Different Diodes	Staff	80
Big technical article. Rouser.		
A Good Five Cent QSO	W4MLE	90
George fights a losing battle with the lids.		
Letters	19, 76, 93	Push Pull 23
Quaker Xtal Kit	21	Mike Versatility 48
	Transceiving	65

73 Magazine is published monthly by 73, Inc., Peterborough, N. H. The phone number is 603-924-3873. Subscription rates are still abysmally low at \$3.50 for one year, \$6.50 for two years, and \$9.00 for three years in North American and U.S. possessions. Foreign subscriptions are \$4.00 per year. Second class postage is paid at Peterborough, New Hampshire and at additional mailing offices. Printed in the U.S.A. Entire contents copyright 1962 by 73, Inc. Postmaster: please send form 3579 to 73 Magazine, Peterborough, New Hampshire. Readers should stop reading the fine print and stick to the articles and editorial.

de W2NSD/1

On the Air Again

BETWEEN THE seven-day-a-week night and day job of getting 73 going and the restrictions of one of the nastiest landlords I've ever encountered, my hamming has been badly pruned back for several years. Even under the best of conditions it is difficult to make much of a mark while operating from Brooklyn. Antenna space is nil, the cement sops up all the rf, and you have more TVI per square inch than is believable.

This had a lot to do with our leaving the city. One of the important factors in our choice of a new home for 73 was the height and the clearness of the shot to the southwest for VHF operation.

Once moved into the new headquarters we set about getting a ham shack in operation. I'm not counting the Clegg 99'er and the halo hung out the attic window for local six meter contacts . . . this was installed and working before we had finished unloading the first truckload. The first installation was the Central 200V driving a Central 600L into a Hy-Gain tribander up on a forty foot Rohn tower. The receiver was a National 303. The results were marvelous! Every DX station I called came back and gave me encouraging reports. I hadn't been able to work out like that since my old ham station up in Troy, New York, at college where I racked up a rather good DX score and won several of the SS and DX contests.

Outside of some difficulty in getting the tribander to the top of the 40 footer, it was a snap getting a good signal onto the 10-15-20 meter bands. Dipoles hung from a couple of our 80' and 90' trees brought in nice reports on 40 and 80 meters. This left us with a lack on the VHF bands. This would never do. . . . I've been a staunch VHF'er ever since I started in ham radio (my first contact was on 2½ meters).

There is a big difference between getting on two meters with a Gonset and a halo and really putting a DX signal on the air. If you

are going to do a serious job on two you have to have a minimum of a 16 element beam, two or three hundred watts, and a low noise converter. That beam has to be up in the air a ways, too. I looked over my gear and decided to throw caution to the winds and put up the best we could manage.

The first step was to order sixty feet more of Rohn tower and get the antenna above the 90' trees. The tower came in a few days, complete with erecting tool and guys. Art, VE1EY, arrived at this time with XYL and three harmonics in tow. Art announced that he was a rigger and could swing the tower into place in a couple hours. "Nothing to it." They moved in with us and five days later the tower was in place. I don't think Virginia likes kids any more.

Then, the day before our Open House, Bob Cushman of Cushcraft came over in his TR3 and unloaded a formidable pile of aluminum. He spent the whole day converting this "pick-up-sticks" into a 64 element beam. What a monster! It filled the whole backyard. This left only the small matter of putting the beam up on the tower. Ho, ho.

We needed an expert.

We got one. Pat Harris, W1HIV, son of Sam and Helen Harris, W1FZJ and W1HOY (also W1BU), who tends their forest of one hundred-plus footers, drove up with his safety belt and spent two days on the top of the tower getting the 64 elements in place. I hate to think how long it would take someone who didn't know what he was doing to put up a tower and beam like that.

The results were not quite as great as I expected. I hooked my Tapetone 417A converter through the NC-303 and used the Gonset Communicator with the Gonset linear, running about 50 watts output and worked over a range of about 100 miles. Over the next few days the band opened a little now and then and I managed many contacts with New York and New Jersey and even two with Philadelphia. As the

LAFAYETTE RADIO

SMASHING VALUES!

TOP DESIGN!

MADE IN U.S.A.

STARFLITE™



KT-390

90 WATT
PHONE
and
CW

TRANSMITTER KIT

79⁵⁰

NO MONEY
DOWN

COMPARE QUALITY!
COMPARE PRICE!

- 90 Watts Phone or CW on 80 Thru 10 Meters
- Built-in 3-Section Low-Pass Filter
- Clear, Chirpless Grid Block Keying

Dollar for dollar you can't beat this new Lafayette Starflite transmitter. Easy to build and operate, it glistens with quality and performance all-over. Features in addition to those listed above: 5 crystal positions and provisions for external, VFO, illuminated edgewise panel meter and pin-net work output for proper antenna match. Buy one now — we know you'll be satisfied with it.



THE LAFAYETTE HE-30

Professional Quality Communications Receiver

- TUNES 550 KCS TO 30 MCS IN FOUR BANDS
- BUILT-IN Q-MULTIPLIER FOR CROWDED PHONE OPERATION
- CALIBRATED ELECTRICAL BANDSPREAD ON AMATEUR BANDS 80 THRU 10 METERS
- STABLE OSCILLATOR AND BFO FOR CLEAR CW AND SSB RECEPTION
- BUILT-IN EDGEWISE S-METER

Sensitivity is 1.0 microvolt for 10 db, Signal to Noise ratio. Selectivity is ± 0.8 KCS at -6 db with Q-MULTIPLIER. TUBES: 6BA6—RF Amp, 6BE6 Mixer, 6BE6 OSC., 6AV6 Q-Multiplier—BFO, 2-6BA6 IF Amp., 6AV6 Det-AF Amp. ANL, 6AQ5—Audio output, 5Y3 Rectifier.

99⁹⁵

NO MONEY
DOWN

NEW LAFAYETTE HE-50A DELUXE 6-METER TRANSCEIVER



MADE IN
U.S.A.

114.95

NO MONEY DOWN

- Highly Sensitive Superheterodyne Receiver Section for 28-29.7 Mc
- Effective Series Gate Noise Limiter
- 3-Stage, 12-Watt Transmitter with 2E26 Final
- Illuminated Panel Meter for Plate Current and "S" Readings
- Pi-Network Transmitter Output
- Built-in 117 VAC and 12 VDC Power Supplies
- Push-To-Talk Ceramic Microphone

Provides maximum convenience and flexibility in either mobile or fixed operation.

LAFAYETTE HE-45A 10-METER TRANSCEIVER

Similar to above except for 6 meter operation 114.95

TOP VALUE COMMUNICATION RECEIVER

KT-200
in Kit Form
64.50

HE-10
79.95
WIRED AND TESTED



- SUPERHET CIRCUIT UTILIZING 8 TUBES AND RECTIFIER TUBE
- BUILT-IN "S" METER WITH ADJUSTMENT CONTROL
- FULL COVERAGE 80-10 METERS
- COVERS 455KC TO 31 MC
- VARIABLE BFO AND RF GAIN CONTROLS
- SWITCHABLE AVC AND AUTOMATIC NOISE LIMITER

The Communications Receiver that meets every amateur need—available in easy-to-assemble kit form. Signal to noise ratio is 10 db at 3.5 MC with 1.25 microvolt signal. Selectivity is -60 db at 10 kc, image reflection is -40 db at 3 MC. Tubes: 3-6BD6, 2-6BE6, 2-6AV6, 1-6AR5, 1-5Y3.

LAFAYETTE RADIO ELECTRONICS



FREE!

CUT

OUT

PASTE ON CARD

SYOSSET	JAMAICA	NEW YORK	BRONX	NEWARK
PARAMUS	PLAINFIELD	SCARSDALE	NATICK	BOSTON

LAFAYETTE RADIO DEPT. 73K-2
P.O. BOX 10, Syosset, N.Y.

Send me the FREE
388 Page 1963 Catalog 630


Name

Address

City Zone State

FREE

1963 INTERNATIONAL CATALOG

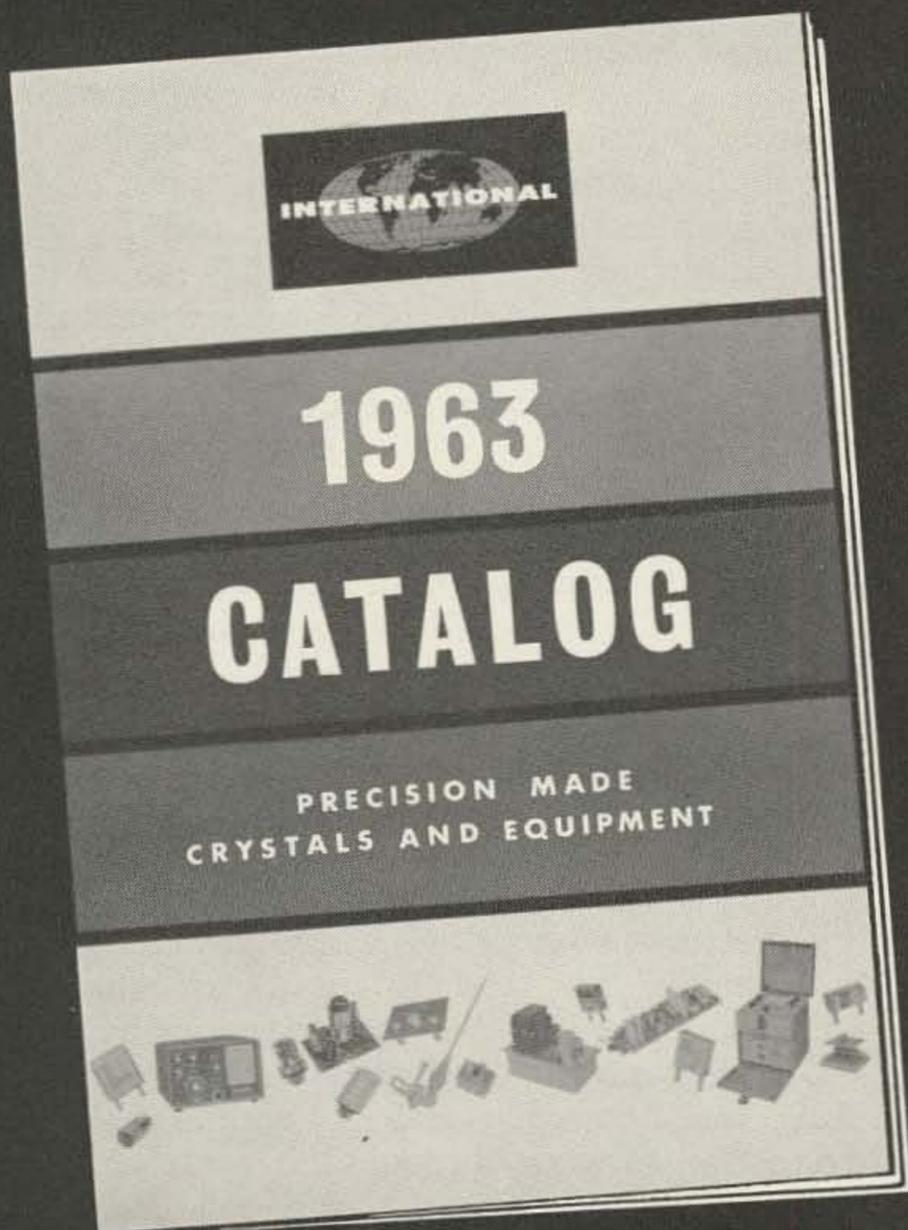

... your buying guide for precision radio crystals and quality electronic equipment ...

- Transmitters
- Amateur Crystals
- Citizens Band Crystals
- Citizens Band Transceivers
- Converters
- Transistor Subassemblies
- Converters
- Power Supplies
- Antennas
- Oscillators

AMATEURS • EXPERIMENTERS • CITIZENS LICENSEES

Mail coupon today for your FREE copy of International's 1963 catalog.



18 NORTH LEE • OKLAHOMA CITY, OKLAHOMA

International Crystal Mfg. Co., Inc.
18 North Lee, Oklahoma City, Okla.
Rush FREE 1963 Catalog.

73M

Name _____

Please Print

Address _____

City _____ Zone _____ State _____

1296 mc Converter


A CONVERTER IS described that operates at a signal frequency of 1296 mc utilizing semiconductors throughout. The converter is intended for ham communications on the 1296 mc band and could easily be adopted for moon bounce operation. An *if* frequency of 30 mc permits the use of any communications receiver capable of tuning this range.

Six transistors are used in functions previously performed by tubes. The use of transistors reduces the amount of heat generated both by the *if* stages and harmonic generators, thereby increasing frequency stability. A diode is used as a frequency tripler in the last stage of the frequency multiplier section. A low noise mixer diode is used in conjunction with a low noise *if* preamplifier (2.7 db) to provide extremely low noise operation. This converter has a measured overall noise figure of 8.5 db with a power gain of better than 50 db. The image response was at least 10 db down from the signal frequency.

Circuit Description

Fig. 1 shows the schematic diagram of the entire converter.

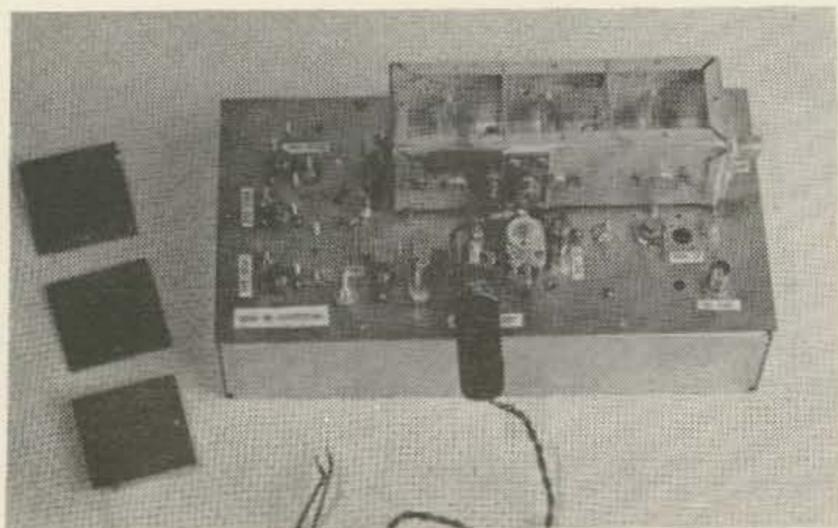Philco's 2N1742 MADT transistors are utilized in the oscillator and the three frequency doubler circuits. All are operating in the common-base configuration. A 1N147 type mixer diode is used as the diode frequency tripler. The 2N1744 MADT type which is specified for oscillator service was considered for the multiplier stages but was found to have lower power gains than the 2N1742 which



Top View of 1296 mc Converter.

due to its higher gains provided more drive to the diode tripler stage.

The 1266 mc heterodyning signal for the 1N263 diode mixer is generated by a 52.75 mc crystal controlled oscillator, three Class "C" frequency doublers and a diode frequency tripler.

In the oscillator output circuit, capacitor C_1 and coil L_1 are tuned to 52.75 mc. The 1.5 to 7.0 mmfd trimmer in the emitter circuit is adjusted for maximum output consistent with stable oscillator operation. With certain crystals it may be necessary to add about 1.0 mmfd of capacitance between the collector and emitter terminals. Winding L_2 couples the output from the oscillator to the input of the first doubler. Capacitor C_3 and coil L_3 tune the output of this stage to 105.5 mc. A tap on coil L_3 couples the 105.5 mc output to the emitter of the second doubler. Capacitor C_4 and coil L_4 tune the output of this stage to 211 mc.

A low impedance tap on coil L_4 couples the 211 mc output to the input of the third doubler. A strip line tank circuit consisting of capacitor C_5 and coil L_5 tune the output to 422 mc. A copper type shield serves as the enclosure for this tank circuit.


Driving of the 1N147 multiplier tripler diode to 1266 mc is through the variable matching capacitor C_6 tapped onto L_5 . Inductor L_{15} with the capacitance C_6 formed by the tuning screw SC_3 is tuned to 1266 mc.

Inductors L_{13} and L_{15} and capacitors C_A and C_B formed by the tuning screws SC_1 and SC_2 respectively, are preselectors tuned to 1296 mc. Loops L_{11} and L_{12} couple the signal from the antenna through the preselectors to the 1N263 diode mixer.

The 30 mc output of the mixer is amplified in two common-emitter *if* stages. Coupling to the T2364 first *if* amplifier is through a network consisting of coil L_6 and capacitors C_7 , C_8 and C_{13} . C_8 and L_6 are adjusted for the lowest noise figure. The *if* system noise figure was measured to be 2.7 db. A T2028 can be used in this stage with a slight deterioration in the noise figure. Capacitor C_{10} and coil L_7 are tuned to 30 mc. Inductive neutralization is provided by the tapped output coil L_7 and capacitor C_9 .

Secondary winding L_8 provides the coupling to the 2N1742 second *if* amplifier. Capacitor C_{12} and coil L_9 are tuned to 30 mc. Inductive neutralization is obtained by the tapped output coil L_9 and capacitor C_{11} . The converter output is coupled to the input of the receiver through secondary winding L_{10} .

Application of forward bias to the 1N263

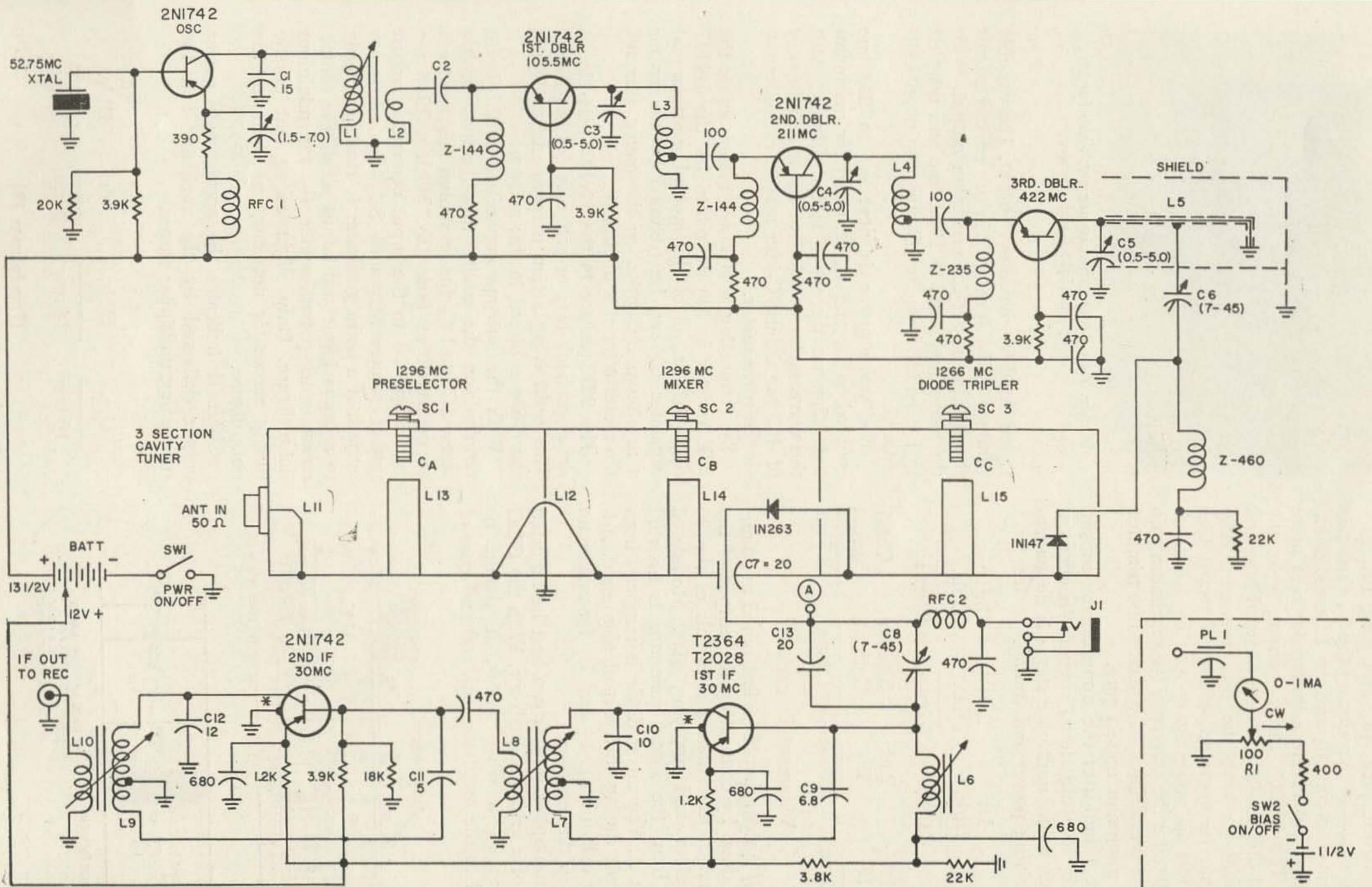

* CASE GROUNDED
 ALL CAP VALUES IN mmf.

FORWARD BIAS CIRCUIT
 FOR IN263 MIXER

FIG. 1

diode mixer gives about a 3 db improvement in noise figure. Jack, JK₁ and plug, PL₁ provide the means of introducing the forward bias in the mixer circuit. R₁ and the 1266 mc diode tripler tank circuit are adjusted for best noise figure. The 1N263 mixer current is in the range of 300 to 400 μ a with forward bias and about 200 μ a with the bias removed. The mixer can be operated without forward bias if the loss in noise figure can be tolerated. After aligning the converter for maximum gain the input preselectors may need to be trimmed for the minimum noise figure.

Chart I indicates the approximate current drawn by the individual stages. The current that flows in the multiplier stages is dependent upon driving power and tuning.

Osc.	1st Dblr.	2nd Dblr.	3rd Dblr.
5.0 ma	3.0 ma	5.0 ma	2.0 ma
1st IF	2nd IF	Bleeder Current	Total Current
0.6 ma	1.7 ma	1.2 ma	18.5 ma

Alignment Procedure

The *if* system should be first tuned to 30 mc. This is done by connecting the output of the *if* section to the antenna terminals of the 30 mc receiver and applying bias. Modulated output from the signal generator is inserted at point A. The mixer diode is removed from the circuit during this part of alignment. Adjust the coils of L₆, L₇ and L₉ for maximum output on the receiver.

The multiplier section can best be adjusted by use of a grid dip oscillator. With the GDO operating as a wave meter, it should be coupled to the oscillator tank coil and core of

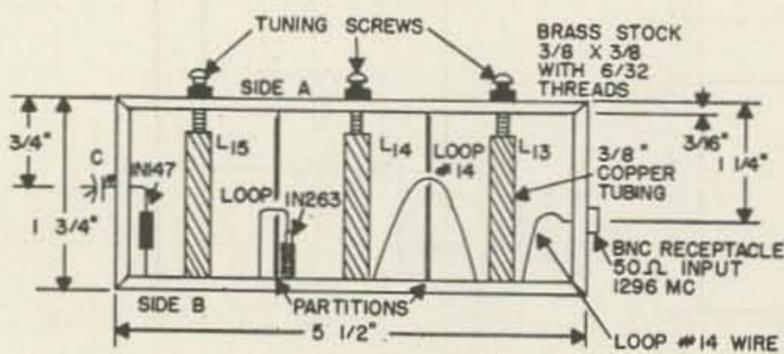


FIG 2


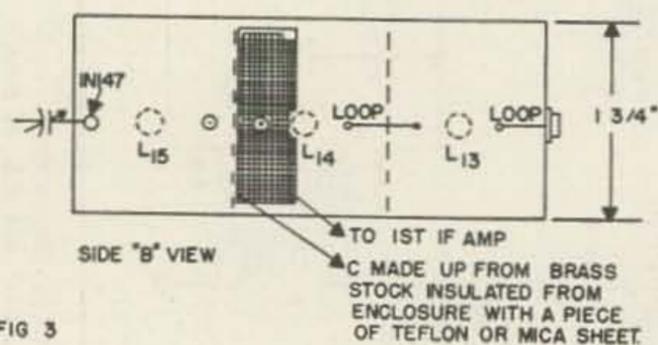


FIG 3

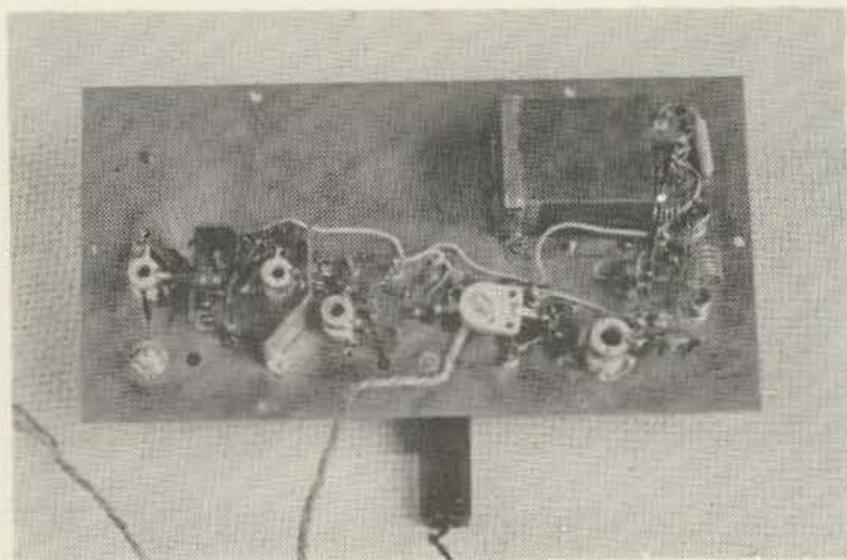

Bottom View—Note the copper enclosure for L₅ in upper right hand corner.

L₁ adjusted for maximum output. The variable trimmer (1.5-7.0 mmfd) in the emitter circuit should also be set for maximum output. With the wave meter set to 105.5 mc and coupled to L₃, adjust capacitor C₃ for maximum indication.

The wave meter is next set to 211 mc coupled to L₄ and C₄ adjusted for maximum indication on the wave meter. Finally, with the wave meter coupled to L₅ at a frequency of 422 mc, adjust C₅ for maximum indication on the wave meter.

By connecting a 0-5 ma meter across the 22K resistor in the dc return for the 1N147 diode tripler, all of the multiplier stages and capacitor C₆ can be trimmed by tuning for a maximum indication on the meter. Remove the meter after this alignment.

The 22K resistor in the 1N147 bias circuit develops back bias or self bias for the diode. The multiplying action is more efficient when the diode is biased in this manner.

With the antenna connected to the input terminal on the cavity tuner, adjust tuning screw SC₃ and C₆ for maximum mixer current as measured at Jack JK₁. With a 1296 mc signal applied to the input connector, adjust tuning screws SC₁ and SC₂ for maximum output. If a noise generator is available, apply to antenna input and adjust all of the tuning screws and potentiometer R₁ for minimum noise figure. Only slight adjustment of the tuning screws is necessary to optimize the noise figure.

Chart II indicates the approximate power output delivered by the oscillator and the succeeding multiplier stages.

Osc.	1st Dblr.	2nd Dblr.	3rd Dblr.
10 mw	14 mw	9 mw	6 mw

(Turn to page 79)

SSB ^{ON} 2 ^{OR} 6 ?

Telco "SB" Line
DEPENDABLE • RELIABLE



Telcos New "SB" Series in Action

ALL "SB" SERIES
 ARE HOUSED
 IN SAME
 CABINET

HEAR YE..... SYSTEM
 DESIGNED...
 FOR YOUR
 SYSTEM

All those interested in SSB

TELCO ANNOUNCES THE Following . . .

**SB
50**

6 meter heterodyne converter allows your 20 meter transmitter to operate on 6. Only 5 watts 14mc drive needed. Input is 90w AM or CW, and 125w P.E.P. SSB on 50mcs. Input & output 50 ohms. **\$85.00**

**SB
50
C**

A must for S-LINE owners. Puts your S-line on 6 meters with nothing else to buy. Complete Plug-In operation. Makes use of converter output and power supply of S-line. Delivers 175w P.E.P. on 6 meters, using 2-6146's. Built in with 201 converter for optimum reception, and allows use of transceive feature. Complete with all interconnecting cables. **\$239.00**

**SB
2-C**

A must for S-LINE owners. Same as SB-50-C, but for 2-meters. **\$289.00**

**SB-80
M1**

Same as the SB-40-M1, but converts the KWM-1 to 80 meters. **\$175.00**

**SB-80
40-M1**

For the KWM-1. Allows 80 and 40 Bandswitch Operation (next month).

**SB
TWO**

Similar to the SB-50 XMTG Converter, but for 2 meters. **\$139.50**

**MODEL
SIX**

Complete 6 meter single sideband (USB & LSB), AM, and CW transmitter. 175 watts P.E.P. (2-6146 finals) filter sideband generation, complete with built-in VXO, wait till you see the low price (next month).

**SB
40
M1**

Converts your KWM-1 to 40 meter transceive operation. Obtains power from the KWM-1 power supply and provides a clean 175 P.E.P. punch. Outstanding TELco 40 Meter Converter assures excellent reception on 40. Completely ready to go mobile or fixed, with all cables. **\$175.00**



ALL MODELS ARE AVAILABLE NOW

SEE THE SB SERIES AT YOUR DISTRIBUTOR, OR
 ORDER DIRECT

Ask about the Time Payment Plan.

Write to:

Howie Ryder—WI-WGH
Amateur Sales Manager



TAPETONE ELECTRONICS LABORATORIES INC.

99 Elm St., West Newton 65, Mass.

Tel. (617) 332-1123

Deluxe your Transceiver

Fred Blechman K6UGT
23958 Archwood Street
Canoga Park, California

IF you would like to add some "deluxe" features to your inexpensive transceiver, this article will show you how to add: an illuminated meter for tuning both the receiver and transmitter; a tuning control for the transmitter; a "spotting" switch; an earphone jack that can also be used for tape recording and modulation monitoring. "Bandspreading" the tuning range of the receiver will also be covered.

The Lafayette HE-35A Six Meter Transceiver has been chosen as the example for several reasons. It is a "natural" for modifications, since half the front panel is not occupied. It is a "typical" unit, having a superheterodyne receiver, variable noise limiter and 7-watt transmitter neatly packaged in a steel case 10 $\frac{1}{2}$ x 5 x 6 $\frac{1}{4}$, with a built-in speaker and 117 vac power supply. Made in the U.S.A., the HE-35A comes completely wired, with a ceramic hand microphone and a third-overtone 50.2 megacycle crystal, for \$57.50 (Lafayette Radio, 111 Jericho Turnpike, Syosset, L.I., New York Catalog #HE-35AWX).



G-16—The front panel of the "Deluxe" HE-35A. The small switch under the meter turns on two small bulbs included in the meter case. Note the added "pointer" on the receiver tuning dial.

Two other nationally available transceivers are virtually identical to the HE-35A: The Lincoln 6 Meter Transceiver (Allied Radio, 100 N. Western Ave., Chicago, Illinois. Catalog #78SZ195, \$57.50) and the DeWald 6 Meter Transceiver, Model TR-850 (Burstein-Applebee Company, 1012 McGee St., Kansas City 6, Missouri Catalog #35A468, \$69.95). Ready-wired power supplies are available for 6 or 12 volt mobile use that plug into the cigarette lighter for connection to the battery, and plug onto the back of the transceiver.

The modifications described are relatively simple, and enough explanation is given to allow their application to similar Amateur and Citizens-Band equipment.

Adding A Meter

Perhaps the most desirable change to any piece of communications equipment, not already having a tuning device, is the addition of a meter. Normally, this is a relatively expensive device, and consumes a lot of panel space. However, with the availability of the Lafayette TM-11 Illuminated "S" Meter, the expense and space problem has been overcome. Only 1 $\frac{1}{2}$ inch square, with a sensitivity of 1 milliamperes full-scale, jeweled bearings, plastic front, 3-color dial face with 3 sets of scales, and two built-in grain-of-wheat bulbs for 6 or 12 volt illumination, this meter sells for only \$2.95! It is added to the HE-35A front panel as shown in Photo G-16. A single-pole-single-throw (SPST) slide switch (S2) is placed directly below the meter to control the built-in bulbs. A double-pole-double-throw (DPDT) toggle switch (S1) is used to select meter function, and it is placed alongside the meter.

The meter serves three useful purposes when wired as shown in Fig. 1. With the meter selector switch (SI) in the "S-Meter" position, the relative strength of incoming signals is shown, and the receiver can be tuned to the "center" of the received carrier; also, when used with the "spot" switch described further on, it gives definite indication of transmitting crystal activity and frequency on the receiver dial. In the "RF Output" position of

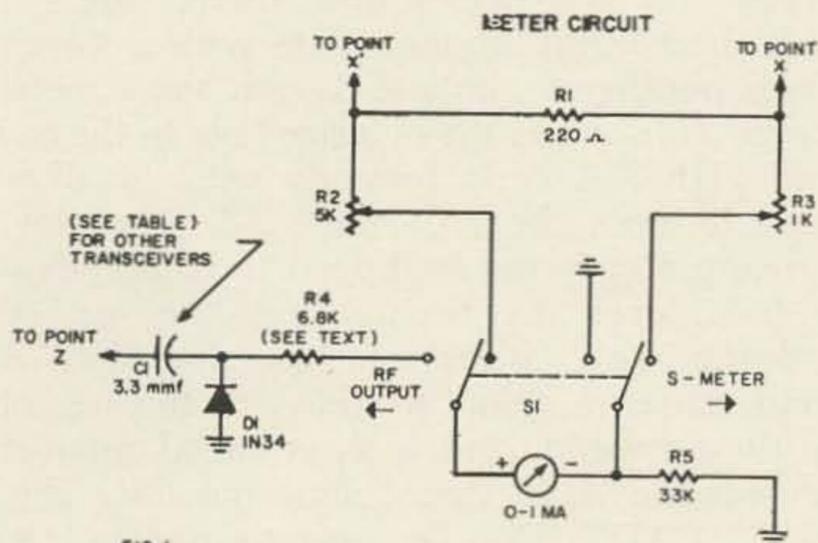


FIG. 1

SI, the transmitter final tuning capacitor may be adjusted for maximum output on the meter.

To add the meter circuit break the connection at "X." This can be located by following the normally-connected lead of the transmit receive switch. This lead goes to a terminal strip under the chassis. Locate the 10K resistor (brown, black, orange) that goes to pin 3 of V2 (via the *if* can), and disconnect this resistor from the terminal strip. Connect this free end of the resistor to an unused lug of the terminal strip. Now wire in the circuit in Fig. 1.

An explanation of the circuit allows its use in almost any transceiver. When SI is in the "S-Meter" position, fixed resistors R1 and R5, and variable resistor R3, form three legs of


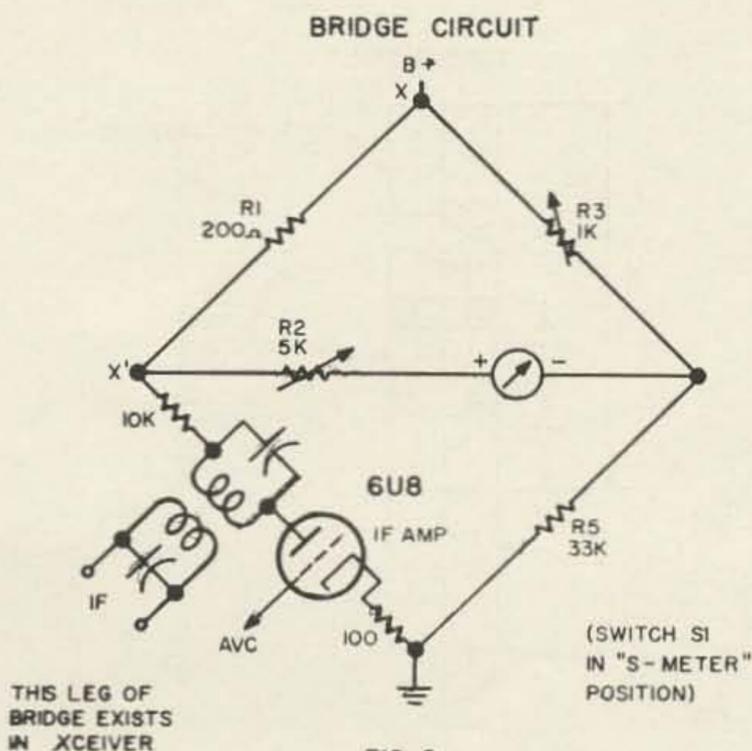


FIG. 2

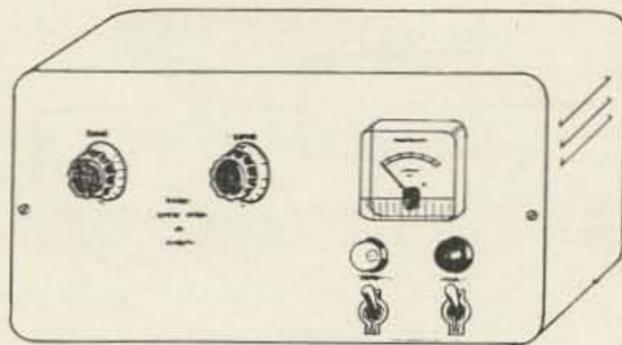

Our New Model 1062 for 6 & 2 Meters

This new model will give up to 500 watts AM & CW linear, up to 1000 watts pep on 6 & 2 with a 7034 final. 60 C.F.P.M. blower. Requires approximately 5 watts drive on 6 & 2. Voltage required—plate 800 to 2000 at 250 ma, screen 300 volts, bias—50 volts.

Price—\$199.95 less power supply.

Power supply \$119.95

Both only \$319.90

J&D LABS 73, Hwy. 35
Eatontown, N. J.
(201) 542-0840

G·A·M HIGH GAIN ANTENNAS CONTROLLED RADIATION

Pattern is beamed toward the horizon for optimum response.

Mounting Structure Does Not Affect Radiation Pattern

"TEAM-MATES"

TG-5-S (144-170 mc) TG-2-R

\$74.25 Net
3 ELEMENTS
Fixed Station
3X Power of
TG-2-R

\$18.00 Net
Half Wave
Element
Maximum
Possible Gain

Although independent use of the TG-5-S and TG-2-R give amazing performance, their combined use as "Team-Mates" produce the ultimate in gain and efficiency. The engineered compatible characteristics of pure vertical polarization and matched feed points, with the elimination of horizontal polarization, make the "Team-Mates" leaders in the field of communication. Gain Figures, Radiation Patterns and Catalogs Listing All Models are Available

SEE YOUR DISTRIBUTOR OR WRITE GAM DIRECT

G·A·M Electronics inc.

138 Lincoln St., Manchester, N. H.

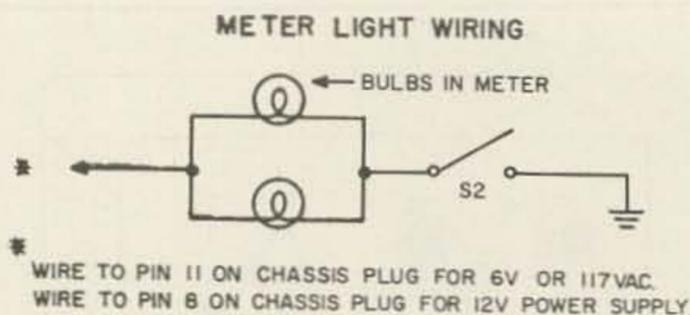


FIG. 3

a Wheatstone Bridge circuit, with the transceiver *if* amplifier circuitry as the fourth leg. See simplified schematic, Fig. 2. The meter is used as a voltmeter across the bridge output, with R2 used to limit meter current. The bridge is powered at point X, and is balanced in a no-signal condition by adjusting R3 for a zero meter reading (about 400 ohms). When a signal is received, the receiver AVC action changes the impedance of the *if* amplifier leg of the bridge, thus throwing the bridge out of balance, and creating a voltage across the series combination of R2 and the meter. R2 is adjusted for a full scale reading (about 1300 ohms) on the strongest local signal. Do not be alarmed if the meter "pins" when the transceiver is turned on; the bridge is severely unbalanced for a few seconds until the *if* tube warms up.

The meter lights should be connected as shown in Fig. 3. If to be used on 6 volts or 117 VAC, connect to chassis plug pin 11. For 12 volts use only, connect to pin 8. Switch S2 is in the circuit to allow the meter illumination to be shut off when not needed, since the bulbs have a limited life (about 50 hours on 12 volts).

When S1 is in the "RF Output" position, radio frequency energy from the antenna connection is coupled thru C1 and rectified by D1, with the resultant dc voltage fed to the meter through R4. The reactance of C1 should be approximately 1000 ohms at the operating frequency, so the rf power drawn by the meter is negligible compared to the much lower antenna impedance of around 50 ohms. Suggested values of C1 for various frequencies are shown in Table I. The value of R4 should be selected to provide near-full-scale reading when the transmitter is tuned to maximum output into the antenna to be used. The meter reading is only to indicate relative output on a given antenna, and will give different maximum readings with different antennae; it is essentially an rf voltmeter, and therefore reads the standing wave voltage on the antenna line at the point to which it is connected.

When changing crystals in the HE-35A, it is usually only necessary to adjust the variable

slug-tuned capacitor (C-1) for maximum output on the meter. Slug L-4 and capacitor C-4 can be adjusted to cover a broad range of crystal frequencies, and very little is gained by retuning them each time the crystal is changed. As shown in Fig. 4, a tuning wand to adjust C-1 may be made from 1/4 inch diameter polystyrene tubing. A thin metal sliver, or a piece of fine music wire, is heated and inserted through the side of the tubing to form a "key" for the slot in the tuning slug. A small sheet-metal adapter plate with a 1/4-inch hole is positioned above C-1 with sheet metal screws. This covers the oversize hole in the top of the HE-35A case, formerly used to allow access to tuning both C-1 and C-4. The polystyrene tuning wand is slipped thru the adapter hole, over the tuning slug, and turned until the "key" drops into the slug slot. A round set-screw knob is added to the top of the tuning wand, and a sheet metal retainer prevents the wand from falling out. See Figure 5. CAUTION: Be sure to remove the wand before attempting to remove the HE-35A from its case.

Spotting Switch

The addition of a "spotting switch" to a transceiver allows the operator to locate his own transmitting frequency on the receiver dial. This is useful for receiver calibration purposes and to judge the frequency of an incoming signal. If your transmitter has a variable-frequency oscillator (VFO), a spotting switch allows you to "zero-beat" (match the frequency) of an incoming signal. The addition of a spotting switch is usually a simple wiring job, and the HE-35A is a good example as shown in Figure 6. Break the connection between pins 1 and 6 of the oscillator-amplifier tube (6CX8 V4) and add a SPDT pushbutton


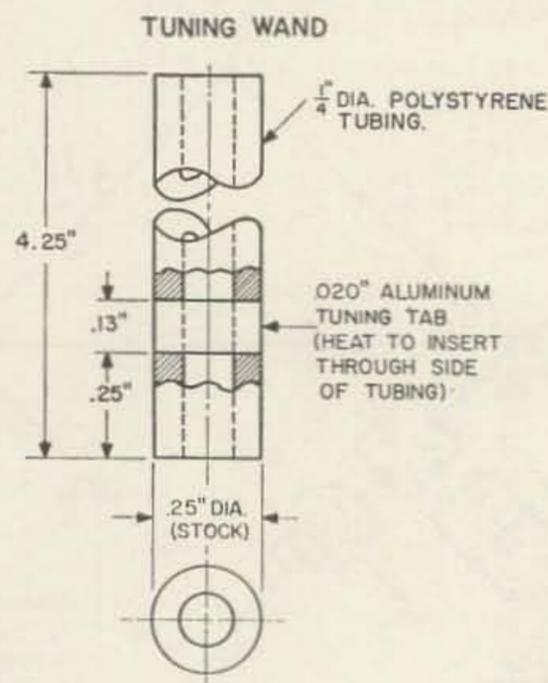


FIG. 4,

T.M.

Here's the rig you've been waiting for — Clegg's new THOR VI Transceiver for 6 Meters.

Astonishing performance... Priced right!

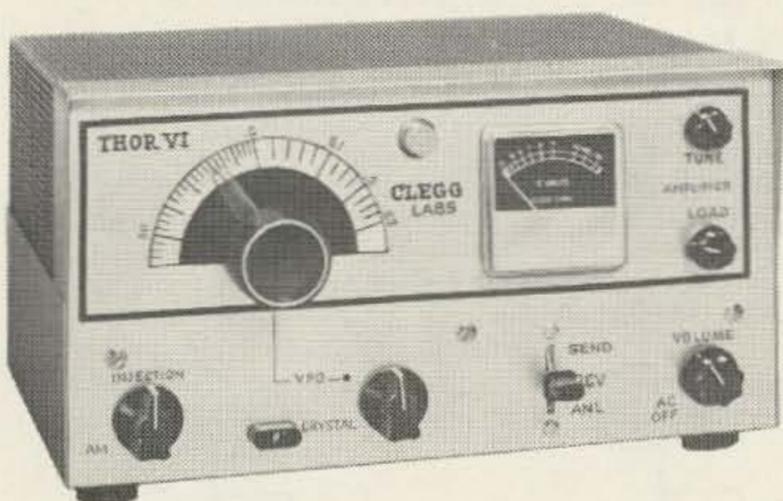

Fixed station or mobile, this little power package reflects all the advanced engineering and design features that have made CLEGG the "most wanted" gear in the VHF field.

Talk about performance . . . listen to this: **Fifty solid watts** on both AM and CW; high level modulation with full speech clipping to give you famous CLEGG "Talk Power"; true transceiver operation with tuneable oscillator in the receiver serving as the VFO in the transmitter; provision for keying the transmitter.

A low noise double conversion super-heterodyne receiver complete with BFO and ANL provides maximum selectivity and sensitivity with stability equal to the exacting requirements of SSB and CW; separate power supply/modulator for 115V AC operation. A fully transistorized power supply/modulator for 12V DC available soon.

And best of all, this rig is priced at a level that every ham can afford. Place your order with your distributor today. Deliveries start late in November.

And here's one for you VHF sidebanders!

It's the new CLEGG VENUS six meter transceiver for SSB, AM or CW! Once you've used or heard this rig you'll appreciate the engineering and design "Know-how" that made it possible.

Here's what you can expect: A superbly engineered crystal lattice filter; SSB transmitter of greater than 120 watts PEP input; amazing frequency stability, VFO controlled by the receiver's tuneable oscillator; full power input on CW and a substantial signal on AM phone. There is also output provision to drive a KW linear final.

In the receiver section a double conversion, low noise super-het of extreme sensitivity and selectivity, with crystal lattice filter and product detector provides flawless reception of sideband, AM phone or CW. A 115V AC power supply of adequate capacity is a separately mounted unit which can be installed at any convenient distance from the transmitter.

This rig, too, is priced within reach of every ham. Watch for it at your distributors late in January. Place your order now to be sure of early delivery.



And here's a winner and STILL champion in it's class! The famous Clegg 99'er, six meter transceiver favorite of thousands of VHF hams is small in size, low in price and tops in performance.

The 99'er offers operating features unequalled in far more costly gear. The double conversion super-het receiver provides extreme selectivity, sensitivity and freedom from images and cross modulation. The transmitter section employs an ultra-stable crystal oscillator which may also be controlled by an external VFO. An efficient high level modulated 8 watt final works into a flexible PI network tank circuit. A large S meter also serves for transmitter tune-up procedure.

Clegg LABORATORIES

504 ROUTE 53, MT. TABOR, NEW JERSEY
OAKWOOD 7-6800



"THE "SIX" XMTR CONVERTER ONLY \$99⁹⁵
. WORKS LIKE A CHARM!"
 In North Dakota, South Dakota, See It At The John Iverson
 Company, Minot, North Dakota
Continental Electronics, P. O. Box 16, Sumter, S. C.

whistling are evident in this mode of operation, increase the value of R6.

Bandspread

Most 6 meter and Citizens-Band receivers cover the entire band, but it may be desired to tune only part of the band. This allows less critical tuning, making it somewhat easier to separate adjacent stations, and to tune quickly without missing a station. On 6 meters only the first two megacycles of the 50-54 megacycle band are active, so the HE-35A was modified to tune only to 50-52 megacycles. This was accomplished by merely changing the 15 mmfd capacitor in series with the tuning capacitor to a 6.8 mmfd NPO (zero drift) unit. Various other values may be tried to "spread" the tuning range the desired amount. The smaller the value of the substitute capacitor, the smaller the portion of the band covered. It will be necessary in each case to reset the receiver oscillator slug (L-3) to bring the desired portion of the band in the tuning range of the receiver.

If your tuning arrangement is not like the HE-35A, bandspread may not be a simple matter. The better superheterodyne receivers have dual-ganged tuning capacitors for im-

proved selectivity and image rejection. The HE-35A has a broad-band RF amplifier, and only the oscillator is tuned by the front panel control for station selection. In most super-regenerative receivers, however, the tuning arrangement is similar to the HE-35A and the series capacitor, as shown here, will provide

SPEAKER SELECTOR


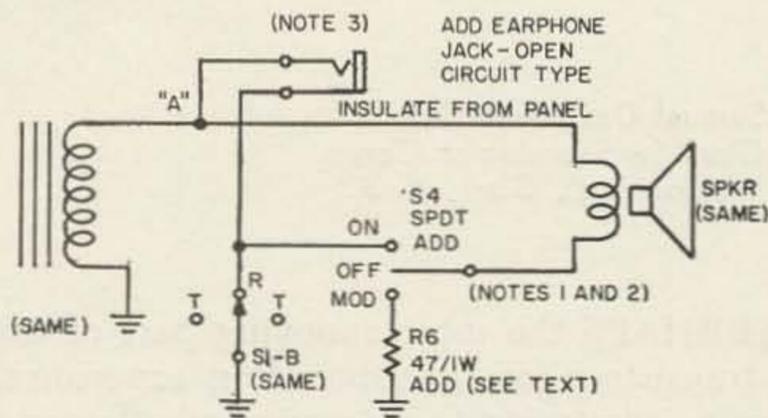


FIG. 7

NOTES:

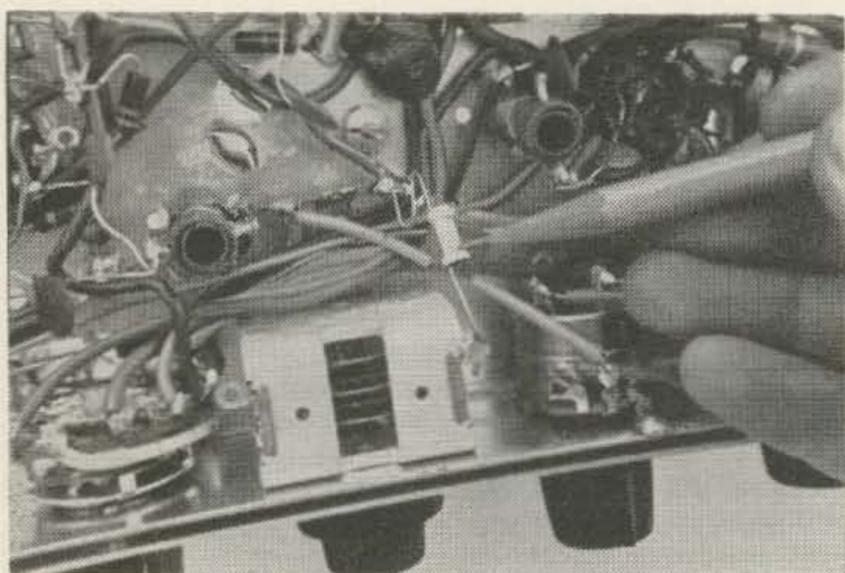1. Switch should be SPDT center off.
2. Position 1: Speaker on
Position 2: Speaker off
Position 3: Modulation monitor (when transmitting or testing mike)
3. This jack may be used for input to tape recorder. Switch allows monitoring while recording.
4. Earphones: 6-2000 ohms.



H-17—Under the HE-35A chassis. Changing the capacitor indicated (the new one is shown) will "bandsread" the receiver.

bandsread.

Reading the receiver dial of the HE-35A is somewhat of a guess, since the indicator dot on the tuning knob is far from the numbers on the panel, and parallax is extreme. This can be corrected by simply gluing a thin triangular-shaped piece of plastic or celluloid to the bottom of the main tuning knob after scratching a line in the plastic and filling it with white ink to act as a "pointer."

There are many other potential changes to a versatile rig like the HE-35A. Conversion of the oscillator to use cheaper 8 MC. crystals in place of the presently used third overtone crys-

tals, could be done by adding another tube. However, this is not such a simple change, and the harmonics generated could lead to television interference problems. Front-panel tuning of the transmitter output would be nice, but hardly worth all the trouble. Addition of a beat frequency oscillator (BFO) to receive CW code would be useful to only a limited number of operators; transmitting CW would require the addition of a keying jack, and "chirp" would be a problem.

The HE-35A and similar units will look better and be more efficient and convenient to operate if the changes described are incorporated. The effort and cost are small; the result: a deluxe transceiver!

... K6UGT

PARTS LIST

- R1—220 ohm 1/2 watt composition resistor.
- R2—5000 ohm variable resistor (Lafayette VC-58 29¢)
- R3—1000 ohm variable resistor (Lafayette VC-57 29¢)
- R4—6.8 K 1/2 watt composition resistor (see text)
- R5—33k 1/2 watt composition resistor
- R6—47 ohm 1 watt composition resistor (see text)
- S1—DPDT toggle switch (Lafayette SW-22 32¢)
- S2—SPST slide switch (Lafayette SW-14 9¢)
- S3—SPDT pushbutton switch (Lafayette MS-449 19¢)
- S4—SPDT center off toggle switch (Lafayette SW-27 39¢)
- C1—See Table I
- C—bandsread—6.8 uufd. NPO (Allied Radio 19L960 29¢) (see text)
- M1—0-1 ma. meter (Lafayette TM-11 \$2.95)
- J1—Open circuit phone jack (Lafayette MS-441 19¢)
- Insulating washers for J1: Lafayette P-204 35¢/box of 20
- 1/4 diameter polystyrene tubing (Lafayette P-470 10¢)

Junction Checks

Quick and Dirty


Samuel Daskam K2OPI
Clark Semiconductor Corp.
Walnut Ave., Clark, N. J.

PERHAPS the most annoying part of using transistors for breadboarding experimental circuits is in trying to determine whether or not the junctions are still good after the initial use. There are many types of transistors and rectifiers on the surplus market, some of which have to be bought "as is." Without some kind of measuring instrument to check the collector-to-base and emitter-to-base junctions, it is very difficult to utilize these devices.

A method is described here which utilizes a resistance-capacitance comparator bridge. This instrument is widely used by many experi-

menters and a new application of existing equipment is always welcome. Although an Eico Model 950B Bridge was used to investigate this application, other makes should work equally well.

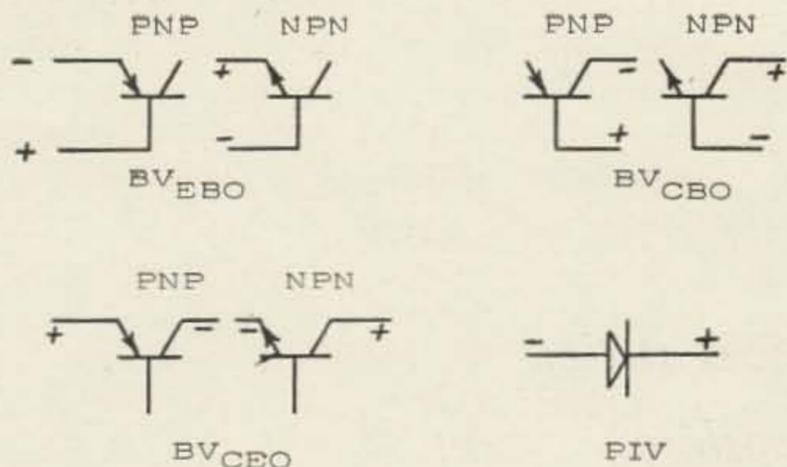The "electrolytic test" position of the bridge is normally used for checking the leakage of electrolytic capacitors as a function of the voltage across the capacitor. As the voltage applied across the electrolytic is increased by turning the front panel control on the bridge, the relative leakage is indicated by the closing of the tuning eye.



Since a semiconductor rectifying junction acts in a manner similar to an electrolytic capacitor in a test such as this, it was only a matter of making a few experiments to determine if the RC Bridge could be used for checking transistors and rectifiers. Fig. 1 gives the hook-ups needed to measure the various breakdown voltages such as BV_{EBO} , BV_{CBO} , BV_{CEO} , and the peak inverse voltage of rectifiers.

The procedure is simply to connect the transistor or rectifier leads to the correct terminals of the bridge so that the applied voltage reverse biases the junction. The easiest way to make the connection is to use alligator clip leads. A voltmeter should also be connected across the terminals since loading down the bridge will cause inaccuracies in the voltage dial calibration. Next increase the voltage control and watch the magic eye tuning indicator. When the eye starts to close, the voltage is approaching the breakdown voltage of the junction. No harm will come to most transistors and rectifiers if the breakdown voltage is exceeded during this test, since only 4 or 5 milliamps are required to close the eye. The voltmeter reading will usually only go as far as the breakdown voltage of the junction under test regardless of the voltage setting. This is because loading the power supply in the bridge causes the voltage to be dropped internally. . . . K2OPI

AN INTRODUCTION TO AND PROGRESS ON THE BASIC NATURE OF

COILS

Written by Russ Summerville K8BYN
50¢


Published by P & H Electronics, Inc.
424 Columbia, Lafayette, Ind.

This little twelve page booklet will be an interesting addition to your library. It will not only give you quite a rounded body of information about all sorts of coils, but is a fine thing to whip out and show someone who is interested in learning about radio. Marvelously written by Russ Summerville K8BYN, it is also well illustrated. It covers all types of coils and discusses their resistance, inductance, reactance, Q, and distributed capacitance. only 50¢

LOW ANGLE	HIGH GAIN	<i>the</i> HOTTEST on 6!
<p>The Eeco "446"</p>		P. O. Box 23 Stoneham 80 Mass.
		P. O. Box 895 Los Amigos Sta. Downey, Calif.
<p>Eeco Antennas</p>		\$19.95

NEW! from P & H

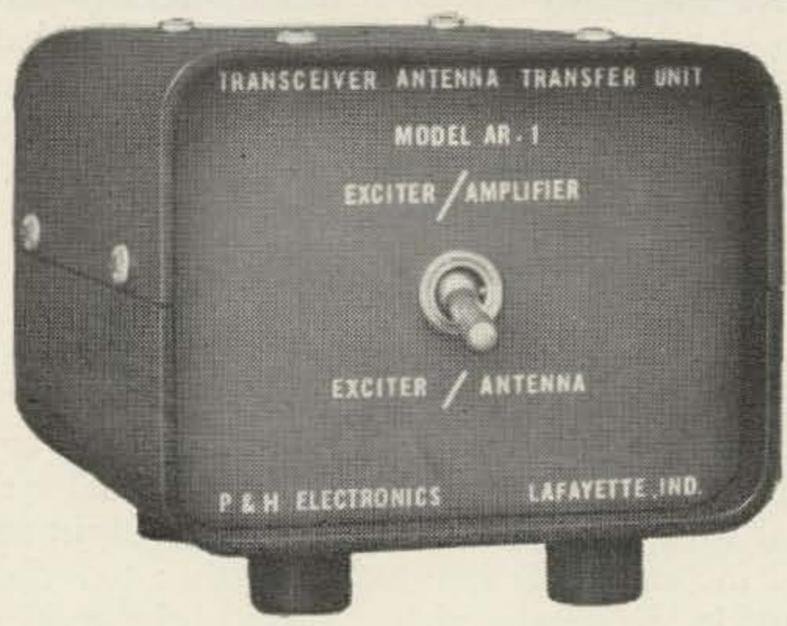MODEL AR-1 TRANSCIVER ANTENNA TRANSFER UNIT



Here is the answer to the problem of using your transceiver as an exciter for any linear amplifier. The AR-1 transfers the antenna to the transceiver while receiving and provides the necessary switching to connect the exciter to the amplifier, and the amplifier to the antenna when transmitting. A front panel switch also permits the exciter to operate straight through to the antenna. The relay is shock-mounted and the case is insulated to reduce noise. Standard SO239 connectors are provided for low impedance coax lines.

LOW INSERTION LOSS: Transceiver output to amplifier input, less than 1.02:1 SWR, 3 to 30 Mc. Amplifier output to antenna, less than 1.12:1 SWR, 3 to 30 Mc. The AR-1 requires 6.3VAC (6.3V jack on KWM-2) and normally open auxiliary contacts on the exciter relay. (ANT. RELAY jack on KWM-2). The AR-1 may also be used as a conventional antenna change-over relay. Size 3" X 4" X 4".

PRICE..... **\$32⁵⁰**

P & H ELECTRONICS INC.
424 Columbia Lafayette, Ind.

The Continental Six

first six meter SSB station

in New Hampshire

Paul Day WIPYM

Strange things are happening on six. In almost any part of the country nowadays, Donald Duck type noises can be heard on the low end of the 'phone band. The success of SSB on the lower bands has inspired not a few VHF men and several manufacturers to think about what it might do for six. With low band SSB exciters in common use, the logical approach seems to be a simple heterodyne converter. Several of these have appeared on the market and one of the neatest is the Continental "Six" designed by K4RLX.

Circuit Description

The Continental "Six" uses a 6U8 as a triode crystal oscillator/pentode buffer amplifier combination to provide a 36 mc local oscillator signal to the grid of a 5763 mixer. Output of a 14 mc exciter is injected through a tuned circuit in the screen of the mixer and the 50 mc sum frequency is selected by the 5763 plate circuit. A 2E26 operates as a straight through final amplifier on 50 mc. The final screen voltage is regulated by two OB2 miniature VR tubes. A 1N34 crystal diode coupled to the pi-section output tank provides relative output power indication on the front panel meter.

Controls and Adjustments

The front panel of the Continental "Six" consists of only two tuning adjustments, two switches, two indicator lamps and the meter. Nothing else is necessary and even these few controls may be left alone after initial adjustment. The 36 mc oscillator and amplifier tuning and the 5763 plate tank are slug tuned coils preset at the factory and normally need not be touched. These are located on the chassis and easily accessible with the case removed. The 2E26 plate tank is the familiar pi-section coup-

ler. Its tuning and loading capacitors are the two controls on the front panel. One setting on these controls is normally all that is required for SSB operation, but they may need readjustment for frequency changes of 250 kc or more away from the original operating frequency. One of the switches on the front panel switches the 2E26 plate voltage off and on. The other selects either 2E26 plate current or relative power output to be read by the meter. A sensitivity adjustment for the power output position is provided inside the cabinet.

Trying it Out

So much for the internal workings. Now let's make it work and see what happens. Making it go is so easy it's hardly worth writing about. Simply plug in the power supply and the drive, connect your 6 meter antenna relay and away we go. A word of caution. The converter only needs 5 watts maximum of 20 meter drive. Most popular exciters provide much more than this and must be padded down. Continental has 3, 6, and 9 db pads available or roll your own, but don't put more than 5 watts in the input pipe. Full instructions for tuning up are provided in the instruction book. Once I had the sample unit tuned up, I never had to touch the controls again. In fact my exciter (a 32S1) required more retuning than the converter.

Results

After the initial tuning up and playing around to get the feel of operation, the first single sideband station on six in New Hampshire was put on the air. As luck would have it, I got going just too late to catch the Summer sporadic E season and had to be satisfied with local contacts. With a 3 element beam hardly off the ground good solid contacts were made

all over southern New Hampshire and eastern Massachusetts. The exciter was recognized immediately as an S-Line by most of the regular SSB gang. Contacts were made on CW and AM as well with excellent results. In fact, anything the 32S1 would do on 20, it did on six with enough sock from just the barefoot converter to be heard. All in all the Continental "Six" seems destined to be the flyweight champ on six and should do its part to popularize SSB as a practical VHF mode of operation.

Continental "Six" Specifications

Power rating: 30 watts p.e.p. SSB and CW, reduced ratings on AM

Drive requirements: 1-5 watts from 20 meter source

Drive available at output for next stage: 15 watts minimum

Dimensions: 5 3/16 inches high, 8 5/8 inches wide, and 1 1/8 inches deep

Power supply required: 400 VDC at 100 ma.
150 VDC regulated at 30 ma.
6.3 VAC at 2 amperes

Price: \$99.95

Letter

Dear Wayne:


I wish to compliment you on that portion of your editorial in October 73 which deals with the League. It has always been my feeling that membership in the League is much more than a mere subscription to QST and I encourage all amateurs to subscribe to more than one amateur magazine, but to consider that their League affiliation is their democratic voice in the internal affairs of amateur radio. Your description and explanation of ARRL should do much to put into proper focus the purpose of the League and to encourage all active amateurs to support it.

Do you anticipate any further aims of the Institute of Amateur Radio than that of the proposed ham flight to Europe? If so, I would be most interested in hearing about them with a consideration of charter membership.

Carl L. Smith W₆BWJ
Director, Rocky Mtn. Division

The Institute will, if our mail is any indication, be involved with the fostering of technical improvements and dissemination of information on special amateur interests such as TV, RTTY, beacons, repeaters, scatter tests, moon-bounce, etc.

WALKIE-TALKIE RADIOPHONES

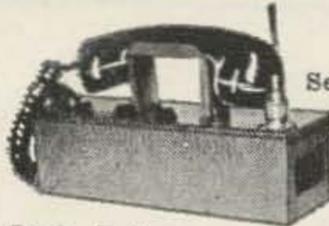


Dept. H-11

FROM \$59.98

Send for FREE literature on the complete line of VANGUARD radiophones, for industry, Civil Defense, CAP, Citizens and Amateur bands. Made in the U.S.A. and guaranteed 5 years.

VANGUARD ELECTRONIC LABS.
190-48 99th Ave., Hollis 23, N. Y.

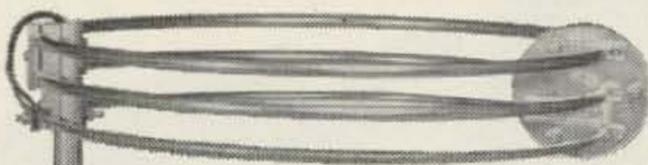

SATURN 6

the original

HALO

Saturn 6 Antenna only \$11.95

Saturn 6 plus mast & bumper mount \$16.95

HI-PAR Products Co.
FITCHBURG, MASSACHUSETTS


MAXIMUM POWER — MINIMUM SWR

To Your Antenna System

New! Nortronics
6A2 v-matcher.

Matches 6&2 meter 50-75 ohm xmtr output to balanced or single wire feed line 150-600 ohms.

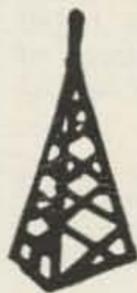Built-in VHF-type SWR bridge for 1:1 match. For powers of 5 to 500W. Complete bandswitching. Silver plated tank coils for max. Q. At least 40DB harmonic attenuation for TVI reduction.



V-Matcher \$59.75 net
A "Must" for Serious VHFers

The Following Also Available:

- 1—TU-6 Tuner (as above for 6M only) less SWR Bridge \$15.75
- 2—TU-2 Tuner (as above for 2M only) less SWR Bridge \$15.75
- 3—MM-V VHF SWR Bridge.....only \$29.75
- 4—BPF-2 2M Cavity Bandpass TVI filter (superior to all other types of filter)....\$14.75

NORTRONICS DIV. Avtronics, Inc.
3920 Garfield Ave.
Traverse City, Mich.

TERRIFIC!

VHF COLINEAR ARRAYS

LOOK TO CUSHCRAFT for SUPREME PERFORMANCE

- LIGHT WEIGHT
- HIGH FORWARD GAIN
- LARGE CAPTURE AREA
- MECHANICALLY BALANCED
- HIGH FRONT TO BACK RATIO

32 & 64 ELEMENT STACKING KITS ARE AVAILABLE

430 Mc.—\$9.25; 220 Mc.—\$12.95; 144 Mc.—\$16.00 (16 ELEMENTS)

WRITE FOR CATALOG

Cush 621 Hayward Street
Manchester, N. H. **Craft**

A FULL LINE OF

● AMATEUR COMMUNICATION
ANTENNAS

HARMONIC/TVI PROBLEMS??



GAVIN HAS THE SOLUTION FOR YOU
IN THIS NEW SERIES OF FILTERS
WITH EXCEPTIONALLY LOW
INSERTION LOSSES

6 METERS—TUNEABLE LOW-PASS MAVERICK

The only low-pass filter designed expressly for 6 meters. With 9 individually shielded sections and 5 stages tunable forming a composite filter of unequalled performance. Providing the sharpest cutoff with the lowest insertion losses. Less than 1 DB loss. Handles 400 watts PI. 35 DB rejection. Size 5" by 2" by 3"

AMATEUR NET \$16.95

MAVERICK II WITH POWER MONITOR

Same as above but with 6 meter power indicator calibrated in watts output. Supplied with 6 foot cable which plugs into receptical on filter Indicator Size 4" by 4" by 4½".
Slant Face, Reads 0-50. 0-400 watts.

AMATEUR NET \$34.95

2 METERS — BAND-PASS MODEL BP-144

A narrow band-pass filter with 6 mc pass band and 146 mc center frequency. Less than 1 DB insertion loss. At least 35 DB attenuation of harmonics out of pass band. Handles up to 185 watts PI.

Size 4" by 2¼" by 2¼"

AMATEUR NET \$11.85

80 THRU 10 METERS—SECOND HARMONIC FILTER

MODEL F810

Five separate filters housed in one package and selected by a front panel switch. Each filter is tuned for maximum attenuation of the second harmonic for that particular band. Second Harmonic Attenuation—35 DB. Handles up to 1 kw. Size 5" by 6" by 4".

AMATEUR NET \$24.75

MODEL LPF 80-40-20-15 or 10

The above filters are available in single band packaging for each band. Specifications are the same as F810.

Size 5" by 2" by 3" AMATEUR NET \$7.65

Write for complete brochures.

See your local dealer or order direct from . . .

Gavin Instruments, Inc.

Depot Square & Division St.
Somerville, New Jersey

Build Your Own Mobile Mike

Jim Kyle K5JKX


IN the early days of transistors, one of the favorite construction projects for ham use was a transistorized microphone for mobile use.

The superb semiconductor is more than 10 years old now, and most of the homebrew-mike projects have long since gone by the boards, but here's one far simpler than any which appeared in print in earlier years—which can still find a place in most any mobile station.

The circuit is an adaptation of a custom mobile mike built by Two-Way Radio Communication Co., of Oklahoma City, for its customers, which in turn was an adaptation of the Shure transistor dynamic mike and the Motorola model of the Shure.

Its main feature is complete elimination of any dc power supply for the transistor. This mike is a plug-in replacement for any carbon microphone; the transistor is powered from the same source originally used to power the carbon button.

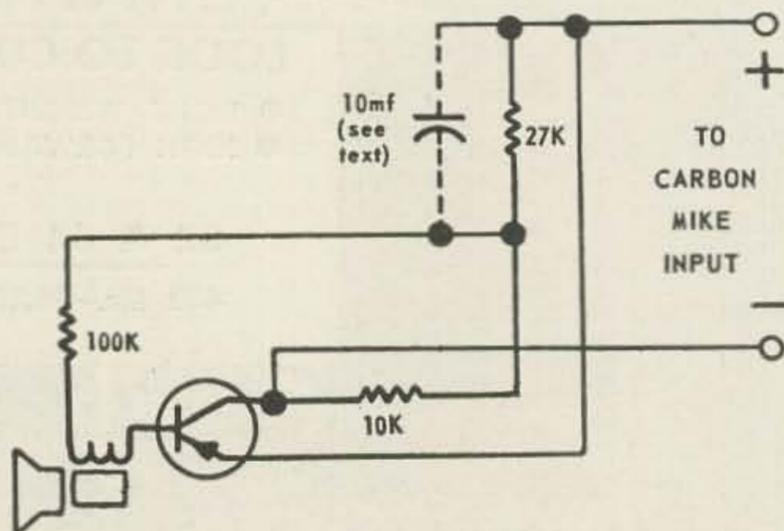If you want to be as fancy as the commercial version, scrounge up an old Shure-type carbon



mike case and buy a Shure VR dynamic mike cartridge for approximately \$15. On the other hand, if you're out to save some pennies here and there, use a tiny 2½-inch transistor-radio speaker and contrive a housing from brass, aluminum, or tin-can scraps.

In either event, you can put the circuit together most easily on either a printed-circuit board or a cardboard chassis. In addition to the transistor, all you need is the speaker or VR unit and three ½-watt resistors.

In operation, current through the 27K resistor produces a voltage drop. This voltage powers the single-stage common-emitter amplifier. Bias for the base is fed through the speaker coil. Ac generated by sound striking the cone is superimposed on the dc bias, and the transistor amplifies this up to approximately 1½ volts RMS output for average speech.

Virtually any common PNP transistor will work in the circuit as shown; the 2N107 is ideal and was used often in the commercial version. By simply switching polarity of the power leads, an NPN unit can be substituted.

Note that neither side of the circuit is grounded; this enables the mike to be connected to its plug in such a manner that power polarity is correct without introducing signal-ground problems. Occasionally, shunting the 27K resistor with a 10 mfd capacitor may boost output; however, it's not usually necessary.

The Quaker Electronics Crystal Etching and Grinding Kit

THERE ARE MANY surplus crystals around that fall just outside the ham bands, probably because the hams have already bought up the ones inside the bands. These crystals, almost useless to hams, are available for a ridiculously low price because of the lack of demand. Some hams have tried grinding these crystals to raise the frequency slightly, but the grinding method makes it difficult to make small changes. Small changes should be made by the more controllable method of etching, since with this process it is possible, with some practice, to get a frequency within a few cycles. A new kit, manufactured by Quaker Electronics, Mountain Top, Pa., and selling for only \$3.50, makes the process of changing crystal frequencies so easy that you really can't afford not to own one.

If I owned a Poly-Comm would I have to buy a VFO?

NO! It's built-in

A microphone?

NO! It's furnished

A mounting bracket?

NO! It's furnished

An AC/DC power supply?

NO! It's built-in

POLY-COMM®

for 2 or 6



What's the inside story?

Maximum Performance!

FEATURING • Dual NuVistor Pre amp/RF for .1 μ v for 6 db. S + N/N • Noise figure better than 4 db • Mini-load VFO for ultra stable transmit and receive • Noise limiting that will amaze you • RF output at least 10W on 6, 6W on 2 • Illuminated "S" meter that doubles for tune-up • Heavy gauge perforated steel case • Handcrafted teflon wiring throughout.

What's the cost?

POLY-COMM "2" **\$339.50** complete

POLY-COMM "6" **\$319.50** complete

and there's NO EXTRA CHARGE FOR CD UNITS!

Sounds like a good value, tell me more!

Gladly, just send in the coupon.

Please send complete data on:

Poly-comm "6" Poly-comm "2"

NAME _____

ADDRESS _____

CITY _____ STATE _____

Intended use _____

POLYTRONICS

LAB
inc.

388 Getty Avenue
CLIFTON, NEW JERSEY

Now!

for discriminating amateurs
who are satisfied
with nothing less than *THE VERY BEST*

McCoy SINGLE SIDE BAND FILTERS

The GOLDEN GUARDIAN (48B1)

TECHNICAL DATA

Impedance: 640 Ohms in and out (unbalanced to ground)

Unwanted Side Band Rejection: Greater than 55db



Passband Ripple: $\pm .5$ db

Shape factor: 6 to 20db
1.15 to 1


Shape factor: 6 to 50db
1.44 to 1

Package Size: $2\frac{7}{16}$ " x $1\frac{1}{32}$ " x 1"

Price: \$42.95 Each

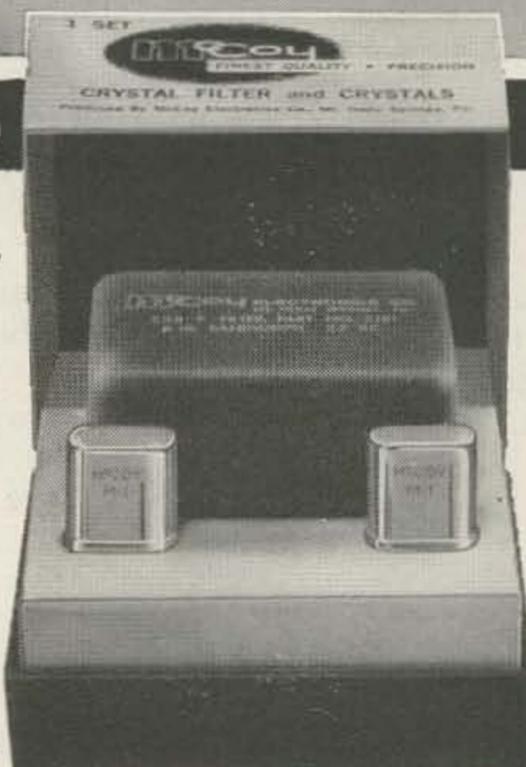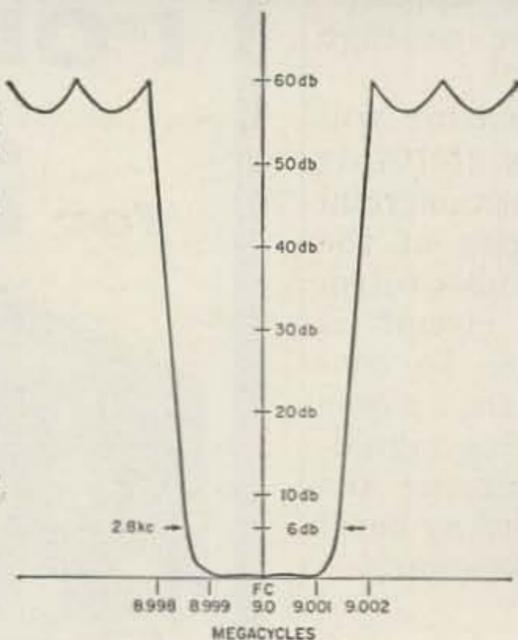

The SILVER SENTINEL (32B1)

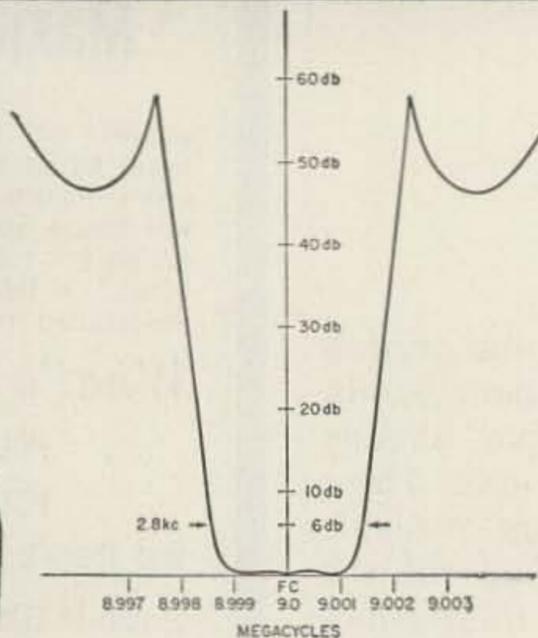

TECHNICAL DATA

Impedance: 560 Ohms in and out

Unwanted Side Band Rejection: Greater than 40db

Passband Ripple: $\pm .5$ db

Shape factor: 6 to 20db
1.21 to 1

Shape factor: 6 to 50db
1.56 to 1

Package Size: $1\frac{3}{4}$ " x $1\frac{1}{4}$ " x 1"

Price: \$32.95 Each

Both the Golden Guardian and the Silver Sentinel contain a precision McCoy filter and two of the famous M-1 McCoy Oscillator crystals. By switching crys-

tals either upper or lower side band operation may be selected. Balanced modulator circuit will be supplied upon request.

Both sets are available through leading distributors. To obtain the name of the distributor nearest you or for additional specific information, write:

McCoy

ELECTRONICS CO.

Dept. 73-11

MT. HOLLY SPRINGS, PA.

Phone: HUnter 6-3411

SUBSIDIARY OF OAK MANUFACTURING CO

The kit contains a package of Ammonium Bifluoride, used for etching the crystals, a package of grinding compound, six assorted crystal blanks, twelve assorted crystals in holders which can be modified for use on the ham bands or for practice, and the necessary tools.

With this kit it is possible to raise the frequency of a crystal from a few cycles to somewhat more than a megacycle. The crystal is ground until the area of the desired frequency is reached, and then etched to the exact frequency. Under some conditions this kit can even restore activity to somewhat inactive crystals.

The instructions are clear and well written, and good results can be obtained by anyone the first time. The instruction sheet has many hints in insure good results, as well as a diagram for a calibration oscillator.

The Ammonium Bifluoride can also be used to etch glass, numbers on tubes, etc. To do this, coat the glass object with paraffin and scratch the wax off where the etching is desired.


Results from this kit have been good. Several crystals were moved to within a few cycles of a frequency for VHF net operation and more moved from one part of the band to another.

This kit is quite a bargain at \$3.50 and can be ordered from Quaker Electronics, Mountain Top, Pa. . . . WA2INM


Push - Pull

Few hams are blessed with a well stocked junk-box or a surplus of cash. The idea presented here is intended to help you make use of what is in your junk-box.

The diagram hereabouts shows how a driver transformer with a single un-tapped secondary may be used to drive tubes in push-pull. Since the voltage across resistors R1 and R2 is equal to the voltage across the secondary of the transformer, the midpoint of the transformer can be grounded effectively by making R1 equal to R2 and grounding their junction. The effect is the same as with a center-tapped secondary winding, providing equal voltage to each grid. . . . W4JKL

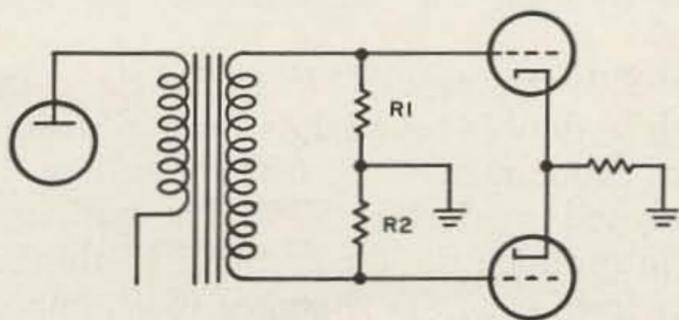

2 ANTENNAS IN 1

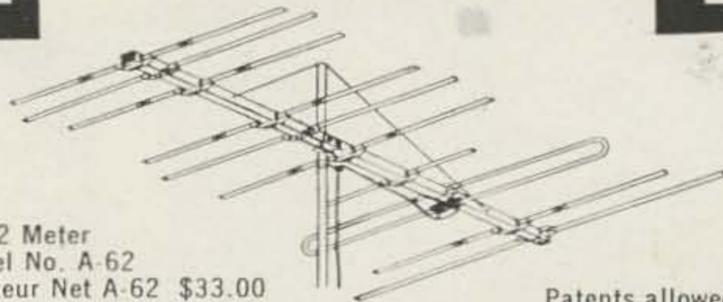

6 & 2 Meter
Model No. A-62
Amateur Net A-62 \$33.00
Stacking Kit AS-62 \$2.19

Patents allowed
and pending

**The Only Single Feed Line
6 and 2 METER
COMBINATION YAGI ANTENNA**

another first from **FINCO**[®]

ON 2 METERS

18 Elements
1 — Folded Dipole Plus
Special Phasing Stub
1 — 3 Element Colinear Reflector
4 — 3 Element Colinear Directors

ON 6 METERS

Full 4 Elements
1 — Folded Dipole
1 — Reflector
2 — Directors

See your FINCO Distributor
or write for Catalog 20-226

THE FINNEY COMPANY

Dept. 20

Bedford, Ohio



STYLE 10
SERIES

how WONDERODS
beat

"highway waggle"

You've seen it on the car ahead . . . maybe you even own a whip that lashes out like a run-away guillotine as your car reaches road speed. "Highway waggle" produces multiple vibrations, increases road noise — spoils reception.

A WONDEROD whip — Style 10 series — licks this problem with its Shakespeare construction. Inch for inch, fiberglass absorbs more energy — the factor that sets metal whips swaying.

— Besides, there's fewer inches in a WONDEROD than in metal antennas of comparable resonant length.

COLUMBIA PRODUCTS COMPANY
SHAKESPEARE CO. SUBSIDIARY, COLUMBIA, S. C.





Charles Spitz W4API
Associate Editor

73 tests the

Gonset Communicator IV-220

GONSET UTILIZED A LOT of engineering skill in producing six and two meter transceivers that were identical in appearance and performance. Now they have come out with a 220 mc Communicator that conforms to this pre-set pattern. In common with other Communicator models, the IV-220 is a transceiver in the functional sense only. It utilizes a separate transmitter and receiver with the only common portion being an audio section. Just like the six and two meter versions, the IV-220 has a directly calibrated and illuminated slide-rule receiver dial, geared by a dual ratio planetary drive for fast or slow tuning. The illuminated meter can be made to read signal strength, a frequency spot, or relative power output. The new model 3357 vfo shown in the photograph may be plugged into one of the six crystal sockets on the rear apron. The vfo dial is directly calibrated for the output frequencies of any of the Communicators, and even has a provision for FM!

Unfortunately the Gonset Company no longer gives out microphones as standard equipment, and this change has been carried over to the later two meter models. The IV-220 uses a standard three contact PJ-068 jack for the mike connector.

On older Communicators it was necessary to switch meter function between receive and transmit, and be restricted to push-to-talk operation. Not so on the IV-220! Transmitting on manual will automatically change meter function from S readings to power output. A spot-

ting switch in the metering circuit shows not only your transmitting frequency, but the relative merit of your crystal by meter readings.

Receiver Section

There are many ways of arriving at 220 mc from some lower frequency, and the way that Gonset does it is interesting. The receiver portion of the system uses one of the new 6^{FY5} frame grid tubes as an rf amplifier, which is responsible for the low-noise front end. A 6^{J6} oscillator with an overtone crystal operating at 65.667 mc multiplies to 197 mc for injection into another 6^{FY5} which acts as the first mixer. The crystal controlled conversion thus achieved provides for excellent frequency stability. The second oscillator, a 7059 triode section, is tunable over the frequency range of 25.3 to 30.3 mc, and combines with the first *if* frequency of 23 to 28 mc. A 6^{AV6} is used as a second mixer, and produces a fixed frequency output of 2.3 mc. The pentode half of the 7059 second oscillator is used as another oscillator when crystal controlled fixed frequency operation is desired. These crystals may be selected from 6.9 to 8.566 mc so that they can be tripled to 20.7 or 25.7 mc for injection into the second mixer.

The 2.3 mc second *if* signal is coupled through a double-tuned bandpass transformer to the third mixer (a 6BE6) where it is heterodyned against a 2755 kc oscillator in order to produce the desired 455 kc third conversion frequency. Two stages of *if* amplifica-

tion are employed at 455 kc. Six tuned circuits in these stages are responsible for the outstanding selectivity. A vacuum diode (one-third of a 6AV6) is used as a detector, while the other portions are used as a rectifier to furnish delayed AVC to the rf amplifier. One-half of a 6AL5 is used as a conventional noise limiter, and the other half is used for squelch operation.

The triode section of the 6AV6 is used as the first audio amplifier. This audio is fed into the triode section of a 7059 in the modulator, and then into one of the 6BQ5 modulators that functions as the audio output amplifier as well. An audio jack is available on the rear apron and may be used for either headphones or external speaker.

Transmitter Section

The transmitter uses the plentiful and low priced 8 mc crystals or a vfo for the frequency source. The crystals connect to the input of a broad-banded 12BY7 that triples to 24 mc. A second 12BY7 triples between 73.332 and 75 mc, and is followed by a 6939 that triples to the 220 mc operating frequency. This signal then gets amplified by a pair of 6360's in push-pull. The Gonset people certainly had simplicity of operation in mind, because the only transmitting controls are plate loading and plate tuning.

The modulator uses the pentode section of a 7059 as a speech amplifier and the triode section as a phase inverter. The 7059 is followed by a pair of 6BQ5's operating in push-pull. This modulator is enough to provide 10 full watts of class AB₁ audio for real high level plate modulation.

The antenna changeover relay is built right in here, so it'll save you the expense of buying one.

Power Supply and Control System

Just as in the six and two meter models, the universal power supply uses two 2N1554 transistors for 12 vdc operation. Regular 117 vac can be used by merely changing the line cords in back of the set. The secondary winding of a two way power transformer feeds a power silicon diode bridge rectifier with a regular capacitor input filter. The push-to-talk relay changes the antenna connections between transmit and receive, as well as B plus from the modulator to the receiver, and ground from transmitter keying to speaker.

Observations

Even though the IV-200 was given its test

PREVERTER 50 & 144



THE BEST PREAMPLIFIERS AVAILABLE
AT ANY PRICE — TRANSISTORIZED —
12 volt. NO NEED FOR EXPENSIVE HIGH
VOLTAGE SUPPLIES — LOW NOISE
FIGURE—

6 or 12 Meter model . . . \$14.95 post paid.



KITS
MAILED POSTPAID
ANYWHERE IN USA.




Send for free list of
more than 80 printed
circuit kits.

Let's "kit" Together
Use YOUR Parts & PAPPY'S wiring
IRVING ELECTRONICS CO
POST OFFICE BOX 9222 SAN ANTONIO 4, TEXAS



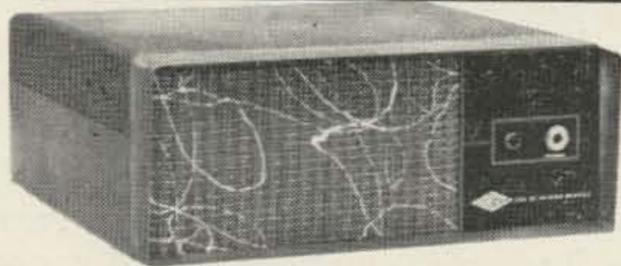**THE GONSET G-76
IS EQUALLY ADAPTABLE TO
MOBILE USE
OR FIXED STATION!**



The G-76 operates on 6, 10, 15, 20, 40 and 80 meters. It is easily installed in vehicle, office or home. As a fixed station with AC power supply and speaker it is completely compatible with the 3357 VFO to provide amateurs with 6 meter band coverage.

For additional information contact your Gonset Distributor or write Dept. 73-11

GONSET
DIVISION OF YOUNG SPRING & WIRE CORPORATION
801 SOUTH MAIN STREET, BURBANK, CALIFORNIA



runs with a poorly oriented 12 element Yagi, good signals were sent as far as 50 miles. My thanks go to the many hams who unwittingly took part in the tests with their unsolicited observations and constructive criticisms, not realizing the help they were giving.

Many good 5 x 9 contacts were held with Ernie, W3UJG in Maryland, and with other hams through Virginia and the District of Columbia. To give an idea of band possibilities, W3UJG has been working twice a week schedules with W3ARW 120 miles away in Scranton. This has been going on for years . . . and they've never had any QRM.

Scope patterns were clean as on the six and two meter versions. A better than average converter was placed ahead of a 75A4 receiver, and pitted against the IV-220. Every station that was heard on the 75A4 was heard on the IV-220. Frequency readings were within the parallax of the dial configuration; for practical purposes it was as accurate as anyone could desire.

I suppose that if modifications were to be made, a bfo would be one of the first things on the list. It sure would help in locating weak stations and working CW. Many veterans of the band may applaud the fact that there is no gain control, but a screw driver adjust positioned to discourage the over-modulators would have been an aid to my weak voice, provided more gain were available.

All on-the-air reports were very good without having to solicit them. All controls function uncritically in a manner one would expect from low frequency professional equipment. Shorting the antenna terminals on receive did not disclose any self-generated birdies.

It cannot be emphasized too much that there is a lack of activity on the band. The band must see more operation if we are to keep it and we all can help by devoting some time to these higher frequencies of ours. I am sure the availability of the Communicator IV-220 will do much towards that end on 220 mc. Amateurs who have not ventured on the

band will find much pleasure, companionship and the thrill of joining the pioneers in this portion of the spectrum. . . . W4API

Specifications

Frequency Range	: 219.7 mc to 225.3 mc
Frequency Control	: Front panel selection of 6 crystals, 8 mc and/or external VFO
Final Power Input	: 20 Watts, DC Plate.
Power Supply	: 12.6 VDC; Receive 7.2 amps, transmit, 10.3 amps. 117 VAC; Receive 87.5 watts, transmit 110 watts.
Modulation	: High Level, 10 watts, amplitude, 100% with high level clipping.
RF spurious and harmonic attenuation	: Down 50 db
Tuning Indicator	: Panel mounted meter for relative RF output or receive S meter.
Receiver Sensitivity	: 1.0 uv for 10db S/ N/N ratio.
Receiver Tuning	: Rear apron switch for one fixed crystal frequency or manual.
Triple Conversion	: 1st Conversion crystal, 2nd manual tuning, 3rd six tuned circuits.
Spurious Rejection	: Main image down 48db.
Noise and Hum	: Down 40db
Squelch Sensitivity	: 0.1 uv to 50 uv
Audio Output	: 2 watts nominal
Dimensions & Weight	: 5" high, 12½" wide, by 11" deep. 21.8 lbs
Power Supply	: 2-way 117 VAC/12 VDC built-in, solid state.
Microphone	: High impedance push to talk
Price	: Model 3351 Transmitter-Receiver \$394.50 : Model 3365 Universal Mounting Kit 3.95 : Model 3152 Telescoping Antenna 3.95 : Model 3363 Carrying Bag 12.00 : Model 3250 Ceramic Microphone 9.95 : Model 3357 VFO 69.50
Manufacturer	: Gonset Divison, Young Spring & Wire Corp., 801 South Main St., Burbank, California.

In Defense of the Operator

Douglas G. Hedin KØOFB/2
219 Blanchard Blvd.
Syracuse 9, New York

"The amateur that does not build his own equipment does not deserve to have a license!" These sentiments echo mockingly through the hallowed halls of the best (and worst) radio amateur circles. Unfortunately, though they are uttered with deepest conviction, they are based more on misguided sentiment than on

considered judgement. A thoughtful glance at the past, as well as the present, will bear this out.

In the beginning, there was static, bits of galena, slop jars, and pencil-lead resistors. The only way to get an amateur rig on the air was to build it yourself, and more than likely you made most of the components too. Contradictory ideas were a dime a dozen.

For a while, as the pulse of technology quickened with new-found adventure, amateurs kept pace with it, building their own equipment and contributing as much to the fledgling science as they benefited from it. But as new rungs were added to the ladder of knowledge, the amateur soon found that he had neither the time to spend studying nor the money to spend on components in order to keep up with the Jack-and-the-beanstalk growth of electronics. At the same time, many of the amateurs at first drawn to amateur radio by the thrill of building equipment with which to communicate discovered even deeper satisfaction in the communications themselves. True, they came to build, but they stayed to talk!

As more amateurs shouldered their way onto the bands, equipment that was more dependable, stable, selective, and easy to operate was demanded. Also, the amateurs found that they had to consider the demands of their jobs, the needs of their families, and the limits of their pocketbooks. Against these they had to equate the love of their hobby. If they could not both build and operate, which should they do?

Such a choice undoubtedly is difficult. Those of us who once had the time to build remember with nostalgia absent-mindedly munching on a piece of insulation; watching the surface of a newly-soldered joint slowly shrink and change from shiny silver to mossey grey as the metal cooled; snipping off the excess wire from a new component; blowing the old solder off an "old faithful" that had been used again and again; drilling a jillion little holes in a circle or square because we didn't have a socket punch; or flipping the switch when it was finally finished, keeping one eye on the filaments and the other on the rectifier plates (hoping that the former would glow cherry red and that the latter would not).

On the other hand, there is the promise of that first hissing rush of electrons when the receiver is turned on; the cacophony of little sounds as the rig warms up; the beam, sweeping the horizon like a great electronic spyglass; the thrill of a new contact in another state or country; the warm voice of an old friend, perhaps never seen but as real and close as a brother; the walls and ceiling a patchwork quilt of 3 x 5-inch memories; and the pile of old logs stained with sweat and other liquids, and growing dumpy with age.

Yes, the choice is hard. But it must be remembered that the choice is ours to make, and we make it only because we must, not because we want to!

... K ϕ OFB/2

ELIMINATE HETERODYNES


and other Unwanted Signals with
WATERS

Q-MULTIPLIER/NOTCH FILTER



The WATERS Q-MULTIPLIER/NOTCH FILTER will permit you to tune out annoying heterodynes. It gives a null of at least 40 db tunable across the entire IF passband.

The WATERS Q-MULTIPLIER/NOTCH FILTER combines an isolating amplifier and a tunable LC Bridged-T network with a Q Multiplier.

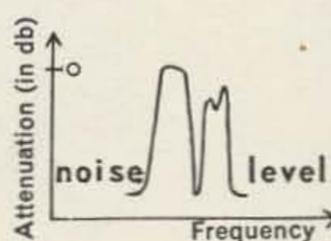Designed specifically to fit the Collins 75S-1 or Collins KWM-2, the unit comes assembled ready for installation. Escutcheon plates and knobs are matched to equipment so there is no discernable change in appearance of equipment.



337-M2

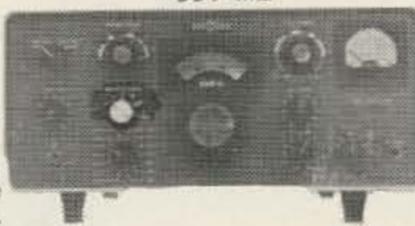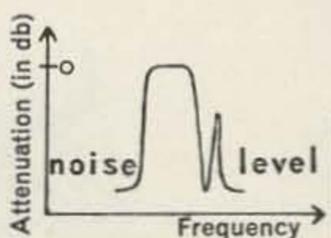

Response of IF Passband for Various Positions of Q-Multiplier / Notch Filter

3 Models Available:

337-S1 for Collins 75S-1	-----	\$33.95
337-M2 for Collins KWM-2	-----	\$33.95
340 PT for Collins KWM-2 with external VFO	-----	\$44.95

OTHER WATERS PRODUCTS:



Universal Hybrid Coupler (See Sept. '62 Adv. in 73)	-----	\$49.50
Coaxial Transfer Switch (See Aug. '62 Adv. in 73)	-----	\$11.45
Coaxial Selector Switch (See Aug. '62 Adv. in 73)	-----	\$12.95
Antenna System Transfer Switch (See Aug. '62 Adv. in 73)	-----	\$11.45

Available at leading distributors

Some territories available for representation

WATERS MANUFACTURING, INC.
WAYLAND, MASSACHUSETTS

Catch All

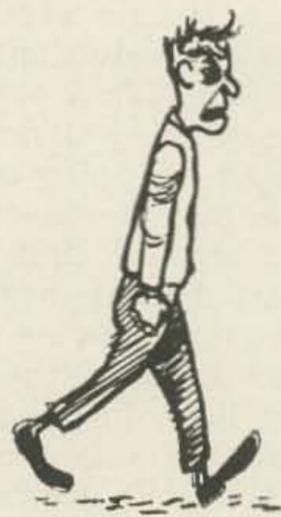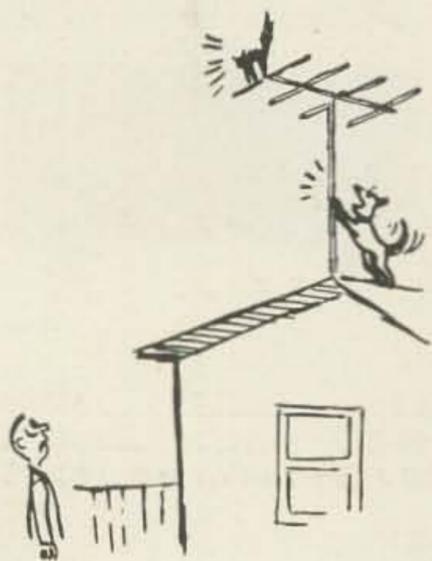

**"HAM SHACK" OR
"ON THE AIR" SIGNS**

Controllable, illuminated, "ON THE AIR" sign shows that you are XMTG. Can hook right into coil of antenna change-over relay. Matching "HAM STATION" sign dresses up your shack. Heavy gauge steel, 10½" long, 3½" high, 3" deep; operates on 110 VAC. Specify choice of sign. **\$6.95 ea.**




SUPEREX HAM HEADPHONES

Full comfort even after many enjoyable hours of continuous use. Superb comfort even for eyeglass wearers. Crisp, distortionless reproduction and high sensitivity allows you to single out that weak signal and hard to reach station. 600 ohms impedance, completely adjustable head harness. **\$24.95**

CLEGG 99'er 6 METER TRANSCEIVER


A true ham station, ideal for both fixed station and mobile operation. Double conversion superhet gives you extreme selectivity and freedom from images and cross modulation. Transmitter section has an ultra-stable crystal oscillator which also may be controlled by external VFO. Efficient, fully modulated 8 watt final works into flexible Pi network tank circuit. Large S meter serves for transmitter tune-up procedure. **Amateur net price \$159.95.**

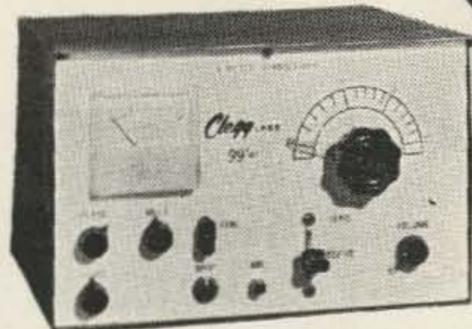

ZEUS and INTERCEPTOR also in stock.

SWAN MOBILE SSB TRANSCEIVER

3 tunable models available: SW175 (3.8 to 4.0 mc); SW140 (7.2 to 7.3 mc); and SW120 (14.2 to 14.35 mc). See QST Aug. '62, pp. 52-54 for details on unit. 180 W. PEP, crystal lattice filter, 3kc bw on Transmit/Receive, exceptional mechanical, electrical and thermal stability. Receiver sensitivity less than 1 microvolt. Tuning controls are common to Transmit/Receive. **Transceiver with mounting bracket. Specify model. \$275.00**
SW12A - 12 VDC mobile power supply. \$99.50

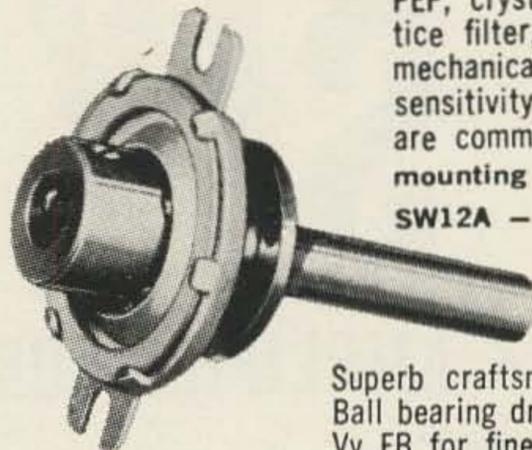


Shown approx. actual size.

**PRECISION PLANETARY-VERNIER
for exceptionally fine tuning**

Superb craftsmanship by Jackson Bros. of England. Ball bearing drive, ¼" dia. Shaft 1½" long, 6:1 ratio. Vy FB for fine tuning. Easily adaptable to any shaft. Comparable value \$5.95. **Amateur net \$1.50 ea. 10 for \$13.50**

PRECISION BALL DRIVE DIAL

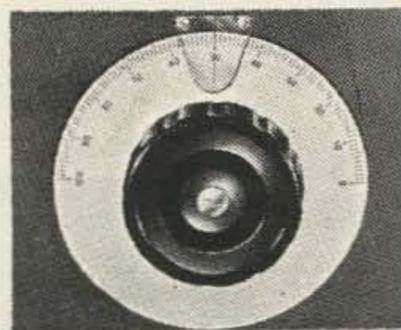Another superb product of Jackson Bros. of England. 4" dia. dial with 6:1 ball drive ratio. Fits standard ¼" shaft. For that velvet touch... **Amateur net \$3.95**



VERSATILE MINIATURE TRANSFORMER

Same as used in W2EWL SSB Rig—March, 1956 QST. Three sets of CT windings for a combination of impedances: 600 ohms, 5200 ohms, 22000 ohms. (By using center-taps the impedances are quartered). The ideal transformer for a SSB transmitter. Other uses: inter-stage, transistor, high impedance choke, line to grid or plate, etc. Size only 2" h. x ¾" w. x ¾" d. New and fully shielded.



**Amateur net \$1.39.
3 for \$3.49.
10 for \$10.75**

Trade-ins welcomed.

SEND FOR FREE CATALOG

**MAIL ORDERS
PROMPTLY PROCESSED.
SAME-DAY
SHIPMENT FROM STOCK.**

TO SAVE C.O.D. CHARGES, PLEASE INCLUDE SUFFICIENT POSTAGE WITH YOUR ORDER. ANY EXTRA MONEY WILL BE RETURNED.


ALL PRICES F.O.B. N.Y.C.
Arrow's Export Dept. Ships To All Parts Of The World!
Prices Subject To Change Without Notice.

**BULLSEYE
BUYS
AT
ARROW**

**hand-picked
for hams
by hams...**

ARROW ELECTRONICS, INC.

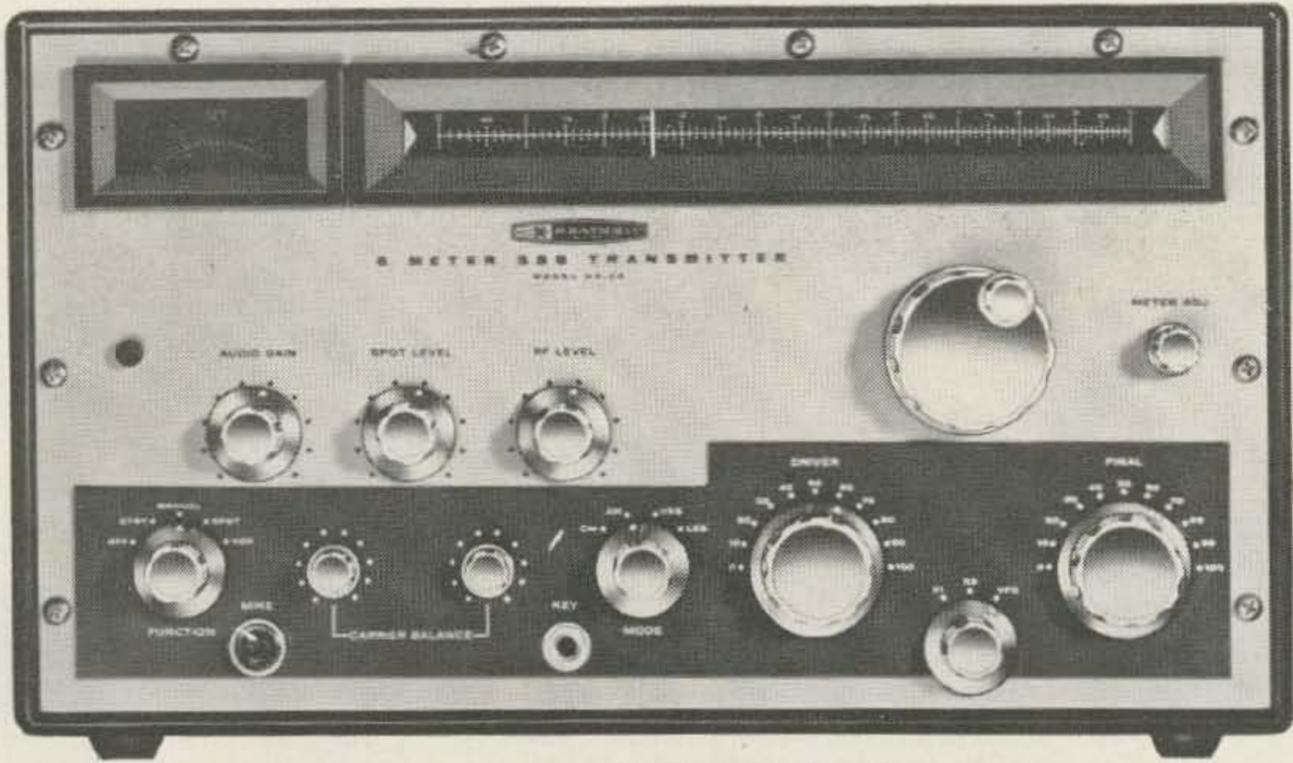
65 Cortlandt St., N.Y. 7, N.Y. • 525 Jericho Tpke., Mineola, N.Y. • 225 Main St., Norwalk, Conn.
212 — Dlgyb 9-4730 516 — Pioneer 6-8686 203 — Victor 7-5889




HEATHKIT HX-30 SIX METER SSB TRANSMITTER

SSB SIX PACK

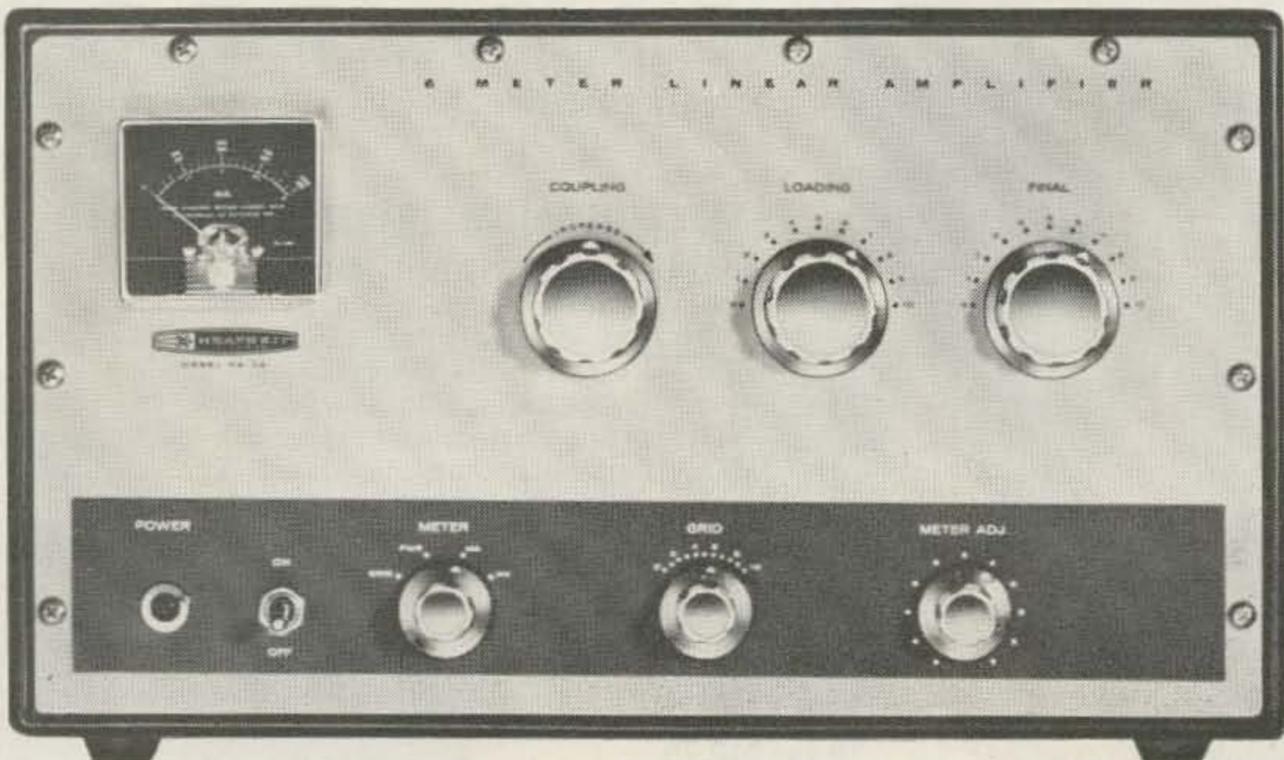A NEW EXCITER & AMPLIFIER FOR 125 WATTS PEP ON SIX




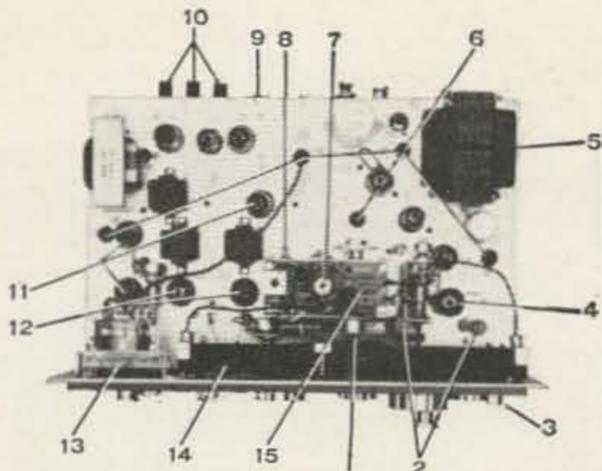HEATHKIT HA-20 SIX METER LINEAR AMPLIFIER



**HEATHKIT HX-30
SIX METER SSB TRANSMITTER**

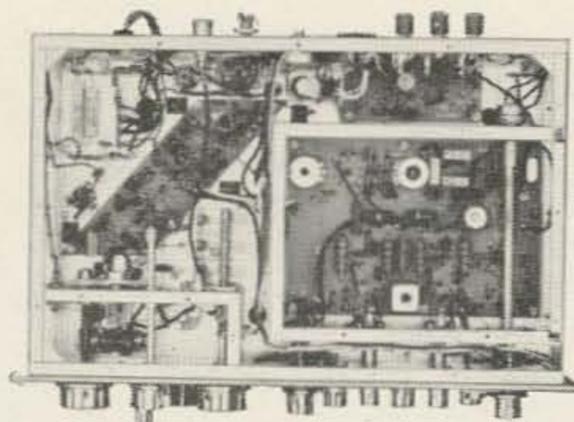1. Anti-backlash helical gear for smooth VFO tuning. 2. Adjustable final amp. coupling and loading. 3. Meter control with push-button over-ride to check carrier null. 4. 6360 final amplifier for 20 watt PEP RF input. 5. Regulated power supply. 6. Five test-point jacks for easy alignment using panel meter. 7. Low frequency heterodyne VFO electronics on circuit board. 8. VFO frequency determining components mounted on "heat-sink" plate in enclosure. 9. Accessory socket for control functions. 10. Built-in VOX & anti-trip circuitry. 11. Three audio stages with speech filter. 12. Phasing type SSB generator heterodyned to output frequency. 13. Meter indicates relative power output. 14. Lighted slide-rule dial with 9" per megacycle of bandspread. 15. Two crystal sockets for net or MARS operation (provides frequency coverage down to 49.8 mc).




TAKES LESS THAN 30 HOURS TO ASSEMBLE:

3 extra-strength circuit boards and 3 precut, cabled wiring harnesses simplify assembly and insure correct parts placement. Compartmentalized construction and thorough shielding assure stable, reliable performance. Advanced design features provide 50 to 54 mc coverage in four 1 mc segments (crystal for 50 to 51 mc supplied); USB, LSB, CW, AM operation; 50 db carrier suppression; 40 db unwanted sideband suppressions; grid block keying with filter; 50-75 ohm coax output and many more. Overall dimensions only 16⁵/₈" W x 10¹/₈" H x 10" D.

**Kit HX-30, 50 lbs., no money down,
\$18 mo. \$189.95**


**SSB
SIX PACK
as low as
\$27 per mo.**

Attention all six-meter fans! Here's another Heathkit first! A brand new SSB exciter and linear for six meter operation at sensational savings! Only \$289.90 for the pair . . . less than the cost of most transverters. Together they form a complete, high performance 6-meter SSB station designed for maximum efficiency and operating convenience. Check the many features of these two units . . . you'll find them the perfect pair for your station . . . enter your order today and go SSB on Six!

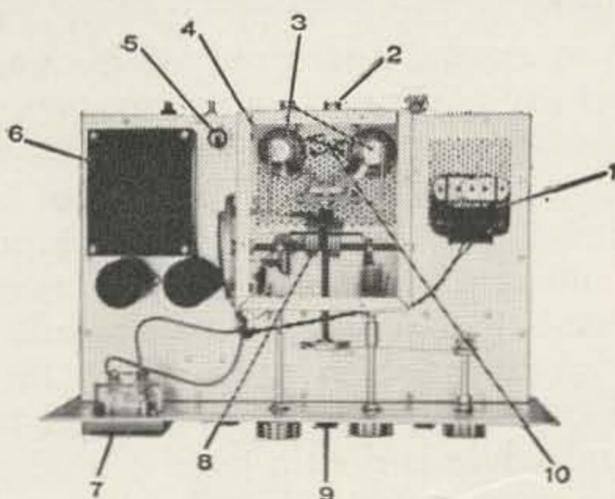

**HEATHKIT HA-20
SIX METER LINEAR AMPLIFIER**

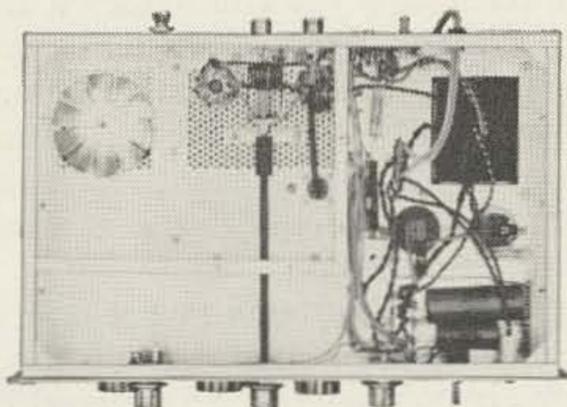1. Fan forced-air cooling of final amplifier. 2. Only 2.5 to 10 watts PEP driving power required. 3. 125 watts PEP input. 4. Completely shielded RF circuitry. 5. Regulated screen voltage. 6. Solid-state rectifiers for cool, efficient operation. 7. Metered grid current, plate current, plate voltage & relative power output. 8. Link coupled RF output, 50-75 ohm coaxial. 9. 50 ohm tuned grid input to accommodate various levels of driving power. 10. Neutralized push-pull 6146 final amplifiers.




EASY ASSEMBLY: Clean, open circuit layout permits conventional wiring with less than 10 hours actual construction time. As in the HX-30, a heavy steel copper-clad cabinet provides strength, beauty and superior shielding, measures just 16⁵/₈" W x 10¹/₈" H x 10" D. Frequency coverage is 49.8 to 54 megacycles. All power supplies are built in. A tremendous value at this low Heathkit price!

**Kit HA-20, 43 lbs., no money down,
\$10 mo. \$99.95**



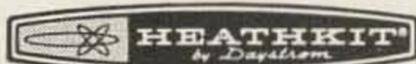**FREE 1963
HEATHKIT
CATALOG**
New edition — more than 100 new kits since last issue — over 250 kits in all.



HEATH COMPANY
Benton Harbor 11, Michigan

Please Send FREE 1963 Heathkit Catalog

Name _____

Address _____

City _____ Zone _____ State _____

Of RTTY — and Filters

Frank VanBrunt W3TUZ

Teleprinter operation by amateurs usually consists of the transmission of two frequencies, one separated from the other by 850 cycles. One frequency represents the mark signal and the other the space signal. With frequency shift keying (FSK) normal practice is to have the lower of the two frequencies as the space signal and the higher frequency the mark signal. The problem in reception is, briefly stated, to use specialized receiving equipment which, when the frequency representing the mark signal is received, provides current to the selector magnet of the machine and when the space signal is received cuts off the flow of current to this magnet. A filter (or a discriminator, which is basically a specialized form of a filter) must be used for separating this information. Our objective here will be to give some indication of the considerations that go into the choice of filter, and some help in getting a reasonably adequate filter operating.

One of the simplest systems to get operating is a system which uses only one of the two signals. Briefly, if you have an FSK signal being received by a receiver with either a 500 cycle mechanical filter or a good crystal filter you can tune the receiver so as to pass only one of the two signals. If you then rectify and filter the audio tone coming from the receiver you will have a dc signal that switches on and off depending on whether a mark or a space is being transmitted. This can then be amplified (by relays, tubes, transistors, or magamps) and used to control the printer. It has the virtue of simplicity, but unfortunately it also has the accompanying defects. It is quite sensitive to noise and to interference. It also discards half of the information being transmitted, a luxury we can seldom afford with the present level of ham band occupancy. Quite obviously the transmitting station could save power by merely transmitting either the mark or space only—this is sometimes done and is known as

make and break keying (m.a.b.). Some countries do not permit amateur FSK operations and the hams are forced to this less efficient system.

Another relatively simple type of filter that is sometimes used is a cycle counter. This circuit, which is used in simple frequency meters, gives a dc voltage output which is proportional to the frequency of the input signal. This voltage output is fed to circuits which give a current *on* condition for a voltage output below a certain level and a current *off* condition for a voltage above a certain level. This level is adjustable and is normally set at an output voltage level corresponding to an input frequency half way between the mark and space output frequencies. The circuitry is simple, consisting only of resistors, capacitors, and tubes or transistors. No complex adjustment procedures are involved and it is quite tolerant of varying input frequencies and receiver drift. The very tolerance and simplicity which are so appealing are also the qualities which make it less than adequate. It is very sensitive to noise and interference, and while it does a good job when conditions are good, it fails dismally when the going gets rough. Somehow it seems the going always gets rough for me!

By far the most widely used filter systems are those which employ what is basically a discriminator. The simplest forms are those operating at the intermediate frequency of the receiver and having a peak to peak separation of about 1000 cycles. The circuits are substantially the same as conventional FM receivers and, unlike the two systems previously described, have the noise cancellation characteristics of FM discriminators. They can also tolerate a modest amount of drift and will work for signals ranging from relatively short shifts (short shift is the term usually applied to shifts of less than the usual 850 cycles) up to those with shifts of the order of 1000 cycles. This has considerable merit for even the most casual of

checks will indicate that while 850 cycles is generally accepted as the standard by the amateur fraternity, some of the gang only have a very foggy notion of what constitutes 850 cycles.

Receiving short shifts is a distinct advantage—you can copy some of the commercial stations using 425 cycle shift, and you can experiment with even smaller shifts. However, if your primary concern is with short shift signals, it would be far better to have a discriminator with a peak to peak separation of only 10% more than the desired shift. With this circuit the output voltage is proportional to the frequency shift from the center frequency, thus with a 1000 cycle discriminator being used on a 170 cycle shift signal, an interfering signal of equal strength but 500 cycles away from the center frequency will give far greater output voltage than the desired signal.

This technique has another disadvantage however—it won't work conveniently on an AFSK signal. You can, by careful tuning and continuous watching make it play, but in the process you lose the freedom from drift problem that make AFSK operation on VHF such a pleasant change.


The most widely used system is the audio discriminator type which uses one resonant circuit for the mark channel and another resonant circuit for the space channel. With relatively low Q resonant circuits this is substantially the same as the *af* discriminator (See Fig. 1). However, it does have the added advantage of being equally useful for both FSK and AFSK. With higher Q inductors you sacrifice the ability to operate with short shifts but you improve the interference rejection capabilities of the system, and at the same time decrease the effective bandwidth with a resulting increase in the signal to noise ratio. (See Fig. 1). The problem for the amateur RTTY operator has been two-fold, first obtaining inductances with reasonably high Q, and secondly, actually tuning up the unit once suitable inductors had been procured.

As for inductors, some of the earliest units which were described used conventional chokes or transformers with laminations removed or


GOOD MOBILES GO

HUSFLER

MOBILE ANTENNA 10-15-20-40-75-METERS

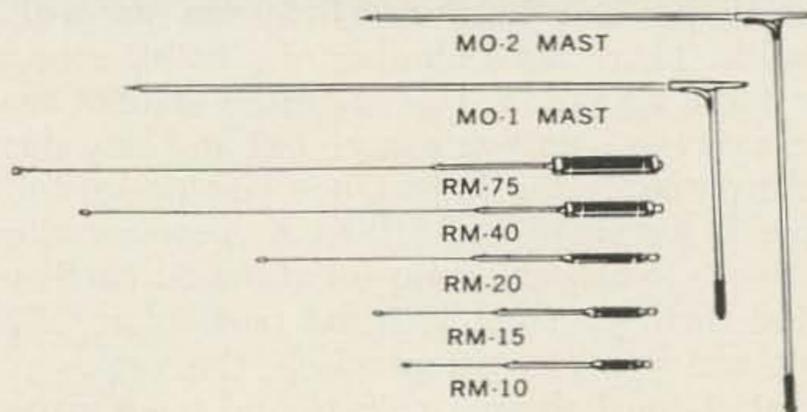

Buy only the mast and resonators for the bands you operate. NO NEED FOR MATCHING DEVICES, NO FEED LINE LENGTH PROBLEMS. Use any length of 52 ohm cable. New, efficient concept of center loading. Each resonator has a coil specially designed for maximum radiation for a particular band. Center frequency tuning is by an adjustable stainless rod in the resonator. The fold-over aluminum mast permits instant interchange of resonators. Mast folds over for garage storage. Mast has 3/8-24 base stud to fit standard mobile mounts, but will perform better with New-Tronic mounts. Power rating is 75 watts dc input A.M. - 250 watts PEP input for SSB.

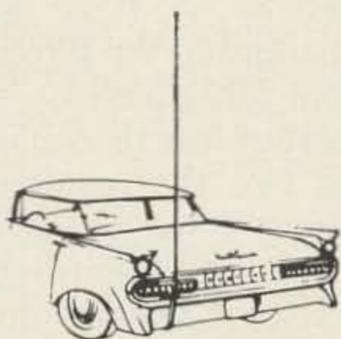

Mast and resonator in mobilizing position



Mast and resonator folded over

RESONATOR WILL WORK PROPERLY ONLY IF USED WITH MO-1 OR MO-2 MASTS. ANTENNA ASSEMBLY CONSISTS OF 1 MAST and 1 RESONATOR.

MODEL	DESCRIPTION	TOT. HGT. of ASSY.	NET
MO-1	54" mast folds at 15" fr. base	Rear deck or fender	\$ 7.95
MO-2	54" mast folds at 27" fr. base	Bumper	7.95
RM-10	10 meter resonator	80" max. - 75" min.	5.95
RM-15	15 meter resonator	81" max. - 76" min.	6.95
RM-20	20 meter resonator	83" max. - 78" min.	7.95
RM-40	40 meter resonator	92" max. - 87" min.	9.95
RM-75	75 meter resonator	97" max. - 91" min.	11.95

ANY MAST OR RESONATOR MAY BE PURCHASED SEPARATELY

MODEL BM-1 BUMPER MOUNT

Flat alloy steel strap fits any shape bumper, large or small. "J" bolts require only 1/4" clearance between top of bumper and car body. Heavily chrome plated 1 1/2" die cast Zamak ball has 3/8"-24 thread. Adjustable for true vertical position. Gray Cycloc base. Heavily cadmium plated...\$6.95



Ask your distributor to show you these and other fine NEW-TRONICS products. Write for literature on the complete NEW-TRONICS line.

NEW-TRONICS CORP.
3455 Vega Avenue Cleveland 13, Ohio

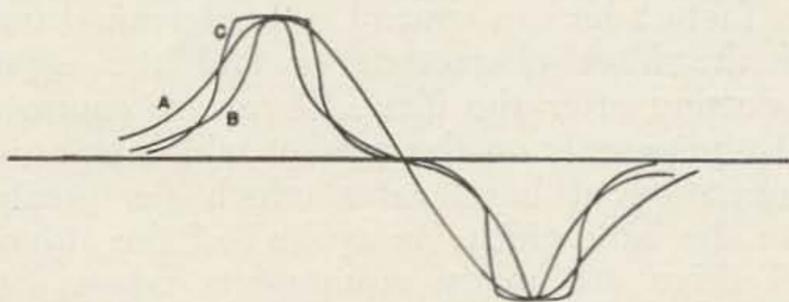


FIG. 1

Discriminator response curves:

- Simple if type discriminator
- Single toroid in each section
- Double toroid in each section

otherwise modified. These were very low Q units and while some of them used multiple resonant circuits to improve the performance they were still relatively poor filters. A number of subsequent units used slug tuned inductors which were designed for television sets. While the Q of these inductances was reasonably good at higher frequencies, their Q and thus their resulting performance at 2125 and 2975 cycles was poor. The best Q and the best performance are to be had from molybdenum permalloy toroids. There are a number of possible sources for these toroids. If you are more affluent than the average ham you can go out and buy them with precisely the inductance you desire for a price between \$5 and \$10 each. A second alternative is to buy the cores for about \$1 each and wind them yourself. It is not particularly difficult and you can get precisely the values you want. A third alternative is to find some surplus filters which have usable toroids in them and disassemble the filters. This technique provided about 300 excellent toroids for the local gang at a cost of less than 25¢ a doughnut. This I might add was the result of a trip down radio row buying a sample of every likely looking filter, then taking them home and unpotting them to find what was inside. The last and most common source of these toroids is the 88 mhy loading coils that are used by telephone companies in large quantities. These are widely advertised and in small quantities cost on the order of \$1 each. If you are alert and find a junkyard with large sealed cans of these the costs can be cut significantly—you will end up doing a considerable amount of labor and have an awful lot of toroids on hand.

So much for supply problems, back to performance. The 88 mhy units used in a single resonant circuit for each of the two frequencies have a number of drawbacks. The response is more sharply peaked than is desirable for general use. Ideally this could be improved by using larger inductances which would result in a higher L/C ratio—inductances of 500 mhy or so are better in single tuned circuits. Another drawback is the fact that using the same value of inductance in each resonant circuit results in a L/C that is significantly different in the two circuits (by a factor of about 2/1). An added source of variation is the change in Q of the inductors as a function of frequency.

Ideally one not only wants the peak output of each of the two response curves to be equal in value (and this condition is readily achieved by adjusting the inputs of the two circuits), but you also want the area under the two curves to be equal. The latter requirement will result in optimum noise cancellation in the output of the discriminator. This assumes, of course, that

by noise you are referring to an input which is stochastically distributed within the relevant frequency limits.

The next step toward this ideal and toward improved performance is to use a more complex filter. The most common is a simple filter using two toroids in each channel with capacitive coupling between the two resonant circuits. This is just two resonant circuits in which the over coupling is adjusted to broaden the response curves so that the bandpass in both the mark and space channels are the same. This type of filter has been widely used and was discussed in detail some years back by Bob Breitbach (WØNRM) in an article in RTTY News. The basic filter with the appropriate values is shown in Fig. 2. The values given are


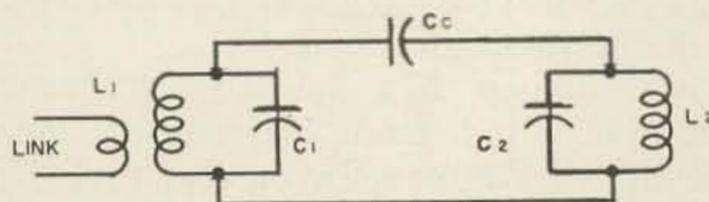


FIG. 2

	L ₁ & L ₂	C ₁ & C ₂	C _c	Link
2125 cps	88 mhy.	.06	.0059	9 turns
2975 cps	88 mhy.	.03	.0022	5 turns

for a bandwidth of 200 cycles. This bandwidth is recommended for general operation, and represents a compromise between a desire for a better signal to noise ratio and better rejection of interfering signals that results from a narrower bandwidth—and the ease of tuning, tolerance of moderate drift, and ability to accept inaccurate shifts that result from wider bandwidths. If you have a good stable receiver and don't mind retuning now and then you can use a narrower bandpass.

The question often arises as to how narrow a bandpass can be used, and considerable controversy, information, and misinformation have been published on the subject. This will in fact depend on the signal to noise ratio, the printer speed (baud rate), the characteristics of the filter you use, the number of errors you are willing to tolerate, and the signal processing after the filter. For the average ham the only two factors he can control in his terminal unit are the filter characteristics and the signal processing after the filter. There are commercial equipments on the market which transmit information at baud rates which are greater than the bandwidth (in cycles) of the circuit, and there are many equipments where this ratio is almost 1:1. Thus it should be feasible (since amateur operation is at 60 wpm or about 45 bauds) to use filters which are considerably sharper than the 200 cycle figure suggested for general use. The error rate a ham can tolerate

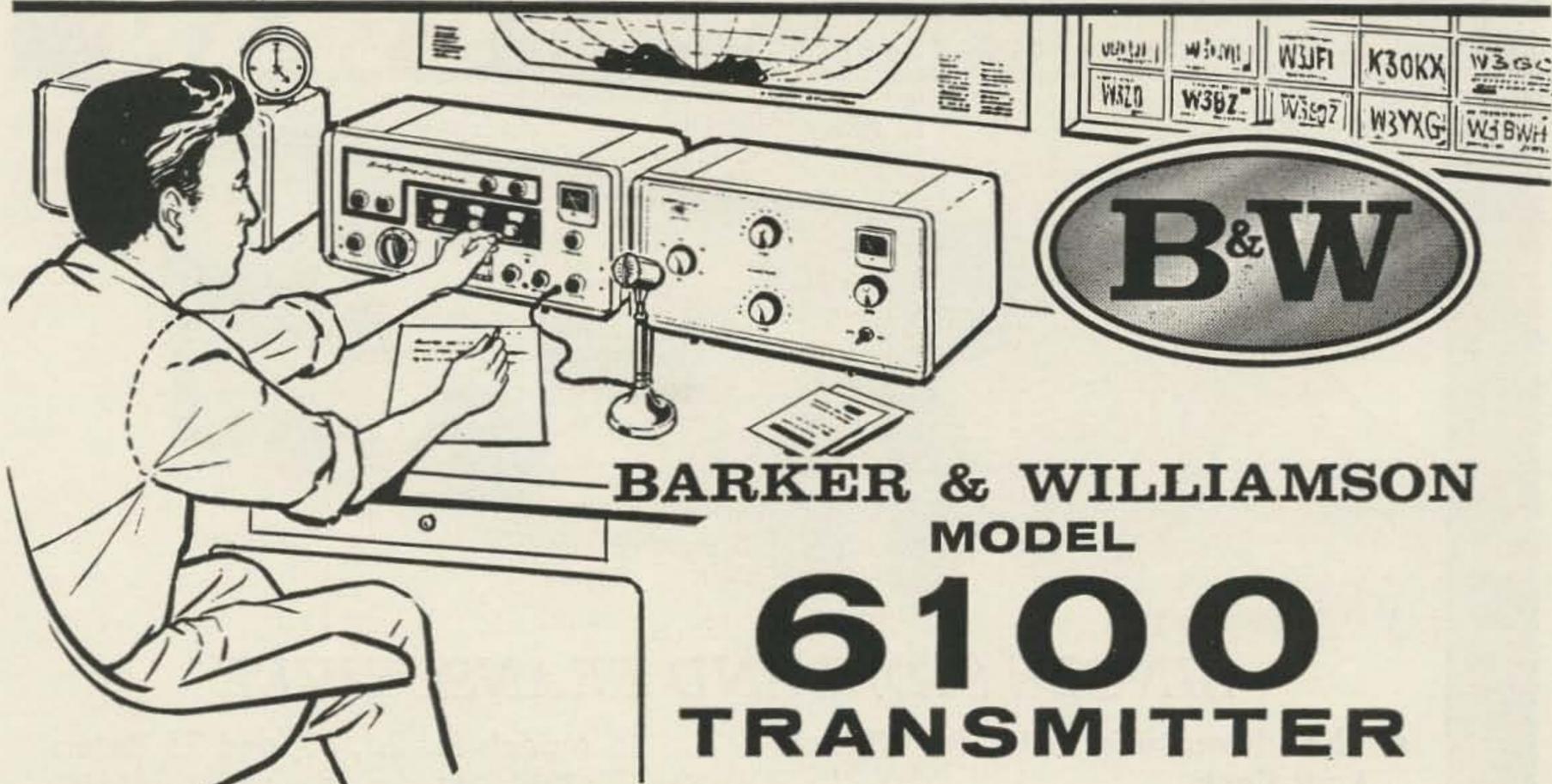

**BARKER & WILLIAMSON
MODEL**

6100 TRANSMITTER



SSB - CW - AM

With the
ALL NEW
CRYSTAL CONTROLLED
FREQUENCY
SYNTHESIZER

MODEL
LPA-1

GROUNDING GRID 1 KW LINEAR AMPLIFIER

The B&W LPA-1 Grounded Grid Linear Amplifier is the ideal companion high powered final for Model 6100. The LPA-1 produces a signal of extremely low distortion because of a unique negative feed-back arrangement.



MODEL 6100 - A NEW STANDARD OF FREQUENCY STABILITY

Engineered and built for outstanding performance and lasting satisfaction. The B&W 6100 is unsurpassed in stability, sideband suppression, signal quality, talk-power and many other features.

It is the first SSB amateur transmitter employing a crystal frequency synthesizer.

Send for colorful, descriptive brochure.

BARKER & WILLIAMSON, Inc.

Radio Communication Equipment Since 1932

BRISTOL, PENNSYLVANIA • Stillwell 8-5581

Here is the sensational **SWAN**



SINGLE SIDEBAND TRANSCEIVER

- **The ultimate in TALK-POWER at Low Cost**
- High Efficiency, One Band Design
- Proven Reliability; Highest Quality
- 240 Watts PEP with 800 Volt Supply
- Mobile, Portable, or Fixed Station

Models for 20, 40, and 75 Meters
Now in Production

\$275

Net Price

Ask your dealer for additional information


• **ASK THE HAM WHO OWNS ONE**

Swan Engineering Company

OCEANSIDE,
CALIFORNIA

(or for that matter be quite pleased with), is far higher than would be considered acceptable in normal commercial practice. Luckily languages have a relatively large order of redundancy and an error in one letter of a word now and then does not normally destroy the meaning of a sentence.

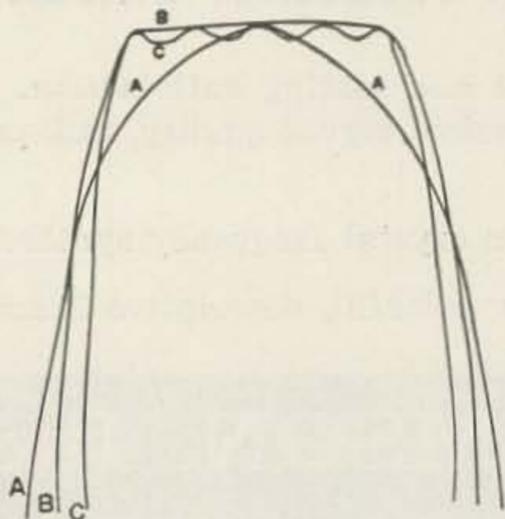When one starts considering sharp filters another factor becomes important: these filters do not merely have to discriminate between two frequencies, they must respond (and the faster the better), to pulses of the given frequencies which at the fastest reversal rate are



Filter response curves:

- Maximally linear phase design
- Butterworth (maximally flat amplitude)
- Chebyshev

22 milliseconds in length. If the risetime of the filter is too long relative to the pulse length, you will have poor performance regardless of the fine shape of the steady state frequency response curve. You can design three basic types of filters, the most common being the Butterworth or maximally flat amplitude response type. These have a flat response across the top and relatively steep skirts. A second type is the Chebyshev*, which is becoming increasingly popular. Briefly put, if you are willing to tolerate some ripple across the pass band of the filter, you can achieve better skirt selectivity characteristics; and the more ripple you can tolerate the steeper you can make the skirts. The third class of filters are those designed for maximally linear phase variation across the passband of the filter. This type does not have as steep skirts as either of the other types, and it does not have a flat amplitude response across the passband—it is in fact peaked in the center of the passband and falls off gradually toward the edges of the passband. It does have a significant advantage, it has a faster risetime than the other types of filters and hence is more appropriate for use with pulse inputs. It is also less subject to ringing

*The spelling varies considerably, depending on how you transliterate the Russian.

which often becomes a significant problem with sharp, steep sided filters. If you want to try better filters than the simple two section variety described earlier, by all means use the maximally linear phase characteristic. Detailed design procedures would be much too lengthy to go into at this time but an excellent summary and the necessary tables can be found in "Reference Data for Radio Engineers" *Fourth Edition*, published by I.T.&T. The information is *not* in the third edition.

A number of articles on filters have asserted that, since the objective was to recover from the two tones information in the form of 22 millisecond pulses, and since in the fastest possible case—successive mark space signals (reversals) this was in fact a square wave of about 23 cps.—and that you had to recover the third order products in order to reasonably reconstitute this square wave which was being transmitted. The argument then continued that since this involved both sidebands on each side of the center tone frequency, that the bandwidth of the filter had to be at least twice the third harmonic of 23 cps and that therefore the minimum bandwidth that could be used was of the order of 135 or 140 cycles. This argument is only valid if you have no provision for pulse reshaping following the discriminator.

Each audio tone may be considered as consisting of a carrier on the particular center frequency (2125 or 2975) which is modulated by a square wave. At the fastest reversal rate you have 22 millisecond pulses or a square wave of approximately 23 cycles, this is approximately what you have when RYRYRY . . . is being transmitted. The average modulation rate is lower than this, but this represents the maximum requirement of the system. This square wave produces the usual Fourier series of sidebands, thus you have the 2125 cycle carrier, the first order sidebands at 2125 ± 23 cycles, the third order sidebands at $2125 \pm 3 \times 23$ cycles, and all the rest of the odd order sidebands. The major portion of the energy is in the carrier and the first order sidebands, with decreasing amounts of energy in the higher order sidebands.

We can separate the input to the filter into three basic components: the tone carrier, noise (by which we mean stochastically distributed inputs), and interference (by which we mean signals with a coherent frequency distribution which may appear within the passband of the filter). When we narrow the bandpass of the filter we are affecting all three inputs: 1. We are discarding higher order sidebands of the desired signal; 2. We are decreasing the noise,



EVERYONE'S TALKING ABOUT

A NEW DC POWER SUPPLY... *the*

CONSERVATIVE RATINGS AT 13 VOLTS DC INPUT

800 V	250 MA
275 V	200 MA
0-90V	NEG. BIAS

OTHER TRANSISTORIZED CONVERTERS

ADCOM 500-500 WATTS at 1250 V
PLUS 300 V & BIAS

ADCOM 1000 - 1 KW at 2250 V
PLUS 300 V & BIAS

ADCOM 250AC AVAILABLE
FOR OPERATION FROM
115V 50/60 CYCLE

SEE YOUR NEAREST DEALER



only
\$125.

ADCOM 250 DC-DC TRANSISTORIZED CONVERTER

THE IDEAL SUPPLY FOR YOUR
FAVORITE MOBILE



QUALITY ASSURANCE

at

LOW COST

LINEAR SYSTEMS INC.

605 UNIVERSITY AVENUE - LOS GATOS, CALIFORNIA

and 3. We are decreasing the probability of receiving an interfering signal. The first mentioned effect is the price we pay for the advantages of the last two. When we go from a filter that passes the fifth order sidebands to one that passes only the third order sidebands we find we have decreased the noise to 60% of the former value and the probability of interference by the same amount, and since the loss in information in the fifth order sidebands is not this large we increase the signal to noise ratio and the efficiency of the system. Now if we decrease the filter from a bandwidth that passes the third order sidebands to that which passes only the first order sidebands we have decreased the noise by a factor of three, the probability of interference by the same amount, and the information we have lost is substantially less than this amount. Don't try to take it any further or you start losing ground. Note that the modulation rate is not normally the 23 cycle square wave, it actually varies from nearly zero to this figure, and with quite a number of ifs thrown in this represents the limit of a function. This is not to imply that you can't go further—there is a theorem in information theory that says you can transmit an infinite amount of information in an infinitely small bandwidth if you have an infinitely high signal to noise ratio. The last is what you don't have. Even to go to the limit indicated of a 46 cps bandpass which recovers only the first order sidebands would require perfect stability, excellent filters, and the best in signal reprocessing techniques.

Any terminal unit of reasonable design will,

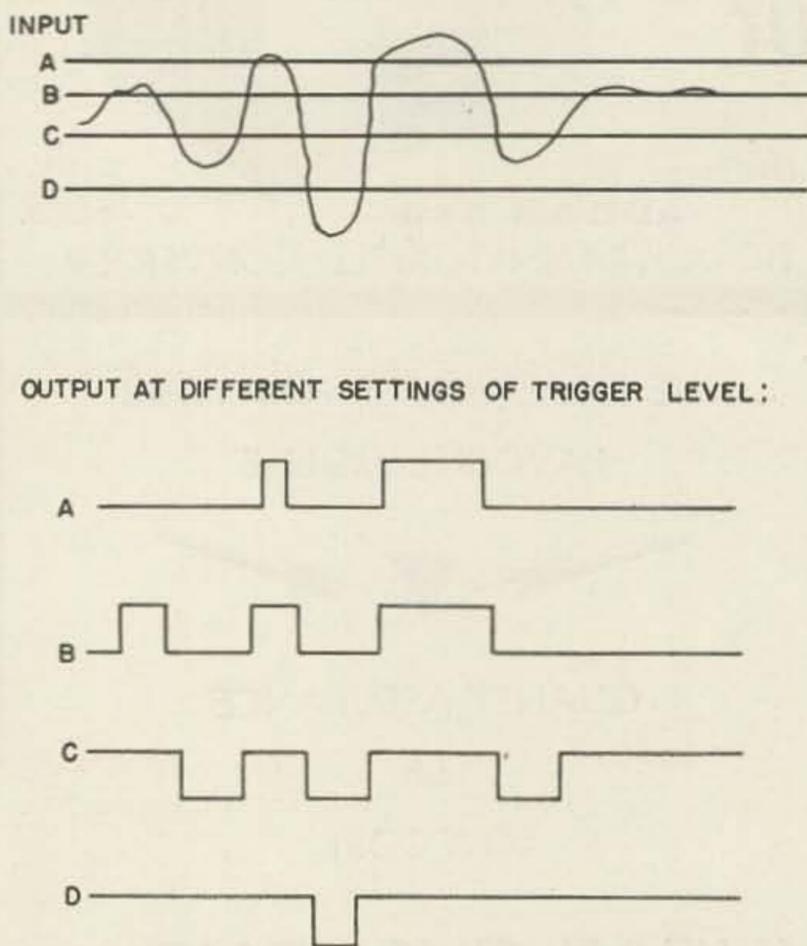



FIG. 3

in fact, incorporate some facility for pulse reshaping—perhaps the most common and elementary device is a relay. With inputs above a certain level this will be on and at inputs below a certain level it will be off, and if you feed low frequency sine wave input to it you will get a square wave out of it. There is in fact no requirement for a reasonably square wave input. It has the obvious disadvantage that the hysteresis or difference between pull in and drop out levels is too great and that the adjustments of the characteristics are usually mechanical and extremely difficult. Because it is a mechanical conversion device the speed at which it reacts is limited. Further it tends to stray from optimum adjustment over time and has contacts which generate a species of noise which is very difficult to eliminate.

The same object can be accomplished electronically, and it can be done in a fashion so that the action can be readily adjusted and the noise of mechanical contacts eliminated. Probably the simplest electronic means of reconstituting a square wave is to overdrive an amplifier that is fed by the degraded waveform. This technique has been widely used and while it gives relatively good square wave output it lacks flexibility, and it is possible with certain settings to get intermediate outputs which are neither on nor off. A better technique—which can be easily adjusted over a wide range and gives only on and off outputs—is the Schmitt trigger. These can be readily built with either tubes or transistors (although with this circuit the transistor version is simpler and easier to work with).

Fig. 3 gives an excellent illustration of the action of a Schmitt trigger when the trigger level is varied over the operating range. Here the positive direction corresponds to a mark signal and the negative direction to a space. Levels A, B, and D give misprints, while setting C gives a practically perfect letter F. I confess that when one draws illustrations one tends to stack the cards—but its function in actual practice is equally impressive. Note here that regardless of the input voltage wave shape that the output from the trigger is a perfect square wave. The filters do not have to deliver a reasonably square output—they merely have to separate the input signal into two channels and deliver the resulting outputs to the discriminator. The Schmitt trigger then electronically makes the decision as to whether a mark or a space is being transmitted. This decision is based on the relative amplitudes of the outputs of the two channels. The bias level setting compensates for continuous unwanted signals in either channel, or in the case of AFSK for variations in the levels of mark and space tones

WIN

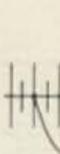this complete  **hy-gain**
ANTENNA SYSTEM

WITH 56 foot Spaulding Tower

WORTH OVER \$500.00
or one of 24 other valuable prizes

IN HY-GAIN'S
SECOND ANNUAL

Skyhook

CONTEST

Contest open to any Licensed Amateur* on Planet Earth. All entries must be postmarked no later than 23:30 GMT, 31 December, 1962.

NOTHING TO BUY ... Here's all you have to do — Simply pick up an Official Skyhook II Entry Blank from your favorite Hy-Gain distributor and, in twenty-five words or less, complete the following statement: "If I were the New Product Manager of Hy-Gain, I'd ask my engineering department to develop an antenna design that would (25 words or less)." Send your entry to Hy-Gain Antenna Products, NE Highway 6 and Stevens Creek, Lincoln, Nebraska. All entries will be judged on the contribution the suggestion offered will make toward universally improving reception or transmission and will remain the property of Hy-Gain Antenna Products, Inc.

FIRST PRIZE.... 3.5-500 MC including RBX-1 Rotator and Directional Indicator, DS-1 Discone with range of 50 thru 500 mc., TH-4 Tribander, 402-B 40 Meter Monobander, 2BDP Multiband Doublet and 56' Spaulding Tower.

2nd PRIZE — DB-24 Duobander, 20-40 meters


3rd PRIZE — 18HT All Band Vertical


4th PRIZE — TH-4 Thunderbird Tribander


5th PRIZE — TH-3 Thunderbird Tribander

*Sorry, we must exclude entries from Cities, States or Countries where contests are prohibited by law.

BE A WINNER! Pick up an Official Entry Blank TODAY and submit your suggestion NOW to:

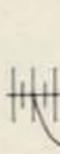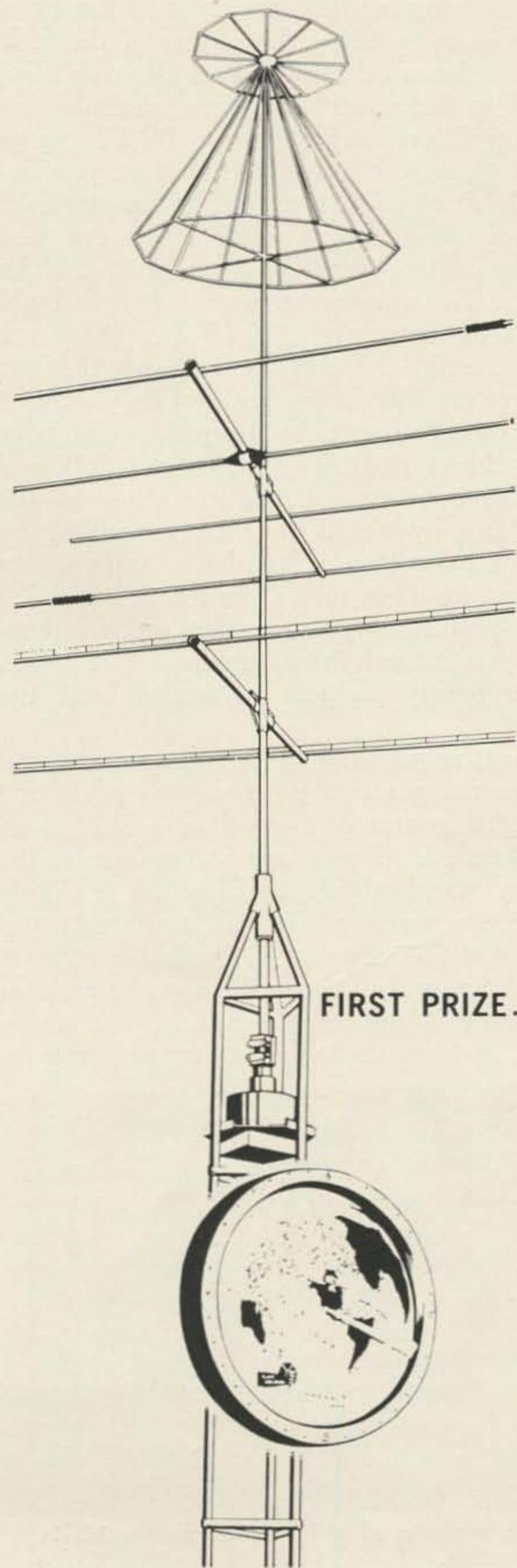 **hy-gain** antenna products
8405 NE Highway 6
Lincoln, Nebraska



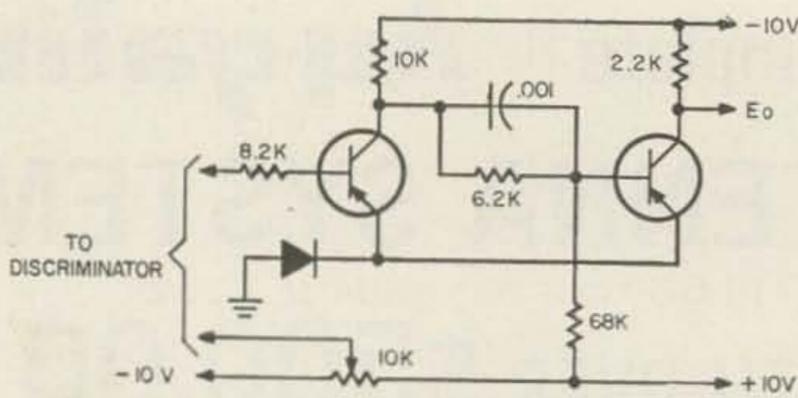

NOTE:
 1. DIODE: HOFFMAN HB-1
 2. TRANSISTORS 2N2374 (HIGH BETA PNP)

FIG. 4

being transmitted. (This varies more widely than you would suspect, having these within 25% is better than par for the course.)


Fig. 4 gives the circuit of a typical transistor Schmitt trigger. The trigger level without the bias potentiometer is about $-.8$ volts, but with the variable bias this point may be varied over a ± 10 volt range. Provision should be made in the terminal unit to insure that the discriminator output voltage range does not exceed this 20 volt peak to peak range. In actual practice there is a small amount of hysteresis in the circuit, the output flips to the on condition when the input exceeds $-.83$ volts and turns off when the input falls below $-.80$ volts. This difference of $.03$ volts is of no import when compared with the 20 volt range of the input from the discriminator. Compare this with the typical relay which has a 2:1 range between pull in and fall out.

It should be noted that even if no explicit restoration technique is used in the terminal unit, you will get it in the printer as a result of the action of the armature of the selector magnet of the machine. This is the poorest of all techniques, adjustment will be critical, and the range of the machine will be very narrow. This function should be provided in the terminal unit, should have minimum hysteresis, and should have as wide a range of adjustment as possible.


The next step, once you decide on the filter you want, would logically be to tune up the filter. But for those of you who don't have counters available it might be best to turn your attention to some sort of frequency standard. If tuning up the filter is going to be a one shot affair the most reasonable procedure is to use the standard audio tones broadcast by WWV or one of the other standard frequency stations, along with an oscilloscope to give you the appropriate Lissajou patterns and after your audio signal generator has warmed up completely calibrate it as accurately as possible in the 2000-2250 and 2850-3100 cycle regions. For those who desire greater precision than

this or plan to do an appreciable amount of work, either borrow from one of the local gang or build a standard for the common RTTY frequencies. There are two types of standards in use, both of which do an admirable job. The first and most common—although not the easiest to build is the tuning fork standard. This uses a tuning fork as a resonant element and normally operates on a frequency of 425 cycles. These are made with standard 435 cycle tuning forks which have been lowered to 425 cycles either by loading the ends of the tynes with solder or by filing the crotch of the fork. There have been a number of articles published on building these and they serve admirably for tuning up filters and checking RTTY equipment. With an oscilloscope they give you 5:1 and 7:1 Lissajou patterns with the standard 2125 and 2975 frequencies. They are also handy for setting the 850 cycle shift in FSK operation. The alternative approach is to build a crystal oscillator for 446.25 kc (there are standard surplus FT-241 crystal units that are approxiamtely this frequency and they may be easily brought to precise frequency by edge grinding the crystal). The oscillator is followed by two successive multivibrator dividers—the first dividing by 6 and the second dividing by 5. The end result is a standard frequency of 14,875 cycles. This, too, gives the 5:1 and 7:1 Lissajou patterns with the standard frequencies. If you intend to do much RTTY work, they are handy gadgets to have about the shack.

The next requirement is a voltage indicator, if you are using a counter or a well calibrated audio signal generator a good ac VTVM is all that is needed. If you are using one of the frequency standards an oscilloscope is highly desirable since you can check amplitude and frequency at the same time. The basic set up is to feed the output of the audio signal generator through an isolating resistor to the circuit under test, and in turn, through another isolating re-

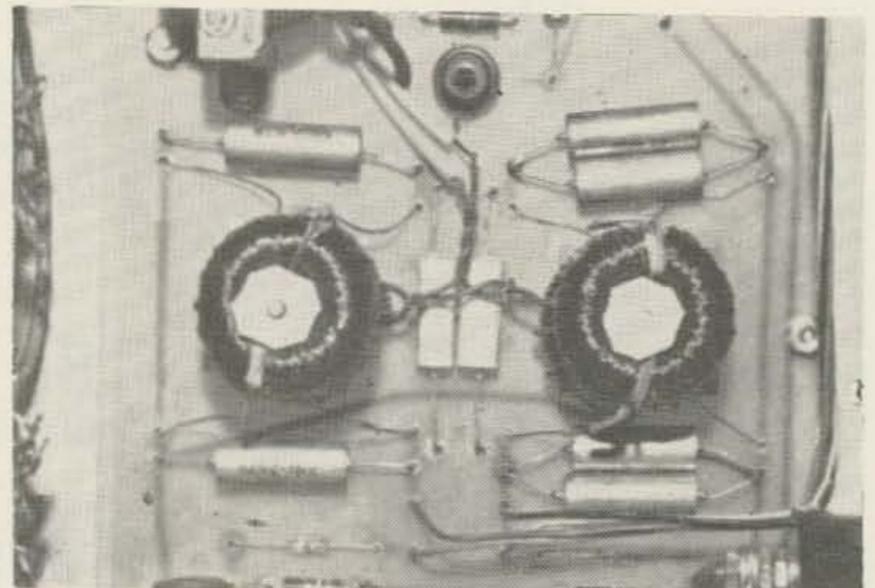

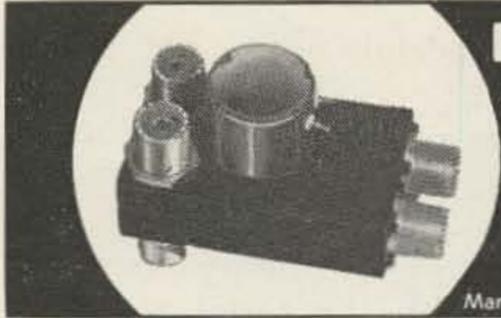Here is a photo of a TV using two toroids in each section.



DOW-KEY'S DK2-60

DPDT r.f. SWITCH

DK2-60 with UHF Connectors, each \$19

Manufactured and Guaranteed by

DOW-KEY CO., Thief River Falls, Minn.

For Switching 2 Coaxial Lines Simultaneously!

Freq. 0 to 500 mc; Power Rating to 1 kw;
VSWR, less than 1.15 to 1 from 0 to 500mc;
Standard coil voltage.....and other r.f.
Connectors available.

sistor feed the Y axis of the oscilloscope. (See Fig. 5). The two resistors should be 1 megohm or higher. The standard signal generator should be fed to the X axis of the scope to permit observation of the Lissajou patterns for calibration purposes. With this set up you tune the circuit for resonance (which is indicated by maximum amplitude) at the proper frequency (which is indicated by the Lissajou patterns).

Tuning the circuits to resonance is naturally the basic process of varying L or C. With the usual 88 mhy toroids there is usually not much variation from one unit to the next—they seem to be wound to relatively tight tolerances. The easiest method by far is to have a large number of capacitors of approximately the correct value and just keep trying different ones until you find the right value. The typical spread on capacitors is fairly wide and the selection process is fairly simple. A similar technique which requires fewer capacitors is to use two capacitors to get a given value—the .06 mfd that is needed to tune up the 2125 cycle unit may be obtained from an .01 and an .06 in parallel, and resonance can be achieved from a relatively modest supply of each by successively trying various combinations of the two. Of course, if a given capacitor falls slightly below the desired capacitance a small capacitor can be added for precise resonance. If your stock of capacitors is small, the easiest adjustment is in the number of turns on the toroid. It is easy to add a few turns or peel off a few to tune the circuit to resonance.

A simple two toroid filter and approximate values were given in Fig. 2. There are two basic ways to attack this problem. The first, and most elegant, is to tune both L_1C_1 and L_2C_2 to a frequency of 100 cycles (i.e., half the desired bandwidth of the filter) higher than the desired center frequency. In this case the frequencies would be 2225 cycles for the pair intended for the mark filter and 3075 cycles for the pair intended for the space filter. If you have a 425 fork standard you will find it quite convenient to use a 21:4 Lissajou pattern, which gives you a frequency $425/4$ or 106 cycles high. On the space filter use a 29:4 Lissajou. Then assemble the filter and try successive values of coupling capacitors—the correct value will extend the passband of the filter to the desired limit on the lower side of the cen-

ter frequency. The larger the value of coupling capacitor the wider the bandpass of the filter. For narrower filters, the pairs are initially tuned to frequencies closer to the center frequency and the coupling capacitors are not as large. An excellent approximation of the coupling capacitor can be obtained by shunting a single LC circuit with the coupling capacitor—the circuit should then tune to the center frequency.

The other method is to select the value of the coupling capacitor (C_c in the table) and tune each pair individually to the center frequency. Thus you will first resonate $L_1(C_1+C_c)$ to 2125 cycles, then remove C_c from this circuit and resonate $L_2(C_1+C_c)$ to 2125 cycles, and finally assemble the filter in the final configuration. This is easier than the first method and only requires the use of the 2125 cycle reference frequency rather than shuttling back and forth between the two sides of the center frequency. This procedure should best be followed with the filter in place or at least with the operating load circuit connected since when it is actually installed there will normally be added capacitance across at least the last of the two toroids. Merely shorting out the toroid not being tuned will place the coupling capacitor across the appropriate resonant circuit.

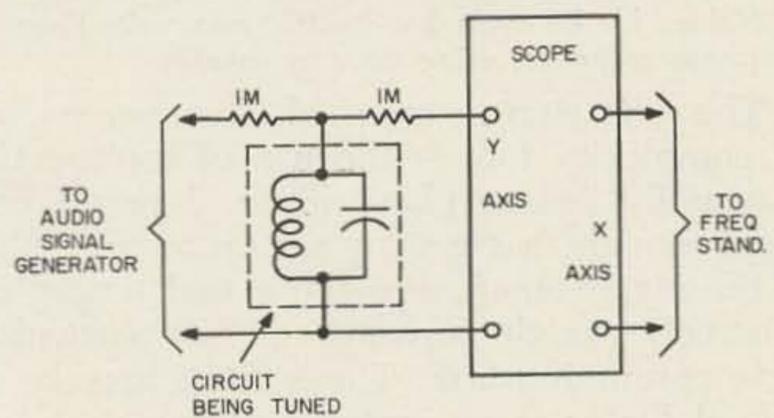


FIG. 5

You will quite probably find when you have finished the tuning that the pass band is not flat—this will depend on the loading of the filter. The response can be smoothed out by adding a resistor across the final toroid. Do not do this until it is installed in the operating circuit, however, since this may provide sufficient loading. If you still have a double humped response add a resistance of whatever value is required to smooth out the response. This value of resistance will not be the same for both the mark and the space filters, since the loads will be approximately the same for the two while

their impedances vary by a factor of about 2:1.

The values given are for the standard 88 mhy units but if you have other toroids you can merely adjust the capacitance values by the appropriate ratios and use the same tuning procedures. If you have different inductance toroids you should use the larger inductances in the 2125 cycle filter and the smaller inductances in the 2975 cycle filter.

The input to the filter is easily accomplished by winding turns on the toroids. The output section preceding the filter should use a plate to voice coil or collector to voice coil transformer—the voice coil winding provides matching to the links wound on the toroids. The number of turns on the links are adjusted to give equal output from each of the two filters. This adjustment, while not difficult, is important since the outputs of the two filters are so arranged that when there is an interfering signal or noise with equal amplitude in both channels the resultant outputs cancel. We found 9 turns on the 2125 filter and 5 turns on the 2975 filter gave these desired results, but you should check the performance before you consider the job complete.

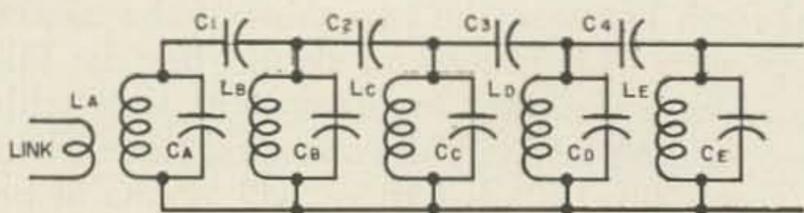


FIG. 6

freq.	C_1	C_2	C_3	C_4	C_{n-e} (Approx.)
2125	.0074	.0037	.0026	.002	.06
2975	.0025	.00125	.0009	.0007	.03

Values for 85 cycle bandwidth, maximally linear phase response, using 88 mhy toroids

The next step in order of effectiveness, and of complexity too, is the use of multisection, maximally linear phase filters. I might comment though that getting set up to tune filters is the major chore, and the actual tuning is a relatively straight forward and not particularly time consuming task. These filters may be designed for as many sections as you wish, and for whatever bandwidth is desired. The one we built up used five toroids in each channel and the basic circuit is given in Fig. 6. The bandwidth chosen, 85 cycles, is compromise between the requirements for optimum signal to noise ratio and interference rejection capabilities, and the necessity of accommodating a moderate order of drift and not have hypercritical tuning requirements. The performance is excellent, particularly when the going gets rough. The skirt selectivity is impressive indeed and in practice the tuning is not particularly difficult. The tune up procedure is the same as that outlined in the latter part of the discussion of



the procedure for two section filters. The values of C_1, C_2, C_3, C_4 are not critical and are either ordinary 10% tolerance units or combinations of them. Mount and wire up the filter with the toroids and coupling capacitors in place. For a convenient mounting, ordinary terminal boards serve nicely with the terminal points providing mountings for the capacitors and the toroids mounted on alternate sides of the board. One note of caution on mounting toroids in general—don't have them completely surrounded by metal—it is equivalent to a shorted turn and the performance (if you can discern any!) is very poor. To tune up the first section, short the second section and tune the first using the same set up described before—either by varying the capacitance or adjusting the turns on the toroid. When this is completed remove the short from the second section, short the first and the third section and proceed to tune up the second section. The successive sections are then tuned up in precisely the same manner, always making sure that the short has been removed from the section you are tuning and that the two adjacent sections are shorted. For the final section, which when the filter is operating will be connected to additional load—it is best to tune this after the unit is connected to the terminal unit. The coupling is accomplished in precisely the same way as before—in fact, you can try the same number of turns suggested before as a starting point. Although the values given here are for 88 mhy toroids, other values can be used by making the proportional changes in capacitance. This assumes that the Q of the toroids you use is not too far off from those of the 88 mhy units; the design of the linear phase shift filters is based on the Q of the toroids as well as the frequency and bandwidth of the filters.

A further point to note is implicit in the tune up procedure. C_a has C_1 in parallel for resonance, C_b has C_1 and C_2 in parallel, and so on—hence the values of capacitance will not be the same for C_a through C_e . The actual values may readily be computed since you need .064 mfd to resonate 88 mhy at 2125 cps and .033 mfd to resonate 88 mhy at 2975 cps. Thus the actual values will run under the approximate values given. This has the merit of using different values for each capacitor—the probability of your having a quantity of identical value capacitors is relatively small. Some mention should also be made for those few of you who will actually consult the references given on these filters. The standard design lists a resistor across L_a to degrade the Q of this section for optimum phase performance. In actual practice the loading by the input circuit takes care

SINGLE
SIDEBAND

SBT-1K

TRANSMITTER SERIES

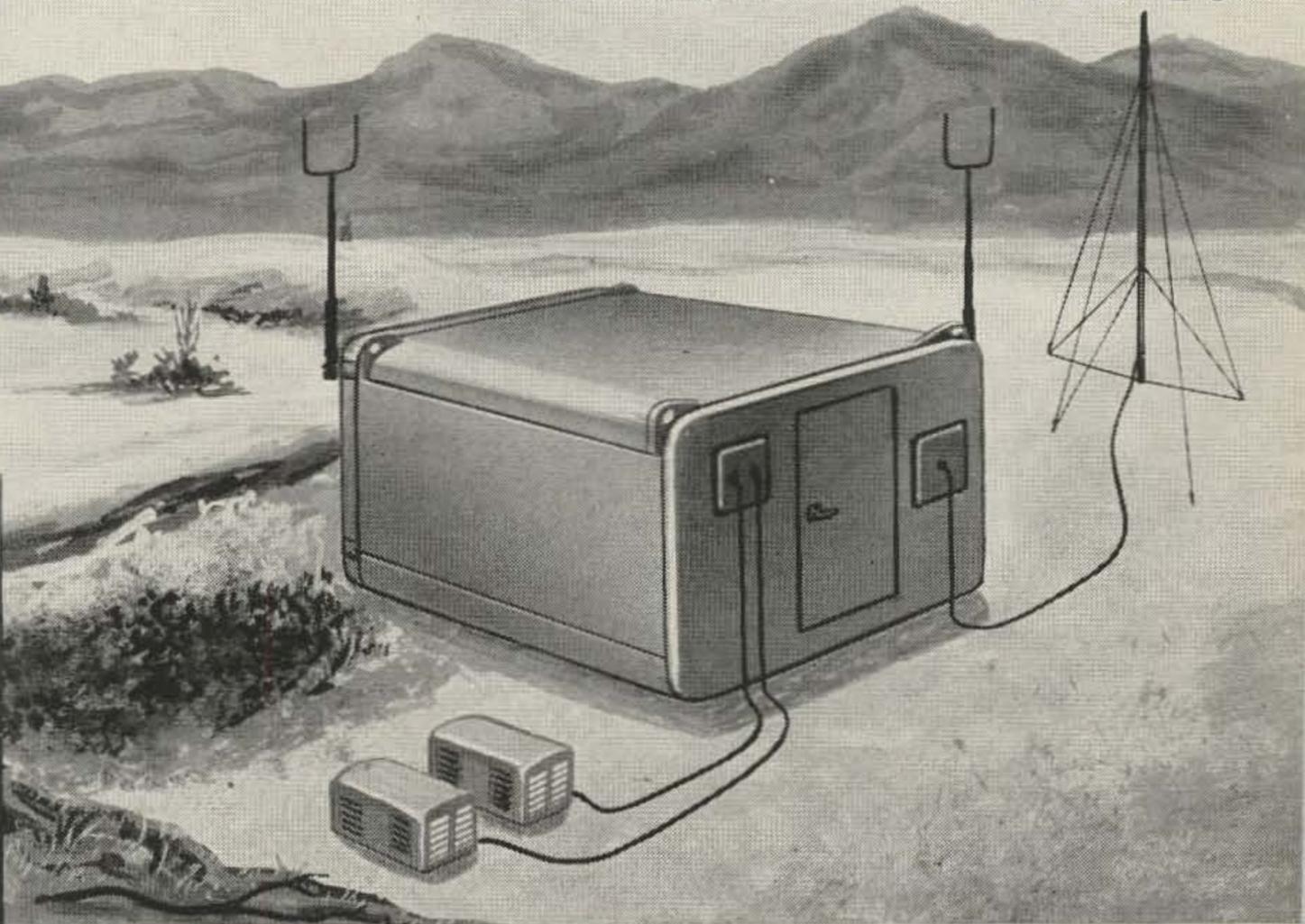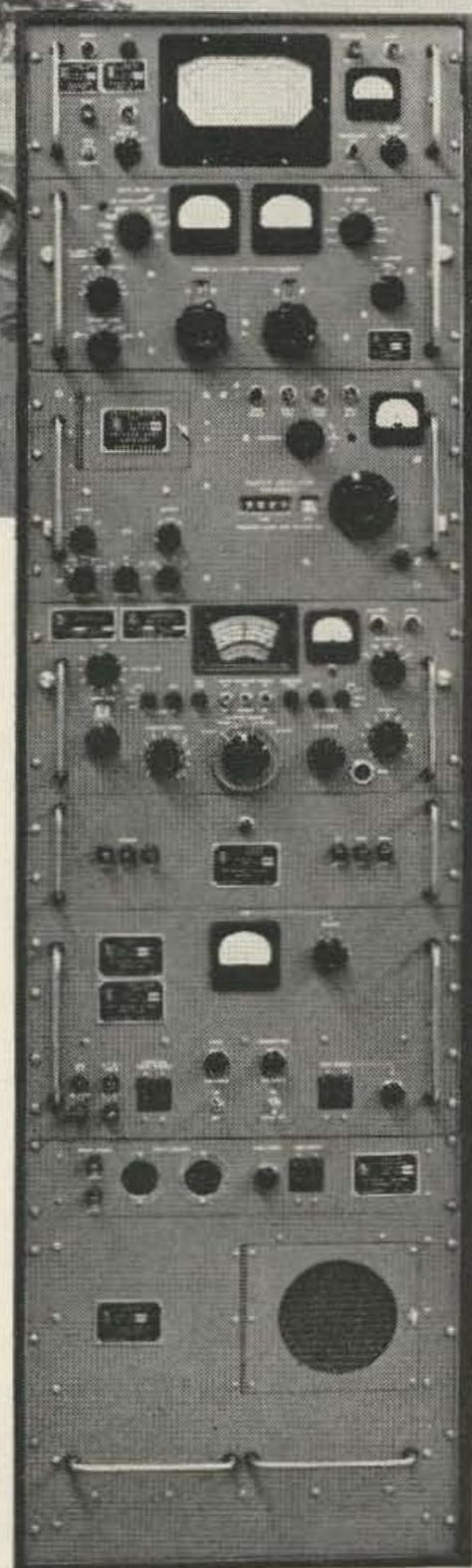

AM · FSK · SSB · ISB · CW · FAX

AN/FRT-53

AN/FRT-56

AN/FRT-57

TMC Models SBT-1K series of transmitters provide conservatively rated 1 kw PEP output in SSB modes, with Signal to Distortion ratio of 40db, and 1 kw average power in conventional communication modes within the frequency range of 2 to 32 Mcs.

Stabilities of 1 part in 10^6 to synthesized accuracy of 1 part in 10^8 , with 100 cps incremental tuning, are featured in this series of transmitters.

The TMC SBT-1K series of transmitters are attractively housed in semi-pressurized cabinets with many customer options for wide band or narrow band audio, antenna tuners, base mount or rugged MIL accepted shipboard mounts for all mobile applications.


For information on this transmitter series, request SSB number 1001.



THE TECHNICAL MATERIEL CORPORATION

and Subsidiaries

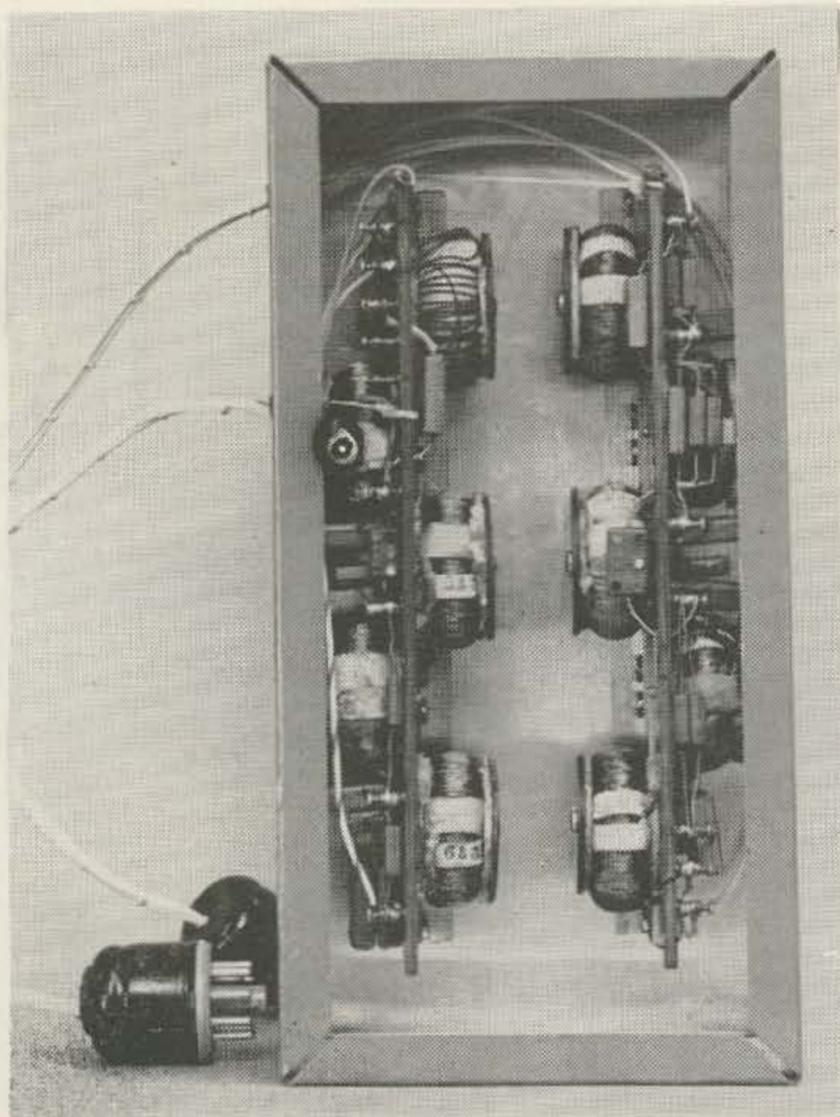OTTAWA, CANADA • ALEXANDRIA, VA. • GARLAND, TEXAS • LA MESA, CALIF. • POMPANO BEACH, FLA. • LUZERN, SWITZERLAND



A five section maximally linear phase filter. This does not use 88 mhy toroids but the techniques are identical and the L/C ratios are appropriately scaled.

of this problem handily, but if there is any doubt as to whether you have enough turns on the input link—by all means err on the side of overcoupling.

The filters were made on the terminal boards mentioned before, and after the filters were tuned they were both mounted beneath a 5x10x3 chassis with 4 leads 10 inches long coming from each filter to an octal plug. By removing the regular two section filters (which were mounted in Vector C-12 cans with octal bases) and plugging in the two octal plugs we are able to convert from the broad to the sharp filters in a matter of seconds. Since our terminal unit is built on a 5x10x3 chassis also, we merely place the t.u. on top of the filter and have a very compact unit. (See Photo).

You will find the performance of this filter decidedly better than the simple two toroid filter. The passband is adequate for good performance and the unit has high selectivity without the attendant ringing of other designs. If you use the conventional scope tuning indicator with the output of the mark channel to the horizontal plates of the scope, and the space channel to the vertical plates of the scope, you will note that the lines are considerably sharper with this filter. In addition, since the passband is not flat but is slightly peaked in the center

(the 85 cycle bandwidth figure here specifies the width to the -3 db points) the tuning is actually easier in some respects since there is no ambiguity in the setting. However, don't throw away your old filters, there will be times when you need them—particularly when the other station is using only a rough approximation of 850 cycle shift. The ideal arrangement would be one in which you could merely switch from the two section to the five section filter—however, in actual practice we have found the plug-in technique quite adequate.

We have mentioned short shift a number of times and you might wonder why—if you can in any case build filters with bandwidths on mark and space, respectively, equal in width to those used on short shift signals—there should be any advantage in using short shift. The most significant advantage in short shift is a result of the propagation characteristics of electromagnetic waves; the closer two frequencies are to one another, the smaller the probability of selective fading. Since the basic method of detecting the RTTY information is to make a decision based on the relative signal in the two channels, it is desirable to have a minimum amount of selective fading. Another advantage for many is the possibility of supplementing the selectivity of the terminal unit with the more selective *if* filters which are found in the better ham receivers. A further advantage is the possibility, with the more compact signal that results, of avoiding certain types of interference.

An advantage of the plug-in technique used for the filters we have mentioned is that you can build up one extra section for short shifts. If you have filters for 2125 and 2975 and are interested in short shift, say 170 cps, you have only to build a unit for 2295 cps and use it in conjunction with the 2125 cps unit for this short shift work. In addition you may also want to build a unit for 425 cps shift for copying a number of the commercial stations using that shift.

The first filter is the hard one—once you've gone through the procedure the rest are easy and the returns in terms of actual on-the-air performance are impressive. If more attention is turned to putting together a satisfactory terminal unit with adequate filters you will get much more effective and much more enjoyable RTTY operation.

For the adventurous—and for those who don't like graphs, mathematics, and such, I have included Figs. 7, 8 and 9. These give design data for 3, 4 and 5 section maximally linear phase shift filters, with a choice of bandwidths which you can use according to your receiver stability and personal tastes and inclinations.

I suspect it will save a number of inquiries and make life a little easier for those who want to strike off on their own. I might comment that one of the reasons both the maximally linear phase shift filters and the Chebyshev filters were not more widely used before was the mathematics involved. More recently tables have been compiled which make the procedures far easier and in addition, the advent of electronic computers that make formerly impossible tasks merely the subject of a modest amount of machine time have changed these from the realm of interesting theoretical possibilities or the objects of arduous cut and try procedures into relatively common everyday items.

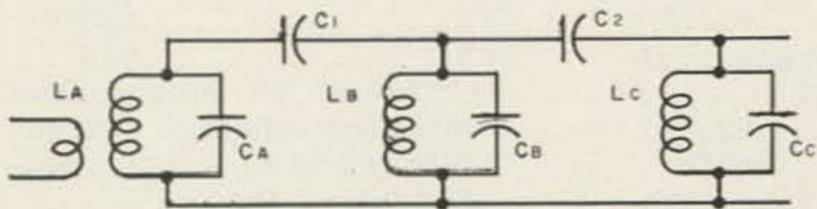


FIG. 7

Width	Freq.	C ₁	C ₂	C _{a-c}
60	2125	.0027	.0014	.06
60	2975	.00082	.00048	.03
85	2125	.0043	.0021	.06
85	2975	.0014	.0008	.03
120	2125	.0062	.003	.06
120	2975	.0021	.0011	.03

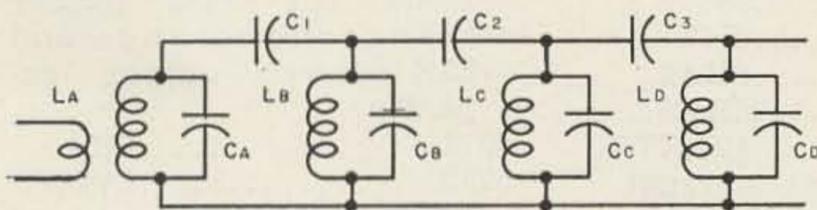


FIG. 8

Width	Freq.	C ₁	C ₂	C ₃	C _{a-d}
60	2125	.0038	.0020	.0014	.06
60	2975	.0011	.00064	.0005	.03
85	2125	.0058	.0029	.0020	.06
85	2975	.00195	.0010	.0007	.03
120	2125	.0087	.0042	.0029	.06
120	2975	.0029	.0015	.00105	.03

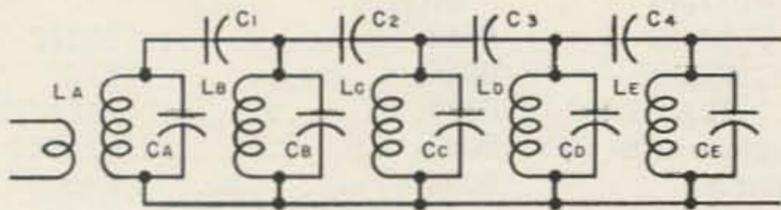


FIG. 9

Width	Freq.	C ₁	C ₂	C ₃	C ₄	C _{a-e}
60	2125	.0049	.0024	.0018	.0014	.06
60	2975	.0015	.0008	.0006	.0005	.03
85	2125	.0074	.0037	.0026	.002	.06
85	2975	.0025	.00125	.0009	.0007	.03
120	2125	.0113	.0055	.0038	.0029	.06
120	2975	.0039	.0019	.0014	.0010	.03

... W3TUZ

CLUB SUBSCRIPTIONS: \$3.00 per year in groups of five or more subscriptions at one time.

"BIG MIKE"

MARK I MICROPHONE

**MORE MICROPHONE
THAN YOU'VE EVER
HAD BEFORE!!**



NOW MATCH YOUR MIKE
TO YOUR NEEDS
INCREASE RANGE,
MODULATION AND
AUDIO QUALITY

Mark I "BIG MIKE" Microphone:
Net, complete with Transistor
Amplifier, Cable, Clip and
Battery Compartment (less batteries)

\$29⁹⁵

- MORE THAN -39 DB OUTPUT!
- VARIABLE OUTPUT CONTROL!
- VARIABLE TONE CONTROL!
- MINIATURE TRANSISTOR AMPLIFIER!
- RUGGED, FUNCTIONAL DESIGN!
- SQUEEZE-TO-TALK SWITCH!

Order from your distributor,
dealer or:

instruments and communications, inc.
33 Danbury Road Wilton, Connecticut



Premium Tube Replacement Guide

Roy Pafenberg W4WKM

HERE is a seemingly endless series of "four digit" tube types designed as "premium," "reliable-ized" and "rugged-ized" replacements for the more common types. The listing presented here is compiled from many sources and is designed for the amateur. That is, it is a "one way" list showing which of the more common tubes will plug into those "four digit" holes in surplus equipment and pointing out the more obvious uses for the "four digit"

tubes that are flooding the surplus market.

Although care has been taken in the preparation of this listing, much of the source material could not be verified from available references. Also, caution must be exercised in using the list. Minor differences, both electrical and mechanical, exist between many of the types listed. Therefore, in critical applications, any substitution should be made on a "try and see" basis.

<i>Premium Tube</i>	<i>Prototype</i>			
1201.....	7E5	5692.....	6SN7	5915.....
1221.....	6C6	(5692 plate dissipation rating is 30% less)		5920.....
1267.....	OA4G	5693.....	6SJ7	(5920 is 3/8" longer, has 10% lower heater current rating and 34% lower amplification factor)
1291.....	3B7	5694.....	6N7	5930.....
1293.....	1LE3	(5694 has separate cathode connections)		(5930 has .3" greater base diameter)
1294.....	1R4	5719.....	6AD4	5931.....
1299.....	3D6	(6AD4 transconductance is 17% higher and grid to plate capacitance is 12% lower)		5932.....
1603.....	6C6	5721.....	6AU6	5933.....
1609.....	6J7	5725.....	6AS6	(5933 has .3" greater base diameter)
1612.....	6L7	5726.....	6AL5	5961.....
1613.....	6F6	5727.....	2D21	5964.....
1614.....	6L6	5731.....	955	(5964 has 14% higher transconductance and 20% lower output capacity)
1620.....	6L7	5732.....	6K7	5977.....
1621.....	6F6	5749.....	6BA6	5992.....
1622.....	6L6	5750.....	6BE6	(6V6GT filament current rating is 25% lower)
1629.....	6E5	5751.....	12AX7	5993.....
(1629 is 12.6 volt filament version of 6E5)		(12AX7 filament current rating is 14% lower, transconductance is 33% higher and amplification factor is 43% higher)		6005.....
1631.....	6L6	5755.....	6SU7	6006.....
(1631 is 12.6 volt filament version of 6L6)		5764.....	2C37	6021.....
1632.....	12L6GT	5765.....	2C37	(6BF7 is 1/8" longer and has lower transconductance)
1634.....	12SC7	(Electrode rings differ)		6028.....
1635.....	6N7	5766.....	2C37	(20 volt heater version of 6AK5)
(6N7 filament current is 33% higher and plate load resistance is 33% lower)		(Electrode rings differ)		6042.....
1644.....	12L8GT	5767.....	2C37	6045.....
1852.....	6AC7	(Electrode rings differ)		6046.....
1853.....	6AB7	5784.....	6AS6	6046.....
5591.....	6AK5	5812.....	2E30	25L6GT
(6AK5 filament current is 16.6% higher)		5814.....	12AU7	6057.....
5602.....	12AT7	(5814 has 16% higher filament current rating)		6058.....
5608.....	6AK5	5824.....	25B6G	(6058 is 3/8" longer and has 27% higher voltage ratings)
5651.....	OA3	5838.....	6X5GT	6059.....
5654.....	6AK5	5844.....	6J6	6060.....
5659.....	12A6	(5844 has 33% lower filament current rating, 26% lower amplification factor and 30% lower transconductance)		12AT7
5660.....	12C8			(12AT7 interelectrode capacitance is higher)
(12C8 transconductance and screen voltage rating are 25% higher)		5852.....	6X5GT	6061.....
5661.....	12SK7	5871.....	6V6GT	6063.....
5670.....	2C51	5873.....	12AU7	6064.....
(2C51 filament current rating is 14% lower)		5881.....	6L6WGB	6065.....
5679.....	7A6	5910.....	1T4	(6065 has 33% greater heater current rating and half the Gm of 6BH6)
(5679 has added filament center tap)		(1T4 plate and screen ratings are 18% lower)		6066.....
5691.....	6SL7			6AT6
(5691 has .6 A heater and plate dissipation rating is slightly less)				



BUY THE FINEST TOWER MADE — BUY TRI-EX!
THERE IS A TRI-EX TOWER TO FIT
YOUR ANTENNA REQUIREMENTS






NOW! GUY SAFELY — FROM THE BOTTOM — UP!

AND REMEMBER —

A GUYED TOWER WILL CARRY THE REALLY BIG ANTENNAS.

Now you can avoid the hazard of raising — then guying an antenna tower. With TRI-EX guy-as-you-go towers, you guy-off one section at a time, from the bottom-up, as the tower is raised! Here is how it works: *First, all sections but the bottom section (which is guyed before you start) are raised nested together. The second section is then guyed off and the rest are raised nested, etc. until the tower is all the way up.*

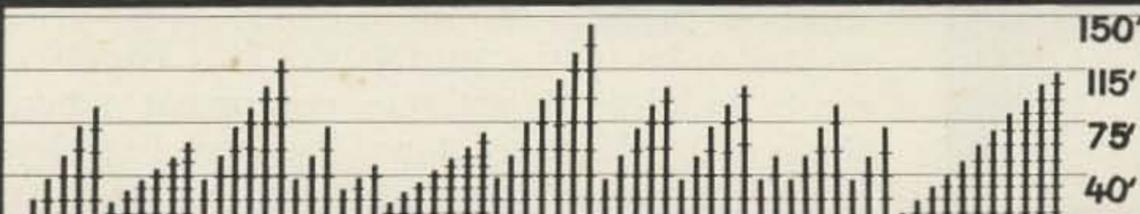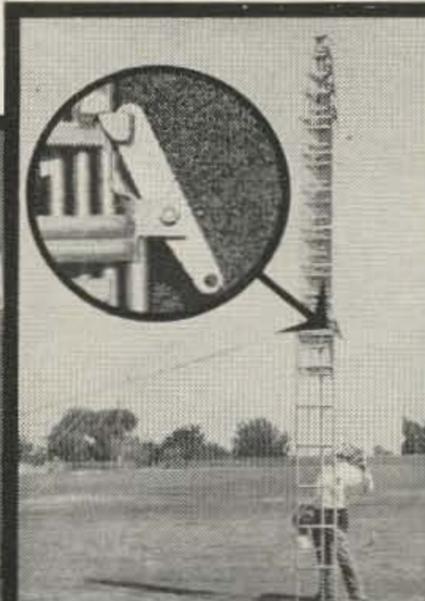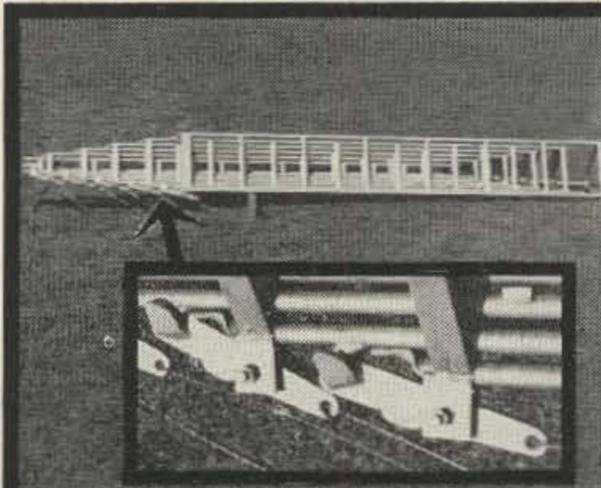

SEND FOR THE NEW
TRI-EX ANTENNA TOWER
SELECTOR CHART

TRI-EX TOWER CORPORATION / 127 EAST INYO STREET / TULARE / CALIFORNIA / MU 6-3411

(Maximum rating of 6AT6 is 22% lower)	6132.....6CH6	plate dissipation and 160% greater Gm)
6067.....12AU7	6134.....6AC7	6355.....6AF6
6072.....12AY7 (12AY7 heater current is 14% lower and interelectrode capacitance is 6% lower)	6135.....6C4 (6135 has higher heater current)	6384.....6AR6
6073.....OA2	6136.....6AU6	6385.....2C51
6074.....OB2	6137.....6SK7	6485.....6AH6
6080.....6AS7G	6145.....7AD7 (7AD7 plate voltage rating is 100% higher and transconductance is 5% lower)	6626.....OA2
6082.....6AS7G (6082 is 26.5 volt heater version of 6AS7G)	6169.....7F8	6627.....OB2
6085.....12AU7 (6085 has 100% higher heater current, 80% higher transconductance and 77% higher amplification factor)	6180.....6SN7	6660.....6BA6 (6660 is 1/4" longer)
6087.....5Y3GT	6185.....2C51	6661.....6BH6
6094.....6AQ5	6186.....6AG5	6662.....6BJ6
6095.....6AQ5	6187.....6AS6	6663.....6AL5
6096.....6AK5	6188.....6SU7	6667.....6CL6
6097.....6AL5	6189.....12AU7	6669.....6AQ5
6098.....6AR6	6197.....6CL6	6678.....6U8
6099.....6J6 (6099 has balanced plate currents)	6201.....12AT7 (6201 amplification factor is 10% higher)	6679.....12AT7 (6679 has 10% greater amplification factor)
6100.....6C4 (6100 is 3/8" higher and has 25% higher interelectrode capacitance)	6202.....6X4 (6X4 has 40% higher output rating)	6680.....12AU7
6101.....6J6	6215.....1B3GT	6681.....12AX7
6106.....5Y3GT	6265.....6BH6 (6BH6 heater current is 14% lower and plate resistance is 40% higher)	6830.....OA2
6113.....6SL7GT	6268.....4C35	6831.....OB2
6118.....6Q7	6277.....3B28	6922.....6BQ7 6BK7
	6279.....5C22	(Reliable substitute but not directly interchangeable)
	6288.....816	7000.....6J7
	6336.....6AS7G (6336 has 230% greater	7184.....6V6
		7193.....2C22
		7700.....6C6
		7752.....6AS6
		7755.....6AJ5
		7758.....6AR6
		8016.....1B3GT
		... W4WKM

40 FT. CRANK-UP TOWER

At

68 MPH

*At 40 Feet

USING A TRI-BAND
10-15-20 METER BEAM

Assembled Weight—20 lbs.
Wind Surface Area—4.9 sq. ft.
Wind Load—86 lbs.
Maximum Element Length—26'8"
Boom Length—12'
Turning Radius—14.9'

OR

148 MPH

with your Tri-Bander at 25'



*Certified by Reg. Prof. Eng.

\$119.50

Model 40-1

F. O. B.

WITH HEAD MOUNT PLANT

BRACKET MTG. KIT \$9.50

Tilts over on a heavy base plate for access to motor and array.

Horizontal bracing throughout.

Available from your local distributor, or direct from manufacturer.

**SUPREME
ELECTRONICS
INC.**
FRONT & MAIN STS.
UPLAND, PENNA.


Mike Versatility

Would you like to be able to use either a carbon or a crystal mike in the same speech amplifier? This might come in very handy in equipment used in both mobile and fixed service. The secret of this versatile operation lies in the cathode follower configuration. For carbon mike service the control grid is grounded and the mike lies between cathode and ground. In crystal mike operation the cathode is grounded and the grid is operated in the standard manner.

There are several methods of accomplishing the switching required to bring about this small miracle, the simplest of which is shown in Fig. 1. This circuit employs two closed circuit phone jacks, one in the cathode and one in the grid. For operation, either a carbon mike is plugged in the cathode jack, or a crystal mike in the grid jack. This circuit is most useful in homebrew equipment where there is no shortage of panel space. Fig. 2 is slightly more sophisticated; here a single three circuit jack is used, with switching done in the plug. This circuit is of advantage where space is at a premium.

Both circuits have been used in assorted speech amplifiers with a great deal of success.

... WA2AKT

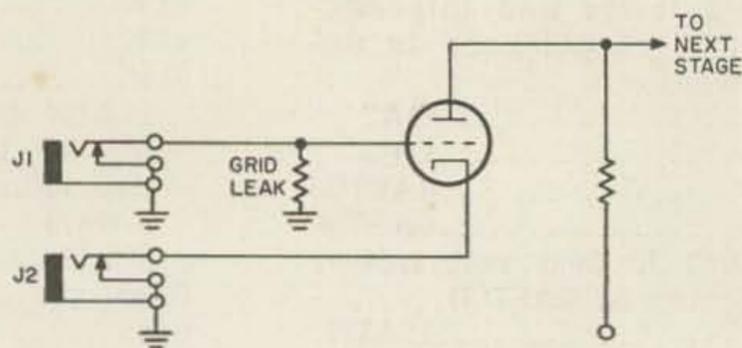

J1, J2 - NORMALLY CLOSED PHONE JACKS CIRCUIT.

FIG. 1

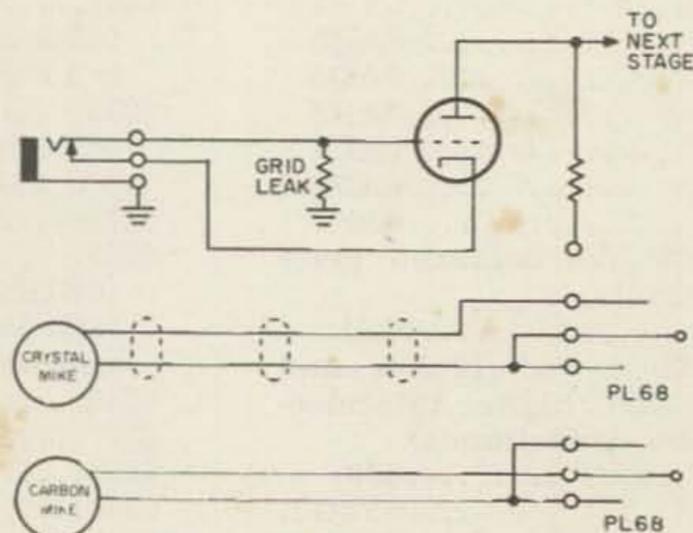


FIG. 2




Supreme SIX METER *SSB Transmitter*

- Using The McCoy 32B1 Silver Sentinel Crystal Filter
- 75 Watts PEP Input, 6146 Final
- USB - LSB - CW - AM Operation with Carrier injection
- 7360 Balanced Modulator
- Unwanted Side Band Suppression better than 40 db.
- Carrier Suppression better than 50 db.
- Size—Width 12" Height 6½" Depth 7½" Weight 7¼ lbs.

Model SSB-6 \$199.50
 Wired & Tested

Model SSB-6 Kit \$159.50

For additional information, write:

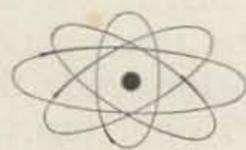

Supreme Electronics, Inc.

FRONT AND MAIN STS.

UPLAND, PA.



73

Tests the Lafayette KT-390 Starflite

and likes it

Leonard Tamulonis WIMEL

EIGHTY DOLLARS, ninety watts, phone and CW. Those are the things that make the new Lafayette Starflite KT-390 transmitter a really desirable piece of gear for the ham-shack. While looking over the specifications, I wondered how Lafayette could get so much into such a small package for such a small price. Well, this transmitter comes as a kit, so *you* supply most of the labor, and cut most of the cost. The whole thing measures only 13 x 12 x 6¼ inches, and is very attractive in its two-tone steel cabinet. Size, cost, and performance make it even more attractive for the beginning ham who has to watch his cabbage.

There are 266 steps to final assembly, and since the instruction manual is liberally salted with diagrams, the job is foolproof (almost).

The circuit is simple enough for what it does. It consists of an oscillator that acts as a buffer stage with vfo operation, a driver, a modulator, and a 6146 final. A low-pass filter is built into the back of the cabinet, and the shielding of the entire rig is pretty thorough. This should help out the ham who lives in a forest of TV antennas (and who doesn't nowadays?).

A schematic of the Starflite is shown in Fig. 1. The 6CL6 (V1) functions as a modified Pierce oscillator with crystal control. When vfo operation is desired, the vfo is plugged into the appropriate jack, and the 6CL6 then functions as a buffer stage between vfo and driver.

The driver tube (V2, another 6CL6) operates as a class C amplifier. The plate circuit of this stage is tuned by the "DRIVE-TUNE" variable capacitor, and the coil L_3 (or sections of the coil that are selected by the band switch). The entire stage operates straight through on 80 and 40 meters, functions as a doubler on 20, a tripler on 15, and as a quadrupler on 10. The drive level control (pot R5) controls the screen voltage of the driver, and therefore controls the output that is fed to the grid of the final.

A 6146, complete with parasitic suppressor, is used in the final, and operates straight through on all bands as a shunt-fed, neutralized amplifier. The tank circuit is made up of C20 (the final tuning capacitor), L_3 (or sections of it that are selected by the band switch), and variable capacitor C22 (final loading). This final loading capacitor consists of three 450 mmfd capacitors in parallel, so that there is no need to switch fixed capacities in and out when band changing. A 69 mmfd disk ceramic was added to the tank coil to maintain a good L-C ratio on 80 meters. The whole thing is a pi network output, so any of the regular dipoles and antennas having 50 to 75 ohm impedance should work out well.

A metering switch is located just below the modern horizontal meter on the front panel. In the "GRID" position, the meter reads the voltage developed across a 620 ohm resistor in the final, and in effect measures the current passing through the resistor. In the "PLATE"

position, the meter reads voltage that's developed across R13 on the cathode of the 6146, and as before, the effect of measuring current is achieved. Although cathode current is actually a combination of grid, screen and plate current, the readings may be taken as actual plate current. The error caused by the addition of grid and screen current is very small, and on the legal side.


The Starflite uses carrier-controlled modulation, and judging by some on-the-air-reports that I've gotten, there seems to be a lot of misunderstanding about this sort of modulation in general. The 2 triode sections of a 12AX7 (V4) act as a regular resistance coupled audio amplifier. The output of the second triode section is coupled to the first half of the modulator tube through C28. The modulator tube is a 6DE7 (V5) that contains two dissimilar triodes, one with a power rating of 1.5 watts, and the other with a rating of 7 watts. The output of the low power triode is directly coupled to the grid of the higher powered triode which actually functions as the modulator. Bias voltage on the 6DE7 is arranged so that conduction is low when there's no audio input signal. This lowers the screen voltage of the 6146, and naturally when the screen voltage goes down, so does the plate voltage and output. An audio input signal that's caused when someone speaks into the mike reduces resistance in the modulator sec-

tion, and raises the screen voltage of the final. Naturally, this jacks up your plate current and output, giving you carrier-controlled modulation.

Grid block keying is used in the Starflite, and a good thing too! This method of keying gives the least trouble as far as clicks and things like that go. Grid block keying in the Starflite is accomplished like this: with an open key, a high bias voltage is fed into the grids of tubes V1, V2, and V3. This high bias voltage cuts off these tubes and eliminates any output. In the key down position, R8 is shorted, and this cuts out the high bias to V1, and V2. It leaves a small amount of bias on the final (V3) to protect it in case the drive is suddenly removed. The values of R8 and C2 were chosen by the Lafayette people to give the most desirable CW waveform.

Lafayette is using a unique power supply for this transmitter in that it uses four silicon diodes in a voltage doubler circuit. These diodes are more efficient than their tube counterparts because they use no filament power, and voltage drop is much less. Filtering is accomplished through a capacitor input filter that is made up of R28, R29, and C34, 35, and 36. Of course there is an accessory socket that provides the necessary voltages for convenience in operating vfo, CW monitor, etc.

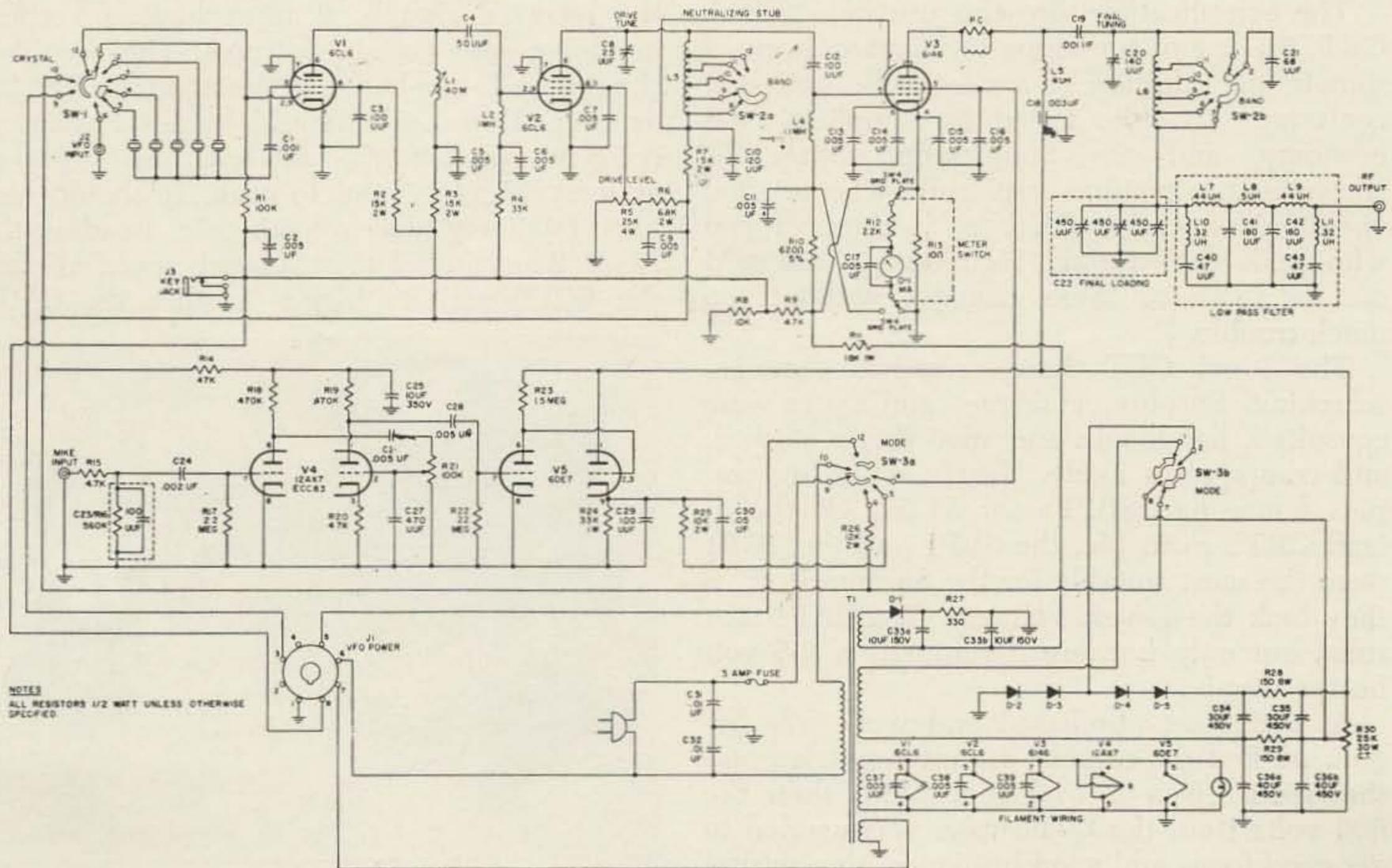On the air tests proved this little transmitter to be extremely satisfactory (satisfactory



SCHMATIC DIAGRAM

enough so that the writer had a short fist-fight with the editor when the latter decreed that the Starflight had to be sent back to Lafayette after testing). Operation on 80, 40, 20, and 15 meters was good, but a little critical tuning on 10 was necessary to keep a good quality signal going out.

All in all, this rig turned out to be quite

a surprise, and just a hair short of fantastic for the price tag. It makes a sweet rig for the Novice who will get his general class license and won't be able to afford a new rig. It makes a swell rig for the ham who'll want to keep it around as a standby rig, or who'll use it portable on Field Day or vacation.

... WIMEL

Complicating the Simplescope

Harvey Pierce W6OPA
5372 E. Bald Eagle Blvd.
White Bear Lake 10, Minnesota

THE "Simplescope"* was conceived as the simplest form of an oscilloscope that would give adequate service as a phone monitor. But it was too simple for some ambitious builders who wanted to complicate it by adding various features they felt a scope should have. Of all the ideas for improvement, a few had merit. Here is how you can "Complicate the Simplescope" to get the "LARGE Economy Size."


The complications are the use of a 3-inch CRT, the use of the scope to monitor received signals, the addition of a pilot light, and spot centering. All were tested for simplicity and economy, and the Simplescope Mark II, shown in the pictures was built. The original circuit was merely added to, so those of you who built the original Simplescope can add one or more of these changes without too much trouble.

The 3-inch CRT change required some researching. Surplus catalogues and flyers were consulted, handbooks and spec sheets studied, and comparisons made. Nearly every big surplus house had 3BP1's for \$1.95. Of the 3-inch CRT's available, the 3BP1 and the 3GP1 were the most suitable for the Simplescope, as they took the lowest voltages. The 3AP1 was ruled out only because it required a 2.5 volt heater supply.

A 3BP1 was purchased and work was begun. At first the original circuit was tried and the 3BP1 given a trial run. More than the 600 volts from the quadrupler was needed to get good focus and good brilliance, so a second power transformer with a voltage doubler cir-

cuit was added and connected in series. With about 900 volts pushing the electrons, the 3BP1 worked fine. Focus was good, brilliance good, and deflection sensitivity good. 'Scope design is a compromise between brilliance and sharp focus on one hand and deflection sensitivity on the other. This one is no exception. The 2AP1 and 3AP1 should have at least 500 volts, the 3BP1 and 3GP1 at least 850.

If the Simplescope is to be used to monitor the received signals, it must have a vertical amplifier with certain features. The amplifier should be broad-band, at least up to 500 kc, or even 2 mc, so it could be used with all common receiver *if's*, and have an output of at least 75 volts peak-to-peak. It should also have relatively high voltage gain. Reading the RCA Receiving Tube Manual revealed that the 6CL6 and its bigger brother the 6AG7

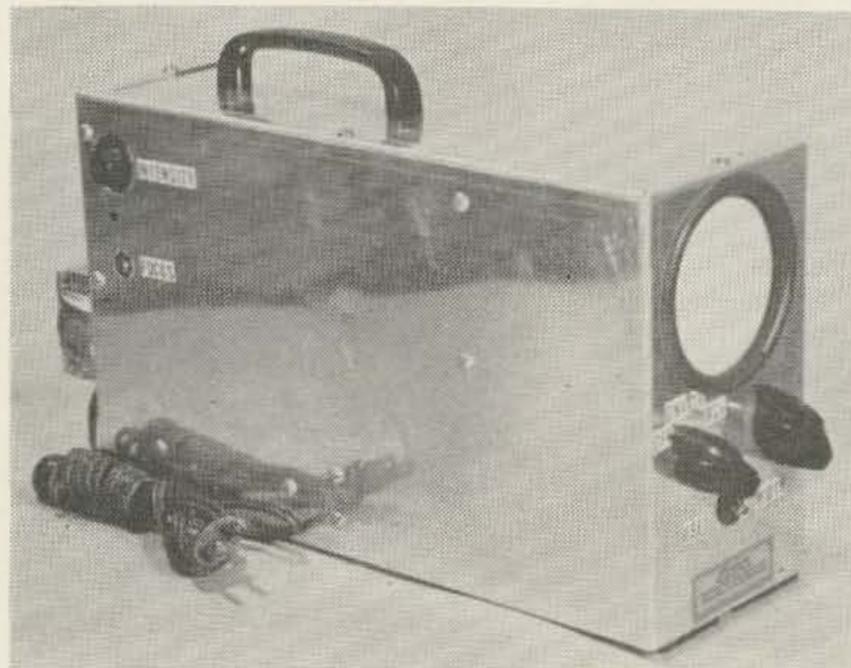

The "Large Economy Size" Simplescope. Handle is mounted toward the rear for proper balance. Note NE2 pilot light below knobs on front.

*See the Sept., 1961, 73 Magazine.

were both capable of 130 volts output in a broadband video amplifier up to 4 mc. The voltage gain was a shade over 40, so that a bit over 1 volt would be enough input for a good clear pattern on the 'scope.

Heater and plate ratings for these tubes were a trifle high for the additional power transformer added to the original Simplescope power supply circuit to build up the voltage to 900 volts for the 3BP1 CRT, but no trouble was experienced in using this transformer to supply the amplifier. The amplifier and added power supply circuit are shown in Fig. 1 added to the original Simplescope circuit of my previous article. Points of attachment are marked with an "X," and other added parts marked by a °.

Switching is now done by a 4-pole, 4-position switch to give an added position to turn on the amplifier and the high voltage for monitoring received signals. From long experience in using 'scopes, I felt there was no need for continuous receiver monitoring, so this provision was made for turning the amplifier off. The life of the CRT phosphor is extended this way, and the overload on the added transformer reduced.

Switching of the vertical deflection plate from the transmitter to the amplifier was avoided by coupling it to the "ANT" jack by a 22 mmfd mica capacitor. This value gives adequate coupling at 4 mc, yet a minimum of bypassing at a 455 kc *if* frequency from the amplifier. Switching would be better, but complicated, as the switch would have to be at the rear, otherwise the long leads to a front panel switch would bypass more rf than the 22 mmfd capacitor does. As an added bonus, this circuit will monitor *both* transmitted and received signals during a QSO without added relays or switching when the "USE" switch is in the "RCV" position.


The amplifier can be built as a separate unit if you wish, to use with an already constructed Simplescope. With its own power supply it can be permanently connected to your receiver and its output plugged into the rf jack of the Simplescope as needed. The original Simplescope circuit must be changed for use with this amplifier by the addition of a 15 K ½-watt resistor between the rf choke and ground at the rf jack. This will not change the original operation of the 'scope in any way.

The addition of a pilot proved easy and cheap. It can be added to any Simplescope. A rubber grommet, an NE2 neon bulb and a 180 K ¼-watt resistor are all the parts needed. The grommet should have a hole that fits the NE2 snugly, and is mounted on the front panel

Only Cleveland Institute guarantees*

A First Class FCC License

...or Your Money Back!

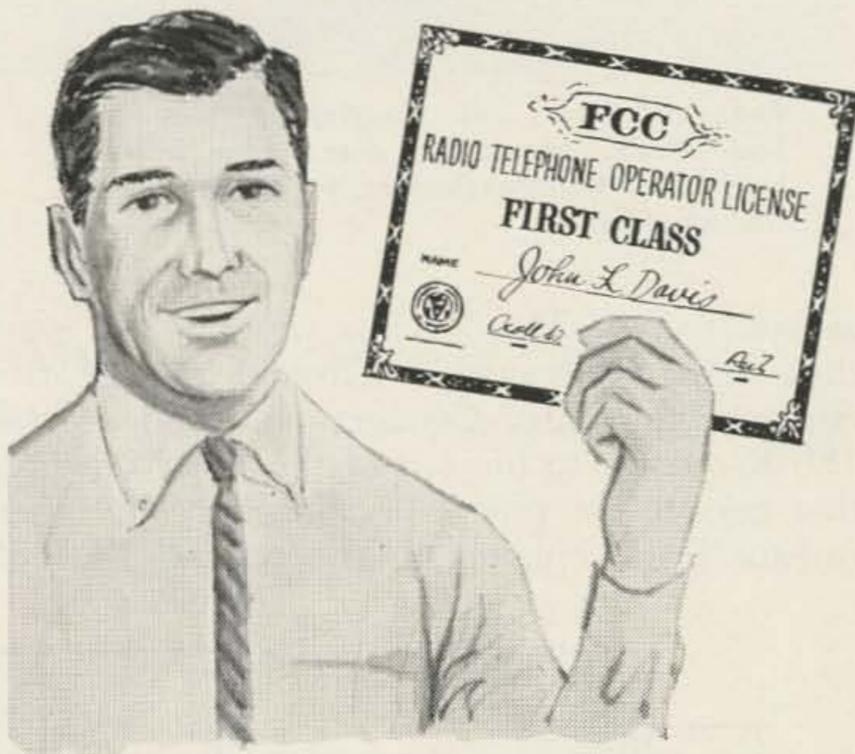

Your key to future success in electronics is a First-Class FCC License. It will permit you to operate and maintain transmitting equipment used in aviation, broadcasting, marine, microwave, mobile communications, or Citizens-Band. Cleveland Institute home study is the ideal way to get your FCC License. Here's why:

*Our training programs will *quickly* prepare you for a First-Class Commercial Radio Telephone License with a Radar Endorsement. Should you fail to pass the FCC examination after completing your course, you will get a *full refund* of all tuition payments. You get an FCC License... or your money back!

You owe it to yourself, your family, your future to get the complete details on our "guaranteed effective" Cleveland Institute home study. Just send the coupon below TODAY. There's no obligation.

MAIL COUPON TODAY FOR FREE CATALOG

Cleveland Institute of Electronics

1776 E. 17th St., Dept. ST-1
Cleveland 14, Ohio

Please send FREE Career Information prepared to help me get ahead in Electronics, without further obligation.

CHECK AREA OF MOST INTEREST -

- | | |
|---|--|
| <input type="checkbox"/> Electronics Technology | <input type="checkbox"/> First-Class FCC License |
| <input type="checkbox"/> Industrial Electronics | <input type="checkbox"/> Electronic Communications |
| <input type="checkbox"/> Broadcast Engineering | <input type="checkbox"/> _____ other _____ |

Your present occupation _____


Name _____ Age _____
(please print)


Address _____

City _____ Zone _____ State _____

Accredited Member National Home Study Council

How to Succeed in Electronics

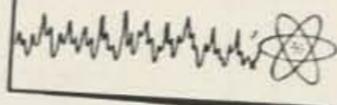

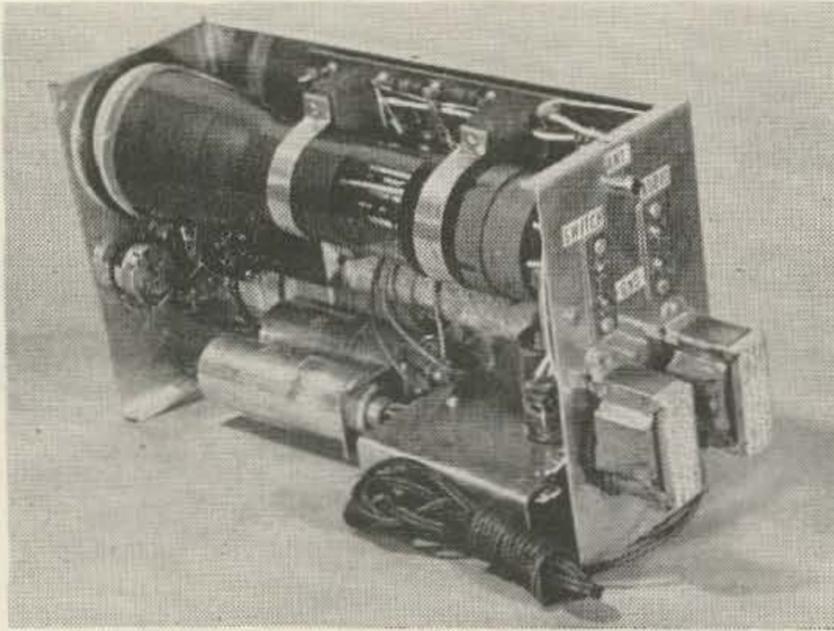


Rear terminals and transformer mounting. The "RCVR" phono jack is at center, bottom, hidden by the transformer, for short lead to the amplifier.

as convenient. The NE2 is pushed half way thru, wire leads inside. Ground one of the wires to the case. Connect one lead of the 180 K resistor to the lug of the "USE" switch that goes to the power transformer. The other resistor lead connects to the unused lead of

the NE2. Use insulating sleeving to avoid shorts.

Connected this way, the neon light shows three things. If everything is hooked up right to the 'scope, it acts as a pilot light, indicating if the power is off or on. If the 'scope is not grounded it will not light at all, or very dimly. Lastly, if the ac cord is plugged in wrong it will light when the switch is off.

The spot centering problem seemed to be due to the magnetic field of the earth, and the spot was always left of center, no matter which way the tube was rotated. With the deflection plates connected in Fig. 1, and the locating guide slot of the socket on the bottom, two resistors and a bypass capacitor added to the circuit will pull the spot over near the center. The bottom or ground end of the width control is bypassed to ground by a .1 mfd capacitor, and connected to the -300 volt tap on the power supply thru a 10 megohm 1/2-watt resistor. Various resistors of up to 1 1/2 megohms are tried in parallel with the .1 mfd capacitor until one is found that centers the spot, and then this resistor is

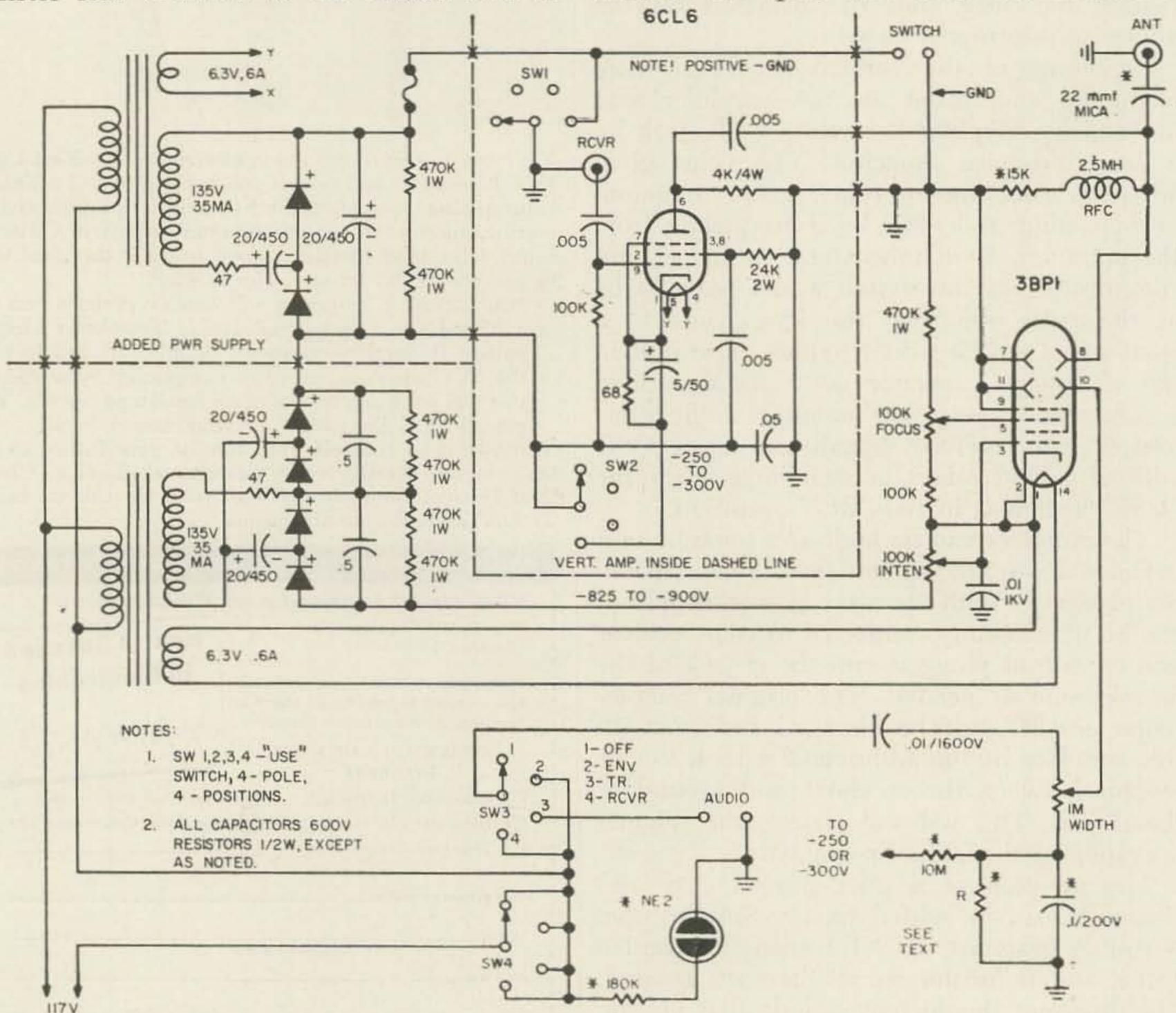

Corrections: eliminate connection to position one on SW4—change "X to Y" at transformer heater winding.



Request Our New General Catalog No. 63

by sending us one of your QSL cards.

J.W. MILLER CO. 5917 South Main St., Los Angeles 3, Calif.

soldered in place. This is much cheaper and simpler than putting in a control.

No vertical centering was attempted because the vertical position of the spot was not far enough from center to matter.

The pictures show the general construction of the "Large Economy Size Simplescope." The vertical amplifier is mounted on a 4 x 4 inch subchassis, and uses two 8.2 K 2-watt resistors in parallel to make up the required 3.9 K 4-watt plate resistor called for by RCA. Also, the screen resistor is two 47 K 1-watt resistors in parallel to get the 24 K 2-watt value required. Power transformers are mounted on the outside rear to prevent distortion of the spot by their ac magnetic field. Rf leads are as direct and short as possible, and away from the chassis to avoid losses. No other precautions (outside of the usual care in insulating high voltage leads) are necessary.

The Large Economy Size Simplescope was built in a Premier Minibox, 12 x 7 x 4 inch size, and cost me, (except for bolts, nuts, wire, handle, and knobs, which came from my junk box) just \$13.85. Many items came from kits and only the Minibox was purchased at what might be called the standard price, and was the most expensive item, at \$3.17. The two power transformers are \$1.35 each (Cat. #T-173 from Olson Electronics). The silicon diodes costs 36¢ each (#T200, from TAB, New York). The three potentiometers used should be linear taper if you must be particular, but it really isn't too important. The rubber tubing used as a grommet around the CRT opening is a section of an old Stethoscope tube donated by a doctor friend.

Installation of this version is the same as for the earlier Simplescope, except for a connection to your receiver. Enough rf from the transmitter is fed into the "ANT" jack to produce a satisfactory pattern and enough audio from the modulator is fed into the "AUDIO" connectors to give a good Trape-

USED EQUIPMENT— GUARANTEED A-1 CONDITION

4—VIKING "500" Transmitters (new price \$1050) only \$495. VIKING VALIANT \$269; KWS-1 \$895; GLOBE 500-C (\$895 new) \$425; B & W 5100 \$199; DX-100 \$149; NC60 w/5 coils \$329; NC183-D \$199; B & W L-1000-A \$229; NC-300 \$229; COLLINS 32V3 \$299; KP-81 PIERSON \$225; VIKING II & VFO \$149. Many others in stock. Write & ask.

Complete line of Antennas & Ham Parts.


Distributor for Collins, Hammarlund, Johnson, Hallicrafters, Gonset, National, Drake, B & W.

TOP TRADE-INS! MISSION HAM SUPPLIES

5472 Mission Blvd.

Riverside, Calif.

Phone (area code 714) OV 3-0523

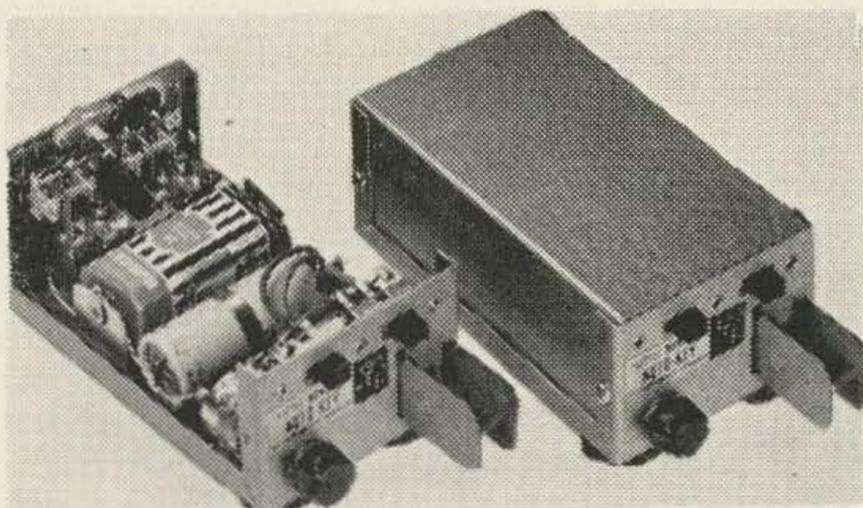


"Little Monster" AUTO-KEY Pat. 2,988,597 BATTERY powered: 3 MILS NO tubes, NO transistors, NO warmup. 20-45 WPM. SELF-COMPLETING RIGHT or LEFT handed. INTERLOCKED. Straight, semi, FULL automatic Prototype tested on the air FOUR years. Price, ready to go \$39.95 ALEX J. TREMBLAY W1CQJ, 27 North Avenue, St. Johnsbury, Vermont

Simplified MATH For The Hamshack

F - F²
SQUARES - ROOTS - POWERS
FREQUENCY - METERS
L/C
LOGS
etc.

50¢

K8LFI has come up with a booklet on "Simplified Math for the Hamshack" that you mustn't miss. This booklet presents the simplest and most understandable explanation of the math that we need for ham radio work that we have ever seen. It covers with utter simplicity Ohm's Law, squares, roots, powers, frequency VS meters, L/C, logs, etc. It even introduces you to the slide rule. This will be one of the best investments you've ever made. 50¢

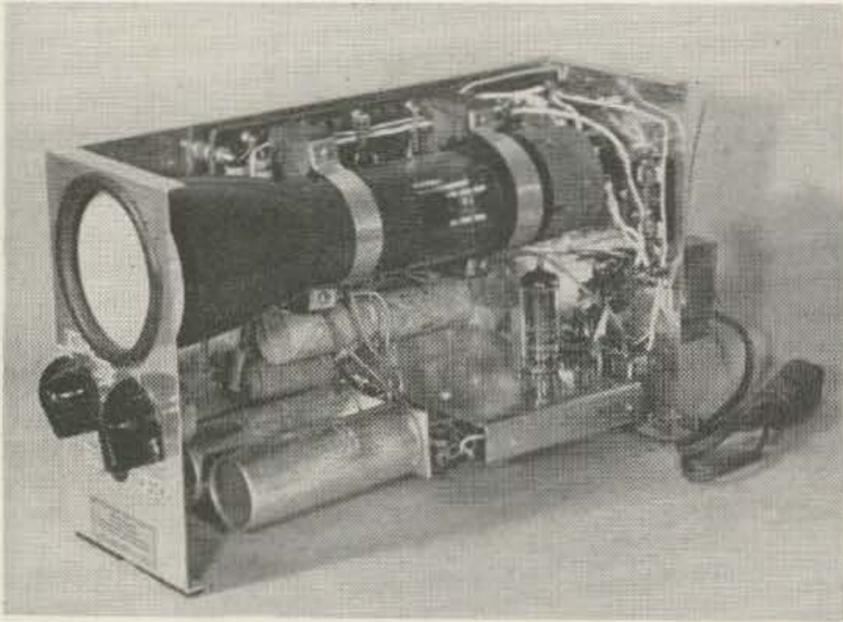

Interior view, showing method of mounting the 3BP1. 'Saddles' are wood, straps of thin (.015") aluminum. Insulation board holds saddles, quadrupler supply, and "Focus" and "Brilliance" controls, is mounted $\frac{3}{8}$ " away from metal case.

zoid. The best method of getting rf from the transmitter is by coupling thru a small capacitor to the coax output connector. The size of this capacitor depends on several factors, and cannot be specified. Start at a couple of mmfd and increase as needed. If you have really wild SWR's on your antennas, it may have to be a variable.

The audio *must* come from the actual modulated voltage, regardless of the type of modulation used. It should be at least 25 v rms, or 80 v peak-to-peak for a good pattern. In AM rigs, add one, 1-megohm, 1-watt resistor in series (inside the transmitter) with the audio lead for every 250 volts of modulated voltage over 250 v. In some SSB and DSB rigs the available audio may be insufficient. If so, a hi-fi audio transformer may be tried to step up the voltage, but there is a possibility that phase shifts might distort the pattern.

Connecting to the receiver is more complicated. First locate the plate terminal of the last *if* amplifier (the one that feeds the detector) and the lead from it to the last *if* transformer. The connection is made to the transformer plate terminal if it has one, otherwise the tube socket plate terminal is used. The 'scope is coupled to this terminal thru a small capacitor. The size of this capacitor cannot be predicted precisely, but should not need to be over 75 mmfd to give a good pattern with an S9 signal. Start with a few mmfd and increase the value until you get a readable pattern from a moderately strong signal.

Use low-capacity shielded wire inside the receiver for this connection to prevent possible *if* feedback and oscillation. Keep all leads short, and *don't forget* there is *plate voltage* on that *if* tube! Every time the cou-

pling capacitor is changed peak up *only* the input (plate) side of the detector *if* transformer for maximum pattern height on the 'scope, using a steady signal or a signal generator. The wire to the 'scope should have as little capacity to ground as possible. Be sure the 'scope is grounded to both transmitter and receiver.


The 6CL6 amplifier needs about 2 volts of rf on its grid for the maximum, and $\frac{1}{2}$ volt for the minimum, useable pattern.

Remember, the oscilloscope is very susceptible to stray magnetic fields, so for the cleanest patterns do not place it near any magnetic devices such as transformers, relays, clocks, motors, or even solder guns! For practical purposes all transformers should be at least 6 inches away, relays, clocks, and motors a foot or more.

The "SWITCH" terminals should be connected to switch or relay contacts that close when the transmitter goes on the air. While these terminals are shorted when the use switch is in the "RCV" position, spot switching is required in the other two positions to avoid "burning" the CRT phosphor.

There is little need for a vertical gain control. The weaker received signals have so much "grass" on them from QRN and QRM that more gain wouldn't help, and the strong signals can always be reduced by the receiver's rf/*if* gain control. The transmitter always puts out the same power and about the same rf voltage into any reasonably "flat" coax line.

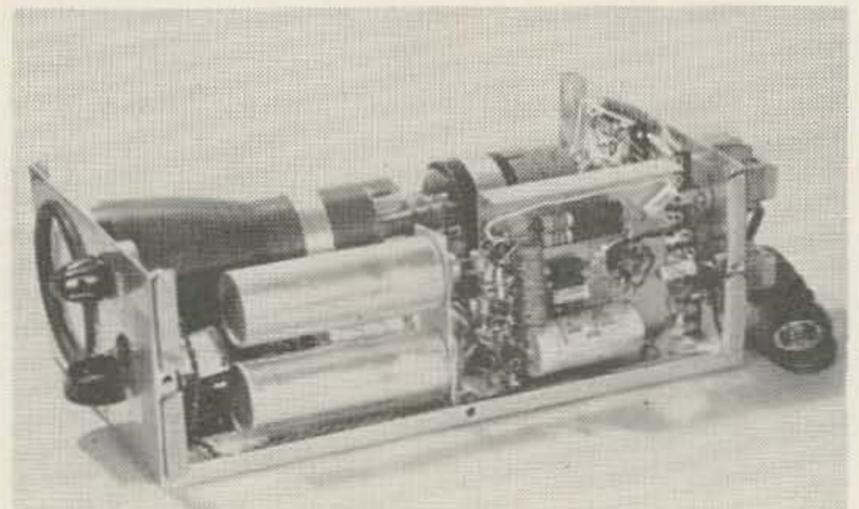With the "USE" switch turned to the "ENV" position, the 'scope is turned on, and shows the envelope type pattern on transmitting. The "TR" position gives a trapezoid pattern on AM when transmitting, or a bow-tie pattern on SSB. The "RCV" position turns on the vertical amplifier, and the 'scope shows



Underneath view, showing amplifier layout. Tie point strip (center) holds voltage-doubler supply connections and parts. Each electrolytic can contains two 20mfd 450 volt electrolytics, with separate positive and negative leads. Upper can is used for the doubler circuit.

Announcing the opening of DOW ELECTRONICS SANTA MARIA STORE

222 W. Main, Santa Maria, Calif. WA 2-1765

Complete stock of Radio & Electronic Tubes & Parts, Tools, CB & Amateur Crystals, Transceivers and HI-FI Equipment

Featuring—All major amateur brands of equipment including:

National	Heathkit	Gonset	Moseley	New-Tronics
Hallicrafters	Daystrom	B & W	Globe	Master Mobile
Johnson	Eico	Swan	Webster	Antenna Specialists
Hammarlund	Hy-Gain	Drake		

Other Stores to serve you:

DOW RADIO INC., 1759 E. Colorado Blvd., Pasadena. MU 1-6683
 DOW ELECTRONICS of OXNARD, 1505 S. Oxnard Blvd., Oxnard. HU 6-6353
 DOW ELECTRONICS of GOLETA, 5857 Hollister Ave., Goleta. WO 7-3401
 A Division of Electronic Components, Inc.



DOW RADIO, INC.

Your Complete Electronics Store

the envelope type pattern on both transmitted signal and the received signal, without further switching.

The first two positions are necessary to monitor your transmitted phone signals properly and monitoring by 'scope of received signals is not needed 95% of the time. Once you have checked a guy's modulation and told him about it, and perhaps checked again as he adjusted his gain, there's not much use in watching any more. So switch back to "TR" or "ENV" so you can keep your own modulation right up there and conserve the CRT phosphor while receiving.

The envelope pattern of the received signal is not always a true presentation of the transmitted signal due to the limitations of the receiver and the propagation path. The receiver bandwidth affects the apparent modulation of the higher frequency sidebands, and the truest pattern is shown with the greatest bandwidth. Yet even with an 8 kc bandwidth it could be possible for the signal to be over-modulated by a 10 kc parasitic the receiver wouldn't show! Fading on the lower frequencies is often selective enough to remove either carrier or sidebands, giving wide variations in apparent modulation. Such a signal must be watched for some time and averaged to get the approximate modulation percentage.

Despite these limitations, monitoring received signals by 'scope is a rewarding experience. Certain makes and models of transmitters can be identified by their patterns! Good, clean, well-modulated signals look as good as they sound. Surprisingly, over-modulation is NOT the prime cause of severe splatter! Broad signals are often apparently undermodulated, while the definitely overmodulated ones are often surprisingly narrow.

There are so many variations of power supplies possible for the high voltage that it would only be confusing to even list a few. You're welcome to try any and all varieties of rectifiers and multiplication circuits that you want. The one shown in Fig. 1 is OK and inexpensive, but is just one of many possibilities. What is needed is 900 volts at 2 ma, -250 volts at 40 ma, and two 6.3 heater windings at .6 amp or more each.

WARNING! Ordinary insulation does a pretty good job below 1,000 volts but is risky above that, so don't get any ideas about using 1,250 or 1,500 volts in these Simplescopes. It isn't worth the trouble. And don't get careless with the 800 to 900 volts in this 'scope! It bites real hard! Be sure all insulation is clean and unbroken.

The complications added to the original Simplescope circuit as described in this article

are about as far as it is advisable to go in an instrument of this type. Anything further would bring it into a class with kit and commercial type scopes. The 3-inch Simplescope with vertical amplifier does a very adequate job of monitoring at a very reasonable price, without complicated circuitry, requires no special parts, and should not prove to be a

difficult building job.

I want to thank Dick St. Amant WøGZQ, for his thorough testing of the model shown at his station under typical conditions. I almost didn't get it back, he liked it so well! And again my thanks go to my friend Bob Rode WøBRE, for the excellent photographs.
... WøOPA



Capt. John Sury W5JSN
139 Nebraska Road
Dyess AFB, Texas

The Heath IM-30 Transistor Checker

Here is a piece of test equipment that has been misnamed. Instead of a transistor tester it should have been named the transistor analyzer. This is exactly what it does. It measures $5\frac{1}{2} \times 10\frac{1}{4} \times 10\frac{1}{4}$. The tester tests transistors and diodes under conditions that correspond to actual dc operating conditions. Since the author has specialized in transistors for the past 7 years this equipment is right up his alley.


The kit is complete and the instructions are thorough. Only precision components were used in this kit. It was constructed and tested by the author in approximately 20 working hours.

With transistors coming into the amateur

field more each day this piece of test equipment fills the bill. It would almost be impossible to cover all the parameters this tester covers in this article.

Just about everyone who even has a slight interest in transistors wonders what the gain is of a particular transistor. This is a good way to find similar transistors when using 2 PNP in conventional push pull amplifiers or PNP and NPN in complementary symmetry amplifier for receivers or modulators.

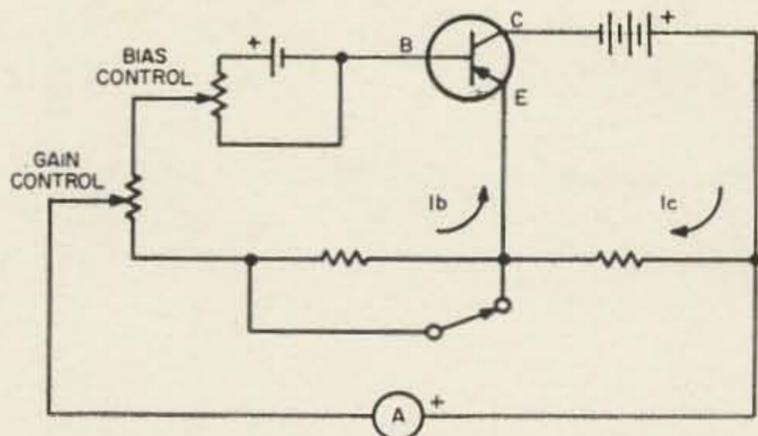Let's cover the gain test (dc beta-dc alpha). Readings are taken off of a calibrated direct gain dial after the 10-0-10 micro-amp 100K/volt meter has been nulled. The following is the gain circuit:



GAIN TEST (DC ALPHA) (DC BETA)

The following additional information may be obtained direct:

Base current (I_b) Collector to base leakage (I_{cbo})

Collector voltage (E_c) Leak voltage

Collector current (I_c) Short test

Collector to emitter leakage (I_{ceo}) Diode Test

With some of the above information and an external voltmeter used in several instances the following information may be obtained:

AC current gain DC Transconductance

$$\frac{I_{c1}-I_{c2}}{I_b}$$

$$\frac{I_{b1}-I_{b2}}{E_b}$$

AC Transconductance DC Base resistance

$$\frac{I_{c1}-I_{c2}}{E_b}$$

$$\frac{E_{b1}-E_{b2}}{I_b}$$

AC Base resistance DC Collector resist.

$$\frac{E_{b1}-E_{b2}}{I_c}$$

$$\frac{I_{b1}-I_{b2}}{I_c}$$

AC Collector resistance

$$\frac{E_{c1}-E_{c2}}{I_c}$$

$$\frac{I_{c1}-I_{c2}}{I_c}$$

What difference is used in the formulas two different bias or voltage points have to be taken.

The author selected a bargain basement transistor audio *if* type which costs less than a dollar and made several checks with some surprising results. It was a PNP with a gain of 90 which is excellent. A transistor has good gain if it has a gain of 70. The base *ac* resistance was 750 ohms and the collector *ac* resistance was 1500 ohms.

The base and collector resistances become important when a transistor is to be used in a circuit. This allows the builder to properly match the input and output. The checker in itself is an education in transistors. It takes a little practice and usage to master it. Remember it is a piece of laboratory test equipment. Instructions with the tester are very clear to follow.


... W5JSN

SKYLANE QUADS

"famous the world over!"

\$59.95 Three Bands **\$99.95**

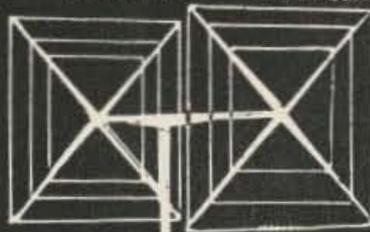Bamboo 40 M QUAD KITS AVAILABLE Fiberglass



FOR FREE LITERATURE
WRITE DEPT. C

- HIGH F/B RATIO
- VERY LOW SWR
- HIGH GAIN
- LOW Q — BROADLY TUNED
- EASY TO MATCH
- LOW WIND RESISTANCE
- RUGGED CONSTRUCTION

SkyLane PRODUCTS 406 BON AIR DR.
TEMPLE TERRACE, FLA.

K T V

We spent our years advertising budget last month, so look back on pages 40 and 41 of the October 1962 issue of 73 and see what we have. You'll find complete prices and ordering information there.

KTV TOWERS, SULLIVAN, ILLINOIS

SINGLE POLE, SIX-THROW COAXIAL RELAY



**DOW
DKC
71**

FOR MOUNTING ON MAST AND
REMOTE SWITCHING UP TO 6 ANTENNAS

Weatherproof, electro-magnetic, less than 1.1:1 VSWR at 100 mc, 1 kw power rating, available in UHF, N, BCN, TNC, C connectors. Continuous duty, over 1,000,000 operations. 5 3/4" x 2 3/4", silver plated connectors.

DKC-71
with UHF
Connector
\$4950

Manufactured and
Guaranteed by ...

DOW-KEY COMPANY

THIEF RIVER FALLS, MINNESOTA

Q T H AMATEUR RADIO LOCATION MAP

United States & Adj. Parts Canada-Mexico
BRAND NEW — UP TO DATE!

SHOWS MANY CITIES OF 250 POP. & ALL OVER 5,000
TOPOGRAPHIC FEATURES, RAILROADS, HIGHWAYS
& RIVERS

PERTINENT DATA ALL STATES IN THE LOWER MARGIN
IN 6 BEAUTIFUL COLORS 52" x 34" IDEAL MURAL SIZE
CO-ORDINATES FOR QUICK QTH DETERMINATION

A CALLBOOK COMPANION — IDEAL PIN MAP
CHART SHOWS ALL FREQUENCIES OF RADIO SPECTRUM
(AMATEUR & COMMERCIAL) (500 KC-30,000 MC)
SCALE 1" — 65 MILES; MAILED IN STURDY MAP TUBE

PRICE: \$3.00

See picture of map in June 73, page 19.

Make checks payable to Norman Walker W5GOS


905 Midland Savings Bldg., Midland, Texas
ADDL. POSTAGE OUTSIDE U.S.A.

Simple Squelch

David Bernays K4UWX
HAMBOARDS
Box 13158
Pine Castle, Florida

THERE is one basic circuit missing from most receivers currently available to the modern amateur—squelch control. Essential for VHF operation, squelch can also provide a tremendous increase in operator enjoyment on the lower bands or wherever QRM and background noise levels are high. The lack of such a circuit becomes extremely obvious whenever one of our present communication receivers is used as a tunable *if* for VHF converters. Fortunately the problem is easily solved, as a squelch circuit may be incorporated in most receivers with minimum effort and without disfiguring the equipment. A simple, proven circuit for this purpose is outlined below.

First, however, for those who have never used a receiver with squelch, it will be worth while to back up and define exactly what this circuit does. Stated simply, the squelch circuit is an active circuit which effectively silences the receiver in the absence of signals stronger than a certain preset threshold. The word active should be noted, for it is what separates a true squelch circuit from judicious adjustment of the various receiver gain controls. Squelch circuits are normally tied, either directly or indirectly, to the receiver AVC bus and obtain their controlling voltage therefrom. Squelch circuit operation is based on the fact that most noise and QRM, while of high audio content, actually represent little signal strength and therefore cannot develop significant AVC voltages.

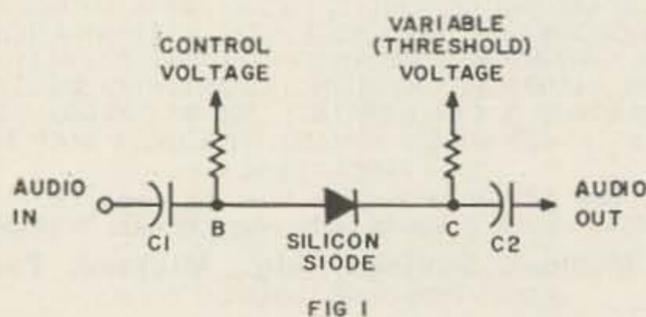


There are three basic requirements that must be met by any squelch circuit before it can be considered acceptable for inclusion in a typical communications receiver. These are:

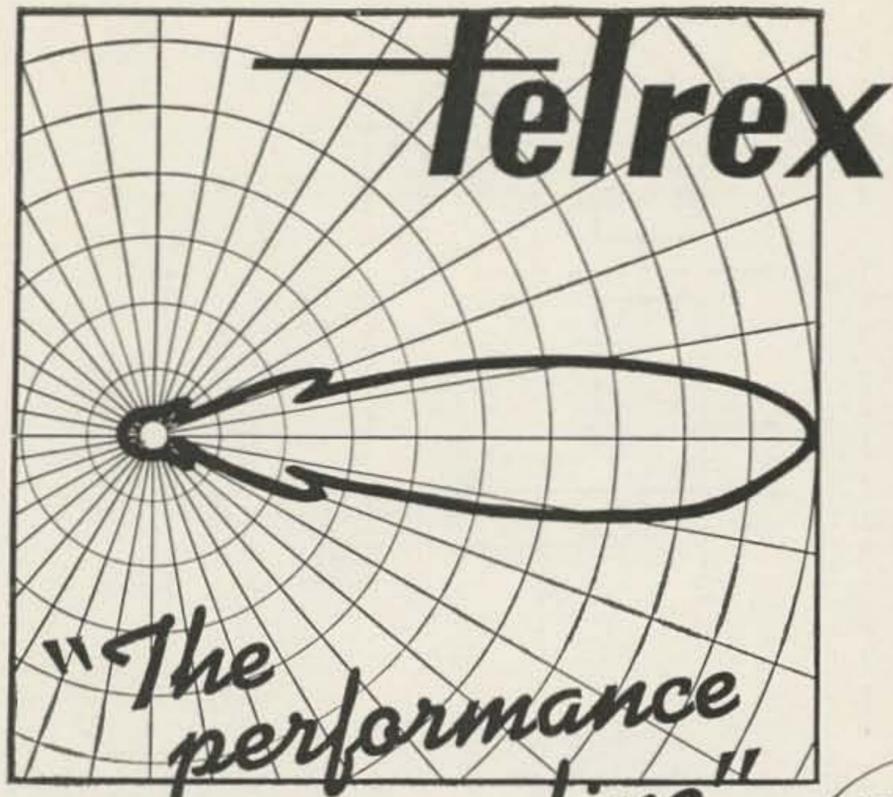- 1) The circuit may be installed without making any mechanical alterations to the receiver.
- 2) The squelch threshold must be a front panel control.
- 3) The squelch must operate reliably on the weakest signal that may be discerned above the background noise level.

The requirements of item one are obvious as most of us are unwilling to compromise the resale value of an expensive receiver. Thanks to TV (there must be something good about TV!) requirement two is easily satisfied. Squelch threshold can be made a front panel control by substituting a dual potentiometer with concentric shafts for the original receiver audio gain control. One section remains a volume control, the other is used for squelch threshold. These dual pots mount in the same size hole as the original volume control and are readily available from any parts house. The last requirement is operational in nature and based on a rather fundamental premise—none of us like to miss the weak ones as this is where the DX usually hides!

A simple circuit which fulfills the above requirements is shown in basic form in Fig. 1. Its operation is based upon the unique characteristics of a silicon diode. Such a diode, when forward biased, represents a very low impedance. When back biased the same diode has an effective impedance of ten or more megohms. Germanium diodes, because of their low back resistance, will not work. The best silicon diodes available are the high back resistance types. The Hughes 1N457 used here is typical (and also inexpensive). When it is con-



"— with a MATERIAL DIFFERENCE!"

"BEAMED-POWER" ANTENNAS and ANTENNA SYSTEMS

The Choice of the Discriminating Communication Engineer... the Man who Never Settles for Anything Less than THE-VERY-BEST!

You too — can enjoy World renowned Telrex performance* and value!

Send for PL77 condensed data and pricing catalog, describes 107 popular amateur antennas from \$6.95 to \$999.00. Expanded data sheets — Your favorite band, also available.

ANTENNAS

SINCE 1921

Communication and TV Antennas
telrex LABORATORIES


ASBURY PARK 40, NEW JERSEY, U.S.A.

nected as shown in Fig. 1, squelch action is obtained in the following manner. The variable voltage lead is connected to a potentiometer which allows this voltage to be set as desired. This is the squelch threshold control. The other side of the diode is connected to what will be called the control voltage and must be one which varies depending on the strength of the signal being received. Audio is applied to the circuit through dc blocking capacitors C1 and C2. As can now be seen, in the absence of signal it is possible to set the variable voltage (threshold) to where the diode is just slightly back biased, blocking the audio. Any increase in the control voltage will cause the diode to conduct. The diode then represents a very low impedance and allows the audio to pass. The control and variable voltages are both applied through isolating resistors whose combined parallel resistance must be greater than ten times the typical audio impedance of the circuit wherein the diode is placed in order to avoid bypassing a significant portion of the audio voltage.

The first source to be considered for a control voltage is the AVC bus itself. Unfortunately this bus normally operates at an extremely high dc impedance and will not tolerate the degree of loading the squelch circuit would impose upon it. A much better point to obtain the control voltage is the series fed screen grid on the last AVC controlled *if* amplifier. This screen grid's current (and therefore voltage) varies in accordance with variations of the dc bias applied to the control grid of the tube. As the control grid obtains

its dc bias from the AVC bus it can be seen that the screen grid voltage will shift significantly for even the smallest of AVC bus fluctuations. The screen grid therefore provides an excellent source of control voltage, one that has both convenient magnitude and low dc impedance.

There are some cases, such as in the ARC-5 series of surplus receivers, where all the screens are fed from a common stiff medium voltage source. If this is the case on your receiver, the particular screen grid should be disconnected from the common line and the circuit shown in Fig. 2 substituted. The screen dropping resistor is chosen to provide the same screen voltage as was originally present. The value of 100 K shown on the diagram is typical and may be considered a good starting point to experiment from. The screen grid dropping resistor can also be optimized to provide the greatest voltage swing for small changes in the AVC bus voltage. This value is best determined by trial and error. So long as the screen grid voltage that results remains within 20% of the original value operation of

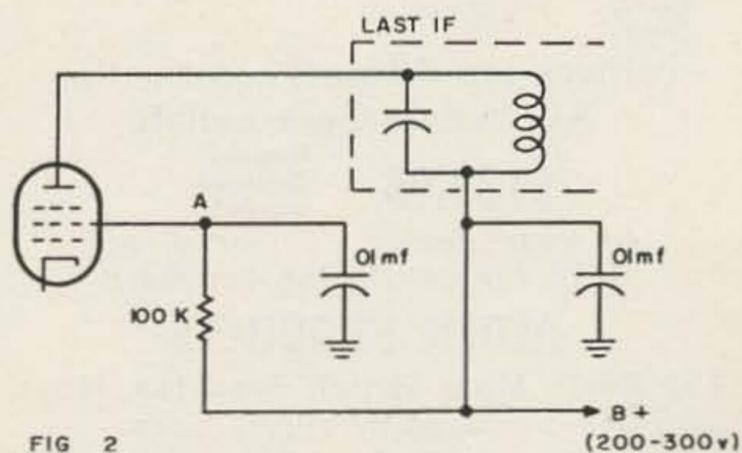


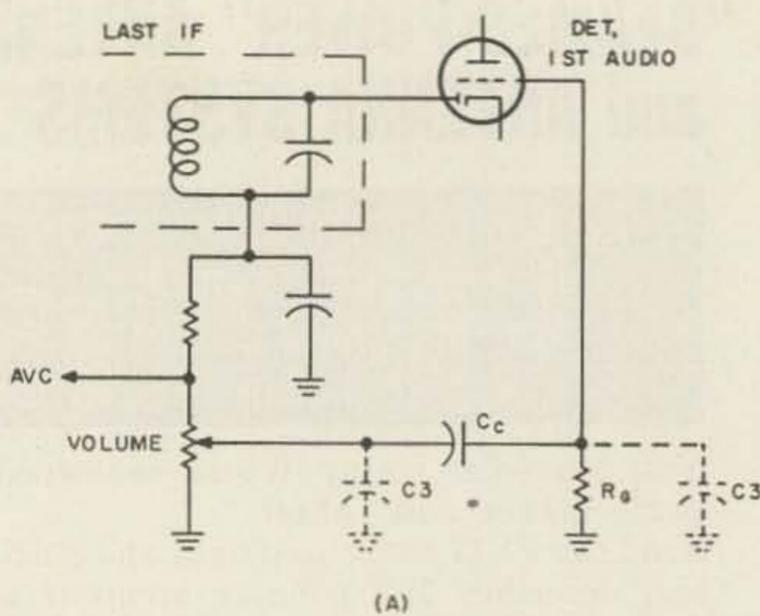


FIG 3

the last *if* stage will not be materially altered.

The best point in a typical communications receiver to apply this squelch is between the audio gain control and grid of the first audio amplifier. This stage, in its typical form, is shown in Fig. 3A. Fig. 3B shows a practical installation of the squelch circuit. Coupling capacitors C1 and C2 have been chosen so as to represent, in series, the same impedance as the original coupling capacitor. Resistor R2 has been split into three components so that the actual squelch threshold may be spread over a larger portion of the pot's rotation. R2B should be chosen so that it can swing

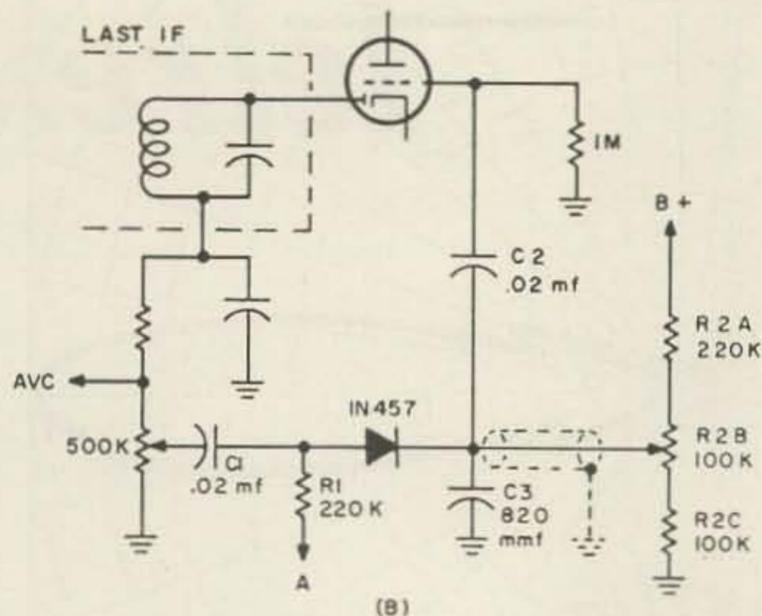


the variable voltage over a greater range than will be present under any conditions at point A on Fig. 2. R2A through C can all be part of the same potentiometer, but this is not recommended. For the circuit to work in a positive manner, resistors R1 and R2A-C should be made the lowest possible values consistent with satisfactory performance. Their combined minimum value may be determined in the following manner. Before the squelch is installed, bypass the centertap of the volume control to ground through various resistors. (During this test the volume should be set at a comfortable listening level.) The smallest resistor which can be so inserted without degrading either the audio volume or quality will constitute the minimum ac resistance that the squelch circuit should be allowed to represent between the audio grid and ground. Examination of Fig. 3B will show that in the squelch circuit the equivalent to this resistance is actually composed of three separate parallel components. (For purposes of calculation consider the squelch to be at the high voltage end of R2B.) These are R1, R2A, and the total of R2B and R2C. The three resistances should be essentially equal in value. Their total parallel resistance should approximate the minimum value determined above. The values shown in Fig. 3B may be considered typical.

Capacitor 3C has been neglected so far in order to avoid confusing the basic fundamentals. It may be present in original equipment at either of the locations shown in Fig. 3A. When so placed its presence serves either or both of two purposes. The first is to remove any trace of *if* frequency components from the audio. The second is to provide a degree of tone control. C3 serves both of these functions in the squelch circuit plus one more. When the diode is back biased, there is still a very small amount of audio leakage. If this

**ALL THAT NICE NEW
EQUIPMENT ON THAT
DIRTY OLD TABLE!
UGH!**

You need an ALDEN HAMBENCH

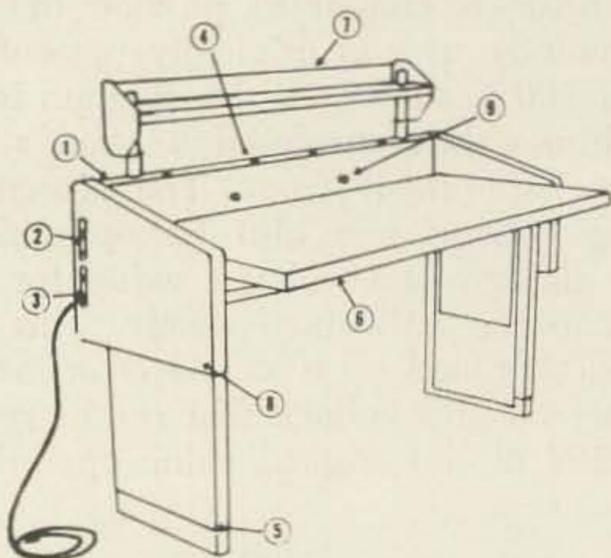

Formica top All steel construction
AC outlets Coax outlets

\$139.95

Super
Deluxe
Model

At your dealer . . . or direct
Send for convincing brochure

ALDEN PRODUCTS

117 North Main Street, Brockton, Mass.
(Ad composed by Wayne Green)

is allowed to go directly to the first audio amplifier grid an audible output will be present at the receiver speaker. Placing C3 as shown in Fig. 3B shunts this small audio component to ground, allowing the squelch to achieve 100% quieting. The optimum value of 3C is best determined experimentally by substitution. The larger the value of 3C the better, the limiting factor being how much capacity can be inserted before the receiver's high frequency audio response is reduced to an unacceptable point. Some attenuation of highs will normally be beneficial in communications work, as will be noticed when experimenting with 3C. Typical values are 820 or 1000 mmfd.

A brief examination of the impedances involved in the complete squelch circuit is now possible and will help to explain the operation of the circuit. When the squelch is closed (diode conducting) the diode represents an impedance of several thousand ohms. Since the audio impedance of the circuit between the volume control and first audio amplifier grid is typically 100 K-500 K, the additional series resistance of the conducting diode reduces the available audio voltage only a few percent, an effect that is not noticeable. The combined shunt impedances of R1 and R2A-C decrease the available audio 1-3 db, depending on the values chosen. This is not a serious loss either as most receivers can provide considerably more audio than is ever needed. The impedance of 3C is also parallel to these resistors but varies according to frequency. (If it is chosen as outlined above, its presence, rather than detracting from, will probably enhance the audio characteristics of the receiver.) When the squelch is open (diode non-conducting) the diode represents a minimum impedance of 10 to 100 megohms. It, together with C3, may be considered an ac voltage divider. As C3 now represents a relatively low impedance (approximately 100 K at audio frequencies) compared to the non-conducting diode, it can be seen that negligible audio voltage will be present at their junction, or therefore at the first audio amplifier grid. This effectively silences the receiver.

Physical installation is extremely simple. The original volume control is replaced with a dual potentiometer, one section of which has the value of the original audio gain control, and the other section that of R2B. Most of the additional components may be mounted between the volume and squelch control terminals. An additional multilug terminal strip can usually be mounted somewhere near the volume control to provide convenient tie points

MORE SIGNALS PER DOLLAR From Money Invested in an Antenna

Self Supporting STEEL TOWERS

For Rotary Beams, FM, TV



Width of Base Equal to 1/5 Height

You can erect this tower yourself. Just dig four holes, set anchor posts in place, bolt the pieces together. 5 1/2 ft. ladder sections make it easy to work higher as tower goes up. It's a lot of fun to build your own tower — and saves you money, too!

HURRICANE PROOF! VESTO TOWERS HAVE NEVER FAILED!

- 4-Post Construction for Greater Strength!
- Galvanized Steel — Will Last a Lifetime
- SAFE — Ladder to Top Platform
- COMPLETE — Ready to Assemble
- Attractive—no guy wires

SMALL DOWN PMT.—EASY TERMS

Vesto Towers are available in a wide range of sizes to meet requirements of amateurs and commercial users alike. Note the low prices for these quality lifetime towers:

22'	\$ 159,
28'	\$ 194,
33'	\$ 229,
39'	\$ 276,
44'	\$ 313,
50'	\$ 362,
55'	\$ 408,
61'	\$ 463,
77'	\$ 724,
100'	\$1132.

Towers are shipped to your home knocked down, FOB Kansas City, Mo. 4th class freight. Prices subject to change... so order now! Send check or money order... or write for free information.

WRITE TODAY
FOR COMPLETE
FREE INFORMATION
AND PHOTOGRAPHS


VESTO CO., Inc.
20th and Clay
North Kansas City, Mo.

Want High Efficiency and Small Size?

6 10 15 20 METERS

MINIATURIZED-4-BANDS

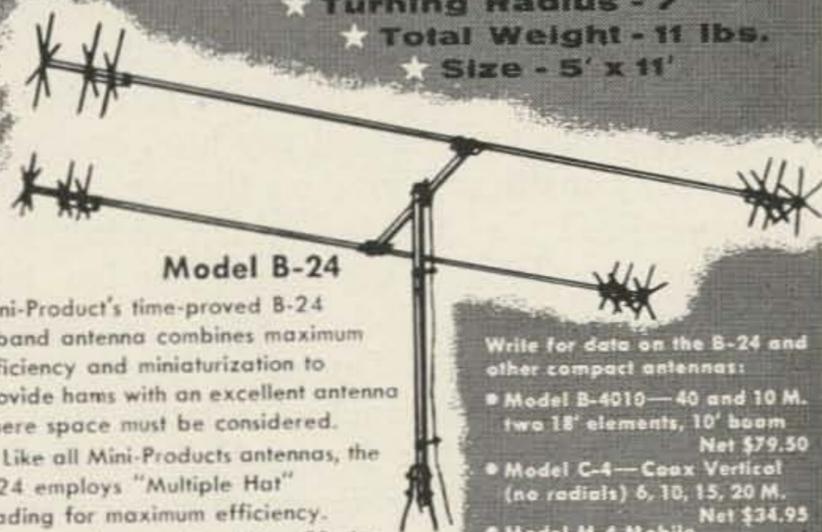- ★ 500 Watts AM.
- ★ Turning Radius - 7'
- ★ Total Weight - 11 lbs.
- ★ Size - 5' x 11'



Model B-24

Mini-Product's time-proved B-24 4-band antenna combines maximum efficiency and miniaturization to provide hams with an excellent antenna where space must be considered.

Like all Mini-Products antennas, the B-24 employs "Multiple Hat" loading for maximum efficiency. TV rotor adequate; Feed line, 50 ohm coax; SWR 1.5:1.

Amateur Net
\$59.95

Write for data on the B-24 and other compact antennas:

- Model B-4010—40 and 10 M. two 18' elements, 10' boom Net \$79.50
- Model C-4—Coax Vertical (no radials) 6, 10, 15, 20 M. Net \$34.95
- Model M-4 Mobile 6, 10, 15, 20 M. Net \$16.95

Patents pending

Mini-Products, Inc.

1001 WEST 18TH STREET • ERIE, PENNSYLVANIA
See your local distributor or order direct from factory

for the remainder of the circuit. Long leads should be avoided if they are part of the first audio amplifier grid circuit. Where this is not possible, such leads should be shielded to avoid hum pickup.

This circuit has been installed in several receivers by the author, providing satisfactory results in all cases. The actual performance of this squelch appears to be more effective and reliable than many of the circuits commonly used in commercial communications equip-

ment. It is certainly simpler! Effective squelch action, from fully silenced to fully open, is consistently obtained from signals 3-6 db above the background noise level. This corresponds to AVC bus variations of less than .05 volts. The advantages of adding such a squelch circuit are many and worthwhile. Once you have used a receiver so equipped, you too will probably consider squelch an essential control. . . . K4UWX

Good old



Charlie Queen

Ralph Morris WIQUE

The other night when all the shows in Tennessee Valley had the odor of our local Clark's Cove mud flats at low tide, I placed a pair of cans on my dit happy head. After shooting the 60 cycles to my cabinet of used tubes, my hearing aid came to life. It was then that I heard a Space Jockey calling a Charlie Queen. Not being the type of fellow that drinks and shoots electrons into space at the same time, I put my glass of milk back into the ice-box and slapped the AC to the 55½ pounds of #12 that I got from an old battery charger. As soon as my 1A2's got red on the plates, the neighbors buzzed my land line and I knew for sure that I was on the air. As the XYL answered the twisted pair, giving the names of our local TVI committee to the Video Ranger that called, I gave the Space Jockey calling Charlie Queen a long shout. My signal must have punched a large hole in the QRM, because this Space Jockey started to pump my call letter down the coax and into my hearing aid. At once I knew that I had snagged a DX station. This RF Jockey lives a good five city blocks away from my QTH! He at once thanked me for shouting at him and gave me 10 Dog Biscuits. This made Duke, the canine member of our little family very happy. He also reads the mail.


My contact then told me that he had his rig mounted on a bread board. Knowing that most bread comes already sliced, there must be plenty of these boards on the surplus market. He did however put a good signal into my bucket of tubes, in fact enough to make my cans rattle. At this point I switched to my Pretty Mary Squacker, and gave this Space Jockey an RST report of 5 square. I could not give him a true reading from my S meter, as it is one that I picked up at a surplus store and only reads "The Flow Of Fuel Per Hour." He told me that he could not have a long winded Rag Chew at this time as his favorite gun-slinger would soon appear on the one-eyed monster. He thanked me for the shout and the QSO which he said was Real Arm Chair Copy all the way. He asked me to send him some wall-paper for his shack. I told him that I would send his wall-paper by the next Pony Express. I thanked him for the chew as I sent him 73. Then I slung it back at him to tie the ribbons on it saying that I would see him down the log. After that I pulled the Main and slapped his name along with his XYL's handle on the log. I must finish this now, for some Joaker in a white coat is standing in back of me with a big net,——"Must be a TVI Complaint!"

Transceiving

Dean Cupp W4JKL

DID you ever build a transceiver and end up with a switching circuit using so many contacts you didn't know what to do? Relays and switches with many contacts are expensive and are more subject to failure. If you share this common problem Fig. 1 may be for you.


V1 is an ordinary class C power amplifier, V2 is the controlled stage. When the power amplifier is operating a negative voltage is developed across R1, the grid bias resistor. Since this negative voltage is only present during transmit it may be applied to the control grids of one or more stages of the receiver driving the tube(s) to "cut off." In this condition no (or very little) plate current is drawn and no signal is passed. AVC acts the same way with a very strong signal.

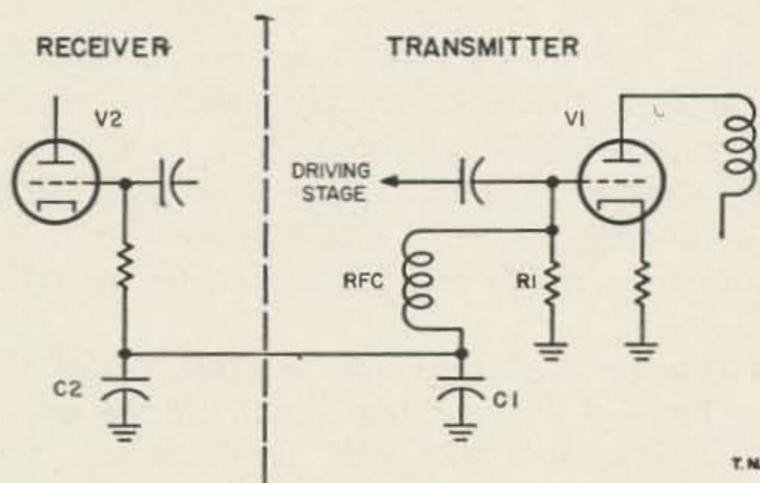

RFC, C1, and C2 are to prevent robbing V1 of drive or interfering with the operation of the controlled stage, and should be values appropriate to the frequencies used. (C2 will probably be larger than C1.) C1 and C2 are in parallel, as the lead could pick up a signal causing interference to the circuit at the end un-bypassed. Check to see that you have enough negative voltage across R1, or in the case of a higher powered transmitter, R1 could be made a voltage divider. It is recommended that the mixer and audio stages be controlled. Happy soldering and 73.

... W4JKL

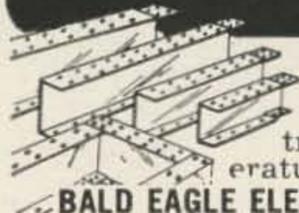TAKE THE SHEET METAL GRIEF OUT OF ELECTRONICS



Preformed sections make chassis and boards easy to assemble and wire! Makes electronics fun. Write for **FREE** literature on new circuit technique.

BALD EAGLE ELECTRONICS DEPT. 2 LA CROSSE, WIS.

TRI-BAND-QUAD

\$1.00 Foreign postage 15¢ extra
COMPLETE PLANS

- No Stubs
- High F to B
- Very Broad
- High Gain
- Low S. W. R.
- 30 Lbs. Max.

BARRINGTON SPECIALTIES,
Box 154-S, Barrington, R. I.

CO-AX CONNECTORS

All are **BRAND NEW**, current production to latest mil specs.

			postage prepaid
PL-259	45¢ each;	5 for \$2.00;	5 for \$2.20
SO-239	40¢ each;	5 for \$1.85;	5 for \$2.00
PL-258	55¢ each;	5 for \$2.65;	5 for \$2.90
UG-175/U	11¢ each;	10 for \$1.00;	10 for \$1.25
UG-176/U	11¢ each;	10 for \$1.00;	10 for \$1.25
UG-173/U*	9¢ each;	12 for \$1.00;	12 for \$1.25
M-359*	23¢ each;	5 for \$1.00;	5 for \$1.25

*Unused military surplus, clean and bright. Orders for Illinois delivery, please add 4% to net prices.

Manufacturers and dealers, inquire our "out of this world prices" on lots of 1,000 or more.

"GOODIE" sheet with every order.

BC ELECTRONICS

2333 S. MICHIGAN AVE.
CHICAGO 16, ILL. CALUMET 5-2235

HAVE YOU EXPERIENCE IN DESIGNING RADIO EQUIPMENT?

SSB? VHF? TRANSMITTERS? RECEIVERS?

You may fill an important place in our Engineering Department. Engineering degree preferred. Call or write Milt Sullivan, K8YDO, Chief Engineer.

R. L. DRAKE COMPANY, MIAMISBURG, OHIO

TELETYPEWRITER EQUIPMENT • COLLINS

51J2, 51J3, R-390A/URR Receivers (.50-30.5 MC). Teletype Printers #14, #15, #19, #20, #26, #28. Kleinschmidt Printers #TT-4A, TT-76, TT-98, TT-99, TT-100, GGC-3. Teletype Frequency Shift Converter. For general information & equipment list, write to **TOM, W1AFN, ALLTRONICS-HOWARD CO.,** Box 19, Boston 1, Mass. Richmond 2-0048.

Spotting Simplified

George Thurston W4MLE
3407 Prock Drive
Tallahassee, Florida

THE Heath Apache and other transmitters are equipped with shiny bright red "spotting" buttons which, according to the manufacturers, are supposed to let you find your own signal in the receiver without putting a signal on the air.

But in practice, it often takes two left hands or an assistant operator to do the job in less time than it takes to tune up the rig on a new band.

These "spotting buttons" generally do nothing but turn on the VFO (and all subsequent stages) without actuating the antenna change-over relay or receiver muting device.

In phone operation this is usually OK, except that the signal is often so strong you can't zero a weak signal accurately because you just can't hear the beat note.

CW operation goes something like this:

(1) You find an S-5 DX signal down the band calling CQ

(2) Turn off B-plus to the final

(3) Hold the "spotting button" down with one left hand

(4) Turn the VFO knob with the other left hand

(5) Reduce the receiver RF gain with the right hand to avoid arcing between your ear drums as the "spotting" signal screeches into place.

(6) Restore B-plus to the final and restore Rx gain to normal.

Failure to kill B-plus, of course, defeats the purpose of the spotting switch. Since the switch in effect simply closes the key, you'd put a carrier on the air if the final B-plus stayed on.

The solution—in the Apache, DX-100, or almost any other transmitter of whatever make—is a simple DPDT relay with a 6.3v AC coil.

The relay is connected so that one pair of contacts will close the key line when the relay pulls in.

The other pair of contacts disconnects the plate voltage from the buffer and/or driver stages following the VFO. This automatically keeps the spotting signal off the air.

The former "spotting" button on the front panel may now be used to close the circuit to the relay coil. A still better system, however, is the one I've installed in my Apache.


The switch lead for the relay coil is brought out through the accessory plug and connected to a micro-switch mounted next to the key. Thus, simply by moving my forefinger from key to switch toggle, I can actuate the relay, leaving my (only) left hand free to twist the VFO knob.

With only the driver stage disabled by the relay, I found the spotting signal still too strong for comfortable CW work. So I rigged it to cut off plate voltage to both the buffer and driver. This worked fine for CW but gave too weak a signal to use on strong phone signals.

The solution was a two-position rotary switch mounted on the front panel in the place formerly used by the "spotting" pushbutton. In one position, this switch causes the relay to kill only the driver. In the other position, the relay kills both the driver and buffer.

Spotting with this arrangement is absurdly simple.

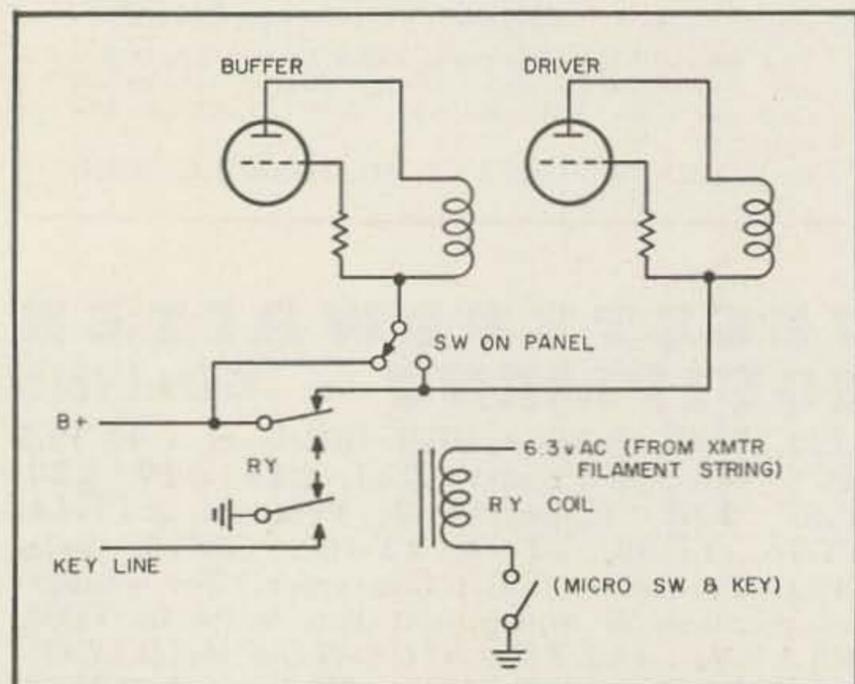
- (1) Hit the spotting switch at the key
- (2) Twist the VFO knob
- (3) Release the spring-return spotting switch.



CUTS WIRING COSTS!

**PLUG-IN
MASTER POWER
CONTROL
BOX**

MODEL 24
\$8.50

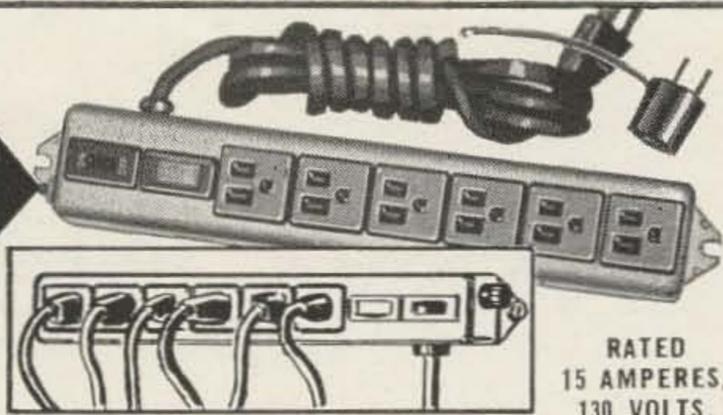

RATED
15 AMPERES,
130 VOLTS.

OFFERS YOU 6 SOCKETS WHERE YOU NOW HAVE 1

Heavy duty features insure long-life and complete utility for use on equipment or in shop or plant!

SEND FOR LITERATURE

QUOTATION FOR SPECIAL UNITS ON REQUEST

WABER ELECTRONICS, INC.

Hancock & Somerset Sts. Phila. 33, Pa.



- Panel Mounted Fuse
 - On-Off Switch
 - Pilot Light
 - Tough U. L. Cordset
 - Molded Plug
 - U. L. Approved Components
 - Mounting Ears
 - Silver Gray Seamless Hammertone Case
 - "U" Ground Receptacles
 - Adaptor Free
- Model 24CB (Circuit Breaker Type) \$10.50

Coax VS Open Line

Bill Roberts W9HOV
Gain, Inc.

Sometimes progress does more harm than good. World War II brought us the coax cable. Almost every amateur has used it in or around the shack. Up to the point when cable became available for amateur use,

everyone used a variation of open wire feed. We feel that we should make a box score on this old feed style and let you decide which is best. Score it honestly and let the chips fall where they may:

<i>Weight</i>	<i>Open Wire Light</i>	<i>Coax Heavy</i>
Losses mount heavily with High SWR	No	Yes
Will excessive losses render Line Inoperable	No	Yes
Will insulation burn through	No	Yes
Losses at 220 mc (100 feet) Pwr pct.	6 per cent	80 per cent
(using 144 mc	4.8 per cent	70 per cent
RG58U as 50 mc	2 per cent	46 per cent
com.) 14 mc	1 per cent	14 per cent
Cost	Cheap	Expensive
Deterioration with age	Negligible	Noticeable
Capitance in mmfd	0 (virtually)	28.5
When used as untuned line	Good	Questionable
Precautions for water on the line	None	Must be sealed
Effected by nearby objects	Some	Very Little


Now that I have given the pros and cons, it would seem that the score is 10 to 1 in favor of open line.

Let's assume we have a 2 meter antenna 100 feet in the air. Using coax all the way could result in the loss of 70 per cent of the power. Using open wire cuts this to a 4.8

per cent loss (1/14). After reaching the shack it should be converted (balun) to coax. This takes a little matching but maybe the saving of 65 odd percentage points of power makes it well worth the "trouble?"

We are not asking you to go to open line, we are just asking if you can afford not to.

New, New

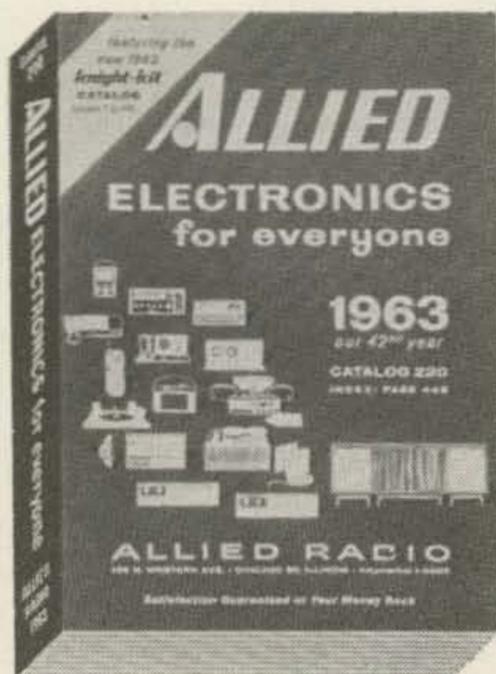

The Biggest

Allied Radio is not only a good 73 supporter, but they also have an interesting line of ham gear and test equipment that they turn out. The Allied catalog has for years been considered the most complete parts and equipment catalog available. The 1963 issue is now out and if you haven't already received one you would do well to let them know of your interest with a postcard. Mention 73.



Coax Switch

Bay Roy Electronics, well known for their coax relays, now has a cute little DPDT coax switch which will work at frequencies up to 3000 mc. The switch will handle 100 watts and has BNC connectors. Drop a line to Bay Roy for prices, 16608 Madison Avenue, Cleveland 7, Ohio.



HE-45


HE-50

Lafayette Radio is coming out with new ham gear so fast that it is difficult to keep up with them. Their newest releases are a pair of six and ten meter transceivers. The HE-50 is the ten meter model, runs twelve watts to a 2E26 final and uses the popular 7 mc crystals. The built-in dual 117 vac/ 12 vdc power supply allows the unit to be used either at home or in the car without changes or separate power supplies. Comes complete with push-to-talk mike for \$109.50, all set to go. The HE-45 six meter model is similar, using the 8 mc crystals and sells for the same remarkable price. The receivers are superhets with a 1650 kc *if* and an rf stage for good sensitivity and rejection of images. Both are 15 pounds, great for portability. Write Lafayette, 111 Jericho, Syosset, N. Y. or just buy one from this writeup or their ad on page 3.

Heath Catalog

The Heath Company is getting out a larger and larger catalog every year. Now it's beginning to look more the size of a Sears catalog. If you can read the latest catalog without eating your heart out for all that ham gear then you're suffering from a lack of imagination. Boy, if I had money could I tear into an order blank! Heath has more ham gear than any other classification, too! Write to Heath for their new 100 page catalog. Benton Harbor, Michigan.

**NEW FROM PEL
GRID DIP METER**

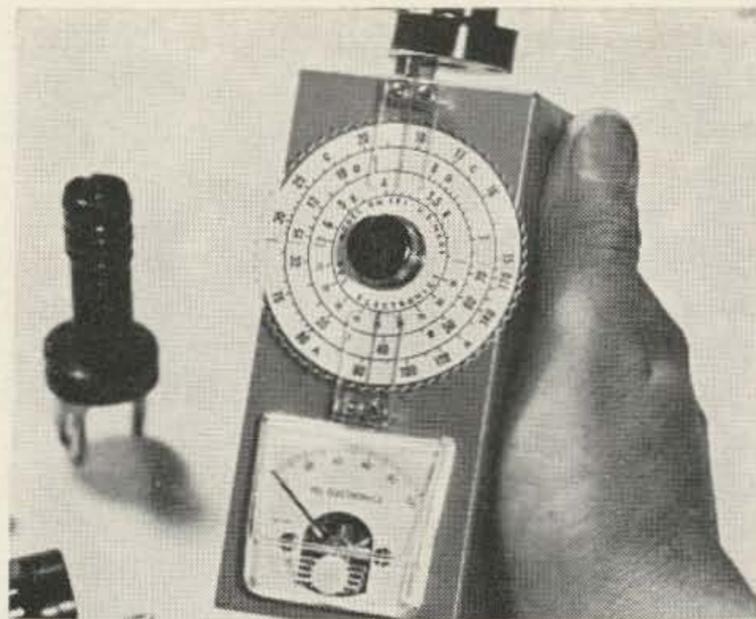

PEL ELIMINATES THE ~~GRID~~

AND FREES YOU FROM POWER LINES

TRANSISTORIZED • BATTERY POWERED • CONVENIENT ONE HAND OPERATION • WEIGHS ONLY 14 OZ. • LETTER KEYED COILS AND SCALES • FREQUENCY RANGE 3.5 TO 230 MC. • EPOXY COATED COILS WITH RELIABLE BANANA PLUGS.


KIT \$29.90 • ASSEMBLED \$39.90
SEND FOR TECHNICAL BULLETIN

Another Exclusive Item — TRANSISTORIZED SIGNAL GENERATOR • 135 KC. TO 120 MC. • CB XTAL SOCKET ON FRONT PANEL.

KIT \$34.90 • ASSEMBLED \$54.90
At Better Dealers


PEL ELECTRONICS

214 MAIN ST. • HACKENSACK, N.J.

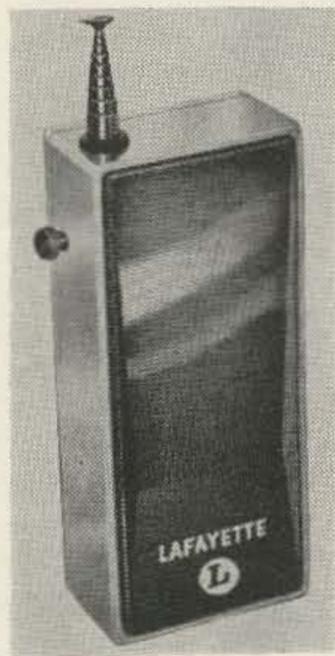

CB Walkie-Talkie

While we don't ordinarily pay much attention to the new CB gear that is announced, this one looks worth a mention. Lafayette's HE-66L CB Walkie-Talkie sells for \$19.95 each and uses crystal control for both receive and transmit, plus a superhet circuit in the receiver! Four transistors and a diode are used. Complete with leather carrying case, antenna, crystals and batteries. 85 mw power so you don't even have to have a CB license to use it. A pair of these (\$38.95) are mighty handy around any ham shack. Lafayette Radio, Syoset, L. I., N. Y.

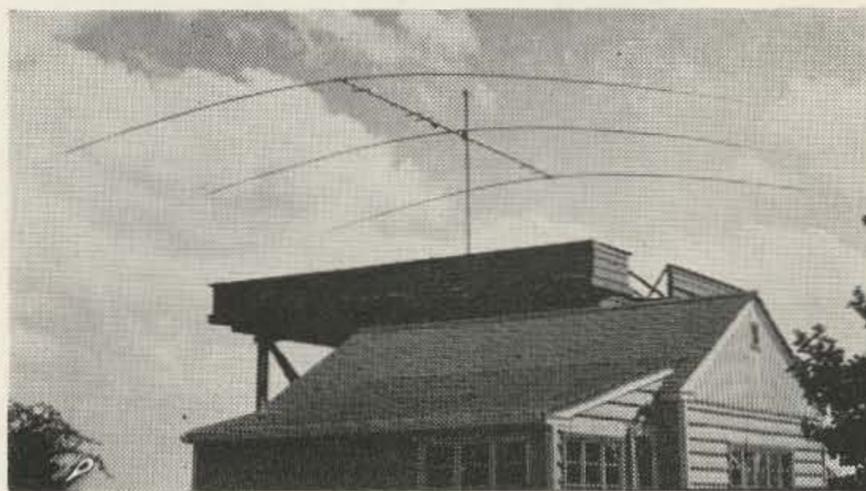

Bigger Than a House

The Telrex full size 40 meter beam, complete with 46' boom! Price? \$725.00 without the cottage.


Books

Radio Frequency Systems is the first volume of the **Modern Communications Course** written by Mr. Edward M. Noll, W3FQJ, and published by Howard W. Sams and Co., Inc., of Indianapolis, Indiana. It is designed to fit with others in the course to give a practical and comprehensive coverage of radio communications. The reader is assumed to have a basic understanding of radio receiver

operation and some fundamental knowledge of electronics. However, basic theory and modern design concepts are included in each volume.

Radio Frequency Systems contain comprehensive coverage of Radio Fundamentals, Class C Amplifiers, Oscillators, Exciters and Frequency Multipliers, Power Amplifiers, Antennas and Lines, Antenna Matching and Tuning Systems, and Transistor R.F. Circuits. Although the course is primarily intended for use as a classroom text, the style of writing is so explicit that it is readily usable for home study. This should prove a worthwhile addition to your library. Price: \$4.95. H.P.

Having Fun With Transistors is another Howard W. Sams Photofact publication by Ken Buckwalter. If you have any old oatmeal boxes laying around, this is the book for you. There are thirteen simple transistor circuits that you can amaze and mystify your friends with. Sample chapters: Home Broadcaster, The Speaker Mike, "Boris" the Talking Skull, and the Musical Oatmeal Box. Aside from a brief chapter on construction hints, there is nothing specifically for the ham. L.T.

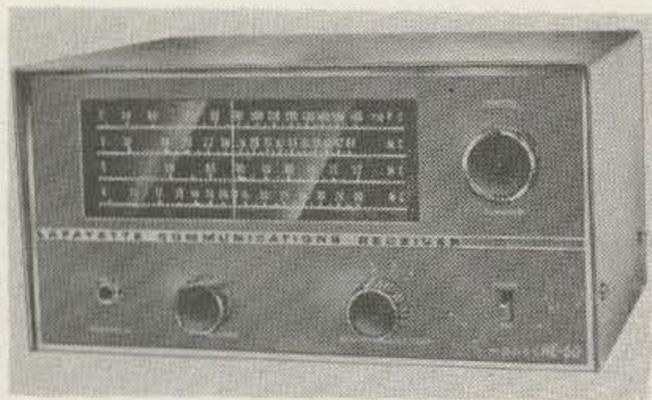

General Coverage Receiver

The Lafayette HE-60 covers from 550 kc to 30 mc in four bands and is priced at only \$39.95. Three tubes plus diode for five tube performance. Built-in speaker. Superhet circuit, bfo, etc.



SWR Bridge

Lafayette has come out with a power meter and SWR Bridge. This is designed for CB use

primarily, but is quite useful for ham applications up to 50 mc and up to 15 watts, which covers a lot of territory. The SWR function will handle up to 1 kw, but the power meter is limited by the 15 watt dummy load built in. Model TM-58 (\$27.95). Lafayette Radio, Syosset, L. I., N. Y.

The Inverted Vee-Beam

Paddy Labato W8DLU


YOURS Truly—may or may not have been the inventor of the Inverted Vee antenna, however in 1926 I discovered that by slanting two wires earth-ward I began getting better reports from my one tube CW transmitter than with a horizontal Vee and long wire antenna that I previously had been using.

Through the years since that time I have tried every conceivable type of antenna from the bed spring to the super rhombic, etc., but for all-around performance, simplicity of construction, ease of feeding and pruning I give the Inverted Vee top honors.

During the past year I have been using a modified form of the vee which I call The Inverted Vee-Beam. And I have found results most gratifying. From W8DLU running 150 to 250 watts I have proof of WAC with QSL's from most all of Europe, S. Africa, S. America, Pacific Islands and Japan, all on 80 meter CW, and Europe, S. America and Pacific on 75 meter AM fone.

As many readers know, the Vee can be hung from house top, tree, window ledge, borrowed utility pole etc. I have selected to use a 25 foot mast above the house top with pulley hung thereto for raising or lowering antenna at will. The reflectors as shown here may or may not be used but I have found that besides providing extra gain they also serve as extra guy wires.

Due to slight rise in resonant frequency when slanting wires toward ground, the Inverted Vee will require slightly longer legs than the standard dipole requirements. Coax cable of most any type may be used for feeding if builder intends to work within 50 to 100 kilocycles of desired portion of given band. However, for covering an entire band such as 80, 75 and 40 meters with one antenna, it is suggested that open wire feeders with a suitable antenna coupler be used. In making checks with other hams in this area I have found that 300 ohm TV twin lead and/or the com-

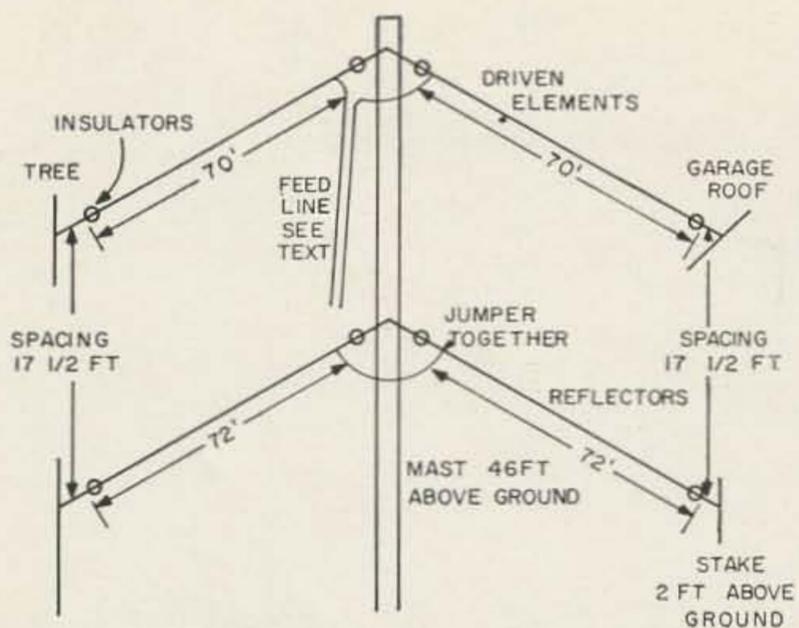

mon 1 inch spaced open wire line that is used in some TV installations also make suitable feeders for the Inverted Vee. The coupler used at W8DLU is on the order of one described in March 1959 QST (McCOY). If open wire or twin lead is used it is desirable to cut feeders $\frac{1}{4}$ or $\frac{1}{2}$ wavelength long. However if slightly shorter or longer line is necessary the antenna coupler will tune out enough reactance for desirable operation. Coax feedline may be of any length.

Dimensions as shown here are for 80 meter antenna and may be cut in half for a 40 meter antenna and so on for 20 meters. However keep feed point as high as possible. You will note through checking with grid dipper or SWR bridge that these measurements may not hold true for you. This is due to ground conductivity, surrounding objects, etc. The simplest way is to add or cut antenna length for the lowest SWR reading.

Some readers may ask, how can reflectors directly beneath the antenna act as reflectors? Will they reflect skyward or what? As far as I can determine, the Inverted Vee is a semi vertical-semi horizontal antenna. While making field strength checks we have found strongest lobes off the upper portions of the antenna and those lobes increased further along the antenna legs with the use of reflectors. Signal reports especially from DX were stronger when reflectors were used. ... W8DLU

TONS OF AMATEUR EQUIPMENT IN STOCK

WESTERN RADIO
SAN DIEGO

1331 India Street BE9-0361

MON - FRI 8:30 to 8:00 SAT 8:30 to 5:00

National Wide-Band FM Calling
and Working Frequencies

52.525 mc 146.94 mc



TR SWITCH
(TRANSMIT/RECEIVE SWITCH)



MODEL 381B

An electronic antenna changeover switch. Transmitter is continuously connected to antenna, antenna circuit to receiver is blocked during transmit. No switch contacts to arc or burn. Switching is instantaneous. Selectable band-switching insures no loss in receiver sensitivity. Substantial gain in receiver sensitivity results in most installations. Ideal for break-in operation on CW, SSB and AM. Bandswitch conveniently located on front. Three coax connectors are mounted on rear. Conservatively designed for full legal power. Operates from 115 volts, 60 cycles. For 52.75 ohm lines.

Size 4 3/4" x 4" x 5 1/2"

BARKER & WILLIAMSON, Inc.
Radio Communication Equipment Since 1932
BRISTOL, PENNSYLVANIA • Stillwell 8-5581

DOW-KEY DK60 SERIES

4 VERSATILE MODELS
A.C. or D.C.



COAXIAL RELAYS

Also Available with Type C, TNC, BNC, N & UHF Connectors

Outstanding favorite for amateurs . . . Versatile combinations for industrials! Low VSWR — less than 1.15:1 from 0 to 500 mc. LOW LOSSES . . . High Contact Pressures. LOW CROSS-TALK through use of patented "isolated connector" arrangement. HIGH POWER RATING. All coils encapsulated in epoxy resin for quieter operation and resistance to moisture.

- ★ UNCONDITIONAL GUARANTEE for one year. (We will repair if faulty within 1 year.)
- ★ All Relays in weatherproof boxes for exterior installation.
- ★ Ganged, multiple position switch arrangement available for remote control selection of antennas.
- ★ See one of our 700 dealers and distributors in U. S. and Canada for catalog sheets or write:

STANDARD RELAYS: DK60, DK60-G, DK60-2C and DK60-G2C —

PRICED FROM . . . \$12.45

DOW-KEY COMPANY
Thief River Falls, Minnesota

Choke Evaluator

Ronald Ives
2075 Harvard Street
Palo Alto, California

IT is customary and traditional in electrical and electronic work to evaluate large inductances by use of an impedance bridge, an instrument so costly that few amateurs and experimenters can afford it. Impedance bridges range in price from a kit (Heath IB-2A), costing \$69.95 plus several evenings of work, to beautiful laboratory instruments costing about as much as a new car. Unless the bridge is to be used many times a day, or in work where precision is of great importance, its purchase is not usually justified.

More than a decade ago, when the grid-dip oscillator became a standard laboratory instrument, it was found that small inductances could be evaluated by shunting them with a known capacitance, and then determining the resonant frequency of the circuit. From this, the inductance was computed. This method works very well indeed for radio and *if* frequencies, but is impractical for large inductances, because few grid-dip oscillators will go low enough in frequency, and the *Q* of large choke coils is so low that a nonambiguous resonance point is hard to find.

There should be some method of evaluating large chokes by use of ordinarily-available shop instruments. There is! Requisites are a voltage source of known frequency, a low drain multimeter or ac VTVM, a resistor of known value, and some brains.

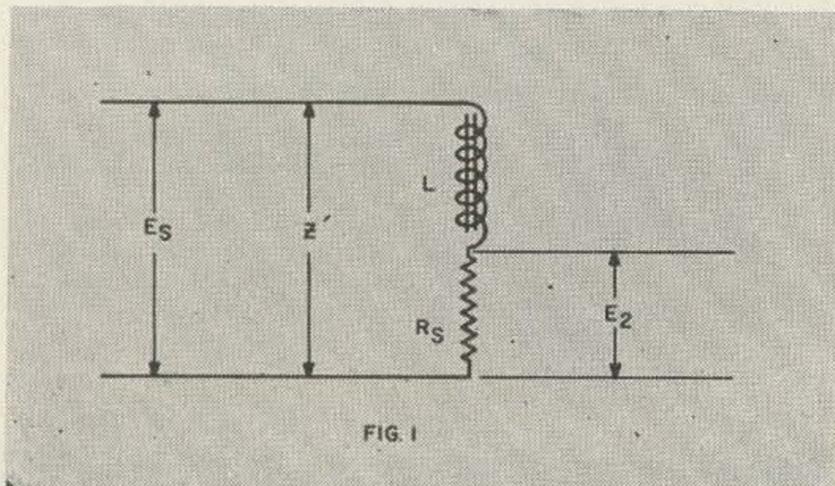


Fig. 1 Simple ac circuit containing inductance and resistance.

In any ac circuit, such as that of Fig. 1, containing both inductance and resistance, the impedance can be found from the ac adaptation of Ohm's law:—

$$1) \quad Z = \frac{E_s}{I}$$

In which:—

Z = impedance of circuit (ohms)
 I = current through circuit (amperes)
 E_s = supply voltage (volts)

Quite obviously, E_s can be measured directly by use of the multimeter or ac VTVM. Current through the circuit, I , seems to be a problem at first, as few amateurs or experimenters have access to an ac milliammeter. However, known the value of R_s (we can measure it with the multimeter if necessary), and the voltage drop across it (measure it with the multimeter or ac VTVM), E_2 , we can compute the current through the circuit from:—

$$2) \quad I = \frac{E_2}{R_s}$$

Substituting these obtained values in (1) gives us the impedance of the circuit of Fig. 1. Computation is simplified if we combine the formulae, by substitution, obtaining:—

$$3) \quad Z = \frac{E_s R_s}{E_2}$$

Even though we know the impedance of the entire circuit, we still cannot compute the inductance of the choke by any reasonable method, as most chokes have a finite internal resistance, which must also be taken into consideration. Actual circuit, in the configuration of Fig. 1, taking into account the internal resistance of the choke, R_i , comprises Fig. 2. Impedance of this circuit, already found experimentally from (3), is also given by:—

$$4) \quad Z = \sqrt{(R_s + R_i)^2 + (X_L)^2}$$

Radio Xmasshop

Give generously this year to the needy . . . yourself. You certainly need to do something about that scattering of worn out grimy books you call a library. Ogle the below and pick out some good ham literature for yourself. Surprise yourself with a goodly supply of these carefully chosen reference books. Select either by title, writeup or at random, you can't lose. Money back if not tickled pink.

- 4—**RADIO AMATEUR CALL BOOK**—Fall Edition. \$5.00
- 5—**ANTENNAS**—Kraus (W8JK). The most complete book on antennas in print, but largely design and theory, complete with math. \$12.00
- 13—**REFERENCE DATA FOR RADIO ENGINEERS**. Tables, formulas, graphs. You will find this reference book on the desk of almost every electronic engineer in the country. Published by International Telephone and Telegraph. \$6.00
- 18—**SO YOU WANT TO BE A HAM**—Hertzberg (W2DJJ) Second edition. Good introduction to the hobby. Has photos and brief descriptions of almost every commercially available transmitter and receiver, plus accessories. Lavishly illustrated and readable. \$2.95
- 21—**VHF HANDBOOK**—Johnson (W6QKI). Types of VHF propagation, VHF circuitry, component limitations, antenna design and construction, test equipment. Very thorough book and one that should be in every VHF shack. \$2.95
- 22—**BEAM ANTENNA HANDBOOK**—Orr (W6SAI). Basics, theory and construction of beams, transmission lines, matching devices, and test equipment. Almost all ham stations need a beam of some sort . . . here is the only source of basic info to help you decide what beam to build or buy, to install it, how to tune it. \$2.70
- 23—**NOVICE & TECHNICIAN HANDBOOK**—Stoner (W6TNS). Sugar coated theory: receivers, transmitters, power supplies, antennas; simple construction of a complete station, converting surplus equipment. How to get a ham license and build a station. \$2.85
- 24—**BETTER SHORT WAVE RECEPTION**—Orr (W6SAI). How to buy a receiver, how to tune it, align it; building accessories; better antennas; QSL's, maps, aurora zones, CW reception, SSB reception, etc. Handbook for short wave listeners and radio amateurs. \$2.85
- 28—**TELEVISION INTERFERENCE**—Rand (W1DBM). This is the authoritative book on the subject of getting TVI out of your rigs and the neighbors sets. \$1.75
- 32—**RCA RADIOTRON DESIGNERS HANDBOOK**—1500 pages of design notes on every possible type of circuit. Fabulous. Every design engineer needs this one. \$7.50
- 40—**RADIO HANDBOOK, 15th EDITION**—Orr (W6SAI). This is far and away the best amateur radio handbook ever printed. Over 800 pages. \$8.50
- 45—**CURTA COMPUTER**. The world's smallest computer. Send for detailed information. Makes the slide rule look sick. Like a big Monroe computer only hand size. \$125.00
- 52—**HOW TO READ SCHEMATIC DIAGRAMS**—Marks. Components & Diagrams; electrical, electronic, ac, dc, audio, rf, TV. Starts with individual circuits and carries through complete equipments. \$3.50
- 53—**BASIC ELECTRONIC TEST PROCEDURES**—Turner. This book covers just about every possible type of electronic test equipment and explains in detail how to use it for every purpose. Testing: audio equipment, receivers, transmitters, transistors, photocells, distortion, tubes, power . . . etc. \$8.00
- 55—**TRANSISTOR CIRCUIT HANDBOOK**—Simple, easy to understand explanation of transistor circuits. Dozens of interesting applications. \$4.95
- 63—**G.E. TRANSISTOR MANUAL 6th EDITION**. \$2.00
- 66—**DESIGN MANUAL FOR TRANSISTOR CIRCUITS BY CARROLL**. Tested transistor circuits for design engineers. Interesting reading too. \$9.50

67—**TRANSISTOR CIRCUIT ANALYSIS AND DESIGN** by Fitch. Written primarily as a college text to teach circuit design. \$13.00

68—**HANDBOOK OF TRANSISTOR CIRCUIT DESIGN BY PULLEN**—This is a handbook which teaches a systematic system for transistor circuit design. Highly recommended by radio schools. \$13.00

74—**HANDBOOK OF ELECTRONIC TABLES & FORMULAS**—Formulas & laws, constants, standards, symbols and codes. Math. tables, misc. data. \$2.95

76—**MODERN OSCILLOSCOPES & THEIR USES**—Ruiter. Second edition. Shows what a 'scope is, what it does and how to use it for radio, TV, transmitters, etc. 346 pages. \$8.00

G94—**TRANSISTORS**. Selected articles from Radio Electronics on how to test transistors and how to build all-transistor test equipment. \$1.95

731—**HAM-TV-W Φ KYQ**. This is the only book available on this fascinating branch of ham radio. Describes complete ham TV station that costs under \$50. Very simple. \$3.00

734—**INDEX TO SURPLUS**—Bibliography of all surplus articles printed in all radio magazines to date. Brief description, etc. \$1.50

735—**BOUND VOLUME**—October 1960 through December, 1961, 15 issues (Vol. 1). \$15.00

736—**Yearly Binders for "73" Magazine** October 1960 through 1961, or 1962. \$3.00

738—**SIMPLIFIED MATH FOR THE HAMSHACK BY K8LFI**—Unbelievably simple explanation of Ohm's Law, squares, roots, powers, L/C, logs and the slide rule. No student should be without this booklet. 50c

739—**COILS** by K8BYN—Wonderfully written and illustrated through discussion of coils, their resistance, reactance, impedance, Q, and distributed capacitance. 50c

R235—**RADIO CONTROL FOR MODEL BUILDERS**—Winter. One of the best and newest books available on RC. \$4.25

R245—**HOW TO USE GRID-DIP OSCILLATORS**—Turner (K6AI). Construction & uses, an important book. \$2.50

MMD—**ELIMINATING MAN MADE INTERFERENCE**—What makes it, how to find it, how to cure it in homes, factories, automobiles, aircraft, boats, etc. Or maybe you haven't been plagued lately. 160 pages. \$2.95

NHP—**BUILDING UP YOUR HAM SHACK**—Pyle (W7OE). A practical discussion of points to consider when you are buying ham equipment, complete with descriptions of much of the available commercial gear. It's just possible that Pyle might keep you from making a mistake which would cost a lot more than his book. \$2.50

QAN—**SECOND CLASS RADIOTELEPHONE HANDBOOK**—Noll (W3FQJ). Everything you need to know to pass the FCC exam and get started servicing two-way equipment. Much more than just a Q & A manual \$3.95

Circle the book numbers you wish to order.
Please include cash, check, money order . . .
or something we can deposit in the bank.

Name Call

Address

City State

RADIO BOOKSHOP
1379 East 15th Street, Brooklyn 30, N. Y.
(N.Y.C. add 3% tax)

Add 8 1/2% to Canadian Checks

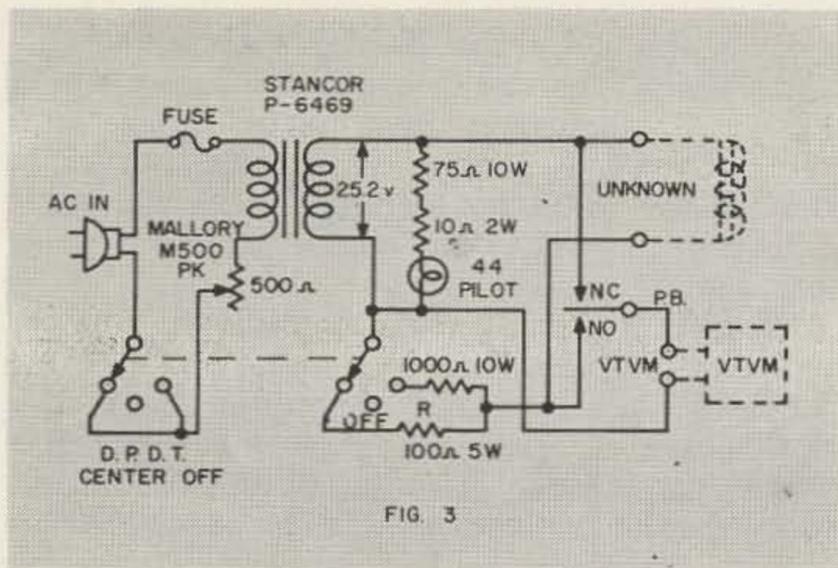


FIG. 3

Fig. 3 Circuit of choke evaluator.

ductances, both by this method and by use of a high-grade laboratory bridge, showed that the difference between the two methods seldom exceeded two percent, which is surprisingly good when it is noted that this simplified method minimizes the effects of distributed capacity in the choke by use of low frequency (60 cycles), whereas the laboratory bridge, by a series of somewhat involved measurements and computations, is supposed to eliminate its effects entirely.

These tests also showed that the actual measurement time, including computation, was shorter with the evaluator here described than with the more complicated bridge; but the set-up time—i.e. finding and connecting the instruments and components—was about half an hour. To stop this waste of time, which adds up to a considerable figure over a period of months, the essential parts of this choke evaluator were assembled in a bakelite utility box, using the circuit of Fig. 3, and made a permanent addition to the laboratory instrument stock. Parts actually used are noted on the diagram, but electrically equivalent parts of other manufacture will work just as well. Construction is extremely simple and noncritical, there being no high frequencies, high powers, or high resistances involved. Ordinary good workmanship will give entirely satisfactory operation.

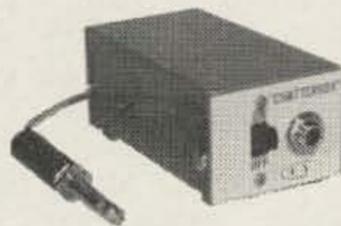


Fig. 4 Panel layout of choke evaluator.

THE CHATTERBOX!!!

ALL TRANSISTORIZED SPEECH CLIPPER-FILTER

Maintain Full Modulation—Multiply Audio "Punch"



- Rugged P.C. Board
- Not a Kit—Ready To Use
- No Modification To Xmitter.
- Self Powered—Batteries Incl.
- Shaped Audio Response
- High Q Toroid Filter
- True Clipper, Not Compressor

Phone Plug and Jack Standard—Other Types Available

C-Y ELECTRONICS
3810 E. 365th Street
WILLOUGHBY, OHIO


\$24.95 Postpaid
Ohio Res. Add 3%
Send For
Free Flyer

mars

STANDING WAVE BRIDGE

Measures both 52 or 75 ohms. Takes full kilowatt.


\$17.95

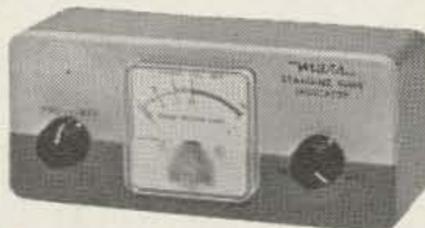

TRANSISTORIZED OSCILLATOR-MONITOR

Complete unit — 2 transistors. Pitch and volume controls.


\$14.95

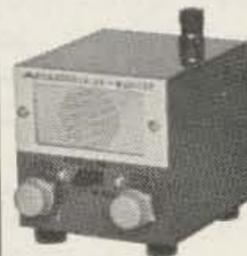

LOW-PASS FILTER

4 Shielded sections — Up to 80 db attenuation. 52 or 75 ohms — negligible loss.

\$11.45

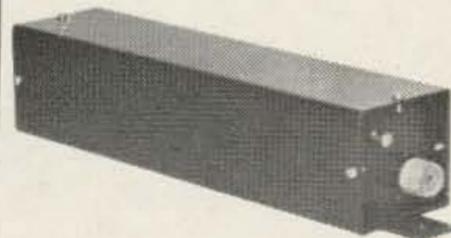

HYBRID PHONE PATCH

Use on AM or SSB. Built-in R.F. Filters. Gain controls, null controls. VU-meter.

\$27.95



PAUSAN COMPANY · SAN RAFAEL, CALIF.

ALL BAND AMATEUR RADIO TRAP ANTENNAS!



Reduces Interference and Noise on All Makes Short Wave Receivers. Makes World Wide Reception Stronger. Clearer on All Bands!

For ALL Amateur Transmitters. Guaranteed for 500 Watts Power for Pi-Net or Link Direct Feed. Light. Neat. Weatherproof

Complete as shown total length 102 ft. with 87 ft. of 72 ohm balanced feedline, Hi-impact molded resonant traps. (Wt. 3 oz. 1" x 5" long). You just tune to desired band for beamlike results. Excellent for ALL world-wide short-wave receivers and amateur transmitters. For NOVICE AND ALL CLASS AMATEURS! NO EXTRA TUNERS OR GADGETS NEEDED! Eliminates 5 separate antennas with excellent performance guaranteed. Use as inverted V for all band power gain. NO HAYWIRE HOUSE APPEARANCE! EASY INSTALLATION! 30-40-20-15-10 meter bands. Complete.....\$14.95 40-20-15-10 meter bands. 54-ft. ant (best for w-w swl's) 13.95 SEND ONLY \$3.00 (cash, ck., mo) and pay postman balance COD plus postage on arrival or send full price for postpaid delivery. Free information.

Available only from:

WESTERN RADIO - Dept. A7-11 - Kearney, Nebraska

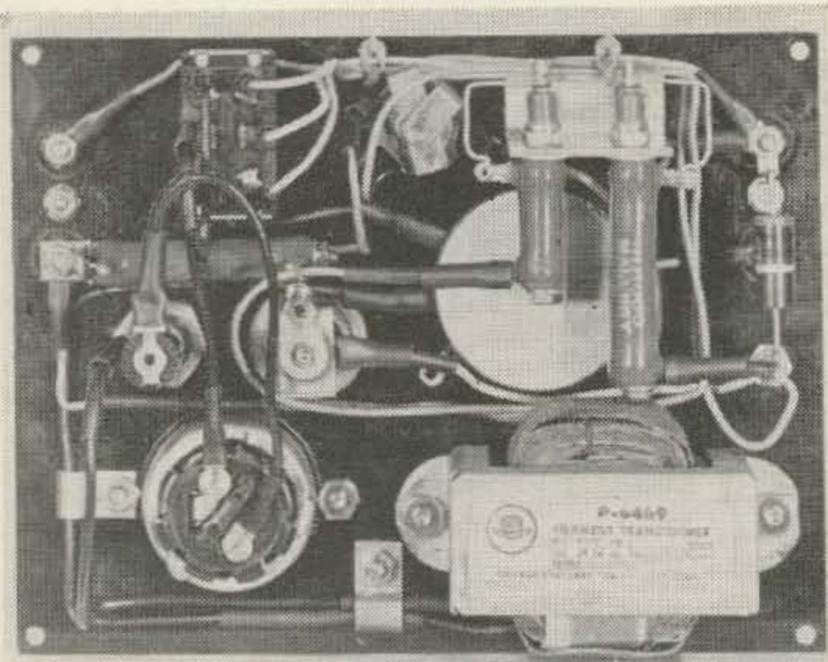


Fig. 5 Interior of choke evaluator.

Panel layout, shown in Fig. 4 is functional, and is designed for a right-handed operator. To simplify construction, and to eliminate long internal leads, all parts are mounted on the lid of the bakelite utility box (Smith #2257). Two series resistors, selectable by means of a double-pole double-throw center-off power switch, are provided, giving an effective measuring range in excess of from 0.1 henries to 100 henries. Panel labels are made

on Metalphoto, by the Kohler techniques¹.

Interior of the choke evaluator is shown in Fig. 5. Construction here is perhaps more rugged than is actually necessary, but it is much easier to make things a little stronger while building than to patch and fix at a later date.

Using this device, it is possible to answer the question "How many henries" in a little less than ten minutes. Obtained answers have been found entirely satisfactory in the frequency range from 60 cycles to about 3,000 cycles. As the frequency increases, the readings become less accurate and less consistent, due to distributed capacitance and core characteristics. Because of these extraneous factors, few cored coils have the same inductance at all frequencies.

Because of these limitations, this method of choke evaluation should be limited to selecting components for power and voice frequency filters only. Components for use in ultra-high-fidelity equipment, or for supersonic frequencies, should be evaluated either by use of an inductance bridge, or by use of an evaluator built on this general plan, but having a supply frequency nearer that at which the components will be used.

... Ives

¹Kohler, George M. *Prototype Labels*, Electronics, Vol. 33, No. 1, Jan. 1, 1960, p. 100 et seq.

Letters

Dear Wayne:

Just a short word of sincere thanks to you for the great pleasure I have each month in reading "73." The magazine is a work of art. In particular your own column is a veritable jewel and I wouldn't miss it for a mint.

As a Porsche aficionado and ex-newspaper editor I can well understand and appreciate everything that you muse about from the joy of driving a Porsche to the relentless pressures of producing a publication. And this is not to neglect the fine technical articles you feature in each edition. All in all, "73" is far and away at the top of the ham publications list.

I hope that you have found your new quarters in that lovely, huge New England mansion to be all that you had anticipated. Your description of the move was wonderful.

Best of luck on everything!

Mark McCormack K3LOVEA

Dear Wayne:

I was aghast to note your no smokee, no drinkee stand taken in your Sept. editorial. Heavens! Don't you realize, with a clean-lifer approach like that, you are ruining your chances of appearing in Camel cigarette ads (in full color) when you're rich and famous??

The above, plus your constant humor and slightly right-of-center stand, insidiously compels me to kick in another \$3.50 to see what happens next!

At the rate you are going, I can only conclude that

you honestly enjoy giving Brand x and OLD MEN fits! This cannot go unrewarded! Please renew me with the Oct. issue.

Terry F. Staudt W4WUZ

Dear Wayne:

You have reached me. Here is a check to help pay the wolf before he slips on the coming ice.

From past record this is for my economic protection. Every time I go to the store for the latest 73, I end up with too many ham type goodies and a torn up copy of the word. I figure the back issues have cost me about 700 dollars.

Hope you continue the fine work in the new QTH.

George A. Howland W4AIY

Dear Wayne:

I am just back from the convention at Disneyland. WOW!!!

What's all the talk about a staff of two for 73? I went up to the "73" booth to say "Hello" to you and Virginia. First thing I know this smiling YL is twisting my arm and crooning in my ear. "So what if you do already subscribe to '73'. You can extend your subscription at these terrific convention rates." She says.

OK, Says I—"So I'll extend" Maybe even pick up a couple of back issues for some friends who are not charter subscribers."

"Back issues" she says—"Sure but don't be cheap.

3 KW PEP "BALUN" ↓ \$16⁹⁵

NEW!
MODEL IV5C81
ONLY \$13⁹⁵

A COMPLETE MONO-BAND KIT - INCLUDES
5C1080 "BALUN", WIRE, INSULATORS
AND COMPLETE INSTRUCTIONS
TO PROPERLY INSTALL "BALUN"
on 80 or 40 or 20 or 15
or 11 or 10 Meter
HIGH PERFORMANCE INVERTED "V"
ANTENNA

1 KW PEP "BALUN" \$12⁹⁵

ALSO AVAILABLE -
3 KW PEP MODEL
IV3K81 \$17⁹⁵

MFG. UNDER TELREX PAT. No. 2,576,929
TELREX LABORATORIES ASBURY PARK N.J.

WRITE FOR FREE "BALUN" & INVERTED "V"
BOOKLET or PL-77 DESCRIBING 107 POPULAR ANTENNAS.

Get a binder to keep them in." "OK"—I said—as the arm starts to turn blue.

Just then up comes good old Jim WA6EUX—"How you doing—? Gracie." He says, "Fine" she says, still smiling—just fine." "Now how about a binder for your own copies" she says, applying a little more pressure.

"O.K., O.K.," I plead, shoving a \$20.00 into her eagerly waiting hand.

Please, Wayne, How many of these Green Sales Amazons have you turned loose on us? Do they all train by carrying 65 lb. packages of "73". Do they all look cute and feminine? Are they all married? Is Gracie Jim's XYL? and please can you tell me What will my 95 year old grandmother do with a life subscription to "73".???

I am very much against anonymous letters but if I sign my name I may find Gracie selling me two more maps and a forever subscription.

Dear Friend Wayne:

Nice contact the other day—sounded real FB from that new location. Also talked to one of your boys over your station a few days later in the week.

I have just been awarded the first and only Empire DX Certificate on Two Way SSB by the Radio Society of Great Britain. The award has been in existence for about 25 years and quite a few amateurs have won it on CW and AM phone, but I am the first amateur to qualify on SSB. This award took me five years to get the proper two way contacts.

Chas. W. Boegel, Jr. W6CVU

Good work Chuck.

Dear Wayne:

Why didn't you ask your readers to make donations to YOUR Building Fund?


Andy W3NL

I'd rather not.

Dear Sir:

Here is a stunt I have used . . . a selenium rectifier across a key or relay stops the inductive kick that sometimes can be heard in the receiver. Both Federal and International are making units for this purpose.

H. F. Watson W3ALY

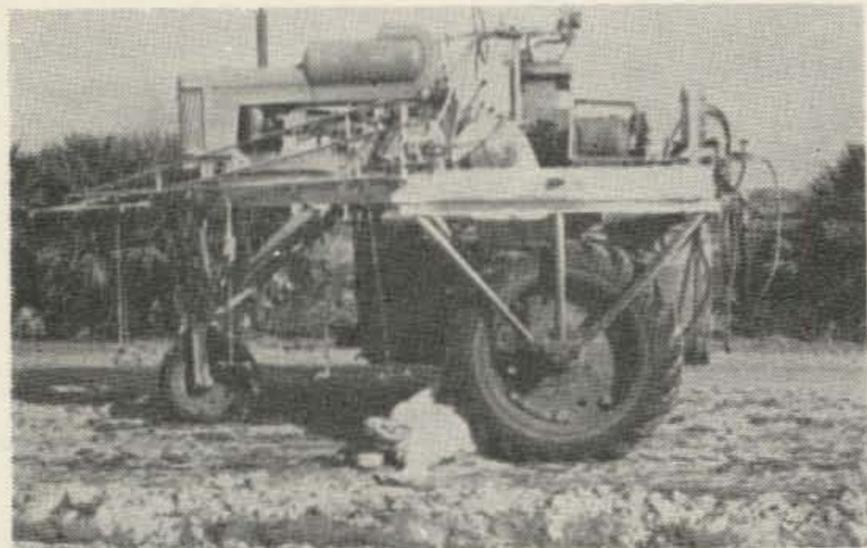

Dear Wayne:

I have, as you can see, been quite careful after subscribing to 73 for Life.

Vance V. Vogel W4OVE

Looks promising Vance. And thanks a megohm for the beautiful box of deadly nightshade fruit that you sent . . . it was delicious. Please send antidote.



Dear Wayne:

Thought you might like to see the vehicle in which your peripatetic Western Representative, Jim Morrisett, WA6EXU, mobiles about his territory. It must be seen to be believed, and even then it rather boggles the imagination.

Jim stopped by to see me one recent afternoon, but my camera wasn't handy at the time. Next morning, on my way to the office, there was Jim's Volkswagen bus, parked about 150 feet from the ocean. Had my camera along that time, and the enclosed photo resulted.

I'm not quite sure what kind of radiation pattern Jim must get from any of the antennas, but apparently they all work. The outer antennas are a stacked pair of six element two-meter yagis, and the center device is a two-meter "Dual Diversity" beam. I asked him what he did when he was mobilling along and wanted to work stations on either side of the highway. "I use the J," he said, and, sure enough, amongst that mass of aluminum tubing there lurks a J (right above the door, on the driver's side). Both Heath and Clegg VHF gear are installed in the bus.

I shuddered at the thought of high winds while traveling and their effect on this rather top-heavy arrangement, and the havoc low-hanging tree limbs could cause, but these have not—at least not yet—been problems to Jim.

And where was Jim when the picture was taken? Well, he was still sacked out in the bus (it is his mobile home-away-from-home) and if you look closely you may be able to see a big toe sticking up back there somewhere.


Richard F. Van Wickle, W6TKA
Santa Barbara, California

LEMONS - NO GUARANTEE POOR SERVICE - UNRELIABLE

WHY TAKE A CHANCE! FOR 26 YEARS WRL HAS SERVED THE HAM, PROVIDING THE BEST EQUIPMENT, FULLY GUARANTEED, PROMPT PERSONAL SERVICE, AT LOWEST PRICES. WRL IS THE "HOUSE THE HAMS BUILT."



Leo I. Meyerson, W0GFQ

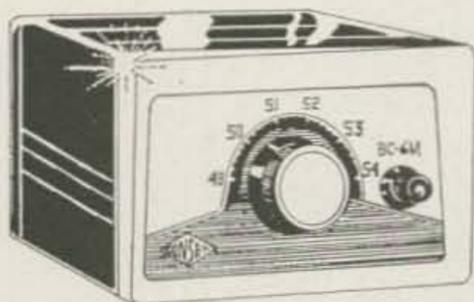

GONSET TUNABLE 6M CONVERTER

\$39⁹⁵

"Hot Special" on Brand New Gonsets #3275, 6 Meter MOBILE TUNABLE CONVERTER. Triple Conversion with Car Radio - Full 90 day Warranty.

12 VDC No High Voltage Required. 49/54 MC coverage. Plug into Car Radio - Built-in ANL. 6" x 8" x 4". Wt. 5 lbs. Wired.


Nationally advertised
for \$74.50.

6 Meter Vertical

The only colinear 6 Meter Vertical on the market. 13 feet high - self supporting. Provides over 3 DB gain on 6 meters. DX power gain by the 5/8 electrical wave vertical. Use 52 ohm wax feed-line. Shipping wt. 10 lbs.


\$29⁹⁵

Express Only.

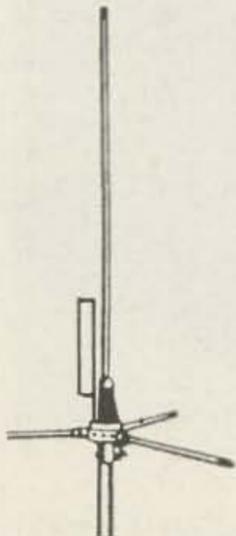

6 Meter Beam **\$12⁹⁵**

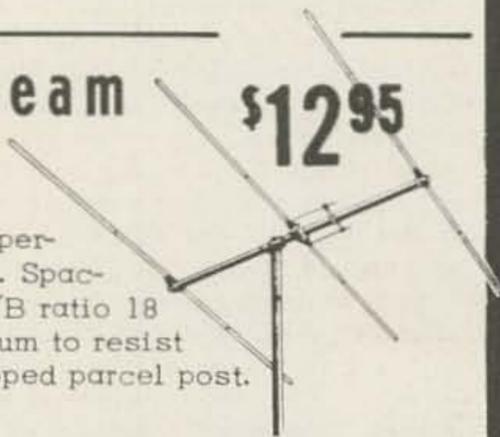Economical and great performance. Lightweight. Spaced for 6.8 DB gain, F/B ratio 18 DB. 4 1/2' boom. Aluminum to resist corrosion. Can be shipped parcel post. Wt. 6 lbs.



Antenna Tuner **\$10⁹⁵**


Universal "Longwire tuner". Use on any transmitter with

power input of 100 watts CW, 75 AM watts or less. Matches 52-75 ohm coax transmitter output to any end fed antenna wire 1/2 wave length or multiples. Reduces TVI. Steel case 4 x 5 x 4". Wt. 3 lbs. Kit.

WRITE FOR OUR FREE FLYER & LIST OF OVER 1,000 PIECES OF QUALITY RE-CONDITIONED EQUIPMENT.

WRL 12A Generator

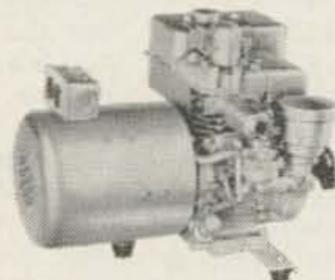- 1,250 Watts
- Briggs & Stratton motor
- Shielded Ignition
- Re-wind Starter



\$149⁹⁵

Multi-purpose portable (85 lbs.) generator—Emergencies—Field Days—Camping or Picnics. 120 VAC, single phase 60 cycle current at 1,250 watts. 4 cycle 3 HP engine with governor. Oil bath air concentric Float Carburetor. Automatic Recoil Rope Starter. Silent muffler—Shipping Wt. 100 lbs. (Shipped FOB Milwaukee, Wisc.)

WRL Multitester MT-100



\$11⁹⁸ VOM Multitester - Also Capacity - Inductance

Precision 1% resistors. Sensitivity 2,000 ohms/volt. All ranges. 16 position selector switch. Voltage (AC & DC) ranges, 0-1,000. Ohms (with zero adjust) 0-1 Meg. Current 0-1/2 mil, 0-500 mil. Measures capacity, .001-1 MFD. Inductance, 0-1000 Henry. Calibrated for both 50/60 cycles. Audio output scale - 20DB to +36DB. Metal case, plastic front panel. Size: 5-1/8 x 3 1/4 x 1". Sh. wt. 1 lb.

WRL

WORLD RADIO LABORATORIES, Inc.

3415 W. B'dway • Council Bluffs, Ia.

Hi Leo! Send me Gonset Converter 6M Vertical 6M Beam Ant. Tuner Generator Multitester Add to my Charg-A-Plan Check enclosed 73-11

Write for "Flyer" Special - FOB WRL.

Name _____ Call _____

Address _____

City _____ State _____





(1296 from page 8)

Construction Data



The entire converter was constructed on a 9½" by 5" brass plate 1/16" thick. Figs. 2 and 3 show the details of the cavity tuner. Silver plating of the cavity tuner is advisable but not essential. . . . W3HIX

Coil Data

- L1—7 turns #28 enam. coper wire space wound to occupy 5/16" on 3/8" dia. from slug tuned with powdered iron core.
- L2—4 turns #28 enam. copper wire interwound with low potential end of L1.
- L3—5¾ turns #18 tinned copper wire ½" I.D. air wound to occupy ½" output tap ½ turn from ground end.
- L4—5⅛ turns #18 tinned copper wire ¼" I.D. air wound to occupy 7/16".
- L6—13 turns #30 enam. copper wire spaced to occupy ½" winding area on ¼" form with powdered iron core (VHF Grade).
- L7—18 turns #30 enam. copper wire close wound on ¼" form with powdered iron core, ground tap 14½ turns from collector end.
- L8—4 turns #30 enam. over low potential end of L7.
- L9—18 turns #30 enam. closewound on ¼" form with powdered iron core (VHF Grade) ground tap 14½ turns from collector end.
- L10—3 turns #28 enam. wound over low potential end of L9.
- L13, L14, L15—1 7/16" long 3/8" dia. copper tubing tuning screws SC1, SC2, SC3 enter the hollow copper tubing to form tuning capacitors as noted below.

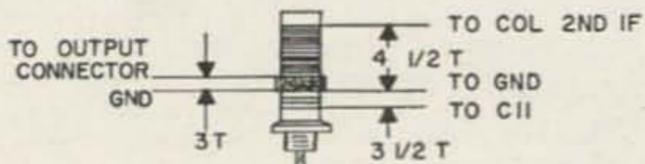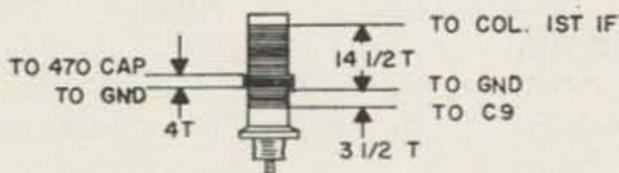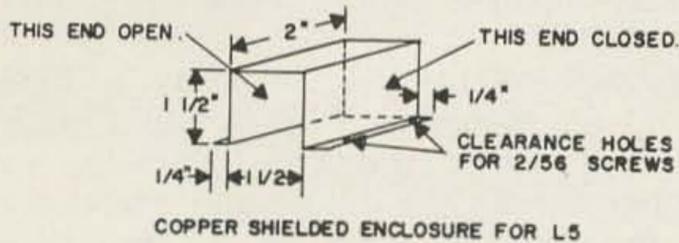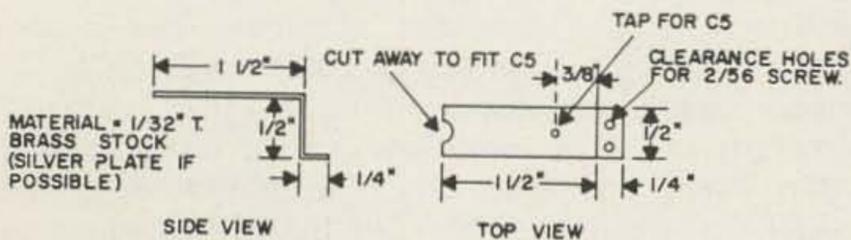

RFC 1 = 50 MC CHOKE
RFC 2 = 30 MC CHOKE

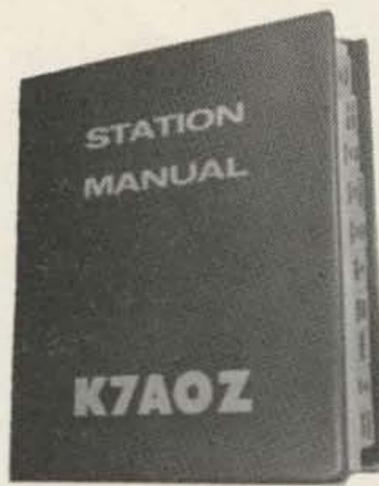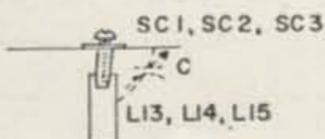


TNX . . . for your congratulations and fine compliments on the **STATION MANUAL** from the world over. TEN sections of operating aids and records . . . Station Log . . . Call-Name-QTH Index . . . Prefixes . . . DX Records . . . ETC. Top quality throughout . . . Beautiful vinyl cover . . . loose leaf versatility. At leading dealers or direct. Only \$5.95 postpaid. Add \$1.00 your station call on cover.

The perfect gift for the radio amateur

HAM AIDS, Box 8072, Spokane, Wash.

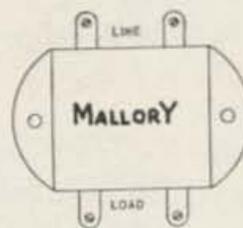NOISE FILTERS NEW MALLORY TYPE NF15-220 RADIO NOISE FILTER (FULL WAVE)



Removes A.C. line disturbances for a 5-9 QSO (wash. machines, fluorescents) used for T.V., ham receivers, Hi-Fi, moderate pwr xmtrs
15 amps @ 220 vac
30 amps @ 115 vac
easily installed

Value \$15.00


Limited supplies @ \$3.95 (p.p.)

R. Lumachi

73 Bay 26th St.
Brooklyn 14, N. Y.

THREE IMPORTANT REASONS WHY YOU NEED THE

NEW, FALL 1962 CALLBOOK

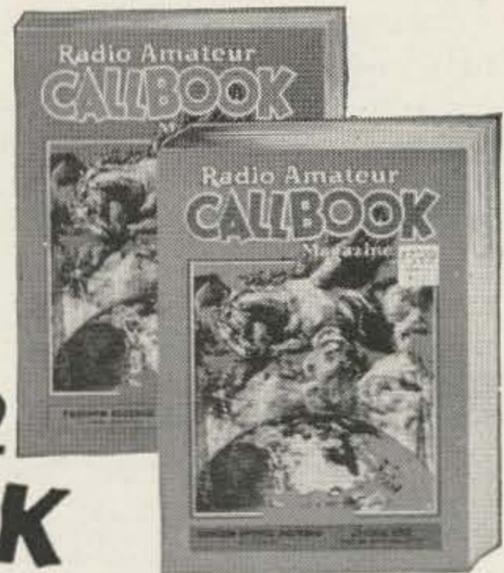

Foreign Listings (All outside U.S.)

\$3.00

U.S. Listings (All K and W calls)

\$5.00

- If your present CALLBOOK is only a year old, over 20% of the listings have been changed or added!

- Over 16,000 new amateurs added since the Summer, 1962 issue—biggest license increase in history!

- Completely revised essential data—latest international prefixes, Q signals, postal info., airline distances, time chart, etc.

Now on sale at your amateur equipment dealer; if not conveniently located you may order by mail (please add 25¢ for mailing) from:

RADIO AMATEUR CALLBOOK, INC.
Dept. B, 4844 Fullerton Ave., Chicago 39, Ill.

PS. Write for illustrated brochure on exclusive **WORLD ATLAS . . . DX GUIDE . . . SPECIAL FULL COLOR MAPS.**

Those Different Diodes

Staff

AT A HAM convention not too long ago, one of the speakers described the updating of a mobile receiver. Among the improvements added, he said, was a Zener diode to regulate oscillator filament voltage. At the conclusion of his talk, when he asked "Any questions?", half the hams in the room raised their hands with the same query:

"What's a Zener diode?"

The situation is a general one today; with many hams employed in the military electronics field where the phrase "state-of-the-art" is a watchword, and others in far different vocations, we're developing a technological split in our ranks. Many of today's construction articles call for strange and exotic devices which are totally unknown to those of us not working on the thresholds of the particular field involved.

In a small effort to remedy this situation, we've collected definitions, explanations, and some workable circuit information for three of the latest diode-type devices. Naturally, by the time you read this, a new crop of gadgets will have appeared — but this may at least take some of the mystery out of those *different* diodes.

Since Zener diodes touched off the whole idea, let's start with them. First, what are they? Second, what do they do?

The answer to the first question makes more sense if the second is answered beforehand: The Zener diode is the semiconductor version of the old familiar VR tube. It is used in the identical manner, current-limiting resistor and all, for the same purpose. However, it requires less room, doesn't break, and is available in a wide variety of voltages and power ratings.

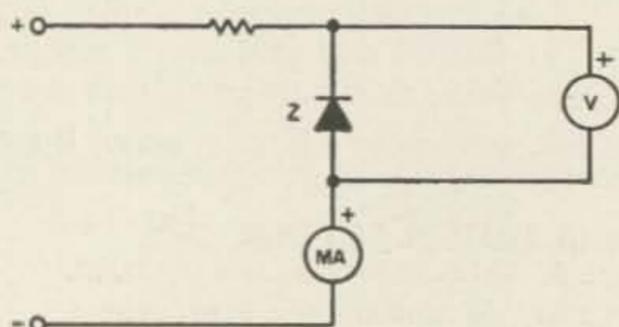


FIG. 1

Now, what is it? Basically, the Zener diode is just a conventional *silicon junction* power rectifier. All silicon junction rectifier diodes have a rated "peak inverse voltage" at which they break down and conduct in the reverse direction. If the diode is specially processed during manufacture, the voltage value at which it breaks down can be kept constant over a wide range of reverse current flow—and you have a Zener diode!

Since special processing is required, the cost of most Zener diodes is rather high. However, ordinary silicon junction rectifiers can sometimes be used as Zeners if you're willing to do some experimenting, and if the current through them is kept low (high current will burn them out instantly). For instance, the rectifiers produced by Diodes, Inc., show a particularly sharp "Zener break" just above their rated PIV.

To use a conventional diode as a Zener, hook it up as shown in Fig. 1. Start with a high value of series resistance. Note the voltage reading across the diode, and the current through it; multiply these two values to get the power going into the diode. So long as this power is less than $\frac{1}{2}$ watt (for the conventional 750 ma power rectifier) the diode is safe; you can reduce the resistance by small steps, recomputing the power after each change, until you reach about two-thirds of the $\frac{1}{2}$ -watt level (some margin must be left for regulating action). The diode will then regulate over a wide current range, at the value you read on the voltmeter.

Note that the diode is hooked up *in reverse*, with the cathode to positive and the anode to negative. This is necessary with all Zeners, since it's *reverse* current flow that provides the regulation. Hooked up in the forward direction, they're just like any other diode except that they cost more.

Average cost (as this is written) for the least expensive low-voltage Zener diodes is around \$4 each (although Hoffman produces a line of them for about 75 cents per diode); these units won't handle much more current drain than a conventional VR tube, but are available in a wide range of voltages from 3.9 volts up.

For higher current, you have a choice. You can use a bigger diode, at rapidly skyrocketing cost, or you can use the little Zener as a reference element in a transistorized regulator such as that shown in Fig. 2. Here, a small current flow through the Zener can regulate up to 3 amps through the transistor—and bigger transistors can be substituted for higher current still.

Of course, if you want to use the Zener without the transistor, you can use the circuit of Fig. 1 omitting the meters and putting the load where the voltmeter is shown.

These two basic circuits take care of nearly all voltage-regulation applications, but the Zener diode has more uses than that. Unlike the VR tube, the Zener requires no "firing-voltage" margin; it's more of a "built-in battery" as one text describes it. What's more, this battery never wears out.

Thus, you can eliminate the fixed-bias supply for a class B modulator by putting a

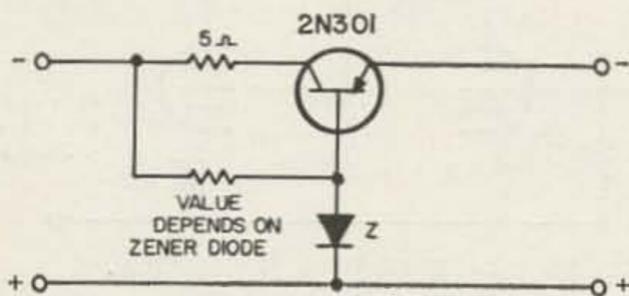


FIG 2

GENERALIZE YOURSELF! LEARN RADIO CODE

The EASY WAY

No Books To Read—No Visual Gimmicks To Distract You. Just listen and learn

Based on modern psychological techniques — This course will take you beyond 13 w.p.m. in

LESS THAN 1/2 THE TIME
Available also on magnetic tape
See Your Dealer Now!



PRICE \$9.95

Album Contains
Three 12" LP's
2 1/2 Hr.
Instruction

**EPSILON
RECORDS**

2769 CAROLINA
REDWOOD CITY, CALIF.

WATCH FOR the 180 watt P.E.P.

S-20B SSB Transceiver by Transceivers, Inc.

Xtal-lattice filter 3 kc bandwidth
"S" meter 16:1 tuning ratio
Excellent sensitivity 65 watts AM
and best of all . . . \$295.00

Write for complete specifications

TRANSCIVERS, INC.

158 Longbeach Road
Island Park, New York

IoAR

Though I have noticed a not unpredictable chill from down Connecticut way, the response to my announcement of the formation of the Institute of Amateur Radio was quite well received. The Institute has been launched and we have a lot of interesting plans afoot for it. Charter Membership, which will have some decided advantages later on, will be open only until the end of this year, but will be good for the entire year of 1963.

Charter memberships are piling in and Charter Membership cards are being sent out. Many members have good suggestions about further organization and possible activities of the IoAR . . . I think we are going to have some fun. One member suggested that we ask age on our application forms, but I have known too many 52 year old children and 18 year old adults to feel that this should be a factor.

. . . Wayne

Application for Charter Membership in the Institute of Amateur Radio (Valid only if postmarked before January 1, 1963)

Name Call: (must be licensed)


Address

City Zone State County

Class of license: Novice Technician General Advanced Extra Conditional

Year first licensed Old calls

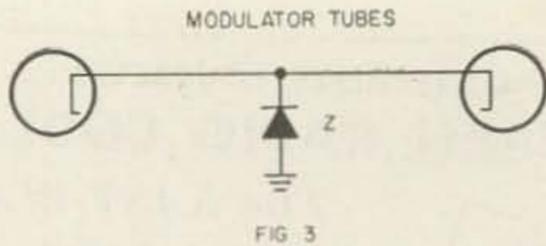Charter membership fee of \$1.00 must accompany this application. This will pay dues in full until December 31, 1963.



Zener diode (of the right value to provide proper bias) in the common cathode circuit as shown in Fig. 3. Where a conventional cathode resistor will give you a bias which varies with current drain through the tube, the Zener's voltage drop is constant so long as you don't fall below its minimum current or go above its upper current limit; most class B modulators fill both these requirements.

The same trick can be used to put fixed bias on any amplifier stage, either audio or rf. In addition, the Zener diode doesn't require any bypass capacitor, since its ac impedance is almost zero (and at any rate is far below that of most bypass capacitors).

The voltage-limiting property of this diode can also be used to build a most simple audio speech limiter for addition to any modulator, as shown in Fig. 4. Here, two Zeners must be used back-to-back; otherwise, half the audio cycle would be shorted out to ground. As in all clipper-limiter circuits, a low-pass audio filter would follow this to remove the harmonics generated by clipping.

One of the most sophisticated uses of the Zener diode is in the construction of direct-coupled amplifiers. If the Zener is put in series with a dc voltage, it will effectively subtract its own voltage drop from that voltage and pass on the rest.

Thus, if the resting plate voltage of an amplifier tube were 150, and if a 120-volt Zener were connected from the plate of that tube to the grid of the next stage (in place of the usual coupling capacitor) the voltage at the next grid would be 30.

This doesn't sound so good, but now we place a 33-volt Zener in the cathode circuit of the second tube to give a fixed 33-volt bias, and the net voltage from grid to cathode becomes -3 . This is more like conventional amplifier operation — except that the circuit will respond all the way down to dc.

While such circuits aren't too useful in most ham equipment, they're occasionally essential in special test equipment. A complete circuit giving a 100-volt output swing for 0.025 volts peak-to-peak input is shown in Fig. 5.

Another new diode you've undoubtedly heard

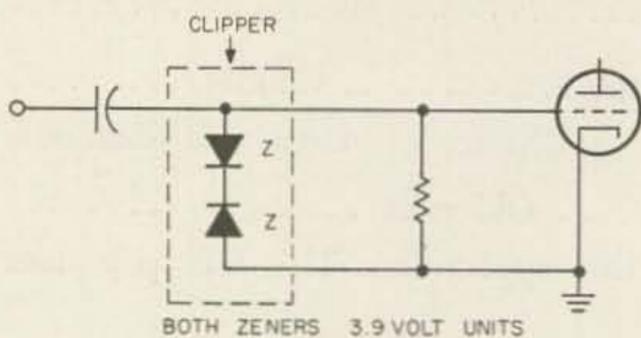


FIG. 4

something about is the Esaki, or "tunnel," diode.

These little varmints can drive you crazy if you let them. Let's try to stay sane while going through the same study of them that we did for the Zeners. First, what are they? Second, what do they do?

The tunnel diode is, again, a specially-treated semiconductor junction diode. The main characteristic keeping it in the spotlight at the moment is its negative resistance under certain conditions—heretofore, negative resistance has been a tricky thing to obtain.

What does it do? Well, if you could cancel out all the resistance in a tuned circuit you would have an ultra-stable oscillator. If you cancelled out most but not all the resistance, you would have a high-gain low-noise amplifier—which would also work in both directions. The possibilities are (theoretically at any rate) limited only by your imagination.

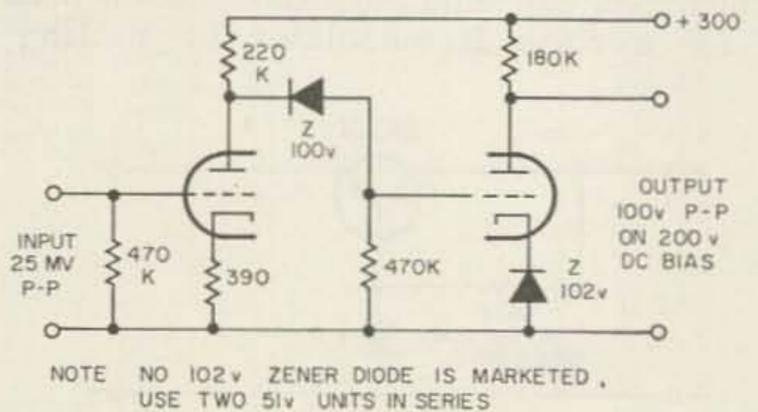


FIG. 5

The trouble with the tunnel diode is that it works too well. One of the biggest problems with them is that of keeping them from oscillating at any number of frequencies simultaneously. They can amplify af, oscillate at a dozen places in the rf spectrum, and mix all the various signals together—all at the same time, without batting an atom. What's more, if you give them the slightest opportunity, they'll do it!

Fig. 6 shows a typical *theoretical* tunnel-diode circuit you can find in any textbook new enough to talk about them. If the inductance and capacitance of the tank circuit are the only reactances present in the circuit, this gadget will act as either an amplifier or an oscillator at the resonant frequency of the tank circuit. The choice of amplification or oscillation depends on the impedance of the circuit; if the impedance is lower than the tunnel diode's negative resistance value, the circuit amplifies. Otherwise, it oscillates.

The trouble, of course, is that the inductance and capacitance aren't confined to just the tank circuit where you want them. The inter-

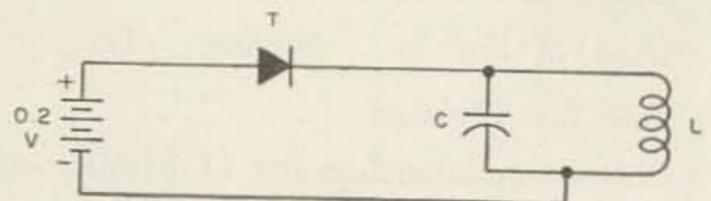


FIG. 6

EXCLUSIVE

SAVINGS ON NEW SEMICONDUCTORS !!

ZENER DIODES

3/4 watt 20% 4.3piv	\$1.15
3/4 watt 20% 6.2piv	1.15
3/4 watt 20% 8.5piv	1.15
3/4 watt 20% 15. piv	1.15
3/4 watt 20% 22. piv	1.15
1 watt 20% 4.3v	1.35
1 watt 20% 6.2v	1.35
1 watt 20% 8.5v	1.35
1 watt 20% 15. v	1.35
1 watt 20% 22. v	1.35
Double anode 6.3v ±20%	.50

TRANSISTORS

Similar CK721, CK722, CK786 2 for 60¢	
PNP repl'm't 4-trans radio	2.10
PNP repl'm't 5-trans radio	2.45
PNP repl'm't 6-trans radio	2.75

DIODES

German'm replaces 1N34A	10 for \$0.98
Similar 1N137, 1N137A, 1N138, etc.	1.20
Gen. purp, glass silicon	.98
R-f gen. purp replaces 1N82A	.98

RECTIFIERS

100ma 1000piv hi-V silicon	\$1.70
100ma 1500piv hi-V silicon	2.25
100ma 2000piv hi-V silicon	2.95
100ma 3000piv hi-V silicon	4.45
500ma 200piv epoxy, sim. 1N2069	.30
500ma 400piv epoxy, sim. 1N2070	.40
500ma 600piv epoxy, sim. 1N2071	.70
750ma 50piv replaces 1N599	.11
750ma 100piv replaces 1N600	.20
750ma 200piv replaces 1N602	.33
750ma 300piv replaces 1N603	.39
750ma 400piv replaces 1N604	.48
750ma 500piv replaces 1N605	.60
750ma 600piv replaces 1N606	.75
750ma 700piv	.95
750ma 800piv	1.25
750ma 900piv	1.50
750ma 1000piv	1.95
750ma 1500piv	3.25
750ma 2000piv	4.15
2amp 50piv replaces 1N2026	.17
2amp 100piv replaces 1N347	.30
2amp 200piv replaces 1N2027	.45
2amp 400piv replaces 1N2029	.90
2amp 600piv replaces 1N2031	1.35
2amp 800piv replaces 1N1236	1.75
2amp 1000piv replaces 1N3366	2.90
2amp 1500piv replaces 1N3371	4.70
2amp 2000piv	6.50
2amp Cont. Rect. similar 2N1600	3.50

RECTIFIERS

2amp 50piv axial lead	\$0.15
2amp 100piv axial lead	.27
2amp 200piv axial lead	.40
2amp 400piv axial lead	.85
2amp 600piv axial lead	1.20
2amp 800piv axial lead	1.60
2amp 1000piv axial lead	2.80
2amp 1500piv axial lead	4.30
2amp 2000piv axial lead	6.00
12amp 50piv replaces 1N1199	.75
12amp 100piv replaces 1N1200	1.20
12amp 200piv replaces 1N1202	1.75
12amp 400piv replaces 1N1204	2.60
12amp 600piv replaces 1N1206	3.75
12amp 800piv	6.90
12amp 1000piv	9.50
20amp to 400 piv. Cont. Rect.	14.00
25amp 50piv replaces 1N248A	1.50
25amp 100piv replaces 1N249A	2.50
25amp 200piv replaces 1N250A	3.70
25amp 400piv replaces 1N2136A	4.75
25amp 600piv replaces 1N2138A	7.75
25amp 800piv	10.00
50amp 25piv	2.70
50amp 50piv similar 1N411B	3.98
50amp 100piv similar 1N412B	5.98
50amp 200piv similar 1N413B	6.50
50amp 400piv	9.75
50amp 600piv	16.00

NOTE: All semiconductors listed above are NEW-CLEAN! Fully guaranteed. Subject to your approval. AMERICAN MADE and individually tested to meet above ratings.

SEND FOR FREE CATALOG

Order Direct
Shipped Prepaid

ALCO ELECTRONICS

21 SO. BROADWAY
LAWRENCE, MASS.

connecting wires have both self-inductance and capacitance both to ground and to each other. The diode itself has some inductance and capacitance. So does the power supply. And every possible resonant circuit with an impedance greater than the diode's negative resistance produces oscillations!

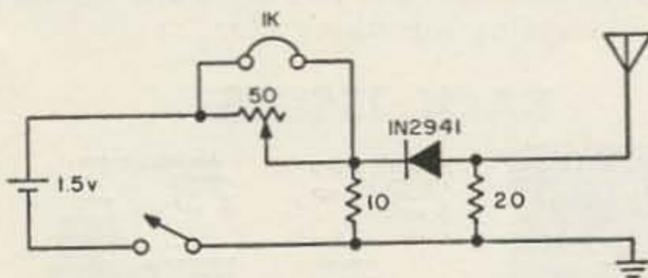


FIG. 7

One way of getting around this problem, by brute force, is that shown in Fig. 7. This circuit may be familiar; it's from "Lost In a Tunnel" in our January, 1961, issue. Here, the 10-ohm resistor in the power supply swamps out any possible oscillations there, while the 20-ohm resistor swamps out the undesired oscillations in the rest of the circuit. Somewhere around 50 mc, the inductance of the 20-ohm carbon resistor and its own capacitance to ground form a resonant circuit with impedance great enough to force oscillations, and the result is a 50-mc-or-so sine wave with nearly 1-volt peak-to-peak amplitude. The headphone is used as a mike to modulate the rf.

HEY!

WE WANT YOUR OLD RECEIVER

WE WILL ALLOW IN TRADE FOR GOOD USED RECEIVERS AS FOLLOWS

Halli. S38E	\$75.00	Hamm HQ129X	..	\$150.00
Halli. S108	150.00	Hamm HQ140X	..	175.00
Halli. SX110	...	170.00	Hamm HQ100..	..	160.00
Halli. S85	125.00	Hamm HQ110..	..	225.00
Halli. S99	150.00	Hamm HQ160..	..	250.00
National SW54.		65.00	National NC88.		110.00
National NC60.		80.00	National NC98.		135.00
National NC125		150.00	National NC188		120.00
National NC173		135.00	National NC109		145.00
Natl. NC 183D.		200.00	Natl. NC240D..		125.00

If Your Receiver is Not Listed, Please Ask for Special quote.

TOWARDS THE PURCHASE OF THE
NEW HALLICRAFTERS

SX101A at \$445.00 AMATEUR NET.

GRAHAM RADIO INC.

AMATEUR DEPT. 5

505 MAIN STREET • READING, MASS
Tel. 944-4000 (Area Code 617)

BOUND VOLUME \$15

If you've missed the early issues of 73 this is a fine way to rectify that oversight. This book will keep you up to all hours of the night for weeks trying to catch up with the hundreds of articles we have published and the ridiculous editorials. This volume contains the first 15 issues of 73, from #1 in October 1960 to December 1961. Bright RED, stamped in gold.

YEARLY BINDERS \$3.00

These are also BRIGHT RED and stamped in Gold! Specify what year you are collecting: 1960-1, 1962, or 1963. Preserve those copies for prosperity.

MRT-90 CONVERSION: 50c

This booklet gives complete conversion instructions for converting the little pack-set surplus units into a fine two meter walkie-talkie. An article appeared in 73 on this unit in the October 1961 issue.

HAM-TV \$3.00



TV is one of the newest and most exciting phases of ham activity. This book gives clear and simple instructions for getting an operating TV station on the air for under \$50 outlay! It is no wonder that hundreds of fellows are rushing to get on the air. The interest has been so high that a bi-monthly bulletin has now been started to keep everyone up to date on the advances and latest stations to get into operation.

IMPEDANCE BRIDGE \$1.00

Here is a complete set of full scale drawings of the parts for the Impedance Bridge which was featured in the August 1961 issue of 73. This bridge is one of the most useful pieces of test equipment that you could possibly build. It would cost you hundreds of dollars to buy this unit commercially made. This set of plans comes complete with a reprint of the original article.

SSB TRANSCEIVER SCHEMATIC \$1.00

There have been many requests for a giant sized schematic of the wonderful little transceiver that appeared in the November 1961 issue of 73. This schematic comes complete with a spare issue of the magazine in case you missed it.

73 Magazine Peterborough, New Hampshire

INDEX TO SURPLUS

INDEX TO SURPLUS \$1.50

This is a masterful compilation of all articles that have ever been printed on surplus conversions, complete with a brief run-down of the content of each article



TV BULLETIN \$1.00 per year

The first issue of the TV Bulletin is now ready for mailing. This is a bi-monthly bulletin designed to keep all fellows interested in Ham-TV up to date on technical improvements in Ham-TV gear and on all activities. In the first issue of the Bulletin there is a list of all known hams who are reported to be getting on the air on TV. The Bulletin is edited by Mel Shadbolt, WØKYQ, the author of the popular HAM-TV book. Get in on this from the first issue and have a complete set of information at your fingertips. The present plans call for six issues of the Bulletin per year, with at least 12 pages per issue.


MICKY MIKER 50c

This is the first of our small booklets to come off the press. It is a complete description of the construction and operation of a little device which will measure capacity to a high degree of accuracy. This is a gadget that can be built out of most junk boxes and will forever be a handy item to have around when you are building something new or fixing something old.

BACK ISSUES

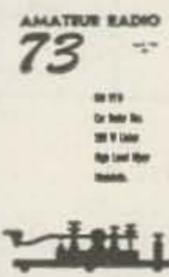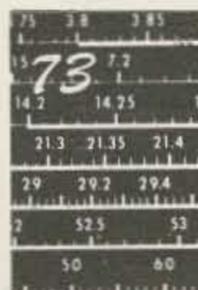

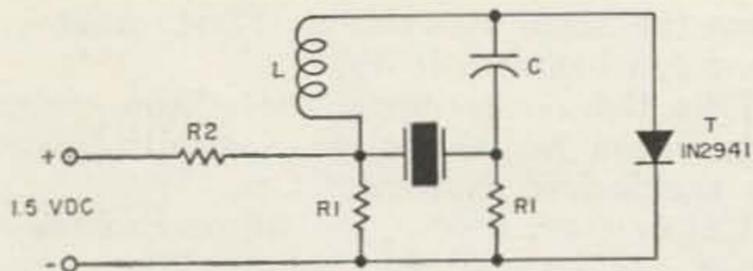We have a diminishing stock of all back issues except January 1961. We are willing to part with this stock for only 50¢ each. How about that!



L AND C RESONANT AT CRYSTAL FREQ

$$R_1 = \frac{0.06 \times L}{C} \text{ FOR IN2941}$$

$$R_2 = 5 \frac{1}{2} \times R_1$$


FIG. 8

This circuit is an interesting laboratory curiosity, but isn't too useful. More quickly adaptable to our uses is the crystal oscillator of Fig. 8, developed by GE engineers. In this one, resistors damp out all oscillations except at the crystal frequency. At this frequency, the crystal bypasses some of the resistance and allows oscillation.

Recently, the Heathkit people came out with a "tunnel dipper," similar to the familiar grid-dip meter. One circuit for such an instrument is shown in Fig. 9. Since we haven't tested it, we can't guarantee results—but the fact that Heath sells such a product means that it can be made to work.

When working with tunnel diodes, you'll have to get used to dealing with minute voltages and currents. All the interesting action takes place with voltages of about 50 to 300 thousandths of a volt across the diode! Many meters won't read accurately in this region; the bias-supply circuit of Fig. 10 is recommended to make sure that your supply voltage is at least in the right township.

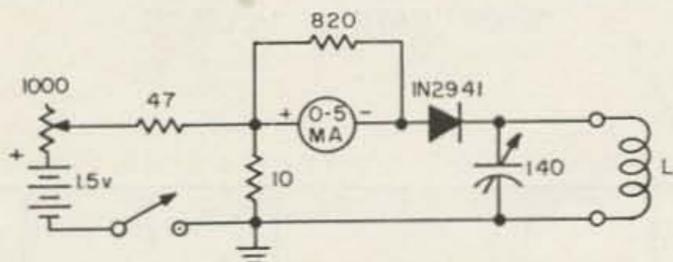So far, we've looked at diodes which amplify,



L PLUG-IN COIL TO RESONATE WITH TUNING CAPACITOR AT DESIRED FREQUENCY

FIG. 9

5-18mc 40 turns #20, 1/2" dia, 1 1/4" long
(B & W 3004 or Air Dux 432T)

12-45mc 16 turns #20, 1/2" dia, 1" long
(B & W 3003 or Air Dux 416T)

43-160mc 3 turns on #20, 1/2" dia, 3/16" long
(B & W 3003 or Air Dux 416T)

Start with 1K pot at max. resistance, decrease its setting slowly. Meter reading will increase, then decrease. Set for approx 3 ma reading in decreasing portion. Pot need be adjusted only when battery ages or is replaced.



DIODE IS ANY SILICON-JUNCTION UNIT
VALUE OF R IN OHMS = 20 X INPUT VOLTAGE

FIG. 10

JEFF - TRONICS

Now, in our new, bigger store, we can offer more of the best in new equipment, as well as a continually changing stock of military surplus bargains.

The DRAKE 2-B Receiver for AM-SSB-CW \$279.95

Speaker \$16.95 Xtal calibrator \$16.95
Q-Mult-Speaker \$39.95

The New-Tronics "HUSTLER" deluxe
all-band Mobile antenna system, in stock.

The National NC-155 receiver, \$199.95

Ameco converters, kits, accessories.
Hy-gain antennas, all types, in stock.

On new equipment orders over \$10.00
we ship prepaid in U. S.

Surplus Department:

Zener diode regulators, Texas Inst. IN756A
8.2 volts, 400 mw. \$1.00 each. 4 for \$3.00.
2N1681 Tung-Sol switching transistors 60¢ each.

Please add postage on surplus items.

Our new catalog is in preparation.
Send for your copy.

4791 Memphis Ave. Dept. C3
Cleveland 9, Ohio

TEST GEAR

Surplus—New—Used—OK

BC-221 Freq. Meter 125 kc-20,000 kc, w/case, ok,
\$75.00

TS-175 80mc-1000mc New, \$225.00

TS-186-B/U-100-10,000mc CW, MCW, pulse, \$225.00

Oscilloscope-OS 8/U 115v, 60cps, dc to 2.5mc, \$85.00

TS-497 (measurement model 80) rf sig gen,
2-400mc, 6 bands, .1-100,000 uv, \$350.00

Oscilloscope-Dumont-248 115v 60cps operate, 20cps-
5mc and driven sweeps 1/10/100 micro-sec.
markers, \$195.00

Oscilloscope-Dumont-256E 115v 60cps operate, 8mc
response, \$195.00

Hewlett Packard-803A VHF Impedance and SWR
Bridge, 50-500mc, 2-2000 ohms imped., \$450.00

Berkley Decimal Scaler model 2000, \$150.00

Spectrum Analyzer TS148/UP w/accessories, less
transit case, \$450.00

In Stock—Tekronix 511-513—Quotes on Request

Rex Radio Supply Co.

88 Cortlandt St., New York, N. Y., CO 7-1617

GONSET COMMUNICATION SPEAKERS

BRAND NEW, High Quality 5" x 7"

Speaker in attractive grey cabinet.

Regularly \$19.95 SPECIAL \$7.95

SIGNAL ELECTRONIC SUPPLY

13618 S. WESTERN, GARDENA, CALIF.

FA 1-4867 (213) FA 1-2318

SAVE AT SIGNAL!

All orders FOB Gardena, Calif. Minimum 25%
with order. Minimum order \$3. Calif. Res. add
4% state tax.

diodes which oscillate, and diodes which behave like batteries. How about the diode which acts like a variable capacitor?

These are known by many trade names. Pacific Semiconductors Inc. calls their version "Varicaps," International Rectifier calls them "Semicaps," and Amperex uses a string of words: "Silicon Variable Capacitance Diode." Hughes shortens this to "Silicon Capacitor," but they're all talking about the same kind of a diode.

In many ways, the "silicon capacitor" is like a Zener diode; it is effective only when reverse-biased, and it requires special processing. However, unlike the Zener, the silicon capacitor is never used in the breakdown region, so it never carries any current. Let's approach it

from the same viewpoints: First, what is it? Second, what does it do?

Like the Zener diode, the silicon capacitor is a silicon *junction* diode, specially processed for the desired characteristics.

Unlike other diodes, the silicon capacitor behaves like a variable capacitor. When reverse-biased, it has a certain capacitance. Just how much capacitance depends on the voltage across the diode.

As you probably know, a reverse-biased diode looks like an open circuit; now, the definition of a capacitor is also that of an open circuit: two conductors separated by an insulator. The amount of capacitance depends on how far the conductors are separated.

In the silicon capacitor, the insulator is

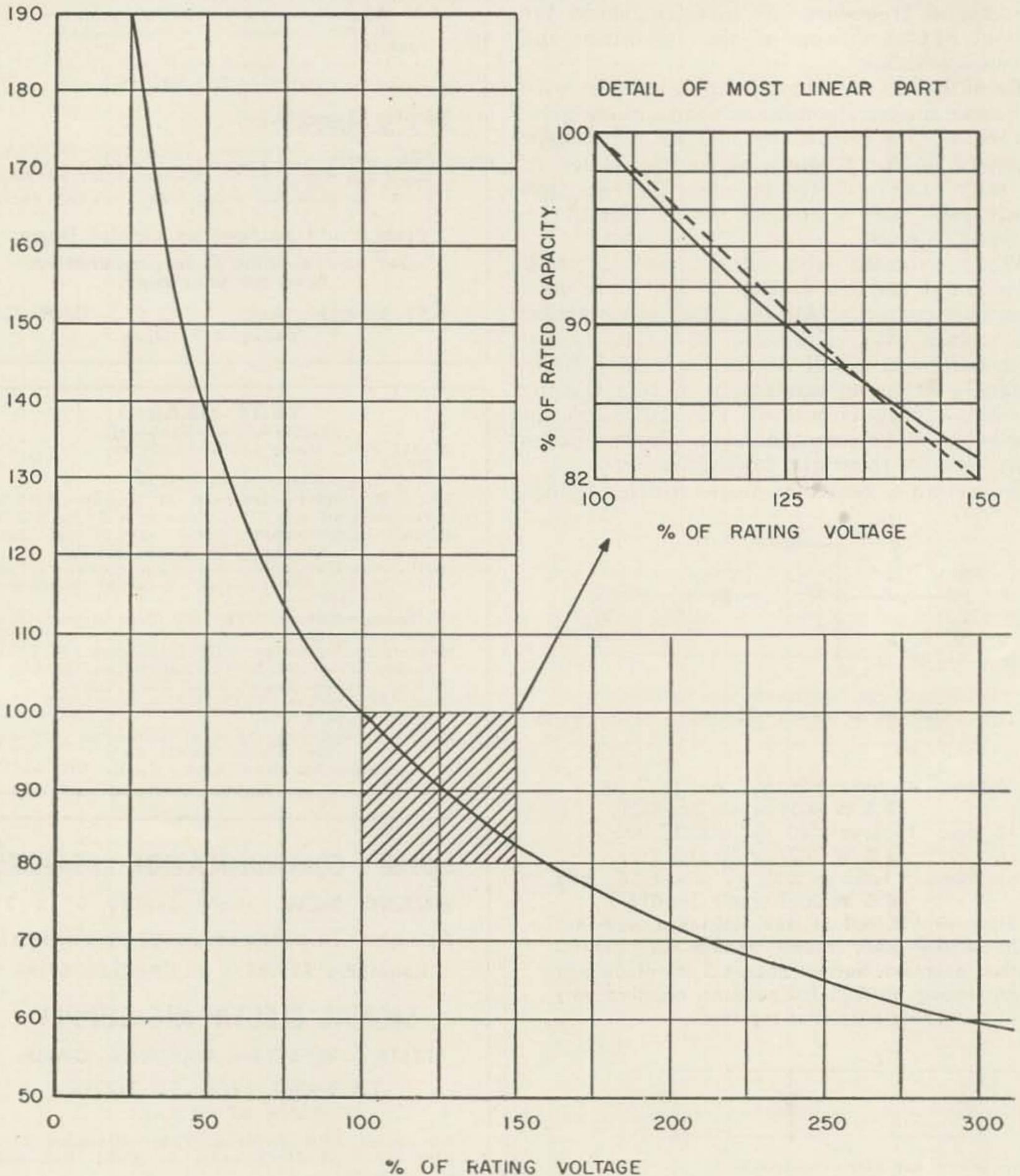


FIG II

MESHNA'S EYE POPPERS

TELETYPE PERFORATING PAPER carton of 40 rolls, 11/16 wide. If you are on RTTY or going on RTTY you will want to stock up on tape at this extraordinary price. Buy two cartons at least. carton—47 lbs \$5.00

BC-191 POWER SUPPLY 80 lbs 30.00

PHONE PATCH KIT includes genuine commercial phone co. coil, cond. switch. Make yourself a professional patch. 8 lb 4.00

28 VOLT DC SUPPLY 4 amp out from regular house current. Brand new packaged. Cost Uncle Sam \$500. Stick a one amp Variac in it and you have a variable 0-28 volt DC supply for running all that 6-12-24-28 volt surplus gear or charging car batteries. Invaluable for servicing auto radios. 22 lb 12.50

ABK TV MONITOR. Just uncovered in our warehouse (lost for 2 years) a few boxes factory packaged 7" TV monitor. Includes cables, and viewing hood. 28 volt input. 60 lb 29.00

PANADAPTOR, NAVY "RBU" 400 kc "IF." Brand new with book. Made by PANORAMIC. Easily modified for "455 IF" using a broadcast set for a converter. 50 lb 75.00

CRYSTAL MIKE, Turner, hand type brand new with cord and plug. 3.00

CRYSTAL FILTER brand new, made for the Super Pro. Conversion sheet included for making a variable selectivity control for your receiver. 4.50

ARC-3 RECEIVER, all tubes & conversion sheet. As written up in the December '61 issue of

73 this converts to a fine 100-156 mc continuous tuning receiver with plenty of bands spread on two meters. 12 lb 15.00

ARC-5 TRANSMITTER, BC-458. This model converts to many uses and bands. Ours are govt. rebuilt like new. w/conversion sheets. 16 lb 8.50

ARC-5 MD/7 MODULATOR, brand new. 8 lb 8.50
Buy an ARC-5 as above with modulator and get a "Deal" both for 15.00

ARR-2 Receiver with conversion sheets for "CB" or 2 meter converter. 5.50

RA-62 POWER SUPPLY for SCR-522 operation from 115 volt 60 cycle. 50 lb 35.00

THOMPSON CO-AX SWITCH 2 position, operates from 115 volt 60 cycle. Brand new, list price of \$50.00. 12.50

RG-8A coax (52 ohm) 30 ft roll with connectors. 2.25

RG-9B coax (52 ohm) 25 ft roll with connectors. 2.75

CRYSTALS—FT 243 holder, 50¢ each 7150-8350-8366.7-8375-8400-8425-8440-8441.7-8483.3.

DISC CERAMICS, bag assorted, contains over 100 pieces, marked 1.00

ALL MATERIAL FOB LYNN, MASS. Send for 60 page catalog of surplus material. Our prices will amaze you. All types of radio material, transformers, diodes, power supplies, aircraft camera lens, etc. Come visit us, open every day 9-5, Saturday included.

MESHNA, 19 ALLERTON ST., LYNN, MASS.

furnished by what physicists call "the depletion layer" at the junction. The thickness of this "depletion layer" depends on many things; among these factors are the way in which the diode was processed during manufacture, and the voltage across the junction.

Note those last five words: the voltage across the junction controls the thickness of the insulating layer, or in other words, the distance between conductors—and thus, the capacitance. It works something like the familiar mica compression trimmer, except that voltage controls the capacitance.

If the preceding three paragraphs suggest to you that any silicon junction diode can be used as a silicon capacitor, you're right. However, the specially-processed units often have a greater range of capacitance, and in addition, can be obtained in known values.

The actual amount of change in capacitance with change in voltage follows a rather complicated set of equations; the graph in Fig. 11 shows this change in "normalized" values. If you know the capacity of the diode at any one voltage, you can find the percent change in capacity with percent change in voltage from the graph. Thus, a diode with 22 mmfd capacitance at 7 volts bias will have 14.3 mmfd at 250 percent of 7 or 17.5 volts, and will show 33 mmfd at 2.8 volts (40 percent of 7). This chart is accurate for all diodes, even though various manufacturers rate their units at different bias voltages.

The circuit for using a silicon capacitor is shown in Fig. 12; the silicon capacitor is the symbol which looks something like a diode and something like a trimmer. You can see that the only difference between this and a conventional tank circuit is the dc-blocking capacitor in series with the silicon capacitor. If this blocking capacitor is very large in comparison to the silicon capacitor (10 times or larger), it will have no noticeable effect on the capacitance in the circuit.

Going back to Fig. 11 for a moment, you can see that the change in capacitance is almost exactly proportional to changes in voltage over any very small range. The most linear part of the curve has been expanded for the region from rated voltage to 150 percent of rated voltage; over this spread, the departure from true linearity is no greater than 0.5 percent, which immediately suggests the use of these capacitors for tuning oscillators and receivers.

As a matter of fact, the new Hallicrafters FPM-200 is tuned in just this way, and several articles on use of the silicon capacitor for automatic frequency control have been published as well.

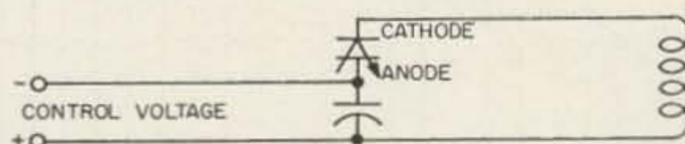


FIG. 12

A bit of thought will remind us, though, that the frequency of an oscillator is *not* directly proportional to the capacitance in the tuned circuits; for very small changes, it is, but for large changes, the calibration is far from linear.


Fortunately, if a silicon capacitor is used in an oscillator tuning circuit, some of the non-linearities cancel each other out. Fig. 13 is a graph of frequency versus voltage for the circuit of Fig. 14; the dotted line is a true linear calibration while the solid line is the actual calibration curve. You can see that the departure from linearity is a very small part of the actual tuning frequency.

Like Fig. 11, Fig. 13 is "normalized" to starting conditions. Thus, if the circuit tunes to one frequency at a given voltage (say, 7 mc at 5 volts) it will tune to 105 percent of that frequency (in the example, 7.35 mc) at 123.5 percent of that voltage (or 6.7 volts).

The linear region of the curve isn't quite long enough to cover the entire 80-meter band at one setting, but is more than adequate to cover all our other bands; you can set your frequency with a voltmeter.

The advantage of such a hookup is primarily that you can now put the rf-carrying leads right where you want them; the tuning is done with dc, which can (and should) be decoupled with high-value resistors, allowing you to put the tuning controls wherever you like.

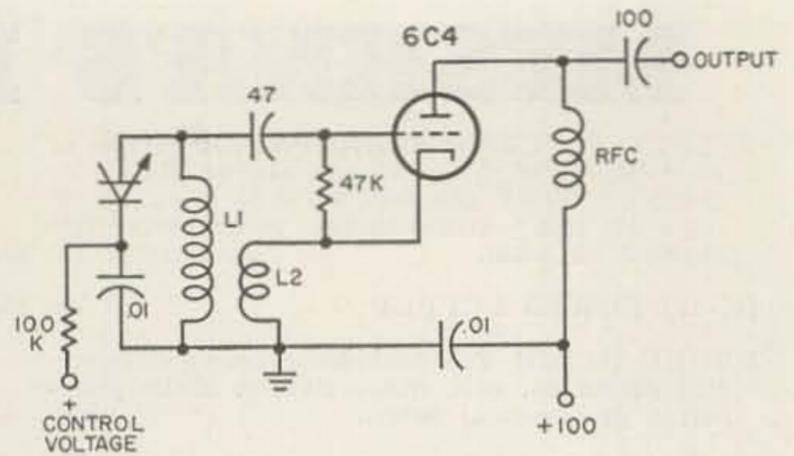A word of caution: all these characteristics hold *only* when the diode is reverse-biased. If the rf voltage swing across the capacitor is



- L1 - VALUE DEPENDS ON FREQUENCY DESIRED; SLUG-TUNED COIL IS SUGGESTED.
 L2 - 1/4 AS MANY TURNS AS L1, WOUND OVER COLD END OF L1 IN SAME DIRECTION; ADJUST NUMBER OF TURNS AS NECESSARY FOR STABLE OPERATION

FIG. 14

greater than the dc bias, anything can happen. This can be prevented by tapping the diode down on the coil, or by using circuits which do not put a high rf voltage across the diode-capacitor.

In addition, voltage must be closely controlled. In our example above, it took only 1.7 volts change to swing the frequency clear across the 40-meter band; a 0.17-volt change would move you 35 kc, and just 17 millivolts would swing the frequency 3½ kilocycles—outside the bandpass of many receivers. This effect can be put to use to get FM the simple way (see the references) but is quite a headache when it happens unexpectedly.

In a single issue of this magazine, there's not room to do more than scratch the surface

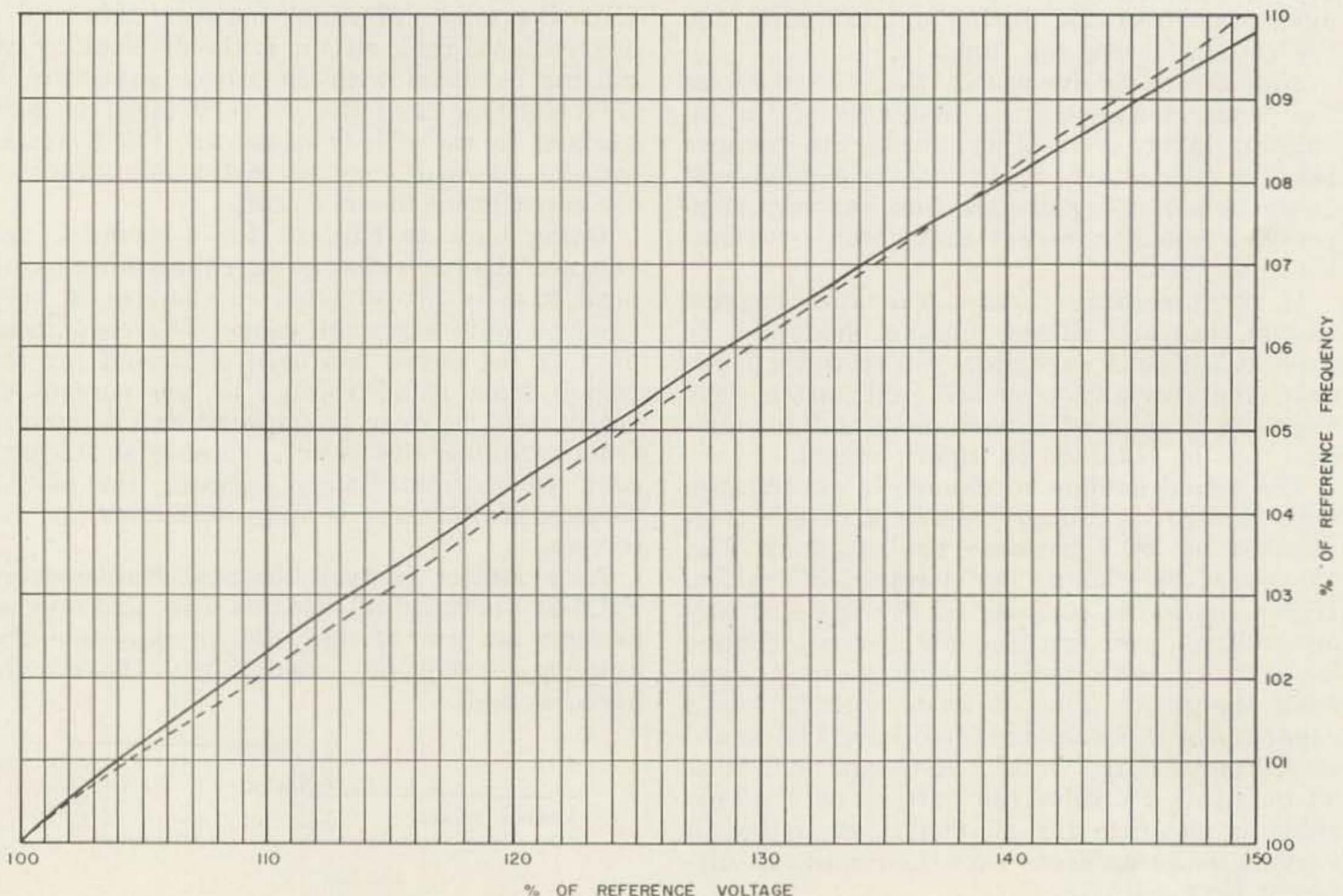


FIG. 13

of the strange world of semiconductors. A number of other exotic semiconductor devices have been announced in the past few months: the thyristor, the binistor, the unijunction transistor, the four-layer diode, the silicon-controlled-rectifier, to name but a few. The only way to keep up with them all is to read the dozen or more high-level engineering publications, including three devoted to semiconductors exclusively—but at least, this may have taken some of the mystery from these three *different* diodes.

REFERENCES

Zener Diodes

Anonymous, *Zener Diode Handbook*, International Rectifier Corporation, El Segundo, Calif., 1960.

Anonymous, *Silicon Zener Diode Handbook*, Semiconductor Products Division of Motorola, Inc., 2nd edition, 1961.

Charles Caringella, W6NJV, *Multi-Purpose Low Voltage Supply*, *Electronics World*, August, 1961, page 44.

Harold Reed, *Zener Diode Testing*, *Electronics World*, December, 1960, page 57.

R. J. Shaughnessy, *The Zener Diode*, *Popular Electronics*, June, 1961, page 76.

Dave Stone, *Voltage Regulator Diode-Tube Combinations*, *Electronics World*, April, 1961, page 104.

Don Stoner, W6TNS, *Zener Diode Regulator*, *Electronic Equipment Engineering*, April, 1960, page 41.

Tunnel Diodes

Anonymous, *Developments in Tunnel Diode Circuits*, *Electronic Equipment Engineering*, April, 1960, page 28.

Anonymous, *Transistor Manual Including Tunnel Diodes*, 5th edition, Semiconductor Products Department, General Electric Company, Liverpool, New York, 1961.

Lester A. Earnshaw, ZL1AAX, *Home-Made Tunnel-Diode CW Transmitter*, *Radio-Electronics*, March, 1961, page 34.

Jim Kyle, K5JKX, *Lost in a Tunnel*, 73, January, 1961, page 20.

Don Stoner, W6TNS, *Tunnel Diodes Simplified*, *Electronics World*, March, 1961, page 44.

Rufus P. Turner, *Build This Tunnel-Diode Dip Meter*, *Radio-Electronics*, April, 1961, page 42.

Rufus P. Turner, *Care and Handling of Tunnel Diodes*, *Radio-Electronics*, May, 1961, page 88.

Silicon Capacitors

R. E. Baird, W7CSD, *Something New in FM*, 73, October, 1960, page 10.

John Ellison, W6AOI, *Panadapting Adaptor*, Part 1, 73, June, 1961, page 33.

Don Stoner, W6TNS, *Do It With Diodes*, *Radio-Electronics*, February, 1961, page 38.



"... then it's all arranged. You'll win all the DX contests for the next seven years, at which time I'll . . ."

FREE Catalog

OF THE WORLD'S FINEST ELECTRONIC GOV'T SURPLUS BARGAINS



HUNDREDS OF TOP QUALITY ITEMS—Receivers, Transmitters, Microphones, Inverters, Power Supplies, Meters, Phones, Antennas, Indicators, Filters, Transformers, Amplifiers, Headsets, Converters, Control Boxes, Dynamotors, Test Equipment, Motors, Blowers, Cable, Keyers, Chokes, Handsets, Switches, etc., etc. Send for Free Catalog—Dept. 73.

FAIR RADIO SALES
2133 ELIDA RD. • Box 1105 • LIMA, OHIO

KEEP CANDEE HANDEE!!

WRITE FOR OUR FALL FLYER!

★ ★ ★ WE'LL HORSE TRADE and give you Top \$\$ Dollar \$\$ for your PRC, GRC, VRC & Test Equipment!

J. J. CANDEE CO.

509 No. Victory Blvd., Burbank, Calif.
DDD area 213 — VI 9-2411

TRANSFORMER, 115V 60 cyc, 2 secondaries each 350 V @ 4 amps.....\$22.50
TRANSFORMER, 115V 60 cyc, sec. 1460VCT 290 MA, plus bias winding 736 V 33 MA\$10.00
CHOKE, 5.5 Hy. 900 MA, 26 ohms, 1.5 KVA test.\$8.95
SWINGING CHOKE, 2.3/5.5 Hy. 850/100 MA, 6 KVA test\$12.50
DYNAMOTOR, Model D-401 EICOR, input 12V @ 9.9 amps, output 440 VDC @ 200 MA. Brand New! Only\$2.25
CHOKE, 1.72 Hy. 400 MA, 10 KV.....\$3.75
850 WATT MODULATION TRANSFORMER, Chicago Xfmr Co., FS-type frame. Pri. 10,000, Sec. 3750 and 7550 ohms\$32.00
CHOKE, 2 Hy. 1.15 Amp. 5 KV test.....\$12.50
CHOKE, 6 Hy. .5 Amp. 3.5 KV.....\$4.50
CHICAGO FILAMENT XFMR, 115V 60 cyc, sec. 5V @ 15A, 5KV AC hipot\$7.50
MULTI-TAP FILAMENT xfmr, pri. 210-240V 60 cyc in 5V steps, sec. 5/7.5/10/11V @ 35A, common CT\$19.95
FILAMENT XFMR, 115V or 220V 50/60 cyc, sec. 5V @ 20A CT, 35kv ins.....\$12.00
FILAMENT XFMR, 117V 50/60 cyc, two 10V 13A @ 12.5KV, one 10V 13A @ 7.9KV, one 6.3V 1A..\$11.00
CAPACITOR 8MF 2KV, Cornell-Dubilier, with brackets\$3.15
CAPACITOR 4MF 3KV, Goodman, with brackets.\$3.75

VERN'S 7701 S. Normandie
Los Angeles 44, Calif.
All Orders FOB L. A. — Phone (213) PL 1-0278

U. S. #1 ELECTRONICS

1920 EAST EDGAR ROAD, LINDEN, NEW JERSEY
Open Saturdays only until further notice. WA 5-3040

SURPLUS BARGAINS

TELEVISION CAMERA—Fine for ham or closed circuit use. Vertical resolution 350 lines at 40 frames/sec. Complete with all tubes, lens, and conversion sheet. L/NEW \$99.50

TELEVISION TRANSMITTER—A really beautiful 264-372MC unit using a push-pull 8025 final modulated by a pair of 8025's for 25 watts output. Easily converted to 420MC. NEW \$35.00

TELEVISION MONITOR—for use with above units. \$29.50
1215MC TRANSCEIVER—APX-6 Hard to get popular unit for easy conversion to 1215MC. See Sept. '60 QST. Complete, but less 3E29. L/NEW \$22.50

6 METER TRANSMITTER—A really beautiful unit with an 815 final AM modulated by an 815 for 50 watts input. Metered. L/NEW \$24.50

2 METER TRANSCEIVER—SCR-522 Most common surplus piece on 2!! AM modulated 832 runs at 30 watts. Complete with tubes. L/NEW \$18.50

WRITE FOR CATALOG

All prices FOB Linden, N. J. Some quantities limited. Prices subject to change without notice. Min. order \$4.00.

DPDT Relay 115vac/60cy coil, ceramic insulation, Leach #1177BF 10 amp contacts, NEW **\$3.95 delivered**

Transformer for 24vdc supply, 117/60/1 primary, tapped secondary 31, 32, 35 & 36.7vac at 6 amps, NEW, thermador **\$8.50 delivered**

Rectifier for above, NEW **\$5.50 delivered**

Capacitors 4,000mfd, 50vdc **\$2.25 delivered**

Modulation Transformer, 20 watts, 1-1, pri. and sec. Z-6,000, potted Chi. Trans. Shipping weight 5 lbs. Send postage, we'll send trans. **FREE**

SATISFACTION GUARANTEED

HIWAY COMPANY

1147 Venice Blvd., Los Angeles 15, Calif.

ARC-3 and ART-13A TECH MANUALS!

Handbooks mainten., oper., theory, schem. dwgs, etc. Either book postpaid **\$10.00**


RADIO RECEIVER AND/OR SPECTRUM ANALYZER
AN/APR-4 revr is the 11-tube 30 mc IF etc. for its plug-in tuning units; has S-meter, 60 cy pwr sply. Pan. Video & Audio outputs. AM. Checked, aligned. with heads for 38-1000 mc, pwr plug & Handbook, fob Los Ang. **\$164.00**

Add \$59.50 for 1-2.2 kmc; add \$79.50 for Test Oscillator TS-47/APR, 40-3000 mc $\pm 1\%$, CW, AM, PM, w/built-in 60 cy pwr sply, fob Los Ang. Add \$45.00 to get AM/FM revr instead of AM.

2-METER RECEIVER & 2/6/10 METER XMTR

SCR-522 revr, xmtr, rack & case, exc. cond. 19 tubes include 832A's, 100-156 mc AM. Satisfaction grtd. Sold at less than the tube cost in surplus. Shpg wt 85 lbs. Fob Bremerton, Wash. **\$14.95**

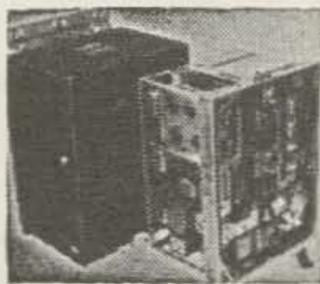Add \$3.00 for complete technical data group including original schematics & parts lists, IF, xtl formulas, instruct. for AC pwr sply, for revr continuous tuning, for xmtr 2-meter use, & for putting xmtr on 6 & 10 meters.



COMMUNICATIONS RECEIVER BARGAINS

BC453B: 190-550 kc 6-tube superhet w/85 kc IF's, ideal as long-wave revr, as tunable IF & as 2nd convert. W/all data. CHECKED ELECTRICALLY Grtd. OK! 11 lbs. fob Los Angeles **\$12.95**

Same, in handsome cabinet w/pwr sply. spkr. etc., ready to use, is our QX-535, 19 lbs. **\$37.50**

RBS: Navy's pride 2-20 mc 14-tube superhet has voice filter for low noise, ear-saving AGC, high sens. & select. IF is 1255 kc. Checked, aligned, w/pwr sply, cords, tech data, ready to use, fob Charleston, S. C. or Los Angeles **\$79.50**

R-45/ARR-7 brand new, 12-tube superhet .55-43 mc in 6 bano's, S-meter, 455 kc IF's, xtl filter, 6 sel. positions, etc. Hot and complete, it can be made still better by double-converting into the BC-453 or QX-535. Pwr sply includes DC for the automatic tuning motor. **\$179.50**
Fob San Antonio

Time Pay Plan: \$17.95 down, 11 x \$16.03

R. E. GOODHEART CO.

Box 1220-GC BEVERLY HILLS, CALIF.

A Good Five Cent QSO

George Thurston W4MLE
3407 Prock Drive
Tallahassee, Florida

WHAT this hobby needs is a good five-cent QSO.

We have plenty of the 50 cent variety—the kind we're all familiar with, which last a minimum of 15 to 20 minutes and consist entirely of an exchange of signal report, name, QTH, a description of the rig (in greater or less detail), a run down on the local weather. And the final five minutes is an exchange of totally banal fond farewell, as though you might mortally insult the guy at the other end by just signing off with him.

"Well OM, guess I better QRT pretty soon. The Jr OP just fell out of the tree and seems to have broken his leg. So thanks a lot for the QSO. Hope to see you again before too long. Sure has been pleasant. Oh oh. XYL just called chow so 73 DX. Good luck. 73 now Tom OB SK K4XXX DE W4MLE 73 GN GL DX SK GE DIT."

We need a procedure signal meaning "I don't want to make RCC. I just want to swap sig reports and scram." Some one has suggested "QCQ" for this purpose. Perhaps you could call CQQ CQQ CQQ DE—and in answering another station's CQ, you might try "W4MLE DE W4XYZ QCQ."

This style of operating—similar in some ways to contest style used in Sweepstakes, CD parties and DX contests—offers many advantages both on phone and CW.

One of my favorite sports is to pick a relatively clear spot (if I can find one) on 40 or 80 CW and call CQ using complete break-in (QSK):

CQ CQ CQ DE W4MLE BK CQ CQ CQ
DE W4MLE BK CQ CQ CQ DE
W4MLE BK and so on until someone answers. The reply to his call goes "W7YYY DE W4MLE GE UR 579 TALLAHASSEE FLA NAME GEORGE BK"

And W7YYY almost always will reply in

FALL SURPLUS SPECIALS DE K2BBC

Read-N-Save

DB Meters 3 1/2" rd -10 to +6db 1mw @ 300 ohms	NEW	\$2.75
Sperti Vacuum Switches for ART-13, etc.	NEW	\$1.00
M-359 Coax Right Angles	5 for	\$1.00
Velvet Verniers w/large knob	NEW	\$1.00
600 Ohm 300 Watt Non-inductive Resistors		\$2.50
WE-255A Polar Relays for TTP		\$4.50
Sockets for use with above relay	NEW	\$2.50
Dummy Loads 27 to 40 mcs 30 watt A-83		\$1.00
Choppers Stvns Arnold #222 AC-DC 110vdc max		\$5.00
Nicad Storage Batteries 1.2v 6amp hrs.		\$2.00
Bank of 10 batteries in plastic case (12v)		\$17.50
Chargers for above (12v) 115ac input		\$4.95

NEW SURPLUS TUBES GUARANTEED

2C39A	\$7.50	6F4 (acorn)	\$1.75	5881	\$1.50
3CX100A5	\$14.50	100TH	\$11.00	6AN5	\$1.25
6161	\$35.00	250TH	\$18.50	6146	\$2.95
829B	\$9.50	6159	\$3.75	446A	\$0.50

MONEY BACK GUARANTEE ON ANYTHING WE SELL

We stock large quantities of Military and Commercial Test Equipment. We buy AN/GRC, PRC, TRC and test equipment TS and AN/UPM or URM. What have you for sale or trade?

Dumont Scopes 256D	\$110.00
304H	\$195.00

SPACE ELECTRONICS CO.

218 West Tremont Ave., Bronx 53, N. Y.
TRemont 8-5222

4X150A Tubes	\$5.50 ea.
Removed from equipment & tested	2/10.00

Sockets for 4X150A etc.	\$6.50 ea.
Eimac #SK-610	2/12.00

T-179/ART-26 Transmitters 300-1275 mc	
Brand new w/tubes	\$59.50

SP-600-JX Receivers .545-54 mc	
Like new	\$425.00

Model 15 TTP complete with synch. motors. Excellent	\$225.00
---	----------

Berkeley Model 5500C Universal counter & timer Lab tested—perfect	\$425.00
---	----------

Low Freq. Marine Receivers—RCA	
3 bands 240 to 2000 kc—115vac	
New condition	\$69.50

BC-463A Transformers and Modulators converts to 6 mtrs. uses	
815 tubes. New	\$19.50

Coax Relays SP3T 28vdc	
General Communications 3N120RC or Thompson Products 10566. New	\$17.95

Bird Model 6250 Milliwattmeter	
0-250mw, 30-500 mc, for Handi-Talkies	
New	\$42.50

kind, often dropping a word about rig, weather or a comment on a new antenna, a question about conditions, DX, traffic or something else.

The QSO usually lasts 3 to 5 minutes because unless it shows promise right away, I "73" the other op on my second transmission. SK is immediately followed by QRZ? And it is surprising how often this will bring an immediate call from some operator who has been reading the mail. Otherwise, the CQ BK is resumed.

Occasionally this has produced eight or ten QSOs or more in an hour of operating but more often the third or fourth—and sometimes the first—of such a series strikes a spark and some really colossal QSOs result.

The third of one such series raised VE3AWE one night and the QSO lasted 56 minutes. Another series produced K2UKQ and Kay and I have had many pleasant QSOs since then.

The first CQ BK not long ago produced W4IEI and the resulting QSO lasted more than two hours and a half and was repeated in similar length the following night and a shorter one (only two hours) two nights later.

Far from being "anti-social," the quick QSO is a fine way to add many new friends. They come around more often for second

QSOs if they weren't bored to death the first time.

A K3 called me one evening and got the stock "UR 579 TALLAHASSEE FLA NAME GEORGE BK" and reproached me with "are you in a contest or something? I try to make friends in my QSOs, not just fill my log with numbers."

Before telling him I had just finished a 75-minute QSO with a perfect stranger I asked my K3 friend whether he considered brevity unfriendly.

Is it more friendly to say "UR 579 TALLAHASSEE FLA NAME GEORGE BK?" Or to say "R R R R R GE OM TNX FER FB CALL UR SIGS HR 579 579 579 HR IN TALLAHASSEE FLA THE CAPITAL CITY OF THE SUNSHINE STATE? TALLAHASSEE FLA? TALLAHASSEE FLA BT THE HANDLE HR IS GEORGE? GEORGE? GEORGE BT SO HWS THE WX THERE IN K3 LAND OM? AR K3XXX DE W4MLE?"

They both convey exactly the same information. So why is the five minute variety "friendlier" than the ten second variety?

Certainly the latter approach is more time consuming if the object is sheer length in QSOs.

But I'm inclined to like the briefer and friendlier ones. . . . W4MLE

(W2NSD from page 4)

of a screen dropping resistor, self biasing and a clamp tube would even eliminate the need for the two surplus supplies. The 2000 volts (modulated) come from an old National 600 transmitter, vintage 1937. The power supplies from Meshna replaced a couple of bread-board supplies that I whipped up the last time I ran the final back in Brooklyn in 1956-7-8. It makes it neater. By judicious surplus scavenging and a careful eyeballing of the ham ads you should be able to duplicate my feat quite reasonably.

Once you are on two meters with higher power you will find an entirely different operating world from the Twoer-Halo type of operating. When the band begins to open up you can be in there working the weak ones. When aurora starts you can get answers to your calls. It may be fun to sit there calling station after station, only to hear them come back to someone else, but it doesn't in any way match the fun when they come back almost every time you call. It is worth the effort necessary. Like all other things in this life, you get fun out of ham radio in proportion to the effort you put in.

FM

Our article on the Friendly Frequency in the June 1962 issue of 73 has resulted in a lot of mail and considerable interest. We are preparing a booklet on the conversion of the AN/VRC to six meter FM, which should get a few more fellows interested. In case you are fuzzy on this, there are several hundred fellows set up on 52.525 mc wide-band FM around the country. Most of them are using converted Motorola gear and surplus gear. The idea is to have a completely separate station with squelch set up on the calling channel so that anyone calling in will have someone or group to talk to. It sure helps tie clubs together and adds a new dimension to mobile operating in cities. Jack Cunkelman W3JKE has published a listing of the FM nets all over the country and the individual stations active in these nets. He also lists the phone number and type of equipment used by each station. It is quite a list and should be in your car if you travel and are set up for 52.525 mc. Copies may be obtained for 25¢ each from Jack.

Anthem

The anti-communists are still in there pitching, trying valiently to sacrifice ham radio for a few moments of their own personal glory. What ever happened to the Old West where they went to lynchings instead of drive-ins?

Come on, California, clean up those nuts.

It is heartening to see that the FCC is clamping down on the broadcasting of political nonsense from these guys. I hope they scuttle that incredible request to allow us to play the National Anthem twice a day which has been sent as a petition to the FCC. I can just hear 20 meters now with 100,000 amateur radio stations playing the Anthem twice a day, seven days a week . . . you wouldn't hear much else. With a market like that you can bet that some record company would come out with a long-play rendition of the Anthem that would run 45 minutes.

Ham radio is a fine hobby . . . let's not ruin it with nationalism. We know we have a great country and this comes through every time we talk to a DX station. Let's sell ourselves that way. Let's not try to sell politics, religion and other relatively unsalable items over the air. If you have an urge to sell, dissipate it by selling all comers on the advantages of subscribing to 73.

Mobile Monitor Scope

A reader advises that the 2BP1 or 2BP1A are better alternatives for the obsolete 913 specified in the article in the August '62 issue of 73 than the suggested 2AP1, which requires a higher anode voltage.

Flagging Interest

There were several interesting things in the July issue of CQ (no fooling!). #1 was the USA-CA column by K6BX. This column started out with two waving American flags and reached a crescendo with a huge full page reproduction of the actual USA-CA award certificate, which features not only a large American flag waving, but all fifty of the State flags. In this day and age where we are used to seeing the American flag being waved more by charlitans and subversives of the far left and far right, it is nice to see someone with honesty and purity in his heart using the American flag as a rallying point.

Further along in this column Cliff has a flash announcement that we are coming out with some sort of award which will do away with all other awards. Good for us.

There are several questions which the column did not resolve for me though. (1) Who originated the idea of an award for working counties? (2) Did Charlie Vogelsong W3BQA send the idea for this award to K6BX together with the rather complete set of proposed rules which were later published as K6BX's? (3) Did this award pave the way for K6BX to

get a position on the CQ staff? (4) Did K6BX offer W3BQA USA-CA Certificate Number One in return for his not revealing the situation leading up to the announcement of the new award? (5) Was Charlie foolish to turn down this great honor and thereby miss out on being the feature attraction at the Dayton Hamfest dinner? (6) Are the USA-CA awards all legitimate? (7) What will happen next? (8) Did you know that there is a fine wall-sized map of the US showing all counties available from the Gov't Printing Office and put out by the Dept. of Commerce?

Advertisers

It is encouraging to note that several advertisers have had such good success with 73 that they have decided to run all further ads in 73. Each month there are a few new advertisers who are testing the ability of 73 to sell their products for them. Since it is these advertisers who are buying your magazine for you (the newsstand and subscription price doesn't begin to cover printing costs) it sort of behooves you to take more than a casual look at the ads and to talk up 73 with any advertisers that interest you. Just a few more ads and we will be able to expand the magazine and bring you more pages of articles each month. I call your attention particularly to our Surplus section of the magazine. We have the largest collection of surplus ads of any radio magazine and it will stay that way if you keep after them. Barry, Meshna, Rex, TAB, Goodheart, Verns, Hi-Way, Fair, US #1, Space, Columbia, Candee, JJ Glass, Signal, Jeffronics, all have some great buys. Don't miss the catalogs they put out and stop in to see them if you can. I visited Meshna recently and really loaded up the car . . . what a collection he had. The new Barry catalog eats your heart out. Fair has a terrific selection, ditto Columbia and Candee.

73 TESTS

Perspicacious readers may notice that we have more than the usual sprinkling of tests of new gear this month. There are obvious reasons for the spate at this time. 1) The increased sales which these test reports might bring on will undoubtedly result in a much merrier Christmas for the manufacturers involved . . . and this may just result in a merrier New Year for us when the new ad contracts come in. 2) The test reports are very handy for you to use as a sort of shopping list for the XYL and harmonics for Christmas. Buy them one each of the products tested and watch their surprised expression on Christmas morning.

COLUMBIA GEMS!

SPECIAL! 144 or 220 mc TRANSMITTER

20 watts! Simple to convert 242 mc DXT-2 Beacon Transmitter, measures 4" x 4" x 11" complete with antenna, water-tight case and sidetone modulator. Power required 300V DC & 6.3V. Uses two 12AT7 and one 6360 final (not furnished). Schematic and 2-meter conversion data included. Hundreds sold already at this fabulous price. BRAND NEW, only **6.95**

BC-453 Q-5'er Receiver, 190-550 kc, Excellent Condition **12.95**

Send for Columbia's New 48-Page Catalog of Surplus Electronic Bargains!

Name..... Call.....
QTH
City..... Zone..... State.....

COLUMBIA ELECTRONICS

4365 WEST PICO BLVD. LOS ANGELES 19, CALIF.

J. J. GLASS

THIS MONTH'S SPECIALS

12V TCS Power Supply consisting of 1 Transmitting Dynamotor, 420V @ 200 MA., and 1 Receiving Dynamotor, 220V @ 100 MA. Fully Filtered, mounted on base which includes starting solenoid, 12V relay, choke, etc. This supply can be used to operate ARC-1, ARC-3, ARC-5, etc. Diagram for easy hook-up included. ALL NEW.....\$9.95
Spare Parts Kit for above, consisting of Transmitting & Receiving Dynamotors, Relay, Choke, Brushes, Fuses, etc. NEW.....\$4.95

12-24V INVERTER. No more bother to change surplus 24V gear to 12V! Just use this converter, feed in 12V, output supplies 24V @ up to 4 Amps. Enough to operate 24V Xmtr & Rcvr without internal changes. Compact metal container 4½" x 10" x 7". ONLY.....\$8.95

SOMETHING NEW! Just Purchased—24V Generator, produces 25 Amps. Complete with spline, Very compact, 9" x 6". BRAND NEW.....\$7.50

J. J. GLASS CO.

1624 S. Main St., Los Angeles 15, Calif.
RI 9-1179 (213)

Fridays 'til 9

Send for Catalog!

WANTED:

TUBES, DIODES, TRANSISTORS, MILITARY, COMMERCIAL LAB-GRADE TEST EQUIPMENT, COMPONENTS, PRC, GRC EQUIPMENT, AIRCRAFT EQUIPMENT BY COLLINS. TOP PRICES. WRITE DETAILS,

BOB SANETT

W6REX, V & H RADIO ELECTRONICS, 2053 VENICE BLVD., LOS ANGELES 6, CALIFORNIA.

Advertisers

Ad Com	37
Alco	83
Alden	62
Allied	96
Alltronics-Howard	65
Arrow	29
Bald Eagle	65
Barrington	65
Barry	94
BC Electronics	65
B & W	35, 71
Callbook	79
Candee	89
Clegg	13
Cleveland	53
Coil Book	17
Columbia	93
Columbia Products	23
Continental	15
Cushcraft	19
C-Y	75
Dow	57
Dow Key	41, 59, 71
Drake	65
Ebco	17
Epsilon	81
E-Z Way	4
Fair	89
Finney	23
Gam	11
Gavin	20
Glass	93
Gonset	25
Goodheart	90
Graham	83
Ham Aids	79
Hammarlund	Cover 3
Heath	30
Hi-Par	19
Hi-Way	90
Hy-Gain	39
Institute of Amateur Radio	81
Instruments and Communications	45
International Crystal	5
Irving	25
J & D	11
Jefftronics	85
KTV	59
Lafayette	3
Limachi	79
Maps	59
Math Book	55
McCoy	22
Meshna	87
Miller	55
Mini-Products	63
Mission	55
National	Cover 4
Newtronics	33
Nortronics	19
Pausan	75
Pel	69
P & H	17
Polytronics	21
Radio Amateur Callbook	79
Radio Bookshop	73
Rex	85
Signal	85
Skylane	59
Space	91
Subscription	74
Supreme	48, 49
Swan	36
TAB	95
Technical Materiel Corp.	43
Telco	9
Telrex	61, 77
Transceivers	81
Trembley	55
Tri-Ex	47
US #1	89
UTC	Cover 2
Vanguard	19
Verns	89
Vesto	63
V & H	93
Waber	67
Waters	27
Western (Calif.)	71
Western (Neb.)	75
WRL	78
W5GOS Maps	59
73 Products	84
73 Subscription	74

1963 BARRY GREENSHEET!

OUT AT LAST

Write

RCA PRECISION 500 KC CRYSTAL OSCILLATOR \$5.00

Accuracy plus or minus 0.0012%. Contains Precision 500 KC crystal, BMS Labs Crystal oven, 5840 sub-miniature tube. Hermetically sealed nickel plated rectangular case. Mounts in standard 7 pin miniature socket. Requires 6.3 VAC or DC, 75 to 100 V.D.C. With schematic. RCA Type A828300-1. Size: 4½"H x 17/16"W x 1½"D. Wt.: 1 lb. Cat. #4-500 CRV. (Orig. Govt. Cost: \$172.00.)

VERY SPECIAL . . . ONLY \$5.00 Postage Prepaid.

Eimac 4X15A/4010 air socket \$6.95
Sale on the following: NC-400, Mosley Antennas, CD Rotators, Electro-voice mikes, SP-600, SP-200, prop-pitch motors, full line of Ameco.
Silicon rectifiers—750 Ma/600 PIV ea 36¢

COME IN SATURDAY. From 10 A.M. to 2 P.M. Free parking on Saturday. Mon to Fri.: 9 A.M. to 6 P.M.

BARRY ELECTRONICS CORP. DEPT. 73-11
512 BROADWAY, NEW YORK 12, N. Y.
WALKER 5-7000 AREA CODE: 212

Enclosed is money order or check and my order.
 Send copy of "Green Sheet" Catalog.

Name _____ Title _____

Company _____

Address _____


City _____ State _____

"TAB" SILICON 750MA^o DIODES

Factory Tested Gtd.!

NEWEST TYPE! LOW LEAKAGE

D.C. or Batty. Derate 30%

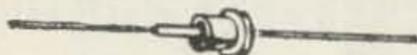

rms/piv 35/50 .07	rms/piv 70/100 .14	rms/piv 140/200 .19	rms/piv 210/300 .29
rms/piv 280/400 .34	rms/piv 350/500 .44	rms/piv 420/600 .53	rms/piv 490/700 .69
rms/piv 560/800 .85	rms/piv 630/900 .96	rms/piv 700/1000 1.06	rms/piv 770/1100 1.50

Low Priced T300 Silicon Diodes
Rated 400 pvi/280rms @300Ma @100°C
.25 each; 30 for \$7; 100 for \$20;

Diode order \$10 shipped Post free

ZENER DIODES 150 to 400 MW
CASED TO24 Pckg. Within 20%
V-Range \$1, 3 for \$2, 20 for \$10,
KIT ZENER DIODES up to 400MW,
SINGLE & DOUBLE ENDED 2
for \$1; 12 for \$5; 100 for \$36.

SILICON POWER DIODE STUDS^o

Operation Up to 125°C Case Temp.


D.C. Amps	50Piv 35Rms	100Piv 70Rms	150Piv 105Rms
2	.23	.34	.42
3	.60	.85	1.10
6	.70	.95	1.15
12	.85	1.15	1.35
35	1.80	2.20	2.95
70	3.75	4.50	5.00
240	4.50	5.40	7.70

D.C. Amps	200Piv 140Rms	300Piv 210Rms	400Piv 280Rms
2	.49	.60	.84
3	1.25	1.50	1.80
6	1.40	1.65	1.95
12	1.60	1.85	2.07
35	3.25	4.90	6.10
70	5.60	8.80	Query
240	9.00	Query	Query

*Derate 20% for Battery or Capacitive Load or D.C. Blocking!

*Stud mounted on Heat-sink

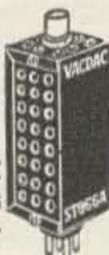LO PRICED SILICON TUBE REPLACEMENTS WITH BUILT IN SURGE AND SERIES BALANCING PROTECTION



TYPE	VRMS/PIV	AMPS	PRICE
T866	5000/10400	0.3	\$16
T5R4	1900/2800	0.5	\$7

"TAB FOR TRANSISTORS & DIODES!"

Full Length Leads Factory Tested

& Guaranteed! U.S.A. Mfg.

PNP Hi Power 15 Amp. TO3

& TO36 Round Pckg.

2N441, 2N277 \$1.25, 4 for \$4;

2N442, 2N278 \$3@, 2 for \$5;

2N143, 2N174 \$4@, 2 for \$7;

2N677 \$1@, 12 for \$10;

2N677A \$2@, 6 for \$10; 2N677B \$3@,

4 for \$10; 2N677C \$5@; PNP 2N123,

2N107, CK722 4 for \$1, 25 for \$5; NPN

2N292, 2N293. PNP 2N223 \$30@, 15 for

\$4, 100 for \$22; PNP 2N670/300MW \$40@,

20 for \$7; PNP 2N671/1W \$60@, 10 for

\$5; 2N597, 2N598, 2N599 PNP \$1.50@,

4 for \$5.

\$10 or more this item POSTPAID U.S.A.

RND(TO36), or Diamond (TO3)

mica kit 30¢ ea. Power Heat Sink

Finned (80" sq.) \$1.25, 5 for \$5.

GTD! Power-Diamond-Transistors

Factory Tested

***MFGD In U.S.A.

Univ. Replcmnt

2N155, 2N156, 2N234,

2N256, 2N307, 2N554

SPECIAL TO3GP55¢, 10 for \$5

40 for \$18

\$10 or more this item we pay P.P./U.S.A.

Kit Glass Diodes equiv. 1N34A, 46,

48, 51, 60, 64, 87, 105, 109, 147, 267,

268, 295, 12 for \$1, 100 for \$7.50.



"TAB" THAT'S A BUY

"TAB" Tubes Factory Tested, Inspctd,
Six Months Guaranteed! No Rejects!

Boxed!
GOVT & MFGRS Surplus! New & Used

0A2 1.00	6J799	56S1 1.20
0A395	6K779	56S6 3.00
0B265	6L699	56T090
0C365	6SN772	568775
0D3 2/81	6T898	572565
OZ479	6Y6GT70	573260
1B399	6X549	5751 1.00
1L4 2/81	12AT659	581460
1R4 5/81	12AT785	5879 2/81
1S460	12AU663	5894 13.50

We Swap Tubes! What Do/U Have?

1T460	12AU769	2AP5 3.00
1T555	12AX775	3BP1A 5.00
1U4 5/81	12AY789	3KP1 6.00
1U565	12BA790	3SP1 3.00
1X299	12BE6 2/81	5CP1 5.00
2C39A 10.00	12H6 3/81	5CP4A 6.00
2C40 5.00	12J569	5MP1 6.00
2C43 5.50	12J769	5MP4 6.00
2C51 1.25	12K870	5NP1 6.00
2D21 2/81	12SC7 3/81	5ABP1 20.00

Send 25¢ for Catalog!

2E22 1.75	12SG760	5AQP1 20.00
2E24 1.80	12SH760	5AQP7 20.00
2E25 2.50	12SJ760	5AP1 5.00
2E26 1.80	12SK775	5ADP1 35.00
2K25 6.50	12SL759	5ADP7 25.00
2V3C 2/81	12SN769	5BP1 6.00
2X2 2/81	12SR769	5BP2 6.00
3C24 3.00	24C 3.00	5BCP7 25.00
3D23 2.40	25A6 1.25	5BG7 35.00
3E29 5.90	25L6 2/81	5BHP2 25.00

Wanted 304TL Tubes

3Q585	25T 5.00	5CP1A 7.00
4-65A 9.50	25Z572	5CP5 4.00
4-125A 21.00	25Z675	5CP7A 4.00
4-250A 33.00	35Z585	5CP11A 5.00
4X150A 14.00	RK39 2.50	5FP1A 18.00
4X250 34.00	50L6 2/81	5FP4A 18.00
4X500 37.00	7581	5FP5 3.00
5R4 1.00	83V 2/81	5FP7A 3.00
5T4 2/81	2000T 150.00	5FP14 3.00
5U475	4X150G 12.00	5FP14A 6.00

125°C SILICON PNP TRANSISTORS

250 to 400 MW

FULL LENGTH LEADS

Factory Tested & GTD!

\$5 to \$11 - SMALL - TO5 & TO18 Pckg.
Replaces 2N327A; 332, 3, 4, 5, 6, 7, 8;
474, 5, 6, 7, 8, 9; 2N480, 541, 2, 3;
2N935, 36, 37; 2N1034; 2N1131, 2; 1276,
7, 8, 9. "TAB" SPECIAL \$69@, 7 for \$4,
20 for \$10.

\$10 or more this item, we pay P.P./U.S.A.

5V489	4X250B 30.00	5HP4 10.00
5Y359	4-400A 33.00	5JP1 2.00
5Z389	250TL 18.00	5JP2 1.00
6A799	307A 3/81	5JP14 25.00
6AB99	VR92 5/81	5LP1 18.00
6AB4 2/81	388A 2/81	5LP1A 25.00
6AC769	350A 1.00	5LP4 6.00
6AG559	350B 1.00	5LP7A 6.00
6AG7 2/81	6146 2.45	5RP1 25.00
6AK569	450TH 25.00	5SP7 15.00

Wanted Test Sets and Equipment

6AL559	450TL 24.00	5SP7A 21.00
6AQ565	460 11.50	5OP4 8.00
6AR675	707B 1.25	5UP1 6.00
6AS7 2.85	715C 10.00	5XP21 36.00
6AT665	723AB 2.50	5YP1 25.00
6AU670	725A 3.50	7BP1 5.00
6B880	805 3.35	7BP4 5.00
6BE659	807 1.10	7BP4A 5.00
6BG6 1.49	811 3.90	7BP7 2.00
6BH679	811A 4.75	7BP7A 5.00

Top \$\$\$ Paid for 304TL, 813, 811A, 812A Tubes

6BK799	812 3.95	7EP4 5.00
6BL7 1.30	813 12.00	7GP4 7.00
6BX7 1.11	815 1.75	9AUP7 5.00
6BY5 1.19	829B 7.50	9JP1 5.00
6BZ673	832A 5.00	9LP7 1.00
6C445	833A 36.00	10BP4 6.00
6C5 2/81	837 1.50	10KP7 11.00
6C8 2/81	866A 1.50	12CP7 7.00
6CB670	954 10/81	12QP4 9.00
6CD6 1.49	957 10/81	12KP4A 9.00

Top \$\$\$ Paid for 304TL Tubes!

6E579	991 5/81	12SP7 11.00
6F4 1.85	1619 5/81	14EP4 10.00
6F5 2/81	1620 1.00	16CP4 12.00
6F6 2/81	1625 3/81	16DP4A 12.00
6F874	1626 12/81	17AVP4 14.00
6H6 4/81	1629 4/81	17AP4 14.00
6J4 1.72	2050 1.20	17CP4 14.00
6J5 2/81	5517 2/81	17KP4 14.00
6J6 2/81	5608 3.95	19DP4 16.00

"TAB" TERMS: Min Order \$5-25% with order F.O.B. New York. Ten day guarantee, price of mds. only. Our 18th year.

Prices shown are subject to change.

111MG Liberty St., N. Y. 6, N. Y. • RE 2-0245

"TAB" FOR THE BEST KITS!

Each "TAB" Kit Contains The Finest Selection!!!!

- Kit 75 Mica Condensers
- Kit 8 Crystal Diodes
- Kit 200ft Hook Up Wire
- 4 Rolls, 50ft/ea. Asstd. Color
- Kit 100 Ceramic Condensers
- Kit 5 FT243 Xtal Holders
- Kit 4 Microswitches
- Kit 8 Xtal Osc-Blanks
- Kit 4 Asstd Rectifiers
- Kit 100 Self-Tap Screws
- Kit Adj Wire Stripper & Cut
- Kit Hi Gain Xtal Mike
- Kit 6 ea Phonoplugs & Jacks
- Kit 2 pair SO239 & PL59
- Kit 12 Binding Posts Asstd

Order Ten Kits—We Ship Eleven!!!
99¢
(ONE EACH ABOVE KIT ONLY.....)

TWO 866A's and FILAMENT \$6
XFMR 10 Kv Insitd SPECIAL \$6

Transistor Power CONVERTER
12VDC to 500VDC up to 200MA
100 Watts; Tap at 250VDC
DB500 \$33
12VDC to 250VDC up to 150MA
Type C1225E \$30

Leece Neville Charger Systems
Sealed Silicon Stud Rectifier
Finned Stack, Direct Replacement
FOR 6 or 12VDC @ 100A.
Type YJ9 \$18

"TAB" BARGAINS
New Variacs/or equiv 0-135V/7.5A \$15.30
New Variacs/or equiv 0-135V/3 Amp \$10.65
DC-METER Dejur 800 Ma/2 1/2" \$3@.
DC MTR 100Ma/2 1/2" \$3@.
RF-MTG GE/475 Ma & 5 Amp \$4@, 2/\$7
DC-METER One Ma/4" Rd...\$5@, 2/\$8
SNOOPSCOPE TUBE 2"....\$5@, 2/\$9
MINI-FAN 6 or 12VAC/60 Cys \$2@, 3/\$5
Xmitting Mica's .006 @ 2500V, 5 for \$1.00
4x150 Ceramic/LOKTAL 2 for \$1.00
866A Xfmr. 2.5V/10A/10KV Insl...\$3.95
Microswitch B1/SPNC/30 Amp 49¢@,
Tube Clamps Bircher..... 5 for \$1.00
.012 at 25Kv CD Condenser....\$4@,
WE Choke 4Hy/450Ma/27 Ohms \$4@,
Line Filter 50Amp/250VAC...\$10@,
Line Filter 200Amp/130VAC...\$18@,
Bruning Parallel 8" Rule...69¢@,
KS15138 Linear Sawtooth Pot.. 2 for \$1.00
"CTC" Delay Line 1 Microsec'd \$1@, 3/\$2
Vacuum Condrs 50Mmf/7.5Kv \$3@.

D.C. Power Supply 115V/60 to 800
Cys. Output 330 & 165 VDC up to 150
MA. Cased SPECIAL \$5.


SELENIUM F. W. BRIDGE RECTIFIERS

DC AMP	18VAC 14VDC	35VAC 28VDC	72VAC 54VDC	130VAC 100VDC
1/2	\$1.00	\$1.90	\$3.85	\$5.00
1	1.30	2.00	4.90	8.15
2	2.15	3.00	6.25	11.10
3	2.90	4.00	8.60	13.45
6	4.15	8.00	18.75	31.90
10	6.10	12.15	26.30	41.60
12	7.75	14.90	30.95	43.45
20	12.85	24.60		
24	15.00	29.45		

Write For Rectifier Catalog

Send 25¢ for New Catalog

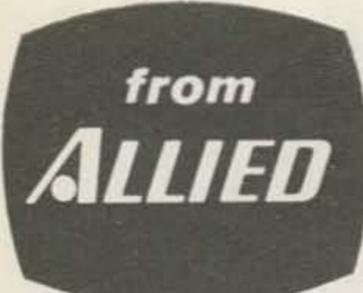POTLUCK SEMICONDUCTOR KITS
(NO OPENS OR SHORTS)
SILICON STUD-DIODES ASSTD.
2 to 6 Amp..... 6 for \$1
TRANSISTORS TO5 GERMANIUM
PNP 6 for \$1
TRANSISTORS TO5 GERMANIUM
NPN 4 for \$1
TRANSISTORS SILICON up to
400MW/PNP 3 for \$1
SILICON DIODES up to 750Ma.. 18 for \$1
ZENER DIODES up to 10 Watts.. 4 for \$1
\$10 or more this item, we pay P.P./U.S.A.



Punch Out a Great Signal with this *knight-kit*® 150-Watt AM-CW Transmitter

MOST "WATTS-PER-DOLLAR"!

- 150-Watt Input 80-10 Meters; 100-Watt on 6 Meters
- Controlled-Carrier Screen Modulation for Max Power
- Stable Built-in VFO with Planetary Drive Tuning
- Clean, Chirpless Keying—No HV at Key Terminals
- Adjustable Pi-Network Output Matches 40-600 Ohm Antenna



New! Matching R-100A Receiver Kit

ONLY
\$99⁹⁵

\$5 monthly Tremendous quality and value! Covers 540 to 30 mc; bandspread on 80-10 meters; better than 1½ µv sensitivity for 10:1 S/N; selectivity 300 cps to 4½ kc continuously variable; built-in Q multiplier—60db notch really knives through QRM; exalted BFO injection; printed-circuit bandswitch; MVC; delayed AVC; noise limiter—and many other professional features. With all parts, tubes, gray metal cabinet (9½ x 17½ x 9½"). Less S-meter, speaker kits. 31 lbs.

83 YU 406DM. R-100A Receiver Kit, only **\$99.95**

83 Y 423. S-Meter Kit. Reads to +20 db over S9, only..... **12.95**

83 Y 424. Speaker Kit. 4 lbs..... **19.95**

New T-150 Transmitter Kit

ONLY
\$119⁹⁵

only \$6 monthly on Allied's Credit Power Plan

Packed with features to put out a solid signal that really punches thru the QRM! 150 watts AM/CW input on 80 thru 10 meters, 100 watts on 6 meters. Highlights: Highly stable VFO has illuminated dial and planetary drive; socket for optional switch-selected crystal operation; efficient controlled-carrier screen modulation; adjustable pi-network matches 40 to 600 ohm antennas; buffer stage isolates oscillator from final; parallel 6146's in output stage; silicon diodes for reliable high-voltage and low heat; voltage regulator in B+; single knob bandswitching; TVI suppressed with all leads in and out of case by-passed for RF; switched meter reads buffer, final grid and final plate currents and relative power output; mode switch provides for VFO spotting and tuning without placing a signal on-the-air; clean chirpless keying—no high voltage at key terminals; plus a host of other fine features. With all parts, tubes, plugs, wire, solder and step-by-step instructions and handsome gray satin metal case, 8½ x 17 x 10½". Less mike, key, crystals. For 110-125 v. 60 cycle AC. 28 lbs.

83 YU 403DM. T-150 Transmitter Kit, only..... **\$119⁹⁵**

satisfaction guaranteed or your money back

NO MONEY DOWN!
Now! More Buying Power with your Allied Credit Fund Plan

manufactured by
KNIGHT ELECTRONICS CORP.
A DIVISION OF
ALLIED RADIO

ALLIED RADIO

100 N. Western Ave., Chicago 80, Ill.

Ship me the following:

- T-150 Transmitter Kit 83 YU 403 DM
- R-100A Receiver Kit 83 YU 406 DM
- S-Meter Kit 83 Y 423. Speaker Kit 83 Y 424.
- Ship No Money Down on Allied's Credit Fund Plan →
- \$_____ enclosed (check) (money order)

Name _____
PLEASE PRINT

Address _____

City _____ Zone _____ State _____

ORDER TODAY

New Credit Customers Only: Send name and address present employer, how long employed, position, monthly salary (also same for prior employment); rent or own home, how long at present address (also same for prior address); 2 credit account references; give age (21 min. for credit accounts).



RED HOT and ready!

the Scintillating Single Sideband SPECIALIST

HAMMARLUND'S NEW **HQ-170A**

TRY THIS COMBO



Take one
Hammarlund
HQ-170A



Hammarlund's
"Fabulous '50"—the
new, compact, crystal
lattice filter-type
SSB transmitter.



**THE BEST AMATEUR
RADIO STATION
MONEY CAN BUY!**

Fill-in the attached coupon and let us send you complete technical data on this revolutionary new equipment.

We did more than add a letter to the famous HQ-170: we added

- ★ Significantly improved electrical and mechanical stability.
- ★ Silicon rectifiers—for cool, high efficiency operation.
- ★ 144 to 148 mc dial scale for 2 meter converter use.
- ★ Accessory power supply socket for converters, etc.
- ★ Separate system socket for convenient transmitter/receiver control.
- ★ "Flip-open" top for greater convenience.

It wasn't easy. We set out to improve the receiver recently voted **FIRST IN ITS CLASS**. The one and only amateur band receiver that offers so much for SSB and AM/MCW. Full coverage of 6, 10, 15, 20, 40, 80, and 160 meter bands—plus 2 meter calibration for converter use. Triple conversion with fixed IF frequencies provide optimum spurious response rejection.



AMATEUR RADIO EQUIPMENT
COMMERCIAL
COMMUNICATIONS EQUIPMENT
OUTERCOM 2-WAY RADIO
VARIABLE AIR CAPACITORS
SUPERVISORY REMOTE
CONTROL SYSTEMS

HAMMARLUND Manufacturing Company —Dept.

A Giannini Scientific Company
53 West 23rd Street, N. Y. 10, N. Y.

Please send me brochures on:

HX-50 \$399.50 HQ-170A \$369.00*
(*24 hour clock-timer \$10 optional)

NAME _____

ADDRESS _____

NATIONAL'S NEW NCX-3 Tri-Band Transceiver!

- Complete SSB, AM and CW coverage of the 80, 40, and 20 meter amateur bands!
- Full 200 watts PEP!
- Every desirable operating feature!



Now from National — a brand-new Transceiver concept that brings you the three most popular amateur bands at a price equivalent to economy single-band units! No need to compromise on only one band — no need to spend a \$300 to \$800 premium for coverage of the two steadily deteriorating high frequency bands! The handsome, rugged, NCX-3 complements both your car and the ham shack, and provides you with a solid 200 watts of SSB punch — plus — every feature National could think of for easy, relaxed ham band operation — vox or push to talk, CW break-in, SSB/CW AGC, S-meter — even a separate AM detector! The specifications below really tell the story . . . study them carefully and see your National dealer as soon as possible. We're devoting additional production facilities to the NCX-3 to assure maximum delivery rate, and will start delivery December 30 — don't postpone your enjoyment of the new NCX-3 — get your advance order in now!

NCX-3 SPECIFICATIONS

Frequency Range: 3.5, 7.0, 14.0 Mc. amateur bands • **Types of Emission:** SSB (LSB 80 and 40 meters, USB 20 meters), AM (SSB with carrier inserted), CW • **R. F. Power Input:** 200 watts SSB PEP, 180 watts CW, 100 watts AM • **R. F. Power Output:** 120 watts SSB PEP, 108 watts CW, 30 watts AM • **Output Impedance Matching Range:** 40-60 ohms • **SSB Generation:** 5200 Kc crystal filter; bandwidth 2.5 Kc at 6 db • **Frequency Stability:** 400 cycles long-term after warm-up • **Suppression:** carrier —50 db; unwanted sideband —40 db • **Operating Facilities:** all modes — full AGC and S-Meter on receive; SSB-VOX or PTT transmit, product detector on receive; AM—VOX or PTT transmit, separate diode detector on receive; CW — grid block break-in transmit, product detector on receive • **Audio Input:** High impedance, low level • **Controls:** Front panel — Main Tuning, Band Selector, Audio Gain, R. F. Gain, Microphone Gain, Mode (off, SSB, AM, CW, tune), Carrier Balance, Driver Tune, PA Tune, PA Load; Rear panel — Vox Sensitivity, Anti-Vox, Vox Delay, Bias Adjust, Vox Input, PTT Input, Key, Phones, Ext. relay • **Metering:** PA

cathode current on transmit; S-Meter on receive • **Receiver Sensitivity:** 1.0 μ V. for 10 db S/N ratio • **Receiver Selectivity:** 2.5 Kc at 6 db • **Receiver Audio Output:** Better than 2 watts; 3.2 ohms • **Size:** 6" H., 13 $\frac{1}{2}$ " W., 11 $\frac{1}{2}$ " D. • **Shipping Weight:** 20 pounds • **Power Requirements:** 700 V.D.C. @ 300 ma., 280 V.D.C. @ 100 ma., —80 V.D.C. @ 10 ma., 12.6 V. @ 5A. • **Tube Complement:** 17 tubes, 4 diodes; parallel 6GJ5's in final amplifier. • **Mechanical:** $\frac{1}{2}$ " solid extruded aluminum front panel; perforated steel enclosure; cadmium plated steel chassis; chromium plated steel mobile mounting bracket. • **Main Tuning Ratio:** 45:1, employing planetary and split gear drive. • **Finish:** Front panel — Hydro-etch off-white matte with brushed aluminum trim; Knobs — Mil-Spec, matte black; Enclosure — gray-blue wrinkle enamel. • **Accessories:** NCXA 115 V.A.C. power supply/speaker console; NCXD 12 V.D.C. power supply

New NCX-3 only

\$369



National Radio Co., Inc.

National Radio Company, Inc., Melrose 76, Mass. Dept. 0000
A Wholly Owned Subsidiary of National Company, Inc.

World Wide Export Sales: Ad Auriema Inc., 85 Broad St., N.Y.C.

Canada: Tri-Tel Assoc., 81 Sheppard Ave. W., Willowdale, Ontario