

73

APRIL 1965
A Balmy 40c

Special SSB Transceiver Issue

Amateur Radio

\$120



\$350



\$350




\$370



\$395



\$395

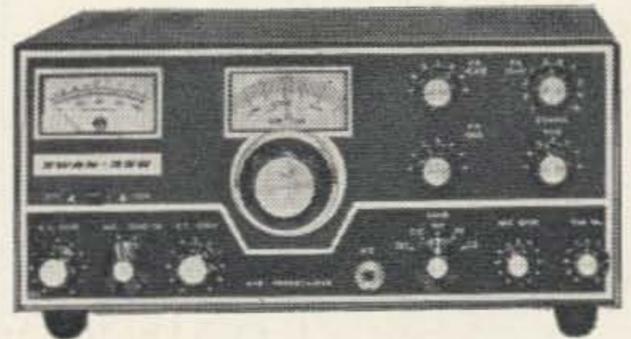

\$550



\$1150



GOT A SIGNAL TO RADIATE?

MAKE YOURS A REAL SIGNAL

... use a **CUSH CRAFT ANTENNA!**

Whether you are ...


- TRACKING SATELLITES
- MOON BOUNCING
- DX-ING
- RAG CHEWING
- WINNING CONTESTS

... you will do it better, more efficiently, and at a lower cost with a **CUSH CRAFT ANTENNA.**

YOU WILL HAVE A SIGNAL THAT REALLY RADIATES WHEN YOU BUY CUSH CRAFT ... THE ANTENNAS WITH A "PATTERN OF FIRSTS" IN AMATEUR COMMUNICATIONS.


SQUALO

ANOTHER
CUSHCRAFT
FIRST!

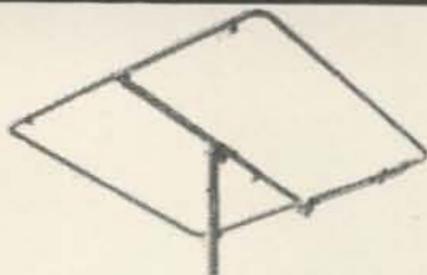

SQUALO is a full half wave, horizontally polarized, omni-directional antenna. Outstanding all around performance is achieved through a 360° pattern with no deep nulls. The square shape allows full electrical length in compact dimensions. Direct 52 ohm Reddi Match feed provides ease of tuning and broad band coverage.

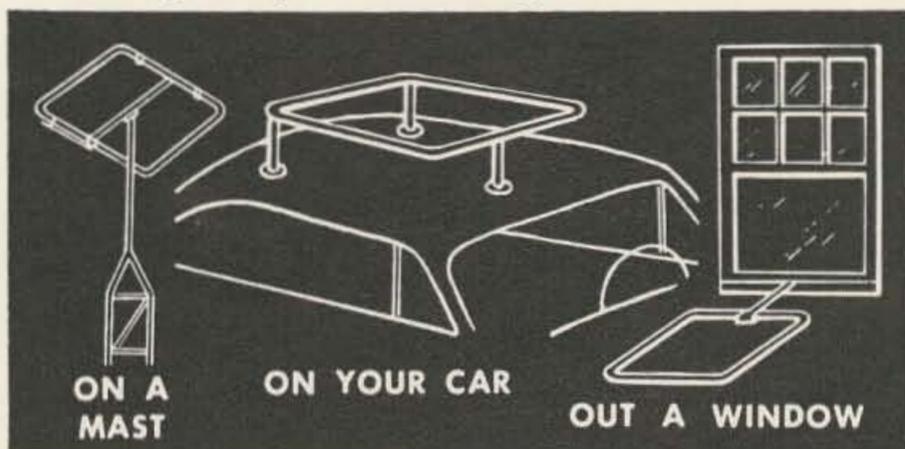
The 6 meter Squalos are completely universal for mounting anywhere. They are packaged with rubber suction cups for car top mounting and a horizontal center support for mast or tower mounting. The 10-15-20 and 40 meter Squalos are designed for mast or tower mounting. Squalo is ideal for net control, monitoring, or general coverage.



MODEL NUMBER	DESCRIPTION	NET PRICE
ASQ-2	2 Meter 10" square	\$ 8.45
ASQ-6	6 Meter 30" square	12.50
ASQ-10	10 Meter 50" square	19.50
CSQ-11	11 Meter 50" square	19.50
ASQ-15	15 Meter 65" square	23.50
ASQ-20	20 Meter 100" square	29.50
ASQ-40	40 Meter 192" square	66.50

SQUALO TREE

Design a complete multi band antenna system to meet your own requirements. Squalos can be mounted one above the other or above existing beams on a single mast. The Squalo tree is a horizontally polarized, omni-directional system in any combination of the 6 through 40 meter amateur bands. The Squalo tree takes a minimum amount of space, and does not require extra radials, ground wires, or rotators common to most multi band systems.

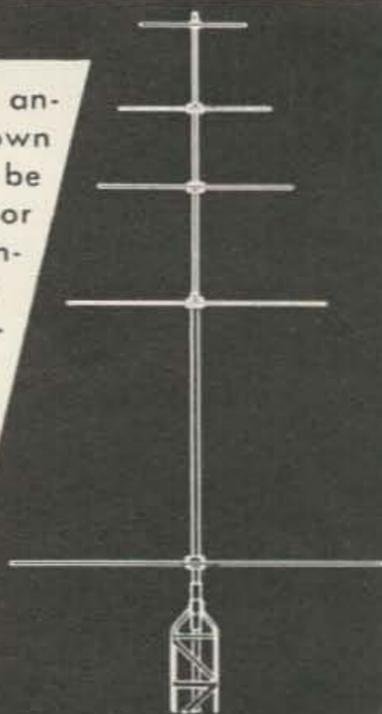

BUY FROM YOUR DISTRIBUTOR
OR WRITE FOR FREE CATALOG

Cush Craft

#65

621 HAYWARD ST.

MANCHESTER N. H.

73

Magazine

Wayne Green W2NSD/1

Editor & Publisher

Paul Franson WA4HWH/1

Assistant Editor

April, 1965

Vol. XXX, No. 1

Europe on Two?	W7SMC/6	3
Get ready for Oscar III.		
Letter from Gus	W4BPD/AC5H	4
Beginning 73's monthly letter from the DX King.		
1 KW PEP	W9EWL/Ø	6
811's in a small box.		
6 Meter Heterodyne VFO Transmitter	K1CLL	10
A simple, stable, easy-to-build transmitter from Bill.		
Kostless Keyer	W8MQW	14
Well, maybe not kostless, but klose to it.		
Double Hula	K2ICF/6	16
A small new antenna. Looks like a halo, but good for HF.		
Propagation	Nelson	20
Looks like an interesting month		
Special SSB Transceiver Section		22
All the dope on all the HF SSB transceivers.		
IoAR News	WA4PDX	32
What's new with the Institute.		
Versatile Code Monitor	W8GXU	34
Transistorized with p.c. board, yet.		
432 mc Noise Generator	W6GXN	38
So you think <i>your</i> converter has a noise figure of 3 db?		
KWS-1 on VHF	W4API	44
It adapts easily for use with transmitting converters.		
Amateur, Spare that Meter	W8BPY	48
And a chuckle with K3SUK.		
Transistor RF Power Amplifier Design	WA2DJU	52
This month's technical article is a first in the ham field		
Some Worthwhile Seneca Modifications	K6VNT	56
To improve its fine performance.		
Two Meter Low Noise Transistor Converter Rohde		62
From our European correspondent.		
A Novel AFSK Oscillator	K8ERV	66
For the VHF RTTY'er.		
Signal Generator for VHF and UHF	K1CLL	70
You'll have to turn to page 70 for the real title.		
Converted Converter	W3ZPJ	74
Turn that old converter into a receiver.		
73 Tests the Galaxy V	W2NSD/1	78
And is happy with it.		
Unusual Philological Diversion	K2PIJ	80
Sometimes known by other names.		
Caveat Emptor?		92
Send in your ad now. CE works!		

73's Advertising Rates

2 pages	\$520	12 times*	\$456**
1 page	268	6-11 times*	236**
1/2 page	138		122
1/4 page	71		63
1/8 page	37		33
1/16 page	20		18

Add fractional page prices for sizes not listed.
 $\frac{3}{8}$ p = $\frac{1}{4}$ p + $\frac{1}{8}$ p.
 *We must have a written contract for frequency discount.
 **No extra charge for second color for full page ads on contract.
 Second color (usually red, but our choice) . . . \$25 per page or fraction.
 Half or full page bleeds are 10% extra.
 No special positions can be promised for color pages.

73 Magazine is published monthly by 73, Inc., Peterborough, N. H. The phone number is 603-924-3873. Subscription rates \$4.00 per year, \$7.00 for two years, \$10 for three years world wide. Second class postage is paid at Peterborough, New Hampshire and at additional mailing offices. Printed in the U.S.A. Entire contents copyright 1965 by 73, Inc. Postmaster: please send form 3579 to 73 Magazine, Peterborough, New Hampshire. Read Gus (p. 4) and CE (p. 92), not this fine print.

De W2NSD/1	2	Marsy SB-33	46
KWM-1 on LSB	45	New Products	55
High Power Swan 240	46	Letters	64, 82



de W2NSD/1

never say die

OK fellows, I've got you right where I want you. While I've been pot shooting away at the ARRL from up here in the wilds of New Hampshire from my lofty perch on 73 Mountain, my cohorts have been busy making arrangements for me to step in and take over the League and run amateur radio as my own personal empire.

My man on the ARRL Executive Committee has thrown dust in the other eyes . . . a simple matter, really . . . and that detested Article 12 of the ARRL Articles of Association has been thrown out the window. I thought we might have a battle getting it dumped, but there was nothing to it. I sat up here telling them how awful it would be to have Dannals on the Board of Directors and they went ahead and moved heaven and earth and got him on.

Article 12? Oh, that was that old hangover from the early days of ham radio when everyone worried that someone would use the League for commercial purposes.

Article 12 states: "No person shall be eligible for the office of Director, Vice-Director or President who is commercially engaged in the manufacture, sale or rental of radio apparatus capable of being used in radio communication or commercially engaged in the publication of radio literature intended in whole or in part for consumption by radio amateurs."

So I had to wait until they threw that one out before I could announce for Director, and scheme my way, with some inside help, onto the Executive Committee. He, he.

Article 12 stood in the way of Dannals being accepted, so Article 12 got the axe instead of Dannals. Now, as seems absolutely certain, if the Board of Directors seats Dannals as the Hudson Division Director at the May Board meeting, the rule will have been completely bypassed. Dannals, you see, works for Sperry Gyroscope at Lake Success, New York. According to the Electronic Engineer's Master, Sperry makes the following radio apparatus capable of being used in radio communication: Aircraft

communications systems, airport traffic control systems, microwave communications systems, telemetering systems, microwave transmitters, radar transmitters, telemetry transmitters, VLF UHF and VHF transmitters, beacon, command, direction finding, interrogation loran microwave and UHF/VHF receivers. Obviously Dannals is intimately engaged in the specific activity that is prohibited by Article 12 OK, so the Directors have a choice of throwing out either Dannals or Article 12. How about that Vice-Director, Stan Zak K2SJO? Well Stan works for Madam Bell, that ubiquitous gal who is even more involved in manufacturing, sale and rental of radio communication equipment than Sperry. With over 7% of the Hudson Division members of the League dropping out last year, perhaps they don't need any representation anyway.

K6BX Really Does It

For some months now I have been devoting quite a few spare moments to a compilation of facts which are under the working title of the "ARRL Black Paper." This accumulation of data, letters, bulletins, statements, etc., all document in considerable detail events which the League headquarters is trying desperately to keep secret. Few amateurs realize the extent that the ARRL is ruled by commercial interests, for instance.

So along comes a twenty-two page exposé of ARRL management from Clif Evans K6BX that makes my effort look puny. Clif, in his usually pungent style, quotes at length from confidential letters written by directors to other directors and assistant directors, exposing plots and events that would be considered completely unbelievable if they were not thoroughly documented. This is an incredible tale of corruption and callous disregard for the ARRL membership that will shake the League to its core.

Frankly, I would like to print some of the material here so you could see the fantastic extent that things have gone, but Clif has the

Continued on p. 86.

Europe on Two?

Oscar III will make a number of firsts possible. Will a trans-Atlantic QSO in the 2-meter band be one of them? There is a chance that this will be possible with the help of this amateur Telstar.

When Oscar's I and II were in orbit, their altitudes were about 250 and 270 miles, respectively, and they were heard by tracking stations at distances of more than 1000 miles. If they had been repeating satellites, contacts would have been possible between stations more than 2000 miles apart; how much more difficult to estimate. Analysis of observation reports on Oscar's I and II shows that Oscar I was heard by stations on the east and west coasts at the same instant, giving a range of about 2200 miles.

How does this make trans-Atlantic 2-meter contacts possible? The range prediction for Oscar III, more than 2000 miles, is based on the Oscar's I and II observation reports, and on the assumption that the altitude of the Oscar III orbit will be similar to the altitudes of the Oscar's I and II orbits. These represent near minimum altitudes, since a satellite placed in a lower orbit would not remain there long. Oscar II, with an apogee of 249 miles, reentered the earth's atmosphere before completing 300 orbits.

Obviously more altitude will be necessary to enable contacts between the U. S. and Europe, but not much more, since the distance from New England to Great Britain is between 2500 and 3000 miles. A 300-mile high orbit would do it. If the Oscar III orbit is higher than those of its predecessors, or if the Oscar III orbit is similar in altitude to the Oscar's I and II orbits but more elliptical, trans-Atlantic contacts should be possible.

The contacts would be at extreme range and so would be short, probably similar to

meteor scatter contacts, lasting perhaps a minute or so at a guess. Prearranged schedules would be a necessity for contacts, but anyone monitoring the satellite output frequencies might be able to hear a European or two, most likely in England, Scotland, or Ireland.

A kilowatt would be helpful, as would a good antenna mounted high with a good view of the Atlantic horizon. The antenna need only rotate in azimuth, as the satellite will be travelling along the horizon.

The Oscar III frequencies are as follows: input pass band 144.075 to 144.125 mc, output pass band 145.875 to 145.925 mc, telemetry transmitter output 145.85 mc, and the coherent beacon output 145.95 mc. Frequency inversion takes place within the satellite, so a signal at the low end of the input pass band will come out at the high end of the output pass band. A signal entering the satellite at 144.080 mc would come out at 145.920 mc, and so on. Also, due to the frequency inversion, signals passing through the satellite will have their sidebands reversed. Upper-sideband SSB will come out as lower sideband, and RTTY signals would have their mark and space frequencies reversed when using frequency-shift keying.

To determine when Oscar III will be in common view of an English and a U. S. station, see the article on an orbit predictor in the March issue of 73. As a line between the two stations becomes more perpendicular to the path of the satellite track across the surface of the earth, the possible length of contact will increase.

No-one can promise that trans-Atlantic contacts will take place, but the possibility is there. Will you be the first to work Europe on 2 meters?

. . . W7SMC/6

ROHN sets the standard

for
**CRANK-UP
TOWERS**

Why settle
for less
than the best?



K7ASK

TWO CATEGORIES TO CHOOSE FROM

Standard Duty Guyed in
Heights of 37 - 54 - 88 - 105
and 122 feet

Heavy Duty Self Supporting
and Guyed in Heights of
37 - 54 feet (SS)
71 - 88 feet (guyed)

ROHN has these 6 IMPORTANT POINTS:

Ease of Operation—roller guides between sections assure easy, safe, friction-free raising and lowering. **Strength**—welded tubular steel sections overlap 3 feet at maximum height for extra sturdiness and strength. Unique ROHN raising procedure **raises all sections together**—uniformly with an equal section overlap at all heights! **Versatility**—designed to support the largest antennae with complete safety and assurance at any height desired! **Simple Installation**—install it yourself—use either flat base or special tilting base (illustrated above) depending on your needs. **Rated and Tested**—entire line engineered so you can get exactly the right size and properly rated tower for your antenna. The ROHN line of towers is complete. **Zinc Galvanized**—hot dipped galvanizing a standard—not an extra—with all ROHN towers! Prices start at less than \$100.

SEND FOR ROHN TOWER HANDBOOK

—\$1.25 Value

—ONLY \$100 postpaid (special to readers of this magazine). Nearest source of supply sent on request. Representatives world-wide to serve you. Write today to:



ROHN Manufacturing Co.

P. O. Box 2000

Peoria, Illinois

"World's Largest EXCLUSIVE Manufacturer of Towers; designers, engineers, and installers of complete communication tower systems."

Letter from Gus

Feb. 5, 1965
Dechencholing, Bhutan

I suppose many of the DX gang has been wondering about why I did not show up in AC land before now. Well that's a story all by itself. You ask anyone who ever tried to get that all important "Innerline Permit." About all I can say is this was the toughest one that I have ever tackled. Peggy and I were at the point of leaving Calcutta any number of times because it was really touch and go all the way, even though things I thought had been pretty well fixed a long time before we left the U.S.A. In fact I thought they were all OK even before I departed from here early last Spring. Well many things have been happening in this section of the world, and many of these things have a strong tendency to not encourage permits to be issued to visitors, even though I had been here before and had made good friends with many of the high officials. It's a very long story, much too long to tell in a few words. Eventually I hope to get around to the whole works.

Well we arrived at Phuntscholing, Bhutan on the 21st. of Jan. with no equipment. My equipment was due to arrive from N. Y. on about the 27th. To this day it is still not here. We departed from Phuntscholing, Bhutan for here on Feb. 1st. We arrived here on the 2nd. Boy, my wife Peggy almost had a fit on that mountain road. If you can picture a narrow unpaved mountain road that's only 127 miles, that takes 2 days to cover you may have some idea of what she went through even though she had taken 2 tranquilizers, aspirins, and a few other nerve controlling medicines. When you leave Phuntscholing you go about one city block and "Slam Bang" you are in the mountains. The road starts by going uphill, with hair pin curves about every 100 feet, and it just keeps on going up and up and up, with the sheer drop offs getting deeper all the time. Every time I have made this trip it seems to give me another thrill and I have now made it 7 times. I am on the air with AC5PN's transceiver which will tune just 2 kc from my operating frequency. I am expecting my good equipment anytime now.

Tell the fellows to call me very close to my frequency, call down the band but not over 3 kc at the most. I will indicate when to call me further than this. Will be on 7 mc and 3.5 mc in a few days with a good antenna. Boy the band sure is stinko. But it's still W3CRA S8 when the other fellows are at the best S4 or 5. It has been Long Path from 1145 to 1330 GMT. No W6's or 7's yet at all. I am really going to work on my antenna and try to get a better signal. I am surrounded by mountains, being in the middle of the Thimphu Valley. Long path looks good so far. Trying 0100 to 0300 GMT—also but no soap yet. Two VE8's only.

. . . Gus

Gus' Travels and Tribulations

This is the first installment on Gus' current activities. We hope, mail service permitting, to have a letter every month from Gus telling what he is hearing and what is going on in the DX world. In addition to this letter we will start next month with a regular series of articles on Gus' adventures. 73, the new DX magazine.

INTERNATIONAL FREQUENCY METERS


 *designed for servicing!*

Equip your lab or service bench with the finest . . .
Discover new operating convenience.

FM-5000 FREQUENCY METER 25 MC to 470 MC

The FM-5000 is a beat frequency measuring device incorporating a transistor counter circuit, low RF output for receiver checking, transmitter keying circuit, audio oscillator, self contained batteries, plug-in oscillators with heating circuits covering frequencies from 100 kc to 60 mc. Stability: $\pm .00025\%$ $+85^{\circ}$ to $+95^{\circ}$ F, $\pm .0005\%$ $+50^{\circ}$ to $+100^{\circ}$ F, $\pm .001\%$ $+32^{\circ}$ to $+120^{\circ}$ F. A separate oscillator (FO-2410) housing 24 crystals and a heater circuit is available. Dimensions: FM-5000, 10" x 8" x 7 1/2".

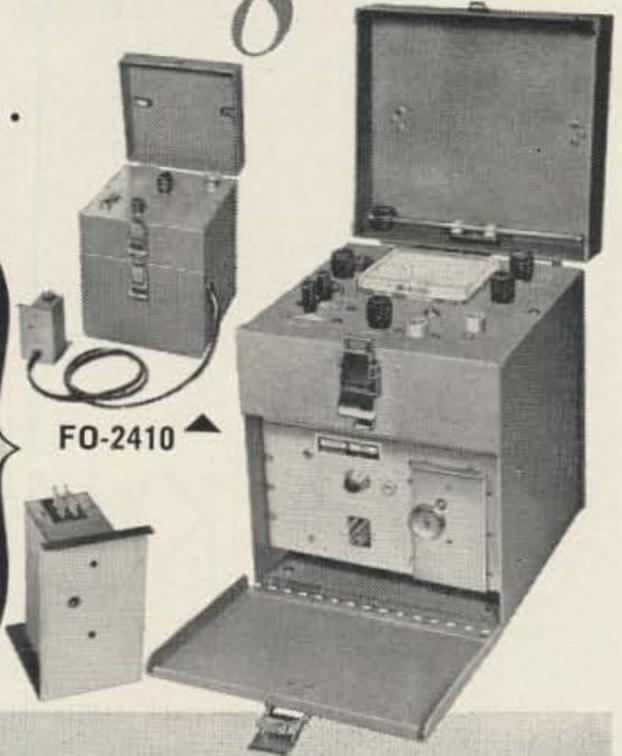FM-5000 with batteries, accessories and complete instruction manual, less oscillators, and crystals. Shipping weight: 18 lbs. Cat. No. 620-103 . . . \$375.00
 Plug-in oscillators with crystal \$16.00 to \$50.00



FO-2410

C-12B FREQUENCY METER For Citizens Band Servicing

This extremely portable secondary frequency standard is a self contained unit for servicing radio transmitters and receivers used in the 27 mc Citizens Band. The meter is capable of holding 24 crystals and comes with 23 crystals installed. The 23 crystals cover Channel 1 through 23. The frequency stability of the C-12B is $\pm .0025\%$ 32° to 125° F, $.0015\%$ 50° to 100° F. Other features include a transistorized frequency counter circuit, AM percentage modulation checker and power output meter.


C-12B complete with PK (pick-off) box, dummy load and connecting cable, crystals and batteries. Shipping weight: 9 lbs. Cat. No. 620-101 . . . \$300.00



C-12 CRYSTAL CONTROLLED ALIGNMENT OSCILLATOR

The International C-12 alignment oscillator provides a standard for alignment of IF and RF circuits 200 kc to 60 mc. It makes the 12 most used frequencies instantly available through 12 crystal positions 200 kc to 15,000 kc. Special oscillators are available for use at the higher frequencies to 60 mc. Maximum output .6 volt. Power requirements: 115 vac.

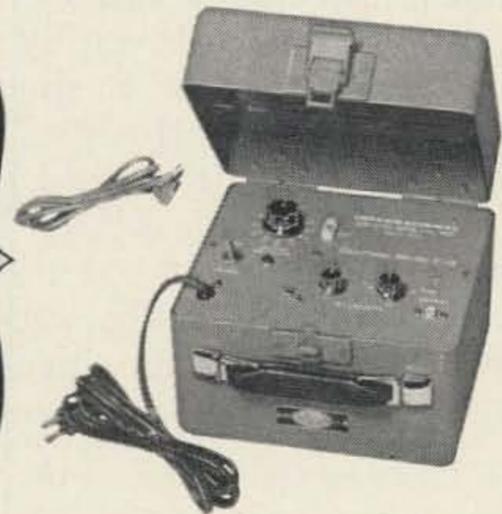C-12 complete, but less crystals. Shipping weight: 9 lbs. Cat. No. 620-100 . . \$69.50



C-12M FREQUENCY METER For Marine Band Servicing

The International C-12M is a portable secondary standard for servicing radio transmitters and receivers used in the 2 mc to 15 mc range. The meter has sockets for 24 crystals. The frequency stability is $\pm .0025\%$ 32° to 125° F, $\pm .0015\%$ 50° to 100° F. The C-12M has a built-in transistorized frequency counter circuit, AM percentage modulation checker and modulation carrier and relative percentage field strength.


C-12M complete with PK (pick-off) box and connecting cable, batteries, but less crystals. Shipping weight: 9 lbs. Cat. No. 620-104 . . . \$235.00
 Crystals for C-12M (specify frequency) \$5.00 ea.



KEEPING YOU ON FREQUENCY IS OUR BUSINESS...



18 NORTH LEE OKLAHOMA CITY, OKLAHOMA

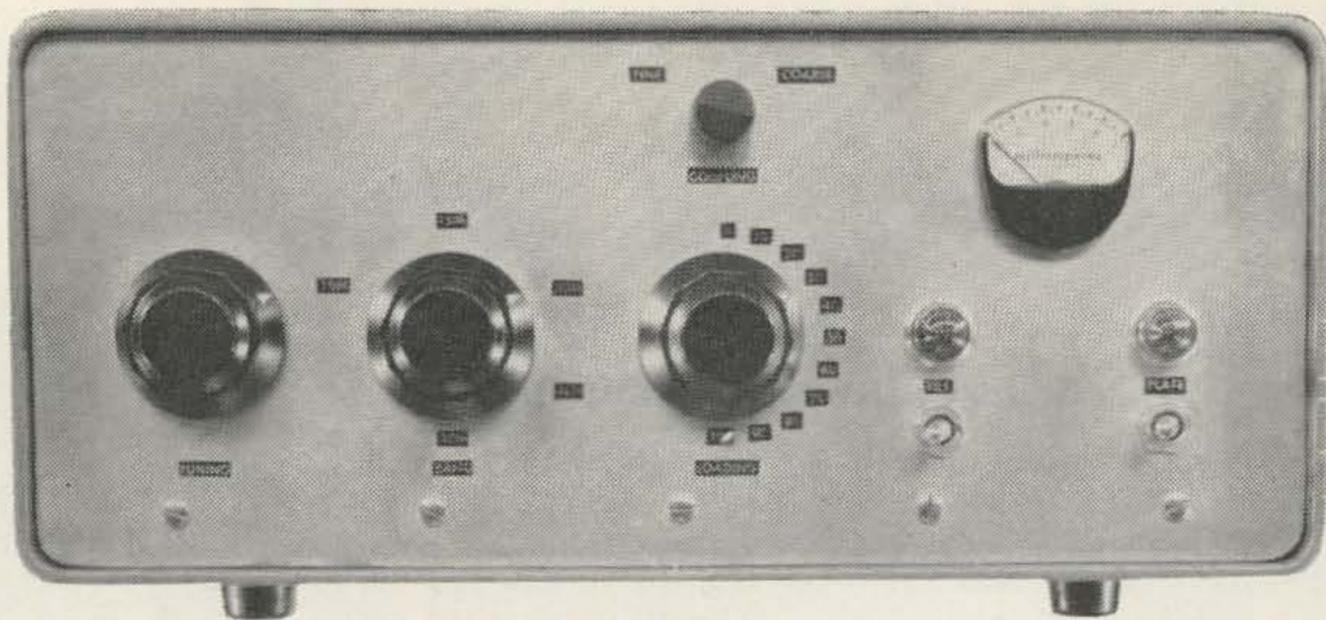

1 KW PEP


Whit Daily W9EWL/Ø
4411 Forest Park Blvd
St. Louis 8, Missouri

In an amazingly short number of years, the emphasis on amateur radio gear has changed from "the bigger the better" to "let's have it neat and compact as possible." This amplifier was designed primarily to be used with one of the many fine transceivers on the market today. For this use, we felt that certain requirements were definitely in order: 1. The amplifier should be small and neat in appearance so as not to disrupt the order of the household. 2. It should be easily driven by and compatible with the transceiver. 3. It should run enough power to make it worthwhile. 4. It should be bandswitching. 5. It should be inexpensive and practical to build. 6. Last but not least, it should be challenging but not impossible to build. This amplifier is the size of the SR-150; is driven to full output with about 30 watts;


runs 500 watts DC input (that's 1000 watts PEP); is fully bandswitching; uses common parts; has a total cost under 100 dollars; and is certainly not beyond the scope of the average builder with a little ingenuity.

The adequate driving power of most transceivers suggests grounded grid operation. The 811A is a proven favorite and it has established a reputation as a lot of tube for the money. The B&W tapped coil was chosen because it is compact, relatively inexpensive, provides an acceptable Q on all bands, and is a very easy way around the problem of bandswitching. One could use a roller inductor coil, but this necessitates the need for a counter dial. However, the nice thing about using the roller inductor is that L-C ratios can be juggled to have optimum operating efficiency on each band.


The loading condenser is a five gang, 425 pf per section variable condenser that was obtained at the local surplus house. This condenser has been advertised by many of the surplus houses across the nation and should not be difficult to obtain. Three gang broadcast variables are readily available from any supply house and could be used, but some loading flexibility would be sacrificed. The five gang variable is set up in such a way as to provide using two sections alone or a total of five sections after switching in the other three sections when more output capacitance is required. This gives a tunable capacitance range of 850 or 2125 pfd and eliminates the need for messy switchable capacitors. A B&W FC-15 filament choke is used to isolate the filament transformer so that the driving power is applied directly to the filaments (cathode)

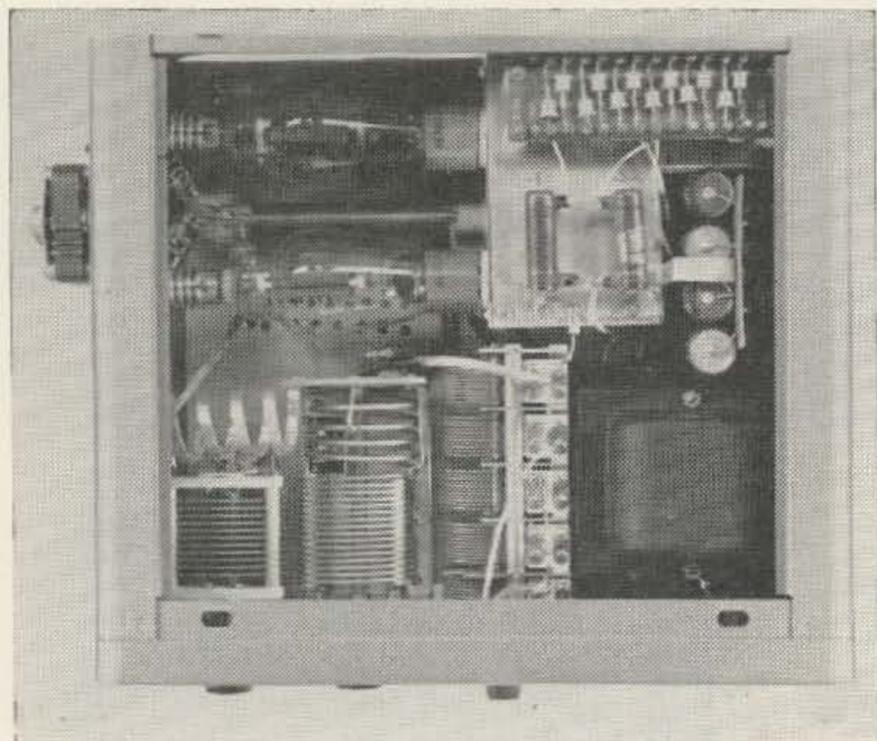

Top view of Small Fry.

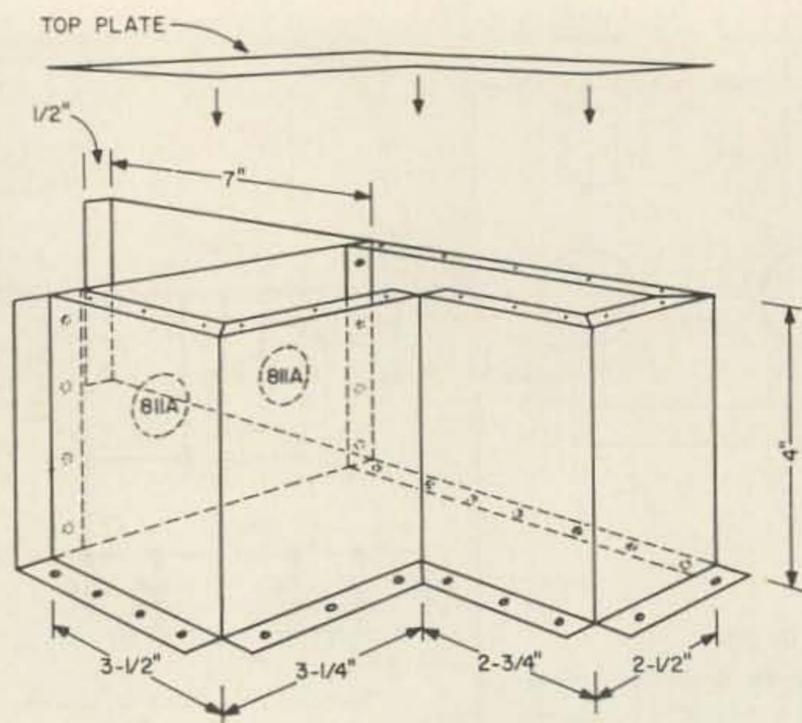

Construction of shield box.

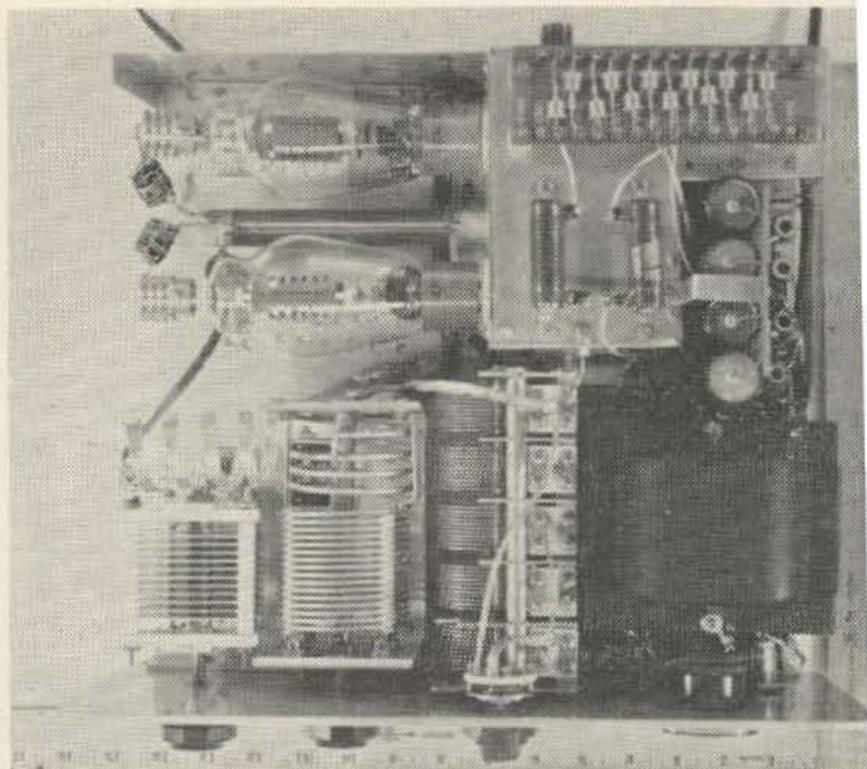

Top view of a cabinet.

certain size box and then try to cram everything into it. The cabinet used in this instance was the same as that used to house the Hallcrafters SR-150. It should be no problem to have a good sheet metal man construct a cabinet from light weight steel or to build a cabinet using Reynolds' $\frac{3}{4}$ " angle stock and do-it-yourself perforated aluminum. Styling is up to you.

The front panel and the chassis plate were cut from $\frac{3}{16}$ " aluminum plate stock. Standard $\frac{3}{8}$ " aluminum panel available in any supply house should be fine though. The front panel and the bottom plate are mated with a piece of $\frac{3}{4}$ " aluminum angle. It was surprising, but more than adequate strength was present in this instance without the use of side braces.

The initial problem of shielding the grid and filament circuit was solved by the sheet metal man down the street (at a cost of \$2.50). The L shaped box was constructed of light sheet aluminum as shown in the drawing. This box is mounted to the bottom plate with $\frac{1}{4}$ "-6/32 screws tapped into the bottom plate.

At this point, may it be noted that instead of using nuts on the mounting screws, the holes in the bottom plate were tapped with a 6-32 or 8-32 tap so that protruding nuts on the bottom would not prevent the assembly from easily sliding into the cabinet.

This L shaped box provides just enough room for the filament choke, the filament transformer and the tube sockets. The leads from the filament transformer (AC primary, pilot light, and center-tap) are passed through rubber grommets on the side facing the power transformer. The coax connector for the input to the amplifier is mounted on the back side of the box. The grids of the 811A's are directly grounded by bending the pin down and

soldering to the frame of the tube socket. The box is flanged as noted, and an aluminum plate is fastened to this flange by small $\frac{1}{4}$ " meta screws to complete the top.

The power transformer is mounted directly in front of this L-box using two lengths of 8-32 threaded stock through the core to the bottom plate. By using the L shaped custom aluminum box, we have a cutout just large enough to hold the four electrolytic condensers and their equalizing resistors that have previously been mounted on a $3\frac{1}{2}$ " \times $5\frac{1}{2}$ " \times $\frac{1}{16}$ " phenolic board. The resistors are mounted on the phenolic board facing the outside in order that they might have adequate ventilation. This condenser-resistor assembly is mounted by using a small piece of aluminum angle to the bottom plate and is braced at the top by a small $\frac{3}{8}$ " aluminum strap connected to the L-box. There is just enough room between the power transformer and the front panel to provide space for the filament and plate switches, the pilot lights, and the plate meter.

The top plate on the L shaped aluminum box is used for the mounting of the surge resistors and the bank of silicon diodes. A piece of $\frac{1}{16}$ " phenolic board is again used with the diodes mounted on the top side and the 470K ohm equalizing resistors and the .01mfd capacitors mounted on the underside. This assembly is mounted on four one inch porcelain standoff insulators. The 811A's are mounted horizontally as shown in the photograph with the plate choke mounted horizontally and somewhat below the tubes. The blocking capacitor is mounted on a porcelain insulator that is fastened to the bottom plate. The tuning condenser, plate coil, and loading condenser are mounted side by side as shown in the photograph. The two condensers are mounted

aluminum spacers in order that the shafts will all be at the same level. There is just enough room directly above the loading condenser to mount the ceramic switch for switching the ganged sections of the loading condenser. Copper strap (actually the outside shield of RG-59U coax pressed flat) is used to connect the plate tuning components together.

A short piece of RG8U coax is used to connect the coax connector on the back aluminum plate to the B&W coil. This runs close to the bottom plate and under the tubes and RF choke.

A small phonograph motor with a three inch fan blade is mounted on the cabinet and blows directly on the tops of the 811A's to provide ventilation and cooling. A series of 1/4" holes are drilled into the bottom plate directly under the tubes to provide for additional airflow. Heat dissipating type connectors are also used to help keep the tubes cool.

Check for parasitic oscillations on twenty and fifteen meters. We finally wound up with five turns of #16 enamel wire around two 100 ohm 2 watt resistors in parallel for parasitic chokes in the 811A plate leads. One may have to experiment with the number of turns on the resistors but the least number that one can get by with is best. This amplifier is certainly wild without the chokes in the plate leads though.

The static plate current for the 811A's under these conditions is approximately 60 ma. The amplifier should be loaded as heavily as possible into the antenna and then talked up to 300 to 350 ma plate current wise which is the optimum full load operating condition. Plate meter readings are sometimes confusing but are not much good for tuning purposes. It is suggested that an SWR bridge or output meter be used for tuning and everything tuned for maximum output.

In using the amplifier with a transceiver, a transfer switch is needed. We used an old DPDT relay with ceramic insulation and about 10 amp contacts. This is mounted in a small mud mini-box and the coaxial leads brought out directly to coax connectors that connect to the transceiver, the amplifier, and the antenna or SWR bridge. We have encountered no difficulty with this lashup and it works fine. We would have liked to mount the relay in the panel but there just was not room. The amplifier has been in use for a couple of months, is very adequately driven by the SB-33 and has given a good account for itself on all bands. We have even given up on perhaps seeing the little silicon diodes go up in a whiff of smoke!

... W9EWL/Ø

send for New FREE

CRYSTAL
CATALOG

... with New
TRANSISTOR
OSCILLATOR
CIRCUITS

3 BIG MODERN PLANTS
TO SERVE YOU BETTER

2 in Fort Myers

1 in Los Angeles



HERMETICALLY SEALED
PRECISION GROUND
CUSTOM-MADE
NON-OVEN CRYSTALS

Top performance assured with quality controlled throughout manufacture. Gold or silver plating acts as electrodes. Crystals are spring mounted and sealed under vacuum or filled with inert gas. Very high frequency stability. Max. current capacity is 10 milliwatts—5 for overtone type. Conformity to military specifications guaranteed.

1000KC to 1600KC (Fund. Freq.)	Prices on Request
1601KC to 2000KC (Fund. Freq.)	\$5.00 ea.
2001KC to 2500KC (Fund. Freq.)	4.00 ea.
2501KC to 5000KC (Fund. Freq.)	3.50 ea.
5001KC to 7000KC (Fund. Freq.)	3.90 ea.
7001KC to 10,000KC (Fund. Freq.)	3.25 ea.
10,001KC to 15,000KC (Fund. Freq.)	3.75 ea.
15MC to 20MC (Fund. Freq.)	5.00 ea.

OVERTONE CRYSTALS

15MC to 30MC Third Overtone	\$3.85 ea.
30MC to 40MC Third Overtone	4.10 ea.
40MC to 65MC Third or Fifth Overtone	4.50 ea.
65MC to 100MC Fifth Overtone	6.00 ea.

DRAKE 2-B Receiver Crystals\$4.00
(All Channels—Order by Freq.)

OVEN-TYPE CRYSTALS

For Motorola, GE, Gonset, Bendix, etc.

Add \$2.00 per crystal to above prices

SUB-MINIATURE PRICES slightly higher


CITIZEN BAND Class "D" Crystals\$2.95
Over 50,000 CB crystals in stock for all sets and channels, both HC6/U and miniature types. To insure proper correlation and correct freq. operation, order by manufacturer model number and channel.

NOW . . . 48 HOUR SHIPMENT

ALL TEXAS CRYSTALS are made to exacting specifications, quality checked, and unconditionally guaranteed!

Send for new Citizen Band Crystal Interchangeability Chart with Texas Crystals Code System.

ORDER FROM CLOSER PLANT

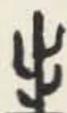

TEXAS CRYSTALS



DEPT. 73-4

1000 Crystal Drive
FORT MYERS, FLORIDA
Phone 813 WE 6-2109

Division of

AND
4117 W. Jefferson Blvd.
LOS ANGELES, CALIF.
Phone 213-731-2258



6 Meter Heterodyne VFO Transmitter

Compactron tubes have many advantages for ham use. They were developed for commercial applications where their main advantage is economy: They are squat tubes with 12 pins, set in an all-glass envelope. Because of the large number of pins, most Compactrons contain more than one unit. For instance, the 6J11 has two completely separate and shielded high gain pentodes, each with a Gm of 14,000. That is high. Compare it with 4300 for the 6BA6! The 6D10 has 1½ 12AT7's in it. That's three good triodes of 2½ watts dissipation each. The 6M11 has two of these (12AT7) triodes and a 14k Gm type 6EW6 as well. In addition, the Compactrons have a large pin circle diameter for more insulation and higher plate voltage. Tube leads are also short and direct for good high frequency performance. You can see the many possibilities for amateur use.

I built a two tube VFO heterodyne transmitter using one Compactron. The final tube is an old 815, but could easily be one of the Compactron power tubes. The most interesting part of the circuit is the heterodyne, or conversion, VFO, where a stable 3 to 4 Mc variable oscillator is added to a 47 Mc crystal oscillator in a mixer. This avoids multiplying the VFO output, so the mixer output on 50 Mc will be very stable as the crystal oscillator can easily be made drift-free.

I started the transmitter with a 6AF11, which has a triode and a 6CX8 in it. This tube is very useful for the heterodyne circuit. As soon as I put the 12 pin socket in *one* hole, wired up *one* filament lead and soldered three cathode tabs to the tube ring, I began to appreciate the economy of labor involved with Compactrons. I checked the various sections of the 6AF11, which has two good triodes and a super-doooper video type pentode with five watt dissipation (almost a 5763). These tube people may be nervous about transistors, but they're not surrendering peacefully.

Those triodes are good! The 47 Mc crystal oscillator starts off with only 8 volts plate voltage. And the pentode section puts out one watt of stable six meter energy even though it is acting as a mixer. All this is one small bottle for \$2.

Now to the details. I used the highest gain triode for the 47 Mc oscillator, since it needs the gain. When I build an oscillator, I always set up a good tuned plate circuit and pick up the least amount of out-of-phase energy possible to the grid. It has always worked well for me. Fig. 1 shows the circuit. Simple, isn't it? L2 is inserted in L1. The coupling may be varied for tests but it is not critical. It is important to keep the plate voltage below 100 volts. You can use a voltage regulator if you like, but I didn't find one necessary.

The Variable Oscillator

Here again, a good plate circuit is set up. After all, it's the plate that generates the power. An airwound coil is used, tuned to 3 to 4 megacycles. There are some who maintain that the plate should be grounded to avoid "heat expansion trouble." They perhaps forget to mention that the plate-grid capacity is still present and would cause frequency shift if the plate did expand with heat. This one is stable, as is.

An air capacitor is used as a parallel pad to set the frequency on the dial. Here also you are interested in a certain amount of power. Don't forget, this is a transmitting circuit. C4 is a Hammarlund MAPC-100 with a screwdriver shaft. C3 is a Hammarlund MAPC-100B with ¼ inch shaft. They are air capacitors so they will not vary with temperature. C5 spreads the frequency out on the dial. The variable frequency control portion may be made a lot more fancy if you like, with slow-motion dial, switching for every half megacycle, etc. I just brought the shaft out with an insulating extender and put a long pointer knob on it.

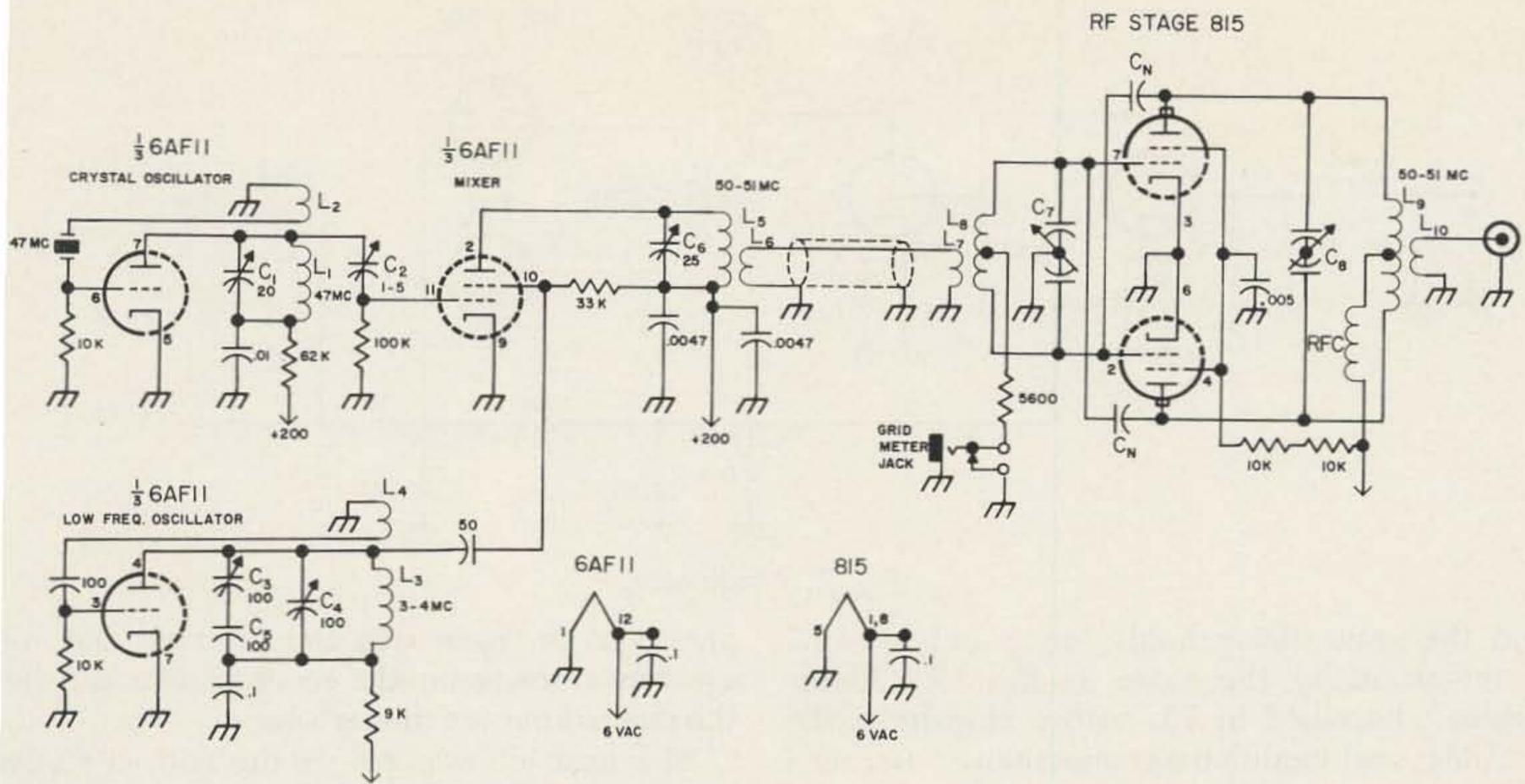


Fig. 1. 6 Meter Heterodyne Transmitter.

- L1. 7 turns airwound, 16 turns per inch $\frac{5}{8}$ in. diameter. B & W 3003, Air Dux 416T.
- L2. 6 turns of plastic covered No. 22, $\frac{1}{4}$ in. O.D., $\frac{3}{8}$ in. long. Inside L1.
- L3. 2 in. of $\frac{1}{2}$ in. dia. 32 turns per in. B & W 3004, Air Dux 432T.
- L4. 15 turns of No. 28 dcc wound on cold end of L5.
- L5. 13 turns airwound 8 tpi.
- L6. 2 turn adjustable link over cold end of L5.
- L7. One turn link near center of L2.

- L8. 4 turns No. 14 enamel, $1\frac{1}{4}$ in. O.D. 1 in. long.
- L9. 6 turns No. 14, $\frac{3}{4}$ in. O.D., $1\frac{1}{2}$ in. long.
- L10. 2 turns near center of L3.
- C1. Hammarlund MAC-20.
- C2. 1-5 pf mica trimmer.
- C3. Hammarlund MAPC-100B. "Tune."
- C4. Hammarlund MAPC-100. "Set."
- C5. 100 pf silver mica.
- C6. Hammarlund MAPC-25B.
- C7. Hammarlund BFC-12.
- C8. Hammarlund BFC-12.

The crystal oscillator is fed into the grid of the pentode mixer through C2, a 1 to 5 pf mica compression capacitor. For adjustment of C2 first open it up and get the crystal oscillator running properly, with a gradual increase in grid current (open the ground end of the grid resistor and put in a milliammeter) on one side of resonance, and an abrupt drop on the other. The presence of the regenerative coil (L2) makes the operation much less critical, as you can check. As you increase the feedback of L2 you will see a greater region of power out and less abrupt drop. C1 should tune to resonance near the middle of the range. With the oscillator running properly, increase C2, putting more power into the mixer grid. Too much C2 will knock out the crystal oscillator and cause self-oscillation of the pentode. It is very stable over the useful range though.

The variable oscillator is coupled into the mixer screen with a 50 pf capacitor. This section worked perfectly right away and has not drifted since. It is very uncritical and very stable.

The mixer plate is simply another good 50 Mc coil, tuned with a Hammarlund MAPC-25B air capacitor. With both oscillators running, 47 Mc and 3 Mc, peaks of energy will be found at 44, 47, and 50 megacycles, the sum and the difference of the two oscillators, and their fundamentals. The 3 Mc fundamental naturally does not show up in a 50 Mc plate circuit. I obtained about one watt out of the plate on 50 Mc. Do not ever use this on the air without at least two more tuned circuits, as the 47 Mc energy is only some 10 db down. Link coupling over to the final grid circuit of an rf amplifier, such as an 815, plus a good plate circuit on the 815, will result in the 47 and 44 Mc energy being way way down.

The RF Stage

Almost any good tube that will put out 25 watts or more and operate on 1 watt input on 50 Mc will do. I used my old favorite, the 815. It neutralizes easily and can be bought for as low as \$1.75 surplus. Fig. 1 shows the circuit. It is quite standard; tunes up easily;

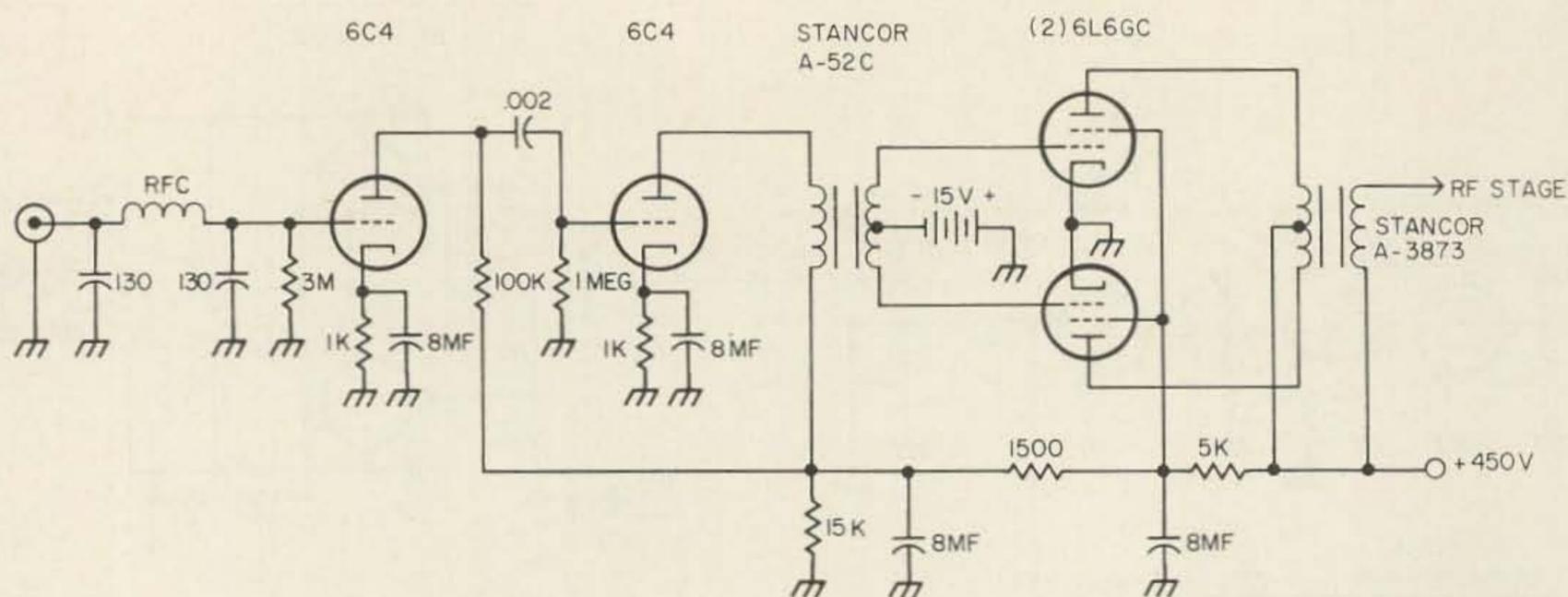


Fig. 2. Modulator.

and the neutralizing holds "once and for all." It is essentially the same as the "Six Meter Linear" described in 73, with a change in the grid bias and modulator connections.

The Modulator

Fig. 2 shows the modulator circuit. It works, and works good enough so that the modulation reports were "better than average," "clear as a bell," and "no trash or hash of any kind."

After getting the 6C4 driver stage running, I put another 6C4 in front and plugged in my low-cost Astatic mike. Immediately, rf feedback. This time I was able to cure it with an rf choke and two 130 pf capacitors between the mike jack and the grid. No feedback at any time since. The two 6C4's just about do the job, but only just. I'm going to put in a 6AT6, which has a much greater amplification factor.

On The Air Tests

This was interesting. I started about 3 pm on a weekday and everything was fine while talking to the student types (it was summer) and retired lads. "No drift," "FB," etc. About 5 p.m. some working type operators began to show up on the band, with more money and thus more selective receivers. Some of these had *sharp* receivers and reported a slight but steady drift. So, off the air again and back to the bench. I checked the variable 3 Mc section. No drift.

I checked the crystal. Drift! Why the crystal oscillator? Well, as I have said many times, these VHF crystals will *not* stand over 100 volts on the plate of the triode. I put my voltmeter on the B-plus and sure enough, 150 volts. My own fault. Increasing the dropping resistor and lowering the volts on the plate to 100 took out the drift nicely and no more drift has been reported since.

For frequency spotting, the 6AF11 power supply is switched on without the final. It

puts a large signal into the receiver, but with a beam antenna on the receiver you can hear the desired carrier through it.

The next job was to get the entire "station" assembled on three shelves with a handle for portability. The top shelf has the conversion VFO, final and the transmit-receive switch. The middle shelf holds the modulator, and down below are the two power supplies. I took it up to 73 Mountain near Peterborough, N.H. for a 6 hour work-out. No drift reported at any time from a number of sharp receivers, and all modulation reports good to excellent.

Conclusion

Some interesting comments were heard. The appearance of a new home-brew rig on the air seems to be a rarity these days. And a for a single tube double-oscillator-converted VFO; well, very few that I talked to had any idea of what it was, even after I explained it. Apparently today the home-brewer type (or rigs, that is) is really scarce. The old division of customers into two distinct classes is becoming sharper. Class 1. Young lads, time on their hands to build, not enough money to buy ready-made gear. Class 2. The working type, busy making money, no time to build. This change over seems to be accompanied by the acquisition of an XYL and numerous junior oscillators I noticed this consistently when building beams, (UHF Resonator Co., Rye N. Y., 1946 to 1950). Class 1 types would ask for dimensions. Class 2 types would send checks for beams. Today with the heavy pressure on a young lad to get his education this deal is accentuated. He doesn't have much money while learning, and he has less time now as well. So maybe some new ideas or low-cost, easy-to-build, circuits, rigs, and beams going from 50 to 1296 megacycles may help. I'm trying anyway. And it's fun too!

... K1CLL

Here is what a Ham thinks about the new 6 meter base station antenna . . .

"I do a lot of 6 meter work since I act as net control for the Michigan, Ohio, Pennsylvania SSB Net and in addition, stations from other midwestern and eastern states check in. My 10 element commercial beam with a 24' boom has met with several accidents due to high winds."

"Recently, I purchased and installed your new Coveya-6 beam antenna. To make a comparison with my previous 10 element beam I went on the air without revealing the change. You'll be glad to know that the results surpassed the performance of 10 element beam and besides, I obtained these additional advantages:

- 1. Better front to back ratio for receiving — at least 25 DB.*
- 2. An improved forward pattern.*
- 3. Much wider coverage of forward pattern on transmit, thus eliminating moving the antenna often.*
- 4. Very low VSWR — 1.1 to 1 across entire band.*
- 5. Completely weatherproofed assembly making weatherproofing spray unnecessary."*

"My greatest satisfaction was the ability of the Coveya-6 to reach out and get the long distance ground wave stations. All comparison checks in the log book were very favorable to the Coveya-6."

Elmer D. Sauers, WA8AUZ, Akron, Ohio

this is just one of numerous favorable comments we received about our COVEYA-"6" see it at your distributors or write for literature

"The Home of Originals" NEW-TRONICS CORPORATION
3455 Vega Avenue Cleveland, Ohio 44113

A Kostless Keyer

All of us at one time or another have had a hankering to own a keyer. Some of us resisted the impulse because the cost outweighed the need. The circuit shown in Fig. 1 is my compromise. Although no claim is made that this keyer will replace a TO keyer, it does make self completing dots and dashes of uniform length at speeds from 9 to 35 wpm. Moreover, aside from the sensitive type relay L, most of the parts can be found in an average junk box.

The theory of operation is based on the fact that good condensers charge very fast. (See Fig. 1.) As the key is closed connecting the common and dot terminals, C_1 charges instantly (almost) to 9 volts, thus applying a charge to the base of T_1 , causing current to flow through T_1 and closing the relay. But then as L closes, the 9 volts across C_1 is disconnected, allowing C_1 to discharge slowly and at a controllable rate across the speed control R_0 . (See Fig. 2.)

Now for practical details. Many transistors were tried for T_1 and T_2 , all with success. For instance, 2N168A and other general purpose types worked. However, if PNP's are

used, the polarity of C_1 , C_2 , and E must be reversed. However, good condensers must be used for C_1 and C_2 , (for instance the Sprague TE 1300 for C_2). As a rough guide, pick 10 to 50 wvdc types, *not* electrolytics. As for the speed control R_0 and R_0' , they must work on the same shaft and can be found surplus for less than .50¢; a distinct improvement would be the use of logarithmic tapers but this is not necessary.

The relay is the only rub. Whatever relay is used, it must have a coil resistance of 6 k to 8.7 k, and a closing current of .6 ma. The upper limit of 35 wpm is due to the slowness of the suggested Advance relay. On the other hand, this slowness provides a pleasing weight to the characters, although a weight control of a 20 k pot across L would be an improvement.

Adjustments of the ratio control and a means of constructing a cheap key are described in the 63 ARRL Handbook, page 253. The current drawn from the battery when the key is closed is at most 1 ma, depending on the speed, and .02 ma when the key is open (battery life is long indeed). As for the choice of dimensions of the box to enclose the Kostless Keyer, I leave that to the builder's taste and steadiness of hand.

... W8MQW


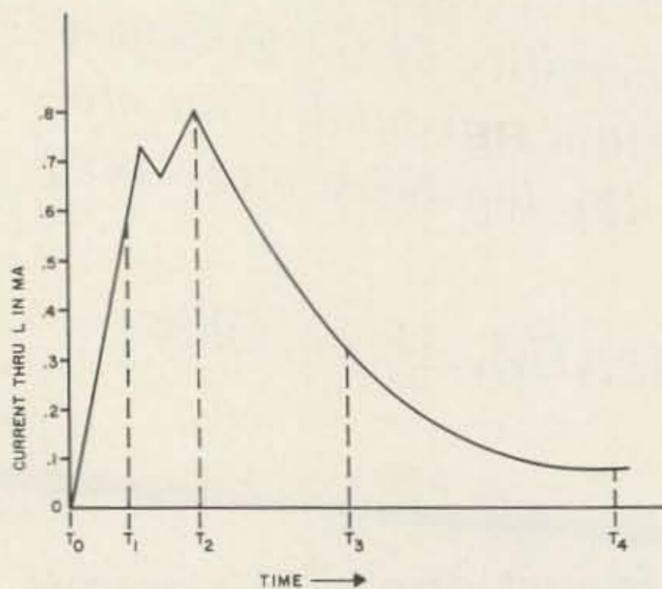


Fig. 2.

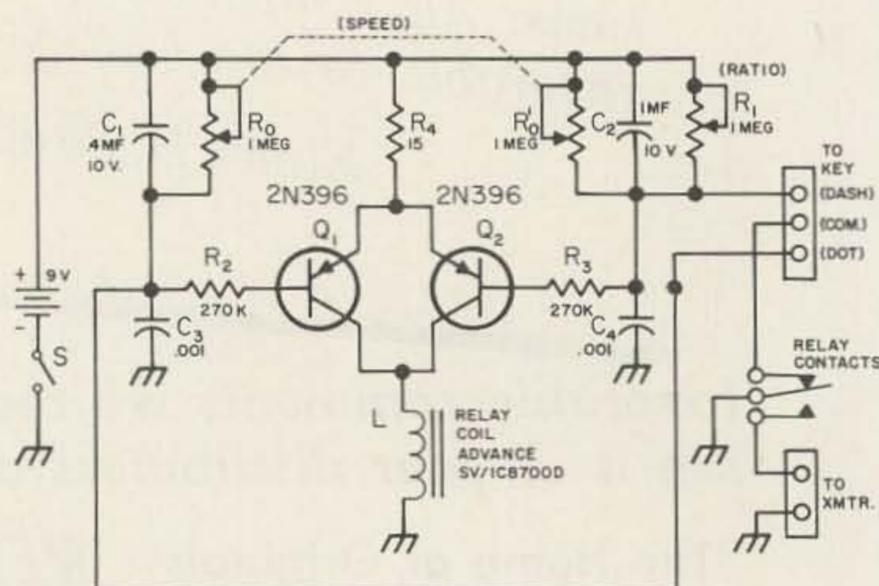- t_0 : key is closed.
- t_1 : attains closing current.
- t_2 : L closes and keys transmitter.
- t_3 : release current, transmitter is off.
- t_4 : relay arm makes contact with open contact and the cycle repeats.



Kostless Keyer.

The accepted standard—Drake TR-3

the complete Sideband Transceiver with

FULL BAND COVERAGE

on both sidebands



\$550.00
AMATEUR NET

FULL FREQUENCY COVERAGE all amateur bands 10 thru 80 mtrs
UPPER and LOWER SIDEBAND on all bands

300 WATTS P.E.P. on SSB

CONTROLLED CARRIER SCREEN MODULATOR for AM built-in

TWO SPECIAL 9 Mc CRYSTAL FILTERS for sideband selection

VOX or PTT

OUTPUT IMPEDANCE ADJUSTABLE with pi-network

SHIFTED CARRIER CW, 260 watts input

LINEAR PERMEABILITY TUNED VFO

SEPARATE RF and AF GAIN CONTROLS

FULL AGC with Drake dual time constant system


2.1 KC PASSBAND

100 KC CRYSTAL CALIBRATOR built-in

SEPARATE RECEIVER S-METER and

TRANSMITTER PLATE AMMETER

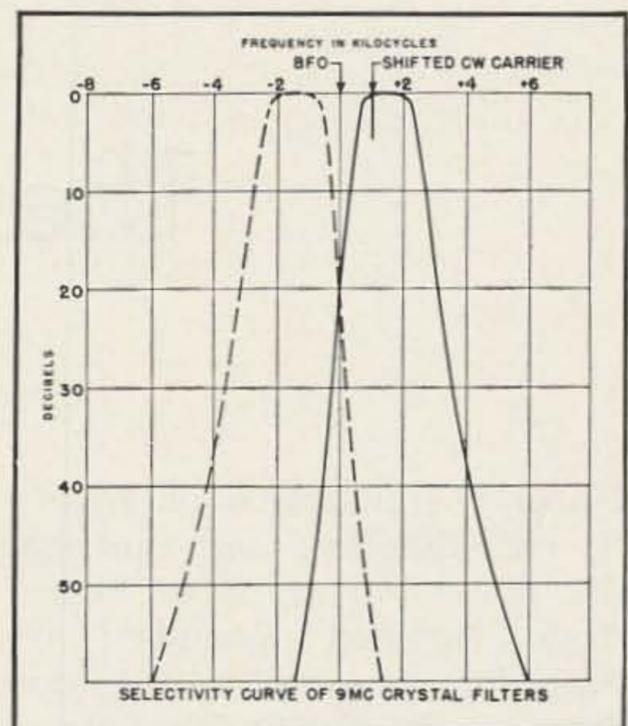ONLY ONE DPDT RELAY USED — RF switching limited to antenna



REMOTE VFO

Model RV-3 . . . \$79.95

MATCHING SPEAKER

Model MS-3 . . . \$19.95


MOBILE MOUNTING KIT

Model MMK-3 . . . \$6.95

POWER SUPPLIES


AC Power Supply Model AC-3 \$79.95

DC Power Supply Model DC-3 \$129.95

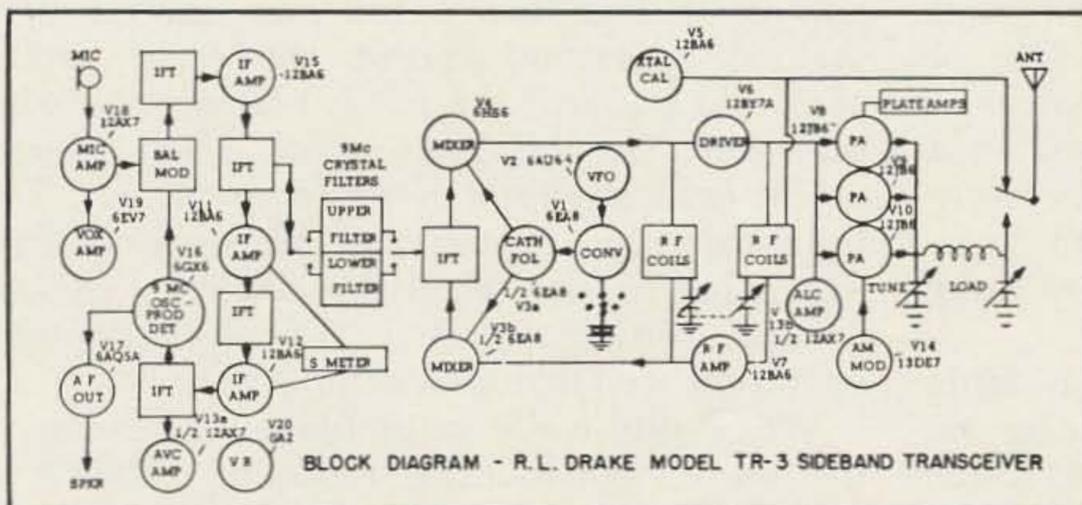

NOTE: A new transceiver model TR-4 will be announced soon. This unit will have all of the TR-3 features, plus a transistorized P.T.O., an AM detector, CW sidetone, semi break-in CW and vox or push-to-talk AM. The amateur net price on the TR-4 will be \$585.00. All TR-3 accessories are usable with the TR-4. For more information, write to:

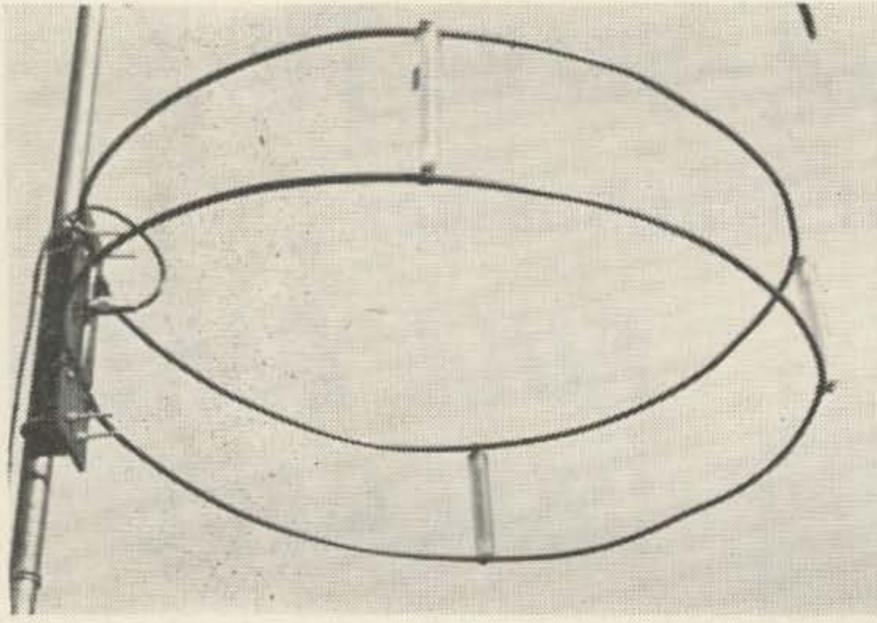R. L. DRAKE COMPANY MIAMISBURG, OHIO, 45342



Peter A. Lovelock K2ICF/6
807 Fourth St.,
Santa Monica, Calif.

The Double Hula

Under the influence of zoning restrictions, TVI, cliff dwelling and unsympathetic landlords, many metropolitan hams have demonstrated frenzied ingenuity in contriving new designs for compact, inconspicuous antennas. Often enough, alas, paying the price of high losses, reduced capture area and low radiation efficiency, resulting in galloping frustration in trying to combat their full sized country cousins on our crowded bands.

A recent commercial innovation that offers remarkable possibilities to the huddled ham masses of suburbia and city is the 'Hula Hoop'. This new concept of radiator has already been introduced in several publications, and is known by the more conservative title of Directional Discontinuity Ring Radiator, a unique vertically polarized antenna utilizing a *horizontal* element mounted at almost zero height above its operating ground. In principle the Hula Hoop functions like a leaky waveguide.

In its originally reported form the Hula Hoop consists of a continuously circular radiating element, the circumference of which is equivalent to a quarter wave at the *highest* operating frequency. The circular element is mounted in a plane parallel to the operating ground-plane. A section of the radiator extends at 90 degrees to the plane of the circle at the driven end to form a short vertical leg, the length of which is shown as 'h' in Fig. 1,

and the length of which is equivalent to the height above ground. The diameter of the hoop may be expressed as 28 electrical degrees at the highest operating frequency, while the vertical leg 'h' is 2.5 degrees. The radiator may be resonated downwards in frequency by increasing the series capacitance 'C' between the terminal end of the element and ground. In practice the Hula Hoop may be tuned over a 2:1 frequency range, permitting two band operation. However efficiency decreases sharply as resonance is lowered.

According to commercial tests the Hula Hoop is capable of radiating a field strength only 3 db less than a full size quarter wave vertical operating against the same ground plane. At one half the normal frequency, when resonated by the appropriate series capacitance, field strength drops as much as 15 db from that by a quarter wave vertical. Even this is not so bad when the efficiency of some 'loaded' verticals used successfully for mobile operation are taken as a comparison.

While physically resembling its cousin the half-wave, horizontally radiating 'Halo', beloved of six meter mobile enthusiasts, the Hula Hoop's functional characteristics are far from similar. The quarter-wave loop, in close physical and electrical relationship to a ground-plane, results in complete cancellation of a horizontally polarized field. The discontinuity effect of the radiating elements circular con-

guration causes it to act as a leaky waveguide' with a highly efficient vertically polarized field.

One published construction article³ describes the application of the Hula Hoop for mobile operation on ten meters or CB band, utilizing the car roof as an effective ground plane. This Hula Hoop is only 27 inches in diameter with height above roof (h) being a mere 3 inches. It is claimed to have outperformed a quarter wave whip mounted on the same vehicle.

For the suburbanite the Hula Hoop brings the opportunity of low-frequency operation on the current 75 and 40 meter DX bands, without having to erect a vertical radiator, the sight and appearance of which will unleash the wrath of neighbors and local officialdom.

Enough real estate is available to accommodate a Hoop diameter of from nine to eighteen feet, supported one to two feet above ground, the surrounding community may not even be aware he has an antenna. Or if they see, will conclude it to be the supporting structure for a plastic swimming pool.

For the compact crowd, the Hula Hoop may well be exploited on the higher frequencies, providing an adequate groundplane is available. Even at 20 meters the hoop diameter is only a paltry 54 inches.

The author's own experiments with a car-top, ten meter prototype were extremely convincing. Half a dozen stations worked on ground-wave reported no discernible difference on their S-meters between the hula and comparison mobile whip. The darn thing works.

But what of the city-dweller without a convenient ground-plane to hook his hula to. Or even his country cousin who wishes to hoist the hula to dizzy heights without compromising compact qualities with bulky ground-plane elements. And let it be understood, on the ground, or in the air, the Hula Hoop requires a highly effective ground-plane, so cast out those slender ground rods and roll out the thick wire, you low-frequency DX'ers.

But wait, there is a solution. At K2ICF fixed location, where it was desired to take the advantage of height for ten meter RACES operation over hilly terrain, top-of-the-mast operation was the dilemma. Then came the blinding inspiration for a ground-planeless Hula-hoop and the Double Hula came into being. Since the conventional Hula-Hoop perched on its vertical leg at height ' h ' above the ground-plane sees a mirror-image of itself in the ground from which it derives its phase-characteristics, why not replace the mirror

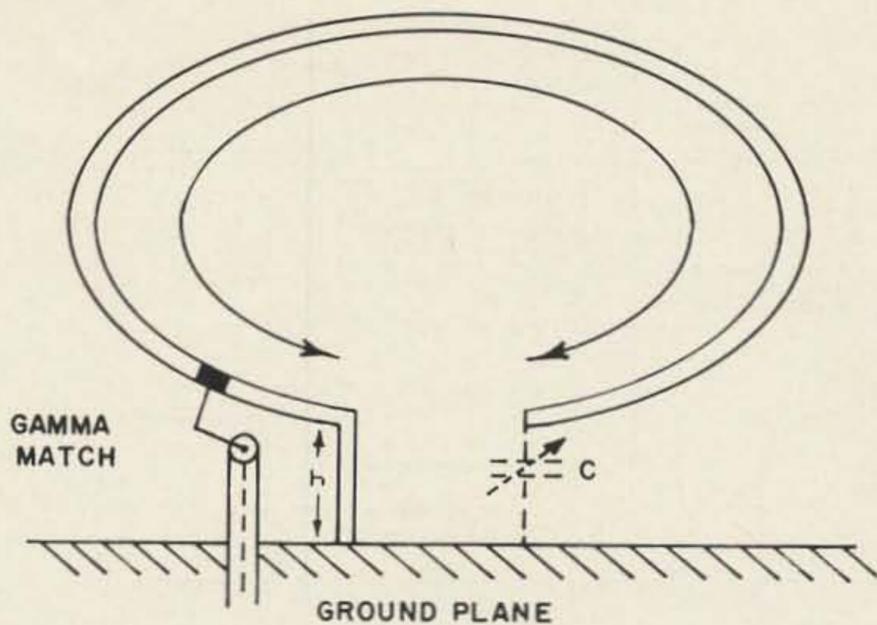


Fig. 1. Total radiator length $L + h = \frac{1}{4}$ wave at highest frequency. $C =$ added resonating capacitor to lower frequency.

image with a physical twin. Why not, in fact, furnish a second Hula Hoop spaced $2h$ below the primary element and electrically connected by a common vertical leg. A doublet Hula?

No time was lost in acquiring a roll of automotive copper tubing $\frac{3}{8}$ inch in diameter, and retiring to the basement to pound this into two parallel hoops spaced 6 inches apart by polystyrene rods. The mounting assembly shown in Fig. 2, was fabricated from a $10'' \times \frac{1}{2}'' \times \frac{1}{4}''$ masonite board, to which the common vertical leg and hoop end were rigidly mounted with clamps made from $\frac{1}{2}''$ copper strip. Variable capacitance was added to the terminal end of each hoop by 3'' lengths of copper strip extended from the mounting clamps adjacent to the vertical leg. The shell of a female coax connector was sweated to the mid-point of the vertical leg, and the center conductor connected by a short length of #14 gauge wire to a copper clamp spaced approximately 4'' along the upper hoop, to provide the required gamma match for the coaxial feedline.

The entire assembly was then wrestled to the roof of the station building (known to other family members as house) and was mounted with the traditional U-clamps to the mid-point of a rugged 12 foot mast that also supports the family TV antenna as shown in the photo.

As was expected the massive bulk of the TV antenna directly above the Double Hula had undesirable results on its radiation pattern, as apparently did the vertical mast extending both above and below the hoops, in the place of radiation. However this initial mounting did permit tune-up and matching adjustments, and close up photographing.

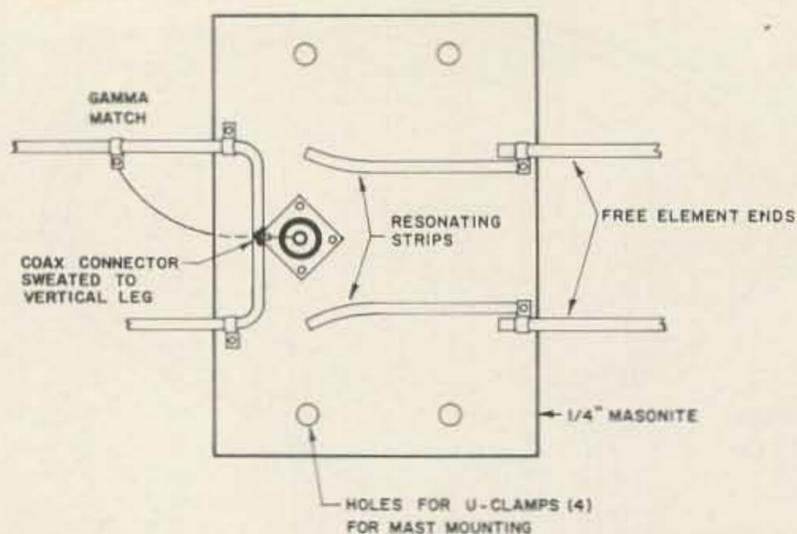


Fig. 2 Double Hula mounting assembly.

The assembly was resonated with a grid-dip meter by varying the proximity of the copper tuning strips to the vertical leg. Final pruning was accomplished by touching up the copper strips, using a long fibreglass rod, to obtain minimum standing wave ratio at the operating frequency of 28.7 mc. When this was accomplished the Gamma Match was adjusted to bring the swr close to 1:1.

Since initial tests indicated the Double Hula wasn't doing so well under its TV umbrella, it was then raised on an auxiliary mast section to a position located some 4 feet above the TV antenna. A recheck showed no significant change in resonance or swr.

But now ground wave signals were heard from New York City and Long Island some 35 miles away, as were strong skip signals from South America. Excellent contacts were had with mobiles at distances up to 40 miles using a ten watt transmitter, and locals reported improvement in signal strength over a commercial tri-band trap vertical mounted on the roof peak.

About this time, came a second blinding flash. If the Double Hula was functioning like a vertical half wave, would it work as a horizontal dipole if its plane was rotated 90 degrees, like a wheel on edge. After a struggle this new orientation was effected. Still no change in resonance or swr, and what's more it worked. Now we had the effect of a 16 ft. horizontal dipole packed into a compact wheel configuration only 27" high and 6" in length. At a pinch it could be made to work on 20 meters. But the equivalent of a 35 foot doublet would only be 54" high and 1 ft. long.

Now suppose we mounted another Double Hula spaced 0.2 wavelengths behind the first could this be phased to act as a parasitic reflector. Visions of a full efficiency 20 meter beam comprising of three sets of 'ear-rings' with a turning radius limited only by boom length danced through my mind. Unfortunately at this juncture the author ran out of time and with none foreseeable in the reasonable future, decided to turn the whole concept over to those of the fraternity who have the freedom of hours to run amuck on roof-tops. At least it had been proved that vertical or horizontal the Double Hula works and offers lots of opportunity for the experimentally minded, as well as practical joy for those who are underprivileged in space.


A few words of caution. Excepting for the basic dimensions of the 10 meter hulas, the author has not attempted to determine exact dimensions for other frequencies, and these should not be critical considering the capability of series capacitance resonance. However length of the circular elements should not exceed a quarter wave at the highest operating frequency desired, or capacitive resonance will not be possible. Height of the vertical leg (h) is approximately 3 inches for 10 and 11 meters and may be multiplied directly for lower ham bands. The Q of the hula is high, and thus the bandwidth somewhat narrow. The Double Hula displayed broader bandwidth, and when resonant at 28.7 mc, could be operated from 28.5 to 29.3 with less than 2:1 swr. The mechanically minded may contrive ways of tuning such antennas remotely for wide frequency coverage.

The 3/8 inch copper tubing used for constructing my Double Hula was found to be reasonably adequate in mechanical strength for several weeks. However there is some doubt to its survival in high winds or ice storms. More rugged material is suggested for permanent use and especially for lower frequency versions.

... K2ICJ

Bibliography

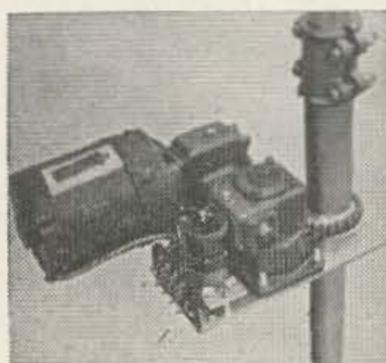1. Electronics, January 11, 1963. "Hula Hoop Antenna's A Coming Trend." J. M. Boyer.
2. R.S.G.B. Bulletin, April, 1963. "Technical Topics A Breakthrough in Verticals?" Pat Hawker, G3VA.
3. Popular Electronics, July, 1963. "The Hula Hoop." Roy E. Pafenberg, W4WKM.



TELREX ROTATOR-INDICATOR SYSTEM MODEL TS250-RIS

Mast Feeds Thru Rotator For Safe, Easier, Installation

- 1300 IN./LBS ROTATION TORQUE
- SELF LOCKING BY STURDY WORM GEARS
- SELSYN AZIMUTH INDICATION
- ACCOMMODATES 2" O.D. MASTING
- MALLEABLE CAST MASTING CLAMP SUPPLIED
- OUTPUT SPEED APPROX. 1 RPM
- WILL FIT INTO OR ONTO A 6" SIDED TOWER

Write for FREE PL65 Describing Rotators and Antennas

A Really Sturdy
ROTATOR-INDICATOR
SYSTEM—
NOT a Modified
TV Rotator!
Designed To
Out-Perform, Outlast!

\$25000
F.O.B.

ALSO:

- TS325-RIS \$325.00
- TS435-RIS \$435.00
- TS535-RIS \$535.00
- TS585-RIS \$585.00

TELREX LABS.
ASBURY PARK, N.J.



Stronger Signals! Stronger Construction!


NEW *Waters* AUTO-MATCH

the Stronger Mobile Antenna

With Waters new AUTO-MATCH, you'll get the signal strength out that's engineered into your modern, compact transceiver. Every precious DB of it! And AUTO-MATCH is built to endure with its stainless steel tapered radiator tip and tough aircraft aluminum mast. It operates on any band with a simple change of top-center loading coils. (Coils are sealed in protective, low-loss Epoxy.) AUTO-MATCH—the permanent solution to your mobile antenna problems!

PRICES


Mast 370-1	\$12.95	Coil 370-20	\$13.45
Radiator Tip 370-2	\$ 9.95	Coil 370-15	\$12.75
Coil 370-75	\$15.95	Coil 370-11	\$11.95
Coil 370-40	\$14.95	Coil 370-10	\$11.95

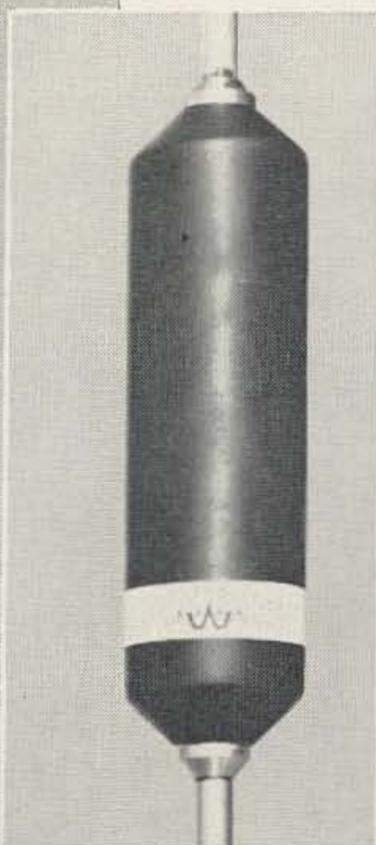

Waters

CODAX — new rhythm-smooth automatic keyer by Waters — never anything like it! Feather-touch double paddle is factory-adjusted for precise gap and tension. Spacing and timing from 5 to 50 WPM is fully automatic. Battery powered all-solid state digital circuitry with sealed Reed Relay output for block grid keying. Also operates into mike jack to work VOX CW on upper or lower sideband. Unique audio circuit provides for monitoring and mixing incoming signals.

NEW CODAX™ Automatic Keyer

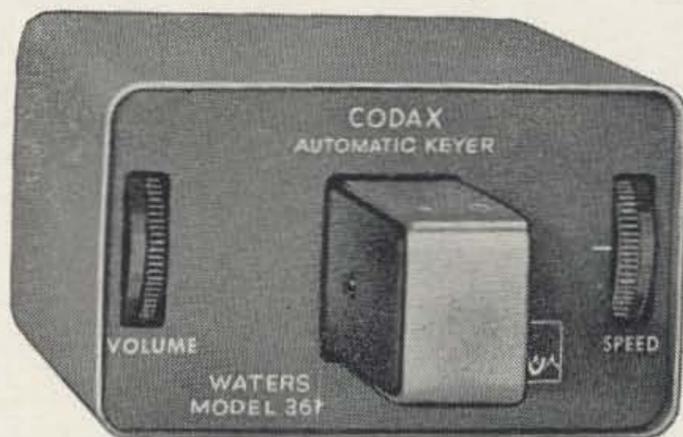

Model 361 \$92.50 (Less batteries)

Introducing . . . *Waters* CLIPREAMP™ to increase your "talk power"


A solid state clipper-preamplifier, the brand new Waters CLIPREAMP will increase your intelligibility and talk-power up to 4 times when band conditions are tough! Self-powered and weighing but 6½ ounces, CLIPREAMP installs externally between microphone and transmitter in a matter of minutes. Front panel controls switch CLIPREAMP IN or OUT, OFF or ON, and permit Compression-Level adjustment to individual requirements. Input: 100K ohms; Output: 50K ohms; Voltage Gain: 10 DB nominal; Power: 9-volt battery.

Model 372 \$21.95
(Less battery)



WATERS
MANUFACTURING INC.
WAYLAND, MASSACHUSETTS

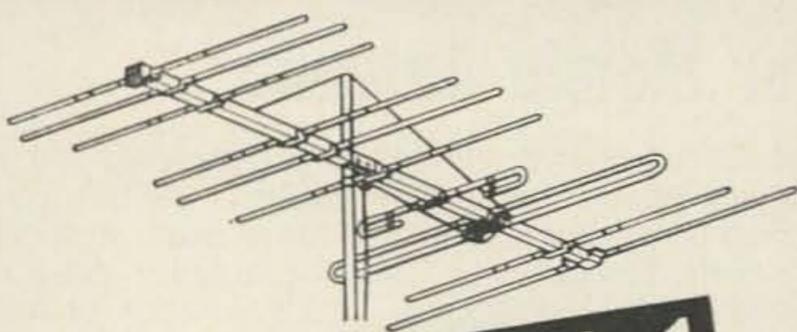FINCO 6 & 2 Meter Combination Beam Antennas



2 ANTENNAS in 1

MODEL A-62 · 300 OHM


On 2 Meters:

- 18 Elements
- 1-Folded Dipole Plus Special Phasing Stub
- 1-3 Element Colinear Reflector
- 4-3 Element Colinear Directors

On 6 Meters:

- Full 4 Elements
- 1-Folded Dipole
- 1-Reflector
- 2-Directors

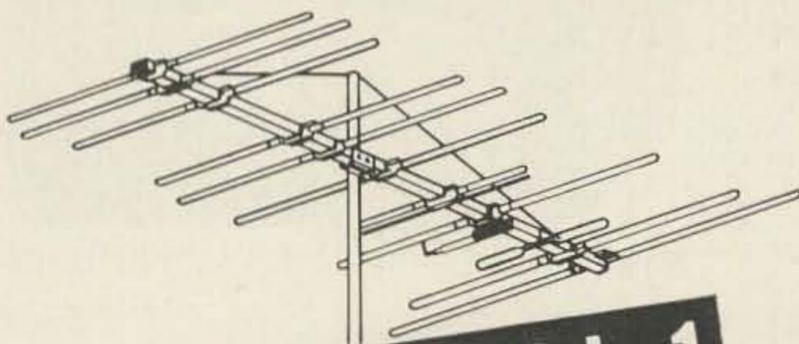Amateur Net . . . \$33.00
Stacking Kit \$2.19



2 ANTENNAS in 1

MODEL A-62 GMC · 50 OHM

On 2 Meters:

- Equivalent to 18 Elements
- 1-Gamma-Matched Dipole
- 1-3 Element Colinear Reflector
- 4-3 Element Colinear Directors

On 6 Meters:

- 4 Elements
- 1-Gamma-Matched Dipole
- 1-Reflector
- 2-Directors

Amateur Net . . . \$34.50
Stacking Kit \$18.00

MODEL AB-62 GMC

On 2 Meters:

- Equivalent to 30 Elements

On 6 Meters:

- Equivalent to 6 Elements

Amateur Net . . . \$52.50

Also:

- 5 New 6 Meter Beams
- 3 New 2 Meter Beams
- 1 New 1 1/4 Meter Beams

Gold Corodized for Protection Against Corrosion
See Your Finco Distributor or write for Catalog 20-226

The FINNEY Company - Bedford, Ohio

Propagation Chart

April 1965

J. H. Nelson

EASTERN UNITED STATES TO:

	GMT: 00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	7*	7	7	7	7	7	7	7	7*	7	14
ARGENTINA	14	14	7*	7	7	7#	14	14	21	21	21*	21
AUSTRALIA	14	14	7#	7#	7#	7	7	7	7	7#	14	14
CANAL ZONE	14	7*	7	7	7	7	14	14	14	21	21	21
ENGLAND	7	7	7	7	7	7#	14	14	14	14	14	14
HAWAII	14	14	7#	7	7	7	7	7*	14	14	14	14
INDIA	7	7#	7#	7#	7#	7#	14	14	14	14	14	7
JAPAN	14	7#	7#	7#	7#	7#	7	7	7	7#	14	14
MEXICO	14	7*	7	7	7	7	7*	14	14	14	14	14
PHILIPPINES	14	7#	7#	7#	7#	7#	7#	7	7	7	7#	14
PUERTO RICO	14	7	7	7	7	7	14	14	14	14	14	14
SOUTH AFRICA	7*	7	7	7#	7#	14	14	14	14	14	14	14
U. S. S. R.	7	7	7	7	7	7#	14	14	14	14	14	7
WEST COAST	14	14	7	7	7	7	7	14	14	14	14	14

CENTRAL UNITED STATES TO:

ALASKA	14	14	7	7	7	7	7	7	7	7*	14	14
ARGENTINA	21	14	14	7	7	7#	14	14	14*	21	21*	21
AUSTRALIA	14	14	14	7#	7#	7	7	7	7	7#	14	14
CANAL ZONE	14	14	7	7	7	7	14	14	14	21	21	21
ENGLAND	7	7	7	7	7	7#	14	14	14	14	14	14
HAWAII	14	14	14	14	7#	7	7	7	7#	14	14	14
INDIA	7	7#	7#	7#	7#	7#	14	14	14	14	14	7
JAPAN	14	14	7#	7#	7#	7#	7	7	7	7#	14	14
MEXICO	14	7*	7	7	7	7	7	7*	14	14	14	14
PHILIPPINES	14	14	7#	7#	7#	7#	7#	7	7	7	7#	14
PUERTO RICO	14	14	7	7	7	7	14	14	14	14	14	14
SOUTH AFRICA	7*	7	7	7#	7#	7#	14	14	14	14	14	14
U. S. S. R.	7	7	7	7	7	7	7#	14	14	14	14	7#

WESTERN UNITED STATES TO:

ALASKA	14	14	14	7	7	7	7	7	7	7*	14	14
ARGENTINA	21	14	14	7	7	7	7	7	14	14	21	21
AUSTRALIA	21*	21*	21	14	14	14	7	7	7	7#	14	21
CANAL ZONE	21	14	7*	7	7	7	7	7	14	14	14*	21
ENGLAND	7	7	7	7	7	7	7#	7#	14	14	14	14
HAWAII	21*	21*	14	14	14	7	7	7	7	14	14	14
INDIA	14	14	14	7#	7#	7#	7#	7#	7*	14	14	14
JAPAN	14	14	14	14	7#	7#	7	7	7	7#	14	14
MEXICO	14	14	7	7	7	7	7	7*	7*	14	14	14
PHILIPPINES	14	14	14	14	7#	7#	7	7	7	7	7#	14
PUERTO RICO	14*	14	7	7	7	7	7	14	14	14	14	14*
SOUTH AFRICA	7*	7	7	7#	7#	7#	7#	14	14	14	14	14
U. S. S. R.	7#	7#	7	7	7	7	7	7#	14	14	7#	7#
EAST COAST	14	14	7	7	7	7	7	14	14	14	14	14

Very difficult circuit this hour.

* Next higher frequency may be useful this hour.

Good: 1, 2, 4-6, 13-17, 19-26, 30

Fair: 3, 7, 9, 10, 18, 27-29

Poor: 8, 11, 12

VHF Dx: 4, 13, 14, 30

NEW 70-FT. FREESTANDING

TRI-EX

LM 470

*Another First
from TRI-EX!*

**ALL-WEATHER
MAINTENANCE
FREE...
PERMANENT!**

Absolutely freestanding. Capable of withstanding 60 mph winds at full 70 ft. height, with up to 16 sq. ft. of antenna. Rust free. All Tri-Ex towers are hot-dipped galvanized *after fabrication*. Unusual strength due to high strength steel tubing, solid steel bracing, all-electric welded by certified welders. Lowest possible wind drag.

STARTS AT
\$995

TILT-OVER AND OTHER
ACCESSORIES AVAILABLE.

WRITE FOR FREE BROCHURE

 **Tri-Ex TOWER CORPORATION**

127 EAST INYO ST. • TULARE, CALIF.

TRI-EX TOWER CORPORATION OPENS FACTORY-DIRECT PROGRAM

Tri-Ex Tower Corporation has inaugurated a new policy of factory-direct consumer sales, it was announced today.

"Tri-Ex has always been dedicated to building the best towers available anywhere at any price," said A. J. F. Clement, W6KPC, president. "Now we will also offer the very best in service to Tri-Ex tower owners.

"By factory-direct sales a number of advantages will be accrued by new tower owners. First, each factory-direct order is assured of faster service. Second, the very finest professional engineering assistance is immediately available. Third **ALL** Tri-Ex towers are now *hot-dipped galvanized* after fabrication (rust-free), at **new lower prices**, (financing available). Fourth, it is well known that Tri-Ex Tower Corp. engineered and developed the crank-up tower from its infancy. Research and development in the crank-up tower field continues unabated as evidenced by the new (LM-470) seventy foot free standing tower recently marketed. The LM-470 is a minimum cost installation, requiring only a single base mount.

"Since most key personnel at Tri-Ex are active Radio Amateurs, they are very well qualified to assist you in selecting the most appropriate tower to fit *your* particular requirement."

The below listed members of the Tri-Ex staff are always available to answer any questions that you may have.

Martin Blackstone,
WA6MFY/VR30

Clyde Blyleven, WA6ONZ

Frank Clement, W6KPC

John Hultquist, W6QMC

Contact us now for your **free catalog** describing Tri-Ex's complete line of free standing towers, guyed telescoping towers, and fixed height towers. Write to Tri-Ex Tower Corp., P.O. Box 298, Tulare, Calif., or call (209) 686-3411.



Part of Swan main assembly line.

HF SSB Transceivers

Two years ago we ran our first sideband transceiver special section in 73. The reader response was so enthusiastic that I decided to repeat the section every year. Then, last year, with the amateur equipment sales at a ten year low due to the panic over the ARRL Executive

Committee's submission of RM-499 to the FCC, there seemed to be little need for a buying guide. Things look much better this year. Quite promising. 16% of our readers told us that they intended to buy a sideband transceiver in the near future. That's a lot of transceivers.

MODEL	DATE RELEASED	BASIC PRICE	FINAL TUBES	PEP INPUT	80 METERS	40 METERS	20 METERS	15 METERS	10 METERS	OTHER COVERAGE	SIDE BANDS	
COLLINS	KWM-2	1960	1150.	2)6146A	175	3.8 - 4.0	7.0 - 7.4	14.0 - 14.4	21.0 - 21.6	28.5 - 28.7	14.8 - 15.0	both
DAVCO	DR-30	10/64	700	8117	200	3.5 - 4.05	7.0 - 7.55	14.0 - 14.55	21.0 - 21.55	28.0 - 30.05	note *1	both
DRAKE	TR-3	6/63	550.	3)12JB7	300	3.5 - 4.1	7.0 - 7.6	13.9 - 14.5	21.0 - 21.6	28.0 - 29.7	- - - -	both
EICO	753	NA	k180. w300.	2)6DQ6B	180	3.49-4.07	6.97-7.33	13.89-14.41	- - - -	- - - -	- - - -	note *2
GALAXY	III	4/64	350.	2)6HF5	300	3.5 - 4.0	7.0 - 7.5	14.0 - 14.5	- - - -	- - - -	- - - -	both
GALAXY	V	7/64	470.	2)6HF5	300	3.5 - 4.0	7.0 - 7.5	14.0 - 14.5	21.0 - 21.5	28.0 - 29.0	28.5 - 29.5 acces.	both
HALLICRAFTERS	SR-150	11/62	650.	2)12DQ6B	150	3.5 - 4.0	7.0 - 7.5	14.0 - 14.5	21.0 - 21.5	28.0 - 30.0	- - - -	both
HALLICRAFTERS	SR-160	11/63	350	2)12DQ6B	150	3.5 - 4.0	7.0 - 7.5	14.0 - 14.5	- - - -	- - - -	- - - -	*2
HEATH	HW-12,	5/63	kit:	2)6GE5	200	3.8 - 4.0	7.2 - 7.3	14.2 - 14.35	- - - -	- - - -	- - - -	*2
NATIONAL	NCX-3	1/63	370.	2)6GJ5	200	3.48-4.02	6.98-7.31	13.88-14.42	- - - -	- - - -	- - - -	*2
NATIONAL	NCX-5	10/64	685.	2)6GJ5	200	3.5 - 4.0	7.0 - 7.3	14.0 - 14.5	21.0 - 21.5	500kc. seg. 1 xtal. incl.	- - - -	both
SBE	SB-34	12/64	395.	2)6GB5	135	3.775-4.025	7.05-7.30	14.1 - 14.35	21.2 - 21.45	- - - -	- - - -	both
SWAN	350	7/64	395.	2)6HF5	400	3.5 - 4.0	7.0 - 7.5	13.85-14.35	21.0 - 21.5	28.5 - 29.0	- - - -	*2
SWAN	400	1964	395.	2)6HF5	400	3.4 - 4.0	7.0 - 7.4	14.0 - 14.4	21.0 - 21.6	28.0 - 29.8	WWV	both
TRANSCOM	SBT-3	3/65	300.	2)8042	165	3.78-4.01	7.18-7.32	14.13-14.36	- - - -	- - - -	- - - -	*2

*1 - Davco has 9.5 - 10.05 Mc WWV on receiver; 50 - 50.55 on both; 2 positions on both for 4 - 54 Mc.
*2 - LSB on 80 and 40; USB on 20; where 15 and 10 are included, mode is USB.

Those of you that have an April 1963 issue of 73 handy can whip it out and compare it with this one. It is very interesting to see what changes have come about during the past two years.

Starting at the top of the list I find that Collins is still selling their KWM-2, originally brought out in 1959. Six years production on one model is a recent record, isn't it? Next we find Davco. At long last, the ingenious Davco receiver is in production. The last I heard they had finally stopped pushing the state-of-the-art ahead in design and were shipping their first production units. The transmitter half of the combo is still a few months off, I believe. My impression of the receiver was that Jim Lovette K4BXO was not going to sell the thing until he had crammed something like the 75A4 into a 3 x 5 file box, transistorized.

The Drake TR-3, first announced in our transceiver section in 1963, has proven to be a real winner. It certainly had a lot to do with more and more five-band transceivers coming on the market. Bob named it after his Triumph TR-3. I think Bob must have a new Triumph because I understand they will soon announce a new model transceiver, the TR-4.

The Elmac ATR-4 never really materialized. One of the fellows that works here has one, but I haven't seen any others around.

The Hallicrafters SR-150, introduced in 1962, is still going strong and has been joined by the SR-160, a three-bander. The FPM-200

was a nice rig, but I guess it was too expensive for us hams.

The Heath transceivers are now history. Their first unveiling was in our transceiver survey.

National followed up their NCX-3, which had just barely come out in 1963, with the NCX-5 five-bander and a beaut of a linear. We'll run a special linear section later on for you.

Sideband Engineers is still going strong. Their SB-33 made quite a hit and their SB-34 seems to be doing it all over again.

Sonar. Hmmm. . . I think they have settled into selling commercial units and are not really trying to do much ham business. I haven't heard anything from them in the last two years.

Swan, the one who started this whole thing, is still giving everyone else in the field a hard run for the customers with their new Swan-350 with five bands and a \$400 price tag.

Transceivers Inc. Their imitation Swan transceiver never actually made it into production.

Galaxy has a new one out, the V. You'll read more about that one in my review of it elsewhere in this issue. Their amazingly low price has not hurt their popularity one bit.

While three manufacturers have dropped out of the transceiver field, only two have recently entered it: Eico and Transcom.

Sideband is here . . . it has grown up. Our recent survey showed that 51% of 73's readers are on SSB. And 35.5% have a rig in their car. Got yours yet?

1st IF, Mc.	2nd IF, Mc.	HEIGHT	WIDTH	DEPTH	WEIGHT	VOX	100 Kc. CAL	S METER	SIDEBAND GENERATION	DELTA or OFFSET TUNING	DIAL CALIB, Kc.	MOUNTING BRACKET	AC SUPPLY	DC SUPPLY	TOTAL PRICE	
2,955-3.155	.455	7	14-3/4	14	18	yes	yes	yes	Collins mech.	acc.	1	120.	115.	12V 200.	1468.	COLLINS
2.405-2.955	.455	4 each	7-1/8 each	DR-30: 6 DT-20: 9	9 11	yes		yes	filter	*4	1		168. incl.	28V 470. incl.	700.	DAVCO
2.955-9.0	-	5-1/2	10-3/4	14-1/2	16	yes	yes	*3	separate xtal filt.	acc.	1	7.	80.	130.	786.	DRAKE
5.2	-	5-1/2	14	11-1/4	25	yes	acc.	yes	xtal	+10	NA	incl.	?	?	?	EICO
9.0	-	6	10-1/4	11-1/4	13	\$25	\$20	yes	xtal	acc.	5	8.	80.	120.	477.	GALAXY
9.0	-	6	10-1/4	11-1/4	13	\$25	\$20	yes	xtal	acc.	5	8.	80.	120.	598.	GALAXY
6.0-6.5	1.650	6-1/2	15	13	17-1/2	yes	yes	yes	xtal	RIT	1	40.	100.	110.	789.	HALLICRAFTERS
5.2	-	6-1/2	13	11	13-1/2	acc.	acc.	yes	xtal	RIT	5	15.	100.	110.	500.	HALLICRAFTERS
2.305	-	6-1/4	12-1/4	10	15	yes	\$9	yes	xtal	no	2	incl.	40.	60.	180.	HEATH
5.2	-	6-1/16	13-5/8	11-5/8	25	yes	acc.	yes	xtal	no	5	incl.	110.	120.	490.	NATIONAL
6.02	3.5	6-5/16	13-5/8	11-5/8	26	yes	acc.	yes	xtal	+5	100cyc.	incl.	110.	120.	805.	NATIONAL
.455	3.225	5	11	10	18	acc.	acc.	yes	Collins mech.	+1	5	12.50	incl.	incl.	408.	SBE
5.174	-	5-1/2	13	11	17-1/2	\$35	acc.	yes	xtal	no	5	20.	85.	130.	545.	SWAN
5.174	-	5-1/2	13	11	17	acc.	yes	yes	xtal	no	2	20.	85.	130.	620.	SWAN
5.1	-	4-3/8	11-3/8	8-3/4	10	PTT only	no	yes	xtal	no	5	3.50	140.	100.	403.	TRANSCOM

*3 - 2nd Drake meter indicates "S" units on receive and ALC on transmit.

*4 - Davco's separate receiver and transmitter allow either transceive or separate operation.



KWM-2

Collins Radio Cedar Rapids, Iowa

Unmatched for versatility, dependability and mobility, the Collins KWM-2 maintains a reputation of outstanding performance in mobile and fixed station applications.

The KWM-2 power input is 175 watts PEP on SSB or 160 watts on CW. It transmits on voice or CW with a nominal output of 100 watts for complete coverage on 80 through 10 meters. Crystals are provided for all HF bands except 10 meters, where one crystal is supplied with provision for two additional crystals.

The transceiver is finished in light gray enamel with a simulated leather front panel to match the S/Line.

The first available amateur mobile SSB transceiver was in the Collins KWM series. The KWM-2 continues to lead the field with the following features: Filter type SSB generation providing unsurpassed performance on both transmit and receive.

Automatic load control which keeps the signal level adjusted to its rated PEP, resulting in an increase in average talk power.

Inverse rf feedback which improves linearity and reduces distortion products, giving the cleanest signal on the air.

Permeability-tuned Variable oscillator with linearity and stability providing the best fre-

quency calibration available.

One kc division on all bands, eliminating frequency searching and allowing you to meet anyone on sked, on any band 80 through 10 meters.

Compactness and efficiency of the KWM-2 are achieved through Collins' advanced design of having all tuned circuits and several tubes function in the dual role of transmitting and receiving. The same oscillators, mechanical filter and rf amplifier serve both the transmitter and receiver. CW break-in and monitoring side-tone circuits are built in.

Easily accessible controls on the front panel of the KWM-2 include the OFF-ON-NB-CAL SWITCH, EXCITER TUNING, ZERO SET, PA TUNING, LOADING, MIC GAIN, BAND SWITCH, AF GAIN, RF GAIN, EMISSION and METER SWITCH.

The KWM-2A is an extended frequency version of the KWM-2 for MARS (Military Affiliate Radio Service) and military applications. The KWM-2A has an additional crystal board permitting the operator to add 14 crystals to cover frequencies outside the amateur bands. The KWM-2A has a front panel switch and indicator, allowing instant switching between the two crystal boards.




TR-3

R. L. Drake Co.

Miamisburg, Ohio

The Drake TR-3 is designed to be a COMPLETE SSB transceiver. All ham frequencies, 80 through 10 meters are covered completely with all crystals furnished. Included also, are both sidebands, selectable as desired, dual metering of transmitter plate, and ALC and receiver S meter. The linear permeability tuned PTO covers 600 kc on each range. It is resettable to less than 1 kc if the dial is calibrated at the closest 100 kc. Amplified AGC is provided for receiving and amplified ALC is used to minimize flat-topping on SSB transmission. The 100 kc calibrator is built in. Vox, push to talk SSB, controlled carrier AM (260 watts PEP), and CW (260 watts PEP) functions are provided. 300 watts PEP input on SSB provides more than adequate output for driving the largest linear. This extra power was provided because a transceiver is often used as a complete station, mobile or portable, with antennas that are less efficient than in home stations. Accessories available are the AC-3 Power Supply for 120 or 240 volt, 50-60 cycle operation; the DC-3 Power Supply for 12 volt DC battery operation; the MMK-3 Mobile Mounting Kit; the MS-3 Speaker Assembly (provides space for AC-3 Power Supply); and the RV-3 separate PTO, speaker and power supply enclosure. The RV-3 provides independent transmitting and receiving frequency control for working DX and other independent uses.

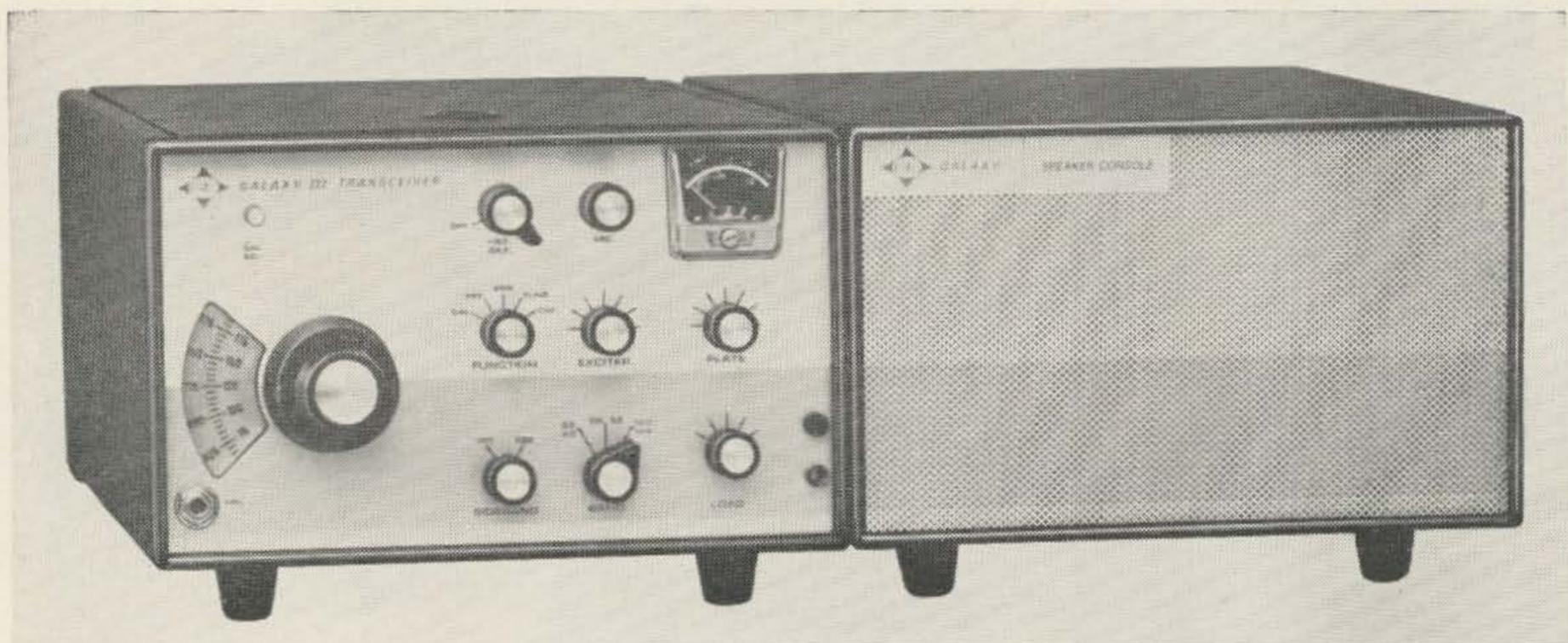

III and V

The Galaxy III and V transceivers have many features. They are easily adapted to mobile operation because of their small size. They use the EZ Vue dial for minimum visual read-out error in mobile use. Their receivers are very sensitive: better than $0.5 \mu\text{v}$ for 10 db S/N. They have dual attack and release AVC to make the receiver virtually block proof. They have eight to ten db of ALC for increased power and minimum flat-topping and distortion. They have selectable upper and lower sidebands. They are manufactured under the strictest possible quality control. They have shifted carrier CW for best operation. Accessories available include a Deluxe console at \$99.95 with 24 hour clock, SWR bridge, speaker, phone patch and a meter calibrated in SWR and VU. The Remote VFO is \$59.95 gives full range coverage. The Standard Speaker Console is \$19.95.

Galaxy Electronics

10 South 34th St.

Council Bluffs, Iowa



SR-150 and SR-160

Hallicrafters Co.

5th and Kostner

Chicago, Ill.

The Hallicrafters Model SR-150 Transceiver is a precision-built, compact, high-performance radio equipment of advanced design. This transceiver utilizes 19 tubes and a dual conversion *if* to provide for the transmission and reception of single-sideband (SSB) and continuous wave (CW) signals on the 80, 40, 20, 15, and 10 meter bands. The SR-160 is a three band single conversion transceiver covering the 80, 40 and 20 meter bands. Both the SR-150 and SR-160 feature AALC for improved talk-power and third and fifth order distortion products down 30 db.

The versatility this equipment permits it to be operated as a fixed station or as a mobile equipment. A 117-volt, 50/60-cycle, AC power supply, complete with speaker is available for fixed-station use; a 12-volt DC power supply and a mobile mounting rack are available when the transceiver is to be used in a mobile configuration.

An advanced feature of these transceivers is the Receiver Incremental Tuning (RIT) control. This control enables the operator to unlock the receiver frequency and tune the receiver approximately two kc either side of the transmitter frequency. Flipping the RIT switch off automatically returns the equipment to the transceiver condition.




HW-12, 22, 32

Heath Company
Benton Harbor, Mich.

The three Heath single band SSB transceivers are neatly styled units providing complete transceiving facilities suitable for mobile or fixed operation. Features include a deluxe fourteen tube superheterodyne circuit for receive that provides a sensitivity of 1 microvolt and selectivity of 2.7 kc at 6 db and 6.0 kc at 50 db. Drift is less than 200 c/hour after warm up. Transmitter final input is 200 watts PEP. The VFO operates on 1.5 to 1.8 mc. PTT and VOX are built in, and provision for a linear amplifier is provided. An optional 100 kc crystal calibrator is available.

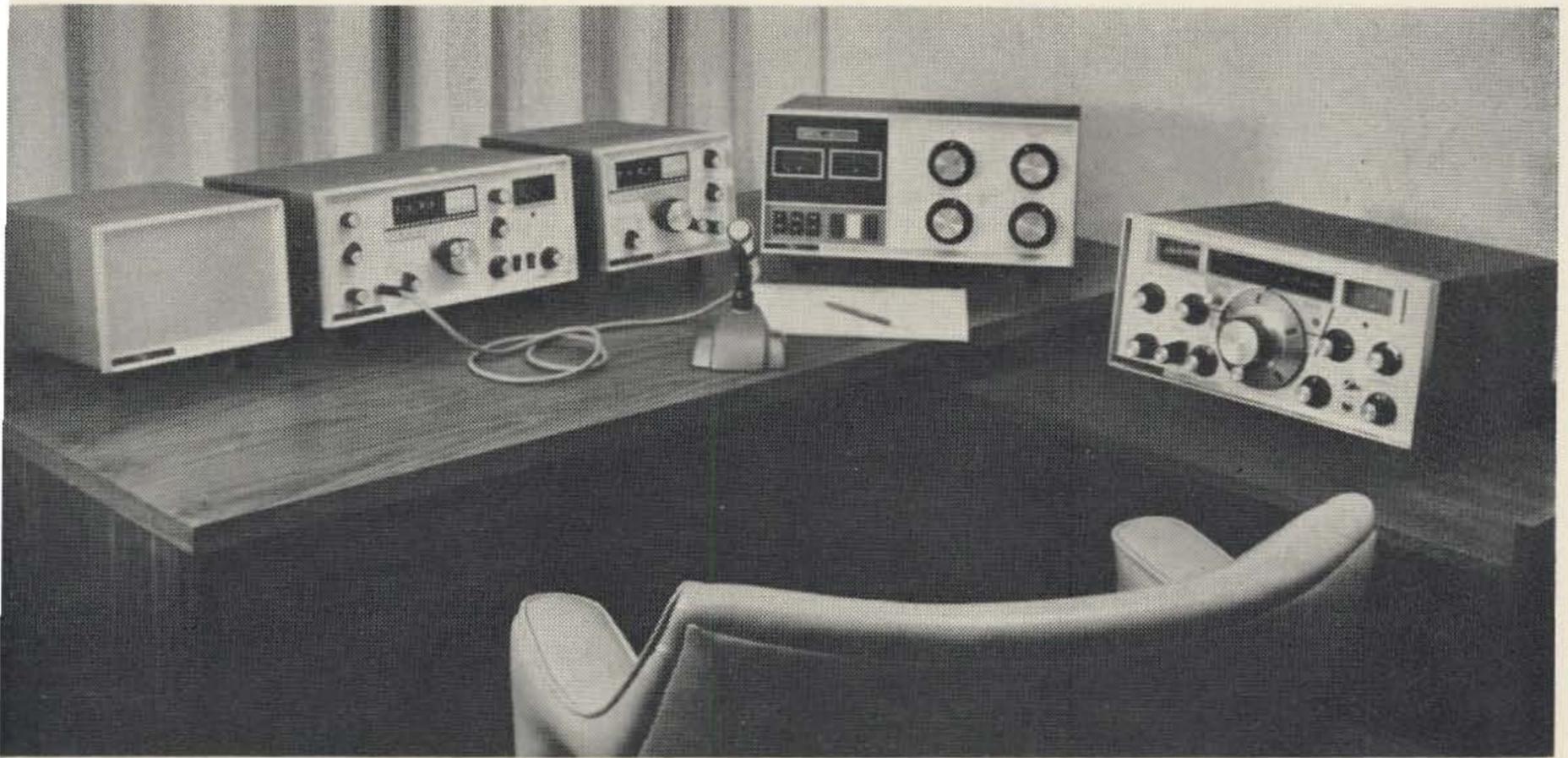Assembly is easy with over 90% of the components mounting on a heavy circuit board. A pre-cut, cabled wiring harness and easy-to-follow instructions further simplify assembly. Alignment is easy as all critical stages are pre-tuned. The gimbel mounting bracket is included.



NCX-3, NCX-5

The NCX-5 is National's 5 band SSB transceiver. It has digital counter tuning readout accurate to 1 kc with dial calibration to 100 cycles. The NCX-5 uses a solid state VFO with no warm-up drift; it is virtually unaffected by large variations in input voltage. The upper and lower sidebands are switch selectable with no retuning. National's new 6.0218 mc 8 pole crystal lattice filter has a shape factor of 1.7:1 and a 6 db bandwidth of 2.8 kc. The Transceive Vernier control allows ± 5 kc receiver separation from the transmit frequency. 10 db of ALC minimizes flat-topping. Among other features are two receiver rf stages to provide $0.5 \mu\text{v}$ sensitivity for 10 db S/N ratio; separate AM detector; VFO input for optional VFO console; choice of built-in VOX, PTT or MOX (manual control); and break-in grid block CW.

The NCX-3 Triband SS transceiver provides complete coverage of the 80, 40 and 20 meter phone and CW bands, VOX or PTT, grid block break-in CW, product detector for CW/SSB and triode detector for AM and geared planetary tuning dial. The handsome front panel is anodized for maximum protection against wear.

National Radio
Company
Melrose, Mass.




SB-34

Sideband Engineers

317 Roebbling Rd.
S. San Francisco, Calif.

The SB-34 is a four band SSB transceiver using 23 transistors, 18 diodes, 1 varactor, 1 zener diode and three tubes. Using transistors so extensively results in lower current drain, cooler operation, longer life and small size. Performance is equivalent to or better than comparable tube-type transceivers. For example, receiver sensitivity is $1 \mu\text{v}$ for 10 db S/N. 2.1 kc selectivity is provided by the Collins mechanical filter.

The SB-34 uses bilateral amplifiers and mixers throughout, on both transmit and receive. They operate by controlling the direction of amplification. This reduces circuit complexity, reduces the number of materials required, simplifies adjustments and eliminates the need for transmit-receive relays. Tuneup and operation of the SB-34 is simple; a unique permeability tuning slug mechanism eliminates separate coil sets for each band. An ingenious Geneva movement combines bandswitch and exciter tuning functions in a single knob. The loudspeaker and both ac and 12 v dc power supplies are built in. Drift is very low: less than 100 cycles in any 30 minute period under any normal ambient condition.

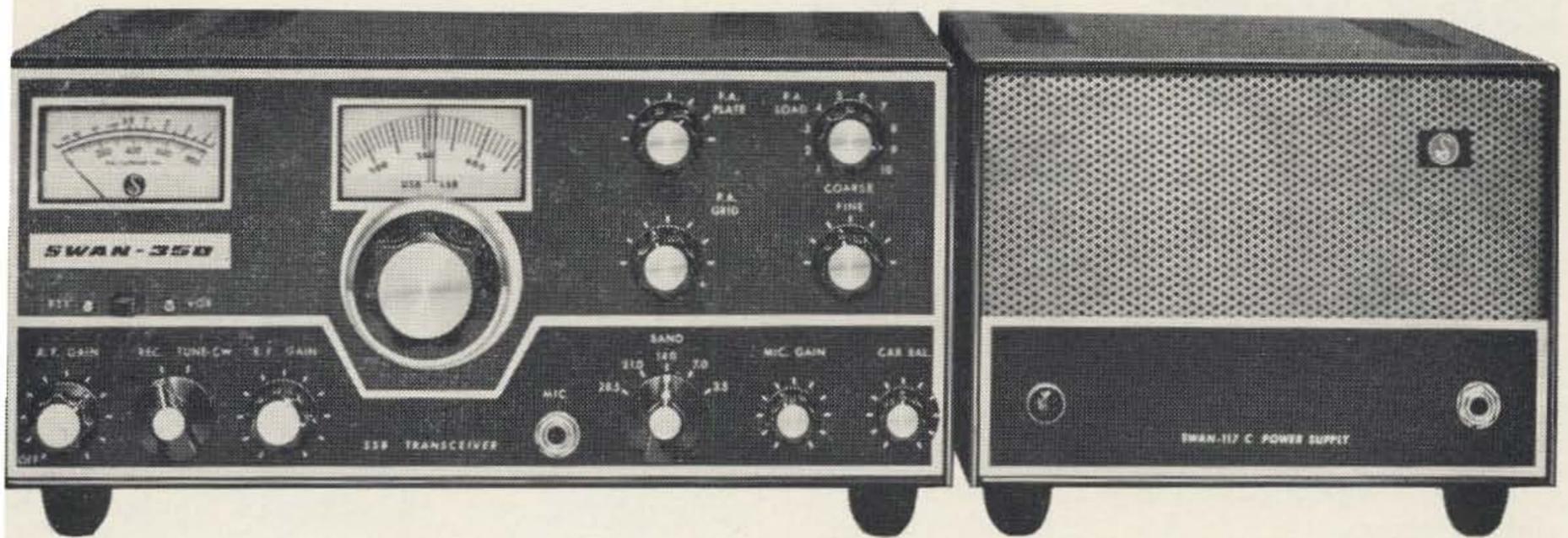

350 and 400

Swan Electronics is currently marketing two 5 band transceivers. Each is rated conservatively at 400 Watts PEP input. These models, the 350 and the 400, are outgrowths of the original SSB single band transceivers and the very popular model 240 tribander.

Swan's outstanding reputation for high performance quality and dependability at a reasonable cost has been built over a relatively short period and these two additions to the line will undoubtedly enhance this reputation.

The 400 is the deluxe model in the Swan line. An external VFO with no built-in heat source provides exceptional stability and calibration. Warm-up drift is negligible and the unit is rockstable after the first few minutes. This unit is readily adaptable for use on Mars frequencies or commercial frequencies without loss of ham bands.

The standard model 350 transceiver includes all necessary features for either fixed or mobile operation on all bands and permits inclusion of non-essential but nice "features" at nominal kit cost. It features the same high quality and reliability of the 400 and other Swan transceivers, and it is priced reasonably.

Swan Electronics
Oceanside, Cal.

IoAR News



Something new has been added for IOAR membership! A new low membership fee has been announced as yearly dues of the IOAR. There's something tangible in it for you, too. Here's how it works—for \$7.00, now you can have an active part in supporting the IOAR as a full member and receive 73 Magazine, too. There's no distinction as to membership levels dependent upon the class of your amateur radio license.

How about those that are already IOAR members and receive the magazine and want to get in on the combined arrangement? Easy! Send in your \$7.00 for IOAR and 73, and your membership will be extended through your current 73 subscription and then will run concurrent with the added 12 issues of the magazine. (No adjustments either way, please.)

Now—how about the fellow who is a current subscriber to 73 only? Send in your \$7.00. Your IOAR membership will start immediately and will remain through your present subscription until expired and then will automatically continue for the additional 12 issues of 73 until the concurrent expiration of membership and 73. All conditions soon come into adjustment. We call it "togetherness." Simple, isn't it?

O. K. fellows, now let's build, Build, BUILD MEMBERSHIP! (Later, arrangements are anticipated to be worked out on a club affiliated membership basis.) Let's get that treasury swelling so we can allocate emergency funds to cover amateur radio contingencies as they occur. IOAR wants to be ready to assist where necessary.

If you didn't already recognize it—it is a fact that 73 is the official organ of the IOAR. Not the entire magazine, but those number of pages carrying the IOAR News and other features pertinent to IOAR.

The constitution and by-laws are forthcoming. They are about ready to be released through our own official news media (IOAR News that is) in 73 Magazine. All IOAR members will have a chance to ratify the rules. Unlike other organizations of similar intent, IOAR will be democratic. Let us all keep it that way. It may take a little longer, but members will have their say.

The IOAR is not and will not become a publishing house. Its prime interest will continue to be devoted to the amateur radio fraternity. 73 Magazine is quite capable of disseminating all official IOAR matters with its national and international wide range of distribution reaching IOAR members and non-members alike all over the world. In this connection, it is sound business management to captivate the largest field of absorption (73 is widespread and influential) on matters of the IOAR to all interested amateur licensees of all classes whether they are members or not.

Get set soon for a voluminous and complex FCC proposal for rule making affecting, to some degree, most all classes of amateur radio licensees. Some of you won't like it. It is anticipated that a sizable minority group will not be affected (again).

Looking on all sides of the problems and having had measured the RM-499 official file of dissenters, the proposal probably won't be identical to this mad, mad, mad approach. But don't be too self assured—read the fine print carefully—rumor—strictly rumor has it that the old guard has rallied again. Don't rule out the possibility that the W4RLS Foy Guinn petition may have been studied with all of its thousands of Joiners in Petition. The FCC certainly has had enough elapsed time to ponder and come up with something really good (we hope) as opposed to the one organization's approach over a year ago.


A lot of you remember FCC's Docket 9295 of the 1949 era. The ARRL, not content with the commission's "Basis and Purpose" and a truly realistic incentive licensing plan, chose to hack away for the protection of the old Class A to avoid their losing operating privileges because the FCC proposed placing them into the General Class bracket (I wonder what it will be this time). Well—that was a long time ago—the battle won but the war was lost—could the ARRL have been remiss?

If you support or disagree with the "new approach" (The FCC proposal), carefully observe the deadline date for filing and get those good reasons of yours off to the FCC in an ORIGINAL plus fourteen (14) additional copies substantiating your comments pro or con.

Yes—the IOAR has stamps. They are a brilliant orange-red and self-adhesive. Perhaps you have seen them. Request your stamps today with your membership application—JOIN IOAR—BOOST IOAR—PUSH IOAR.

E. M. Schaad WA4PDX/W9A1Y
Director

IT'S THE SAME LITTLE OLD BOX

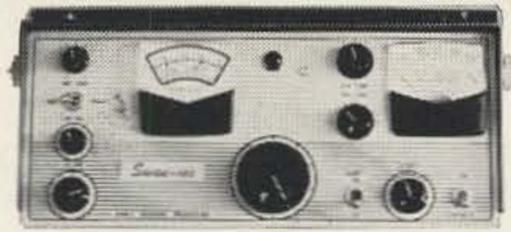

1962 SWAN SINGLE BANDER —
1 BAND — 180 WATTS — \$275



1963 SWAN 240 — 3 BANDS — 240 WATTS — \$320

but we've put a LOT MORE in it!



NOW THE **SWAN-350** TRANSCEIVER 5 BANDS — 400 WATTS AND ONLY \$395

- 3.5 - 4.0 mc, 7.0 - 7.5 mc, 13.85 - 14.35 mc, 21.0 - 21.5 mc, 28.5 - 29.0 mc (10 meter full coverage kit available.)
- Transistorized VFO, temperature and voltage stabilized.
- Precision dual-ratio tuning.
- Crystal lattice filter.
- ALC . . . AGC . . . S-Meter.
- 5½ in. high, 13 in. wide, 11 in. deep.
- 400 watts SSB input
320 watts CW input
125 watts AM input
- Sideband suppression: 40 db
Carrier suppression: 50 db
Third order distortion: 30 db
- Lower sideband on 80M and 40M.
Upper sideband on 20M, 15M, and 10M.
(Opposite sideband kit available.)

WITH THE SAME RELIABILITY AND PERFORMANCE
WE'VE PUT IN ALL OUR LITTLE BOXES

ACCESSORIES:

- AC power supply, matching cabinet with speaker. Model 117-C.....\$ 85
- 12 Volt DC Power supply. Model 412.....\$130
- Plug-in VOX. Model VX-1.....\$ 35

SEE THE NEW SWAN 350
AT YOUR DEALER'S NOW!



SWAN

ELECTRONICS CORP.
Oceanside, California

A Versatile Code Monitor

with bonus features—

As every CW operator knows, a code monitor independent of the station receiver helps in clean sending and in maintaining the receiver tuned to that always elusive signal. During my ten years on CW, I have tried every published circuit on monitors without finding one to completely satisfy me. Most required stealing power from the receiver, practically all were dependent on some connection to the transmitter and others utilized plug-in coils to cover more than one band. I finally decided to build my own and the result is a transistorized self powered monitor that works on all bands without tuned RF circuits and needs no attachments or proximity to the transmitter. It can be used as a field strength meter, code practice oscillator, in the home, the car or in the field. The cost of all new components except the meter runs well under ten dollars.

The Circuit

The complete schematic is shown in Fig. 1. The heart of the circuit is the complementary high gain DC amplifier made up of Q_1 and Q_2 , which precedes the Colpitts oscillator Q_3 . Potentiometer R_2 sets the operating point of the DC amplifier to a threshold condition with diode D_1 , Q_1 and Q_2 barely conducting. Under these conditions the collector of Q_2 rests at near ground potential. The oscillator transistor Q_3 receives its base bias from a tap on the Q_2


collector load made up of R_4 and R_5 . With the collector of Q_2 sitting on ground, the oscillator is biased off. Interception of RF energy by the five foot length of wire used as antenna, causes additional current to flow through D_1 and the base of Q_1 . This current is amplified by Q_1 and Q_2 , resulting in saturation of Q_2 , which now has its collector at near supply voltage. Q_3 now is properly biased and oscillates. With the values shown the frequency is 500 cycles, a very clean sine wave, and the volume is sufficient to annoy the XYL.

A meter in series with potentiometer R_6 , placed between the collector of Q_2 and ground, adds a field strength function to the unit. Since the meter is at the output of the DC amplifier a rather inexpensive movement can be used. I use a 0-1 ma meter, but anything up to 10 ma can be used.


A 9-volt transistor battery is used to power the unit. No ON-OFF switch is used. With the oscillator off, the drain on the battery is only 1/10 ma., and the battery should last its shelf life.

Construction

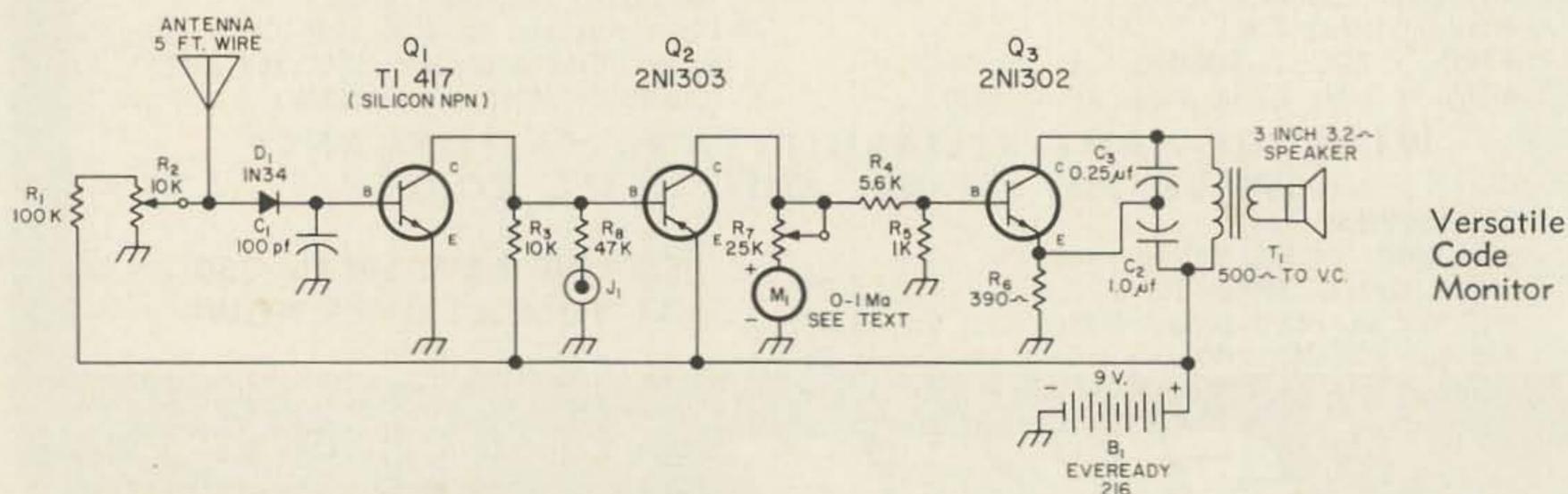A home made printed circuit board is used to mount all components except the two potentiometers, jack, meter, and speaker which mount on the face of 5" x 5" x 7" box. The printed circuit pattern is shown to size in Fig. 2. Lacking a printed circuit board, any con-



Versatile
Code
Monitor

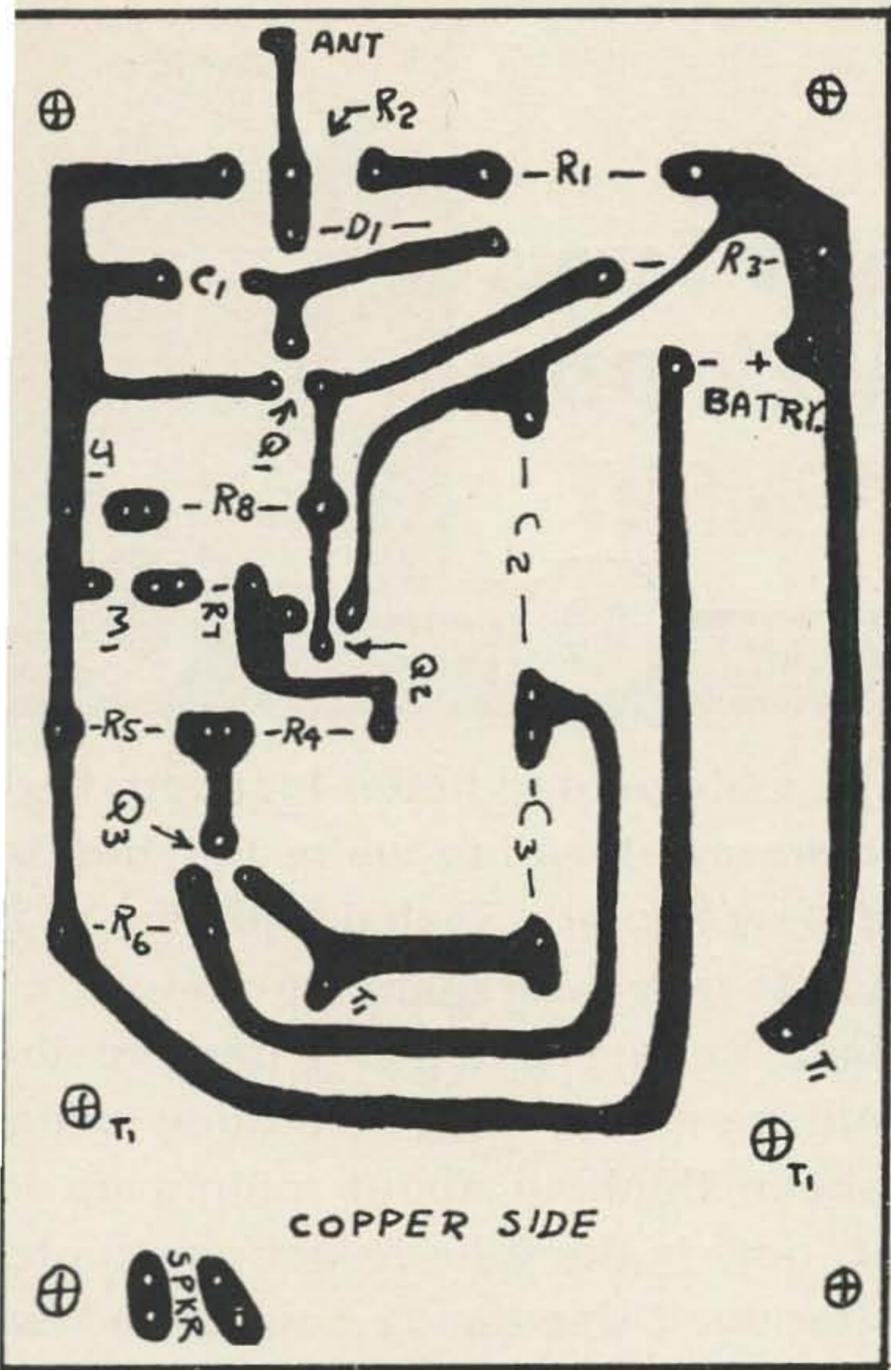

Printed circuit layout.

construction method can be used. Since no RF tuned circuits are used, no particular care need be exercised in layout of components. Make sure that the right output tap is used for the speaker impedance you are using.

Operation


To use the monitor, advance pot R_2 until some broadcast band chatter is heard on the speaker, back off a hair, and you are ready to monitor your transmissions. With my 100 watt transmitter in tune position, positive, chirpless keying is obtained on all bands. If you like QRP, use a longer hank of wire as antenna.

To use the field strength meter, advance pot R_2 until the oscillator is on. Adjust pot R_6 to bring the meter full scale. Leave R_6 alone and use R_2 as the only sensitivity control. Keep the meter reading below 7/10 of full scale. By carefully adjusting R_2 , it is possible to obtain audible changes from the oscillator as the transmitter is tuned for maximum output. This feature may be used by the blind amateur as a means of tuning the transmitter.

After you go QRT, plug in a key in jack J_1 and let the harmonics practice for that long awaited novice license.

... W8GXU

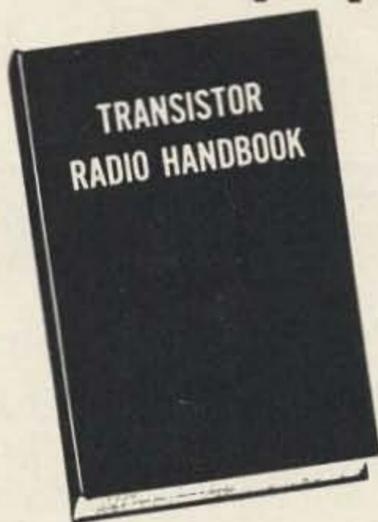HERE'S THE NEWEST KNOW-HOW ON Transistorized Communications Equipment!



a valuable book by
Donald L. Stoner, W6TNS
Lester A. Earnshaw, ZL1AAX

Up-to-the-minute
source book covering
the use of Transistors
in all types of
Communications
Equipment circuitry.

Here's the handbook providing the latest data on the design, construction, and operation of communications equipment using the solid-state circuitry. Covers equipment for both amateur radio and commercial applications. Provides a thorough understanding of basic theory, and offers a comprehensive series of practical construction projects, including amplifiers, VHF equipment, single sideband excitors, and a complete S.S.B. transceiver. This is a book every amateur, builder, and designer will want in his library.


Book No. 044 At your distributor .. \$5.00
(foreign \$5.50)

Get the latest "How-to-Build" data in the Famous RADIO HANDBOOK

Build Practical Equipment:

- New amplifier designs
- New transmitters
- New receivers, transceivers

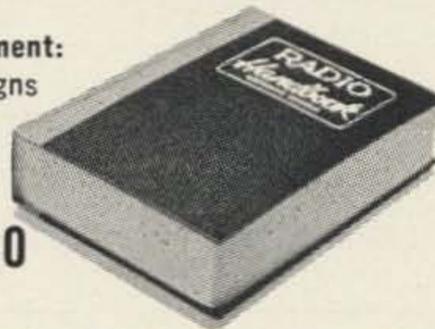Book No. 166
At your distributor... \$9.50
(Foreign \$10.50)



Gives extensive, simplified theory. Provides latest design and construction data for a wide range of advanced amateur equipment. All data is original and up-to-date. Clearly indexed; illustrated; hardbound. 805 pages. No other book like it for builders and designers!

ORDER FROM YOUR ELECTRONIC PARTS DISTRIBUTOR
If he cannot supply, send us his name and your remittance and we will ship.



EDITORS and ENGINEERS, Ltd.

New Augusta, Indiana

Dealers: Electronic distributors, order from us. Bookstores, libraries, newsdealers, order from Baker & Taylor Co., Hillside, N.J. or Momence, Ill. Export (except Canada), order from H. M. Snyder Co., 440 Park Ave. South, New York 10016.

Giant MOVING SALE!

Trade or No-Trade/Cash or Terms

SAVE BIG MONEY on

NEW CLEGG EQUIPMENT



TERRY STERMAN
W9DIA
Proprietor

"We're moving soon to a bigger and better location, here in Milwaukee. At our present location we're bursting at the seams with Brand New Factory-Sealed Equipment. It would cost us too much to move our giant stocks—so . . . we're having this Giant Moving Sale, and passing the savings on to you. Until we move, we'll be trading wilder than ever. If you've been thinking about trading up to some New Equipment, now is the time to get our quote. You'll never get a better deal! Use handy coupon below! There is no obligation."

TRADE-IN Coupon

To: **STERMAN ELECTRONIC SUPPLY**
4828 West Fond du Lac Ave.,
MILWAUKEE, WISCONSIN 53216 7

I am interested in the following new items:

I have the following to trade:

Rush me your SPECIAL MOVING SALE TRADE-IN DEAL by return mail. I understand I am under no obligation.

Name _____

Address _____

City _____

State _____ Zip Code _____

Send latest Reconditioned Equipment Bulletin

We stock the entire
CLEGG Line

**STERMAN
ELECTRONIC
SUPPLY**

4828 West Fond du Lac Ave.
MILWAUKEE, WISCONSIN 53216
Telephone (414) 442-4200

**NOTE: Our firm was formerly known as
AMATEUR ELECTRONIC SUPPLY**

We've changed the name . . . *THAT'S ALL!*

VISIT our Branch Stores, located at:
6450 Milwaukee Avenue | 19 Azalea Pk. Shopping Ctr.
CHICAGO, ILLINOIS | **ORLANDO, FLORIDA**
Phone (312) 763-1030 | Phone (305) 277-8231

LOOK at your low Monthly Payment AFTER JUST \$5⁰⁰ DOWN



SS-IR

SQUIRES-SANDERS

SS-IR Receiver	(32.13)	\$895.00
SS-IRS Speaker	(1.08)	35.00
SS-1S Silencer	(4.69)	135.00
SS-IV Scanner	To be announced	
SS-IT Xmtr.	To be announced	

HAM
NET



VENUS

CLEGG

Zeus Xmtr.	(26.72)	\$745.00
Interceptor B Rec.	(17.69)	495.00
Allbander Tuner	(4.51)	129.95
22'er 2m Xcvr.	(8.46)	239.50
99'er 6m Xcvr.	(6.31)	179.95
Thor 6 RF Unit	(9.20)	260.00
Thor 6 AC Sup.	(4.87)	139.95
Thor 6 DC Sup.	(5.95)	159.95
Venus 6m SSB	(17.69)	495.00
Venus AC Sup.	(3.79)	110.00
Apollo 6 Lin.	(8.75)	247.50
SS Booster	(3.34)	97.50
372 Filter		14.95



NEW SS
BOOSTER
FOR
VENUS



THOR

"If you are considering purchasing, **WITHOUT TRADE**—either Cash or Financed—any **NEW Equipment, Antennas, Towers, or Station Accessories, etc.**—You will want to get our **Special NO-TRADE MOVING SALE DEAL.** You know that the Manufacturers would frown upon our advertising a Discount . . . So, tell us what you are interested in on the Coupon below, and we'll call you Long Distance (at our expense), to let you know how we can save you **BIG MONEY.** You are under no obligation! Sorry, we cannot accept Collect Calls—we'll call you."



RAY
K9KHW
Mgr. Mail
Order Dept.

The above monthly payments are shown for \$5.00 down—regular price—no trade—for 36 months.

Of course if you purchase during our **GIANT MOVING SALE—Trade or No-trade . . .** your monthly payments will be less.

NEW!!
for 2
Meters



NEW SQUIRES-SANDERS 22'ER

Now superior CLEGG performance at the right price. Check these features:

- Full 20 watt input • Nuistorized Triple Conversion receiver • Solid state AC/DC supply • Full frequency coverage for MARS-CD-CAP.

NO-TRADE Coupon

To: **STERMAN ELECTRONIC SUPPLY**
4828 West Fond du Lac Ave., 7
MILWAUKEE, WISCONSIN 53216

I am seriously considering purchasing the following new equipment without trade-in:

I understand you will phone me long distance (at your expense) and tell me how I can save money during your MOVING SALE:

My home phone # is: _____

My phone # at work is: _____

Best time to call: _____

Best time to call: _____

My area code is _____

Name _____

Address _____

City _____

State _____

Zip
Code _____

Send latest Reconditioned Equipment Bulletin

Calibrated Noise Generator for 432



RF Circuitry.

Now that the lid is off the 420-450 mc band as far as power restriction goes, many hams are reaching for the moon-bounce mode on this band, where available transmitting tubes can be used. Groups of 4X150's, 4X250's, 2C39's and such tubes can actually be made to work at 432 mc at the kilowatt input level. Also, the receiver problem isn't quite as hectic as it is at 1296 mc; nuvistors or WE 416B tubes will perform fairly well. Even paramps can be constructed more easily at 432 mc than at 1296 mc, because the pumping source can be of a lower frequency. It sounds as if it is going to be easy to get on, doesn't it, but don't anticipate the world-wide lunar QRM yet—there are some things to be done.

The hams who are going to be successful at 432 moonbounce, are the hams who equip themselves to make *measurements*. The report, "It didn't seem to work" at the termina-

tion of a long, inspired ham construction project, tells one nothing. Since there are many pitfalls, the guy who can instead say: "it doesn't have a low enough sputter ratio" is the one who will persist and, after fixing the trouble, be on "states-worked" page.

As pointed out in previous articles—the temperature-limited noise diode is the best tool for measuring the sensitivity of one's receiver. The measurement made with this device is "noise-figure" or "noise-factor" and this is the magic number by which you can compare your VHF or UHF receiver with Joe's down the street, or Sam's in Massachusetts. These measurements will be comparable between any two receivers because bandwidth, type of detector, and other miscellaneous features (different for each receiver) do not affect the measurement, if it's carefully made (that is, if one's measurement of 3 db power increase, when the diode is turned on, is true).

Past amateur articles on noise-diodes and their use in noise-factor measurement have

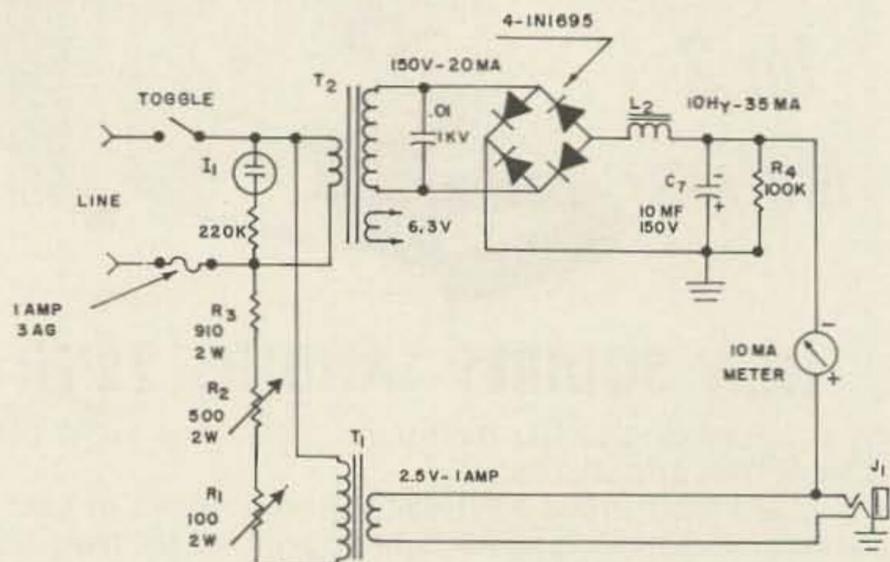


Fig. 1. Power supply.

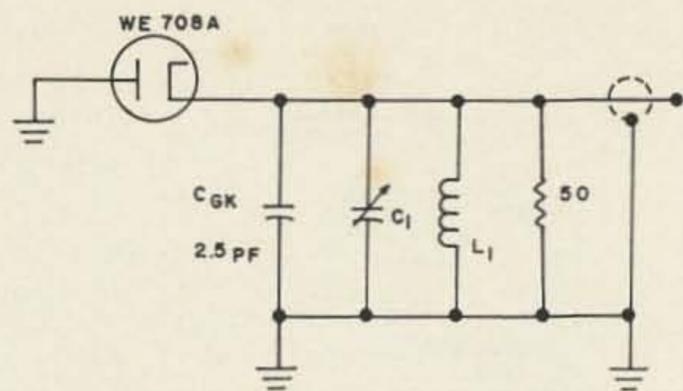


Fig. 2. Basic noise generator circuit.

only shown how to construct units for up to about 200 mc. The noise generators described previously, for amateur use, have used the 5722, the diode wired 24G (3C24), or the diode wired 801A, as their tungsten-filament diodes. The 15E and 01A have also been used occasionally as diode-wired triodes, too. Commercial UHF noise generators use a variety of tungsten-filament tubes, all of which are a bit expensive for most hams. If you can lay your hands on one of these tubes, used or otherwise surplus, by all means employ it in your noise generator. Table I is a list of such gems.

Philco:	L1262A
RCA:	R6212
Bendix:	6144
Marconi:	CV2171

Table I

The tube I used is a triode, a Western Electric 708A, originally designed for grounded-grid UHF amplifier service. The grid and filament are used as the diode elements, ignoring the plate altogether; the plate, if used, could only increase transit time and shunt capacity. The tube is used, as it was intended to be used, with the metal shell (grid) grounded. The 50 Ω load is connected in the filament circuit; the filament power is fed in by means of a concentric inductor, which also tunes out the stray capacity of the tube.

C_1 , a small "tweaker," adds in a tiny additional capacity to make adjustment to 432 mc easier; it makes tuning to anywhere in the 420 to 450 mc band possible. L_1 is constructed of a $1\frac{3}{4}$ " length of $\frac{1}{8}$ " copper tubing and has a piece of No. 20 teflon insulated wire inside it. The use of teflon insulated wire is only necessary because teflon will withstand the heat of soldering.

The effective circuit, then, is as in Figure 2.

At 432 mc, if $C_{gk} + C_1 = 3$ mmfd, then L must be $0.04 \mu h$ to be parallel resonant. The reactance of either $C_{gk} + C_1$ or L_1 is about 100 Ω , so the system has a Q of $\frac{1}{2}$, and hence will be rather broad in its noise output

spectrum—just as we want it to be.

The WE 708A tube was recently available from a Los Angeles surplus emporium at the price of 39 cents each or ten for a dollar. We bought a buck's worth, figuring some would be NG, but all were perfect and saturated well. One was lost in initial test, when we applied too much filament voltage; it was subsequently hack-sawed open to find out the details of its construction and to confirm connections. The details learned are presented in Figure 3 along with its saturation curve.

The filament is a single, fine, straight, tungsten wire through the grid helix. The grid helix is perhaps $1/16$ " diameter and is welded every turn to the shell. All this adds up to: good cylindrical diode configuration, close cathode-grid spacing to cut down transit time, and low grid to case inductance. In short, we have a nearly ideal noise diode for a dime a piece.

Construction details: The rf section of the generator is constructed on an aluminum plate bent into an L, the WE 708A protrudes through a $1\frac{1}{2}$ " round hole to expose its filament pins next to where the UG58A/U connector is mounted on the other side of the L. The WE 708A is held in place by five 8-32 binding-head screws that are tapped into the plate. The UG58A/U has four 200 Ω , $\frac{1}{2}$ w resistors soldered to it each at 90° to its neighbors to form a less inductive load, approximating a resistive sheet. These resistors are

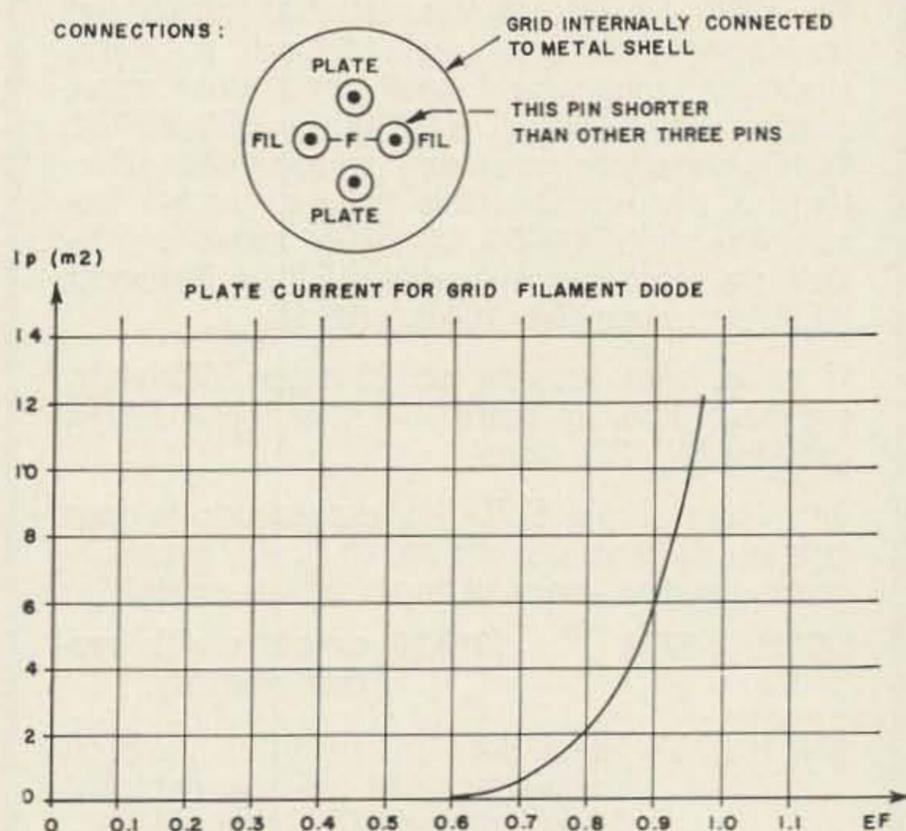


FIG. 3

Fig. 3. Connections of 708A and graph of relationship between "plate" current and filament voltage.

CHANCES ARE***

*** You are not making enough solid contacts or working as much DX as you should!

*** You are picking up far too much QRM with your receiver!

*** Your transmitted signal hasn't got enough punch and is too broad!

You can solve them all by adding a **BAND FILTER** to your present rig!! **NOTHING ELSE LIKE IT ON THE MARKET!!**



The BAND FILTER processes all transmitted and received speech components through a unique miniature solid-state signal generator using, among other devices, a COLLINS MECHANICAL FILTER. Infinitely adjustable steep-skirted selectivity is one very desirable feature. Another feature, the PENETRATION CONTROL, makes a 200-watt rig sound like 1-kilowatt P.E.P.; a 2-kilowatt P.E.P. rig sound like 10-kilowatts!!

If you've been listening on 20-meter SSB lately, you have probably heard what the BAND FILTER does for WINVY's signal.

Only three simple EXTERNAL connections to your present rig and it's set to go!! All necessary cables supplied—no soldering or drilling needed!!!

MODEL B-3234 \$319.00 complete with one-year warranty.

INTERESTED? Space does not permit a technical description here, so why not send \$2.00 for the INSTRUCTION MANUAL.

L. E. BABCOCK & CO., INC.

85 Nob Hill Drive

Framingham, Mass. 01704

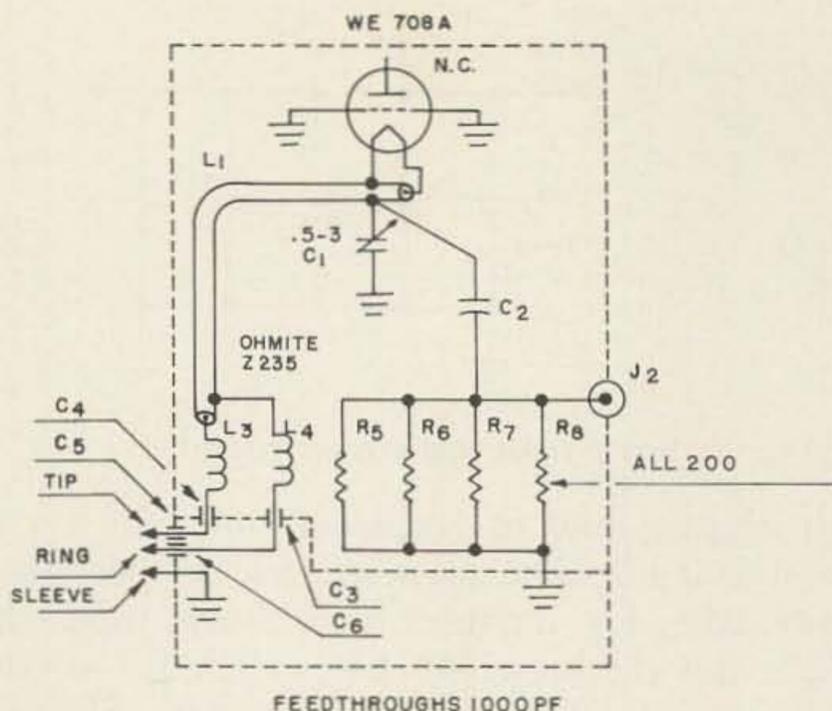


Fig. 4. Circuit of diode noise generator.

soldered to the UG58/U before it is mounted to the aluminum sheet to make soldering easier (less heat required). Then L_1 is formed and soldered from the WE 708A filament pin to C_3 . The center filament lead of L_1 is fed through and soldered to the other filament pin and to C_4 . C_2 is then soldered in; be sure this is the type called for or a similar low inductance stand-off ceramic. The rest is straight forward. Diode and power supply were each built in an LMB 141 box chassis. The details of wiring the diode circuitry are shown in Fig. 4.

A word about R_1 (the "fine" adjust) is worthwhile. Make sure this one is a 2w type A.B. (ohmite) molded carbon pot, if not both R_1 and R_2 . This will make smooth diode-plate current adjustment easy; a wire wound pot will cause the plate current to vary in steps because of the effect of the pot's sliding contact sequentially contacting each wire (the same applies if you use a Variac).

To align on 432 mc, C_2 is temporarily removed and a UHF grid dip meter coupled to L_1 , loosely. C_1 is adjusted for a dip at 432 mc. Then C_2 is reinstalled, and we should be ready for receiver checks.

The above noise generator was compared with a Hewlett Packard 343A noise diode using my own 432 mc converter as the "to be measured" device. The results showed less than 0.5 db difference.

The author wishes to thank Gene Howell, W4RLU, for his photography of the unit.

. . . W6GXXN

Bibliography

1. Jones, F. "V.H.F. For the Radio Amateur," C.Q. Technical Series, p. 178-184.
2. Goodman, B. "How Sensitive Is Your Receiver," Q.S.T., Sept. 1947, p. 13.
3. Geisler, D. T. "Reviewing The Radio Classics," C.Q., June 1963., p. 40.



The revolutionary Davco DR-30 all-transistor communications receiver offers the ultimate in versatility and performance for the ham in a compact package, yet draws less current than a single filament in old fashioned tube-type receivers.

- ✦ COMPLETE COVERAGE
 - ✦ MAXIMUM SENSITIVITY
 - ✦ EXTREME STABILITY
 - ✦ OPTIMUM SELECTIVITY
- and the greatest versatility ever provided.

WHAT ARE YOUR OPERATING REQUIREMENTS?

Whatever the mode, whatever the bands, whatever the conditions of noise and interference and weak signals, you'll find your needs met without compromise in the **solid-state** DAVCO DR-30 receiver. Sure, it takes 25 transistors, 15 diodes, 14 crystals, a Collins mechanical filter and much else, but check the specifications: the DR-30 simply does things no other unit can do! This sensational performer gives you the circuitry and features to let you use every bit of your operating skill on the really challenging contacts, and makes the routine ones simpler than ever. And use it anywhere, mobile or fixed; the unique capabilities of the DR-30 make it your very best investment in superb communications equipment.

Available direct from factory; insured shipping included. A time payment plan is available.

\$337.50

DAVCO ELECTRONICS

Post Office Box 2677
2024 South Monroe St.
Tallahassee, Florida
Phone 305-224-4322

Send for free brochure explaining all of the features of this unique receiver.

- COVERAGE** — Every kc. of 80, 40, 20, 15, 10 meters plus 50.0 - 50.550 Mc. (6 meters) plus WWV at 10 Mc. plus expanded coverage for MARS, etc. plus two more 550 kc. segments YOU can choose
- SELECTIVITY** — 2.1 kc. Collins Mechanical Filter for SSB plus 200 cycle ultra-sharp crystal filter for CW plus broad IF position for AM
- STABILITY** — crystal first conversion oscillator (10 crystals supplied) plus transmitter-type tuning VFO plus crystal BFO-carrier generator plus a new concept in extruded aluminum chassis design for the most rigid construction available
- SENSITIVITY** — .6 microvolt sensitivity, with tuned RF stage using premium UHF-type transistor (2N2495, with rated noise figure of 3db at 50 Mc.)
- PLUS**
 - tunable rejection-notch filter for eliminating heterodynes
 - and blanking-type noise limiter (preselectivity)
 - and built-in 100 kc. crystal calibrator
 - and split-gear ball-bearing tuning mechanism
 - and separate AM and product detectors
 - and plug-in module subassembly construction
 - and new expanded warranty; designed and manufactured in USA
 - and transceive compatibility with companion DT-20 200-watt SSB transmitter
 - and size (1/10 cubic foot) and weight (nine pounds); installs anywhere

SIDEBAND ENGINEERS'

new! SB34


COMPLETE, SELF-CONTAINED,
4-BAND (80-40-20-15) SSB TRANSCEIVER,
NEEDS ONLY MIC., ANTENNA, POWER SOURCE.




12V DC / 117V AC POWER SUPPLY IS BUILT-IN!

Connect the equipment directly to the 12 volt vehicle battery... or plug it into the 117 volt AC wall outlet. (Two power cables are provided—one for AC—a second for DC operation).

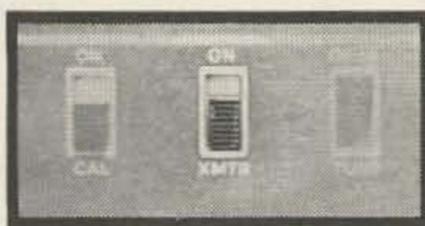ONLY 500 MILLS
STANDBY DRAIN FROM
VEHICLE BATTERY



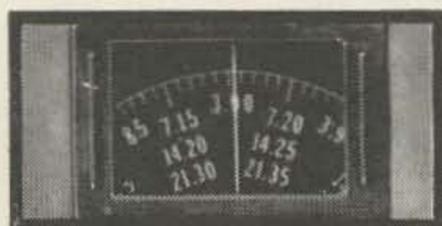Drain-saving panel switch turns off transmitter tube filaments and power supply for casual listening.



EXPANDED FREQUENCY COVERAGE

250 kc, 80-40-20-15, with overlaps covering MARS, out-of-band DX.




DELTA RECEIVER TUNING

Receiver is tunable several kilocycles \pm transmitter frequency.



SOLID-STATE DIAL CORRECTOR

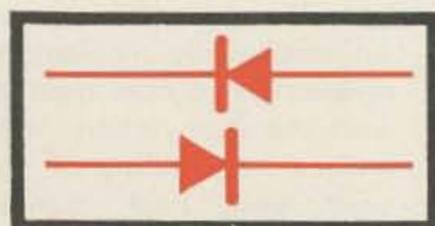Varactor circuit sets transmitter frequency to dial calibration.



SOLID-STATE SWITCHING

Receive to transmit switching is all solid-state. No troublesome relays. **A breakthrough!**

OTHER FEATURES: SINGLE-KNOB, DUAL-SPEED TUNING • LOW FREQUENCY DRIFT • VOX AND 100 KC CRYSTAL CALIBRATOR AVAILABLE AS ACCESSORIES. (SB-34 is pre-wired to accept VOX and Calibrator—has receptacles on rear of the chassis for this purpose).

SBE

SIDEBAND ENGINEERS 317 ROEBLING ROAD, SOUTH SAN FRANCISCO, CALIF.

SBE

SB-34 ... FEATURE-WISE, DOLLAR-WISE, THE BIGGEST SSB TRANSCEIVER VALUE ... EVER!




Photograph shows home station installation of SB-34 with matching amplifier.

Now...from **SBE**...a completely new SSB transceiver, **SB-34**. All of the design features introduced originally in the SB-33, and now well proved, have been retained...and an entirely new series of "plus performance" features have been added. SB-34 is handsome equipment—conservatively styled, attractively appointed...comes in a physical "package" even smaller than SB-33. Transistors and diodes replace vacuum tubes throughout except in RF driver and Final Amplifier stages for substantial reduction in current drain—cooler operation—long life expectancy.




Suggested price. (Including built-in AC/DC power supply)

\$395

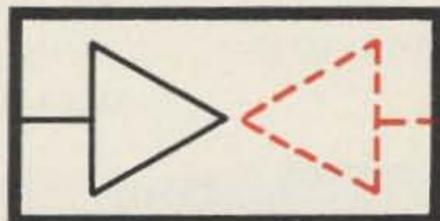

BI-LATERAL MIXERS/AMPLIFIERS

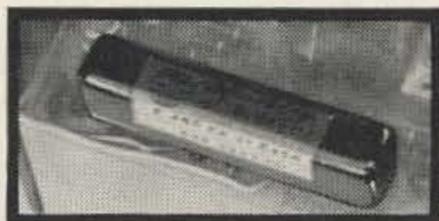Same transistors operate both transmit/receive by switching direction of amplification.




COLLINS MECHANICAL FILTER

Used both transmitter and receiver—gives steep slopes...clean, sharp transmitted sigs.



PANEL SWITCH SELECTS USB or LSB

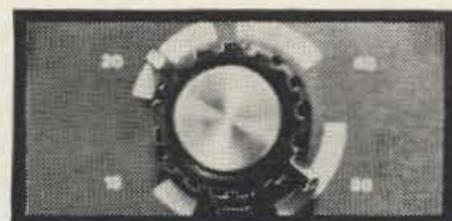Sidebands are locked to carrier—no dial shift.



SIMPLE TUNE-UP AND OPERATION

One knob controls band-switch/exciter tuning.

HIGHLIGHTS: 135 watts p.e.p. input (slightly lower on 15). **Freq. range:** 3775-4025 kc, 7050-7300 kc, 14.1-14.35 mc, 21.2-21.45 mc. 23 transistors, 18 diodes, 1-zener diode, 1-varactor diode, 2-6GB5's PA, 1-12DQ7 driver. **Speaker**

SBE 317 Roebling Road, South San Francisco, Calif.
Please send data sheet on **SB-34** transceiver

NAME _____

NUMBER STREET _____

CITY _____ ZONE _____ STATE _____

The KWS-1 as an SSB Exciter for VHF Heterodyne Converters

Judging by the number of SSB signals now coming up on the VHF frequencies, this is rapidly becoming one of the most popular modes of operation. SSB can do on VHF and UHF what it has done on the lower frequencies: provide more reliable extended range communications. Most transmitting converters marketed are designed for low power exciters, with the higher power ranges requiring attenuation. The KWS-1 is still at the top of the art for high quality SSB, but the high cost of this transmitter has discouraged most experimenters from modifying it.

It is possible to extract the required low level SSB from the KWS-1 on the band of your choice without drilling any holes or soldering internal connections. The attachment may be removed at any time without signs of ever having been present!

The left rear of the rf cabinet has a large plug button which can be removed. It was placed there should it be necessary to remove the band change switch shaft. Note the "before" photograph where the shaft extends above and between the plate coils of the parallel 6CL6's which are the rf drivers to the final 4CX250B's. This photograph was taken with the bottom pan of the chassis removed. To make room for the coax jack the shaft must be shortened. The shaft is of a non-brittle laminated fibre and saws easily with a hack saw


blade. Not much need be removed, about 1½ inches will do. Removing this piece will not interfere with the original purpose of the hole behind it.

The "after" photograph shows the shaft end removed and the coax plug mounted in the shaft removal hole. Either the UG-1094/U or the UG-625/U single hole mount female sockets fit the original hole perfectly. The mating plug for this is the commonly used BNC connector.


A two turn link is wound around the coil of your choice as shown in the photograph. Some converters call for a 14 mc input, and others for 28 mc. It must be remembered that the direction of wind is the same as the original coil, and that it is placed adjacent to the cold side of the coil which is nearest the chassis pan. The "coldest" end of the link goes to a lug placed under the coax socket nut for a ground and the hot side to the inner conductor of the coax socket.

No retuning of the 6CL6 coils was found necessary, and when this exciter function is desired, the KWS-1 high voltage plate switch is turned off, and 4CX250B filament fuse is removed. When you return to normal HF operation, simply return the fuse and remove the coax plug. That is all there is to it.

... W4API

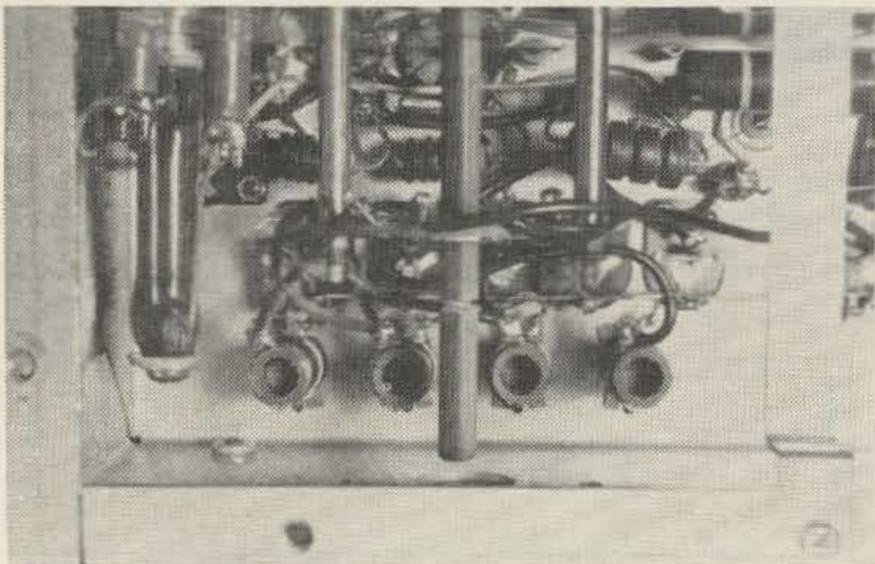

KWS-1 before modification.

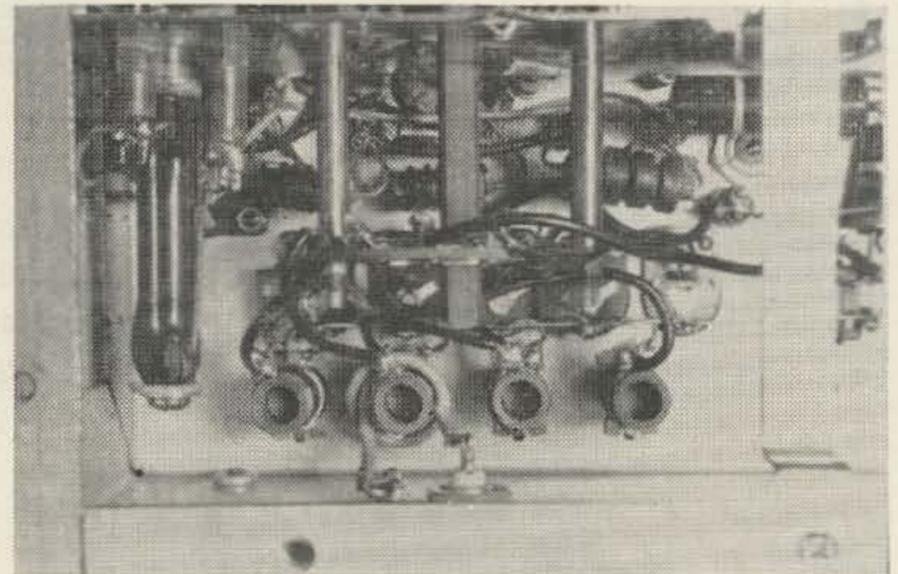

KWS-1 after modification.

KWM-1 on LSB

One of the finest values in used equipment on the market today is the KWM-1 selling for about \$300 to \$350. It is, without a doubt, one of the most rugged, sensitive transceivers ever built. It has a couple of faults, it covers only 10-15 and 20 meter bands, but the sun spot cycle will be bringing back the 10 and 15 meter bands in a couple of years. The other is its inability to operate on lower side-band when the QRM gets tough, this can be easily corrected.


With apologies to Louis Weber, K6GHU, (P. 60 December 1963, 73 MAG), and his excellent article on the KWM-1, I for one always hesitate to actually modify a mfrs. outfit, but Mr. Weber did give me an excellent idea on how to work my KWM-1 on lower side-band without any modifications. First remove the B.F.O. XTAL (the one up front near the P.T.O.) and check its frequency. Next, subtract 455kc from the crystal frequency. Take this remainder from 455kc and you have the frequency of the XTAL you need to get on lower side-band.

As Mr. Weber pointed out, the crystal must be calibrated to .01% as measured into 32 mmfd input capacity. To go on lower side-band, all you have to do is change crystals. I took a piece of Polystyrene rod about 3" long and 1/2 inch in diameter and notched each end so the XTAL's just fit into the notches.

With a couple of turns of "scotch" tape to hold the XTAL's in place in their notches, and a small cork on the top XTAL to hold it firmly in place, when the lid is lowered, it's not much of an effort to lift the lid—remove the cork, swap the rod end for end to insert the other crystal, put the cork back on the opposite crystal and close the lid. The dial will tune off frequency about 3kc from where it normally tunes. I obtained my crystal from R. E. Woods Electronics, 2164 North Parkway Drive, El Monte, California.

. . . W3AQY


INCREASE RANGE AND QUALITY

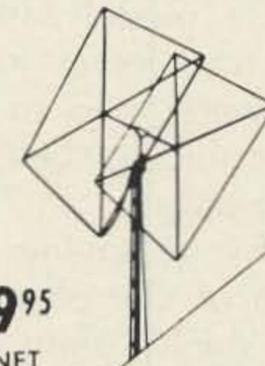

39⁹⁵
NET


CB-5 GROUND PLANE
Half wave gives more gain than 1/4 wave without bulky transformers. SPECIFICATIONS: VSWR (50 ohm cable) 1.3:1 • Bandwidth (under 2.1 VSWR) ± 4%
• 750 watts max. power input
• 50 ohm nominal input imp.
• Intl. feedline RG-8A/U
Termination SO. 239

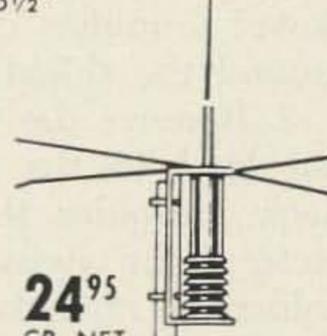**Giant Q-11
BASE STATION
CUBICAL QUAD**
For Class D, 27-mc operation
Light but rugged, it increases CB range. SPECIFICATIONS: 8 db Forward Gain; 40 db Front to Back; 52 ohm coax Feed; horizontal or vertical polarization; Longest Element, 9'3"; Boom, 65 1/2"



24⁹⁵
CB NET

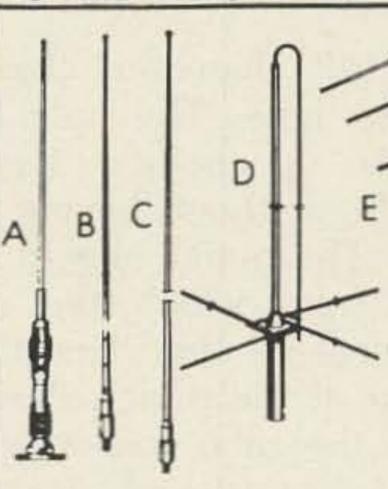**NEW AM-106 BASE STATION. 3/4 WAVE
Ground Plane — 3.7 DB Gain. Net . . . 34⁹⁵**



**MMM-75
MOUNT
7⁹⁵
NET**

**GUTTER
MOUNT
CG-275
7⁹⁵
NET**

**UNIVERSAL
MOUNT
TM-1
4⁴⁵
NET**

A CB-1 Air Sentry "Shorty" — 23" overall with 18" whip — top loaded fiberglass — complete with spring, mount and 12 ft. coax cable. For auto CB use. **10⁹⁵**

B CBS-311 mounts on top, fender or trunk lid. 52 ohms, 60 watts, RG 58 or equiv., 1.5 mc min., 1.1 to 1 at resonant frequency. For auto, plane or boat. **5²⁵**

C FG-103 universal 103" fiberglass whip with 3/8" x 24 thread base fitting. **6⁹⁵**
(Not Shown) 100-1035 Stainless Steel 103" whip with 3/8" stud threaded to fit all mounts. **6⁹⁵**

D SR-600-11 base station monopole for 11 meters. Radiating and ground plane elements grounded to reduce lightning damage. Write for specs. **24⁵⁰**

E SR-500-11 3-element beam antenna with power gain approx. 2 1/2 (8DB) in forward direction — about 10 to 1 interference reduction from sides and rear. Handles up to 1 Kw input. 11 Meters **24⁹⁵**

**SEND FOR "ANTENNA BUYER'S GUIDE"
with over 200 Antennas. It's FREE!**

Master Mobile Mounts

DEPT. 73
4125 W. JEFFERSON BLVD.
LOS ANGELES., CALIF. 90016
AREA 213, 731-2251



DIVISION OF

200 watts with a Swan 240

The Swan Engineering Co. model 240 is a 3 band (3.8-7.2-14.2 mc) transceiver capable of a SSB output of 100 watts pep or more. Adding another 6DQ5 or replacing the 6DQ5's with 6HF5's can double the output.

1. Remove the cover by removing the 3 metal screws on each side of the chassis; remove the screws on the shield plate of the power amplifier cage; remove the back wrap around the shield across the rear of the unit.

2. Remove the 6DQ5 tube and unsolder the red lead to the small capacitor on the PA deck; unsolder the brown-white lead to the meter light above the 0-400 ma meter; unsolder the rf choke that runs from the terminal strip on the chassis to the tube socket; remove the 2 6/32 bolts and nuts that retain the socket.

3. Use a Greenlee 1 1/8" diameter chassis punch to punch the new hole. The hole for the new socket should be up enough to permit insertion of the tube without having to file off part of the base. The punch should be positioned in the hole from which the red lead was removed, as near to the chassis as possible. The female part of the punch should be in the PA cage and the tube socket with the components should be positioned clear of the male part of the punch; use a 7/16" open end wrench to turn the socket punch bolt.

4. Position the socket in the new hole and use a #27 drill to make the new holes for the socket mounting. *Caution!* Use a smaller size drill to start the hole or the bit may damage the components by drifting off the center punch indentations. Remount the socket and insert the 6DQ5 to check for any errors.

5. Punch a 2nd hole and drill the mounting holes and mount the 2nd (upper) tube socket.

6. Resolder all of the leads and lengthen them as necessary. Check the instruction book schematic and parallel the necessary pins from the lower tube socket to the upper tube socket (except the filament wiring). Connect 20 watt resistor in series with the upper tube filament pins, grounding one side and dressing the lead to the rear of the 12 volt filament supply and the male power plug. Add another braid and plate cap for the upper tube. Replace all the shields, blow out all of the metal crumbs, and check the dress of the added wiring against the pin numbers of the schematic for additional confidence.

7. Connect a power supply of 800/900 vdc @ 400/600 ma. Adjust the bias to the proper level—25 volts. Place a 1% resistor across the meter terminals so the meter reads 400 ma at half scale (200) (Total current is then meter reading times 2). Tune up the xmtr into dummy antenna on the 75 m position, with a Micromatch and Termaline preferred. Check the neutralization as in the book. Adjust the loading as usual except limit the current to 225 ma per tube instead of 275 ma.


8. Connect an outside antenna and with normal speech your Micromatch should peak to 200 on a short sustained ahhhh which is a good healthy signal on any man's band. Values of resistances for the filament circuit and meter shunt have purposely been omitted to give the reader a lil' mental exercise.

. . . KØIEG/6

SB-33 on MARS

I imagine there are at least a couple of guys interested in 4.025 mc MARS operation with their SB33's. The modification is simple, easy to do, has only six parts and it does a good job.

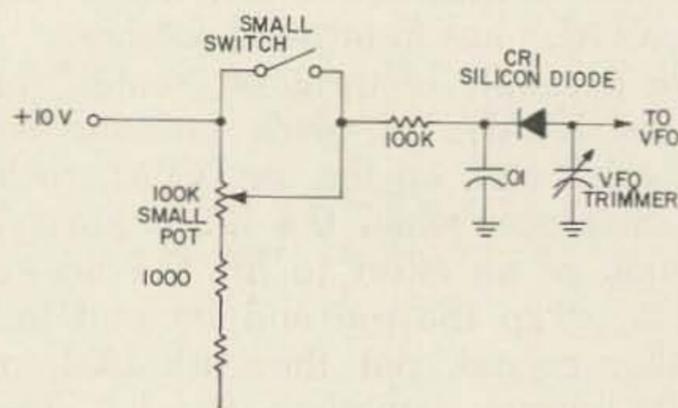The small toggle switch, a Unimax Sub Miniature Snap Acting Switch #1SB-1, is mounted in the upper left hand corner of the front panel just above the dial plate. The silicon diode can be almost any standard type, a 1N456 does a good job.



1. Close S1 adj vfo trim to 4 mc
2. Open S1 set dial to marker past 4 mc
3. Adj pot until 0.025 zeros in on marker past 4 mc

. . . W6PDD

SERVICE TESTED EQUIPMENT



ORDERS PREPAID WITH CASH REMITTANCE IN CONTINENTAL U. S.

RECEIVERS

Collins 75S1	\$369.00
Elmac M-1070 P/S	49.00
Elmac PMR-6A	39.00
Gonset G66	69.00
Gonset G66B	79.00
Gonset 3 way P/S	15.00
Gonset Super 6 Convertors	19.00
Hallicrafters S-85	65.00
Hallicrafters SX-62A	249.00
Hallicrafters SX-99	84.00
Hallicrafters SX-101A	189.00
Hallicrafters SX-111	169.00
Hammarlund HQ129X	85.00
Hammarlund HQ145	199.00
Hammarlund HQ170C	209.00
Mosley CM-1 w/spkr (like new)	129.00
National HRO-60 (w/5 coils)	239.00
National NC-60	39.00
National NC-173	75.00
National NC-183-D	179.00
National NC-270 (like new)	165.00
National NC-300 w/calib.	189.00
National NC-303 w/calib.	259.00
RME 4350A	129.00
RME 6900	189.00
RME DB-23	27.50

TRANSMITTERS

B & W 5100	\$139.00
B & W 5100 w/51SB	269.00
B & W LPA-1 Linear	229.00
CE 20A (factory-wired)	119.00
CE Deluxe 458 VFO (160-15M)	29.50
CE Comp. AMF GC-1	38.00
CE Slicer Model "B"	27.00
CE Q-Multiplier #DQ	17.00
Collins 30L-1 Linear	375.00
Elmac A-54H	29.00
Elmac AF67	49.00
Globe AT-4 Matchbox	34.00
Globe LA-1 Linear	59.00
Gonset GSB-100	199.00

Hallicrafters HT-32	269.00
Hallicrafters HT-32B (like new)	539.00
Hallicrafters HT-37	265.00
Hallicrafters HT-40	65.00
Heath "Apache"	159.00
Heath DX-40	39.00
Heath DX-60	75.00
Heath DX-100	95.00
Heath HA-10 Warrior	219.00
Heath MT-1	49.00
Johnson "Challenger"	55.00
Johnson "Valiant"	199.00
Johnson "Courier" (like new)	219.00
Johnson "Pacemaker"	179.00
Johnson "Navigator"	99.00
Johnson Desk "Kilowatt"	595.00

TRANSCEIVERS

Galaxy III (demo)	\$299.00
Gonset G-76	199.00
Hallicrafters SR-150	459.00
Hallicrafters SR-150 AC P/S	75.00
Heath HW-22 (like new)	125.00
National NCX3 (like new)	275.00
SBE SB-33 (demo)	269.00
Swan SW-120	159.00
Swan SW-140	159.00
Swan SW-175	159.00

VHF EQUIPMENT

Clegg "Venus"	\$459.00
Clegg "Interceptor"	339.00
Gonset Comm II 2M (clean)	129.00
Gonset Comm II 6M	99.00
Gonset Comm III 2M	189.00
Gonset Comm III 6M	159.00
Gonset Comm IV 2M	279.00
Gonset Comm IV 6M	229.00
Gonset Comm 6M Linear	99.00
Gonset Model 3112 (220 Mc)	219.00
Johnson 6N2 Xmtr	109.00
Lafayette HE45B	99.00
Lincoln 6M Transceiver	59.00
Poly-Comm-6	259.00
Poly-Comm 6-2 Transceiver	239.00

**ORDER
TODAY**

MISSION HAM SUPPLIES

3316 Main Street
Riverside 3, California 92501
Phone 683-0523 (area code 714)

MISSION HAM SUPPLIES
3316 Main Street, Riverside 3, Calif. 92501

Attn: Bill Hullquist, K6LOS, Please Ship me the following:

\$ _____ enclosed. (Cash orders shipped FREE in continental U. S.)


- QUOTE trade allowance and terms.
 Please send latest HAM flyer.
 Put me on your mailing list.

NAME _____ Call _____
(please print)

Address _____

City _____ Zone _____ State _____ Zip _____
(Calif. orders add 4% tax)

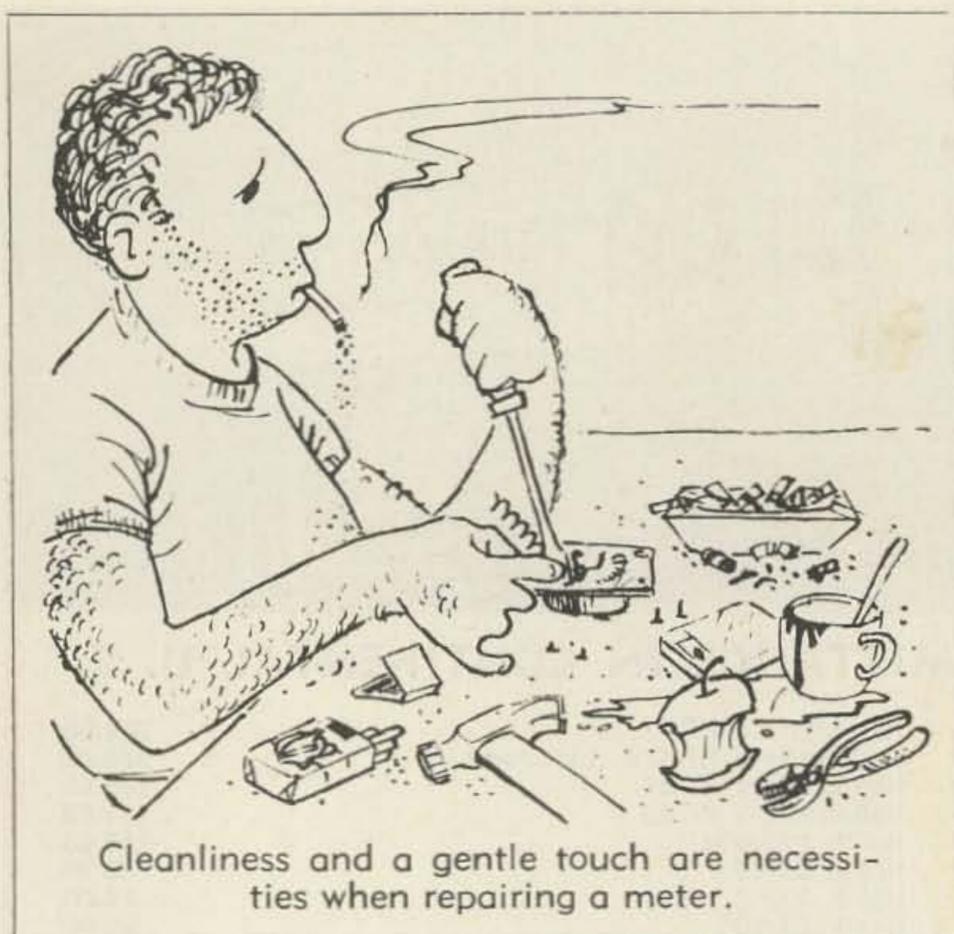Jack Bayha W8BPY
1475 Wilson Mills Rd.
Chesterland, Ohio



Cartoons by Wayne Pierce K3SUK

Amateur, Spare that Meter . . .

There are probably no pieces of electrical equipment so widely used and so little understood as common D'Arsonval meter. Most amateurs use them continually without very much thought as to how they work, and how to get the most out of them. Wide misconceptions exist about many aspects of meter usage, durability, etc.

Most well-designed units can stand a 1000% overload without suffering mechanical damage, although with ac units, rectifier damage may occur. Meters with target type pointers are, of course, less able to withstand severe overload rapidly applied. The movement upscale has very little likelihood of damaging the target pointer, but the sudden stop at the end of the travel on a suddenly applied overload is quite another thing. The target's mass may bend the pointer.

Mechanical damage by dropping is quite common, and needs no discussion.

Poor location of meters in equipment is something few amateurs consider. The meter's accuracy is entirely dependent on the flux value in its gap. While the meter designer uses material of high stability, demagnetizing can, and does occur. It is customary in a meter factory to make all units about 10% more

sensitive than required. This excess sensitivity is then removed by deliberately "aging" or demagnetizing the flux producing element.

This "aging" stabilizes the magnet and assures reasonable lack of susceptibility to further flux reduction under normal conditions. Close proximity to a strong ac field, such as that produced by a motor or transformer, is not considered as "normal." Slow deterioration may occur with resultant loss in meter sensitivity and calibration error.

The use of a soldering gun in close proximity to the magnet will also cause slight flux loss due to the very high ac field present. With a properly aged magnet this effect is very small.

The life of a meter can be badly shortened, if it is not a sealed unit, by environment. Overly humid storage may cause rusty pivots and resultant friction. Steel particles small enough to be airborne can actually accumulate, over a period of time, enough to cause sticking action.

Rough handling may not cause readily observable meter deterioration. Quite often it appears only in the form of friction. This can be detected by running the meter up scale slowly, stopping, then tapping the meter—the

amount of motion after tapping bring friction error. Rough treatment often causes minute pivot blunting with resultant friction. Friction is always more of a problem with more sensitive meters, as increased sensitivity is usually achieved in a design by increasing the amount of wire involved and the flux of the magnet structure, *and* by reducing the power of the springs. The added wire means more weight, the weaker springs less torque. Result: more friction. The added weight also makes pivots more subject to blunting, so it is necessary to handle high sensitivity meters carefully.


Considerable damage is done to meters by people with the best of intentions. It's bad enough to have overloaded a meter by over 1000%, but the real damage will occur when an attempt is made to straighten out the pointer. Usually such repair jobs come to grief, and there is great wonderment on the part of the amateur abruptly turned meter repairman. Why do meters always go bad when the most capable amateurs try to become repairmen?

The first disaster which will befall a meter with a bent pointer, occurs when the amateur sits down at his desk and takes the front off the meter. Unless a sheet of clean white paper was placed on the desk top prior to opening the meter, every tiny speck of steel trash in the area will jump at once into the meter. One almost invisible speck on the core will cause the meter to become "sticky."

So the meter that originally had only a bent pointer, now has an added built-in complication—a tendency towards stickiness.

If our friend did put a sheet of clean paper down, he probably forgot to demagnetize and wipe off all the steel chips from the needle nose pliers he's using.

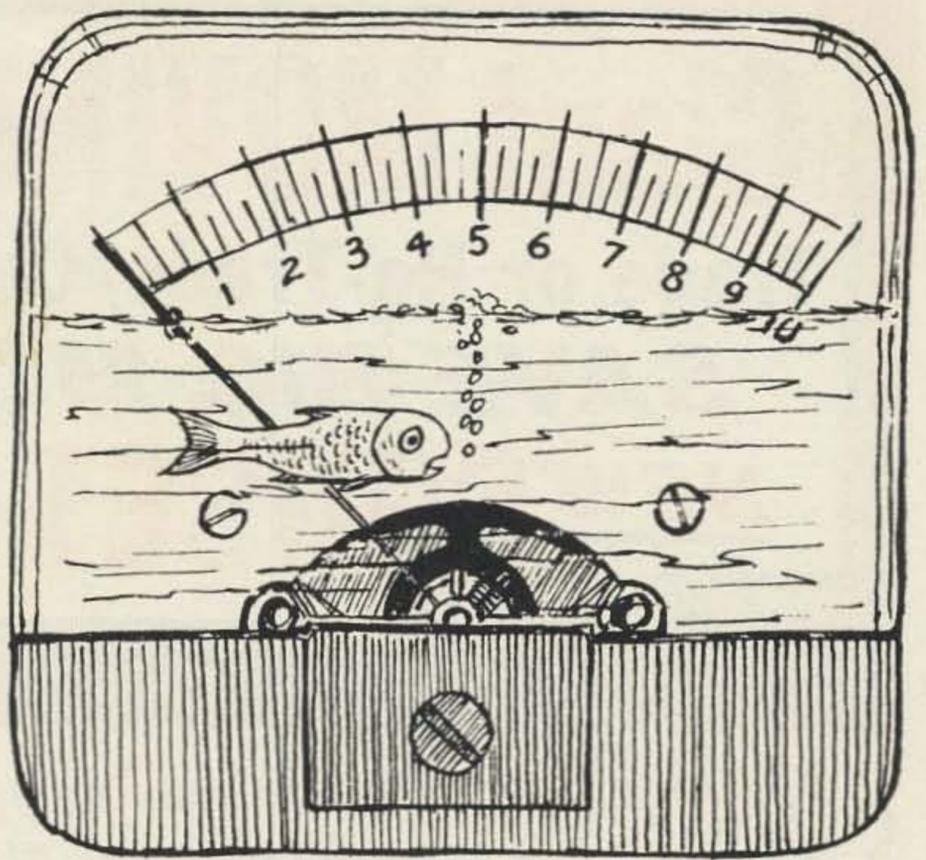If the meter survives thus far, the innate curiosity disease will surely set in. The first symptom of this is the observation, "Say, look at how they do this in this meter." It is natural to touch the point involved while making the observation. Such touching usually ignores the presence of the hair spring, and it gets bent. This seems to be no problem since in about



An overly humid atmosphere may cause deterioration of the meter . . .

half an hour we have it all straightened out, "as good as new," except we now have wrecked the linearity of the meter, as well as its calibration at end scale.

Oh yes, that pointer! With great aplomb it is straightened out. Of course, the meter is now off poise or balance, and won't read the same horizontal and vertical. This fault is usually not observed at first, although some fellows may wonder why the meter makers put those "silly springs" on the pointer base.

Just before the meter front gets put on for the last time, our friend will discover the little screw which adjusts the jewel. The usual reaction to this is to tighten it up just a "hair." The pointer won't wobble so much that way. Indeed, it will hardly move at all, due to the blunted pivot or pierced jewel caused by our repairman.

The front will go on for the last time now. Actually, it'll go on and off several times, since the zero adjuster usually will miss the slot. About this time it's discovered quite often that the meter won't go to zero. Remember the spring trouble and the poise?

A few minutes and cuss words later, our amateur places the meter at arm's length and admires his work.


. . . W8BPY

Telrex "BALUN" FED INVERTED "V" ANTENNA KITS

SIMPLE-TO-INSTALL, HI-PERFORMANCE ANTENNA SYSTEMS:

- 1 KW P.E.P. Mono-Band Kit... 1KMB1V/81K... \$19.95*
- 2 KW P.E.P. Mono-Band Kit... 2KMB1V/81K... \$22.95*

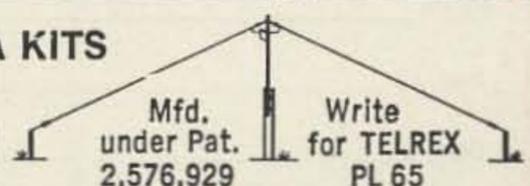*Kit comprises, encapsulated, "Balun," copperweld, insulators, plus installation and adjustment instructions for any Mono-band 80 thru 10 Meters. Also available 2, 3, 4, 5 Band Models.



Mfd.
under Pat.
2,576,929

Write
for TELREX
PL 65

TELREX LABORATORIES
ASBURY PARK, NEW JERSEY



Giant MOVING SALE!

Trade or No-Trade/Cash or Terms

**SAVE BIG MONEY on
NEW GONSET EQUIPMENT**



TERRY STERMAN
W9DIA
Proprietor

"We're moving soon to a bigger and better location, here in Milwaukee. At our present location we're bursting at the seams with Brand New Factory-Sealed Equipment. It would cost us too much to move our giant stocks—so . . . we're having this Giant Moving Sale, and passing the savings on to you. Until we move, we'll be trading wilder than ever. If you've been thinking about trading up to some New Equipment, now is the time to get our quote. You'll never get a better deal! Use handy coupon below! There is no obligation."

TRADE-IN Coupon

To: **STERMAN ELECTRONIC SUPPLY**
4828 West Fond du Lac Ave.,
MILWAUKEE, WISCONSIN 53216

I am interested in the following new items:

I have the following to trade:

Rush me your SPECIAL MOVING SALE TRADE-IN DEAL by return mail. I understand I am under no obligation.

Name _____

Address _____

City _____

State _____ Zip Code _____

Send latest Reconditioned Equipment Bulletin

We stock the entire
GONSET Line

**STERMAN
ELECTRONIC
SUPPLY**

4828 West Fond du Lac Ave.
MILWAUKEE, WISCONSIN 53216
Telephone (414) 442-4200

**NOTE: Our firm was formerly known as
AMATEUR ELECTRONIC SUPPLY**
We've changed the name . . . *THAT'S ALL!*

VISIT our Branch Stores, located at:
6450 Milwaukee Avenue | 19 Azalea Pk. Shopping Ctr.
CHICAGO, ILLINOIS | **ORLANDO, FLORIDA**
Phone (312) 763-1030 | Phone (305) 277-8231

LOOK at your low Monthly Payment AFTER JUST \$5⁰⁰ DOWN



RAY
K9KHW
Mgr. Mail
Order Dept.

"If you are considering purchasing, **WITHOUT TRADE**—either Cash or Financed—any **NEW Equipment, Antennas, Towers, or Station Accessories, etc.**—You will want to get our **Special NO-TRADE MOVING SALE DEAL**. You know that the Manufacturers would frown upon our advertising a Discount . . . So, tell us what you are interested in on the Coupon below, and we'll call you Long Distance (at our expense), to let you know how we can save you **BIG MONEY**. You are under no obligation! Sorry, we cannot accept Collect Calls—we'll call you."

GONSET		
9000A	2m Sidewinder (SSB, AM, CW) Xcvr..	(14.26) \$399.50
901A	AC Power Supply for 900A.....	(2.25) 73.50
902A	DC Power Supply for 900A.....	(- 2.70) 79.50
903A	500 Watt 2m Linear.....	(10.65) 299.00
910A	6m Sidewinder (SSB, AM, CW) Xcvr..	(14.26) 399.50
911A	AC Power Supply for 910A.....	(2.52) 73.50
912A	DC Power Supply for 910A.....	(2.70) 79.50
913A	500 Watt 6m Linear.....	(10.65) 299.50
3341	2m Communicator IV 12VDC + 117VAC	(14.62) 409.95
3342	6m Communicator IV 12VDC + 117VAC	(14.62) 409.95
3409	Civil Defense Kit for Comm. IV.....	(2.16) 64.95
3363	Canvas Carrying Bag.....	12.95
GA-138	108-138mc Xcvr Aircraft.....	(17.51) 489.95
3362	Civil Air Patrol Kit.....	(1.62) 49.95
3357	2, 6, + 1 1/4 meter VFO.....	(3.06) 89.95
3340	GSB-201 10-80m Linear.....	(12.27) 345.00
3221	G-50 6m Xcvr, 117VAC.....	(13.00) 367.30
3300CD	G-50 (CD Version).....	(13.90) 389.95
3448	5DB RF Attenuator.....	10.79
3449	10DB RF Attenuator.....	10.79
3450	15DB RF Attenuator.....	10.79
3365	Mobile Mtg. Brackets.....	4.26
3350	Ceramic Microphone.....	13.60
621-018	Telescoping Antenna.....	3.30



The above monthly payments are shown for \$5.00 down—regular price—no trade—for 36 months.

Of course if you purchase during our **GIANT MOVING SALE—Trade or No-trade . . . your monthly payments will be less.**



One of 1965's hottest products
NEW GONSET 500 WATT LINEARS
for 2 and 6 meters
\$299.00

NO-TRADE Coupon

To: **STERMAN ELECTRONIC SUPPLY**
4828 West Fond du Lac Ave., 7
MILWAUKEE, WISCONSIN 53216

I am seriously considering purchasing the following new equipment without trade-in:

I understand you will phone me long distance (at your expense) and tell me how I can save money during your MOVING SALE:

My home phone # is: _____

My phone # at work is: _____

Best time to call: _____

Best time to call: _____

My area code is _____

Name _____

Address _____

City _____

State _____

Zip
Code _____

Send latest Reconditioned Equipment Bulletin

Transistor RF Power Amplifier Design

The amateur will find solid state circuitry desirable in many transmitter applications such as oscillators, frequency multipliers and power amplifiers. Though there are similarities in tube and semiconductor circuit design, there are also very important inherent differences between transistors and vacuum tubes which must be taken into account in circuit design. Unlike vacuum tubes with high input and output impedance, the transistor is a low impedance device. The input impedance, which is dependent on frequency, may be as low as ten ohms. Collector output impedances in the fifty to one hundred-ohm range are often encountered.

Transistor circuits require crystal controlled oscillators for maximum frequency stability. Since the output frequency is often much higher than the oscillator frequency, several stages of frequency multiplication may be required.


The number of amplification stages required to obtain a specified output power is a function of the power gain of the transistor. The gain in turn is a function of frequency, supply voltage, circuit configuration, class of operation and drive power.

Operation of low level stages in class B or C is inefficient and results in low power gain since drive power is necessary to turn the device "on." Therefore low level stages can be operated in class AB. However, for high drive level, class C operation is preferred because of the high efficiencies which can be obtained.

The goals to achieve in class C amplifier design are high dc efficiency, large power output and low drive power. As is generally the

case, some compromise is required to attain these goals.

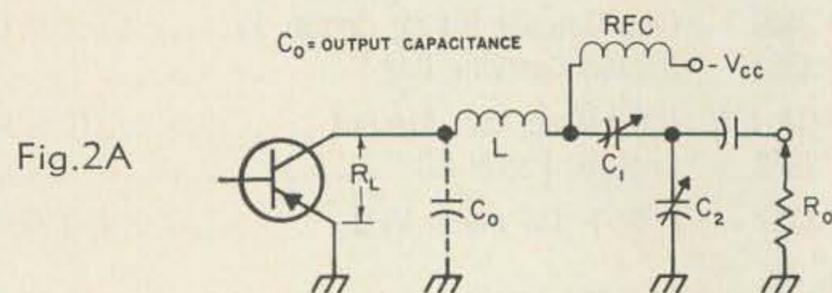Both common emitter and common base circuits are used for rf power amplifier designs. The choice is influenced primarily by operating frequency, power gain and desired bandwidth.



Tank Circuit Design

The amplifier's output tank circuit must supply a proper load impedance and must not consume too much of the amplifier's power. At the same time the output tank circuit efficiency should be high.

Usually the dc supply voltage is known in addition to the desired power output. The load impedance that the collector will see may then be calculated from equation (1) (neglecting $V_{CE\text{ sat}}$).

$$R_L = \frac{(V_{CC})^2}{2 \cdot P_O} \quad (1)$$

V_{CC} = collector supply voltage.
 P_O = power output in watts.

Fig. 1 is a schematic of the familiar Pi network. The formulas for calculating the reactive components C_1 , C_2 , L and the value of R_L are as follows, assuming $V_{CC} = 15\text{v}$, $P_O = 0.5$ watts, and Q_L (loaded Q) = 5, $R_O = 50$ ohms:

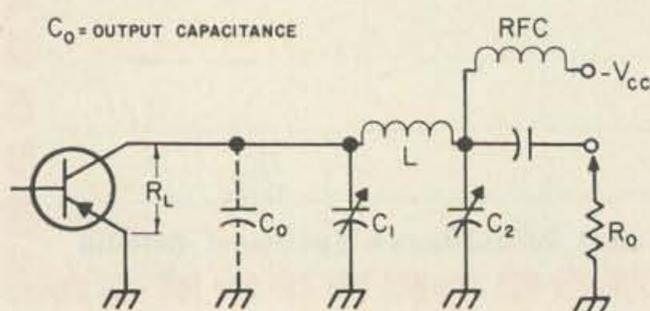


Fig. 1

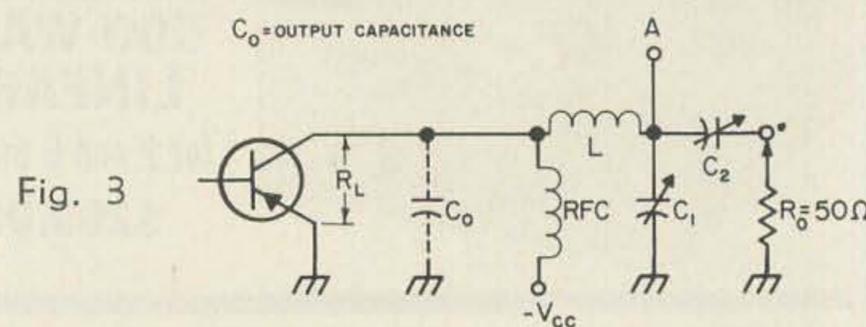


Fig. 3

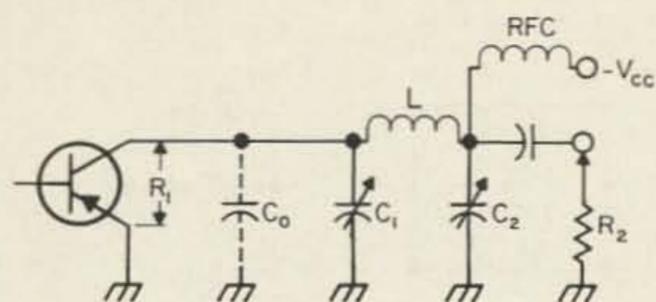


Fig. 4A

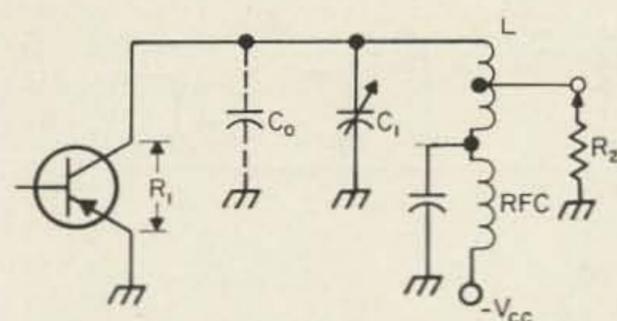


Fig. 4B

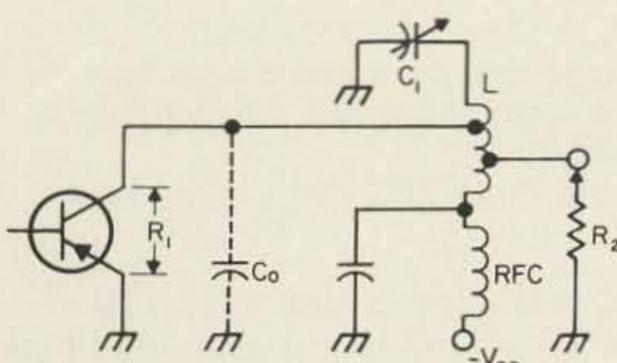


Fig. 4C

$$1. R_L = \frac{V_{CC}^2}{2 P_O} = \frac{(15)^2}{2 \times 0.5} = 225 \text{ ohms}$$

$$2. X_{C_1} = \frac{Q_L}{R_L} = \frac{225}{5} = 45 \text{ ohms}$$

$$3. X_L = X_{C_1} = 45 \text{ ohms}$$

$$4. X_{C_2} = R_O \sqrt{\frac{R_L}{R_O (Q^2 + 1) - R_L}}$$

$$= 50 \sqrt{\frac{225}{50(5^2 + 1) - 225}} = 23 \text{ ohms}$$

The values of the reactive components are calculated as indicated for Fig. 1.

The Pi network is desirable in applications in which feed-through of subharmonics is of no consequence. In many cases, however, in which the operating Q of the matching network is very low the T network shown in Fig. 3 will better meet the needs of the problem. In such a circuit, the loaded Q is increased by raising point "A" to an impedance level of 1 k ohm (or more) and then transforming down to the 50 ohm output impedance. Tuning to resonance is accomplished by means of C_1 ; loading is accomplished by means of C_2 .

Assuming $Q_L = 5$, $R_L = 75$ ohms and R_O is the output load, the values of the components of the T network can be calculated in following manner:

$$1. R = R_L(Q_L^2 + 1) = (50)(5^2 + 1) = 1300 \text{ ohms}$$

$$2. X_1 = \frac{R}{Q_1} = \frac{R}{Q_L} = \frac{1300}{5} = 260 \text{ ohms}$$

$$3. Q_2 = \sqrt{\frac{R}{R_L}} = \sqrt{\frac{1300}{75}} = 4.2$$

$$4. X_2 = \frac{R}{Q_2} = \frac{1300}{4.2} = 310 \text{ ohms}$$

$$5. X_L = Q_2 R_L = 4.2(75) = 315 \text{ ohms}$$

$$6. X_{C_2} = \frac{R_O}{Q_1} = \frac{50}{5} = 10 \text{ ohms}$$

$$7. X_{C_1} = \frac{X_1 \cdot X_2}{X_1 + X_2} = \frac{260(310)}{260 + 310} = 140 \text{ ohms}$$

Interstage Couplings

The input network of the following amplifier must provide coupling between the driving source and the base to emitter circuit. In most applications, the load impedance of the driving stage is much higher than the input impedance of the amplifier. The input impedance must therefore be "transformed up" to the correct load impedance value for the collector circuit of the driver stage. Several circuits which will provide matching between the collector and

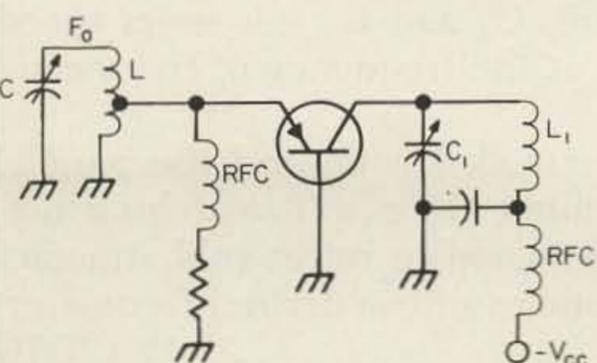


Fig. 5

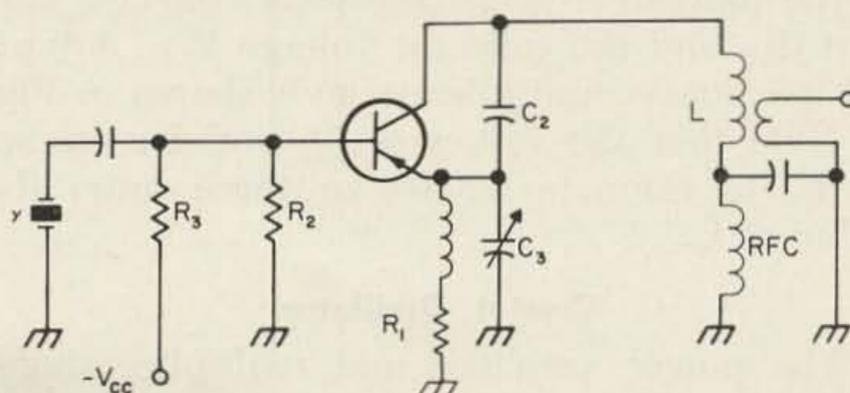


Fig. 6

L RESONANT TO XTAL FREQUENCY

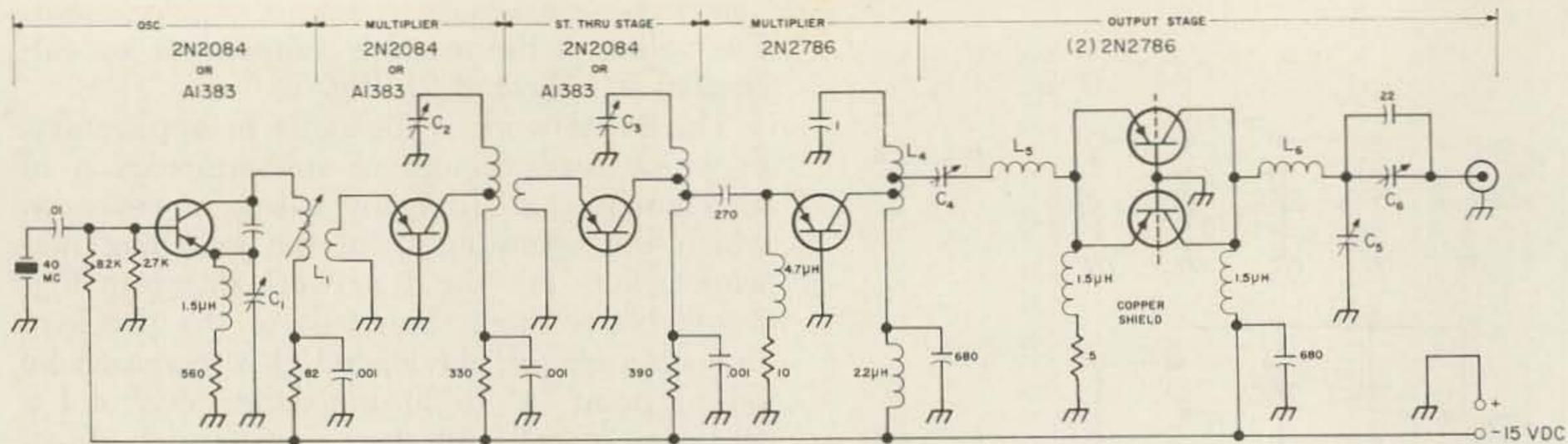


Fig. 7

- L1, 7T #20E 1/4" dia. close wound, 2T link #24 insulated at cold end
 L2, 6T #18 bus bar, 5/16" dia. 1/2" long, tap 3T from ground link, 2T #24 Ins.
 L3, 6T #18 bus bar, 5/16" dia. 1/2" long, collector tap 3 turns, base 1 turn, both taps from cold end of coil
 L4, 2 1/2T #14, bus bar 7/16" dia. 3/8" long
 L5, 6, 2T #14, bus bar 1/4" dia. 1/4" long

- C1, 6, 7-100 pf
 C2, 3, 5, 4-25 pf
 C4, 2-12 pf

All variable capacitors are compression type. Air dielectric type capacitors can be substituted if desired.

Heat sink for the three 2N2786's Wakefield Engr. #207.

the base-emitter circuit of the following stage are shown in Fig. 4.

Fig. 4A is a Pi network while Figs. 4B and 4C are ordinary parallel resonant tank circuits. In Fig. 4C a tap point is provided for the collector circuit. This point is best determined experimentally. It should be noted that parallel tuned circuits provide the best suppression of subharmonics.

In Fig. 4, R_1 is the collector load impedance, R_2 is the input of the next stage and Q_L is the operating Q . The values for the reactive components of Fig. 4A can be obtained by use of the following relationships:

$$1. X_C = \frac{R_1}{Q_L} \frac{R_2}{R_1}$$

$$2. X_{C_2} = \sqrt{\frac{R_2}{R_1} (Q^2 + 1) - 1}$$

$$3. X_L \approx X_{C_1}$$

Frequency Multipliers

A frequency multiplier stage is operated as a class C amplifier. The power efficiency for a multiplier (as is the case for any class C amplifier) is a function of the conduction angle of the individual stage, the peak collector current, I_M , and the collector voltage V_{CC} . A typical frequency multiplier stage is shown in Fig. 5. Note that the values of C_1 and L_1 are selected to resonate at two or three times the value of f_0 .

Crystal Oscillator

The power amplifier and multiplier stages have been discussed and all that remains is to provide an rf signal to drive the other stages.

A typical crystal oscillator is shown in Fig. 6.

The oscillator is a common base, modified Colpitts type, with the crystal used in a series mode. R_1 , R_2 and R_3 provide the transistor biasing, and the feedback is determined by the ratio of C_2 to C_3 . The values of C_2 and C_3 also depend upon the power output and frequency stability desired. Frequency stability is further assured by using a small collector current swing and loose coupling between the oscillator and multiplier circuits. The loose coupling will insure that loading effects of the multiplier on the oscillator are negligible.

Conclusion

The various stages discussed in the previous paragraphs have been treated in a somewhat general manner since individual requirements such as components, frequency, etc. must be considered.


Fig. 7 is an overall schematic of a complete CW transmitter in which the various stages have been combined. It should be noted that this design is only representative of how the final result would appear. The values for the capacitors and coil data given are for 160 mc. Most adjustments will hit 2 meters without much trouble.

The output stage is composed of two class C amplifiers connected in parallel. They are slightly back biased by the 0.5 ohm resistor in the emitter circuit. C_4 and L_5 is a series tuned circuit, resonant at the frequency of the second multiplier.

The output network L_6 , C_5 and the parallel combination forming C_6 is a T matching network which is designed to reject subharmonics and higher harmonics of the desired frequency.

... WA2DJU

New Products

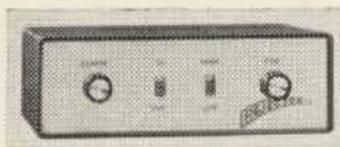

Galaxy Rejector Notch Filter

Galaxy Electronics has introduced the Rejector, a tunable notch filter. This seven transistor notch filter greatly improves the reception on any ham receiver or transceiver. The Rejector is tunable from 300 to 5000 cycles to suppress heterodynes, QRM, ignition noise, background noise and other irritating receiver interference by over 40 db. It connects between the receiver output and speaker. The front panel is reversible for either horizontal or vertical mounting. It's only 7½ x 5¾ x 2½. Price: \$34.95. You can get more information from Galaxy, 10 South 34th St., Council Bluffs, Iowa.



New Amperex SSB Tube

By now, most hams know that there is more to a sideband amplifier than its power output. Amperex' new 8579 beam tetrode is designed to give excellent linearity in SSB service up to 60 mc. A special geometry has been used to keep third order distortion products better than 30 db down. The 8579 can supply 110 watts PEP in AB₁ SSB CCS service. In class C, it gives 110 watts output with only 600 volts on the plate. AM rating is 94 watts and it also makes a fine modulator. The tube is highly efficient and its low drive requirements simplify driver design. The 8579 has double ended construction, a common basing arrangement and a hard glass envelope. Price is \$21.50. Amperex at Hicksville, N. Y. can give more information and data sheets.

NOW!

S.W.R. BRIDGE and FIELD STRENGTH METER

9⁹⁵

Allow 50¢ for
packing and
shipping.
California resi-
dents include
4% sales tax.



**THE BEST
VALUE WE
HAVE
EVER
OFFERED!**

An excellent combination unit for either home station or mobile use... as an accurate Standing Wave Bridge and a sensitive Field Strength Meter. 52 ohm impedance. Will take a full kilowatt and can remain in the line all of the time.

Grey metal case, 5¼" H x 1¼" W x 2¼" D, with standard fittings, 1½" Bright-vue meter, and detachable, telescoping antenna which extends to 10¾". With instructions and schematic.

QUEMENT ELECTRONICS

1000 SOUTH BASCOM SAN JOSE, CALIFORNIA

"Northern California's Most Complete Ham Store"

SINCE 1933

Some Worthwhile Seneca Modifications

Having owned and operated a Heath Seneca for the past two years the author has made numerous modifications to the original unit that have proved rewarding and worthwhile.

For those Seneca owners who may wish to incorporate part or all of these modifications, the following pages will explain how it is done.

Audio Stage Improvements

To preclude the possibility of rf getting into the audio section of the Seneca, add an rf choke in series with the .001 mmfd input capacitor, C28. If you intend to operate primarily on two meters, use an Ohmite Z-144, otherwise a Z-50 should be used.

To reduce hum and incorporate additional B+ filtering two components are added. Re-

fer to pictorial 14 on page 38 of the Seneca manual. The following steps are taken:


1. On terminal strip AA remove the orange jumper between terminals two and four.

2. Replace the orange jumper with a 2-watt 15K or 20K resistor. Solder the connections at terminal four (there will still be three wires on this terminal).


3. Solder a 10 to 15 mfd/450 w vdc—smallest size possible—electrolytic capacitor to terminal two (again, there will be three wires). The negative (-) side of the capacitor is soldered to the most convenient ground point available.

This added filtering and decoupling will reduce existing hum and perhaps some improvement in the audio quality will also be noticed.

Before making the above additions to the

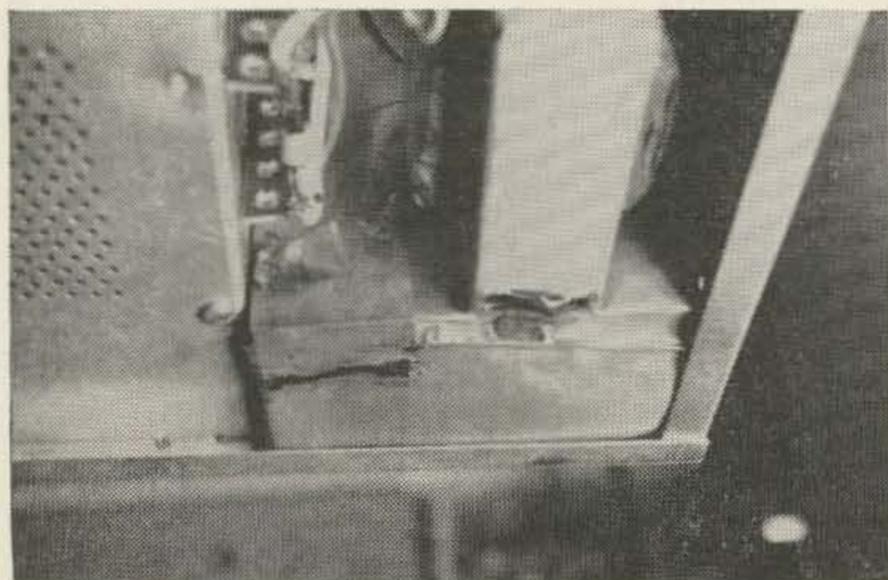


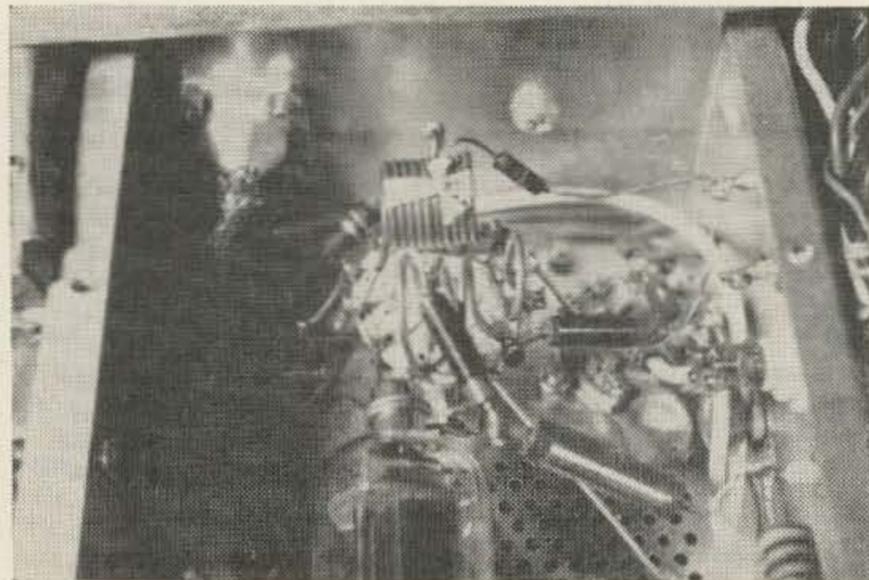Copper shield around audio stage is shown soldered in place. Note that shield is soldered directly to the choke case.



Note lacing cord tied around grid coil L9 compressing the coil for maximum grid current.

TRANSCEIVER HIT PARADE

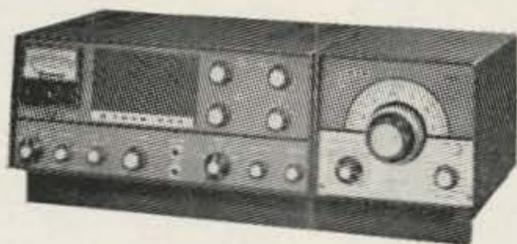

Use our tailor-made
time payment plan.

COLLINS

KWM 2 Transceiver	1150.00
516 F2 AC Supply	115.00
MP 1 DC Supply	198.00
351 D2 Mobile Mount	120.00

DRAKE

TR 3 Transceiver	550.00
AC 3 AC Supply	79.85
MS 3 Speaker	19.95
DC 3 DC Supply	129.95
Mk III	6.95

HALLICRAFTERS

SR160 Transceiver	349.50
P150 AC Supply/speaker	99.50
P150 DC Supply	109.50
MR 160 Mobile Mount	14.50

NATIONAL

NCX-5 Transceiver	685.00
NCX 3 Transceiver	369.00
NCX-A AC Supply/speaker	110.00
NCX-D DC Supply	119.50

SBE

SB 34	39.00
SB 2LA	249.50
SB 2MB	12.50
SB 2VOX	34.50
SB 2XC	24.50
SBE Mike	14.50

SWAN

Swan 350	395.00
Swan 400 Transceivers	375.00
Swan 406 VFO	65.00
Swan 420 VFO	120.00
Swan 1117B AC Supply	75.00
Swan 512 DC Supply	145.00

"HI-OM! Here is another listing of
Good, Fully Reconditioned and Guar-
anteed Gear — At Down to Earth
Prices."

73—Stan Burghardt W ϕ BJV

CASH/NO TRADE

CLEGG VENUS — demonstrator —	\$349.00
GLOBE CHIEF Deluxe Transmitter	39.00
GLOBE SCOUT 680A Transmitter	44.00
GLOBE PSA-63A AC Supply	25.00
HALLICRAFTERS MR-150 Mount for SR-150	20.00
HALLICRAFTERS P-150 DC 12v Supply for SR-150 or SR-160	59.00
HALLICRAFTERS R46B Speaker	7.00
HALLICRAFTERS S85 Receiver	65.00
HALLICRAFTERS SR-150 Transceiver	379.00
HALLICRAFTERS SR-160	229.00
HALLICRAFTERS SR-160 Transceiver — demonstrator —	249.00
HALLICRAFTERS SX-71 Receiver	89.00
HALLICRAFTERS SX-96 Receiver	109.00
HALLICRAFTERS SX-99 Receiver	79.00
HALLICRAFTERS SX-101 MKIII	159.00
HALLICRAFTERS SX-101 MKIIIA Receiver	159.00
HALLICRAFTERS S-108 — demonstrator — (new)	109.00
HALLICRAFTERS SX-110 — demonstrator — (new)	129.00
HALLICRAFTERS CB5 CB Transceiver	79.00
HAMMARLUND HQ129X and Speaker	89.00
HAMMARLUND S-100 Speaker	9.00
HEATH DX-60 Transmitter	59.00
HEATH DX-100B Transmitter	129.00
HEATH HW-12 & HP-13 Supply	159.00
HEATH HW32 Transceiver	109.00
HUNTER BANDIT 2000A	369.00
JOHNSON ADVENTURER	29.00
JOHNSON RANGER	99.00
JOHNSON RANGER — excellent —	119.00
JOHNSON 6N2 Transmitter	99.00
KNIGHT R-100	59.00
KNIGHT T-60 Transmitter	39.00
KNIGHT V-44 VFO	19.00
NATIONAL NC88 Receiver	65.00
NATIONAL NC98 Receiver and Speaker	85.00
NATIONAL NC125 Receiver	79.00
NATIONAL NC300 and Calibrator	169.00
NATIONAL NCX-3 and NCXA Transceiver and AC Supply	379.00
RME-4300 Receiver	85.00
SIMPSON 311 VTVM (new)	39.00
SWAN SW175 Transceiver	139.00
SYLVANIA Model 140 Tube Tester	15.00
TECRAFT Model 150 Criterion Converter 6mtr 28-30 MC IF (new)	35.00
TERADO 50173 12v to 110v AC 200 watt	49.00
WEBSTER BAND SPANNER Antenna	15.00

WRITE FOR LATEST REVISED BULLETIN
ISSUED MONTHLY

Box 37A Watertown, So. Dak. Phone 605 866-5749

Burghardt
RADIO SUPPLY, Inc.

America's Most Reliable Amateur Dealer.

Write for our Special
Transceiver Packet



The front panel crystal socket is mounted directly below the power on pilot lamp and to the left of the meter switch.

audio stage of the Seneca it may be necessary to remove the parallel 6.8K resistor and 2 mmfd capacitor. If you do, don't forget to replace them.

Whatever hum may remain will undoubtedly be removed by the following:

The low voltage filter choke is located next to the audio section and is isolated by cutting some copper sheet stock and completely enclosing the audio section as shown in the photo.

Referring to pictorial 18 on page 52 of the Seneca manual, it can readily be seen that the choke, 46-22, is a most likely suspect in the cause of hum. Be sure that your shield is on the audio section side of the choke and that it does not short out any components.


Solder the shield directly to the top of the filter choke and at two or three places on the chassis that are convenient. The shield will be mostly self-supporting if cut a little oversized and forced into position. The shield is quite effective in eliminating hum introduced by the filter choke.

Lack of Grid Drive?

A number of Seneca owners have complained of a lack of grid drive. Adjusting coils L7, L8 and L9 according to the manual instructions may help but in too many cases it seems that coil L9 wants to be compressed beyond its capability.

This was the case with the author and several other local Seneca owners. The solution?

Take a short length—about 12 inches—of nylon lacing cord and tie the coil into the desired compressed position. This is done with the B+ off of course. A little experimenting here with the lacing cord position and tension will disclose the optimum condition which will deliver grid current plus. Of course you should first check the 2E26 to be sure your lack of grid drive is not just a flat or mushy tube.

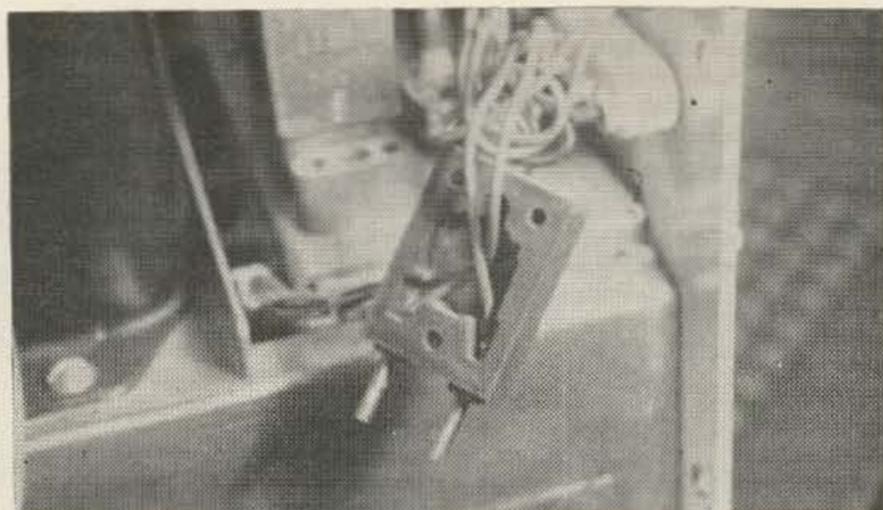

"Dummy" FT-243 crystal holder with cover removed to accommodate new leads.

Adding a Front Panel Crystal Socket

Probably the most inconvenient feature of the Seneca is that of changing crystals. Although this can be done through the top access cover—(we've done it, but don't recommend it)—it certainly leaves much to be desired and may cause many gray hairs to sprout. Crystals may also be replaced by removing the chassis itself. Remove the front panel screws and the rear apron screws and slide the unit out of the case to make the crystal sockets accessible.

A simpler and more desirable feature would be to have a crystal socket on the front panel. Why not? This involves only about 30 minutes of labor to mount the crystal socket.

The best position for the crystal socket is directly below the power on light.


Make yourself a template of the crystal socket you intend to use and gently center punch the points to be drilled. Center punching is almost a necessity to avoid the drill skidding and marring the panel. *Before drilling*, be sure the area directly behind the proposed crystal socket is clear or you may find yourself rewiring the meter switch harness.

After the panel has been drilled and the socket mounted, it will be necessary to make the connections to the front panel crystal socket.

This can be done by wiring directly to the XTAL-VFO selector switch, or a "dummy" crystal may be inserted into one of the original crystal sockets and leads brought up and soldered to the new crystal socket. This is made by removing the crystal cover and insides from an FT-243 crystal holder. Solder new leads to the pins of the FT-243 "dummy" of sufficient length to reach the added crystal socket and solder.

Going to Plate Modulate?

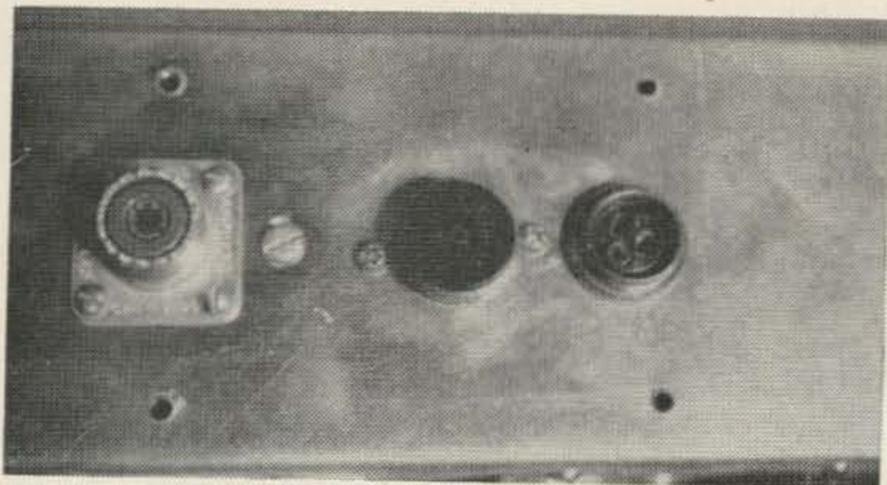The merits of plate modulation versus controlled carrier modulation have been written about many times so we'll bypass that for



Connector for modulator is mounted between the mike connector and coaxial connector.

now. If you want to plate modulate the Seneca it will be necessary to do the following:

1. Break the plate B+ connection to the 6146's and insert the modulator leads.

2. Replace feed-through capacitor FT-15 with a unit of higher voltage rating—preferably 3KV. The original 1KV unit just won't stand the gaff when plate modulating. This can be done easily by installing one of the standard ceramic feed throughs and by-passing with a .001 mmfd 3 KV capacitor.

3. Installation of a two-pin connector on the rear apron of the Seneca chassis to accept a mating plug from the modulator. The author installed this connector between the mike connector and coaxial connector.

4. Disable the existing Seneca audio. This is best done by simply removing the 12AX7 and 6DE7 from their respective sockets.

After you have installed the modulator connector, refer to pictorial 18 of page 52 of the Seneca manual.

1. Remove the orange lead between terminal 4 of terminal strip DD and terminal 1 of terminal strip BB.

2. Connect a lead from terminal 4 of terminal strip DD to one of the pins of the modu-



Original feed thru capacitor is replaced with ceramic feed through and 3KV .001 mmfd capacitor.

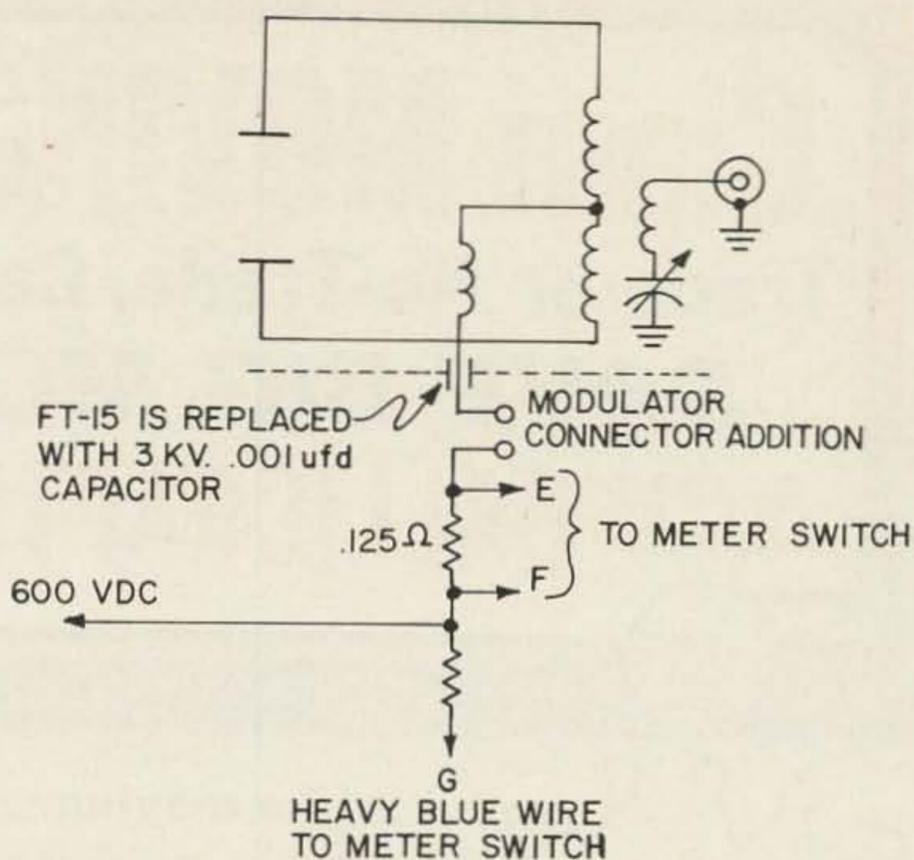


FIG. 1

Fig. 1: Schematic diagram showing modulator connector inserted in 6146 B+ line.

lator connector and solder. (This will be the connection to the low side of the modulation transformer secondary).

3. Connect another lead from terminal 1 of terminal strip BB to the other pin of the modulator connector and solder. (This will be the connection to the high side of the modulation transformer secondary).

Be sure to use good quality high-voltage wire. The type used by the author is test lead cable. This is very good and has a breakdown of 10KV or better.

With this done the modulator may be connected to the Seneca by using a mating plug. Polarized plug and connector are recommended to insure that correct connections are made at all times.

If you decide that you want to revert to controlled carrier operation, put the 12AX7 and 6DE7 back and insert a "shorted" plug into the modulator connector.

Fig. 1 shows the schematic result after adding the modulator connector.

In conclusion, I would like to say that I have made all of the foregoing modifications and am most pleased with the results. There has been a minimum of alterations to the original unit and the re-sale price—(if you ever think of selling the Seneca)—should be maintained if not improved.

Our thanks to Sal, WA6PMP, for his suggestions on improving the audio section and the reduction of hum. 73.

... K6VNT

Giant MOVING SALE!

Trade or No-Trade/Cash or Terms

SAVE BIG MONEY on

NEW HALLICRAFTERS Equipment



TERRY STERMAN
W9DIA
Proprietor

"We're moving soon to a bigger and better location, here in Milwaukee. At our present location we're bursting at the seams with Brand New Factory-Sealed Equipment. It would cost us too much to move our giant stocks—so . . . we're having this Giant Moving Sale, and passing the savings on to you. Until we move, we'll be trading wilder than ever. If you've been thinking about trading up to some New Equipment, now is the time to get our quote. You'll never get a better deal! Use handy coupon below! There is no obligation."

TRADE-IN Coupon

To: STERMAN ELECTRONIC SUPPLY
4828 West Fond du Lac Ave.,
MILWAUKEE, WISCONSIN 53216

I am interested in the following new items:

I have the following to trade:

Rush me your SPECIAL MOVING SALE TRADE-IN DEAL by return mail. I understand I am under no obligation.

Name _____

Address _____

City _____

State _____ Zip Code _____

Send latest Reconditioned Equipment Bulletin


We stock the entire Hallicrafters Line

STERMAN ELECTRONIC SUPPLY

4828 West Fond du Lac Ave.
MILWAUKEE, WISCONSIN 53216
Telephone (414) 442-4200

NOTE: Our firm was formerly known as **AMATEUR ELECTRONIC SUPPLY**
We've changed the name . . . *THAT'S ALL!*

VISIT our Branch Stores, located at:
6450 Milwaukee Avenue | 19 Azalea Pk. Shopping Ctr.
CHICAGO, ILLINOIS | **ORLANDO, FLORIDA**
Phone (312) 763-1030 | Phone (305) 277-8231

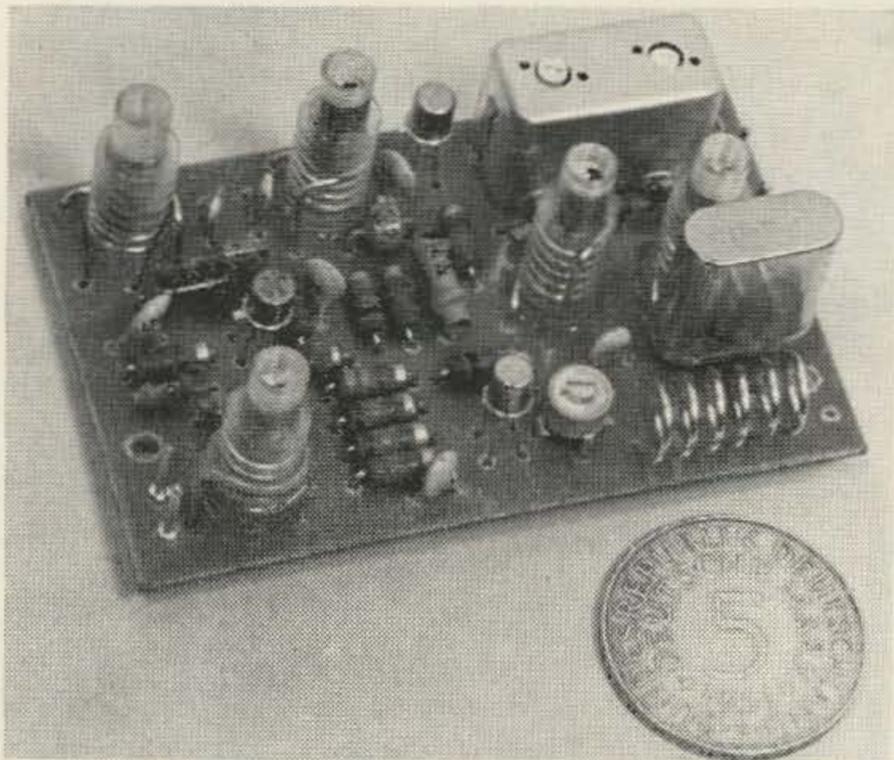

Ulrich L. Rohde
 Technical Consultant
 German Amateur Radio
 Club (DARC)

A Low Noise Transistorized 2 Meter Converter

The electrical performance of modern vhf transistors and their low price now encourage many hams to use them for a number of applications—especially in vhf converter circuitry for 2 meters.

The information given here covers some of the important details of a German 2 meter converter, fully transistorized that has a noise figure of less than 2 db.

This converter compared with one using the famous 417A tube proved to have not only a lower noise figure but also the ability to handle high input signals with amazing linearity.

Glancing at Fig. 1, one can see that the input circuit has a transistor with a series resonance circuit between base and emitter and this is "grounded" by a capacitive voltage divider. Since the emitter configuration requires neutralization, the base configuration has lower amplification but the compromise is a good one. This compromise provides better noise attenuation and better impedance matching. Furthermore, the combination affords a means for feed-back compensation and allows stable operation.

The diode shown connected to the base of the AF-139 transistor is used to provide a distortionless signal to the mixer; but its main purpose of course is to reduce cross-modulation generated mixer products.

A high Q bandpass coupling circuit is used between the rf amplifier and the mixer. The bandwidth of this circuit is ± 1 mc. Measured image rejection is greater than 50 db.

Additive mixing is used applying 170 mv of rf signal from the oscillator to the base of

the mixer transistor. For distortion free operation high emitter current is used on the mixer.

The output bandpass filter in the mixer output at 29 mc has a bandwidth of ± 3 db.

In designing the converter, the most difficult problem encountered was the design of the 116 mc oscillator. In order for it to operate properly the frequency accuracy had to be within ± 15 cps in the temperature region $\pm 5^\circ\text{C}$ (41°F) and 50°C (122°F). The average production tolerance could not exceed 100 cps and this could only be achieved by a very expensive crystal made especially for the set in Germany by a firm which only

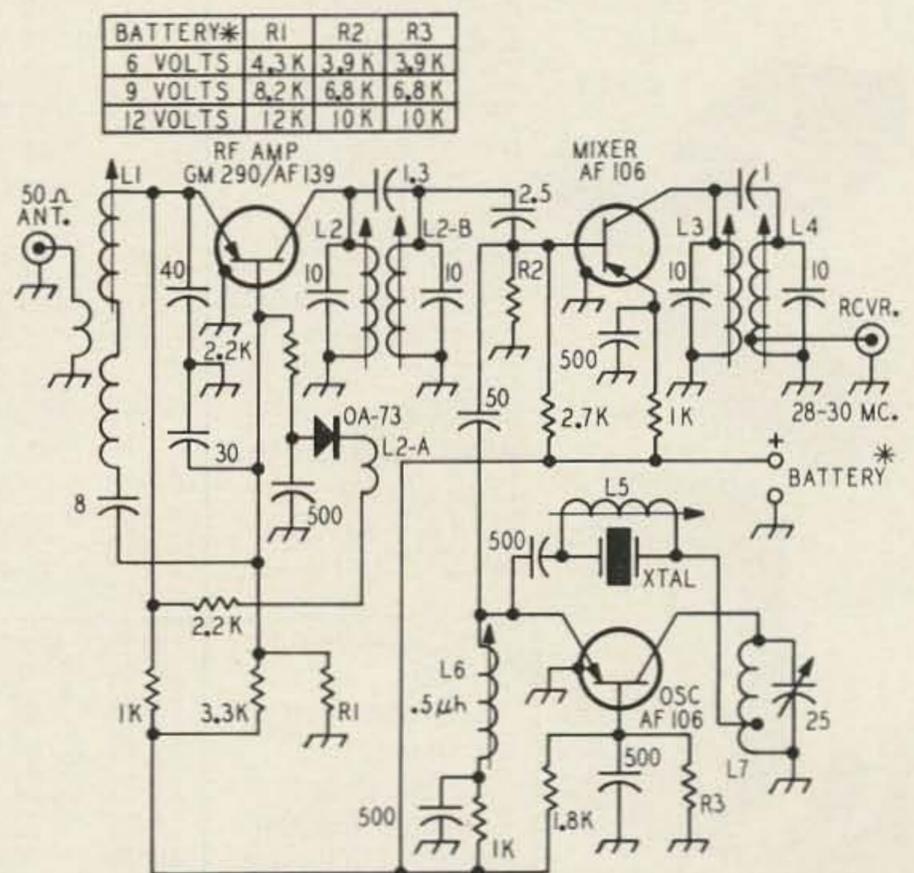


Fig. 1. Two meter converter.

LOOK at your low Monthly Payment AFTER JUST \$5⁰⁰ DOWN



S-120




SX-62B



CRX-2




SX-117

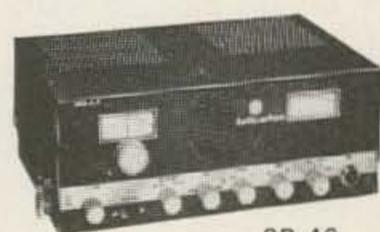

SR-46



CB-10

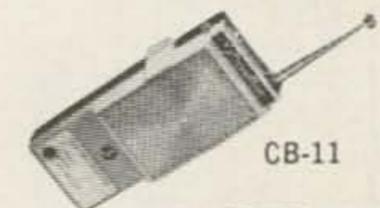

CB-11



VTVM

HALLICRAFTERS

		HAM NET
S-120 AC/DC	(2.34)	\$ 69.95
S-118 5 tubes	(3.42)	99.95
S-108 7 tubes	(5.23)	149.95
SX-110 7 tubes	(5.95)	169.95
SX-122 9 tubes	(10.47)	295.00
HA-7 Calib		19.95
SX-62B 14 tubes	(18.77)	525.00
H-3 Headphones		4.95
Special Receivers:		
CRX-1 30-50 mc	(3.42)	\$ 99.95
CRX-2 151-174 mc	(3.78)	109.95
CRX-3 Aircraft	(3.42)	94.95
CRX-4 30-50 mc	(2.34)	69.95
CRX-5 151-174 mc	(2.34)	69.95
Ham Band Equipment:		
SX-140 Rec.	(4.87)	\$139.95
SX-140K Kit	(3.97)	114.95
HT-40 Xmtr.	(3.78)	109.95
HT-40K Kit	(3.06)	89.95
SX-117 Rec.	(13.53)	379.95
HA-10 Tuner		24.95
HT-44 Xmtr.	(14.08)	395.00
CA-44 Cable		4.95
HT-45 Linear	(13.00)	365.00
P-45 AC Sup.	(7.94)	225.00
SR-150 Xcvr.	(23.29)	650.00
SR-160 Xcvr.	(12.44)	349.50
HA-16 VOX		37.95
MR-150 Rack		39.95
MR-160 Rack		14.95
P-150AC Sup.	(3.41)	99.50
P-150DC Sup.	(3.41)	99.50
HA-1 Keyer	(2.70)	79.95
HA-5 VFO	(2.70)	79.95
HA-8 Mod. Ind.		24.95
R-47 Speaker		12.95
R-48A Speaker		19.95
R-49 Speaker		14.95
SR-42 2m Xcvr.	(6.67)	189.95
SR-46 6m Xcvr.	(6.67)	189.95
MR-40 Rack		11.50
HA-32 Rotor	(7.94)	225.00
Citizen's Band:		
CB-7 6 channel	(3.42)	\$ 99.95
CB-9 "Deluxe" CB-7	(4.51)	129.95
CB-10 Transistor	(5.23)	149.95
P-10 AC Supply		29.95
CB-3A 8 channel	(5.59)	159.95
Hand-Held CB Units:		
CB-6 100 mw ea.	(1.98)	\$ 59.95
CB-8 1 Watt, 2 ch	(3.42)	99.25
CB-11 100 mw—pr.	(2.70)	79.95

Test Equipment:	KIT	WIRED
VTVM	29.95	\$ 59.95
Condenser Tester	29.95	49.95
RF Generator	29.95	64.95
Resistor Decade	14.95	24.95
Capacitor Decade	14.95	24.95
Battery Eliminator	49.95	79.95
Oscilloscope	84.95	164.95

"If you are considering purchasing, **WITHOUT TRADE**—either Cash or Financed—any **NEW Equipment, Antennas, Towers, or Station Accessories, etc.**—You will want to get our **Special NO-TRADE MOVING SALE DEAL**. You know that the Manufacturers would frown upon our advertising a Discount . . . So, tell us what you are interested in on the **Coupon** below, and we'll call you **Long Distance** (at our expense), to let you know how we can save you **BIG MONEY**. You are under no obligation! **Sorry, we cannot accept Collect Calls—we'll call you.**"

RAY
K9KHW
Mgr. Mail
Order Dept.

NO-TRADE Coupon

To: **STERMAN ELECTRONIC SUPPLY**
4828 West Fond du Lac Ave., 7
MILWAUKEE, WISCONSIN 53216

I am seriously considering purchasing the following new equipment without trade-in:

I understand you will phone me long distance (at your expense) and tell me how I can save money during your **MOVING SALE**:

My home phone # is: _____ My phone # at work is: _____

Best time to call: _____ Best time to call: _____

My area code is _____

Name _____

Address _____

City _____

State _____ Zip Code _____

Send latest Reconditioned Equipment Bulletin

produces frequency standards equipment. The crystal used operates at the 5th overtone and produces *no* spurious signals.

The ultra low noise figure (better than 2 db) was achieved by using a special Texas Instruments transistor type GM-290 (uhf-tv-type). Better attenuation of cross modulation and better signal handling capability can be obtained by using the Fairchild IW-8343 (uhf-silicon) epitaxial-planar type. Amperex A1220 is another equivalent.

The mixer and oscillator transistors are not critical but should have an f_T higher than 250 mc. Amperex 2N2495 or 2N2496 are direct equivalents.

The size of the converter is very small, only 2" x 3 1/8" and weights only 46 grams. A glance at the photo of the converter with the 5 mark piece (about the size of the American half dollar) shows the neat layout of all parts on the printed circuit board.


The coils L-1 through L-6 are special units. No data is given here on the coils for competitive reasons. You'll have to dip them if you want to build the converter.

Fig. 2 shows that R-1, R-2 and R-3 should be changed for optimum operation when using different battery voltages. The resistors in question are circled on the diagram.

The overall characteristics of this converter are: frequency range 144-146 mc, oscillator frequency 116 mc, image rejection better than 50 db, spurious signals *none, if* (receiver) 28 to 30 mc, noise figure 1.7 KT_o , power gain 25 db, input voltages 6, 9 or 12 volts and current 7 milliamperes.

The retail price in Germany of the unit is 32 U.S. dollars and can be obtained from the factory, K. H. Lausen, Funktechnische Erzeugnisse, 32 Hildesheim, Bahrfelderstr 11, West Germany. A distributor for the unit in the U.S. is being selected.

... Rohde

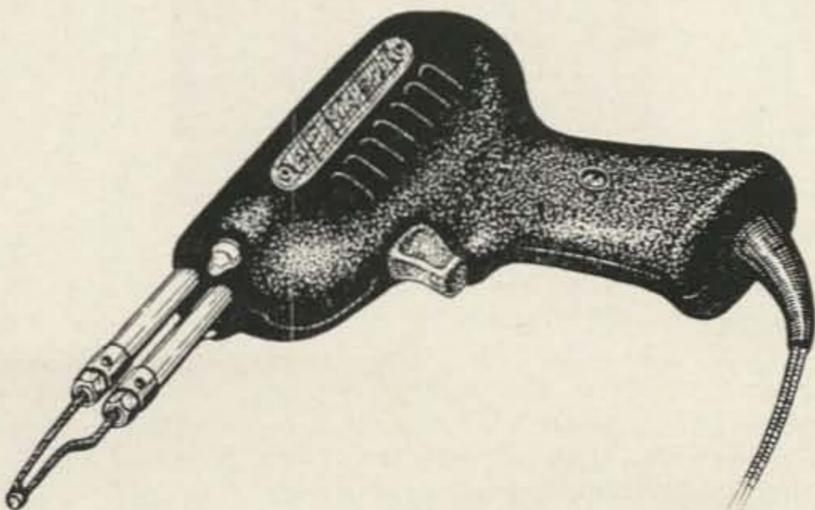

... K3SUK

good mobiles

STILL

go



HUSTLER

by NEW-TRONICS

the home of originals!

HUSTLER is the mobile antenna that has won the widest praise from everyone that has used it. For really reaching out, and for exceptional results on every band, the HUSTLER has no equal. For unbiased opinion of performance, ask any HUSTLER user... there are thousands of them.

See the HUSTLER at your dealer or write us for literature.

NEW-TRONICS CORPORATION

"the home of originals"

3455 Vega Ave., Cleveland, Ohio 44113

14th Annual Dayton Hamvention

of the
Dayton Amateur
Radio
Association

Saturday, April 10, 1965
Wampler's Ballarena
Dayton, Ohio

- TECHNICAL SESSIONS
- EXHIBITS
- AWARDS
- FORUMS • VHF • DX • SSB • RTTY •
ANTENNAS • ARMY MARS
- HIDDEN TRANSMITTER HUNT
- WOMEN'S ACTIVITIES
- HOMEBREW CONTEST

FCC EXAM: 0900 Saturday, April 10.
General Class only. Make exam application
in advance to 8th District Engineer in Detroit.
FCC will issue exam papers.

For information, map, accommodations, write:
Dayton Hamvention, Department T, Box 44,
Dayton, Ohio 45401

advised by my lawyers that
don't you ever proofread y
are a bunch of crooks and
this **Letters** ~~is a~~ ~~for~~
have no other recourse but
should be tarred and feath.

Dear Wayne:

I was intrigued by your article on page 52 of March "73" Magazine. Mr. Ackerson did a nice presentation but it won't work since the ten diodes in half of the bridge will blow on the first half cycle. The bottom diodes are all reversed. Apparently Mr. Ackerson thinks along the same lines we do since even the case, method of mounting the 100 mfd capacitors and parts list are strangely similar to our old Model 250-AC and later 350-AC.

Best regards,
Bernard J. Bisnett, President
Linear Systems, Inc.

Dear Wayne:

I noticed that the price of QST has been raised to 60 cents. I stopped subscribing to their magazine over 4 years ago. One reason for this was that their circuits were so elaborate it would be cheaper to buy commercial gear than to homebrew.

I have successfully built several pieces of gear from your magazine, including a SSB transmitter which is doing a fine job and has since last August. Please keep your magazine practical so that the average ham can build equipment from it.

Your price only went up 3 cents in a great number of years . . . A fine magazine . . . keep up the good work.

Samuel Armstrong WA2JVE

And we went up from 37c to 40c mainly because of the coin shortage which made giving 13c change a lot more difficult than a dime.

Dear Wayne:

Just received the Feb. issue. It is really great. I especially concur with your comments on the stamp. It is almost an insult. I couldn't believe my eyes when I first saw the thing.

Keep up the good work with 73. It is really different to find a good ham magazine in the mailbox with QST.

Charles R. Cox, K8TUO/AREA
Athens, Ohio



Dear Sir,

I am one of your readers and I am enclosing herewith a snap of my SSB generator which gives 50 watts output on 14, 21 & 28 Mc band using Collins mechanical filter and 7360 as balanced modulator. Results are just wonderful. This is a 1965 edition from VU2CQ. I do have two other side band generators, one phasing type and another high frequency filter type.

"Mickey" Mozoomder VU2CQ
Bombay, India

COMPUTER QUALITY

CLEAN! BEAUTIFUL! SURPLUS!

5000 CAPACITORS AS SHOWN BELOW

MIX 'EM




49¢
ea

6 for \$2.50

12 for \$4.75

Mail Order Minimum 6
Add \$1 per 6 for PP & Ins.

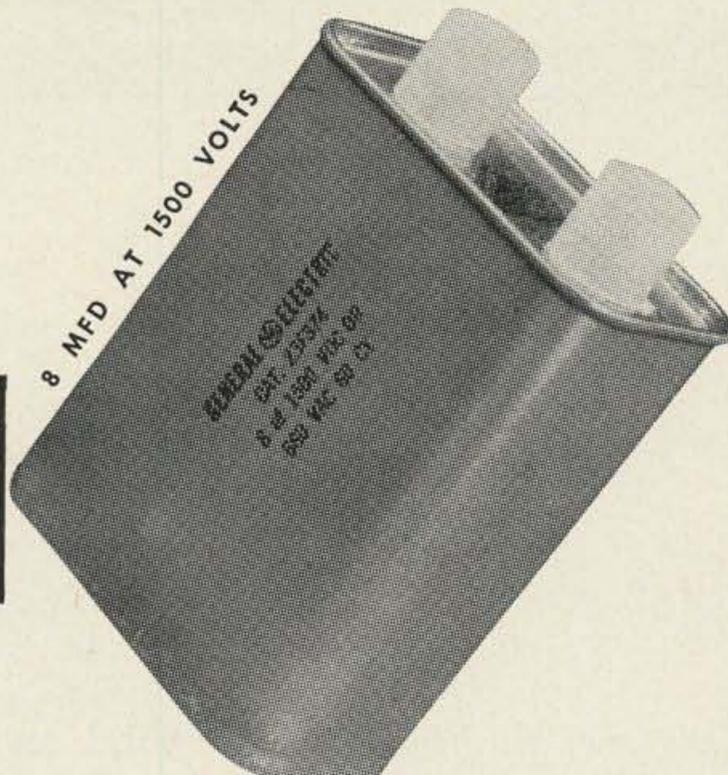

SINCE 1933

FAST SERVICE

Phone CY 4-0464

QUEMENT ELECTRONICS

1000 SOUTH BASCOM AVE. • SAN JOSE, CALIF.

"Northern California's Most Complete Ham Store"

Dear Wayne;

I am certainly not trying to tell you how to run your business but that thing of "Big Brother" re advertising in the current issue makes me mad. Why don't you ask your readers to always mention "73" when ordering equipment?

I have just ordered a VENUS and told them it was because of the write-up in the Dec. "73." I also ordered a "22'er" and told them it was because of the write-up in the current issue of "73."

I ALWAYS say it was because of "73" whenever I write or order—(even if I saw it in "QST"!!!)

Keep up the good work!

Wilmer W5VV
Austin, Texas

Dear Wayne,

Keep up the good work and the fine articles in 73. I want to belatedly thank you for the restoration of the propagation condition forecasts. And for your information, an official first day cover for a stamp is available to anyone merely by sending the amount of the stamp and a self-addressed envelope to the postmaster in the city of issue. If one wants a cacheted envelope there are many commercial firms that supply them for all commemoratives issued. The ARRL statement that "official first-day covers are available only from the League" (italics theirs) is a lie. I would like to know how much they made on that little deal and if they really thought no stamp collectors were hams.

William Farone W5NOK
El Paso, Texas

Dear Mr. Green:

I am an avid follower of your magazine in the Charlotte area, and I would like to say it far surpasses the other same publications in this field. The content is quite informative for the "learning" amateur and complex enough for the old "pro." Even your advertisements prove very interesting. I would like to thank you for this from the Charlotte hams.

Ted F. Goldthorpe, Jr., WA4VCC

Dear Wayne,

I have one gripe. As soon as I open your magazine and I see a hastily thrown together rig using a 2C39 and globs of solder I figure K1CLL has been at work. In general it tends to degrade your otherwise excellent magazine and the overall picture of VHF-UHF construction.

Ken Decker WA6OSB
San Diego, California

Being contrarywise by nature I say a minimum of three buzzaws for Bill and his scissors and solder UHF construction techniques. Sure, I love the look of that beautifully machined brass equipment, but I know that if that is the only thing I publish we are not going to have many fellows on the UHF bands. Bill has shown that anyone can build UHF gear that works well and do it on the kitchen table.

Dear Mr. Green,

You have often spoken well of the Swampscott Convention in your magazine. I have been to the Hudson Division Convention and was very disappointed. I am thinking of driving up from New York if it is worth the trip. What organization do I get in touch with beforehand?

Bert Lane W2HBQ
Wantaugh, New York


For Heaven's sakes don't miss the biggest convention of them all at Swampscott's New Ocean House April 24-25th. I'll be on the speaker's program and have a big booth there to say hello. Write to Eli Nannis W1HKG, 37 Lowell Street, Malden, Massachusetts for further info and be sure to come on up with the family.

Gentlemen:

K4NMV, 1736 28th Street, Ensley, Birmingham, Alabama has available at no charge copies of a callbook of amateurs belonging to the Church of Christ. Please send a #8 stamped self addressed envelope.

K4NMV

More letters on p. 82.

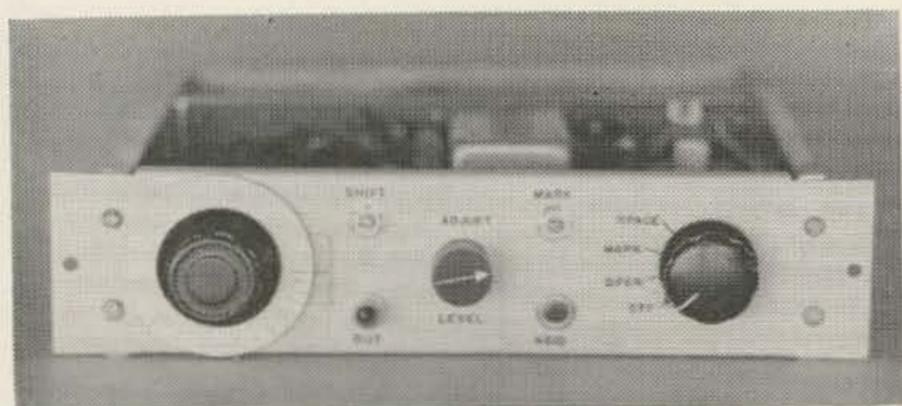

Tom Lamb K8ERV
1066 Larchwood Rd.
Mansfield, Ohio

A Novel AFSK Oscillator

Let's see, this morning I'll build an audio shift oscillator for the expected model 15, and this afternoon I'll . . . As with most projects, building a good AFSK oscillator turned out to be more than a one-morning job.

The standard capacity-switched L-C oscillator left much to be desired. Switching a discharged condenser into an oscillating circuit causes a pause in the oscillation, resulting in a shortened *mark* pulse. Switching transients above the normal output level were seen, which can cause overmodulation or require operation at reduced modulation levels. The switched-C oscillator does not normally have equal *mark* and *space* output levels, and cannot easily be adjusted to exact frequency. It does have the advantages of simplicity and excellent stability.

Next I tried a Clapp vfo, using a three-gang variable condenser to permit variable shift and easy adjustment. The switching transients still existed and the *mark-space* output varied widely.

If the added *mark* capacity were very small compared to the normal circuit capacity, the

oscillator circuit Q and impedances would be nearly constant and there would be no switching problem. A large shift can be obtained from a very small added capacity only if the operating frequency is high, as in a beat-frequency audio oscillator (remember them?). Such a shift bfo was tried and produced an excellent switched waveform having easily adjustable shifts. Unfortunately even a carefully designed transistor bfo has very poor long term drift problems that make it unsuitable for RTTY work.

But cheer up, don't throw away your printers (unless you throw them my way), things are getting better! There is one type of oscillator admirably suited to AFSK service, but apparently never used. It has good stability, constant output, shifts instantly and without transients, and is quite easy to shift and adjust—the lowly relaxation oscillator!

Look at the characteristics of two relaxation circuits, Fig. 1. The neon bulb is probably the more familiar, but the unijunction is more stable and will be used in the oscillator. The output amplitude is determined by the device characteristics, not by the frequency-determining R and C. The frequency is easily and smoothly shifted if the charging resistance R is changed. The sawtooth output is easily smoothed into a sine wave by a low-pass filter.

Fig. 2 shows the circuit of an AFSK relaxation oscillator. The unijunction transistor is an inexpensive and stable solid-state equivalent of the neon bulb. Its operation is thoroughly covered in the *General Electric Transistor Manual* and will be described only briefly here.

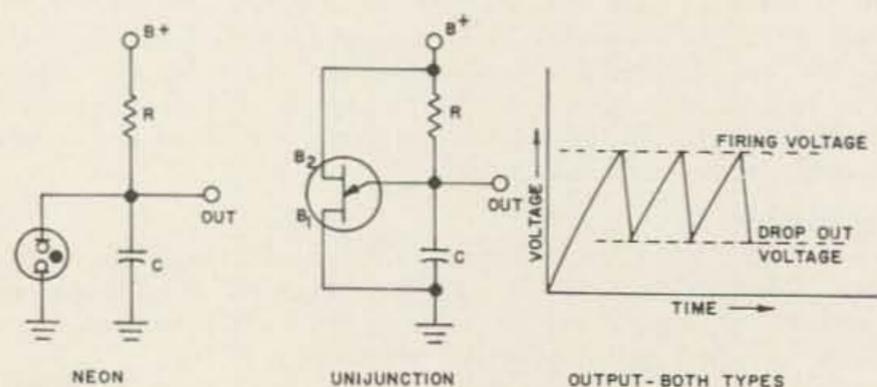


FIG. 1 RELAXATION OSCILLATORS

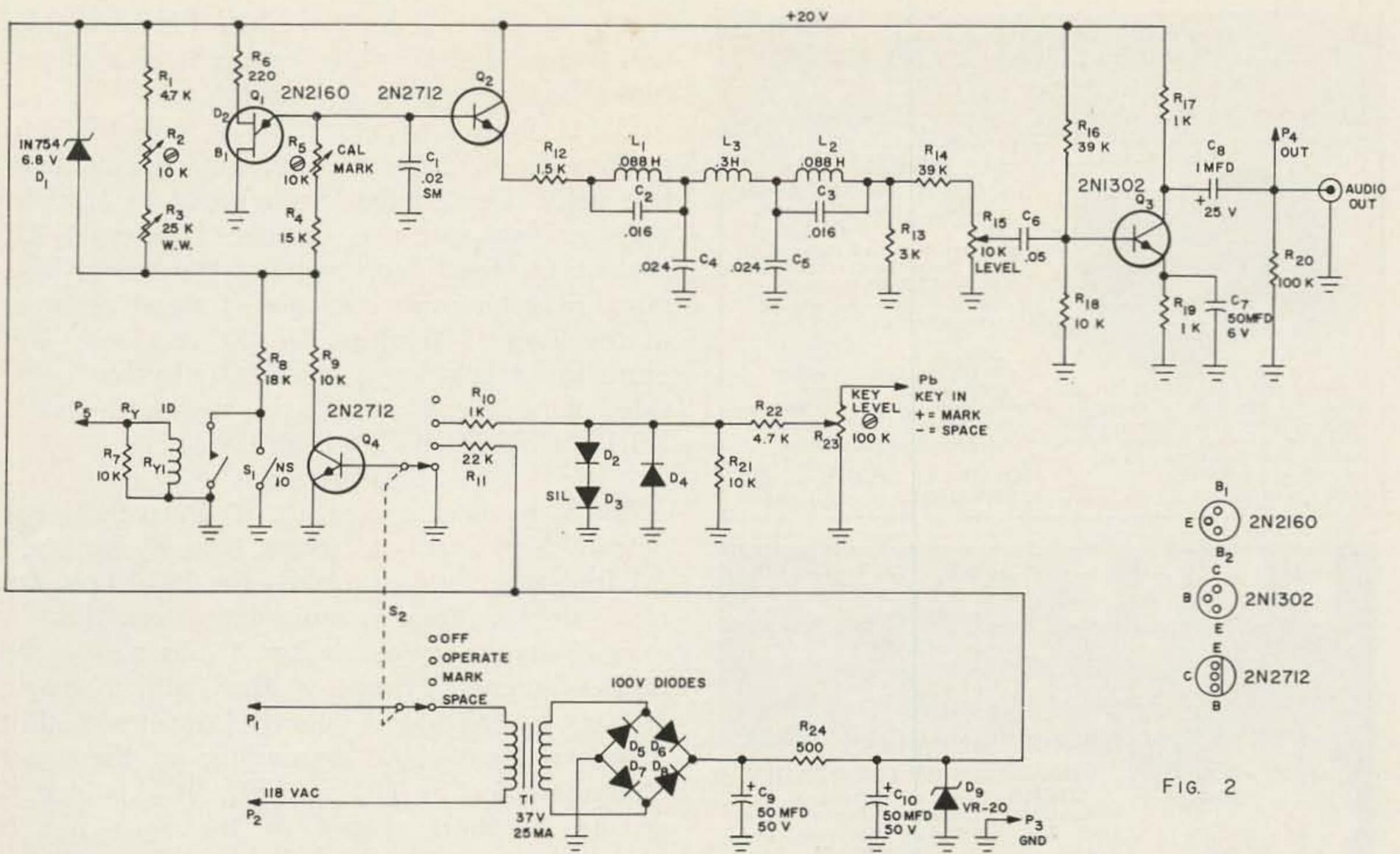


FIG. 2

Fig. 2. The novel AFSK oscillator. Connect bottom 3 terminals of bottom section of S_2 so that the oscillator will be on in operate, mark & space.

Operation

The unijunction is operated with +20 volts on base two. The emitter is an open circuit for voltages below about 10 (varies with the transistor). As condenser C_1 charges through resistors R_1 through R_5 , its voltage builds up to 10 v. At this voltage, the emitter to base-one junction breaks down, much as the gas in a neon bulb, and discharges C_1 . This cycle repeats, producing the familiar sawtooth voltage across C_1 . If the charging resistance is returned to the same voltage point as base two, the relaxation frequency is remarkably independent of voltage and temperature variations.

The generated sawtooth voltage is isolated by emitter-follower Q_2 and fed into a low-pass filter. As seen in Fig. 3, the filter cuts off above the *space* frequency (2975 cps) and is almost 40 db down for all harmonics of both the *mark* and *space* frequencies. The output waveform is a very good sine. The input resistor, R_{12} , can be set so that the output voltage varies less than $\frac{1}{2}$ db over the range of 2125-2975 cps.

Inductors L_1 and L_2 are the familiar telephone loading toroids. L_3 is a toroid removed from a surplus filter. Condensers C_2 - C_5 should be low loss units such as mica or polystyrene, selected for proper value on a bridge.

After filtering, the tones are amplified by Q_3 . R_{14} is set to prevent overloading of Q_3 at maximum level.

Keying is accomplished by saturating (mark) or cutting off (space) transistor Q_4 . With Q_4 cut off, Q_1 oscillates at a *space* frequency determined by the sum of R_1 through R_5 . Diode D_1 does not conduct. With Q_4 saturated, R_9 causes D_1 to conduct at a constant 6.8 volts regardless of the setting of the shift pot R_3 , and Q_1 now oscillates at a *mark* frequency determined only by R_4 plus R_5 . The shift is adjustable from 100 cps minimum to 850 cps maximum by rotating a potentiometer, but the *mark* frequency is held at 2125

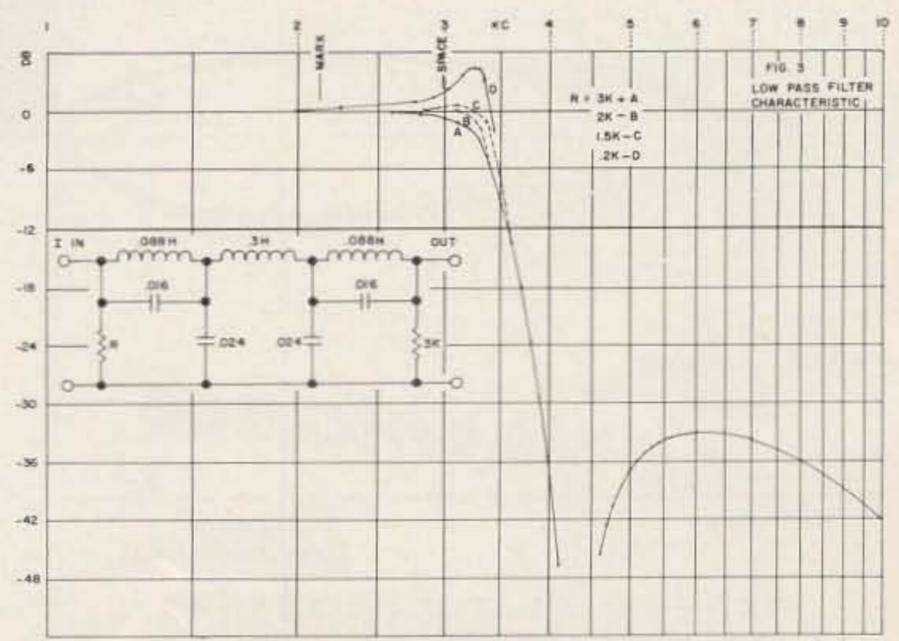


FIG. 3

TRANSTENNA 102A

A PRESELECTOR SECOND TO NONE AND A T-R SWITCH BEYOND COMPARISON

Pat. Pndg. U.S.A. & Canada

MODEL 102A

\$69.45 (Add \$7 for Sidetone
— either model)
15 DAY TRIAL

Return For Full Refund If
You Burn It Out Or Are
Not **FULLY PLEAS**

- Std. coax coupler (xmtr to feedline)
- No TVI or Suck out
- 30 DB Min. Gain (10-80 mtrs)
- No Effect on Transmission
- Monitored switching
- Full Legal Input
- Burnout Proof
- CW Sidetone (optional)

Write for Free Literature

33 Myrtle Avenue
Cedar Grove, N. J.
Tel: CEnter 9-6412

Improved 102A Adjustable Mute Circuit Breaks Any Xmtr-Rcvr Between Dots & Dashes Without Clicks. Improved Semiconductor Through-Position Switch Switches Rcvr Directly to Antenna for Unity Gain 6-80 Mtrs.

FICHTER

ELECTRONICS

102B, \$59.00 like 102A exc. rcvr. muting


FREE Catalog OF THE WORLD'S FINEST ELECTRONIC GOV'T SURPLUS BARGAINS



HUNDREDS OF TOP QUALITY ITEMS—Receivers, Transmitters, Microphones, Inverters, Power Supplies, Meters, Phones, Antennas, Indicators, Filters, Transformers, Amplifiers, Headsets, Converters, Control Boxes, Dynamotors, Test Equipment, Motors, Blowers, Cable, Keys, Chokes, Handsets, Switches, etc., etc. Send for Free Catalog—Dept. 73.

FAIR RADIO SALES
2133 ELIDA RD. • Box 1105 • LIMA, OHIO

HYE-QUE ANTENNA-FEEDLINE CONNECTOR

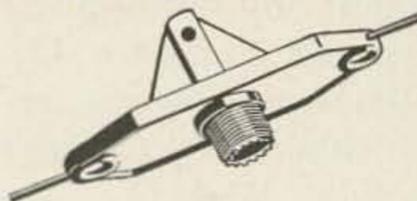

New 3-in-1 melded plastic-and-metal fitting provides: coax feeder connection, heavy copper leads to elements, antenna center support. Hye-Que I Connector fits standard PL259. Reinforced, weather protected, ultra-efficient. At your ham store, or \$2.95 ppd. Companion insulators, 2 for 99¢ ppd. Includes complete instructions.

BUDWIG MFG. CO., P.O. Box 97, Ramona, Calif. 92065

cps by diode D_1 . Narrow shift for identification is provided by push switch S_1 or a miniature relay for remote ID switching.


Q_4 is keyed to *mark* by a one-milliamp positive input current from any source over five volts. The change from *space* to *mark* is very sudden and non critical. Diodes D_2 - D_4 protect Q_4 from loop voltage transients. The input may be connected across shunt resistors in the loop (100 ohms for 60 ma. loop; 300 ohms for 20 ma. loop) or directly to the "cold" side of a positive voltage keyboard as in K6IBE's TU-D (RTTY June 1963).

Calibration

Set S_2 to *mark* and adjust R_5 for a 2125 cps output. Now set S_2 to *space*, turn R_3 for highest frequency and adjust R_2 for 2975 cps. Because of variations in unijunction transistors it may be necessary to change C_1 to obtain the proper frequency range. With S_2 still in *space*, R_3 may be calibrated directly in cycles of shift down to about 100, depending on the exact characteristics of Q_1 and D_1 . R_{12} is selected for constant output as the shift pot is varied over its range. With the oscillator connected to the loop, increase R_{23} just passed the point where marking occurs. Now turn your two meter beam towards Ohio and call K8ERV like mad.

... K8ERV

Gus-see p. 4

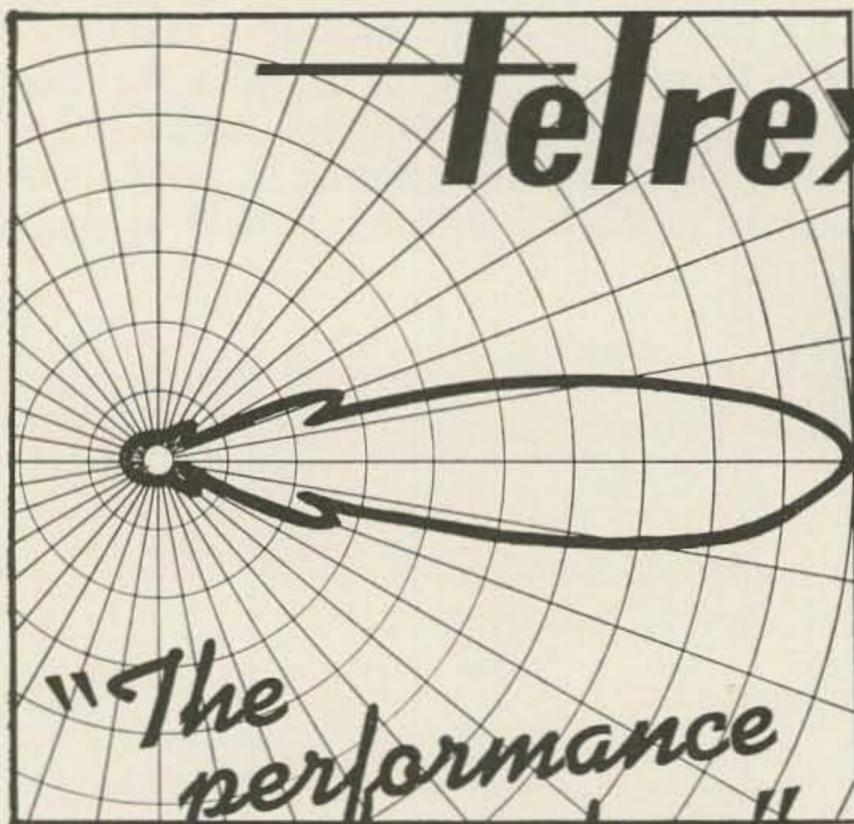

"The performance with a line"
MATERIAL DIFFERENCE
—IN USE IN 135 LANDS!

"BEAMED-POWER" ANTENNAS and ANTENNA SYSTEMS

The Choice of the Discriminating
Communication Engineer . . . the
Man who Never Settles for Any-
thing Less than THE-VERY-BEST!


You too—can enjoy world renowned TELREX performance and value! Send for PL65 condensed data and pricing catalog, describing the lowest priced antennas on the market, in relation to materials and performance! Expanded data sheets—including your favorite band, are also available.

ANTENNAS
SINCE
1921

COMMUNICATION SYSTEMS
telrex LABORATORIES

ASBURY PARK 25, NEW JERSEY, U.S.A.

LOOKING FOR A GREAT LINEAR?

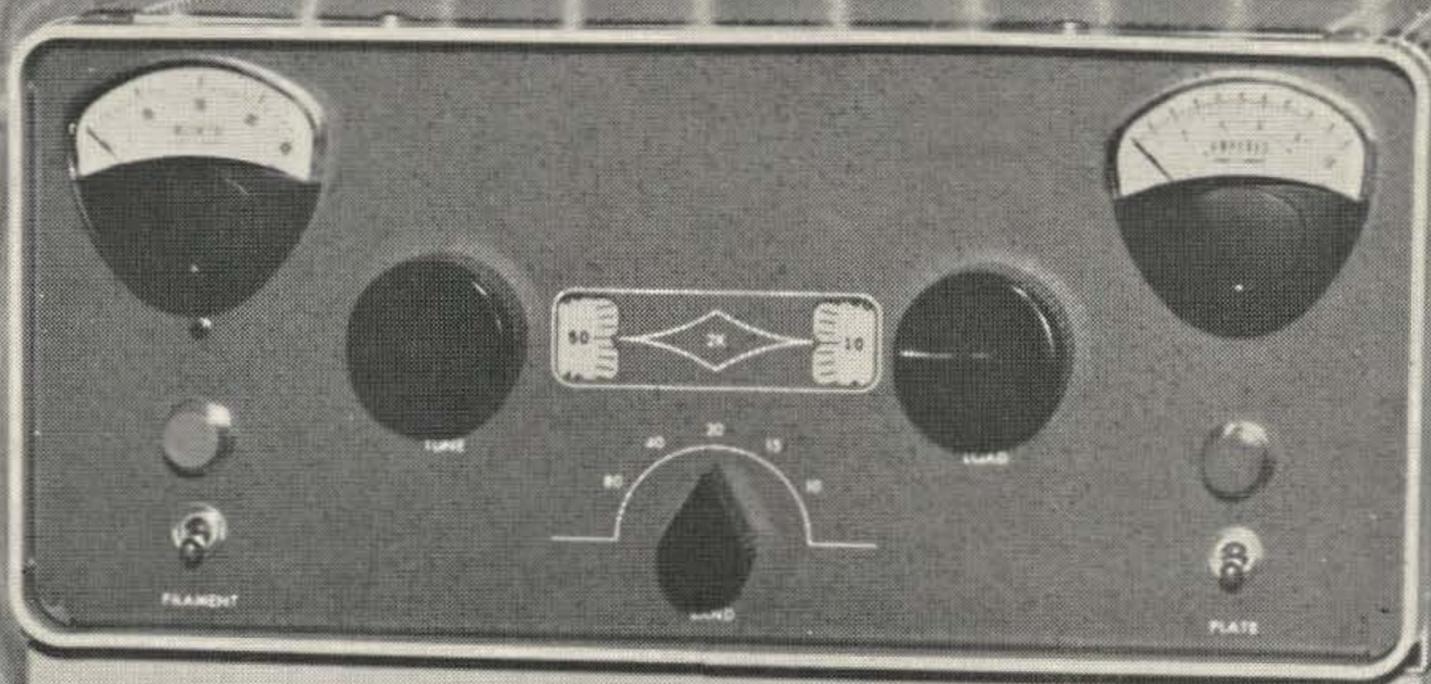

YOU'VE FOUND IT!

Now You Can Have The Strongest, Sharpest, and Cleanest Signal on the Band. Treat Yourself to the Thrill of Owning the Finest.

**THE HENRY "2-K"
LINEAR AMPLIFIER**

**CONSOLE or
DESK MODEL \$675**

Henry Radio Stores

CALL DIRECT . . . USE AREA CODE

Butler 1, Missouri	816 679-3127
11240 W. Olympic, Los Angeles, Calif.	213 477-6701
931 N. Euclid, Anaheim, Calif.	714 772-9200
431 E. Green St., Pasadena, Calif.	213 684-0861
6116 N. 27th Ave., Phoenix, Ariz.	602 AM 4-3895

Low Cost Solid-State Crystal-Controlled Modulated Signal Source with Infinite Attenuator for 2, 220, 432 and 1296 mc

These little units will allow you to do just about any and all low noise front end work you can dream up. You can also carry it in one hand and transport it to your friend's house and calibrate his low noise super-duper and compare it with your 416B, parametric or what have you, for absolute sensitivity. Results are stable and guaranteed equal to actual most extreme DX conditions on the air, including Moon-Bounce. Cut down from 1000 microvolts to 1/20th of a microvolt, 1/100, and on to absolute zero, on a smooth graduated scale. Sounds too good to be true? Yes, it does, but it works and we have several here operating F.B!

How It's Done

It often takes several new ideas working together to make a new device. Don't forget, well-known A and B put together in a certain fashion, can make highly patentable C! As in the following example.

A. A miniaturized transistorized, crystal-controlled, modulated signal source small enough to fit inside a waveguide (or any rectangular

cross section metal tubing of correct size).

B. Metal tubing as per above, whose dimensions are such as to present infinite cut-off for energy on the frequency involved, such as 144, 220, 432, 1215, or 1296 megacycles. The length of course must allow for the attenuation, which is very high per inch!

C. Metal end caps on the tubing, with a coaxial connector on one end, and a hole for a slide-handle or push rod with a graduated scale on the other.

And that's it. Infinite attenuators have been made before, of course, but usually have required also fantastic amounts of shielding, power lead bypassing, etc., for the oscillator. But this one just slides into the waveguide, signal source, power supply and all. As long as it sits well inside the guide, with no conducting metal of any kind coming out it works fine. This is totally important. I mounted one of these on a long piece of copper-clad bakelite which I figured to use also as a push-rod. The results? N.G.! The signal came right out on the copper.

If you want to switch it on and off from the outside you will have to use a rotary switch and a wooden dowel extension.

Two Meter Signal Source

Fig. 1 shows this little unit which starts with a 48 megacycle crystal. The oscillator circuit is your present writer's favorite, the crystal phase reversing job. I have described this before, so this will be a shortie. If regenerative connections were used, that would put the emitter on the coil tap of L1, with the base on the end. Degenerative connections, as used, are the opposite, base tapped up on the coil, with the emitter on the end. However, due to the nature of piezo-electricity, the ac voltage on each end of a crystal is always 180 degrees out of phase, so, it not only oscillates but it will not take off anywhere ex-

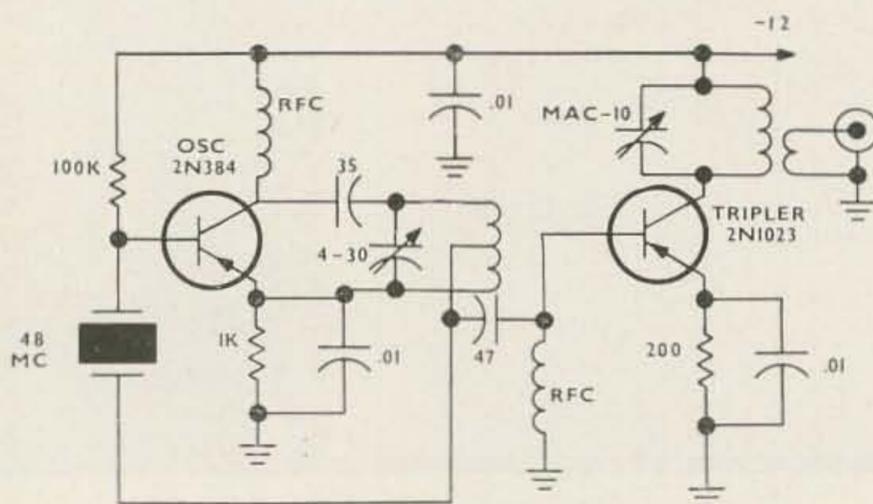


Fig. 1. 2 meter crystal controlled signal source. L1 is 7 turns airwound 16 tpi. Tap at 4 turns from cold end. L2 is 8 turns no. 16 copper airwound 3/16 inch id, 1 inch long. RFC is any good choke resonate below 48 mc.

cept on the crystal frequency. All other frequencies are highly degenerative.

The transistor used is a RCA 2N384. This type happens to be several years old but has always worked ok at 50 megacycles. It also saves my better units for 1296 where you really need the best.

The next one is a 2N1023, also RCA. This is a type that goes up past the 2 meter band. It also was on hand. Any good transistor honestly labelled UHF or even VHF should do all right in either of these positions. Incidentally, sockets are used. They work perfectly ok. Don't forget that germanium transistors should not really be soldered. With silicon units the manufacturer yells "What in the world are you using sockets for?" You can even solder right onto the case!

In spite of my oft-voiced preference for doubling, tripling is used here because it works adequately for the purpose: a good signal on 2 meters. There is much more signal than you need for sensitive receiver tests. In fact, you could use less battery voltage. I just tried it out, between these sentences, and find that 6 volts is as low as the unit described above will go. At that battery voltage the output is down to 20 microamperes as compared with 500 using a new 12 volt battery. As is however, it is nice for peaking antenna coils, rf stages alone, and on indoor antenna ranges. Outdoors too, if you use a receiver for one end of the range.

The tripler stage uses a 200 ohm emitter resistor and a grounded rf choke in the base with no dc excitation other than that furnished by rectification in the base-emitter circuit. The stage draws about one mil collector current while running.

A small copper-clad plate 2 x 1 inches is used to "launch" the signal into the waveguide. Again, there is more signal than needed for sensitive receivers. You could certainly omit the launching plate. An rf output jack allows maximum rf to be obtained for other test purposes. You can also use the unit as a local oscillator chain for a solid state two meter converter if you want to by changing the crystal and retuning a little. Use absorption frequency meters or a grid-dipper to do this. Better even use both!


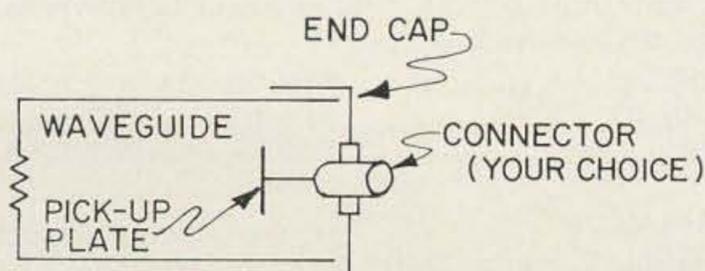


Fig. 2. Detail of pick-up end of attenuator

TRANSISTORIZED!

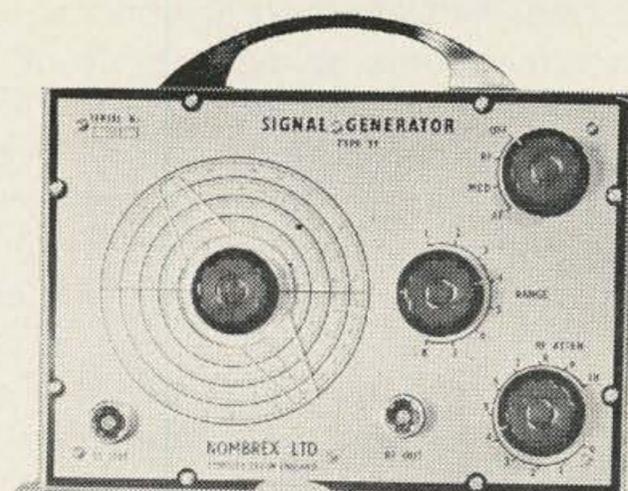

ACCURACY

IN THE PALM OF YOUR HAND

RF SIGNAL GENERATOR

- Battery Powered
- Compact: 1 lb. 12 oz.
6 5/8" x 4 5/8" x 2 5/8"
- Wide Range 150 KC to 350 MC
- Guaranteed: one year
- Other Instruments Available

\$39.95

Postpaid
Completely Wired
Includes Battery
and Cable




ORDER NOW:
PATH PRODUCTS CORP.

55 Halley St. Yonkers 4, N. Y.
Exclusive Dealers Territories Open

"Your Friendly Supplier"

A
SPECIAL

OFFERS

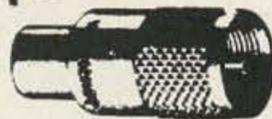

PL-259
STOCK NO. 25



SO-239
STOCK NO. 23

ONLY **32¢** EACH
IN LOTS OF 10 OR MORE



NEW! RG-8U Coaxial Cable
9¢ per foot

Minimum order 100 feet Stock No. 7328

For Prepaid Shipment Continental U. S.
Order by above Stock Numbers

ALSO—we can handle your antenna requirements! We stock ANTENNA SPECIALISTS, CUSH-CRAFT, HY-GAIN, MOSLEY, NEW-TRONICS, & WEBSTER—both fixed station & mobile, plus accessories.

"Write for Latest Used Equipment List"

Evans RADIO

P.O. BOX 312

PHONE
603-225-3358

CONCORD, N. H.

Construction of the Attenuator

As you may have gathered, you can simply take a piece of aluminum waveguide or aluminum drainpipe about three inches wide and about two inches high, by some 4 feet long, tape the signal source to a 2 inch wide by 4 feet long strip of quarter inch plywood, and push it inside. You'll see immediately what happens to the signal if you are listening on your low noise superhet. When the source is well inside the guide, that signal will disappear!

Actually, a little work on the deal is quite rewarding. First an end cap, coax connector and "pick-up" plate, puts the signal right where you want it, that is, into the rf jack of your pre-amp.

Fig. 2 shows detail. The end cap can be formed of flashing copper, if you're good at making metal boxes. I'm not. The cap can be fastened on with tape or metal screws. Solder a small piece of copper clad bakelite to the coax connector, bakelite side in, and away you go.

The real nice feature of this is that instead of putting the signal out in the barn in a tin can, or over at your neighboring ham's shack, you now get all the signal you want, or as little as you want, right at the input jack of your receiver.

Believe me, for rf stages there is nothing like it. (Never mind the "government type" HP generators at \$3,000 to \$4,000 a throw. How much money do you think I get for writing ham articles?)

At the other end of the waveguide you need another end cap, with a hole in it for the "push-rod" handle. I fastened the copper clad base plate of the generator to a piece of thin plastic and then attached a 1/2 by 3/4 inch strip of wood 4 feet long. As seen in the photo this comes out the end, and can be used for calibration purposes. I'll leave fancy stuff to

you, such as remote control switch, (use wood or bakelite) modulator switch, etc. Just remember, no metal of any kind. The ground plane base of the generator has plenty of signal on it.

Results

I checked out the various detectors, receivers and converters I have to see their relative sensitivities in "inches" of push-rod sticking out.

Now I can really find out about the absolute signal sensitivities of the following units around the shack. A. Crystal mixer, including noise comparison of all my crystals; B. 6AM4 rf stage; C. Ditto 6AN4; D. New 2,000 megacycle type transistor stage (at 432 of course); E. The half dozen 416B's that have been knocking around the shack for some years; F. My 417A's; G. Anything else I can think of, such as noise reduction by neutralizing.

Using modulation on the generator, a simple absolute reference check can be made by using a scope on the receiver af output. Sync lock provides an exact reference level that is better than the human ear. Af wave on the scope versus "grass" of the noise can be used also. Signal level is varied by moving the push rod in and out of the waveguide. There is no use arguing with that set up! The complete receiver that locks on with the greatest distance is it! Don't change the af set-up while testing rf, of course. Voice recognition is another whole story yet.

Please excuse my not showing 220 megacycle units. It's just that I like to jump to 432. Then of course, you have to jump to 1215 or 1296. 220 should be easy, just put in another crystal and coils.

So that's all for now, yours for better noise figures.

. . . K1CLL

NOW

EXCLUSIVE 66 FOOT **MOR-GAIN** 75 THRU 10 METER DIPOLE
NO TRAPS — NO COILS — NO STUBS — NO CAPACITORS

Fully Air Tested — Thousands Already in Use



NEW MODELS

40% Copper Clad wire—Under three lbs. Air Weight—Rated for full legal power—AM/CW or SB—Coaxial or Balanced 50-75 ohm feed—VSWR under 1.5 to 1 at most heights—Rust resistant hardware—Drop-proof insulators. Completely assembled, ready to put up. Model 75/40 Amateur Net **\$23.80**. Terrific Performance—No coils or traps to break down or change under weather conditions—Fully Guaranteed. MODEL 75/40HD (HEAVY DUTY DIPOLE) **\$26.00**—RATED 3KW PEP—66'.

NEW SUPER HEAVY DUTY DIPOLES 66' LONG. RATED 4KW PEP-2000 POUND BREAKING STRENGTH—DELRIN CENTER & END INSULATORS—OUT PERFORM FULL SIZE DIPOLES; 75/40 SHD **\$30.00**; 75-20 SHD **\$34.00**; 75-10SHD **\$45.00**

MODEL 40/20.....**\$17.00** • 36 FEET LONG
MODEL 80/40CW.....**\$25.80** • 69 FEET LONG
MODEL 75-10.....**\$40.00** • 66 FEET LONG

ORDER DIRECT OR WRITE FOR FULL INFORMATION

MOR-GAIN

P.O. Box 6006
Alexandria, Virginia 22306

OR THRU YOUR FAVORITE DISTRIBUTOR

Phone: 703-768-7766; Nights and Holidays 703-780-2171

"THE KID FROM TEXAS" (BRYAN EDWARDS, JR.)

COMPLETELY RECONDITIONED USED EQUIPMENT

ADCOM		GALAXY		HEATH	
350-12	\$ 89	300	\$219	HX-10	\$259
500-12	99	PSA300	69	HX-20	149
1000-12	199	III	299	HR-20	99
B & W		III AC Supply	59	MR-1	44
5100B	\$139	GLOBE		MT-1	49
51SB-B	99	65A	\$29	DX-35	35
CENTRAL ELECTRONICS		680	39	DX-40	39
10-A	\$ 55	LA-1	75	DX-100	79
20-A	119	Highbender	69	DX-100B	99
QT-1	9	755A VFO	29	TX-1	129
600L	199	GONSET		SB-10	59
100V	395	G-66	\$ 65	RX-1	139
CLEGG		G-77	89	HA-10	179
99'er	\$ 99	G-76	179	VF-1	9
Thor W/AC	279	G-76DC	49	UT-1	19
Venus	389	GSB-100	219	HP-20	19
COLLINS		Super 12	29	HP-10	35
75A-1	\$169	HALLICRAFTERS		HP-13	45
75A-2	199	HT-20	\$ 99	JOHNSON	
75A-3	269	HT-32	279	Adventurer	\$ 25
75A-4	399	HT-32A	319	Challenger	59
51J-3	429	HT-37	269	Courier	139
75S-1	319	HT-40	49	Pacemaker	149
75S-3	479	HT-41	239	Ranger I	119
75S-3B	519	S-40B	39	Valiant I	159
32S-1	429	SX-62	159	Viking I	59
30L1	379	SX-96	99	Viking II	79
KWM-2	849	SX-99	79	122 VFO	19
516F-2	85	SX-100	129	KNIGHT	
516F-1	65	SX-101	149	T-60	\$35
351D-1	39	SX-101A	199	T-150	75
PM-2	99	SX-110	85	NATIONAL	
CC-2	59	SX-111	149	NCX-3	\$269
516E-1	99	SX-117	279	NCX-5	489
DRAKE		SX-140	69	NCX-A	79
1A	\$139	SR-150	399	NCL-2000	489
2A	179	SR-160	249	NC-98	79
2B	199	P-150-AC	69	NC-109	89
2BQ	25	HAMMARLUND		NC-125	79
2AC	12	HQ-100	\$ 99	NC-140	129
TR-3	439	HQ-110C	119	NC-173	75
AC-3	59	HQ-120	69	NC-183D	139
DC-3	89	HQ-129X	85	NC-300	139
RV-3	59	HQ-140X	109	NC-303	199
ELMAC		HQ-150	139	SBE	
AF-54	\$29	HQ-170C	199	SB-33	\$269
AF-67	49	HQ-180C	279	SB1-LA	189
PMR-6	29	SP-600	299	DC Supply	39
PMR-7	65	SP-600 JX-27	399	SWAN	
PMR-8	79	HX-50	279	SW-120	\$149
				SW-140	149
				SW-175	149
				SW-240	259
				SW-400	319
				SW-350	319
				TCU	79

BUY WITH CONFIDENCE!

ALL EQUIPMENT GUARANTEED

NATIONALLY KNOWN BRANDS.

**CAREFUL RECONDITIONING OF
ALL EQUIPMENT SOLD.**

TOP VALUES.



**Edwards
Electronics**

TELEPHONE PORTER 2-8759
1320 19TH ST. / LUBBOCK, TEXAS 79401

William Kennedy W3ZFJ
1520 James St.
Monroeville, Pa.



The Converted Converter

*Turn a Gonset Tribander
into a complete receiver.*


There have been many articles on conversion of surplus equipment and a few on conversion of old commercial equipment. Here we present a conversion of a converter. I picked up my old Gonset Tribander one evening and wondered what could be done in the way of making a receiver out of it. Out came the paper, slide rule, and coffee pot. I started figuring gains, bandpass circuits, tracking, and etc.; and came up with this little gem. This article is an attempt to show what can be done with one of these converters after a few evenings

at the work bench. This little package, requiring only a power supply and speaker to be complete, can hear anything on ten meters that my 75A-4 can hear. This is where the comparison ends however, but in 10 meter mobile, you need little else.


The Gonset Tribander with its four tubes, when installed in the family chariot, required six or eight tubes in the BC set plus two more for the noise limiter. That is a lot of tubes and power, especially if you are interested primarily in one band. This receiver requires only 150v to 175v at 50 ma and 12v at 1 amp. The circuit in Fig. 2 may be used to power the receiver from the 110v line, and the circuit in Fig. 3 may be used in the car.

The receiver circuitry is simplicity itself. The tribander was used because I had one on the shelf but any of the Gonset converters will do just as well. Only the dial, tuning capacitor, rf coil (10 m), oscillator components, and the "screw in the upper left hand corner" were used. The entire chassis is stripped including tube sockets.

Fig. 1 will show the circuit is quite conventional, consisting of a 6GM6 rf stage, a 6EA8 pentode mixer with the triode section as the local oscillator. The *if* amplifier is an

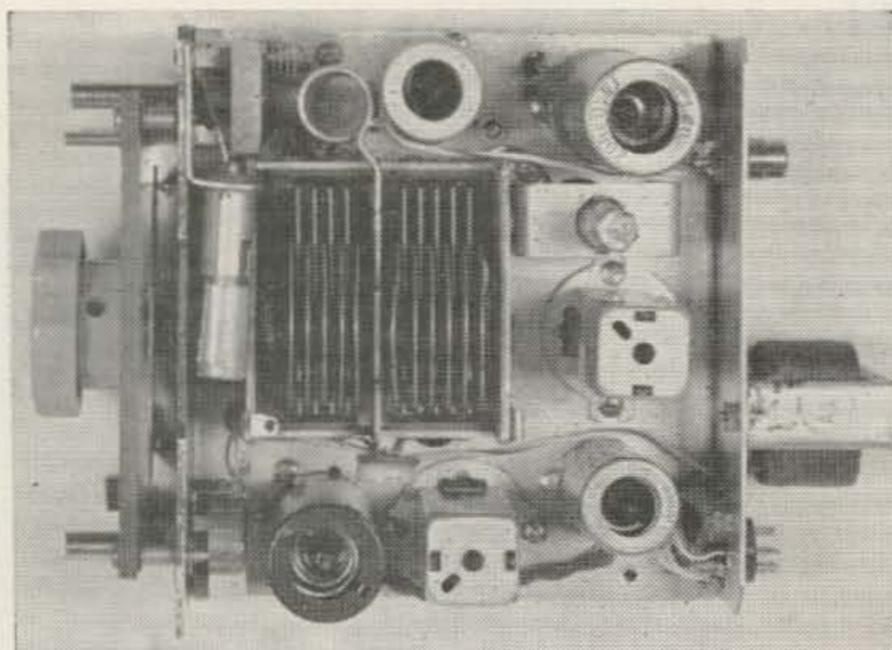

Top view of Converted Converter receiver

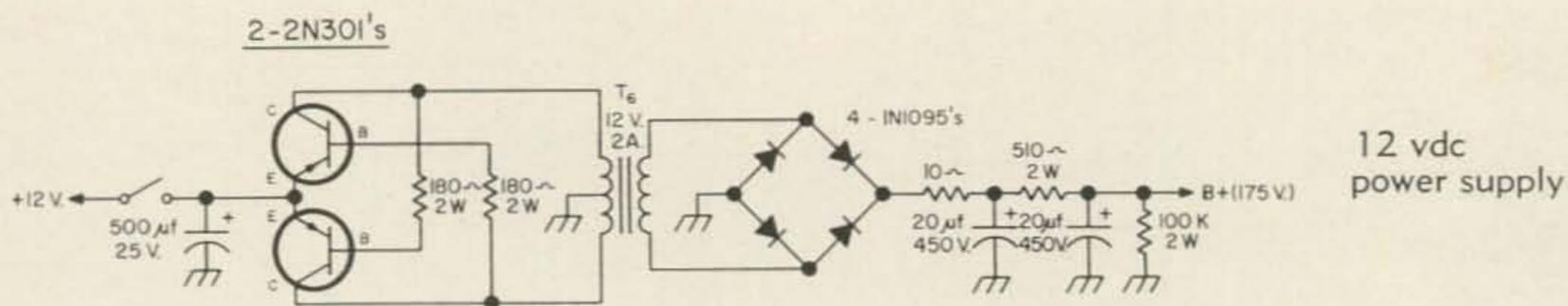


placed the 82 pf and 100 pf negative temp. capacitors with silver micas; however, I retained the 2 pf oscillator injection capacitor. An added refinement is the 1N1797-130V Zener diode to voltage stabilize the oscillator. This may be left out, or a VR105 may be added in the power supply. A band set trimmer is mounted on the variable capacitor frame next to the 6EB8.

The variable capacitor will tune over a much wider range than we need, so a band edge stop must be installed. This may easily be done by removing the dial plate from the main shaft and replacing the set screw with a 1/2" 4-40 bolt. The bolt will stop at each end of the band on the shaft of the tuning capacitor. Take care to replace the dial in the same place as it was or you will upset the tracking. One last point in the oscillator section; don't forget the 2 pf oscillator injection capacitor to the mixer. I did, and spent several days trying to find out why the receiver was so insensitive.

The mixer is a relatively new tube and is straight-forward circuitry. There is a new bottle out by RCA I will try sometime in the near future in this circuit. It is a 6KE8 triode and frame grid pentode. The gm of the pentode is 12,000 μ mhos and is designed for high gain mixer circuits. The *if* amplifier (only one) is conventional.

Now we come to the noise limiter and squelch circuit. The noise limiter is the Rate of Change circuit that appeared in Dec. 1962 of 73. Note that the two input resistors have been increased to 100 k. This gave me more output and a greater degree of noise suppression. I make no claims that this is an improvement, only that it's different.

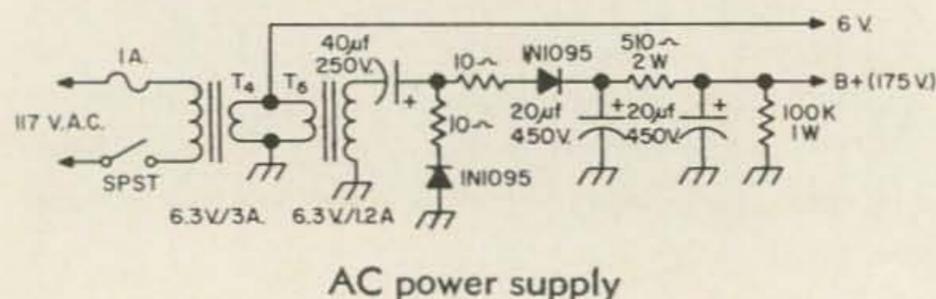The squelch is nothing more than a diode switch. It lets the audio through when conducting and cuts it off when its non-conducting.



AC power supply

I could go on about this circuit but K4UWX described it at great length in his article "Simple Squelch" in Nov. '62 of this magazine.

The 6EB8 in the audio stage takes the place of the usual 6AQ5-12AX7 combination in that it combines power amplifier and voltage amplifier in one bottle. The receiver didn't have quite enough gain in the audio section so a 7895 nuvistor was added for more gain. As you can see in the photograph, it is mounted under the chassis up next to the rf stage.

The input connector is an amphenol miniature "CP" series 7 pin plug mounted in a tube socket ring. The tube socket became the female cable connector. It makes a very small multi contact connector.

The slide switch on the front panel switches the 12v to the filaments and to the output connector to energize a relay in the power supply. The other half of the switch connects the car speaker either to the receiver or to the bc set. Incidentally, if anybody is partial to the TNS noise limiter and squelch there is plenty of room under the chassis if you use a pair of silicon diodes and a pair of 6CW4 nuvistors.


This receiver has performed trouble free for about 6 months and is still going strong. A matching transmitter with vfo, screen modulator, and a power input of 100w is under construction in another converter case.

... W3ZFJ

Parts List

- L1 original antenna coil, antenna tap 1 turn
- L2, L3 12T #30 wire on 3/16" ceramic iron slug form, spaced 3/4" apart. or Miller 4300 form or 4306 coils may be used.
- L4 original oscillator coil
- D1 1N1797 Zener Diode
- D2, D3 Texas Inst. 1N486 or Hughes 1N426 silicon diodes
- T1 10K to 4 ohms output transformer. Stancor A-3879
- T2 Miller 13-W1 1500kc if trans.
- T3 Miller 13-W2 1500kc if trans.
- T4 Thordarson 21F10
- T5 Thordarson 21F09
- T6 Thordarson 26F67

Have you checked these out yet?

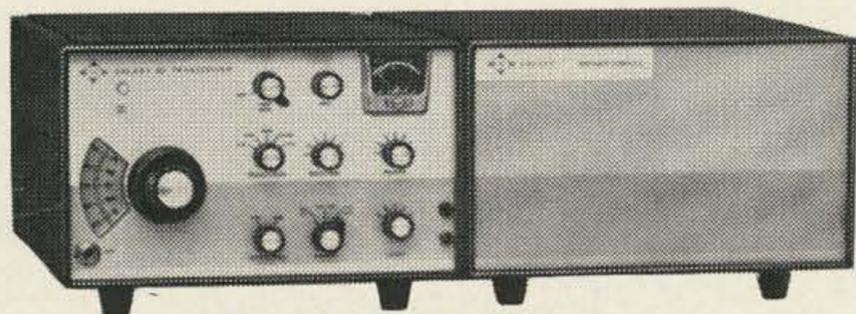

GALAXY III WITH SPEAKER CONSOLE

If not ---

YOU SHOULD !

THESE GALAXY TRANSCEIVERS ARE GREAT



GALAXY V

Point for point the Galaxy Transceivers are hard to beat. Check these features . . . 300 watts SSB/CW • Smallest in size with 5 or 3 band coverage • Narrow filter bandwidth • Built-in upper and lower sideband • Shifted carrier CW for "NO-retune" CW operation • Advanced transistorized circuitry • Built-in carrier suppression • Reduced power tune-up position • E-Z Vue dial • Accessory remote VFO

IF YOU HAVE FINANCING PROBLEMS...CHECK HENRY RADIO'S EASY TERMS *(We're easy to deal with)*

6% FINANCE CHARGE • 10% DOWN OR TRADE-IN DOWN • NO FINANCE CHARGE IF PAID IN 90 DAYS • GOOD RECONDITIONED APPARATUS. Nearly all makes and models. Big savings! 15 day trial — 90 day warranty. 90 day full trade back on new apparatus. Write for bulletin.

Henry Radio Stores


CALL DIRECT . . . USE AREA CODE

Butler 1, Missouri	816 679-3127
11240 W. Olympic, Los Angeles, Calif.	213 477-6701
931 N. Euclid, Anaheim, Calif.	714 772-9200
431 E. Green St., Pasadena, Calif.	213 684-0861
6116 N. 27th Ave., Phoenix, Ariz.	602 AM 4-3895

"Worlds Largest Distributors of Short Wave Receivers"

NEW callbook

**HOT OFF
THE
PRESS!**

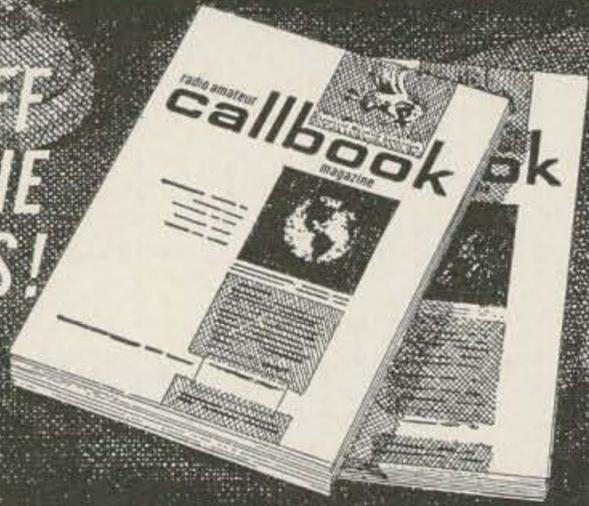

**Over 60% of listings
changed in only a year!**

PLUS THESE EXTRA FEATURES:

- Great Circle Bearings
- Great Circle Charts
- Prefixes by Countries
- "Q" and "Z" Signals
- World Time Chart
- Int'l. Postal Rates

United States Listings...\$5.00
DX Listings..... 3.00

**RADIO AMATEURS
REFERENCE LIBRARY OF MAPS
ORDER YOUR SET TODAY!**



WORLD PREFIX MAP—Full color, 42" x 29", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables.....postpaid **\$1.00**

POLAR PROJECTION MAP—Azimuthal equidistant projection. Shows prefixes on each country, DX zones, cities, prefix index by countries, 29" x 25"postpaid **\$1.00**

UNITED STATES MAP—All 50 States with call areas, prefixes, DX and time zones, FCC frequency allocation chart. Plus interesting information on all 50 States. 29" x 17".....postpaid **50c**

WORLD ATLAS—Only Atlas compiled for amateurs. Polar projection, six continents, prefixes on each country . . . full color, 16 pages.....postpaid **\$1.00**

Complete reference library of maps—set of 4 as listed above.....postpaid **\$2.50**

**WRITE FOR
FREE
BROCHURE!**

RADIO AMATEUR



callbook INC.

Dept. B, 4844 W. Fullerton Ave.
Chicago, Ill. 60639

See your favorite dealer or order direct (add 25¢ for mailing)

73 Tests the Galaxy V


It's driving me out of my mind. The V arrived just a few days ago on loan for evaluation. I was quite surprised at how small it was . . . it looked so big in the ads. Instead of setting it up down in the ham shack I decided to put it on a small typewriter table by my desk and feed the antenna up through the floor.

Frankly, since the Galaxy V is the lowest cost five band selectable sideband transceiver, I expected to be faced with all kinds of miseries in operation. Not a problem of any sort has turned up.

My first try was on 3999 kc, probably the most aristocratic frequency of all the hambands. After a careful examination of my signal on their scopes I was admitted to this elite group and permitted to talk freely with the assembled M-2's. Had there been untoward carrier, unwanted sideband, or distortion I never would have made the club.

That night I tuned up on twenty meters . . . Oh, by the way, the V is a snap to tune . . . even old fumble-fingers me got the hang of it right off. My first call was YV5CEI. When we finished I got trapped by two fellows down Boston way . . . 73 readers . . . and I got another hour behind on my work. This having a rig by the desk is bad news . . . it is too easy to flip it on just to see who is there . . . then I *have* to call in and say hello to some old friend. Yes, I do have some friends.

One control that is left off some of the transceivers is the one for switching sidebands. Sure, you don't need it often, but when you do you do. One of the first stations I heard on 75 was using the upper sideband instead of lower and I switched him in with a chuckle to myself, thinking of all the fellows who could hear the noise, but couldn't tune it in. Obviously this is quite advantageous on CW, where at least one side of the station you are working has a little less QRM than the other.

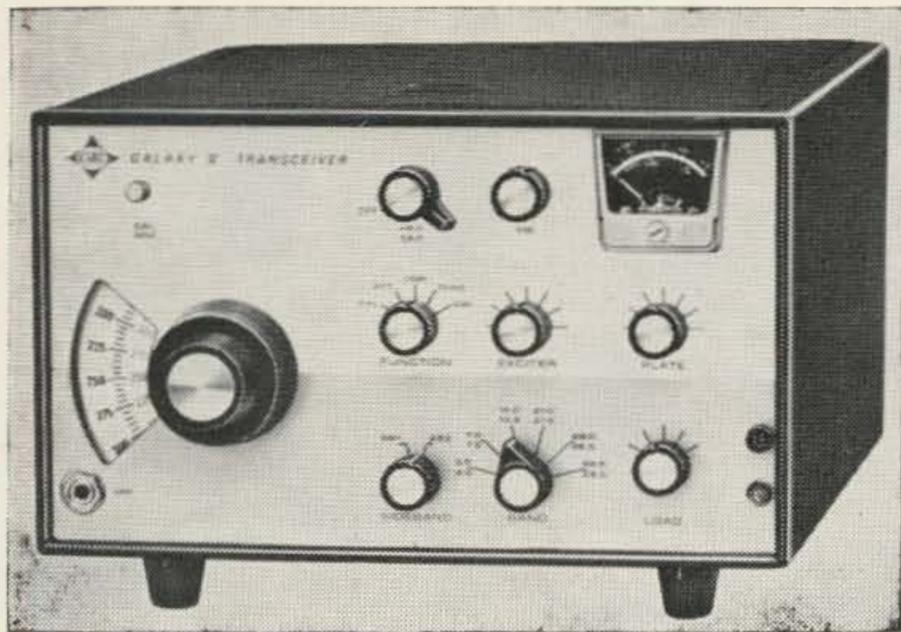

This brings up another considerable advantage of the Galaxy V . . . CW. Many of the transceivers are designed strictly for SSB . . . some permit CW, but don't let you tune the entire CW part of the ham bands. The V covers not only the entire ham bands, but overlaps enough on most bands to permit MARS operation, reception of CHU, and stuff like that. Specifically it tunes from 3.5-4.0 mc, 7.0-7.5 mc, 14.0-14.5 mc, 21.0-21.5 mc, 28.0-29.0 mc. Crystals are available to allow the V to tune other frequencies of course. CW ops will be glad to note that the rig runs 300 watts and that they've shifted the carrier 1 kc into the passband to eliminate "leap-frogging."

Galaxy uses transistors for the audio amplifier, driver and output circuits and in the accessory vox plug-in unit. Not caring for vox myself, I am glad to find it now is optional. The transistors considerably cut down on the size of the unit; good move.

Though I've been conditioned to rely on Galaxy's advertised specs, I still wanted to see if this little black box could really put out 200 watts into my dummy load the way they said it could. In the CW position my Waters Dummy (no offense) Load Wattmeter read 200 watts right on the nose. The wattmeter doesn't read PEP watts (whose does?), but if it will put out 200 CW watts I guess it doesn't have any problem mustering up the 300 SSB watts input they claim.


Perhaps it isn't even necessary to bring this up, but the Galaxy V is every bit as stable as you could ask. I only mention this because I've gotten tired retuning the fellows I'm talking with after each transmission on another make transceiver that I've been using. That one is not in current production, so don't worry about it. The Galaxy V, even when freshly turned on, stays right on frequency. Good show.

. . . W2NSD/1

SG93/URM75 4-220mc Signal & Sweep Generator. Crystal Calibrator & Modulation. Manuals. For 60 cy. EX 67.75
 Ballentine 300 AC VTVM in 19" rack panel . . . EX 38.50
 Lambda 28 200-325VDC @ 100ma 1% Reg. 6.3VAC EX 22.50
 Lambda 32 200-325VDC @ 300ma 1% Reg. 2X6.3VAC. EX 31.75
 T61/AXT2 TV Xmtr W/Video & Sync Amplifiers . . . NEW 17.50
 RT82/APX6 Converts to 1215-1296 mc X'ceiver . . . NEW 21.75
 TS726 Tests APX6.27 Tubes, 10 diodes. For 60 cy. GD 14.50
 Manual for TS726/UPMS above. Navships 91537A . . . NEW 2.90
 SWR Bridge Micromatch-Reflectometer .30-1000mc. EX 8.25
 R23/ARC5 The "Q5-er" tunable IF. 190-550 kc. GOOD 11.75
 RT18/ARC1 100-156 Xceiver. W/tubes & DN9 . . . GOOD 19.75
 Same less tubes and Dynamotor DN9 . . . FAIR 9.75
 T465/ALT7 Xmitter 168-352mc W/2-6161s, 100W out EX 22.50
 Schematic for T465/ALT7 with parts values . . . 1.00
 Tube Type 6161 W/Plate, Grid, Cathode & Heater Connectors
 100 watts o'put to 900mc. 63 watts to 2000mc. . . EX 7.50
 SA325/U Coaxial Relay SP4T W/28 VDC Motor . . . EX 2.75
 UG210/U Coaxial Plugs for SA325 Relay, used . . . EX 3/1.00
 Set of 120 Xtals Type FT243 5675 thru 8650 kc in 25 kc
 increments. US tested and packed . . . 120/17.50
 Tripler Cavity for 2C39A tube. Less tube . . . NEW 3.00
 RF Amplifier Cavity for 2C39A. Less tube . . . NEW 4.50
 CU119A Coupler. 13 1-tube amplifiers w/tubes . . . NEW 4.75
 CU48/ARA6 50 ohm coax to twin-line coupler . . . NEW 2.25
 RE2/ARC5 Ant Relay W/Meter & Vacuum Capacitor EX 1.85
 C45 Control Box for ARC1 and ARC12 Xceivers . . . GOOD 1.35
 C732/ARC2 Control Box for ARC2 Xceiver . . . GOOD 1.85
 MT7A Mounting for one AR5 receiver . . . EX 1.50
 Meter Weston Model 843 500-0-500 microamps. 3" . . . EX 3.85
 Selenium Rectifier, 28VDC @ 4A, full wave . . . NEW 3/3.75
 IC/VRW7 Wire Recorder 28 VDC W/Tubes . . . GOOD 4.50
 RI22A/ARN12 75 mc Superhet w/tubes & xtal . . . EX 3.85
 UPM11A AFC chassis w/8 tubes & wiring diagram NEW 3.75

E. C. HAYDEN BOX 294 Bay Saint Louis
 Mississippi
 Shipment: FOB Bay Saint Louis. Terms: Net, Cash.

2 METER (almost) NON-DIRECTIONAL ANTENNA

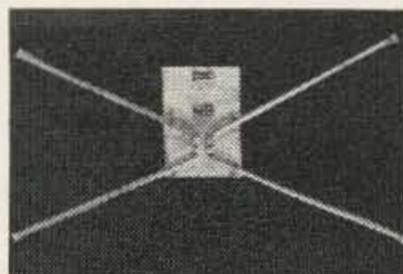

2M Con-ex

A rugged antenna for 2 meters that will give more gain and better coverage than a dipole. The Con-ex will withstand gales in excess of 100 mph. Perfect for local nets. An antenna every VHF ham can afford and should have for local contacts. Mounts for either vertical or horizontal polarizations.

\$8.95ppd in continental USA

ELL-CONN PRODUCTS

Box 83, Ellington, Conn. 06029

WOW

UNBELIEVABLE PRICES

TRANSMITTING, AMATEUR, SPECIAL PURPOSE, INDUSTRIAL TUBES !!

ALL BRAND NEW, INDIVIDUALLY BOXED, EIMAC, RCA, AMPEREX, ETC. NO PULLS, NO SECONDS, NO JAN. INDUSTRIAL QUALITY

FULLY GUARANTEED

6146 \$2.55	829B \$9.00	4X150A \$9.90
417A \$3.95	304TL \$27.50	6J6W \$.65


SEND FOR FREE CATALOG

Orders under \$4.00 include 40c handling. All shipments FOB Stirling, N.J. Include sufficient postage, excess refunded.

VANBAR dist.

P.O. BOX 444
 STIRLING, N.J. 07980

Clever Philological Quizze

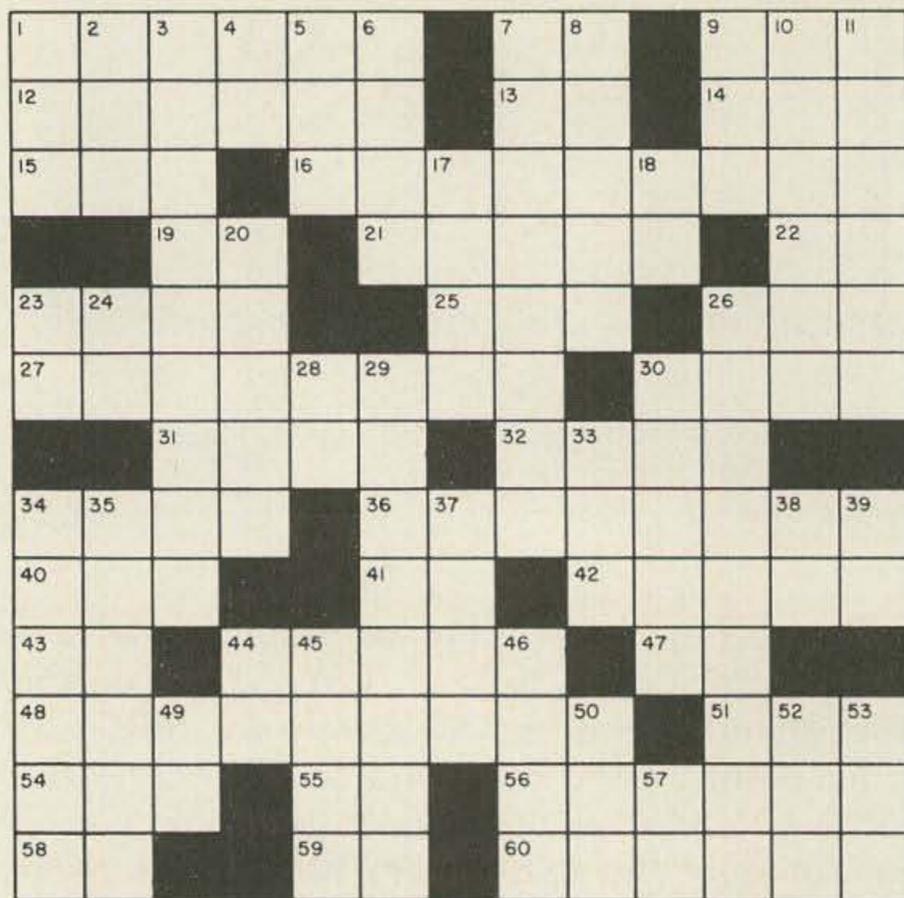

Max Winter K2PIJ
2444 Barker Avenue
New York 67, New York

Across:

1. Colored thread used in wire insulation to aid in identification
7. Abbreviation for radio bands at a higher frequency than broadcast
9. Classified notices
12. Vacuum tube having a specified number of electrons
13. Greek letter having many electronic applications
14. Type of coil winding
15. A square of butter
16. Clipping circuit in TV receivers
19. The: (Spanish)
21. Challenges
22. Marine officer (abbr.)
23. _____ fide
25. Periods of time (abbr.)
26. One side of a ship
27. Slang for microwave coax circuit
30. Physics term concerned with weight and acceleration
31. Mimic
32. Interjection
34. Reclines
36. Rhetorical comparison of negative and positive
40. Numerical value of brown
41. Continent (abbr.)
42. Speaker parts
43. Symbol for cerium
44. Adjust the beam in a cathode-ray tube
47. Continent (abbr.)
48. Units of electromotive force
51. Golfing equipment
54. University degree
55. Symbol for erbium
58. Symbol for tellurium
59. Compass direction
60. Wheatstone circuit used to measure impedance.

Down:

1. Portion of a hill best suited for microwave tower
2. Prominent electronic manufacturer
3. Reduce the strength of an electrical impulse
4. Symbol for cobalt
5. Man's name (plural)
5. Type of frequency meter
7. Arrangement of two electrodes used in early type transmitters
8. Paths for electric current
9. Liable
10. Type of tubes
11. Method of arranging circuit parts
17. Chess piece
18. Like
20. Sources of electric illumination
23. Temperature constant for a liquid
24. Electrical protective device (abbr.)
26. Type of iron core
28. Metal winding in some types of geiger tubes (abbr.)
29. Type of transformer
30. Sub-atomic particle
33. Chemical elements in hydrocarbons
34. Mounting device for tubes
35. Interior
37. Man's name
38. Symbol for tellurium
39. _____Q: abbreviation for Mister
44. British State Department (abbr.)
45. Heated enclosure for a quartz crystal
46. Open impedance path between two conductors
49. Unit of weight (abbr.)
50. Spanish for Mr.
52. Electronics expert (abbr.)
53. Summer: French
57. Symbol for bismuth

Solution on p. 90

Giant Inventory Reduction Sale! BIG SAVINGS on Hy-gain ANTENNAS


First come, first served -- Quantities limited

Hy-gain MULTIBAND DOUBLET


Complete multiband doublet antenna systems featuring Hy-Gain solid state traps for each band...copper clad stranded steel wire...high impact cyclac center and end insulators...52 ohm coax feedline. Built to take unlimited power...withstand winds up to 100 mph.



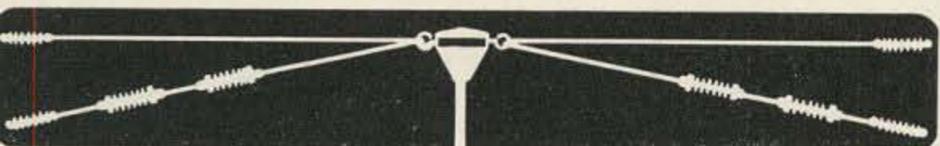Model 2BDT for 40 and 80 meters
Reg. \$19.95 HCJ Close-out \$14.50



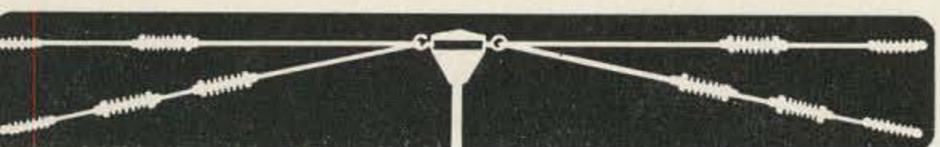Model 4BDT for 10 thru 40 meters
Reg. \$24.50 HCJ Close-out \$17.50



Model 5BDT for 10 thru 80 meters
Reg. \$34.95 HCJ Close-out \$24.50

40 & 80 Meter Trap Kit—Model 2TD
Two factory tuned solid state, slim line traps with hardware for attachment to antenna wire.
Reg. \$12.95 HCJ Close-out \$9.00

Hy-gain MULTIBAND VERTICALS

World Famous 14AVS for 10 thru 40 Meters

The world's most popular vertical — solid state traps completely factory pre-tuned. Delivers outstanding low angle radiation. Matchless weather-proof construction.
Reg. \$29.95 HCJ Close-out \$22.50




The 12AVS for 10, 15 & 20 Meters

Self-supporting trap vertical for 10-20 meters. Completely factory pre-tuned with SWR 2:1 or less. 13.5 ft. overall height. Reg. \$21.95
HCJ Close-out \$16.50

Hy-gain MULTIBAND BEAMS


Model TH3 THUNDERBIRD 3-Element Tribander for 10, 15 & 20 Meters

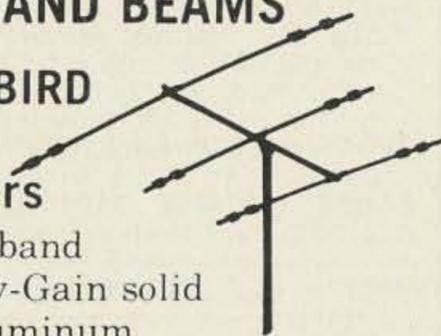A high performance multiband beam featuring famous Hy-Gain solid state traps. Rugged all aluminum construction. Completely factory pre-tuned. SWR less than 2:1. Reg. \$99.75 HCJ Close-out \$75.00




Model TH2 THUNDERBIRD 2-Element Tribander for 10, 15 & 20 Meters

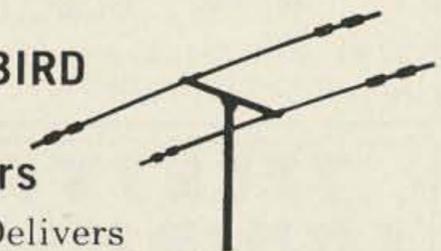Compact, easy to install. Delivers excellent performance. Features Hy-Gain solid state traps and rugged all aluminum construction. Rotates with TV rotator.
Reg. \$69.95 HCJ Close-out \$50.00



3-Element 20 Meter Monoband Beam Model 203B

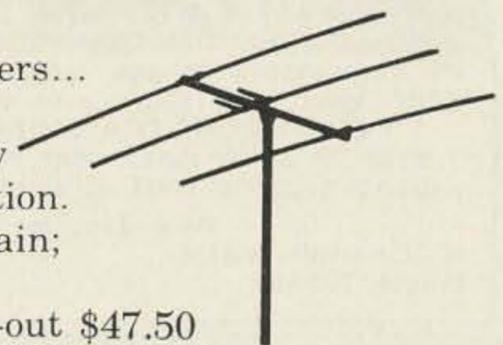A real bomb on 20 meters... featuring full-sized spacing and heavy duty all aluminum construction. Delivers 8db forward gain; 25db F/B ratio.
Reg. \$65.95 HCJ Close-out \$47.50



BARGAINS GALORE!

Outstanding bargains on many other models too numerous to mention...including HF and VHF mobile and base station antennas and VHF stacking kits. If we haven't advertised what you want, send us your requirements... we'll quote rock bottom prices.

H CJ ELECTRONICS

E 6904 Sprague Ave., Spokane, Washington
HAM HEADQUARTERS OF THE NORTHWEST

RUSH ME THE FOLLOWING:

1st Choice _____

2nd Choice _____

Here's my check for \$ _____

NAME _____

ADDRESS _____

CITY _____ STATE _____

RW APRIL BARGAINS

- BC-603 RECEIVER**—20 to 27.9 MC FM, 10 channel push button selector—also tuneable. Complete with all tubes & schematic. Used, Excellent. **\$34.95**
- TM 11-600 MANUAL** for BC-603 & BC-604. New. **\$1.50**
- APR-4 COUNTER MEASURES RECEIVER**—38 to 2,200 MC continuous with 4 plug-in tuning units. 117v 60cy power supply. Used, Excellent. **\$279.50**
- APR-4Y RECEIVER**—Same as above except AM & FM reception. With 4 tuning units 38-2,200 MC & 117v 60cy power supply. Used, Excellent. **\$319.50**
- CARBON COMPRESSION RHEOSTAT**—1500W, 0.01 to 2 ohms. 56 carbon plates 3" x 3". Brand New. **\$24.95**
- T-271/ART-28 RADAR RELAY TRANSMITTER**—Tuneable 460-510 MC. Xlnt for Ham-TV. Has two 4X150A final, with air sockets & axivane blower; 3E29 sync. mod, 6L6W video mod. & 11 other tubes, **two panel meters**, four ten turn dials & Schematic. Xlnt. **\$45.95**
- ART-13 SPEECH AMPLIFIER**—Has carbon & dynamic mike inputs. With 12SJ7 & two 6V6 tubes. Used good. **\$4.95**
- BC-453 VARIABLE CAPACITOR**—3 gang, each 36-346mmf with 2 air trimmers. BRAND NEW. **\$1.95**

WRITE FOR BULLETIN #41—LOADS OF BARGAINS

Send Check or Money Order—Minimum Order \$2.50
PLEASE INCLUDE AMPLE POSTAGE—EXCESS REFUNDED
Minimum C.O.D. Order \$10.00 with 25% Deposit.

R. W. ELECTRONICS, INC.

2244 South Michigan Ave. Dept. 734
Chicago, Illinois 60616 Phone CALumet 5-1281

TELETYPEWRITER EQUIPMENT AND COLLINS

51J2, 51J3, R-390A/URR Receivers (.50-30.5 MC). Teletype Printers #14, #15, #19, #20, #26, #28. Kleinschmidt Printers #TT-4A, TT-76, TT-98. Telewriter Frequency Shift Converter. Boemhe Keyers for CW. For general information & equipment list, write

ALLTRONICS HOWARD CO.,
Box 19, Boston 1, Mass. Richmond 2-0048.

SURPLUS BARGAINS

We have moved to new quarters to start the new year with. Lucky finds and scarce items.

TCS DYNAMOTOR MOBILE POWER SUPPLY
NEW 12 v dc input, 400 v dc @ 200 ma output.
\$3.95 postpaid west of Denver. \$4.95 postpaid east

Dow Trading Company

N. Dowdell W6LR 2057 E. Huntington
Elliott 7-3981 Duarte, California

LOOKING? SHOPPING? TRADING? TRYING TO SAVE MONEY?

Write Bob Graham for Special Deals on New and Re-conditioned used gear. Cash or Budget.

Graham Radio

Dept. C., Reading, Mass. Tel: 944-4000.

AMERICAN MADE TRANSISTORS

WHILE LIMITED
QUANTITY LASTS



4¢

SPECIAL LOW PRICE ONLY Each

A fortunate purchase allows us to offer these high priced computer grade transistors at such ridiculously low prices. All are mounted on printed circuit boards along with assorted components such as resistors, capacitors and a host of other surprises. You pay only for the transistors, other parts are FREE!

BUY 100 FOR \$4.00 or 1000 FOR \$35.00 PREPAID

... NOW TAKE ADVANTAGE OF THIS SPECIAL PRICE

SEND YOUR ORDERS TO **ALCO** LAWRENCE, MASS.

Letters

(Continued from page 65)

Dear OM,

Yesterday, when I returned home from the University of Iowa, I grabbed up the waiting March issue of "73"—a real bombshell. I was really surprised to see the first column and a half in the "de W2NSD/1" dept. devoted to "flying sorcerers." Apparently you have become interested enough to dig beneath a veneer of government smoke-screening and crackpot factions. Welcome to one of the biggest mysteries of the twentieth century.

The implications of the presence within our atmosphere of these strange, unknown objects are overwhelming if you have the courage to really think about it. And there is abundant and continually accumulating evidence that the objects are real, made by and controlled by intelligence, and that they do not originate on this planet; this regardless of what the Pentagon people preach.

Sooner or later, the populace has to find out, and the longer the government keeps playing games with the public, the worse it's going to be when finally it gets too big for the Pentagon boys to sit on.

Just in case you get more response on the saucers than on RM-499, and are stuck for references to reliable data on UFOs, may I suggest the National Investigations Committee on Aerial Phenomena, 1536 Connecticut Ave., N.W., Washington 36, D. C.? Perhaps you have heard NIAP, a private member supported organization, mentioned in some of your serious discussions about UFOs.

As you blaze away in the pages of "73" against the woes that beset the present and future of amateur radio, so has NICAP been crusading for recognition of the reality and the significance to humanity of the UFOs. NICAP has been plugging away for over eight years despite the government clamp down of significant data, and various attempts to discredit the group. Now things are beginning to pay off, especially with the current height of UFO activity in this country. The activity promises to exceed the much publicized saucer "flaps" of the early & mid 1950s, although the lack of news coverage wouldn't indicate this. And the Washington sightings are starting the new year off with a bang, as you well know.

NICAP is international in scope, with over 5,000 members, of which I am one. The group is non-political, non-profit; NICAP is dedicated to the belief that there is something going on in our skies which we should all know more about, MUCH more about. If you are interested in following the current situation, I suggest you join NICAP, or at least get a copy of their 1964 publication, "The UFO Evidence." It is an outstanding contribution in factual reporting, and is the result of years of investigation and evaluation of myriad UFO cases. I can pretty well guarantee that if you read the evidence, you will do some profound thinking about the whole UFO subject. Perhaps "73" will feel disposed to run a monthly column on the subject; "Green's Little Green Men," or something. Hi!

William H. Hunkins
IoAR NICAP
WA5EKQ/WAØKOM


Gentlemen:

DX-pedition may at times be an overworked expression, but I have one to report which is a "first" in the Post World War II Era from SP-land. Andre K. Krzysztolik SP5ALG took part in a DX-pedition from Poland via the Mediterranean to the Dead Sea area in 4X4-land. Andre SP5ALG left his native land on June 9, 1964 with a home-brew 200-watt rig, a Drake 2B receiver and a long-wire 80-meter antenna. After visiting such countries as SM, OZ, DL, PAØ, CN8 and 7X2 (ex-FA), his first transmissions enroute were from Sousse Tunisia with the call sign 3V8GM. A few QSO's were with W stations out of port then 200 contacts made from Tunisia. Enroute from 3V8 land to Israel, he touched on countries such as OD5, YK, and JY. While in Israel he was granted permission to operate with the call sign SP5ALG/4X4WF.

Together with Dr. Eric Friedman 4X4WF ex-SP6WF, he operated a DX-pedition station from the Dead Sea area with the call sign 4XØWF. The prefix 4XØ was used for the first time in Israel. Andre and Eric operated



SP5ALG

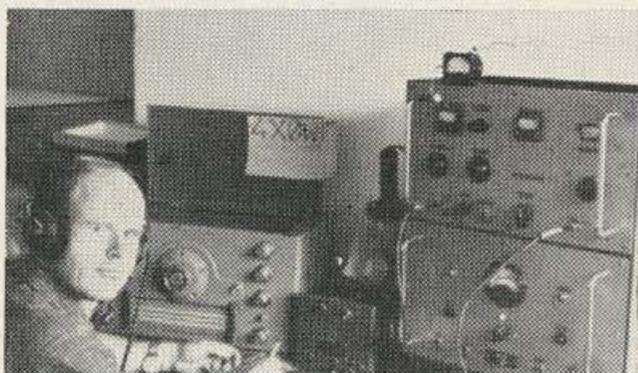

4X4WF

4X0WF for 60 hours continuously on October 18, 19 and 20, 1964. Unfortunately, conditions were very poor during the time that station 4X0WF was in operation; otherwise many more contacts would have been made. U.S.A. stations were worked on the 7 and 3.5 megacycle bands. Due to the depression of the land, conditions to Europe and to North America were very poor. Except for very heavy QRM from U stations, conditions to Oceania and Asia were very fine business. The prefix 4X0 is new for WPX. This DX-pedition was a very interesting one from the standpoint of QTH because the Dead Sea is located 1200 feet below sea level.

A couple of days later, Andre obtained for a call sign 4X4UJ and made scores of contacts from the City of Haifa. Andre left Israel November 25, 1964 for the U.S.A. via such countries as I, EA, ZB2 and EA8. He now hopes to obtain operating privileges on the ham bands. This stems from the fact that the U.S.A. has entered into reciprocal agreements with countries which allow U.S. radio amateurs the privilege of operating in their respective countries. All QSL's will be answered 100%; these include all QSO's made with ex-SP5ALG, 3V8GM, SP5ALG/4X4WF, 4X0WF, and 4X4UJ. Please address all QSL's via W2VLS.

W2VLS

Improving the 4-Band KWM-1*

Dear Wayne:

The following improvements have been made to my expanded KWM-1 resulting in all controls being on the front panel and no frequency jump when switching sidebands.

Replace R-115, the anti-trip pot with a Centralab FI-100K. Use a matching Centralab shaft thru it to actuate the switch in the final compartment. If you did not align the two, use a flexible shaft coupling to connect them.

Replace R-92, the mike-gain pot, with a Centralab FI-100K and matching shaft similar to the anti-trip control. Replace the SPDT slide switch for switching sidebands with a DPDT switch same size and same place. Connect the center of the second pole to ground and connect the upper sideband contact to a 36 pf capacitor in parallel with a 4-12 pf trimmer. Connect the other end of the capacitor and trimmer to pin 7 of V-22.

Connect the slide switch actuator to the shaft thru V-22 with a piece of piano wire so that you can operate the switch. With a little bushing or some shim stock you can use the original knobs on the 3/16" shafts. I cut discs for the knobs for the concentric pots of 1/8" plexiglass. You can probably get some concentric TV knobs to fit.


When you are through, tune in the calibrate note and adjust the trimmer so that it is zero beat on both sidebands.

* Four bands on the KWM-1' "73" Dec, 1963 pg. 60
Lou Weber K6GHU

BUDDY NUVISTOR PRE-AMP

2M - \$9.95 6M - \$8.95

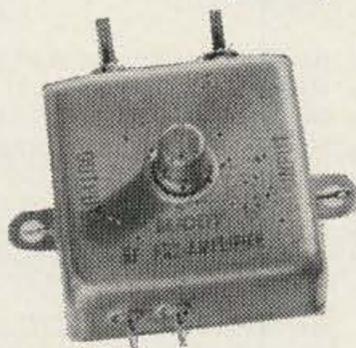- ★ Increases sensitivity up to 20 db.
- ★ Small size 2 x 2 7/8" fits anywhere
- ★ Completely wired and assembled



- ★ Reduces images
- ★ Improves selectivity
- ★ Simply installed
- ★ CB model \$7.95

Marina Communications
2912 Industrial Way
Santa Maria, Calif.

COMING SOON!

NEW AMECO 6 and 2 METER VFO

Heterodyne VFO with solid state oscillators. Highest stability—negligible warm-up time. Model VFO-62—\$59.95—write for details

Ameco Equipment Corp.

178 3/4 Herricks Road, Mineola, N. Y. 11501

URGENT, NEED IMMEDIATELY

Very high prices paid. Freight prepaid. AN/GRC; PRC; APR; APN; ARC; ALT; URM; UPM; TS. We also buy all military and commercial test, radar, and communication equipment.

CALL COLLECT. IT COSTS YOU NOTHING TO HEAR OUR HIGH OFFER.

SPACE ELECTRONICS

4178 Park Ave., Bronx, N. Y. • (212) CY 9-0300

TWO-WAY COMMUNICATION CRYSTALS


AMERICAN CRYSTAL CO.

PO BOX 2366 KANSAS CITY, MO.

NEW FROM TRANSCOM!

SBT-3

Transistor
SSB Transceiver
\$299.50

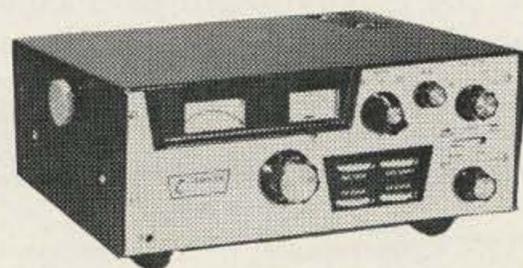

A completely new SSB transceiver styled and designed for mobile operation. The smallest, most compact transceiver and the biggest dollar-value in the field.

Smallest size: 4 3/8 x 11 3/8 x 8 3/4. Low battery drain: 500 ma in receive. Big voice: 165 watts PEP to 2-8042 instant heating tubes. Solid state switching, solid state circuits. Simple operation. Full phone coverage of 80, 40 and 20 m. Stable: Less than 100 cps drift in any 15 min period. Sensitive receiver: .5 uv for 10 db s/n.

SBD-3 mobile power supply: \$99.50

SBM-3 mobile mounting kit: \$3.50

Bank terms available

Western Radio

1415 India Street

San Diego 1, California

BEImont 9-0361

**AMATEUR TELEVISION is the EXCITING NEW FRONTIER
GO ON THE AIR NOW WITH A VANGUARD
MODEL 440 TV CAMERA**



\$149.95

VANGUARD Model 440

only **\$149.95** less
Vidicon and lens.
F/1.9 lens with focusing
"C" mount—\$18.95
Type 7038 Vidicon
Grade A \$85.00
Grade B+ \$75.00
Grade B \$60.00
Grade C \$35.00

Note: Grade C may be any type Vidicon new or used of our choice. Guaranteed to give satisfactory service for amateur use.

Save \$3.95. Camera with lens and Grade A Vidicon only **\$249.95.**

The VANGUARD Model 440 is built to the same rugged specifications as our Model 400 industrial camera and is complete with self-contained synchronizing generators, 4 mc. video amplifiers, power supply, tripod base, and TV transmitter with output in the 436-450 mc. band. You can transmit over

short distances with the output from the camera or drive a simple linear amplifier for any power you want. Sensitivity from one foot-candle to bright daylight using our vidicon and lens. Picture sharpness guaranteed to be equal to the best capabilities of any standard 525-line TV receiver.

Modular construction and printed circuits permit quick replacement and servicing of major circuits. Weighs 12 lbs.—measures approximately 8 1/4" x 6" x 6". Model #440-X with crystal-controlled horizontal scan available for only \$20.00 more.

Building your own TV camera? The following assembled and tested circuits will save you much time and money.

- POWER SUPPLY** with tripod plate—\$28.00.
- SWEEP and SYNC. GENERATOR.** Tested and complete with tubes—\$18.00.
- VIDEO AMPLIFIER** with **MODULATOR** and **R.F. STAGE.** for 436-450 mc. Tested and complete with tubes—\$22.00.

FOCUS COIL and DEFLECTION YOKE. Professional quality with full shielding and cosine wound yoke. Complete with vidicon signal ring contact, yoke and tube clamp—\$36.00.

More parts available—send 10c for complete catalog.



\$10.95 up

**VANGUARD
TRANSISTORIZED CONVERTERS**

New series 300 with 3 VHF-UHF transistors, crystal-controlled oscillator, tuned R.F. stage and low noise mixer. One microvolt sensitivity. More than 30 high quality parts carefully assembled and tested. Measure only 3" x 2 1/2" x 2". Operate at 12 volts DC 4-5 ma.

Nuvistor converters available from \$10. Circuit modules and government surplus equipment also available. Send 10c coin or stamps for complete catalog. For prompt shipment please include postal money order

Available in the following modules:

	Model	Input mc.	Output mc.	Price
2M	300-D	144-148	50-54	\$12.95 ppd.
	300-E	144-145	.6-1.6	\$12.95 ppd.
	300-F	144-146	28-30	\$12.95 ppd.
	300-Q	144-148	14-18	\$12.95 ppd.
6M	300-B	50-51	.6-1.6	\$10.95 ppd.
	300-C	50-54	14-18	\$10.95 ppd.
	300-J	50-52	28-30	\$10.95 ppd.
20M	300-G	14.0-14.35	1.0-1.35	\$10.95 ppd.
CB	300-A	26.965-27.255	1.0-1.29	\$10.95 ppd.
WWV	300-H	5.0	1.0	\$11.95 ppd.
Int'l.	300-I	9.0-10.0	.6-1.6	\$11.95 ppd.
CHU	300-K	7.3	1.0	\$11.95 ppd.
CHU	300-L	3.35	1.0	\$11.95 ppd.
Marine	300-M	2-3	.6-1.6	\$11.95 ppd.
Aircraft	300-N4	121-122	.6-1.6	\$13.95 ppd.
	300-N5	122-123	.6-1.6	\$13.95 ppd.
Fire, Police etc.	300-P	155-156	.6-1.6	\$13.95 ppd.
CUSTOM MADE	300-X	Choice of 1 input freq. and 1 output freq. between .6 mc. and 160 mc.		\$14.95 ppd.

All above converters are supplied with Motorola type connectors. For two SO-239 connectors instead, add 75c. N.Y.C. residents add 4% sales tax.

or cashier's check. COD's must include 20% deposit. N.Y.C. residents add 4% sales tax. Include sufficient postage for all items except converters and circuit modules which are postpaid.

VANGUARD LABS

Dept. H-4
190-48 99th Avenue
Hollis, N. Y. 11423

TWO METERS



**BIG performance—
little money!**

The new **FULRAD** transceiver does the job. A very hot little superhet receiver with excellent front end sensitivity and a transmitter with audio to spare. We work 200 miles with them. Complete with press-to-talk mike, AC power supply and five crystals. Output is monitored by RF take-off to a diode detector and a sensitive meter. Tune to maximum—one control only. Price—only \$165 amateur net. We can supply a 12 v DC to 115 v AC transistorized power supply for the above unit for \$25 extra. If you don't need the DC supply, why should you have to pay for it? We guarantee these units to be as described or your money back. **They are a fine unit.**

ARE YOU RUNNING A KW ON TWO?

Very few are, but—

How about getting the signal OUT?

We have an antenna that does that. With 20 db over on the front, we have only 4 S units on the sides and 3 S units from the back. By using a new design in reflectors we push all the signal towards the front end where it can be used. The beam is a seven element job with two more reflectors than usual (for a total of nine elements) with a special phasing cable that ties both dipoles together. It uses RG-8/U (52 ohm) cable.

Get one and work that DX station! **\$19.50.**

For even better results, get a pair with matching hardware and harness for only **\$45.**

Send check or money order. Antennas shipped prepaid in U.S.A.

Money back guarantee—if they do not work as stated.

FULTON ELECTRONICS
Manteca, California

W2NSD/1 from p. 2.

letters, not me, and he, not me, is thus immune from legal action.

If you are interested in getting a copy of the K6BX Extra News Letter #21, twenty-two large sized pages typed three columns to the page with Clif's extra small type, and packed with dynamite which may sweep the present headquarters heirarchy out of office, then send 50c for each copy (buy several and get the word spread) to K6BX, Box 385, Bonita, California.

Columns in 73? No, no, no, no, no, no!

Yes.

I can't fire 80% of you just because you disagree with me, and that was the percentage that answered the February questionnaire with suggestions for columns. Why you want me to louse up a good ham magazine with that sort of junk I can't imagine, but you do and I will and you'd darn well better keep reading the magazine after it gets junked up. As a matter of fact, you should make it your business to talk some friends or enemies into subscribing to make up for any of the 20% who wanted the magazine to stay the same that drop out in medium or low dudgeon.

What columns are we going to sprout? Well, I really don't know. That all depends upon our finding volunteers to write the columns. I figure that we really should have top experts for each field we try to cover. For instance, our propagation column is prepared by John Nelson who is recognized to be one of the foremost experts in the world on radio propagation. The Bureau of Standards only wishes that they could predict as far ahead and as accurately as John does in 73. His predictions have, time after time, been startlingly accurate when compared to predictions in other magazines.

Since 40.0% of you have requested a VHF column we obviously should have something along this line. I really don't know who should run the department. I'll try to come up with someone interesting. 32.4% requested a column on transistors. Hmmm. I guess we're in a good position to turn out something like this ourselves. Watch for a transistor column headed by Paul Franson WA1CCH, who also masquerades as Assistant Editor around here.

Before you get all excited over 73 filling up with all of this special interest stuff, let me explain what I actually have in mind. Rather than running two, three or four pages each month on each subject it seemed to me that we might be able to present the latest news of interest in something fairly short and

concise . . . something quite akin to the Station Activities segment of QST in looks, though one would certainly hope that it would be more interesting in content. If we devote about a half page to each column then the whole works shouldn't take over two or three pages about the same as other magazines devote to one single column.

Club Stations

The following exchange of letters will be of interest to all ops who plan to operate a club station or to operate any multi-operator station in any contests in the future.

Institute of Amateur Radio

26 January 1965

Secretary
Federal Communications Commission
Washington, D. C.

Dear Sir:

The Institute of Amateur Radio, Inc., a non-profit New Hampshire corporation with somewhat over 2500 licensed amateur members is planning on applying for a club station license with myself, the Secretary of the Institute, as trustee.

May I please have your decision on whether it will be legal for the Institute to permit operation of the club station by operators other than the trustee of the station with the trustee not in control of the station?

May I also have your decision on whether it will be legal for the Institute to permit operation of the club station by paid amateur operators?

I assume that both of these are legal since the precedent has been established by the ARRL with their station W1AW, but I wanted to be sure before any great investments were made in equipment and antenna arrays.

Yours truly,
Wayne Green W2NSD/1
Secretary
Institute of Amateur Radio

FEDERAL COMMUNICATIONS
COMMISSION
Washington, D. C.
20554
February 9, 1965

Mr. Wayne Green, Secretary
Institute of Amateur Radio
Peterborough, New Hampshire

Dear Sir:

This is in reply to your letter dated January 26, 1965, concerning operations in the Amateur Radio Service.

You are advised that, to meet his responsibility, the trustee of an amateur club station is not required to personally supervise and control all operations under the club's call sign. Instead, the trustee may delegate certain supervisory activities to a station manager or to other responsible club members. This leeway is permitted since the nature of a club's station operations often renders it impractical for the trustee to be in a position to exercise direct control at all times. The trustee is, however, expected to be able to assume direct control of the club station if it should prove necessary or expedient. He should also generally supervise operations by checking the station log, testing the equipment, assuring that the station is inaccessible to unauthorized persons, etc.

An amateur operator who has a pecuniary interest in his license or who receives material compensation for operation of an amateur radio station is in violation of the Commission's rules and is, therefore, subject to the imposition of severe administration sanctions.

Very truly yours,
Ben F. Waple
Secretary

CRYSTALS IN SUB-MINIATURE HERMETICALLY SEALED HC-18/U METAL HOLDERS. Half the size of a HC-6/U crystal. These crystals have wire leads 1/2 inches long. **CRYSTALS SELL AT \$1.05 each postpaid USA.** Ideal for transceivers and limited space applications. All crystals fully guaranteed. The following listed frequencies shipped immediately.

Quantity available				Frequency in Mcs.		
16.000	16.250	16.500	16.750	17.000	17.250	17.500
17.750	18.000	18.250	27.000	27.250	27.500	28.500
28.750	29.000	29.250	29.500	29.750	30.000	32.75
33.000	36.050	36.100	36.150	36.200	36.250	36.300
36.350	36.400	36.450	36.500	48.050	48.383	48.716
49.050	49.383	49.716	50.050	51.050	51.383	51.716
52.050	52.383	53.0075	53.050	53.383	53.2575	53.3075
53.7075	53.716	53.7575	53.8075	53.8575	53.9075	53.9575
55.050	55.383	64.992	65.992	66.992	67.992	68.992
69.992	70.992	71.992	72.992	73.000	75.000	78.000
79.000	80.000	81.000	82.000	83.000	84.000	85.000
86.000	87.000	88.000	89.000	90.000	96.000	97.000
98.000	99.000	100.000	101.000	102.000	102.86	103.06
103.26	103.26	103.46	103.66	103.86	104.06	104.26
104.46	104.66	107.000	111.000			

Limited quantity.						
25.750	25.250	32.500	33.250	50.716	61.050	74.000
103.000						

SAME CRYSTALS AS ABOVE. SAME PRICE. THIS LIST OF CRYSTALS IS AVAILABLE. HOWEVER I CANNOT SHIP UNTIL 10 DAYS AFTER RECEIVING YOUR ORDER. LISTING MAY NOT BE IN ORDER SO DISREGARD SEQUENCE.

Available in Quantity				Frequency in Mcs.		
14.000	14.050	14.100	14.150	14.200	14.250	14.300
14.350	14.400	14.450	14.500	14.550	14.600	14.650
14.700	14.750	14.800	14.850	14.900	14.950	16.950
17.000	17.350	17.450	17.550	17.650	17.800	17.850
23.500	23.750	24.000	24.250	24.500	24.750	26.250
26.500	26.750	27.750	28.000	28.250	30.250	30.500
30.750	31.000	31.250	31.500	31.750	33.100	33.200
33.300	33.400	33.500	33.600	33.700	33.800	33.900
36.550	36.600	36.650	36.700	36.750	36.800	36.850
36.900	36.950	41.000	41.050	41.100	41.150	41.250
41.200	41.300	41.350	41.400	41.450	41.500	41.550
41.600	41.650	41.700	41.750	41.800	41.850	41.900
41.950	42.050	42.150	42.250	42.450	42.550	42.650
42.750	42.850	42.950	42.400	44.740	45.50	46.240
46.400	53.0575	53.1075	53.1575	53.2075	53.3575	53.4075
53.4575	53.5075	53.5575	53.6075	53.6575	54.050	54.383
54.716	55.716	56.050	57.716	60.050	73.992	74.992
75.992	76.992	77.992	78.992	79.992	80.992	81.992
82.992	83.992					

JUST ARRIVED — CRYSTALS IN FT-243 TYPE HOLDERS. — CRYSTALS SELL AT \$1.05 each postpaid USA. Frequency Tol. .05%. All crystals fully guaranteed. Quantity available.

1900	1905	1910	1915	1920	1925	1930	1935	1940	1945
1950	1955	1960	1965	1970	1975	1980	1985	1990	1995
2000	2005	2010	2015	2020	2025	2030	2035	2040	2045
2050	2055	2060	2065	2070	2075	2080	2085	2090	2095
2100	2105	2110	2115	2120	2125	2130	2135	2140	2145
2150	2155	2160	2165	2170	2175	2180	2185	2190	2195
2200	2205	2210	2215	2220	2225	2230	2235	2240	2245
2250	2255	2260	2265	2270	2275	2280	2285	2290	2295
2300	2305	2310	2315	2320	2325	2330	2335	2340	2345
2350	2355	2360	2365	2370	2375	2380	2385	2390	2395
2400	2405	2410	2415	2420	2425	2430	2435	2440	2445
2450	2455	2460	2465	2470	2475	2480	2485	2490	2495
2500	2505	2510	2515	2520	2525	2530	2535	2540	2545
2550	2555	2560	2565	2570	2575	2580	2585	2590	2595
2600	2605	2610	2615	2620	2625	2630	2635	2640	2645
2650	2655	2660	2665	2670	2675	2680	2685	2690	2695
2700	2705	2710	2715	2720	2725	2730	2735	2740	2745
2750	2755	2760	2765	2770	2775	2780	2785	2790	2795
2800	2805	2810	2815	2820	2825	2830	2835	2840	2845
2850	2855	2860	2865	2870	2875	2880	2885	2890	2895
2900	2905	2910	2915	2920	2925	2930	2935	2940	2950
2955	2960	2965	2970	2975	2980	2985	2990	2995	2945
3000	3005	3010	3015	3020	3025	3030	3035	3040	3045
3050	3055	3060	3065	3070	3075	3080	3085	3090	3095
3100	3105	3110	3115	3120	3125	3130	3135	3140	3145
3150	3155	3160	3165	3170	3175	3180	3185	3190	3195
3200	3205	3210	3215	3220	3225	3230	3235	3240	3245

THE ABOVE LISTED CRYSTAL FREQUENCIES ARE IN KILOCYCLES

LOW FREQUENCY CRYSTALS IN FT-243 TYPE HOLDERS. Crystals sell at \$1.05 each postpaid USA. All crystals fully guaranteed.

Limited quantity available. Freq. in Kcs. Give 2nd choice select									
1005	1010	1020	1055	1070	1090	1170	1200	1235	1240
1265	1270	1310	1375	1400	1405	1420	1610	1100	1115
1125	1130	1300	1350	1355	1380	1440	1730	1765	1780
3270	3400	3430	3440						

CRYSTAL OVEN — LARGE SIZE — PLUGS INTO 5-PIN TUBE SOCKET. ACCEPTS 1" x 1" TYPE BLANKS. FREQUENCY CAN BE ADJUSTED BY TURNING PRESSURE TYPE ADJUSTMENT SCREW. CAN BE TAKEN APART SO NEW BLANKS CAN BE USED. HEATER VOLTAGE 6.3 V. THERMOSTATICALLY CONTROLLED. IDEAL FOR EXPERIMENTING AND ECT. ONLY \$1.50 each postpaid USA.

QUAKER ELECTRONICS PO. BOX 215 HUNLOCK CREEK, PA.
THE CRYSTAL KING

ARROW SPECIALS

PANADAPTER Convert this IP69C/ALA2 per June 1964 issue 73. New with tubes.	\$22.50
Used with tubes.	\$17.50
R19/ARC4 2 meter receiver—tunable 118 to 148 mc. Complete with 9 tubes.	\$29.95
COLLINS RECEIVER R105/ARR15. 1500 to 18500 kc. Complete with 14 tubes.	\$47.50
T271/ART28 420 mc transmitter	\$69.50
APX6 TRANSPONDER 1296 mc. Complete with tubes.	\$14.95
COLLINS Single Side Band Multiplex Generator using mechanical Filter #F84Z-2 or similar	\$24.50
T179/ART26 TV Transmitter Complete with all tubes	\$49.50
NICAD BATTERIES BB 403—3½ AH	\$1.49
AS 400—20 AH	\$3.95
2C39A Tripler cavity—Less Tube	\$3.95
ELECTRONIC GALVANOMETER Cohu Model 204	\$175.00

Tubes		Tubes	
2C39 — \$5.00	807 — \$1.00	902PI — \$3.00	
2E26 — 2.00	808 — 1.00	5763 — 1.00	
3B24 — 1.00	813 — 9.00	5894 — 12.00	
5R4GY — 1.00	815 — 2.50	6146 — 2.00	
6L6G — 1.00	832A — 4.00	304TH-TL — \$27.50	
4X150A — 6.50	416B — 5.00	866AX — 2.50	

Send for Catalog #131 — FREE —

ARROW SALES-CHICAGO, INC.

2534 S. MICHIGAN AVENUE
CHICAGO 16, ILLINOIS

JUST RECEIVED—SPECIAL BARGAINS

BC-453	190-550 KC rec. used, very clean, with DM-32A, 24v DC dynamotor	\$15.50 \$16.00
R77/ARC-3	100-156 MC, 8 channel, crystal controlled rec. with tubes, internally complete, & schematic, ex. used.	\$17.50
T67/ARC-3	100-156 MC, 8 channel, crystal controlled, transmitter, with two 832A, all tubes, schematic, ex. used	\$17.50
RT18/ARC-1	100-156 MC, 8 channel, crystal controlled, transceiver (2-er). Internally complete, two 832A, all tubes, less dynamotor. With schematic, conversion booklet, ex. used	\$25.00
RT82/APX-6	Transponder. Get on 1215 mc quickly. Excellent used, less all tubes.	\$10.00
Antenna	Collapsible, 4 section, 4 to 10½". ¼" tapering. Chrome plated. For field strength meter, transistor radio; BRAND NEW 4 for \$1.10	29c ea.
5000 mfd. 35v DC lytic, 2" dia. 4½" high, take-outs,		50c ea; 6/\$2.75
9 pin, shield base, ceramic miniature sockets, NEW,		23c ea; 5/\$1.00
9 pin, shield base, TEFLON, miniature sockets, NEW,		29c ea; 4/\$1.10
7 pin, ceramic wafer socket, for 832, 829, 826, etc. SYL. NEW		79, 4/\$3.00
7 pin, as above, take-outs, NAT'L.		50c ea; 4/\$1.85

TUBE OVERSTOCK

I've tired of lookin at 'em! Bigger savings.
6DQ5* was \$1.75—now \$1.35; 5933* (807W) was \$1.50—now \$1.25; 1616 was \$1 now 89c
were 89c—now 79c or 4 for \$3
6AG7*; 5R4GY*; 5T4; 5992 (10,000 hour 6V6); 5751*; 5814
were 79c—now 69c or 4 for \$2.50
VR-105; VR-150; OA2*; OB2*; 5651*; 6AQ5W/6005*;
12AX7*; 12A7WA
were 69c—now 59c or 4 for \$2.25
6AK5*; 6AG5*; 6AL5*; 6AQ5*; 6AU6* 12SX7 (selected 12SN7GT); 12A6
were 29c—now 23c or 5 for \$1
955; 957; 76; 1626; 12C8*; 6K7*; 6H6*; 717A*; 6SH7*;
12SH7*; 7193*

*Pull outs from unused equipment. Fully guaranteed.

Others BRAND NEW. Minimum tube order \$3.00

SAVE YOUR LOOT—bring it to (I'll have a load of GOODIES): Swapfest, DeKalb, Ill. May 2 Hamfest, Sullivan, Ill. Apr. 25.

All orders, except in emergency or I'm at a hamfest, shipped same day received. For free GOODIE sheet, send self addressed stamped envelope—PLEASE, PLEASE—include sufficient for postage & insurance. Any excess returned with order.

B C Electronics

Telephone 312 CALumet 5-2235
2333 S. Michigan Ave. Chicago, Illinois 60616

Secretary
Federal Communication Commission
Washington, D. C.

Dear Sir:

Your letter of February 9, 1965 would seem to indicate rather unarguably that an amateur may not operate an amateur radio station for pay.

Yet I am faced with the seeming contradiction of the operation of amateur radio station W1AW, the official station of the American Radio Relay League, Inc. W1AW has been in operation for many years with, I must assume, paid operators. Of course there is always the possibility that some sort of transparent fiction has been used to circumvent the law.

Please tell me under what arrangement W1AW is able to operate with paid amateur radio operators so that the Institute of Amateur Radio, Inc., a non-profit New Hampshire corporation for the benefit of amateur radio, can establish its own official club station for use in transmitting code practice and messages of specific interest to all radio amateurs.

Very truly yours,
Wayne Green W2NSD/1
Secretary
Institute of Amateur Radio, Inc.

As you can see, the FCC has decided, in an interesting exercise of illogic, that although the licensee of an individual amateur station must be in control of the station if his call is to be used, in the case of a club station the club call can be used with all operators, even with the station trustee not present or in control.

Applying this new interpretation of our rules to contest operations, such as Field Day, we find that club calls can be used where the club has a license of its own, but that in cases where the call of a member would normally be used the operators must each use their own call when operating. The ARRL has indicated that they intend to do battle with the FCC on their interpretations of the rules because the new "rules" will cause considerable difficulty to their contests and awards. Tsk, tsk.

\$100 Reward

The slides I took while DXpeditioning on Navassa during the KC4AF operation are of great sentimental value to me and I will pay \$100 for their return, no questions asked. Last known whereabouts of the slides: CQ had 'em and refused to part with them.

We Want Money


A letter from one of our authors suggested that I take a quick survey to find out how many other authors are owed money by one of our ham magazines. Apparently one of our competitors is considerably in arrears. If all of you who are owed money for published articles will drop me a note giving the name of the magazine, the month and year published and the name of the article I will try to put together an "arrears" figure and publish it in 73. I will not embarrass you by publishing

TS 418A 400-1000 meg signal generators, AM, PM or CW emission	\$325.00
Baird Atomic 162 Glow transfer counters	\$100.00
Ballantine 300 Voltmeter	\$60.00
Millivac MV-17C Voltmeter 1mv-1000V	\$75.00
Hewlett Packard 616A Signal Generator 1.8 KMC-4.0 KMC	\$600.00
Dumont 304A scope with 264B voltage calibrator	\$100.00




Potter model 471 chronograph counter to 8 Mega-cycles with manual \$400.00
 8100 MFD at 20 volts electrolytic condensers, new
 \$.75 ea., 10 for \$6.00

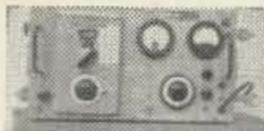RCA WV 84A DC Microammeter without batteries \$30.00



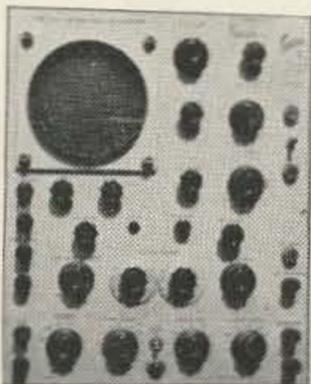TS-497B 2-400 Meg Signal Generator with manual \$225.00



Tektronix 512 Scopes \$225.00
 Tektronix 513D Scopes \$300.00
 Tektronix 514D Scopes \$275.00

All equipment used and surplus, in good condition.

Orders FOB Cambridge, Mass.
 Sorry we do not issue catalogs or lists

ELI HEFFRON & SONS, INC.

321-329 ELM STREET

CAMBRIDGE 39, MASS.

EL 4-8572

your name or call . . . all I will give will be the total figure reported to me.

Late News

More news on the million dollar libel suit facing Huntoon and ARRL. Last month I reported that an expensive law firm had been retained by the League to fight the case. Now I understand that none other than Louis Nizer is to be their counsel . . . and the last I heard his fees start at around \$25,000. Well, the case against them looks formidable to me . . . John really put his typewriter in it this time in a letter to all member clubs (one of his famous "Dirty Letters") and the entire League has to pay for this blunder. Watch for full details in QST . . . hi.

I understand that three Directors are shopping for a new general manager.


Re RM-499 . . . no new news. All is quiet. Stay that way.

Our DX column starts this month on page . . . The mails permitting, we will have a month-long letter from Gus telling us what major things are going on and what he is hearing from up there in Bhutan. I never would have suspected that anyone would have a DX column edited from AC5 land. . . . Wayne

AIRDUX #195-2 1KW PI DUX Assembly	\$14.50 value for \$4.50
Sarkes Tarzian F-6 Sil. Rect. (1N2484) new	10 for \$3.75
600 PIV 750 MA.	
Meters, 2 3/8" square, White fig. Blk. Backgrd.	
Marked "Plate Current" 0-200 ma.	\$3.25
"S-Units" 0-60 ma.	3.25
Dial Plates, 1 7/8" Dia. Aluminum, Black Nos.	
0 to 100 in 180 degrees	\$1.00/Doz.
Crystals, CR-23—10005.000KC, 16105.000KC,	
20505.000KC, 27505.000KC, 34505.000KC,	
35005.000KC, 35505.000KC, 36005.000KC	85c ea.
5894 tubes, New \$6.50, with socket \$7.25,	
socket 85c	
2 Meter Coax Band Pass Filter, Brass, Silver	
Plated, Hi-Q, will also tune to 1.4 meters	
	\$8.75 Prepaid
4 inch National Co. "Velvet Vernier" dials, 5-1	
ratio	\$1.75
2 inch Meter, 500 microamps	\$2.25
4X150As pullouts	\$3.50
4CX300As pullouts	\$11.50
With SK-711 socket	\$ 16.50
With SK-711 socket only	\$7.50
JFD Piston Trimmer Caps Type QS-173, 0.6 to	
5.5 mmf \$8.25 value each, New original	
Pack	20 for \$9.00
Hewlett Packard 475B tunable Bolometer Mts.	\$75.00
General Radio 667A Inductance Bridges	\$135.00
Waterman S-14-A Pocketscopes New	\$249.50
Our price used	\$89.50

Government Warehouse, Inc.
 264 Shrewsbury Ave., Red Bank, N. J.

ARC-1 for 2-meters

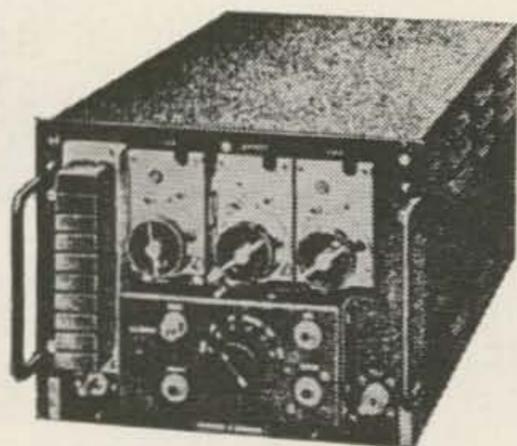

ARC-1 Navy Surplus Transmitter Receiver Xmtr, uses 832A in final, 20 watts input, with AM push-pull plate modulation. Ten crystal controlled channels. Freq range 100-156 Mc. Receiver has extra, separate guard channel which can be tuned for your net frequency. Complete with tubes, schematic diagram, and conversion instructions for AC power supply and tunable oscillator. Shipping wt. 50 pounds. Used good. \$24.95

POWER SUPPLY KIT for ARC-1

115 volts, 60 cycles input. Including transformer, silicon rectifiers, punched chassis, and all necessary parts. Fits inside ARC-1 case. Shipping wt. 10 pounds. \$19.95

Coax connector adapters. New stock, American-made.

UG-201A/U Tflon. Adapts BNC plug to type N jack. \$1.05
UG-273/U. Adapts BNC plug to SO-239 jack. 87c
UG-1094/U Teflon. Single-hole mounting BNC jacks. 48c each.

BEAUTIES IN USED GEAR

Heath Marauder \$279.95
Collins 75A-1 with C. E. Model B Slicer connected \$250.00

Send for our catalog

JEFF-TRONICS

4791 Memphis Ave.

Cleveland, Ohio 44109

Little Known Facts?

RTTY: 3620, 7040, 7140, 14090, 21090 kc.

WBFM: 52.525, 146.94 mc.

220mc: 9 PM Tuesdays

432mc: 9 PM Wednesdays

Don't: XU, HS, XV, 3W, PK, PO, YB, YH, 7A, 7I, 8A, 8I.

Patch: CE, CO, CP, EL, HC, HH, HI, HK, HP, HR, OA, TI, VE, XE, YN, YS, YV, ZP and KB-KZ.

VHF-UHF

Converters & Preamps.
50 thru 432 Mc.

Write for literature

Parks Electronics, Rt. 2, Beaverton, Ore.

Back Issues of 73

All issues after March 1961, 50c apiece.

January 1961 not available

Oct., Nov., Dec. of 1960 and Feb. and Mar. of 1961,
\$1 each.

Beautiful red binders with gold lettering for 60-61, 62,
63, 64, and 65. \$3.

Bound volumes for 1962, 1963 and 1964. \$15

CALL LETTER DOOR MATS

Personalize the QTH with your own call letters permanently molded in a rubber door mat. Made in four (4) colors, red, blue, green and black, large 18" x 28" size.

\$5.98 — prepaid, specify color

United Plastic Mold

9607 S. Atlantic Blvd.

South Gate, California

More New Products

Rub-on Drafting

A fast new way to draw perfect schematics is now available. It is made by Datak and is called the "Electronic Drafting Symbol Set." It includes all common schematic symbols letters and numerals according to MIL-STD-15-1A. This newest dry transfer marking set features a special heat-proof adhesive that will withstand repeated passes through the hottest diazo whiteprinters with no cracking or fraying. Schematics made with this set are so crisp they appear to have been inked and then photographically reduced. The complete opacity of the transferred patterns results in flawless reproduction by any method. Each set contains a complete assortment of 40-5 x 7 inch sheets. Refills assorted to order are available. Electronic Drafting Symbol sets are \$15.95 complete (Catalog #970). Get more data from the Datak Corporation, Guttenberg, New Jersey.

Quig

Sprague is giving a little bonus with their Atom Electrolytic Capacitors. These little connectors fit on cut leads for easy repairs. They are small springs made of a special wire that has a copper-covered steel core, a layer of flux and an outer jacket of solder. They're mighty good for initial wiring and replacement of parts in almost inaccessible places.

Solution to puzzle on p. 80

T	R	A	C	E	R		S	W		A	D	S	
O	C	T	O	D	E		P	I		P	I	E	
P	A	T		S	E	P	A	R	A	T	O	R	
		E	L		D	A	R	E	S		D	I	
B	O	N	A			W	K	S		L	E	E	
P	L	U	M	B	I	N	G		M	A	S	S	
		A	P	E	R		A	H	E	M			
S	I	T	S			O	P	P	O	S	I	T	E
O	N	E				N	A		C	O	N	E	S
C	S		F	O	C	U	S		N	A			
K	I	L	O	V	O	L	T	S		T	E	E	
E	D	B		E	R		U	N	B	E	N	T	
T	E			N	E		B	R	I	D	G	E	

DOUBLE BONUS

\$25

WORTH OF

- TRANSISTORS
- RECTIFIERS
- RESISTORS
- CONDENSERS
- DIODES ■ ETC

Add 25¢ for handling

BOTH FREE WITH ANY \$10 ORDER

PLUS
CHOOSE
ANY
\$100
ITEM
FREE

SILICON POWER RECTIFIERS

D.C. AMPS	50 PIV 35 RMS	100 PIV 70 RMS	150 PIV 105 RMS	200 PIV 140 RMS
7	<input type="checkbox"/> .25	<input type="checkbox"/> .35	<input type="checkbox"/> .49	<input type="checkbox"/> .59
16	<input type="checkbox"/> .45	<input type="checkbox"/> .65	<input type="checkbox"/> .75	<input type="checkbox"/> .90
25	<input type="checkbox"/> .75	<input type="checkbox"/> .85	<input type="checkbox"/> .95	<input type="checkbox"/> 1.10
50	<input type="checkbox"/> 1.60	<input type="checkbox"/> 1.90	<input type="checkbox"/> 2.30	<input type="checkbox"/> 2.80

D.C. AMPS	300 PIV 210 RMS	400 PIV 280 RMS	500 PIV 350 RMS	600 PIV 450 RMS
7	<input type="checkbox"/> .79	<input type="checkbox"/> .95	<input type="checkbox"/> 1.05	<input type="checkbox"/> 1.29
16	<input type="checkbox"/> 1.10	<input type="checkbox"/> 1.35	<input type="checkbox"/> 1.50	<input type="checkbox"/> 1.70
25	<input type="checkbox"/> 1.20	<input type="checkbox"/> 1.50	<input type="checkbox"/> 1.70	<input type="checkbox"/> 1.90
50	<input type="checkbox"/> 3.50	<input type="checkbox"/> 4.20	<input type="checkbox"/> 5.25	<input type="checkbox"/> 7.00

WORLD'S MOST POPULAR \$1 PARTS PAKS

- 4 TRANSISTOR TRANSFORMERS, asst. worth \$25 \$1
- 40 WORLD'S SMALLEST RESIST., 5% too, 1/10W \$1
- 60 CERAMIC CONDENSERS, discs, npo's to .05mf \$1
- 40 PRECISION RESISTORS, asst., 1%, 1/2, 1, 2W \$1
- 10 ELECTROLYTICS, FP & tubulars, to 500mf \$1
- 30 SPRAGUE MYLAR condensers, asst. val., volts \$1
- 75 ASST. HALF WATT RESISTORS, 5% too \$1
- 35 TWO WATTERS, resistors, 5% too, A-B too \$1
- 40 DISC CONDENSERS, to .01 to 1KV, mylars too \$1
- 10 RCA PHONO PLUG 'n' JACK SETS, tun-amps \$1
- 60 HI-Q RESISTORS, 1/2, 1, 2W to 1 meg. 5% too \$1

FACTORY TESTED SEMI-KON-DUCTORS

- 6-1AMP 400V epoxy rectifiers, made by Sylvania \$1
- 3-2N255 TRANSISTORS, or equals, TO3 cases \$1
- 4-2N1059 TRANS., npn, by Sylvania, TO22 case \$1
- 1-2N1613 3W NPN SIL. 120 mc, by "Rheem" \$1
- 1 20W SILICON MESA, 2N1648, 2N424 equals. npn, \$1
- 5-2N107 TRANSISTORS, pnp, audio, by "G.E." \$1
- 3 CBS 35W PWR TRANSTRS. 2N1434, pnp, stud. \$1
- 3-20 WATTERS. 2N1038/42, w/sink by TEXAS \$1
- 3-2N341 NPN SIL. ONE WATT, by Transistron \$1
- 10 PNP SWITCHING TRANSISTORS, TO5 cases \$1
- 4-2N43 OUTPUT TRANSISTORS, by GE, pnp, TO5 \$1
- 4-2N170 TRANSISTORS, by GE, rf, npns \$1
- 10 NPN SWITCHING transistors, like 2N388, etc. \$1
- 5 ONE WATT ZENERS, 6V, gold axial by Transistron \$1
- 4 CK721 TRANSISTORS, in new alum. cases, pnp \$1
- 10 "PIN HEAD" TRANSISTORS, rf, if, pnp \$1
- 2 500MC, 2N964, epitaxial, mesa, pnp, TO18 cases \$1
- 3-300MC TRANSISTORS, 2N1264, by Sylvania \$1
- 4 TRANSISTORS, 2N35, by Sylvania, npn, TO22 \$1
- 2-25-AMP SILICON RECT., (1) 50V, (1) 100V \$1
- 2 TRANSISTORS, 2N497, 2N498, made by Rheem \$1

NEW TRANSITRON SCRs SILICON CONTROLLED RECTIFIERS

PRV	7 AMP	16 AMP	25 AMP	PRV	7 AMP	16 AMP	25 AMP
25	<input type="checkbox"/> .50	<input type="checkbox"/> .85	<input type="checkbox"/> 1.20	250	<input type="checkbox"/> 2.30	<input type="checkbox"/> 2.65	<input type="checkbox"/> 3.10
50	<input type="checkbox"/> .85	<input type="checkbox"/> 1.20	<input type="checkbox"/> 1.40	300	<input type="checkbox"/> 2.60	<input type="checkbox"/> 3.00	<input type="checkbox"/> 3.40
100	<input type="checkbox"/> 1.35	<input type="checkbox"/> 1.80	<input type="checkbox"/> 2.20	400	<input type="checkbox"/> 2.90	<input type="checkbox"/> 3.25	<input type="checkbox"/> 3.75
150	<input type="checkbox"/> 1.60	<input type="checkbox"/> 2.10	<input type="checkbox"/> 2.65				
200	<input type="checkbox"/> 1.75	<input type="checkbox"/> 2.40	<input type="checkbox"/> 2.90				

FULLY TESTED

- MAGNETIC SWITCH burglar alarms, with magnets \$1
- FILAMENT TRANSFORMERS 115 v. to 6.3 V 3.A. \$1
- 25 'CERAFIL' WORLD'S SMALLEST COND. to .05 m \$1
- 10 TRANSISTOR SOCKETS for pnp-npn transistors \$1
- 10 VOLUME CONTROLS to 1 meg. switch too \$1
- 3 INFRA-RED PHOTO DETECTORS, long leads \$1
- 30 'CORNING' LOW NOISE RESIST'S, 1/2, 1, 2W \$1
- \$25 RELAY SURPRISE, assorted SUBMINIATURE \$1
- 50 COILS & CHOKES, rf, if, osc, peaking, etc. \$1
- \$25 RADIO 'n' TV SURPRISE, wide variety \$1
- 10 TRANSISTOR ELECTROLYTICS, 10 to 100mf \$1
- 50 RADIO & TV KNOBS, assorted colors, styles \$1
- 50 MICA CAPACITORS, to .01mf, silvers too \$1
- 30 POWER RESISTORS, to 50W to 24Kohms \$1
- 60 TUBE SOCKETS, receptacles, audio, plugs, etc. \$1
- 60 TUBULAR CONDENSERS to .5mf to 1KV \$1

DUAL TRANSISTORS

NPN SILICON PLANARS \$1.98

	W.	V.	Gain	Freq.
<input type="checkbox"/> 2N1613	.8	50	to 120	100
<input type="checkbox"/> 2N2060	.6	60	to 150	—
<input type="checkbox"/> 2N1132*	.6	35	to 90	100

*pnp, others npn

"Press-Fit" 25 Amp 600V RECTIFIERS \$1

- 3-2N329A NPN TRANSISTORS, by Ratheon \$1
- 5-30 MC TRANSISTORS, 2N247, by Sylvania \$1
- 10-WATT ZENER STUD ANY VOLTAGE 3V to 200V \$1
- 2-2N718 NPN SILICON PLANARS, by Fairchild \$1
- 10 2-AMP RECTIFIERS, 50 - 400 PIV studs \$1
- 1 3N35 TETRODE 150mc TRANSISTOR, silicon \$1
- HOFFMAN SATELITE SILICON SUN CELL, 3/8x1" \$1
- 4 2N219 TRANSISTORS, mixer-conv, by Sylvania \$1
- 15 PNP & NPN SWITCHING transistors, by TEXAS \$1
- 10 1000MIL CERAMIC RECTIFIERS 50 - 400 PIV \$1
- 10 CK722 TRANSISTORS, pnp, made by Raytheon \$1
- 10 MICRO DIODE STABISTORS, EPOXY silicon \$1
- 4-1AMP 700V TOP HAT RECTIFIERS, SILICON \$1
- 4 TRANSITRON 1N429 ZENER REFERENCES \$1
- 2 2N706 500MW, 300MC NPN PLANAR, TO18 \$1
- 15 TRANSISTORS, osc-ifs-driver-p.p. by Ratheon \$1
- 4 . 2N333 NPN SILICON TRANSISTORS Sylvania \$1

TRANSITRON Planar Controlled		FACTORY TESTED Switch		10 WATT ZENERS	
<input type="checkbox"/> 15	9.00	Sale	1.00	<input type="checkbox"/> 5V	1.00
<input type="checkbox"/> 30	11.25	.98	Each	<input type="checkbox"/> 6V	
<input type="checkbox"/> 60	14.70	1.21		<input type="checkbox"/> 12V	
<input type="checkbox"/> 100	21.60	1.37		<input type="checkbox"/> 14V	<input type="checkbox"/> 70V
<input type="checkbox"/> 150	33.00	1.60		<input type="checkbox"/> 20V	<input type="checkbox"/> 80V
<input type="checkbox"/> 200	36.00	2.22		<input type="checkbox"/> 24V	<input type="checkbox"/> 90V
<input type="checkbox"/> 300	41.25	2.40		<input type="checkbox"/> 42V	<input type="checkbox"/> 100V
		2.75		<input type="checkbox"/> 45V	<input type="checkbox"/> 110V
				<input type="checkbox"/> 60V	<input type="checkbox"/> 124V

<h3 style="text-align: center;">3-TRANSISTOR AMPLIFIER</h3> <ul style="list-style-type: none"> • Only 3"x2"x3/4" • Printed circuit • Wired, subminiature <h2 style="text-align: center;">\$1.49</h2>	<h3 style="text-align: center;">GERMANIUM DIODE 100</h3> <h2 style="text-align: center;">Sale FOR \$1</h2> <p style="text-align: center; font-size: small;">untested.</p>
---	---

SOLID STATE XMTR/OSC. PHILCO

Item resembles pic. Only **2.98**

Crystal freqs: 40 to 60mc. Use as freq. standard, marker, osc, etc. Wired, printed circuit. ONLY 2 x 2 x 3/4" With crystal thermistor 1200MC transistor.

PARTS BY THE POUND

500-1000 pcs

ONE POUND DISCS **4⁸⁸**

TRANSISTORS **100 for \$2⁹⁵**

Power, Audio, RF, untested

10¢ GIANT SPRING CATALOG ON:

Parts Zeners
 Rectifiers Transistors SCRs PAKS

POLY PAKS

TERMS: send check, money order, include postage—avg. wt. per pak 1 lb. Rated, net 30 days. CODs 25% down.

P.O. BOX 942A
SO. LYNFIELD, MASS.
"PAK-KING" OF THE WORLD

CAVEAT EMPTOR?

- ★ Price—\$2 per 25 words for non-commercial ads; \$5 per 25 words for business ventures. No display ads or agency discount. Include your check with order.
- ★ Type copy on standard size paper. Phrase and punctuate exactly as you wish it to appear. No all-capital ads. Include your signature with order.
- ★ We can only accept ads related to ham radio. We will be the judge of suitability of ads. Our responsibility for errors extends only to printing a correct ad in a later issue.
- ★ For \$1 extra and an SASE, we can maintain a reply box for you.
- ★ We cannot check into each advertiser, so Caveat Emptor . . .

CLEANING OUT SHACK—Transistors, diodes, etc. Send list of required units or write for list of units on hand. WA5FYF, 4336 Livingston, Dallas, Texas, 75205.

INDIANA HAMFEST: and picnic, July 11, Brown County State Park, near Nashville, Indiana. Come.

HAM MISSIONARY WITHOUT RIG will soon have one if you send your contribution to Brother Thomas Radio Fund, Walsh College, Canton, Ohio. Brother Thomas Paquet K1RCE of the order that directs Walsh College teaches in Bukoba, Tanzania (Box 95).

SAVE \$75. NEW Drake TR-3 and AC-3 supply \$525 plus shipping. First check takes it. Robert D. Corbett, 46 Prospect St., Torrington, Conn. 06790.

HAM TV Deflection & Focus Coil Kit with complete Instruction Manual of a 5 tube Vidicon Camera for only \$16.95. Send 10c for information. ATV Research, P.O. Box 396, South Sioux City, Nebraska, 68776.

GOLD—You will find a "Gold Mine" in our used equipment. Write for list. W9KP—Green Mill Radio Supply, 145 W. 111th St., Chicago, Illinois 60628.

COLLINS 75S-1 with 500 cycle CW filter. Perfect condx with power cord and manual. \$325 C. Boutell, 3059 W. Ruskin Ct., Milwaukee, Wisconsin 53215.

HALFWAVE DIPOLE ANTENNA. Custom built to any frequency you request. Complete with 50' of coax. 2 KW PEP capacity. \$5 postpaid. Adiabatic Enterprises, Box 151, Albany, California.

HW-12 with Heath AC power supply, like new: \$150; RME 6900: \$150; Collins 310B, all bandswitching: \$75. Irvin Weinman, W9HMO, 4718 N. 80th St., Milwaukee, Wis.

WANT Communicator I, II, III or IV. State condition and price. Lile G. Wismer W3DKR, 442 N. Main St., Sellersville, Pa.

RTTY SALE: Model 15, table, P/S, \$85. Model 14 typing reperforator, \$60. Model 14 TD, \$30. All \$150. K1AJE, Box 829, Haley Rd., Kittery, Maine.

BAMBOO FOR QUADS: Highest quality Calcutta bamboo. 18 to 20 ft. lengths cut to 14 ft. Straight with no cracks or splits. Set of 8, \$15.95 FOB. George Faltin K2PNR, PO Box 137, Syosset, L. I., N. Y.

NC-183-D, Eico 720 and 10-40 Mosley vertical. Very good condition. FOB your QTH. \$200.00. Frank Levering K7PFV, P.O. Box 449, Hayden, Arizona.

GLOBE 300A with instruction manual. No shipping \$125.00. W1FDN, Reading, Mass.

QSP far and wide April Extra News Letter exposes ARRL political rot and scandal from 1958 to date. Documented for Historical record. 50c copy. Clif Evans K6BX, Box 385, Bonita, Calif.

DIRECTORY OF CERTIFICATES & AWARDS. ONLY one in world. World's amateur and SWL achievement awards and how to get them, \$2.50. Clif Evans K6BX, Box 385, Bonita, Calif.

UNIVERSALLY ADAPTABLE ECONOMY QSL cards & Eye-Ball QSO cards. 100 for \$1. 200 for \$1.85. Postpaid. Clif Evans K6BX, Box 385, Bonita, Calif.

DIRECTORY EXTRA Newsletter, quarterly. FREE PRESS news of world Amateur affairs. CHC & FHC & SWL-CHC news. Over 2000 DX QSL Manager listings. \$2 a year. Clif Evans K6BX, Box 385, Bonita, Calif.

HEATH SENECA 6-2 METERS with modulator all \$165.00. 720 Eico Transmitter with Crystals \$75.00. WA4HYA. Earl Wood, 120 Noble Ave., N. E. Roanoke, Virginia 24012.

DYNA-PAK—completely transistorized unit; used as signal generator, voltage monitor, continuity tester, code oscillator, code monitor and other uses. \$2.98 Deltronic Labs Box 128, Horsham, Pa.

PRINTED CIRCUIT KIT—complete; two copper clad boards 2½ X 5, etch tray, etchant, etching resist, layout grids, cleaning pad, instructions. \$2.98 Deltronic Labs Box 128, Horsham, Pa.

QSL's \$1.75/100. Eye-catching, different. Sparkling gold or silver printed on six exciting Hi-Gloss cardstock colors. Samples 5c. Nu-Print, Dept. A. 322 Page Boulevard Springfield, Mass.

DUMMY LOAD, 50 ohms. All bands up to legal limit. Size, 3 x 4 x 7. Coax connector. Kit \$7.75, wired \$9.75 plus shipping. Ham Kits. Bx 175, Cranford, N. J.

COMPLETE SHACK—National NC-98 rcvr, Vm Viking II, Heath Kit VF-1, VFO, Pre-Selector RMI DB-23, Speech Clipper RME, Q-Multi, like new, in operation \$325.00 W2JGQ Isaacs 231 East 11th St. N. Y. 3.

COLUMBUS ARC HAMFEST. Columbus, Ga. March 28, 1965. Contact K4UYC for more information.

ORLANDO ARC HAMFEST at the Cherry Plaza Hotel April 23-25. Displays, tech talks, swap shop, Sat. night dance. Contact Betty Kuller WA4JIU, 401 Halsey St. Orlando, Fla.

PLATE TRANSFORMERS for that solid state power supply. 690 v at 450 ma. No CT. 117 v primary. Hermetically sealed. 19 lbs. \$3.95 plus postage. ARC Sales P. O. Box 12, Worthington, Ohio.

75S-3, 312B-3, 32S-3, 516F-2, 30L-1. All mint condition at \$1650. Will ship prepaid. WA5BAU, 7424 Edwin N.E. Albuquerque, N. M.

QRT COLLECTING; Selling antique wireless items and other stuff. What do you want? Free lists. Send large stamped addressed envelope. W6LM. P. O. Box 308, Wrightwood, Cal.

HEATH SWEEP GENERATOR TS-2, \$26. Dumont 241 Scope, \$65. Globe Hibander 6 and 2 meters, \$1.95. Gonset Communicator I, 2 meters, \$105. Heath HG10 VFO, \$25. W2FNT, 18 Hillcrest Terrace, Linden, N. J.

WANTED: Hallicrafters S-51 receiver, covering 132 kc to 13 mc. Describe condition fully, stating price. Peter Spiliotis, 6 Brentwood Circle, Danvers, Mass.

SOUTHERN TIER ARC DINNER, April 3, 1965, 7 pm, St. John's Ukrainian Hall, Johnson City, N. Y. For tickets, contact W2SDA, 1165 Vestal Avenue, Binghamton, N. Y.

FREE! BLUE BOOK LIST. Leo offers hundreds of bargains on reconditioned gear. Viking II \$97.70; NC300 \$189.00; Collins 62S-1 \$625.50; King 500A \$259.00; SP600 \$296.65; HT-37 \$254.15; DX-40 \$40.50; Cheyenne \$49.18; CE-10B \$69.00; SX-101 \$160.65; PRO310 \$299.00. Many more, also free 1965 catalog. WØGFQ, WRL, Box 919, Council Bluffs, Iowa.

ELDICO SSB 100F. Very stable \$300. Joystick antenna and tuner \$15. 6N2 converter \$30. LP filter \$5. Kreco 10 M coax vertical, unpacked \$25. FOB. R. Lamb, 1219 Yardley Rd., Morrisville, Pa.

CONVERTERS \$10 and up. World's largest selection of frequencies. Ham TV vidicon cameras and parts at low factory-direct prices. See them all now in our full page ad in this issue. Vanguard Labs, 190-48 99th Ave., Hollis, N. Y. 11423.

DIRECTIONAL COUPLERS, identical to M. C. Jones, Model 500. Coupler and meter new! \$15.50 post-paid. Jim Morgan 3693 Section Road, Cincinnati, Ohio 45237.

WAN 240—For sale, excellent condition, with HB ac supply, Turner ceramic mike, \$225. Transceiver alone available \$200 fob. K1SCC, Boulder Circle, Glastonbury, Connecticut.

ENGRAVED PLASTIC 7" x 3" signs—first name and all—black, walnut, mahogany, with base \$3.00. Pinbadges 1/2" x 3/4"—black or blue—first name and call \$1.00. I & M ENGRAVING—P. O. Box 2143 Culver City, Calif.

TELETYPE RIBBON modification kit for Model 15. Few surplus. Nylon ribbon automatically re-inks, outlasts 50 ordinary ribbons. \$4.95, postpaid. Telemethods, 3075 E. 123rd, Cleveland, Ohio 44120.

TELETYPE TEST SET I-193C, Government surplus. Generates perfect 22 millisecond pulses (60 wpm) for adjusting RTTY transmitters, repeaters, converters, etc., for zero bias. Also tests and adjusts polar relays. Complete with tool kit, manuals, four polar relays. Brand new. \$24.95, F.O.B. Harrisburg, Pa. Telemethods, 3075 E. 123rd Street, Cleveland, Ohio 44120.

32 THE EASY WAY. Nuvistor superreg receiver-tuner for 432 mc. Add any audio amplifier for exciting listening. Tested and guaranteed. \$12.90. UHF, 5111 Genesee St., Buffalo, N. Y., 14225.

NEW RDR 235 to 395 MC RECEIVER. 15 tubes, built-in 12 volt power supply, 155 page manual, \$25. Manual only, \$4. Conversion Aug '62 73. Precision tuning Fork, 400 cy., \$10. Polar Relay, \$2. 30 Miniature Relay Circuit Board, \$8. Bauer Industrial Supply Co., 17170 Redford, Detroit, Mich.

SPECIAL on single hole chassis mount UHF coax connectors with screw-on hood for either RG/8 or RG/58. Specify which. \$4.99 each or three for \$1.30. Postpaid. A.R.C. Sales, P.O. Box 12, Worthington, Ohio. No COD's. USA only.

THE BEST WAY TO BUY SURPLUS:

Ask for what you need. We will then send you **COMPREHENSIVE DATA** on what we have to meet your needs. **DON'T** ask for a catalog . . . it would take a fat book . . . and then it would give you less details about the thing you are interested in than we will give you in answer to your letter. Be as specific as possible as to frequency, power needed, etc.


For example, we have **THIRTY DIFFERENT MODELS** of calibrated-output laboratory-grade Signal Generators ranging from 10 kc to 21,000 mc, and some with power outputs over 10 watts for R.F.I. work, etc. Some FM, some PM, some CW and/or AM.

We have Meters, VTVM's, Bridges, Galvos, Voltage Dividers DC and AC, Digital Voltmeters DC and AC, Counters, Pulse Generators and Delay Systems, other Frequency Meters than those mentioned above, wide variety of Regulated Power Supplies, Line Voltage Regulators from 1/2 to 10 KVA, Tektronix and other Oscilloscopes, scope Cameras, many types of Graphic Recorders, Spectrum Analyzers, Teletype, Tuning-Fork-controlled Oscillators, Direction Finders, FM Ground Station, Tube Testers, Noise & Field Strength Meters, Ultrasonic generators and test gear, Aeronautical Radio Test Gear, etc. etc. and etc. . . . and we **KEEP BUYING NEW MATERIAL ALL THE TIME!** Just got in some laboratory Calorimeters, a few Magnetometers, a high-vacuum pump, and even a shipboard Rangefinder and two complete Submarine Periscopes! Much material is here today and gone tomorrow, but we keep a lists of WANTS and will notify you if the item you need gets acquired.

We **DON'T** sell mdse the way we get it in just to be able to advertise at a price lower than someone else's. We work it over . . . test it . . . overhaul and calibrate it . . . and **GUARANTEE SATISFACTION OR MONEY REFUNDED!**

We **ALSO BUY** so if you have anything to sell, tell us about it and how much you want for it. When we answer your inquiries and describe material we are offering, we also price it. . . . You wouldn't think very much of us if we asked you to make us an offer!

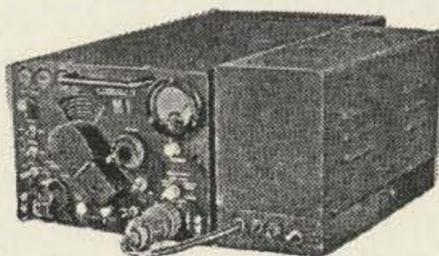BROADCAST-BAND COMMAND RECEIVER: ARC Type 12, No. R-22. Late type! 540-1600 kc, 6 tubes: RF, converter, 2 IF's & AVC, det. & Noise Limiter, & AF. 2 uv sensit. Needs external pwr sply & control ckts & has no tuning dial. With spline tuning knob, chart to turn exact freq. by turns count, lots of tech data, OK **17.95** grtd.
(Add \$3 for extra-clean selected unit.)



ALL-BAND SSB RCVR BARGAIN: Hallicrafters R-45/ARR-7. 550 kc to 43 mc continuous: Voice, CW, MCW: 2 RF's. 2 IF's: S-meter: 455 kc Xtl. 6 select. choices. Ready to use. w/60 cy pwr sply & book aligned. fob Los Angeles **199.50**

Deduct \$30 if you make your own pwr sply from schematic we furnish. Deduct \$20 if SSB not required, or deduct \$15 if you will wire in your own SSB with kit & diagram we furnish.

TIME PAY PLAN: Any purchase totaling \$160.00 or more, down payment only **10%**

ARC-5 Q-5'er Rcvr 190-550 kc w/85 kc IF's. Use as 2nd converter for above or other rcvrs. Checked electrically. w/lots of tech. data. w/spline knob. 9 lbs. fob **14.95** Los Ang.
(Add \$3 for extra-clean selected unit.)

AC PWR for SCR-522: RA-62-B made by Signal Corps for the specific job! 115/230v, 40 60 cy in. Regul. & flt. outputs 300v, .26A; 13v, 4A; -150v, 10 ma. OK **29.95** grtd, w/data, 90 lbs. fob Sacramento

AN/APR-4 RECEIVING UNIT w/tuning units to tune 38-1000 mc plug & handbook. all checked & grtd 100% **179.50** OK, ready to use on 60 cy

Add \$30 for am/fm version modified for 60 cy pwr input: add \$60 for TN-19, 975-2200 mc; add \$125 for TN-54, 2175-4000 mc. All uncond. grtd. OK.

LM FREQ METER 125 kc to 20 mc is combin. heter. freq. meter & signal source. CW or AM, accuracy .01%. xtl calib. Clean, checked 100% grtd. w/plug, data. **57.50** 16 lbs fob L A


Add \$10 for EAO, converts for LM Power Supply w/parts, data, included.

TS-323/UR, 20-480 mc. Crystal. 001%. W/handbook supplement giving supplementary xtl check points & instruc. to closely approach crystal accuracy. W/schematic, instruct., pwr sply data, clean, checked. 100% grtd. fob **199.50** Los Ang.

R. E. GOODHEART CO., INC.

Box 1220-GC BEVERLY HILLS, CALIF. 90213

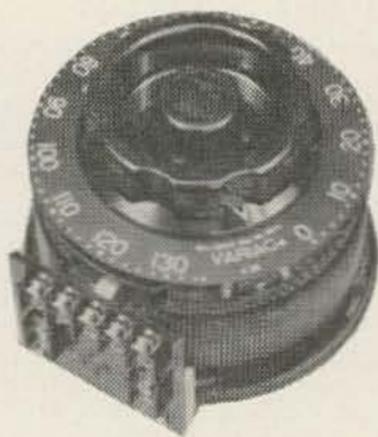Phones: Area 213, office 272-5707, messages 275-5342.




GENERAL RADIO

VARIAC 26 amp max output model V-20, 115 volts AC 60 cycle in. 0-135 volts out. These are brand new surplus w/knob & plate. Priced about 1/2 cost.

\$24.00

88 MH TOROIDS. Two types available. Open and potted. Used for many applications such as power supplies and teletype.

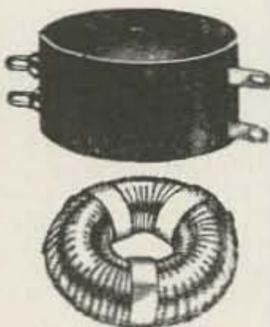Open style 50c each, 12/\$5.00
Potted style 65c each, 12/\$6.00




MESHNA

19 ALLERTON ST., LYNN, MASS.

All Material F.O.B. Lynn, Mass.

SIGMA Relays 115 volt, 60 cycle, 2 amp contacts SPDT.

75c ea. 8 for \$5.00

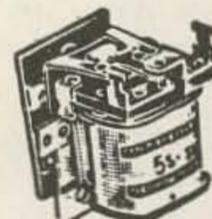


SIGMA: DPDT, 5 amp contacts, operation 1.5 volt dc or 12 v ac. DPDT Enclosed, plug-in \$1.00 ea. 6 for \$5.00

SPECIAL: 6 cartons \$25.00 Carton 40 Rolls \$5.00
TELETYPE PUNCH TAPE Buy 2, save on shipping.

AN/ART-13 100-WATT XMTR
11 CHANNELS
200-1500 Kc
2 to 18.1 Mc

\$39

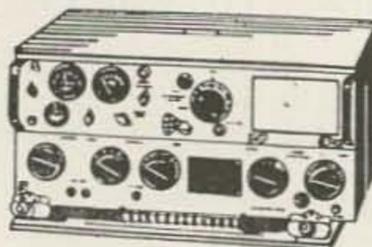

Collins Autotune Transmitter, extremely stable and suited for side band. Written up in QST Oct. issue 1953. Used, with tubes.

CQ's NEW Conversion Book \$3.00. Pages of surplus Conversions plus 3 articles on ART-13.

Meshna's new Winter catalog now ready. Send 20c for yours before they are all gone.

Don't forget:

Subscription to 73: \$4

73 Books: March, page 73

Caveat Emptor?: Only \$2

Gus: page 4

INDEX TO ADVERTISERS

Alco, 82
Algeradio, Jan. 65
Alltronics-Howard, 82
Ameco, 83
American Crystal, 83
Amplidyne, Feb. 65
Amrad, 84
Arrow Electronics, Dec. 64
Arrow Sales, Chi., 88
Atlantic, Oct. 64
ATV Research, Mar. 65
Aztec, Jan. 65
Babcock, 40
Barrett, Dec. 64
Bc Electronics, 88
Budwig, 68
Burghardt, 57
Burststein-Applebee, Jan. 65
B & W, Mar. 65
Callbook, 78
C & H, Feb. 5
Columbia, Mar. 65
Cornell-Dubilier, Jan. 65
Cubex, Jan. 65
Cushcraft, Cover II
Datak, Feb. 65
Dayton Hamfest, 64
Daveco, 41
Denver Crystals, Feb. 65
Denson, Jan. 65

Digication, Nov. 64
Dow Key, Mar. 65
Dow Trading, 82
Drake, 15
East Coast, Jan. 65
Editors & Engineer, 35
Edwards, 73
Electronicraft, Jan. 65
ESL, Dec. 64
Eli-Comm, 79
Evans, 71
Fair, 68
Fichter, 68
Finney, 20
F-M, Dec. 64
Fulton, 86
Gain,
Galaxy, Mar. 65
Gem Electronics, Feb. 65
Gift Shop, 84
G & G, Feb. 65
Glass, J. J., Mar. 65
Gonset, Feb. 65
Goodheart, 93
Government Whse., 89
Graham Radio, 82
Hammarlund, Mar. 65
Hayden, 79
HCJ, 81
Heffron, 89

Henry, 69, 77
Hill, Feb. 65
Hi-Par, 75
Hi-Way, Nov. 64
Hotel Rex, Mar. 65
Hy Gain, Dec. 64
Internal Xtal, 5
Jefftronics, 90
Juge, Mar. 65
Justin, Nov. 64
Lafayette Radio, Dec. 64
Linear Systems, Mar. 65
Mann, Mar. 65
Marina, 83
Master Mobile, 45
Meshna, 94
Mission, 47
Mor-Gain, 72
M & W, Dec. 64
Mosley, Mar. 65
National, Cover IV
Newtronics, 13, 63
Parks, 90
Path, 71
Poly-Paks, 91
Quaker, 87
Quement, 55, 65
Reyco, Mar. 65
Rohn, 4
RW Electronics, 82

Salch, Mar. 65
Saxton, Dec. 64
Scientific Asc., Mar. 65
Selectronics, Feb. 65
Sideband Engineers, 42, 43
Skylane, 84
Space, 83
Spitz, Dec. 64
Squire-Sanders, Oct. 64
Serman, 36, 50, 61
Super-Q, Dec. 64
Swan, 33
T A B, 95
Technical Material, Dec. 64
Telrex, 18, 49, 68
Tepabaco, Dec. 64
Texas Crystal, 9
Transistors Ult., Mar. 65
Tri-Ex, 21
U. T. C., Mar. 65
Vanbar, 79
Vanguard, 85
Viking, Mar. 65
Waters, 19
Western (Calif.), 83
Western (Neb.), 84
Western (Neb.), 84
Wilson, 84
World Radio Labs, 96, Cover III
Yatter, Dec. 64

"TAB" * TRANSISTORS * DIODES!!
GTD! FACTORY TESTED —
FULL LEADS.

PNP 100Watt/15 Amp HlPower
T036 Case! 2N441, 442, 277,
278, DS501 up to 50 Volts/
VCBO \$1.25 @, 5 for \$5.
2N278, 443, 174 up to 80V
\$3 @, 2 for \$5.



PNP 30 Watt, 2N155, 156, 235, 242,
254, 255, 256, 257, 301, 392, @ 35c, 4 for \$1
PNP 2N670/300Mw 35c @, 4 for \$1
PNP 2N671/1Watt 50c @, 3 for \$1

PNP 25W/TO 2N538, 539, 540, 2 for \$1
2N1038 6/\$1, 1039 4/\$1, 1040 \$1
PNP/T05 SIGNAL 350Mw 25c @, 5/\$1
NPN/T05 SIGNAL IF, RF, OSC 25c @,
6 for \$1

Silicon PNP/T05 & T018 25c @, 5 for \$1
2N1046/\$1.40 @, 3/\$4. 2N1907/\$2 @, 4/\$6
Power Heat Sink Finned Equal to 100
Sq" Surface \$1 @, 6 for \$5
T036, T03, T010 Mica Mtg 30c @, 4/\$1
Diode Power Stud Mica Mtg 30c @, 4/\$1

ZENERS 1Watt 6 to 200v 70c @, 3/\$2
ZENERS 10Watt 6 to 150v \$1.45 @, 4/\$5
ZENER Kit Asstd up to 10w 3 for \$1
STABISTORS up to 1watt 5 for \$1

TRANSISTORS—TOO MANY! U-TEST

Untested Pwr Diamonds/T03 10 for \$1
Untested T036 up to 100Watts 3 for \$1
Untested T05/SIGNAL/sistors, 20 for \$1
Untested Power Diodes 35 Amp 4 for \$1
Untested Pwr Studs up to 12Amp 12 for \$1

D.C. Power Supply 115v/60 to 800
Cys. Output 330 : Tap 165V up to
150Ma, Cased \$5 @, 2 for \$9

SILICON POWER DIODES * STUDS

DC AMP	50Piv \$5Rms	100Piv 70Rms	150Piv 105Rms	200Piv 140Rms
3	.08	.14	.17	.24
12	.30	.55	.70	.85
18*	.20	.30	.50	.75
35	.70	1.00	1.50	2.00
100	1.65	2.05	2.50	3.15
240	3.75	4.75	5.75	8.75

DC AMP	300Piv 210Rms	400Piv 280Rms	500Piv 350Rms	600Piv 420Rms
3	.29	.30	.40	.48
12	1.00	1.35	1.45	1.70
18*	1.00	1.50	Query	Query
35	2.15	2.45	2.75	3.35
100	3.75	4.60	5.50	8.00
240	11.70	17.10	23.94	29.70

***P.F. PRESS-FIT AUTOMOTIVE TYPE!**

18 Amp Press Fit up to 200Piv 4/\$1
2 to 3 Amp Studs up to 600Piv 6/\$1
35 Amp Studs 150 to 200Piv 5 for \$5

"TAB" * SILICON 750MA DIODES
NEWEST TYPE! LOW LEAKAGE

Piv/Rms	Piv/Rms	Piv/Rms	Piv/Rms
50/35	100/70	200/140	300/210
.05	.09	.12	.14

Piv/Rms	Piv/Rms	Piv/Rms	Piv/Rms
400/280	500/350	600/420	700/490
.15	.19	.23	.27

Piv/Rms	Piv/Rms	Piv/Rms	Piv/Rms
800/560	900/630	1000/700	1100/770
.35	.45	.65	.75

GTD ALL TESTS AC/DC & LOAD!

1700 Piv/1200 Rms/750 Ma/\$1.20 @,
10/\$10
Same 1100 Piv/770 Rms 75c @, 16/\$11
3 Kv/2100 Rms/200 Ma/\$1.80 @, 6/\$10
6 Kv/4200 Rms/200 Ma/\$4 @, 3/\$9
12 KV/8400 Rms/200 Ma \$8 @, 2/\$14

SCR—SILICON CONTROL RECTIFIERS!

PRV	7A	16A	PRV	7A	16A
25	.60	1.00	260	2.70	3.00
50	1.00	1.35	300	3.00	3.45
100	1.60	2.15	400	3.75	3.90
150	1.95	2.45	500	4.75	4.80
200	2.20	2.80	600	5.45	5.65

UNTESTED "SCR" Up to 25 Amps, 6/\$2
Glass Diodes IN34, 48, 60, 64, 20 for \$1

Two RCA 2N408 & Two Regulators
RCA IN2326 on prtd ckt. 30c @, 4/\$1



"TAB" Tubes Factory Tested, Insptd.
Six Months Guaranteed! No Rejects! Boxed!
GOVT & MFGRS Surplus! new & Used

Low Prices! New XMTTG Tubes!

4-65A	\$7.00	4X150A	\$6.75	OB2	.55
4-125A	15.00	826	Query	5R4WGA	
4-400A	25.00	829B	7.20		3.50
4-1000A	75.00	872A	3.50	24G	Query
		OA2	.65		

We Swap Tubes! What Do/U Have?

OA3	.80	5R4	1.00	6F7	.99
OC3	.70	5T4	.90	6F8	1.39
OD3	.59	5V4	.89	6H6	.59
OZ4	.79	5Z3	.89	6J5	.59
IL4	.82	6A7	1.00	6J6	.59
IR4	5/\$1	6A8	.99	6K6	.59
IS4	.78	6AB4	.59	6L6	1.19
IS5	.68	6AC7	.72	6SN7	.72

Send 25c for Catalog!

IT4	.85	6AG5	.65	6V6GT	.90
IT5	.95	6AG7	.75	12AU7	.69
IU4	6/\$1	6AK5	.69	12A6	.45
IU5	.75	6AL5	.55	25L6	.72
2C39A	Q	6AQ5	.66	25T	4.00
2C40	5.50	6AR6	1.95	28D7	.89
2C43	6.50	6AS7	3.49	50L6	.59
2C51	2.00	6AT6	2/\$1	83V	.95

We Buy!	We Sell!	We Trade!			
2D21	.65	6BA6	.59	250TL	19.45
2K25	9.75	6BE6	.59	VR92	5/\$1
2K28	30.00	6BK7	.99	388A	3/\$1
2V3	2/\$1	6BQ6	1.19	416B	16.00
2X2	.48	6BY5	1.19	450TL	43.00
4X250B	30.00	6BZ6	.91	813	9.95
5BP4	7.95	6C4	.45	815	1.75

Top \$\$\$ Paid for All Tubes!

"VOLT-TAB" 600Watt Speed Control
115VAC \$4.50 @, 2 for \$8

866A Xfmr 2.5V/10A/10Kv/Insl \$3 @
Ballentine #300 AC/Lab Mtr. \$54
(Sd) Choke 4Hy/0.5A/27Ω \$40 @, 2/\$6
"VARIACS" L/N 0-135v/7.5A \$15
"VARIACS" L/N 0-135v/3A \$10
TWO 866A's & Fil. Xfmr. \$6

SILICON TUBE REPLACEMENTS
OZ4 UNIVERSAL \$1.75 @, 2/\$3
5U4 1120Rms/1600Inv \$2 @, 3/\$5
5R4 1900Rms/2800Inv \$9 @, 2/\$15
866 5Kv/Rms - 10.4Kv Inv \$11 @, 2/\$20

Mica Condr .006 @ 2500V 4/\$1
Snooper Scope Tube 2" \$5 @, 2/\$9
Mini-Fan 6 or 12Vac/60Cys \$2 @, 3/\$5
4X150 Ceramic Loktal \$1.25 @, 2/\$2
Line Filter
Line Filter 50Amp/250VAC \$10 @, 2/\$16

DC 3 1/2" Meter/RD/800Ma \$4 @, 2/\$7
DC 2 1/2" Meter/RD/100Ma \$3 @
DC 2 1/2" Meter/RD/30VDC \$3 @, 2/\$5
AC 3 1/2" Meter/RD/130VOC \$5 @, 2/\$9
DC 4" Meter/RD/1Ma/\$5 @, 2/\$9

Battery Charger 6&12V Charges up
to 5Amp "Approved" Heavy Duty De-
sign with Klixon Circuit Breaker.
Operates 220 or 110VAC @ 50 or
60 Cys \$8, 2 for \$15, 7/\$49

Transformers—All Input 115v/60Cys VCT
@ 250Ma, 6V/8A/5A/3A \$6, 2/\$10
400VDC Supply @ 200MA & Silicon Rect
& Filters \$10
20VAC & TAPS/.8,12,16, 20V @ 4A, \$3
32VCT/1A or 2X16V @ 1A, \$8 @, 2/\$5

Line Filter 4.5A @ 115VAC 4 for \$1
Line Filter 5A @ 125VAC 2 for \$1
Converter Filter 400 Ma @ 28VDC 4 for \$1
Converter Filter Input/3A @ 30VDC 4/\$1
2.5MH PiWound Choke/National 5 for \$1

We Buy, Sell & Trade
SEND 25c FOR CATALOG

Terms Min Order \$3
FOB New York.
10 Day Gtd.
Our 20th Year.
111NM Liberty St., N.Y. 6, N.Y. Re 2-6245

"TAB" FOR THE BEST KITS!

Each "TAB" Kit Contains The Finest Selection!!!

- Kit 35 Precision Resistors
- Kit 75 Resistors 1/2, 1 & 2W
- Kit 12 Electrolytic Cond's.
- Kit 65 Tubular Condensers
- Kit 500 Lugs & Eyelets
- Kit 10 Bathub Oil Cond's.
- Kit 5 lbs. Surprise Package
- Kit 10 Transmit Mica Cond's.
- Kit \$ Phone/Patch Xfmr
- Kit 10 Insld Tuning Tools
- Kit 6 "SunCells" Batts
- Kit 10 Sub-Min Tubes
- Kit 12 Alligator Clips Asstd
- Kit (6) Tube Clamps Asstd
- Kit (32) Transistors PNP & NPN
- Kit (12) 2Amp Stud Rectifiers
- Kit 75 Mica Condensers
- Kit 10 Crystal Diodes
- Kit 200ft Hook Up Wire
- Kit 4 Rolls, 500ft/ea. Assorted Color
- Kit 5 FT243 Xtal Holders
- Kit 10 Xtal Osc. Blanks
- Kit 4 Asstd Rectifiers
- Kit 100 Self/Tap Screws
- Kit Adj Wire Stripper & Cut
- Kit Hi Gain Xtal Mike
- Kit 2 pair S0239 & PL59
- Kit 12 Binding Posts Asstd
- Kit (3) T036/50Watt Untested
- Kit (50) TOPHAT 3/4A/Diodes Untested
- Kit (12) T03/SA Transistors Untested
- Kit (4) PF/PressFit 18Amp Studs

Order Ten (10) Kits—We Ship Eleven
One Each Above Kit Only. Each Kit 99c

W.E. Polar Relay #255A/\$5 @, 2 for \$9
W.E. Socket for #255A Relay, \$2.50
Toroids 88Mhy New Pckg \$1 @, 6/\$5
6.3VCT @ 15.5A & 6.3VCT @ 2A \$4 @,
2/\$6
200KC Freq Std Xtals \$2 @, 2/\$3
Printed Ckt Bd New Blank 9x12" \$1 @,
6/\$5
Klixon 5A Reset Ckt Breaker \$1 @, 8/\$5
2K to 8K Headsets Good Used \$3 @, 2/\$5
Xtal Blanks Asst Types 12 for \$1

WANTED TEST SETS & EQUIPMENT

Bandswitch Ceramic 500W 2P/6Pos \$3 @,
2 for \$5
6Hy-305Ma Choke Cased \$3 @, 2/\$5
7-1/2Hy-400Ma Choke Cased \$7 @, 2/\$12
250Mfd @ 450 Wv Lectlytic 4/SSB \$3 @,
4/\$10
Cndsr Oil 10Mfd x 600-2x2.5 & 5Mfd \$1
@, 15/\$10
Cndsr Oil 6Mfd @ 1500V \$4 @, 4/\$10
880Vct @ 735Ma for SSB \$9 @, 2/\$16
480Vct @ 40Ma & 6.3 @ 1.5A CSD \$1.50
@, 4/\$5
10Vct @ 5A & 7.5Vct @ 3A CSD \$6 @,
2 for \$10

WANTED LAB METERS! BRIDGES! K-POTS!

Pwr Sup Kit 900VDC @ 500Ma & 4/
Silicon Diodes 1700Piv FWB \$12
Pwr Sup Kit 1200VDC @ 200Ma/Xfmr
& FWB Silicon Rect \$10 @, 2 for \$18
Modulation Xfmr 60W/15K to 5.7K \$5
Headset Rubber Bunyon Pads pair \$1
Socket Ceramic 1625 Tube 4/\$1
Socket Ceramic 866 Tube 4/\$1
Socket Ceramic 4X150/Loktal 4/\$2

WANTED YOUR ORDER - TODAY!

6MTR Ground-Plane Ant (R Exp) \$4
Knob Spin-Crank BC348 Type \$1
MiniFan 6 or 12 VAC \$1.50 @, 4 for \$5
Beam Indicator Selsyns 24VAC 2 for \$10
Precision TL147 Feeler Relay Gage \$1
8 foot Elec. Cord #16ga & Plug 39c @,
3/\$1
Fuse 250Ma/3AG 5 for 30c, 100 for \$3
DON'T C-WRITE & SEND ORDER!
XMTTG Mica Condr .006 @ 2.5Kv 39c
@, 5/\$1
XMTTG Mica Cndsr .00025 @ 8Kv 75c
@, 4/\$2
Mini-Rectifier FWB 25Ma @ 115VDC
3 for \$1
Micro-Switch Rated 40Amp AC & DC
4 for \$1
BandPass Filters 60 or 90 or 150Cys
3 for \$5
T30 Throat Mikes \$1 @, 4 for \$3
"Bruning" 6" Parallel Rule #1 @
3 for \$2
Linear SawTooth Pot KSI5138/W. E.
3 for \$1
RUSH YOUR ORDER TODAY.
QTY'S LIMITED!

WRL OFFERS YOU A FREE TWO-WEEK TRIAL IN YOUR HOME ON EITHER THE GALAXY III OR GALAXY V!*



WRL GUARANTEES SATISFACTION!
YOU BE THE JUDGE AFTER A TWO-WEEK FREE TRIAL . . . NO OBLIGATION. GALAXY TRANSCEIVERS OFFER YOU MORE FEATURES PER DOLLAR THAN ANY COMPARABLE TRANSCEIVER ON THE MARKET • 300 Watts SSB/CW Input • Best Filter Available • Transistorized AVC/AUDIO/VOX • Most Compact Transceivers With 5 or 3 band Full Coverage • New VFO Side View Dial • Selectable USB or LSB • Portable For Mobile or Fixed Operation.
 *WRITE FOR DETAILS ON FREE TRIAL OFFER!

GALAXY III

80-40-20 Meters

only **\$349.95**

No down payment
 \$17.00 monthly
 WRL Charg-A-Plan

GALAXY V

80-40-20-15-10 Meters

only **\$469.95**

No down payment
 \$21.00 monthly
 WRL Charg-A-Plan

NEW DELUXE CW MONITOR



only **\$29.95**

Monitor and improve your CW. A must for every CW operator. Use with any transmitter or transceiver.

NEW Rejector NOTCH FILTER

Tunable — Transistorized — Powerful suppression of heterodynes and QRM. Use with any receiver or transceiver. Just connects between receiver and PM speaker.



only **\$34.95**

"Got Our 1965 Catalog?"

FINEST SELECTION OF HAM EQUIPMENT EVER ASSEMBLED

ALWAYS the TOP TRADE allowance

ALWAYS the best in terms from

"the house the hams built"

Leo I. Meyerson-WØGFQ
 President



WRL

WORLD RADIO LABORATORIES

3415 West Broadway
 Council Bluffs, Iowa 51504

- Send details on Galaxy FREE Trial offer.
- Ship CW Monitor for \$29.95 + postage.
- Send 1965 Catalog
- Ship Rejector for \$34.95 + postage.
- Send Reconditioned "Blue Book" prices

Name _____

Address _____

City _____ State _____

Zip _____ Call _____



Leo I. Meyerson
WØGFQ

LEO SAYS: BUY DIRECT AND SAVE BIG ON THESE WRL HAM EXCLUSIVES

NEW

WVG MARK II ALL BAND VERTICAL ANTENNA

Low cost — self-supporting 10 - 80 meter antenna. Tunes 3.5 — 30 Mc with manual tap adjustment. Feed with 52 ohm coax. Quick installation. Amazing efficiency for DX or local contacts. Used as portable antenna also.

\$15.95

Postpaid

Continental USA

MECHANICAL SPECS:

Overall ht. — 18'. Tubing diameter — 1 1/4" to 7/16". Max. unguyed wind survival — 50 mph. — Mtg. bracket for 1 5/8" mast. Wt. 5 lbs.

ELECTRICAL SPECS:

Maximum power: 1000 watts AM or CW — 2 KW PEP. Omnidirectional. Vertical polarized.



TECH-CEIVER 6A

Low cost, compact, 6 meter transceiver

Stable superhet receiver. 5 watt transmitter, featuring PTT, using std. (Ft 243) 8 Mc range xtals, non-critical coils, plate modulation, power and modulation indicators, 10 tube performance. Step-by-step manual included. Wt. 9 lbs. 115 VAC Power supply (kit) — 15.95.

- 5 Watt input
- Sensitivity — better than 1 UV

only
\$39.95
kit



- Selective — 20KC @ 6DB points
- 49-54 Mc coverage

PSA-63 POWER SUPPLY


Universal Power Supply: Powers most AM rigs up to 100 watts, SSB units — up to 200 watts, PEP. Silicon rectifiers provide both 300 VDC & 600 VDC @ 300 Ma., ICAS (210 watts total), plus 6 VAC @ 10A or 12 VAC @ 5A, plus 95 VAC @ 10 Ma. Size 11 1/4" x 4 3/4" x 6". Wt. 15 lbs. Kit — 24.95, Wired — 39.95. Opt'l cabinet — 4.95.

- Use with 30-200 watt XMTRS—XCVRs
- Dual voltage B + Fil. power-bias
- Customized units available—Extra

only
\$24.95
kit



DUO-DOUBLET 84

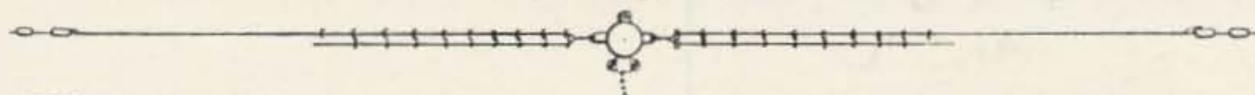

NEW 80-40 meter diapole using proven parallel diapole principle to resonate on both bands. Requires only one 52 ohm feed line (coax not supplied). Kit includes wire, insulators, center connector & full instructions. Complete formula supplied & quick graph chart for easy adjustment. May be used on 15 meters also. SWR: Better than 2:1 at resonance — 80/40. Max. length — 123 ft.; 140 ft. for lowest CW range. Easy to install. Wt. 4 1/2 lbs. Shipped Parcel Post.


80-40 Meter Diapole
One Feed line

\$7.95

NEW

WRL'S 12R GENERATOR

\$149.95

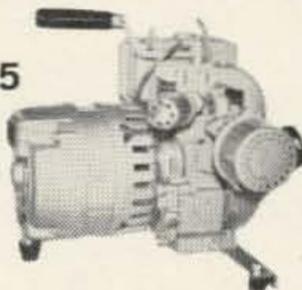

Shielded ignition. 1250 Watts, 115 VAC, 60 cy., 77 lbs. (FOB Milwaukee, Wisconsin)



SS-3 "Q" MULTIPLIER

- Notch and peak
- Self Powered
- One simple receiver connection

Int'l 115 VAC P.S. Plugs into Collins 75S-1, KWM-2 & others. Use with receivers having 455KC-IF: AC or DC powered. Adj. selectivity: 300 cy. to 10 KC. Sharp rejection (50DB) null for heterodynes. 6 1/4" x 4 1/4" x 4 3/4".

\$15.95
kit

ANTENNA TUNER MM-100



\$10.95
kit

Specifically designed to match end-fed long wire which is 1/2 wave, or multiples thereof, to 50 ohm transmitters. Panel lamp indicator. For inputs up to 150 watts SSB, 100 watts CW, 75 watts AM. 4 x 5 x 4 steel case. Reduces TVI.



\$4.98

\$6.37



WRL NUVISTOR PREAMP PRINTED CIRCUITS

PA50-2 Stage preamplifier for 6 meters. Use 2 RCA 6CW4 nuvistors. Highest grade glass epoxy board. Assembled and pre-aligned for 50 ohm input-output. Requires 60-120 VDC @ 10 MA. & 6.3 VAC
Size 2 3/4" x 2 1/4". Wired **\$6.37**
PA-144 Same as above except only 1 6CW4 nuvistors & for 2 meters. Wired **\$4.98** (less 6CW4 tubes).

WRL

WORLD RADIO LABORATORIES, INC.
3415 West Broadway
Council Bluffs, Iowa 51504

Rush me FREE!

WRL 1965
Catalog

Reconditioned
Specials!

Please rush me item _____

Enclosed is Cash Charge* COD (25% cash w/order)

*If new customer, send credit info with your charge order


Name _____

Address _____

City _____ State _____ Zip _____

Clip & Mail

a steal

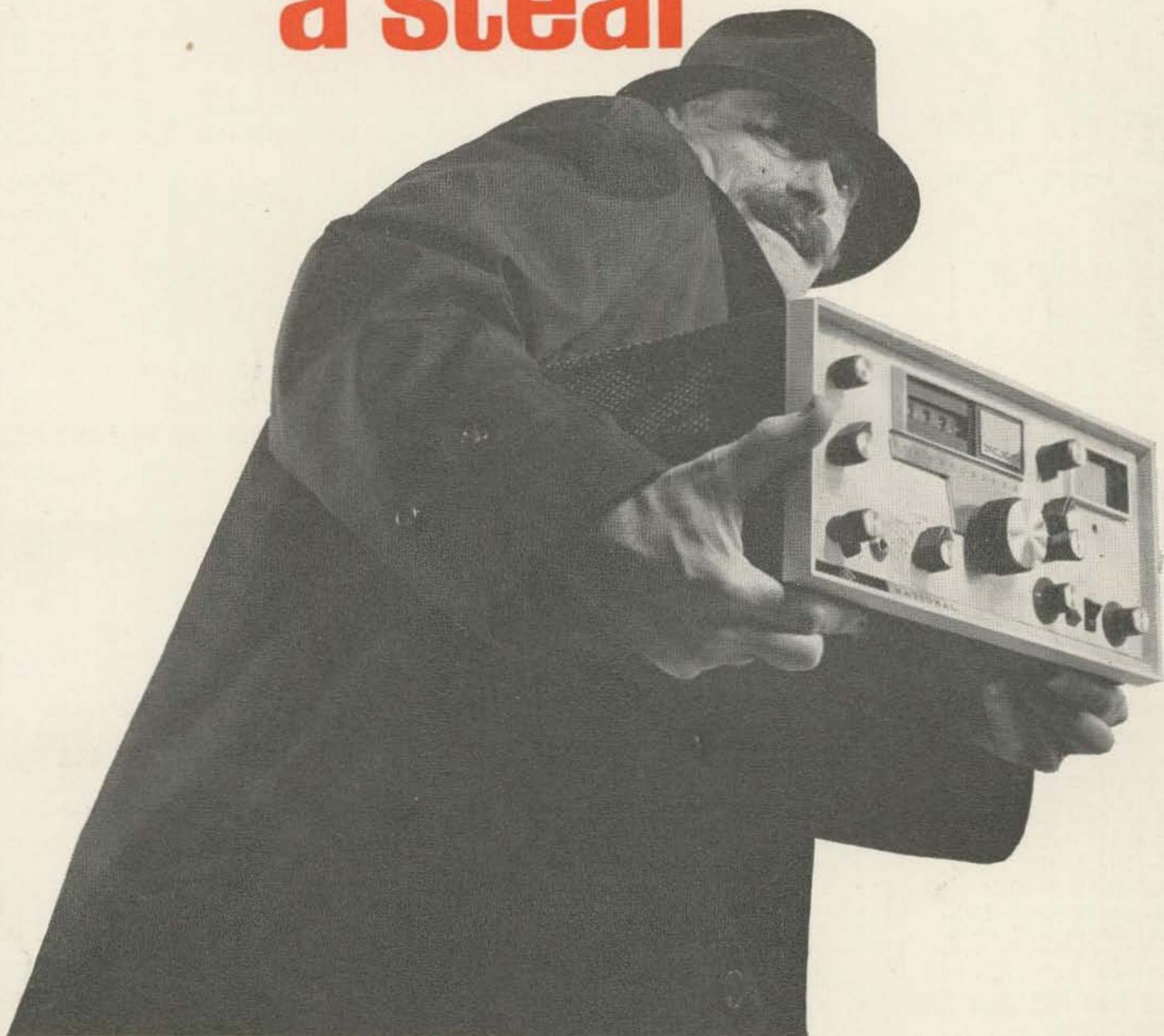

Feel like a little larceny? Go ahead. Take advantage of us. At only \$685.00, National's NCX-5 transceiver is a steal. Here's a total station transceiver for the 80 through 10 meter bands which gives you more features and performance than any other transceiver at any price. Judge the NCX-5 by any criterion: **Dial Calibration** using a digital counter with accuracy to one Kc and read-out to 100 cps—ten times better than any other amateur equipment available. **Stability** from a cold start with a linear solid-state VFO which eliminates tube-type warm-up drift due to electrode structure change with temperature. Each VFO individually temperature compensated and double-regulated against input voltage variation. Long-term stability from a cold start superior to most tube-type VFO's after warm-up. **Selectivity** with an 8-pole crystal lattice filter substantially superior to any filter of any type ever used in commercial amateur gear. 6-60 db shape factor of 1.7:1 and 2.7 Kc bandwidth assures superb sideband suppression and adjacent-channel receive selectivity with pleasing, natural voice quality. **Sensitivity** of $0.5 \mu\text{v}$ for 10 db S/N, using **two** RF stages on all bands. **Split-frequency operation** with built-in **Transceive Vernier** for ± 5 Kc independent receiver tuning. Also accessory VX-501 VFO console to provide completely independent control of receiver and transmitter frequencies as well as transceive operation controlled by either NCX-5 or VX-501. Console also provides choice of five crystal-controlled frequencies for net or novice use. **Complete AM and CW facilities** including separate high-quality AM detector and break-in CW with adjustable release time. **Quality and workmanship** you expect from National—one-year guarantee against component failure and the neatest wiring you've seen since the last sun-spot cycle . . . right-angle component dress, with even the resistor color-codes all lined up in the same direction. **And everything else** you want in a transceiver . . . precision styling that complements the NCX-5's performance . . . 200 watts PEP punch on SSB or CW . . . 10 db of ALC for maximum talk-power without flat-topping or splatter . . . front panel choice of VOX, push-to-talk, or manual operation . . . SSB/CW/AM AGC and D'Arsonval S-meter/PA meter . . . mobile mount included . . . even optional deluxe oiled walnut cabinets separately available for the NCX-5, NCX-A AC supply/speaker console, and VX-501 VFO console for custom home installations.

NATIONAL RADIO COMPANY, INC. 

37 Washington Street, Melrose, Massachusetts, 02176 World Wide Export Sales: Auriema International Group, 85 Broad Street, New York City, N. Y.; Canada Tri-Tel Associates, 81 Sheppard Ave. W., Willowdale, Ontario