

AMATEUR RADIO

73

VHF SUMMER SPECIAL



#130 JULY 1971

STAFF

Editor-Publisher
Wayne Green W2NSD/1

Editor Emeritus
Ken Sessions K6MVH/1

Assistant Editor
Douglas Stivison WA1KWJ

Associate Editor
Jim Kyle K5JKX

WTW Editor
Dave Mann K2AGZ

Advertising Manager
Aline Coutu

Art Director
Roger Block

Graphic Arts
Nancy Estle
Jerry Merrifield

Composition
Ruthmary Davis
Karen Mellor

Subscriptions
Dorothy Gibson

Circulation
Phil Price
Barbara Block

Comptroller
Georgiana Sage

Publications
Biff Mahoney

Traffic
Taylor Sage

Propagation
John Nelson

Drafting
R. K. Wildman W6MOG
Wayne Peeler K4MVW
T. M. Graham W8FKW

FEATURES

- | | |
|---------------------------|----------------------------|
| 2 Radio Amateur News Page | 25 Dipper Thing WB4MYL |
| 4 Never Say Die W2NSD/1 | 72 Call Sign Plaque WA2ITE |
| 4 The FM Scene K6MVH/1 | 73 73 Reader Coupon |
| 8 New Products | 74 Zero Beat W4UZM |
| 10 DX Footnotes | 96 Propagation |
| 12 Letters to the Editor | 96 Advertiser Index |
| 12 Caveat Emptor | |

CONTENTS

- | | |
|---|----------|
| 16 An IC Audio Processor | W2EZY |
| Two IC Project | |
| 20 Audio Signal Generator | W3SGV |
| Wein bridge reinvented. | |
| 24 Questions, Questions, Questions | W9EGO |
| Answers, answers, answers. | |
| 26 A Filter Box for CW Ops | K8TSQ |
| Mind boggling CW selectivity. | |
| 34 Duals | WB2PAP |
| Think piece for this month. Think! | |
| 40 Miniature Add-On Oscillator for 2m FM | WB6BIH |
| Little P.C. unit. | |
| 42 Collinear Gain Antenna for VHF/UHF Repeaters | K6MVH |
| Verticle beam antennas? | |
| 43 Invitation to Transmit | Thurmond |
| This is women's lib? | |
| 49 FM Directory | Staff |
| Everything you always wanted to know. | |
| 56 Desktop Base Stations from Motorola G Strips | W9VZR |
| Another FM article in 73? | |
| 63 Camouflage Extra Class | W4CWB |
| How to sneak a 40m beam past the XYL. | |
| 66 File-Box Transistor Beta Tester | WB4ITN |
| Are your transistors really adequate? | |
| 77 2 KW From Heath | W6BMK |
| Heath does it again! SB-220. | |
| 80 General Class Study Guide: Part X | Staff |
| The listening post. | |

73 Magazine is published monthly by 73 Inc., Peterborough, New Hampshire 03458. Subscription rates are \$6 for one year in North America and U.S. Zip Code areas overseas, \$7 per year elsewhere. Two years \$11 in U.S. and \$12 overseas. Three years \$15, and \$16 overseas. Second class postage paid at Peterborough, N.H. and at additional mailing offices. Printed at Menasha, Wisconsin 54952 U.S.A. Entire contents copyright 1971 by 73 Inc., Peterborough, N.H. 03458. Phone: 603-924-3873. It is henceforth forbidden to permit any friend or relative to read your subscription copy of 73 Magazine. Let them buy their own copies.

Cover: From the dusty reaches of the W2NSD/1 garage comes this collection of ham license plates. We invite all 73 readers to send us their old call plates so we can replace all the shingles on the 73 barn with call plates.

Amateur Radio News Page

JULY MCMLXXI

Monthly Ham News of the World

73 MAGAZINE

"EYEBANK" INQUIRY PLANNED

The "Eyebank" controversy has had its impact on the FCC, with the result that the Commission will conduct an inquiry into applicable "Rules."

The Commission's Rules governing the amateur radio service prohibit issuance of an amateur station license to a "school, company, corporation, association or other organization, nor for its use . . ." (Section 97.39). The only exception is for "a bonafide amateur organization or society." Another Section, 97.107, permits an exception during declared emergencies when normal communications are disrupted.

Over the years, however, amateur stations have been used for nonemergency communications in behalf of certain nonamateur organizations such as the Red Cross, Eyebank Association, and the March of Dimes. There has been general agreement that these operations are meritorious.

Recent developments have required a closer look at the requirements of the rules in relation to operation in the interest of other than amateur organizations. "There is evidence of a considerable proliferation of nonamateur organizations with an interest in the use of amateur frequencies and amateur stations for purposes which may well lack the universal acceptability of Red Cross and Eyebank objec-

tional communications transmitted by amateur stations "to messages of a technical nature relating to tests and to remarks of a personal character for which by reason of their unimportance, recourse to the public telecommunications service is not justified." While there is no similar provision applicable to domestic operations, Section 3(q) of the Communications Act in effect defines an amateur operation "as a person interested in radio technique solely with a personal aim." Extensive use of amateur radio for any third party would not appear to be compatible with that definition.

As previously noted, there is general recognition of the public benefit derived from limited use of amateur stations on behalf of such organizations as the Red Cross, Eyebank, and the National Cystic Fibrosis Foundation. Such recognition may not, however, be nearly as universal when considering the possible use of amateur radio on behalf of other non-profit, public service organizations such as political parties, student organizations, various churches and missionary societies and a large number of other and more controversial groups.

In order to assist the Commission in making determinations in these important and controversial areas, all

National Releases New Receiver



National Radio Company, Inc. of Melrose, Mass. recently announced the attainment of a major milestone in the company's revitalization program. The HRO-600 VLF-HF Full-coverage Receiving System was successfully tested and qualified against an up-graded specification invoked by the United Kingdom Ministry of Post and Telecommunications. NRCI's HRO-600,

frequency range in AM, CW, SSB, FSK, FAX modes, and will accept any one of several frequency control plug-in units (VFO, Synthesizer, Fixed Channel Crystal Control). Both the VFO and Synthesized versions were tested and qualified. The design configurations provide for a wide variety of multimode and multipurpose applications. Additional markets for the

WALKER NAMED FCC CHIEF

A. Prose Walker, an engineering consultant and former FCC staff member, has been named chief of the Amateur and Citizens Division succeeding Everett G. Henry, who retired earlier this year. Mr. Walker had headed his own consulting firm after serving as a consultant with a Washington, D.C. engineering group. He was employed by Collins Radio from 1961 to 1968 in various positions, including most recently, manager of broadcast and general communications in Washington, D.C. From 1953 to 1961 he was manager of engineering for the National Association of Broadcasters and in 1960 was the editor-in-chief of the NAB Engineering Handbook. Mr. Walker joined the FCC in 1940. During World War II he worked in the area of radio intelligence and direction-finding, moving to the Broadcast Bureau in 1946. As chief of the TV allocations branch, he participated in the 1947 Atlantic City World Administrative Radio Conference and attended the high frequency broadcast conferences as a member of U.S. delegations.

tives," the FCC said. Unlimited operation in behalf of such organizations could generate large numbers of new networks and the use of amateur radio as a medium for the organized advocacy of social, political or economic views could preempt amateur frequencies to the exclusion of the individual amateur for whom the service was intended.

The current rule is clear and unambiguous. It permits no such operation other than as previously noted. Therefore, while the Commission essentially agrees with those amateurs who believe that limited communications in behalf of the Red Cross, Eyebank, March of Dimes, National Cystic Fibrosis Foundation, and similarly oriented organizations are meritorious, it concludes that they are not permissible under Sections 97.39 and 97.107 as they now read and, if the communications are to be permitted, the rules must be amended.

If this is done, the question is raised as to whether some restrictions on the kind of organizations to be included and limitations on the type of communications so permitted will be required. The lines of demarcation between organizations to be made eligible and the types of communications to be permitted are by no means clear. It is one of the purposes of this Notice of Inquiry to elicit information and comment on the extent, if any, to which restrictions and limitations should be imposed.

Another factor to be considered is that Section 2 of Article 41 of the International Radio Regulations limits

HW-100 OWNERS

Jim Isham W8TXX of the Heath Company recently stated in the Philmont Mobile Radio Club *Blurb* if the HW-100 owners wanted to increase their receiver sensitivity they can change V-10 and V-11 to 6HS6's and they will see a marked change in receiver sensitivity. No other changes are necessary, just the tubes.

interested parties are requested to submit comments and suggestions relevant to the following issues:

I. Are any restrictions on the use of amateur stations in behalf of non-amateur organizations warranted?
 II. If amateur radio stations should be permitted to furnish a communication service to nonamateur organizations;

(A) To what types of organizations?

(B) What types of activity or communication should be permitted?

(C) If there is to be a distinction between emergency and non-emergency communications, should emergency communications be limited only to those situations where normal communications are disrupted?

In accordance with provisions of Section 1.419 of the Rules, an original and 14 copies of all comments, suggestions, pleadings, briefs, or other documents shall be furnished to the Commission. Tell the boys in Washington what you think.

REGENCY ANNOUNCES ACQUISITION

Instrument Flight Research, Wichita, Kansas, has been acquired by Regency Electronics of Indianapolis, Indiana. Floyd O. Ritter, Regency president, said the purchase was consummated by exchange of Regency stock for all assets and business of the IFR company.

IFR manufactures aviation electronics test equipment. Regency Aviation Division marketing officials, who will assume IFR sales responsibility, state that combining the two companies should result in great sales efficiency for both firms.

the latest in a 40-year genetic line of high frequency radio receivers, is the first U.S.-designed and manufactured equipment to pass this specification. The specification is intended for use by the world-wide maritime services for a ship's main and/or single side-band receiver.

The HRO-600 is capable of operating over the 10 kHz to 30 MHz

receiver; are: maritime shore stations, air-ground facilities, overseas communications networks, VLF-HF monitor installations, radio frequency control activities, and instrumentation programs.

Quantity production of the HRO-600 is currently underway, and it is anticipated that the receiver will be available for delivery in August, 1971.

Price Reduction: SMALL-SIGNAL PLASTIC TRANSISTORS

Phoenix... Motorola has just announced lowered prices for eight popular small-signal plastic transistors. Old and new prices are as follows:

Type	Quantity/Price		
	1-99	100-999	1000-499
1N3903	\$0.55 (\$0.75)	\$0.39 (\$0.50)	\$0.29 (\$0.37)
2N3904	0.55 (0.82)	0.39 (0.55)	0.29 (0.41)
2N3905	0.55 (0.75)	0.39 (0.50)	0.30 (0.37)
2N3906	0.55 (0.82)	0.39 (0.55)	0.30 (0.41)
2N4123	0.39 (0.52)	0.27 (0.35)	0.16 (0.26)
2N4124	0.40 (0.60)	0.28 (0.40)	0.17 (0.30)
2N4125	0.40 (0.52)	0.28 (0.35)	0.17 (0.26)
2N4126	0.41 (0.60)	0.29 (0.40)	0.18 (0.30)

(Note: Figures in parentheses are the former prices.)

These devices include low noise, general purpose, switching, and amplifying transistors, useful to 300 MHz. All are rated at 310 mW power dissipation.

Types 2N3903 and 2N3904 are NPN high speed low-noise devices, while types 2N3905 and 2N3906 are their PNP complements.

The 2N4123 and 2N4124 devices are general purpose NPN transistors, with types 2N4125 and 2N4126 being the PNP complements.

the very lowest in the industry.

For more information, contact the Technical Information Center, Motorola Semiconductor Products Div., Box 20924, Phoenix AZ 85036

ARRL OFFERS TVI INFORMATION

The ARRL has published a sheet on TV set manufacturers who will supply a high pass filter for the suppression of interference. The list of twelve manufacturers is available free for a SASE sent to the League's headquarters, 225 Main St., Newington CT 06111.

REPEATER DIRECTORY UPDATE

We try to keep our open repeater directory current and up-to-date. However, new repeaters are coming on the air every day and others are changing frequency and adding channels. As a result of all this activity many errors and omissions have crept into our directory.

Below are the changes and corrections since the publication of our last comprehensive directory in the April 1971 issue of 73. We invite our readers to write in with any corrections and new information on repeaters anywhere in the world. With continued help from our friends we can maintain the most complete repeater directory available.

34/94 means the standard channel of 146.34 MHz input and 146.94 MHz output. All other frequencies are listed in megahertz with the input channel frequency first.

There is a new repeater in Rodville MD on 52.80/52.68. The call is WA3BMM.

The K3PQZ repeater in York PA is no longer on the air on 34/76.

K8SXO in Ridgeley WV is reported to have moved and is off 34/76, 146.76/52.525, and 52.525/146.76.


There is a new repeater in Dunkirk NY: W2SB is on 34/94 and 146.25/146.85.

There is a new repeater on 146.37/146.97 in Manassas VA with the call WB4URR.

VE7CAP, Kimberley, B.C. has changed from 146.46/147.33 to 34/94.

Again—please keep 73 informed of any other changes or errors.

Moving? Please
Let Us Know!

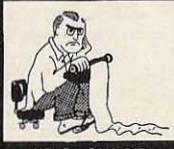

...de W2NSD/1

EDITORIAL BY WAYNE GREEN

An Old Editor?

Ken Sessions, who leaves us with this issue, has been one of the best editors 73 has ever had. Ken was responsible for the new and flashy layouts of the articles, the heavy emphasis on FM, and the virtual elimination of spelling errors. Under his guidance 73 has continued to grow during a time of depression in the electronic fields which has severely hurt some of the other ham magazines.

All of us at 73 will miss the warm personal friendship and enthusiasm he brought to the job. Ken has promised to continue to write articles and keep the FM information coming in, so he will certainly not be dropping out completely. We all wish him well at his new and bigger job.

All of which means that you are stuck with me as editor again. On the plus side I should point out that whatever I lack in maturity and common sense I make up for in impulsiveness.

Good luck, Ken . . . good luck, 73 readers.

FM in 73

Has there been too much FM coverage in 73? A few readers have complained about this. Even more readers are in favor of the FM coverage. Perhaps some perspective is in order — call it justification, if you like.

Amateur radio has been kind of dragging along with little new to fire the imagination since the change to sideband some ten years ago. The changes in the General class band

you can get a fine little FM rig and you are on the air through the local repeaters. You can use it in the car, at home, at work, or even in a boat. More and more hand units are coming out, too. While not too many of us can plunk down a long one for a sideband station, two short ones aren't all that hard to come by.

While I may be patting 73 on the back more than it deserves, I do note that a little over a year ago there were only a couple of FM rigs available and today there are over a dozen and the big problem is back orders. Distributors are raising Cain trying to keep units in stock. This is fine for the amateur equipment industry (and they needed something like this pretty desperately), but the main benefactor is amateur radio itself . . . with thousands of stations coming on FM and having a ball.

While we won't be hitting FM quite as hard in the future, more due to Ken moving on to a much bigger job than any change in our thinking, we will be running all the good technical and construction material we can get our hands on plus keeping little items such as the repeater directory up to date, testing new FM gear and the like. Keep those articles coming in . . . and those repeater changes and additions.

Errors in 73?

Some naive readers have the ridiculous idea that the grammatical, spelling and typesetting mistakes in 73 are accidental. No such thing. This is merely one aspect of our attempt to maintain our image as an amateur magazine. Perfection would be too

WWV-WVVH CHANGES BROADCAST FORMAT

Reported by W2AXU

When you tune in WWV for time signals or propagation information after 0000 hours Greenwich Mean Time (GMT) July 1, 1971, you will hear a different program format than you have been accustomed to over the years. The Morse code transmissions will be gone and the announcements of time and other information will be made in voice. The time will be announced every minute instead of every five minutes. A male voice will be used by WWV and a female voice by WWVH to distinguish between them. The carrier frequencies will remain the same — 2.5 MHz, 5.0 MHz, 10.0 MHz, 15.0 MHz, 20.0 MHz and 25.0 MHz. The frequency accuracy of the two stations is controlled by the NBS Atomic Frequency Standard at Boulder, Colorado. WWV is in Colorado and WWVH is located in Hawaii.

The format of the broadcasts from the two stations will be similar but to avoid confusion between the two stations, they will use alternate time slots for the transmission of tones, announcements, etc. The standard time tick each second will remain.

Each hour will be divided into one minute slots. Each minute (except the first) will begin with an 0.8 second 1000 Hz tone at WWV and 1200 Hz at WWVH. The first minute of each hour will begin with a 1500 Hz tone at both stations. The one minute slots will be divided into a 45 second segment and two 7.5 second segments. On alternate minutes the 45 second segment will contain either a standard tone (possibly 600 Hz) or an announcement.

It is interesting to note that the announcement slots will be available

the FM scene

by K6MVH

Repeater Problems

It certainly is easy for me to sympathize with people who write in telling me of their repeater problems. Perhaps a better word would be "empathize." I've installed a number of repeaters over the past few years and I've never unleashed one yet without controversy, complaint, and hard feelings on the part of at least a vociferous handful.

Here in New England there are dozens of repeaters operating successfully; but the road to success was rocky indeed for virtually all of them. The W1ALE repeater, for example, went up some time ago near Concord, N.H. Its duty cycle was the source of controversy, because it was on the popular .34/.94 set for 12 minutes, then it reverted to .46/.94 and 52.525/.94 for 3 minutes. If the latter operational sets were active, the repeater stayed in that mode, leaving the .34/.94 users with no repeater.

Then one day along came another amateur and another repeater. This repeater, assigned to K1ZJH, was to operate .34/.94 continuously. The only trouble was the fact that the repeater's range overlapped with W1ALE, so a few people — those most affected by the overlap — complained. The K1ZJH machine was running too much power on the output, and mobiles with low power couldn't key the repeater even when they could copy the machine full quieting. The output, they said, was causing interference in some places with W1ALE. But John Bertini, the repeater owner, was convinced that the low-power mobiles should increase their power if they

in addition to all of Rhode Island, most of Connecticut and Vermont, all of New Hampshire, all of Massachusetts, and the greater part of Maine.

Needless to say, the repeater drew its share of fire from the members of the other repeater groups. Amateurs who were not members of the other groups, of course, were delighted with the repeater and the coverage it offered. But stations in Boston found that they could key the 73 Magazine repeater (W1KGO) as well as their own local machine with each transmission. And to their dismay, the output of the W1KGO repeater was as potent in Boston as the Boston repeater itself. Users of W1ALE and K1ZJH had similar reports. They found it difficult to communicate on their own private repeater when the W1KGO repeater was being used.

Wayne and I decided to move the repeater to another set of frequencies (146.37/146.73) to avoid further interference to the other repeaters, but we met with a number of objections from the amateurs who liked the extended .34/.94 coverage.

Should we change the repeater output? Should we leave the repeater on .34/.94? We at 73 are faced with a dilemma of concepts: On the one hand, there are people who believe that .34/.94 should give saturated coverage over as much area as possible — the whole U.S., if such were feasible. On the other hand, there are others who feel that .34/.94 should be used for limited coverage over small areas only. Those who take this latter view feel that transients get the advantage of a repeater no matter where

segments, the dropping sunspot numbers, and other factors have worked to lessen enthusiasm . . . and fun.

Something new was in order. Something fun. Two-meter FM looked to me as if it would fill the bill. Repeaters had added that certain something which changed 2 meters from a frustration to great fun. As soon as I had my first personal experience through a repeater I knew that this was the way to go and, through great luck, was able to get Ken Sessions to guide 73 on the path to FM. Sure, we've gone a bit overboard, but wasn't it worth it? Thousands of 73 readers have succumbed to the siren call and are having the time of their lives.

Look at it this way. A low-band station generally runs about \$1000 by the time you have the transceiver, tower, and antenna. For about \$200

ANN LANDERS IN 73???????

DEAR ANN LANDERS: A few years ago my husband used to play a lot of cards. Harry was gone five nights a week. The only time I saw him was when he'd have the card game at our house. I got fed up making sandwiches, emptying ashtrays and cutting my way through cigar smoke. One day a friend told me how she cured her husband of the same thing. She got him interested in a ham radio.

This is not a cheap hobby, but I decided it was worth it. I bought Harry a set as a surprise birthday gift. Within weeks he gave up the cards to stay home and ham it up. Now he has started a short-wave romance with some woman who lives in San Antonio, Tex. She has a voice like Lady Bird Johnson. Their three-hour conversations are making me sick. Harry rushes home from work, bolts his

professional and put us in a class with, ugh, QST. In order to avoid this we intentionally include fourteen errors in each and every issue, thus preserving our image as blundering amateurs, not only at the radio hobby, but at publishing. We are preparing certificates of merit for readers who manage to spot all fourteen errors three months running.

Why Sideways?

The news pages are printed sideways and in small type for one basic reason: the material is of far less long-term value than the articles and thus doesn't really justify taking as much space as the articles do.

The side pages permit us to get almost 25% more material on a page. The smaller type increases this even more with the result that we are able to cram about two and a half pages of material onto each news page. If we were to print the news the same size as the articles, six double pages of news, letters and caveat emptor would fill over 30 pages of the magazine. Now be honest . . . wouldn't you rather have a little eyestrain on the news and have that many more articles? Your eyes certainly aren't any worse than mine, and I can read the news if I put on my glasses.

. . . W2NSD/1 ■

dinner and makes a beeline for the radio.

Last week he couldn't contact the lady for three days and he was a wreck. When he finally reached her she explained she'd been out of town. He scolded her for not letting him know she was leaving . . . said he was "worried sick." The whole thing was so cozy I felt like belting him one. Furthermore, this ham thing is interfering with our sex life because Harry stays up until 2 a.m. most nights. (I think she does it on purpose.)

Now I wish he were back playing cards. What should I do? — DUMMY

to Government agencies to use for their own purposes. The slots not used will be filled by another standard tone, probably 500 Hz. To prevent interference between the two stations where they can be received simultaneously, one station's announcements will coincide with the other's tone.

The first 7.5 second segment following the 45 second segment will be used by WWVH to announce time while WWV will be silent. The second 7.5 second segment will be used by WWV to announce time, WWVH being silent.

Each station will omit for 5 minutes of each hour all tones and announcements during the 45 second segments. This period will begin for WWV at 45 minutes past the hour and for WWVH at 15 minutes past the hour.

A special 440 Hz tone will be broadcast by WWV for 45 seconds beginning one minute past the hour and by WWVH two minutes past the hour. This tone can be used to mark the hours on strip-chart recorders or other instruments. The tone will be omitted during the zero hour of each UT day.

In summary, the standard time and frequency stations WWV and WWVH will revise their transmission program format on July 1, 1971 at 0000 hours GMT. Time announcements will be made in voice every minute — a male voice from WWV and a female voice from WWVH.

Courtesy of W2AXU and the Mt. Airy VHF Radio Club newsletter *Cheese Bits*.

DEAR DUMMY: Keep quiet. These two will probably talk themselves out. A woman who can't lure her man away from a piece of machinery has no imagination, Toots.

(Reprinted by permission of Publishers-Hall Syndicate and Ann Landers.)

wanted to use his repeater, and he held his ground. Eventually, the inhabitants of both repeaters grew accustomed to having them both on the air, and the controversy abated.

Then along came WAINJR, a repeater in Boston. This repeater was installed because neither ALE nor ZJH offered any kind of coverage from the big city. But the people who were using the K1ZJH repeater moaned and groaned because the NJR machine was cramping their style near the fringe areas between the two repeaters. Clearly, the shoe was on the other foot.

To placate the people using the other repeaters, I'm told, the officers of the WAINJR repeater lowered their power, thereby reducing coverage to the immediate vicinity of Boston. It didn't stop the gripes, but it reduced them to an insignificant whisper. And three repeaters were operational on the .34/.94 pair, all of which had a restricted area of coverage, and all of which overlapped with the others in some places.

Here in New Hampshire, we were repeater shy. Inhabitants of the Peterborough area (and indeed virtually all of Southern New Hampshire) could key any one of the three .34/.94 machines if they were equipped with fairly high-power base stations and efficient beams. But mobile operation was out of the question. So I installed a .34/.94 repeater on a mountaintop near Peterborough.

As it happens, the repeater I put up has no measurable desensitization; this fact, coupled with the elevation at which the system is mounted, accorded a degree of coverage that surprised everyone, including me. With a 10W output signal on the repeater transmitter, reliable two-way communication range can be maintained between 10W mobiles as far south as the New York border to as far north as the central portions of Maine. In essence, the repeater range includes all the areas covered by the three previously mentioned repeaters,

they go because of the proclivity of repeaters operating on that pair of channels. Proponents of the former idea feel that .34/.94 should be a universal, superrange set of frequencies, and that local repeaters should be on off-channels.

So I ask for the opinions of the amateur FM world at large. What do you think? Do you feel that supermachines should dominate .34/.94? Do you think local-coverage repeaters should dominate .34/.94? What we do with the WA1KGO repeater will depend on the opinions and reasoning of the FM readers who write in. Tell me what you think.

. . . K6MVB ■

REWARD

From Mars Newsletter England and *Cheese Bits*

A reward is offered for information leading to the capture of Eddy Current, charged with the induction of an 18 year old coil called Milli Amp, found half choked and robbed of valuable jeules. The unrectified criminal, armed with a carbon rod escaped from a primary cell where he had been kept in ions. The escape was planned in 3 phases. First he refused the electrolytes, then he climbed through a grid, despite the impedance of wardens and finally went to earth in a magnetic field. He has been missing since Faraday. It is thought that he escaped on a megacycle. Amen.

Tell our
Advertisers
You Saw it
in 73

WINDSOR AWARDS '71 DELTA QSO PARTY

International Freedom Festival Award

All contacts must be made in the period from June 24 to July 20, 1971. Only contacts with Windsor club-members shall be counted.

Two-way communications with an exchange of reports must be established. Continental USA & Canada require 5 contacts; DX stations require 3 contacts; Essex county, Ontario, requires 10 contacts.

Send certified copy of log to Windsor Amateur Radio Club, Box 1322, Windsor 14, Ontario, Canada.

Rose City Award

All contacts (after Sept. 1) must be made with members of the WARC.

Two-way communications with exchange of reports must be established. Essex county amateurs require 15 contacts and all other stations are required to work a minimum of 5 stations.

Send certified copy of log to Windsor Amateur Radio Club.

There is no charge for either award.

WORK THE CAPITOL

There is a nice certificate for working W3USS located in the U.S. Senate. They are often active Mondays through Fridays from 1800 to about 1900 GMT. The best place to look for them is between 21350 and 21360 kHz. For the certificate, send 2 IRCs and a large envelope to W3USS, Capitol Hill ARC, Box 73, Senate Office Bldg., Washington DC 20510.

Christian Amateur Radio Fellowship

The Christian Amateur Radio Fellowship will hold a workshop at the North American Christian Convention to be held in Dallas TX July 8, 1971.

'71 DELTA QSO PARTY

All amateurs are invited to participate in the second annual Delta QSO Party which is sponsored by the Delta Division of the American Radio Relay League.

Contacts must take place from 2000 GMT Aug 28 to 0200 Aug 30. No time or power restrictions.

Amateurs outside the Delta Division will attempt to contact as many amateurs inside the Delta Division (ARK, LA, MISS, TENN) as possible. Delta Division amateurs will attempt to contact as many amateurs as possible both inside and outside of the Delta Division.

The exchange will consist of QSO Number, RST, and QTH (ARRL section for non-Delta Division, county and state for Delta Division). Logs must include date/time, station worked, exchange, band, emission, and multiplier. Stations may be worked on each band/mode. Mobiles may be worked if they change county.

For more info, write: Malcolm P. Keown W5RUB, 213 Moonmist, Vicksburg, Miss. 39180.

PENNSYLVANIA

The 34th annual hamfest of the South Hills Brass Pounders and Modulators will be held on August 1 from noon til dusk at St. Clair Beach, McMurray PA, 5 miles south of Mt. Lebanon on Rt. 19. Swap and shop, picnic space for the family, mobile check-in on 29.0 and 50.4. Information and preregistration at \$1.50 per ticket (\$2 at door) from Lou Cowan, 26 Graper St., Pittsburgh PA 15227.


The Two Rivers Amateur Radio Club of McKeesport will conduct its seventh annual hamfest on Sunday, July 18. This event will be held at the Balkan grounds, Coulter Road, McKeesport, Pennsylvania. Our past ham-

WAS-AT AWARD

The Dayton Amateur Radio Association will sponsor a "worked all states-by amateur television" award to encourage and promote the latest mode of communication by amateur slow-scan television. A handsomely engraved plaque will be presented to the first amateur who completes 50 state two-way contacts by SSTV. At this time there may not be SSTV stations in all 50 states, but this novel means of communication is growing so rapidly that all states will soon be covered. In fact, a DX-ATV Centry Club (Worked 100 Countries) recognition is very possible within the next year.

The WAS-AT award will be made with adequate recognition and publicity to the various radio publications at the time of the presentation. The following rules are established for this DARA award:

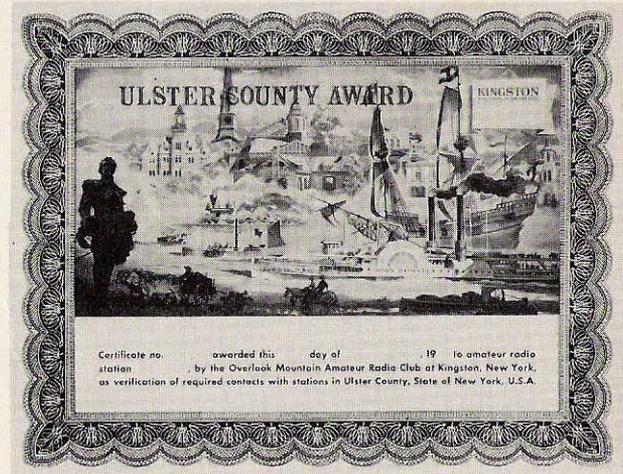1. Contacts must be made to all 50 states from the same transmitter location starting April 14, 1971.
2. Proof of the SSTV contact shall be a photograph taken of a readable received picture showing the contacted station's call letters or his symbol. In lieu of a photograph, a recorded tape (1/4" audio) may be submitted, showing the received picture of the call letters or symbol.
3. A log shall also be submitted showing the station contacted, location, time and date, frequency used, and the type of video equipment of the contacted station. A statement shall accompany the log, stating that the contacts listed are in accordance with the regular station's log and that FCC rules have been complied with on all contacts.
4. Photos and recorded video tapes which are submitted, may be copied by the DARA for the record, but will be returned to the contestant after the award is made.



ULSTER COUNTY AWARD.

County Award. This certificate is issued by the Overlook Mountain Amateur Radio Club, Kingston, N.Y. for contacting amateur radio stations in Ulster County, New York. No time, mode or band limitations. DX stations (including KH6, KL7) must contact any two stations in Ulster County, N.Y., U.S. amateurs must contact three stations. Charge: 50 cents to W-K stations; 4 IRC's for DX stations. Send log data to Harold Twiss, WA2RFX, Country Lane, Lake Katrine, NY 12449.

in advance are \$2; at door are \$2.50. Children 5-12, 75¢. For raffles and tickets write to Eric Strassler WA2NLP, Ticket Chairman, 15 Crescent Ave., Passaic NJ 07055.

MASSACHUSETTS

The first Nobarc hamfest will be held August 22 at the Little Red Schoolhouse, Williamstown, Mass., 11:00 a.m. - 7:00 p.m. Activities include technical talks, demonstrations, transmitter hunts, YL demonstrations, family activities, flea market, and displays. Talk-in on 146.94

MANITOBA B.C.

The eighth annual international hamfest will be held July 10 and 11 at the International Peace Garden. This hamfest is jointly sponsored by the Grand Forks, N.D. Amateur Radio Club and the Amateur Radio League of Manitoba, and is held annually in the beautiful Peace Gardens bordering North Dakota, U.S.A. and Manitoba, Canada. Activities include transmitter hunts, mobile displays, games, dancing, swap tables, prizes - fun for all with good camping facilities.

KELOWNA B.C.

The Penticton Civil Defense Ama-

Fred Basye (K5HOJ) is conducting the workshop entitled, "Ham Radio—Keeping Touch Around the World." CARF is also putting a station on the air during the convention July 6—9 with the sign K9IGB/5.

TEXAS

Swapfest & Picnic, Sunday, August 1, at the city park in Levelland, Texas. Sponsored by the Northwest Texas Emergency Net and the Hockley County Amateur Radio Club. This event is for the entire family. Bring your own picnic basket. Registration begins at 0930. Lunch at 1300. Caprock Repeater Club meeting at 1430. Mobile talk-in is the net frequencies: 3950, 146.94 FM, or through the Lubbock repeater on 146.34.

PENNSYLVANIA

The Foothills Radio Club, Inc. of Greensburg, Pennsylvania, will hold its fourth annual hamfest on July 11 at Wendel Ball Field, Wendel, Pa., 2.4 miles from the Irwin interchange of the Pa. turnpike. Over \$600 in prizes plus 50/50 drawing. There will be check-ins on 10 and 6 meters. Refreshments at moderate prices and BINGO for the Ladies. Just follow the signs if you want to have fun in '71.

MICHIGAN

Cascades Amateur Radio Society announces its second annual swap-and-shop, Sunday, July 25, at the Jackson Armory, 100 Armory Court, Jackson, Michigan. Doors open at 8:00 a.m.; auction at 4:00 p.m. Donation: \$1 in advance, \$1.50 at the door. Table reservations are \$1 (\$1.50 for reserved table). Door prizes, free parking, many tables. Mobile talk-in on 146.94 FM and 3.915 MHz. For tickets, accommodations, or further information, contact Cascades ARS, Box 512, Jackson MI 49201.

feels have been very well attended by hams and others from several states.

OHIO

Mark Sept. 26 for the 1971 Cincinnati 34th Annual STAG hamfest, the one big STAG amateur radio event of the year. Meet all of your friends here. The event will be held at Stricker's Grove, Compton Road, Mt. Healthy, Cincinnati, Ohio. Door prizes each hour, raffle, lots of food, flea market, model aircraft flying, and contests. Identify "Mr. Hamfest" and win prize. \$5 cost covers everything. For further details, contact John Bruning W8DSR, 6307 Fairhurst Ave., Cincinnati OH 45213.

INDIANA

This year the Original FM Hamfest is slated for the first Sunday in August, and it will be held rain or shine, according to members of the Fort Wayne Repeater Association, sponsors of the annual affair. The hamfest is to be held adjacent to Crooked Lake, where plenty of campsites and a nice park are available. A flea market is on the schedule, so load up the family and take your goodies with you. Head for Steuben Co. 4H fairgrounds—take I69, and go 3 miles south of the Indiana Tollway (Hwy 80—90). First prize will be a Regency HR-2 2m FM transceiver. Registration is only \$1.50 per amateur, which includes a ticket for the main prize drawing. Talk-in frequencies: 34.76 repeater, 46/88 repeater, .94 direct, and 52.525 direct—all FM, of course.

Indiana Radio Club Council's annual picnic Sunday, July 11th, LaPorte County Fairgrounds, LaPorte, Indiana. Large flea market with reserved locations available for large exhibitors and vendors on the midway and main building. Mobile FM clinic. Prizes. Tech sessions. For flyer write: Dave Osborn K9BPV, Box 272, LaPorte IN 46350.

5. Logs, photos, and tape shall be sent to WAS-AT Award, Dayton Amateur Radio Association, P.O. Box 44, Dayton, Ohio 45401.

6. Any question of contact authenticity will be submitted to an impartial committee, the members of which are not in the contest. Such members will be selected from the various net control stations of the Saturday SSTV Net which operates on 14,230 kHz at 1900 GMT.

The contest has already started, so start recording those SSTV contacts now.

ILLINOIS

The 14th annual hamfest of the Six Meter Club of Chicago Inc. will be held Sunday August 1 at the picnic grove on U.S. 45, 1 mile north of U.S. 30, 5 miles south of U.S. 6, Frankfort IL. Food and drinks will be available. Swap-and-shop section provided. Advance registration \$1.50, admission at the gate \$2. For tickets and further information contact Al Bagdon K9YJQ, 7804 66th Place, Argo P.O., IL 60501. Talk-in frequencies will be on 50.40 MHz AM and 146.94 MHz FM.

NEW JERSEY

The Knight Raiders VHF Club, K2DEL, will hold its 5th annual hamfest at Westbrook Park, West Milford NJ on Sunday, Aug. 15. Manufacturers' displays, gigantic flea market, contests, auction, 2m transmitter hunt, FM session, Navy MARS meeting, and a good time for all. Main door prize is the Drake TR-22 w/m FM transceiver; other door prizes also. Big raffle for the Drake ML-2 2m FM transceiver; raffles are 3 for \$1 and are available now. Free beer, swimming, picnic tables, and barbecue pits available. Refreshment stand on premises. Talk-in Station K2DEL/2 will operate on 50.425 MHz AM, 145.71 MHz AM, 146.94 MHz FM using Drake ML-2 transceiver, plus operation on local Navy MARS repeater. Follow signs to hamfest site from Route 23. Tickets

MHz FM, 50.4 MHz AM, WAIXFZ repeater 146.04/146.91 output FM, or WA1KGO repeater (146.34/146.94). Admission: \$2 advance registration; \$3 at the door per ham; family, YLs, etc.: Free! For details and advance registration, contact: Charles Doran, 240 North St., Williamstown MA 01267.

MONTANA

The annual WIMU hamfest will be held at Mack's Inn, Idaho, 23 miles south of West Yellowstone, Montana on U.S. 191. The dates are August 6, 7, 8th. Pre-registration is \$3.50 per person before July 24th. Mail pre-registrations to Owen H. Wood WA7IZR, 407 North Main, Livingston, Montana 59047. Registration at the hamfest will be \$4 per person.

TEXAS

Texas VHF-FM Society.

Date: The weekend of Aug. 14. Location: Cibola Inn, Box 1145, Arlington TX 76010. U.S. Highway 80 near Collins Ave. Approximately midway between Dallas and Fort Worth. Host: North Texas Repeater Association (an association representing FM repeaters around Fort Worth and Dallas).

Saturday events: Equipment displays, technical sessions, hospitality room, registration, fashion show and luncheon, then trip to Six Flags Mall for XYL's (tentative), visit to Six Flags Over Texas, caucuses as required to prepare for business meeting Sunday. Sunday events: Business meeting, door prizes, raffle.

Cost: No registration fee. Amateurs attending will pay own cost of lodging, meals, and entertainment. Refreshments in hospitality room free. Raffle: Motorola HT-200 will be raffled. Motorola C & E is making the unit available at reduced price, Sentry Manufacturing Company is providing crystals free.

teur Radio Club is pleased to announce their sponsorship of the annual International Okanagan Hamfest in cooperation with the clubs in Kelowna, Vernon, and Kamloops. Motels, trailer, tenting and camping space are all available, as well as shower, washroom, laundry, small lake and pool with crystal water. There will be a giant auction, transmitter hunt, contests, and games for both young and old. Evening entertainment assured. A registration door prize and a big raffle prize. Admission for licensed OMs \$3, YLs and XYLs \$2; family ticket \$5. Registration begins at 10:00 a.m. Saturday July 24. For further information contact Denny Warner VE7ASY, RR 4, Crawford Road, Kelowna, B.C. Canada.

FT. GEORGE AWARD

The Fort George Radio Amateur Club has made available an award certificate for all amateur radio stations making five contacts with any amateur station in the city of Prince George. These contacts are to be five *different* stations on any mode on any band. Logs should show date, time, mode and call of station worked and should be sent to: Fort George Radio Amateur Club, Box 835, Prince George, B.C., Canada.

CALI VI PAN-AMERICAN GAMES

All radio amateurs of America are invited to take part in the "CALI VI PAN-AMERICAN GAMES" contest. Only amateurs from the Pan-American countries are allowed to take part. Contacts are valid on the 15, 20, and 40m bands. The objective will be to contact as many stations as possible to get points:

Contacts with station HK5 CCP, 20 points
Contacts with station HK5 VD, 10 points.
Contacts with HK5 stations, 5 points.
Contacts with other stations, 2 points.

For further details write Liga Colombiana de Radioaficionados, Apt. 102, Cali, Colombia, S.A.

NEW PRODUCTS

ANTENNA NOISE BRIDGE



Higher frequency range amateur radio gear — including the popular 2m FM systems — can now be tested for resonant frequency and operation impedance with the Omega-t Systems Extended Range Antenna Noise Bridge. The unit combines precision and measurement flexibility normally found only in a collection of expensive laboratory equipment, according to Jack Finney, of Omega-t Systems. "We have previously developed a lower range antenna noise bridge, and now we are moving into high frequencies," he said. Able to be used over the entire range from 1 to 300 MHz, the bridge allows testing and tuning for optimum performance from an antenna and receiver without the use of additional equipment over the HF and VHF spectrum. It also replaces vswr bridges with a more accurate test system. *Omega-t Systems, 300 Terrace Village, Richardson TX 75080.*

QT-5 Continuous Tone Encoder

Alpha Electronic Services introduces the new QT-5 miniature solid-state subaudible continuous tone encoder, especially designed for use in the new amateur FM communications equipment. The unit provides an excellent, reliable method of repeater or multi-function control. The QT-5 is based on the same highly successful design concept used by Alpha for years

Now, with Injectorall's new No. 650 photo-etch PC kit, anyone, beginner or professional, can make professional printed circuits first time, every time. Injectorall's 650 is a completely packaged kit (nothing else to buy) using a photosensitive method for producing professional quality printed circuits. It can be used with assurance by engineers developing a prototype or a hobbyist constructing a home-lab project.

With Injectorall's Kit 650 you don't need a darkroom and you can completely eliminate commercially made boards. And if a magazine has a drawing you want to use, Kit 650 has materials included to let you make negatives from magazine circuits. Hobbyists and professionals alike have found it ideal for solid-state and integrated circuitry.



Kit 650, contains two photosensitized 3 x 4 in. copper-clad boards, a photographic test negative, and an ultraviolet light source. It also contains an exposure glass, clamps, developer, etchant, trays, resist remover, drill and complete instructions.

This low-cost easy way of making quality printed circuit boards is now available at all major distributors and retails for only \$10.80.


Hobbyist Tool Kit

A seven-piece hobbyists' tool kit — an ideal base upon which electronic hobbyists and kitbuilders can build

tor. The standard CM 41 series Tri-A-Lite is available with a choice of six different indicator colors and any long-life Chicago Miniature T-1 lamp. *Chicago Miniature, 4433 N. Ravenswood Ave., Chicago IL 60640.*

Miniature Sine/Square Wave Generator Gives High Accuracy at Low Cost

A miniature transistorized sine/square-wave generator, Model DF-24, is designed especially for exacting electronic work where high frequency accuracy is required, yet it is priced at only \$65. Frequency range, in three bands, is 10 Hz to 166.5 kHz for sine wave... 20 Hz to 20.0 kHz for square wave. Frequency accuracy for sine and square wave is 1% + Hz, accrued by the use of solid-state components and accurate calibration. Output signal amplitude is controlled by a variable attenuator with high resolution.

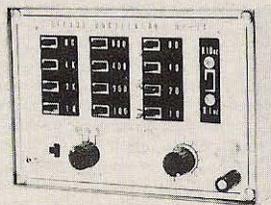

Weighing just over 2 lb, measuring 7 x 3 x 5 in. and requiring no external source of power, the unit may be used anywhere. Power is furnished by self-contained penlight batteries, giving low distortion and constant output... or, if desired, by any external 12V dc source. The unit is available from *Electronic Tools Division, C. H. Mitchell Co., 14614 Raymer St., Van Nuys CA 91405.*

NEW LITERATURE

SIGNETICS

Quantities of the popular "Applications Memos" handbook are once again available from Signetics, free for the asking. Containing approximately 400 pages, the 5½ x 7 in. paperback handbook contains an introduction to digital logic and discusses digital considerations by family, decoding and steering, counters, shift registers and memories, interface and display elements, linear considerations, timing circuits, and parallel data handling. All of these subjects are quite important to the electronic designer or amateur operator who may be unfamiliar with the ways in which integrated circuits may be used.

Furthermore, the experts who prepared the handbook at Signetics are available to answer your questions. Let them know if they can help you with information that might shed some light on integrated circuit technology.

TIME

TIME Corporation is offering a 12-page specification guide describing electronic laminates. The brochure is intended as an aid in specifying copper- or other metal-clad continuous-roll laminates for the printed circuit and flexible cable industry. In many cases these laminates are recognized as a major breakthrough in the printed circuit and flexible-cable industry. In many cases these laminates are recognized as a major breakthrough in the printed circuit and flexible-cable industry. In many cases these laminates are recognized as a major breakthrough in the printed circuit and flexible-cable industry. In many cases these laminates are recognized as a major breakthrough in the printed circuit and flexible-cable industry.

Contact Vincent J. Sardo, TIME Corporation, Salem Industrial Park, Salem NH 03079, (603) 893-1661.

NATIONAL SEMICONDUCTOR

A new brochure describing Tri-State logic circuits is now available from National Semiconductor Corp. The 20 page document (TTL-5) describes the Tri-State logic circuit concept, its unusual characteristics and typical uses. Also included are descriptions and specifications for numerous Tri-State devices, including multiplexers, demultiplexers, flip-flops, line drivers, buffers, hexadecimal counter/latch, decade counter/latch and 256-bit read only memory. For a free copy, write to National Semiconductor, 2900 Semiconductor Drive, Santa Clara CA 95051, Attn: Marketing Services.

GC Electronics Catalog

A new general catalog has been published by GC Electronics (number FR-71-72) which lists over 14,000 products from all of the company's various operating divisions. The 312-page catalog includes complete listings for these GC divisions: GC Electronics, Walsco, Electrocraft, Magic Color, Telco, Audiotec and Calcetro.

The catalog is the first totally new presentation of all its products turned out by GC Electronics in two years. It contains more than 1800 new items which the major American electronics manufacturer and distributor has added to its line in the intervening period.

GC Electronics product lines represented in the catalog include chemicals, servicing tools, printed circuit materials, servicing aids, automotive connectors and hardware, accessories, replacement parts, electronic hardware, replacement knobs and replacement antennas.

Under the "Walsco" trademark are chassis punches and a comprehensive grouping of replacement rubber belts, drives and pulleys for phonos and tape recorders. The "Electrocraft" line includes plugs and jacks, connectors, adapters, switches, cable clamps and ties. The "Magic Color" line consists

THIRD GENERATION OF MONOLITHIC OP AMPS

12th NEW JERSEY QSO PARTY AUGUST 21-22

The Englewood Amateur Radio Association, Inc., invites all amateurs world over to take part in the 12th New Jersey QSO Party.

RULES: (1) The time of the contest is from 1900 GMT Saturday August 21 to 0600 GMT Sunday August 22 and from 1200 GMT to 2300 GMT on Sunday August 22. (2) Phone and CW are considered the same contest. A station may be contacted once on each band—phone and CW are considered separate bands. New Jersey Stations may work other New Jersey stations. (3) General call is "CQ New Jersey" or "CQ NJ." New Jersey stations are requested to identify themselves by signing "DE NJ" on CW and "New Jersey calling" on phone. Suggested frequencies are: 1810, 3555, 3740, 3930, 7060, 7275, 14075, 14280, 21100, 21375, 28800 kHz, 50-50.5, 144-146 MHz. Suggest phone activity on the EVEN HOURS. (4) Exchanges consist of QSO number, RST, and QTH (ARRL Section or country). N.J. Stations will send county for their QTH. (5) Scoring: Out-of-state stations multiply number of complete contacts with New Jersey stations times the number of New Jersey counties worked (maximum of 21). New Jersey stations: W-K-VE-VO QSOs count as 1 point; DX stations count as 3 points. Multiply total number of points times the number of ARRL sections (including NNJ and SNJ—maximum of 74). KP4, KH6, KL7, KZ5 count both as 3 point DX contacts and as section multipliers. (6) Certificates will be awarded to the First place station in each N.J. county, ARRL section, and country. In addition, a second place certificate will be awarded when four or more logs are received. Novice and Technician certificates will also be awarded. (7) Logs must also show

Function Generator IC Produces Square Wave & Triangular Wave Simultaneously

A voltage-controlled oscillator of exceptional stability and linearity is now available in large quantities from stock for application in tone generators, frequency shift keying, frequency modulators, clock generators, signal generators, and function generators. This \$6 integrated circuit is capable of performing all the operations of currently popular \$300 function generators with equal precision and accuracy.

Designated the Signetics 566 function generator, the oscillator produces two outputs simultaneously: a highly accurate buffered square wave and a highly linear buffered triangular wave. Frequency is extremely stable (100 ppm/°C is typical).

Frequency of oscillation is determined by an external resistor, a capacitor, and the voltage applied to the control terminal. The oscillator can be programmed over a 10:1 frequency range by proper selection of the external resistance, and the device can be modulated over a 10:1 range with exceptional linearity by the control voltage.

'Jean' FG7XT Confirms 1st DXCC on RTTY



DX FOOTNOTES



This is Wolfgang Renner, YA1RG, and his new bride Hannelore. Wolfgang should be familiar to most DXers. He is, of course, one of the big guns in the famous Camel Drivers Radio Club in Afghanistan. From the photo, it should be understandable if Wolfgang is spending a little less time on the air.

One of the simpler ways to boost your countries worked total is to check into some of the DX nets currently active. At almost every check-in there are at least a few good ones ready to give you a new country. One net to look into is the Western Hemisphere Net on 7205 kHz at 0200 GMT. KP4CL is net control station.

For tougher DX there is the Arabian Net on Saturdays at 1900 GMT on 14295 kHz. Some very rare Middle Eastern stations can be worked including JY, SU, and ST.

Those who are still looking for Swan Island (KS4) should be able to catch WA1ARF/KS4 on the YL-SSB net, 14332 kHz, on weekends. A

as close to 7085 kHz as possible and listens around 7215 kHz between 0330 and 0400 GMT. QSL cards with an-SAE and-IRC's should be sent to LA3UF.

At the present time, the only legal, genuine, guaranteed for real, operator in Cameroun is TJ1AW. Charlie is a good operator and a fast QSLer. Cards go to Charles Thompson, YAOUNDE, Department of State, Washington DC 20521. Charlie, incidentally, is a life subscriber to 73—and this is just about a guarantee that he is going to be on the air for at least the next 85 years.

ZM7AG, Jim in Tokelaus, keeps on appearing around 0400 GMT on the low end 20 meter sideband. He is often greeted with huge pileups, but he is getting adept at rapid QSYs... so be cagey and do a lot of listening and tuning around when you hear him. The anecdote is getting around DX circles that King Hussein, JY1, made a schedule with Jim in order to bag a new country for His Majesty's countries total. Jim forgot to keep the schedule! Don't you wish you were that rare?

If you are more successful than JY1, you can QSL via the International DX Association (INDXA), Box 125, Simpsonville MD 21150. An SASE speeds things up immeasurably.

RECIPROCAL LICENSING WITH JAMAICA

The Jamaica Amateur Radio Association and the Jamaican government announced the granting of reciprocal licenses between Jamaica (6Y5) and the U.S. The agreement has been in force since the end of April and the Jamaican government is already processing reciprocal license applications.

MORE NEW LITERATURE

New Transistor Substitution Handbook

TRANSISTOR SUBSTITUTION HANDBOOK, 11th Edition, by Howard W. Sams Engineering Staff. Although bipolar transistors are noted for their low failure rate, some of them do have to be replaced. As long as the specific type number required is readily available, replacement of the transistor is no problem because a duplicate of the original should be used whenever possible. All too often, however, the exact replacement cannot be obtained without considerable delay. Furthermore, the great variety of types available make it difficult to determine which transistor can be substituted for the original.

Production of the new 11th edition of this book is possible because of the ability of modern-day electronic computers to handle a large quantity of information in a relatively short length of time. The computer selected the substitutes in this handbook in much the same manner that an individual would select a transistor replacement. The electrical and physical parameters as shown in the manufacturer's published specifications for each bipolar transistor were given to the computer, and then each transistor was compared with all the others. Over one billion comparisons of data have been made in the preparation of this book.


The transistors which matched within given limits are listed as substitutions. Representative types of American, European, and Japanese manufacturers of general-purpose replacement transistors.

A second section contains additional information on general purpose replacement transistors: the manufacturer, the polarity (NPN or PNP), the material (germanium or silicon), and the recommended applications.

The information in this handbook can be used by everyone concerned

throughout the commercial communications industry.

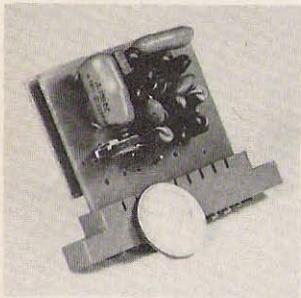No mechanical reeds or relays are required and the frequency determining network is an integrated circuit, enhancing the long-term reliability and stability of the QT-5.



Available assembled and ready to install or in simple-to-build kit form, the unit will adapt to any FM transmitter, and a variety of installation instruction booklets have been prepared to make installation in specific radio models simple and fast.

Tone frequencies are available in a wide choice of standard EIA frequencies from 67.0 to 203.5 Hz or even special frequencies if desired.

The QT-5 is fully compatible with Alpha's QT-10 decoder or any other standard subaudible tone decoder that meets EIA specification. Call or write Alpha Electronic Services, 8431 Monroe Ave., Stanton CA 90680.

PC Kit Aids Beginner or Professional

At one time building an electronics project was hard work for it involved drilling, cutting, reaming and deburring a metal chassis. Some of those early chassis weren't aluminum either, but steel; and so electronics construction meant sore muscles, cut and bleeding fingers, and frazzled nerves.


Injectoral Electronics Corp., Great Neck, N.Y. has taken the sweat out of electronics and put pleasure back in.

their tool needs — is a featured item in GC Electronics' new catalog.



The tool kit consists of long-nose and diagonal cutting pliers, screwdriver, soldering iron, soldering aid tool, heatsink tool, and a coil of rosin-core solder — the most-needed items for the hobbyists' tool chest.

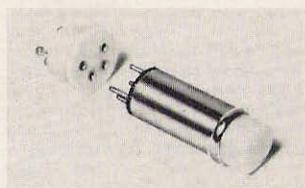
Marketed through GC Electronics' Calcetro Division, the tools are blister packed for store rack display. The kit is designated catalog number H3-378 and retails for \$7.95. GC Electronics, Div. of Hydrometals, Inc., 400 South Wyman St., Rockford IL 61101.



Three-In-One Indicator Lights

The CM 41 series Tri-A-Lite, an exclusive Chicago Miniature design, appears white in the off position and takes on color only when an input voltage is applied to one of its number-coded contacts.

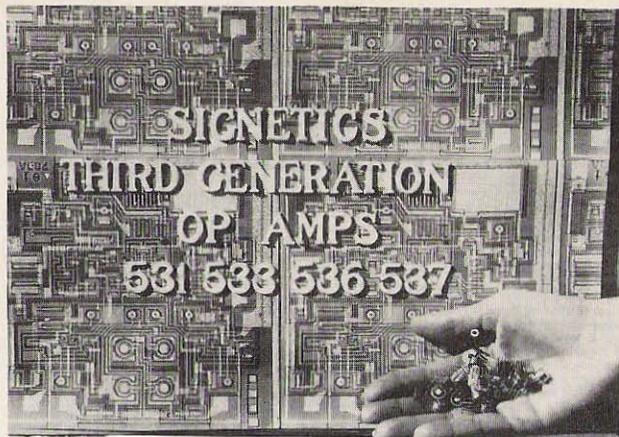By providing three different colors in a variable sequence, the Chicago Miniature CM 41 Tri-A-Lite takes the place of three separate indicators. The CM 41 Tri-A-Lite color sequence is variable with positioning of the mounting pin configuration, and can be predetermined by the user through coded pins and a companion connec-



The electronic industry's "third generation" of operational amplifiers, a family of four new linear integrated circuits, has been developed by Signetics Corp. and is now available in quantity from stock. The announcement was made by Paul Kollar who is in charge of marketing the company's standard linear products.

"We define the 'third generation' as the next line of operational amplifiers that will solve specific problems without sacrificing performance, ease of use, or standard pin arrangements," Mr. Kollar said. "Our devices eliminate the major headaches usually associated with state-of-the-art op amps, and they achieve a new level of performance.

First Generation: 1964

The first generation of operational amplifiers was the 709, which appeared in 1964. It was the first useful linear integrated circuit, and it simplified many of the problems that engineers faced in designing analog systems.

Second Generation: 1968

The second generation of op amps appeared in 1968 in the form of the 101/741 devices. By providing input

and output protection, simplified compensation, and better specifications, these newer devices eliminated the major problems that were associated with using the 709 op amps.

Since the introduction of the 101/741 devices, designers have tried to give operational amplifiers tighter specifications, but the new units were not easy to use. High slew rate operational amplifiers like the 715 achieved faster speeds, and low-power op amps like the 735 drew less current, but they sacrificed dc stability, ease of compensation, and output protection, the very features which made the 101/741 so popular.

Operational amplifiers with FET (Field-Effect Transistor) inputs, such as the 740, offered much promise but few performance guarantees. Input current specifications were not as good as those for existing low-offset precision op amps. Precision op amps like the 108 offered specifications that were attractive to designers, but they sacrificed input protection, standard output drive, and offset null.

Third Generation: 1971

The third generation of op amps is

of outdoor and indoor TV antennas of all types, couplers and splitters. Antenna installation hardware comprises the bulk of the "Telco" product line.

GC Electronics Division of Hydrometals, Inc., manufactures and distributes a full range of electronic parts, hardware, accessories, chemicals and supplies for service technicians, engineering labs, hobbyists, consumers and industry.

being introduced with a family of four new devices: 1) the Signetics 537 precision op amp with extremely low input offset and bias currents, 2) the Signetics 536 general purpose, high performance op amp that uses a high-impedance field-effect transistor (FET) input stage, 3) the Signetics 533 high performance op amp which consumes only 100 microwatts of power at $\pm 3V$ supplies, and 4) the Signetics 531 high slew rate op amp. Precision "Punchthrough" Op Amp

"The Signetics 537 is a punch-through op amp, which has the same parameters as the LM108 and LM108A," Mr. Kollar said, "except that our 537 has a maximum differential input voltage of $\pm 30V$ and the other two devices have a maximum differential input of only 1V. Such a low differential range severely limits the 108's usefulness and makes it susceptible to damage by transients. Why pay for ultraprecision but with no input protection and substandard output drive?"

With standard pinout compatible with the 101/741, the Signetics 537 is packaged in a 8-pin TO can.

"Our 536 is a FET-input op amp," Mr. Kollar said, "that does what op amp design experts said couldn't be done — that is, achieve offset voltages approaching those of general purpose devices and input currents comparable with hybrids. Specially selected 536 units can be supplied which will meet the 7.5V offset specified for the 101 and 748."

GMT date, time, band, and mission, and be received not later than September 18, 1971. The first contact for each claimed multiplier must be indicated and numbered and a checklist should be attached. Multioperator entries should be noted and calls of participating operators listed. Logs and comments should be sent to Englewood Amateur Radio Association, Inc., 303 Tenafly Road, Englewood, New Jersey 07631. A size #10 SASE should be included for results. (8) Stations planning active participation in New Jersey are requested to advise the EARA by August 7th of your intentions so that we may plan for full coverage from all counties.

NEBRASKA QSO PARTY

The Lincoln Amateur Radio Club Inc. of Lincoln, Nebraska announces the 1971 Nebraska QSO Party.

DATE — TIME:

Starts 0000 GMT Sept. 5

ENDS 2300 GMT Sept. 6

FREQUENCIES: 3560—3982

7060—7260

14060—14300

21060—21360

18060—28560

QSO EXCHANGE: Nebraska stations; give signal report and county. All other stations; give signal report and state.

SCORING: Nebraska stations; 2 points for each QSO, each mode. Multipliers are each state, each province, and each country. All other stations; 3 points for each QSO, each mode. Multipliers are each Nebr. county. Mobiles in a different county count as a separate QSO and multiplier.

BONUS SCORING

FOR ALL PARTICIPANTS!!!!

The Lincoln Amateur Radio Club will be operating KQØNEB at the Nebr. State Fair from Sept. 1 to Sept. 9. Any

Team Wegimot, FG3XT of Guadalupe, became the first ham to make DXCC on RITTY. Jean has actually worked 110 countries, but it took WBØAAB on May 1, 1971, to send his QSL to make one hundred countries confirmed. Congratulations are in order for a real achievement in ham operating.

IOWA

The annual Iowa 75 meter phone net picnic will be held on Sunday, August 15, at Riverview Park in Marshalltown, Iowa. All amateurs are invited. There will be a swap table and nice prizes to be given away. The festivities will start with a potluck dinner at noon with the remainder of the festivities occurring Sunday afternoon.

NEVADA

The Annual Sierra hamfest will be held on Saturday, Aug. 14, at the California Bldg. in Idlewild Park, Reno, Nevada.

contact with KQØNEB during the fair week will count for points in the QSO party, regardless of whether it is during the QSO party. The scoring for working KQØNEB as follows: 10 points each contact, each mode. Also count as a separate multiplier. If KQØNEB is worked at least once on four separate bands, add 1000 points to total score.

Certificates will be issued to the high score in each Nebr. county, high score for each state, province, and DX country. Other certificates will be issued where deemed necessary by the Awards Committee.

To be considered for a certificate, all logs must be sent to the Awards Chairman, Michael Nickolaus, 4921 Tipperary Trail, Lincoln, Nebraska 68512, by October 15, 1971. Logs must be in GMT. Final score must be indicated on a summary sheet. Enclosed business size envelope S.A.S.E., for a copy of the results.

particular good time to look for him is 0130 to 0200 GMT on Fridays. On Saturdays try the same frequency from 2100 GMT onward. This should be a good catch for those who still don't have their Advanced tickets. All QSLs for WA1ARF/KS4 should go to WA6MWW.

MP4MBB in Muscat has a new beam which is reportedly helping him put in a much stronger signal into the U.S. He can generally be found Wednesdays at 2330 GMT on 14218 kHz.

Skepticism is accompanying the appearance of 1A1A. However, those who did not work KD3UMP and C21AA thinking they were bogus, are now among the supporters of Gus, W4BPD, when he says to "Work 'em first and ask questions later."

Italian stations are now using the new prefixes. Italian stations can use the first digit in the Italian version of the Zip Code in their prefix. The only problem being with the area in Northern Italy whose delivery unit begins with "1". In the Piedmont area they can use IP1. Also some of the islands can use special prefixes with Sardinia becoming ISØ and Sicily IT9. There are also other island prefixes running from 1A5 to 1MØ. During the weekends in May you may run across 1BØKDB operating on the band edge on twenty SSB. QSL for this one to Box 143, Palermo, Sicily.

Due to civil strife all ham activity in Ceylon (457) has been stopped and the government is reported to have confiscated all ham gear for "safe-keeping."

UJ8AC, Tadzhi, is often found on Saturdays between 0200 and 0400 GMT above 14200 kHz.

CR3DN should be on the air now from Portuguese Guinea where he is stationed for the next two years. QSLs should be directed to CT1BH.

TA3AC, Turkey, looks for U.S. stations on 80 and 40. He transmits as close to 3780 kHz as QRM allows and listens on 3805 kHz between 0400 and 0500 GMT. On 40, he transmits

QSL INFORMATION FROM THE W2NSD/1 DX HIDEAWAY

Cards for ZF1WF and 7Q7AA are now being handled by K4CDZ. QSLs for KG6SW go to W7YBX, for VK9FH to WØKHI, and for WA8FPN/KS6 to WA6BKS. The latest QTH we have for HS3AFB is Box 4954, APO San Francisco CA 96288. YB3AAY can be QSLed to Jess Marino, U.S. Embassy, Surabaya, APO San Francisco CA 96356. Cards for KB6CT go to the Federal Electric Corp., APO San Francisco CA 96401. F9MS is QSL manager for FR7ZU/E, /G, and /T. He requests a self-addressed envelope and 3 IRCs.

Jim Vaughan, K4TXJ, has written to 73 to say that he has become QSL manager for Jack, ZS3KC, in Swakopmund, Southwest Africa. Jim's QTH is 5504 Datura Lane, Louisville KY 40258. The usual SASE would be appreciated.

You can QSL Sam, MP4TDM in the Shaikdom of Ras Al Khaimah, through K2DRN, Vernon Damerson, 265 Davis Rd, Bedford MA 01730. A SASE is essential for U.S. stations and a SAE and IRCs is essential for DX ops who want the MP4TDM card.

Those who worked Kevin, ZK1BM, while he was on Cook Island, should send their cards to W7VRO.

KW6HA cards should go to Gary Davey, 349 Sanford St., Leucadia CA 92024.

Anybody with information on DX operations, QSL managers, or the like, is invited to send it in to 73. Anybody who sends in a good picture of any DX operation which we eventually publish gets a free year of 73 (it could be worse, it could be two years). Just send in your comments and photos to DX FOOTNOTES, 73 Magazine, Peterborough NH 03458.

with transistor replacement — be it in industrial, commercial, or home-entertainment devices.

TRANSISTOR SUBSTITUTION HANDBOOK, 11th Edition, Catalog No. 20835. Size: 160 pages; 5½" x 8½", softbound. List Price: \$2.25 (\$2.85 in Canada).

Allied/Radio Shack Catalog

Described as the "first and only catalog of its kind," Allied Radio Shack's new Spring/Summer 1971 Electronic Parts, Accessories and Kits Catalog No. 212 is a handy buying guide for the builder, hobbyist, fix-it man, experimenter, or anyone wanting a full selection of electronic parts, accessories, maintenance items and kits.

The 116-page catalog includes thousands of hard-to-find or specialized items like tubes, transistors, cables, tools, connectors, wire, plugs, adapters, antennas and test equipment. It also lists many exclusive products, and previews Allied Radio Shack's line of Knight-Kits and Science Fair kits for 1972.

Catalog 212 is available free on request from Allied Radio Shack, 2725 W. Seventh St., Fort Worth TX 76107.

Allied Radio Shack, a Tandy Corporation Company (NYSE), is the world's largest chain of consumer electronics stores. The company has more than 950 stores in 49 states.

"KA NET" CHANGES

Tokyo, Japan... The Far East Auxiliary Radio League (FEARL) has announced a frequency and time change for the "KA Net." Beginning in July, the net will meet twice each Sunday at 0001 GMT and again at 1200 GMT. The net frequency will change to 14,300 MHz. Net call will remain, "CQ Ka Net."

FEARL, sponsor of the "KA Net," is composed of amateur radio licenses assigned to United States Forces, Japan.

advised by my lawyers that
ou goons don't ever proofo
lousy man. I'm sure if you b
back of books are in
LETTERS
you ignored my comments in
I insist that you print ev
should be boiled in oil ov

Old Ads

Enjoyed the 50-year old ads on p.
97 this month. Hope you'll run more
of them.

Ron Wyllys
465 Caromar Dr.
Madison WI 53711

Excellent idea on the 50 year old
ads — would like to see more of them.

Joseph F. Dineen W1JSS
9 Winter Terrace
Westwood MA 02090

Russia

I was just on a trip to Moscow and
Leningrad. Couldn't locate a single
Societ ham! My guide didn't even
know what I was talking about. Any
suggestions in case of future trips??

Lee Barnes
132 Starlite Drive
San Mateo CA 94402

Drop a note to Box 88, Moscow
and tell them you plan to be there
... and watch for the Red carpet.

... Wayne

Two Points

Two subjects:

Referring to the first question on
page 80 of May 73 Magazine (Questions,
Questions), the answer given states
that FM has worse signal-to-noise
ratio characteristics than AM or SSB.
This may or may not be the case
depending on the basis of comparison.
This is clearly pointed out in an article
that appeared in Vol. 3, #5 of FM
Magazine entitled *How Does FM
Stack Up?*, and in standard textbooks
on communication theory (for example
see Chapters 5 & 6 of "Communication
Theory: Transmission of Waveforms
and Digital Information," by D. J.
Sakrison). Both the FM article and

confirming the accuracy of my forecasts.

John Nelson

Beginner

I have been buying 73 for the past
four months and I like it a lot. I am
trying to decide whether to subscribe
or not. I would subscribe in a minute
if I could be sure that there would be
something for the beginner in each
issue. Sure, the first thing I'll do when
I get my General is to get on 2 meter
FM and all, but right now all I'm
interested in is getting my Novice. 73
is my favorite magazine but I get no
help from it right now. I am 15, just
starting out in radio, and sure need all
the help I can get. Thanks a lot.

Mike Lonas
1020 Karenwood Dr.
Maryville TN

*We've got some excellent series
slated and plenty of good beginner
articles in the works. Keep reading!*

... Ken

No Study Course

Just a note to inquire why the
General Class License Study Guide did
not appear in the April issue? If it was
there, I could not find it. In 7 articles,
you have covered 28 of the 52 questions
in the FCC list. Please keep up the
good work.

F. C. Van Widden WA5FF3 (Tech.)
607 E. Oklahoma St.
Wentworth OK 73096

*April was FM month. The General
series is back now, though.*

... Ken

Outmoded

Shades of the U.S. Army and my
many years of operating FM with and
without repeaters. I was rather disappointed
in the magazine when it was
discovered that it exalted an archaic
means of communication. When I
received my last discharge from the
Army I hoped that I would never
again have to use, read or listen to this
dated mode again. To have a magazine



Price — \$2 per 25 words for non-
commercial ads; \$10 per 25 words for
business ventures. No display ads or
agency discount. Include your check
with order.

Deadline for ads is the 1st of the
month two months prior to publication.
For example, January 1st is the
deadline for the March issue which will
be mailed on the 10th of February.

Type copy. Phrase and punctuate
exactly as you wish it to appear. No
all-capital ads.

We will be the judge of suitability of
ads. Our responsibility for errors extends
only to printing a correct ad in a
later issue.

For \$1 extra we can maintain a reply
box for you.

We cannot check into each advertiser,
so Caveat Emptor. ...

6 METER FM (postpaid):
RT-176/PRC-10 transceiver, \$30;
RT-70/GRC transceiver, \$30. Also
T-150, \$40; 300 watt gasoline AC
generator, \$32.50. WB4GEW, CPO
2183, Berea KY 40403.

REALISTIC TRANSMITTER BARGAINS:
Johnson Valiants \$89; Johnson
Factory Wired Valiant with Johnson
SSB Adaptor \$189; Many More.
Get Complete Listing. Stan Burghardt
W0IT, Box 73, Watertown SD 57201.

MILITARY SURPLUS. 12PDT 24V
dual 400 ohm coil, relay 95¢. Silicon
dielectric grease 8 oz. tube, \$1.45. 10
pound surplus assortment, \$4.00. All
new and postpaid USA. Catalog on
request. Electronic Systems. P.O. Box
206, New Egypt NJ 08533.

MECHANICAL FILTERS: 455 Khz
Center Frequency. 2.1 Khz. \$18.95.
300 Hz \$22.95. J.A. Fredricks, 314
South 13th Avenue, Yakima WA
98902.

SWAN 270 with Swantenna, Shure
404C mike. Year old. \$390.00, you
pay postage. WN6OOK, 409 Beverly
Drive, Redlands CA 92373.

MOTOROLA X53GTV-10, 4 xmit, 2
rcve, \$100. 2 GE high band,
M A 3 6 W — 4 x m i t , 3
rcve — MA/E36B, 4 xmit, 4 rcve,
\$110. Ca. All accessories except ovens.
You pay shipping. R. Eckton,
1021 W. Cedar, Redlands CA 92373.

DUAL-GATE MOSFET 2-METER
PREAMP. PC construction, 18 db
gain, 3 db NF typ. Fully wired and
guaranteed, only \$13.95 ppd in U.S.
Mich. res. 4% sales tax. HALE ELECTRONICS,
803 17th St., Bay City MI
48706.

73 MAGS OCT 1960 THRU DEC
1969 National 2 Meter FM BASE
RX & TX BEST Offer. W3YB, 580
Durham Rd., Pennel PA 19047.

RD-112 CW INKING RECORDER.
0-350WPM. Uses standard 3/8" tape.
115v-60Hz. Great for making visual
copy of CW. Used Good
\$125. — TV-10B Tube Tester \$65.00.
Mike Tewksbury, Box 8324, Norfolk
VA 23503.

VHF SELLOUT: Ameco TX 62 \$89;
Gonset GC105 \$69; Johnson 6N2
Transmitter \$69; Swan
250C/TV2B/117CX \$549; Swan
TV2B New \$229. More items. Get
Complete Listing. Stan Burghardt
W0IT, Box 73, Watertown SD 57201.

MANUALS — \$6.50 each:
R-390/URR, SP-60JX, CV-591A/
URR, URM-25D, LM-21, URT-7,
BC-639A, UPM-45, UPN-12, FR-5/U,
FR-38/U, BC-779B, OS-8C/U, ARR-7.
S. Consalvo, 4905 Roanne Drive,
Washington DC 20021.

TRADE: GT550, AC supply, vox,
calibrator. Perfect condition. Inter-
ested in T4XB or SB220 or best cash
offer. Jim Fleming, 7528 Brynmawr,
Chicago IL 60631. 775-8179.

WEST COAST HAMS buy their gear
from Amrad Supply Inc. Send for
flyer. 1025 Harrison St., Oakland CA
94607, 451-7755, area code 415.

SELL: 73 Magazine \$1.00 per year.
Hoehner Melodica w/music \$5.00.
Greystone 20 volume Encyclopedia of
Photography. (Cost \$80) \$20.00. Koss
Pro 4A headphones \$15.00. Stephen
Clifton WA2TYF, 800 W. End Ave.,
New York NY 10025.

NEW SIGNAL-ONE, CX7, unopened
carton, warranty, latest model. Sell/
trade, want Collins, Drake. Don Payne,
K4ID, Box 525, Springfield TN
37172. Days (615) 384-5573, nights
(615) 384-5643.

SELLING OUT WAREHOUSE full of
teletype and facsimile machines, parts
and equipment. Loads of electronics.
No fair, reasonable offer refused.
Weekdays 10-4, Saturdays & Sundays
by appointment. C. G. Goodman Co.,
5826 S. Western Ave., Chicago IL
60636. Phone 312-GR-6-8200.

FM HAMFEST SUNDAY AUGUST 1,
NEAR ANGOLA, INDIANA. Big prizes,
free flea market, entertainment for
the ladies and kids. Picnic grounds
campsites, boating, food, soft drinks
available, rain or shine. Call in Freq.
146.34/146.76, 146.94, 52.525. For
information contact Fort Wayne Re-
peater Assn., Box 6022, Fort Wayne
IN 46806.

CRYSTALS for Regency, Varitronics,
Drake, & Galaxy transceivers and for
police monitors. Receive — \$4.50
postpaid; Transmit — prices vary —
write. One week delivery. Derrick
Electronics, Box 457, Broken Arrow
OK 74012.

CINCY STAG HAMFEST: Attention
hams; Mark this date, Sept. 26, for the
1971 Cincinnati 34th Annual STAG
Hamfest, the one big STAG Amateur
Radio event of the '71 year. Meet all
of your friends here. More details
later. W8DSR, Hamfest Secretary.

FOR SALE: Gonset sidewinder-2
mtr. SSB, CW & AM transceiver with
a.c. power supply, & manual. Excellent
condition. \$195.00. Gonset d.c.
supply (new) \$50.00. W1VYB

the text point that FM has better signal-to-noise characteristics than AM or SSB when the bandwidth of the FM signal is increased. The improvement in S/N of FM over SSB is proportional to roughly the FM bandwidth squared. The FM Magazine article states that in comparing a 15 kHz deviation FM signal with either AM or SSB, the transmitting power being equal, FM is clearly better by a significant margin (27.6 dB difference in S/N provided that the FM signal is above threshold).

I will be set up shortly to operate FM on the 80-10 meter bands. Admittedly, I will have to limit the bandwidth to comply with FCC rules and therefore can't take full advantage of the capabilities of FM. I am looking for stations that desire to experiment with FM on these bands to see what the effect of QRM etc. is. If anyone is interested in participating in such experiments, I would appreciate a letter from them.

H. Stanley Staten WA7IKJ/NØPW5
545 University Village
Salt Lake City UT 84108

Those of us who have used narrowband FM on the lower bands in years gone by found that the major problem with it was the lack of FM detectors on receivers. FM does not stack up with AM and SSB when slope detection is used. Since there seems to be no prospect whatever of getting FM detectors built into amateur low-band receivers, there is little prospect for successful use of NBFM on these bands.

...Wayne

DX Forecasts

The May issue of 73 has a letter from Bill Peterson K9OWQ saying that I used to forecast VHF-DX but do not do it anymore. He wants to know how come. It is true, I used to forecast VHF-DX but I quit because I did not have proper data to use for research purposes and I had no way of

that call itself a ham magazine devote so much of its effort to FM puzzles me. Why not rename it *FM*, a magazine dedicated to the elimination of tuning controls, or *The Senior Citizens Band FM Journal* - a magazine dedicated to channelized communications.

Joe Wimmer W6RFX

Because there are probably already magazines using those names.

...Ken

Encroachment

In the past year the Raritan Bay Radio Amateurs (R.B.R.A.) have been approached and asked if 146.460 MHz can be used as a repeater input channel. The R.B.R.A. has been on .460 for 15 years with 24-hour monitoring by club members. Could you publish the fact that 146.460 is active in the Sayreville, New Jersey area.

Mark Dzuban WB2IRX
329 Lee Ave.
New Brunswick NJ 08902

We'll publish the info, but we suggest you get your net to go over to FM. Stay on 146.46 and use the repeater for check-in. You'll be using the frequency you want in the mode for which it has been adopted as a national channel. Nobody loses!

...Ken

Stolen Rig

I would really appreciate it if you would print the following information: Somebody stole my Heathkit HX-30 6 meter sideband exciter (serial no. 6233), a Dow-Key DK-60 relay and a Turner SSB+2 mike. The sideband exciter is the piece of equipment which is most easy to spot because of the serial number but maybe the guy who ripped it off from me will also try to fence the mike and the relay at the same time.

At least they didn't steal my back

COMDEL SPEECH PROCESSOR, perfect, really boosts SSB signal; MINI-PRODUCTS vertical, 6-20 meters, only 11' high, no radials; best offer, or trade toward 2M FM gear. K1JDF, 65 Morton St., Canton MA 02021.

OUTSTANDING SSB DEALS: Drake T4XB/R4B/AC4/MS4 \$795; Galaxy III and DC Supply \$189; Heath HW32A \$79; National NCX3/NCXA \$219; National NCX5-MKII/NCXA \$399; Many More. Get Complete Listing. Stan Burghardt WØIT, Box 73, Watertown SD 57201.


issues of 73. Those are irreplaceable, y'know.

Any information concerning the stuff should be sent to me (WA1IVB) or the Stoughton (Mass.) Police.

Norman B. Blake WA1IVB
23 Oriole Rd.
Stoughton MA 02072

IC "8-Transistor" Oscillator

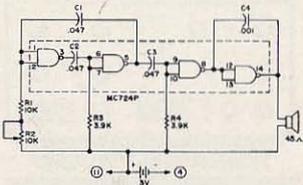I had some trouble building the code oscillator (Sessions, March 1971); keying was unreliable. I made some changes, and the overall operation was improved. Operation was made a great deal more reliable and keying is very consistent. Here is my modification:



Stan
5204 Penelope Lane
Knoxville TN 37918

HAMFESTS 37th HAMFEST AND PICNIC SUNDAY, AUGUST 8, 1971 Santa Fe Park, 91st and Wolf Road, Willow Springs, Illinois Southwest of Chicago. Exhibits for OM's and XYL's. Famous Swappers Row. Information and Tickets, Joseph W. Poradyla, WA9IWU, 5701 S. California Ave., Chicago IL 60629.

YOU ALL COME TO International Independent County Hunters Convention in Kansas City July 2, 3, 4, 1971. ASAS to WAØSHE for information. Cleo J. Mahoney, WAØSHE, 60C1 Blue Ridge Cut Off, Raytown MO 64133.

FOR SALE: Brand new built & aligned Heathkit Model HW-16 transceiver, key, headphones, & books from one who thought she'd like to but decided against it. Call Sharon, Mass. 784-3703 evenings or write Green, 15 Rob's Lane, Sharon MA 02067. Price: Anything within reason.

KWM2, 516F2 W/SPEAKER \$715. GE TPL, complete 30 W wideband FM mobile, now on 34-94, 94-94, \$210. R. A. Hall W1DQO, General Green Rd, Shelburne VT 05482.

STUDY FOR YOUR FIRST PHONE LICENSE at your own pace using the highly-successful Bell & Howell (DeVRY) courses. Contact Bill Welsh (W6DDB), 234 S. Orchard, Burbank CA 91506.

GE POCKET MATE Ht. 34/76 \$185; GE Voice Commander HT less Nicads 34/76 \$85; GE 9 Watt Pre-prog. 34/76-94/94 \$55; Dumont 10 Watt 34/76-94/94 \$40, both with transistorized power supply. GE 25 Watt Pre-prog 2 channel \$65. W8MVZ 20088 Center Ridge, Cleveland OH 44116.

ELECTRONIC ORGAN full spinet, transistorized, two manual. SASE for particulars. Lloyd G. Hanson W9YCB, RR2, Box 52A, Angola IN 46703.

"NIXIE" type readout tubes (w/internal decimal point) \$2.90; 7441A drivers \$2.50; 7490 counters \$1.75; 7475 latch \$1.50; good selection 7400 series gates \$0.35, dual flipflops \$0.90. DIP/IC sockets \$0.17. Everything brand new. SSAE for details, lists and application info. W1DMU, Box 1, Corinth VT 05039.

HAMFEST: INDIANA RADIO CLUB COUNCIL'S annual picnic Sunday, July 11th, LaPorte County Fairgrounds, LaPorte, Indiana. Large Flea Market with reserved locations available for large exhibitors and vendors on the Midway and Main Building. Mobile FM Clinic. Prizes. Tech Sessions. For flyer write: Dave Osborn, K9BPV, P.O. Box 272, LaPorte IN 46350.

UNUSUAL RECEIVER VALUES: Collins 7551 \$295; Collins 7553 \$395; Hammarlund HQ170 \$159; Hammarlund HQ170A/VHF \$199; Hammarlund HQ180AC \$299; National NC300 \$119; Many More. Get Complete Listing. Stan Burghardt WØIT, Box 73, Watertown SD 57201.

HOOSIER ELECTRONICS Authorized dealers for Drake, Hy-Gain, Ten-Tec, Galaxy, Regency. All equipment new and fully guaranteed. Write today for our low quote. Hoosier Electronics, Dept. D, R.R. 25, Box 403, Terre Haute IN 47802.

"1971 TESTS-ANSWERS" For FCC First and Second Class License, plus "Self-Study Ability Test." Proven! \$9.95. Satisfaction guaranteed. Command. Box 26348-S, San Francisco CA 94126.

WARREN AREA 14th HAMFEST - still the friendliest. Sunday, Aug. 27, new site: Yankee Lake, on Ohio Rt. 7, five miles north I-80. Picnic, swimming, playground. Prizes, displays, giant free flea market. For Details & map, send card: Hamfest, Box 809, Warren OH 44480.

RADIO BOOKSHOP BIG DEALS

BOOKS!

ADVANCED CLASS STUDY GUIDE Up-to-the-minute simplified theory, written with the beginning radio amateur in mind. This unique book covers all aspects of the theory exam for the Advanced Class license and has helped hundreds of hams to sail through the exam... nothing else like it in print! 1001 \$3.95
1001H *Hardbound* \$6.95

EXTRA CLASS LICENSE STUDY COURSE BOOK The Extra Class License Study Guide is now available in book form as a permanent addition to your radio library. This is the complete course that was published in 73, covering every technical phase of the new license exams for this highest class of amateur license. This also covers, in the easiest-to-understand form, just about every technical question likely to be asked on the First Class Radiotelephone exam. This is the first study course ever published that is written so the newcomer to radio can understand it. With this book you can face the FCC exams knowing that you understand the theory and with no fear of rewritten questions. 1002 *ppd USA* \$4.95

VHF ANTENNAS This handbook is a complete collection of up-to-date information about VHF and UHF antennas, with design hints, construction and theory. If you've been wondering what array you need, this book will give you enough background to make the right decision. 1003 \$3

COAX HANDBOOK Invaluable book for the ham or the lab and for everyone else who doesn't want to have to keep a whole library on hand for reference... or even worse, have to write to the manufacturer for coax spec. 1005 \$3

73 USEFUL TRANSISTOR CIRCUITS If you've been looking for a transistor circuit to do a special job, chances are there is a circuit in this book that will give you a head start. It covers circuits for audio, receivers, transmitters and test equipment. 1006 \$1

SIMPLIFIED MATH Does math scare you? It shouldn't. This easy-to-understand book explains the simplified exponential system of arithmetic, simple formulas, logarithms, and their application to the ham shack. 1007 \$5.00



1004




1006

AMATEUR TEST AND MEASUREMENTS By W5REZ. Using VOM, Scope VTVM, dipper, SWR bridges, etc. Covers amateur users of test equipment in the ham station. 208 pages, softbound. Interestingly written, covers tuning receivers, all kinds of transmitters, etc. Invaluable for every hamshack. 1012 \$5.50

ELECTRONICS FOR THE AMATEUR By W5REZ. Hardbound book, 272 pages. Covers entire theory needed for passing amateur licenses. Fine book for instructors, and for amateurs wanting a refresher course before exposing themselves to the FCC examiners. Hardbook books look nice and last. 1013 \$7.95

NCX-1000

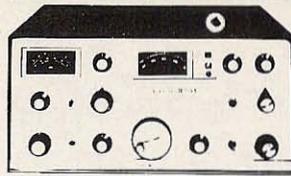

NATIONAL NCX-1000 TRANSCEIVER Transistorized transceiver (except for driver and final) runs 1000 watts, yet is just a bit larger than ordinary transceiver! Complete kilowatt ham station in one small, light unit. Tested by 73 staff and found to be a really great unit. The world of transistors and ICs makes it possible to have a complete kilowatt all band ham station in one small unit! Not much larger than normal transceiver yet runs solid 1000 watts. Extremely sensitive, processed speech for maximum umphs when wanted, everything you need in one little package. Only tubes are driver and final. The NCX-1000 lists for \$1100 and is an unusual bargain at that price. The 73 test unit, used a few days and under brand new factory warranty, is available to the first \$700 check received.

GR 1105

G.R. FREQUENCY MEASURING EQUIPMENT TYPE 1105A This primary frequency standard will measure from 1 Hz to over 100 MHz with an accuracy of one cycle up to 10 MHz. This is a laboratory standard used primarily for calibrating other equipment. This is the last word in frequency standards. Send for details. Special \$ 995

W2NSD/1

MAGNETIC CAR SIGNS Put this easy-to-read magnetic call sign on your car when you are on a trip and meet the hams along the way. Comes right off when the XYL drives the car, if she doesn't want to be bothered by hams tooting at her. Send \$4 along with your call letters today! 1201 \$4

LAPEL BADGES Name and call identifies you at club meetings, hamfests, busted pot parties. Hand engraved by skilled New Hampshire craftsman with loving care. Only one lousy dollar. Send first name and call. 1202 \$1



A HAMSHACK WITHOUT A GLOBE? RIDICULOUS! Particularly when these fabulous Hammond globes (the best in the biz) are available at our low, low price! 13" inflatable globe (guaranteed, by the way) regularly selling for \$15, now special, while they last. 1208 *only \$10*
13" lighted inflatable globe, regularly \$25 now
1209 *only \$15*
We have a few of these in stock and when they are gone, that's it!

DX STUFF

CUSTOM MADE DX CHARTS When you need a DX bearing you need it immediately. You don't want to have to look it up on a map or fiddle with a globe. These Custom DX Charts are computer printouts for your exact shack location and give the bearing and mileage for every country in the world. They are printed out by call prefix for speed of location and the capital city is indicated. *Custom DX Chart, 1206ppd \$4*



FABULOUS DX MAP OF THE WORLD Show visitors DX you've worked. Wall sized (29" x 31"); shipped flat in mailing tube; suitable for framing; most complete map available; up-to-date world prefixes shown; color in countries as worked; shows islands, reefs, rare DX spots; use colored map pins for different bands. 1207 \$1

DX HANDBOOK Includes giant world country-zone wall map. Articles on QSL design secrets, winning DX contests, DXCC rules, DXpeditions, reciprocal licensing and many more. World postage rates, WAZ record lists, time charts, propagation, etc. Special ham maps and bearing charts. A must for the DXer. 1021 \$3

DIODE CIRCUITS HANDBOOK An invaluable reference book. Covers rectifiers, mixers, detectors, modulators, FM detectors, noise limiters, AGC, BFO/Q-multiplier, AFC, Vari-cap tuning audio clippers, balanced mods, fieldstrength meters, RF probes, zeners, control circuits, etc. 111 different circuits.

1004 \$1

"TRANSISTOR PROJECTS FOR THE AMATEUR" A collection of 73's most popular ham projects, selected by you, the readers, and edited by Paul Franon (Mr. Semiconductor himself). This has got to be the best, most authoritative, most universally appealing collection of up-to-date circuits ever published.

1010 \$3

FM BOOKS

FM ANTHOLOGY Vol. 1. This book is largely a collection from FM Bulletin, edited by K67MVH and WA8UTB. The material is taken from the editions of February 1967 through February 1968.

1009 \$3

FM REPEATER HANDBOOK K6MVH. Book is required for all repeater operators and must reading for all FM'ers. Only complete book on the subject. It is also one of the best selling books in amateur radio today.

1010 Hardbound \$6.95

"THE BEST OF FM" A huge selection of FM Journal's finest technical and conversion articles, never before reprinted in any other magazine. The concluding segments of those controversial "CHRONICLES"! Selected FM editorials to show a broad view of the problems faced by FM'ers. This book comprises Volume II of the FM anthology, and includes an "Editor's Choice" selection of topflight articles from FM Journal, from March 1968 to May 1969.

1011 \$4.95



1019



1010

EDITORS & ENGINEERS RADIO HANDBOOK Hardbound. Latest (18th edition) by W6SAI. This is the most complete ham handbook ever published. Makes all other handbooks look like comic books. 896 pages.

1018 \$13.50

EDITORS & ENGINEERS RADIO HANDBOOK Hardbound. W6SAI (17th edition) reduced for clearance, limited supply available for fast acting amateurs. Last chance to get this great book before it is gone forever.

1019 \$10

ELECTRONICS REFERENCE HANDBOOK Hardbound. W6TYH handbook of basics and circuits. Complete analysis of all ssb equipment.

1015 \$6.95

HOW TO FIX TRANSISTOR RADIOS & PRINTED CIRCUITS. Do you throw those little radios away when they stop? Wasted money! Easy to fix with this manual. Worth many times the low price. No serviceman or amateur should be without this tremendous book.

1016 \$7.95

SCHEMATICS AVAILABLE

\$1 each.

1101. ARR-15 from June

1965 73, page 78.

1102. ARC-27 2M Guard

Channel Receiver.

1103. SSB Transceiver, Nov.

1961 73 Page 23.

Buy lavishly! Order today from:
RADIO BOOKSHOP
Peterborough NH 03458

GUNSMOKE

GUNSMOKE? Blow your mind on our back issue bargain bunch, 30 (count 'em) assorted (we hope) back issues, all before 1968, for the incredibly low price of \$6 postpaid (hardly pays for the postage). These are packed by slave labor (to cut costs) so please ignore notes calling for help, etc., that may be slipped into the bundles.

1204 \$6

SPECIAL! RARE BACK ISSUES The back issue of 73 you need to complete your full set—or that has the continued article you only read the end of—can be yours for a mere pittance! Most issues are in stock and are available for \$1 each. The exceptions that prove the rule are listed below:

Dec.68, Nov.69, Feb.70, Oct.

70. \$2

Jan.65, Apr.65, Jan.66, Jan.

67. \$3

Jan.61, Dec.63, Jun.66, Jul.

66. \$100

73 BINDERS



BUY BINDERS FOR YOUR 73 and win the love of a beautiful girl. Gorgeous red binders look great on your shelves and also keep the magazines from disappearing or breaking. Come with set of year stickers. Get enough binders to protect all those back issues too.

1205 \$4

DESK PLATE

DESK CALL PLATE Up to 20 letters on a desk plate, embossed white letters on walnut background; ebony stand. Looks great on rig with your name and call. Watch envy race through your neighborhood. Send along 20 well chosen letters (spaces count as letters too), include a nice fresh two dollar bill, and give us a strong hint on where to mail the exquisite piece of craftsmanship.

1203 \$2

Latest Edition—POPULAR TUBE & TRANSISTOR SUBSTITUTION GUIDE Brand-new updated and revised edition! The most needed substitution data for both tubes and transistors all in one handy brand-new volume! No longer do you have to refer to one substitution manual for tubes and another for transistors—everything is here in one quick-reference guide. Lists 99% of the tubes and transistors you'll ever need to replace. Moreover, only readily-available and comparably-priced substitutes are listed. No longer do you have to search through lists of tubes and transistors you'll rarely see in use, or search through pages of irrelevant material to find a substitute. Why buy a \$10 switching transistor when a 89¢ popular type will do the job better? Contains 8 big sections—four devoted to tubes and four to transistors; Popular Receiving Tubes, Industrial and Commercial Tubes, American Substitutes for Foreign Tubes, Tube Base Diagrams, Popular Transistors, American Substitutes for Foreign Transistors, General Purpose Transistor Substitutes, Transistor Base Diagrams and Manufacturer Abbreviations. You'll find this guide to be one of the most practical everyday aids you've ever used. 224 pps., 8 Sections.

1210 only \$2 ppd.

1022 Softbound \$2.95

1023 Vinyl Cover \$4.95

WORLD'S FINEST LOG BOOK? Designed and executed by W2NSD/1, this is the most relevant amateur radio log ever designed. This is a log for today. It has a column for the date, one for time and off of each contact, a small column to indicate whether you called the station contacted (or CQ) or not, a good wide space for the station call contacted, little columns for the reports, a good space for his location, a QSL column, and lots of room for notes. The log is the long way on standard 8 1/2" x 11" paper and padded into pads of 125 sheets, with room for 20 contacts per page. The whole book of log sheets will carry you through 2500 contacts. There is a place to indicate on each sheet the band being used and the power in case these change now and then. The log pages can be numbered for file card reference. Why use a log book designed in the 1920's? This one was designed for use in the 70's and is exactly right for the DX'er, and rag chews, or even the round-table denizen. It will work for RTTY, ATV or even slow scan television. Never has a log been made available which is as handy as this gem. Why keep struggling with those ring binders which get all bent out of shape? Get this first really modern log.

1210 only \$2 ppd.

RADIO BOOKSHOP

All books and items postpaid in U.S.A. unless otherwise indicated. Send cash, check, money order, etc., to:

Buy lavishly! Order today from:
RADIO BOOKSHOP
Peterborough NH 03458

An IC Audio Processor

John J. Schultz W2EY
1829 Cornelia Street
Brooklyn NY 11227

To write about another type of speech compressor and still, yet, to call it an "ultimate" type may seem a bit overdone at a time when speech compressor circuits of every variety are commonplace. But the unit to be described is by no means just another garden-variety speech compressor.

The phrase "audio processor" as used in the title, may, on the other hand, seem a bit nondefinitive, but it has been used to indicate that the unit provides a far more useful function than just speech compression alone. In fact, it is meant to convey the idea that it has processed a speech waveform on an af basis to such a degree that the waveform is the best possible to be fed to a transmitter for full modulation.

The unit makes use of two ICs — an SL630 amplifier and an SL620* automatic gain control unit. The two ICs were designed to mate together for a speech processing function and, therefore, should be used together even if one is tempted to replace the relatively simple amplifier IC by another type of IC.

The complete schematic of the unit is shown in Fig. 1. The unit is designed for both a low impedance input and output and a matching transformer is necessary for use with a high-impedance microphone. Usually, no transformer is needed on the output even if it is connected to a high-impedance audio input on a transmitter because of the amplitude of the output voltage. The input provides either for a


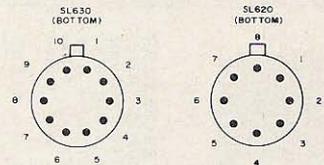


Fig. 1. Complete schematic of the IC audio processor.

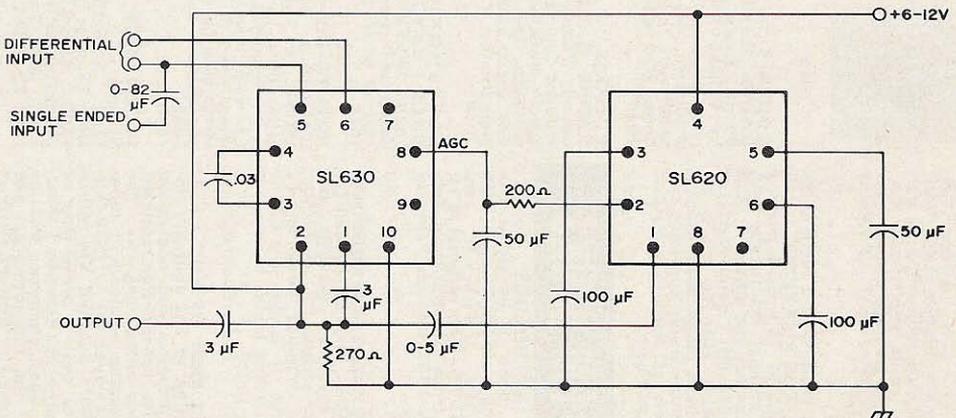

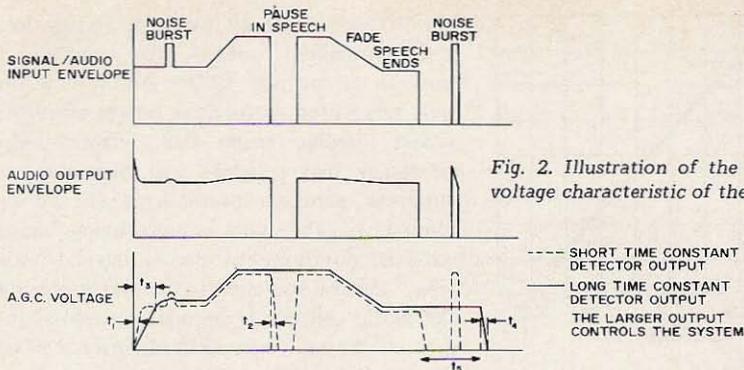


Fig. 2. Illustration of the input/output and agc voltage characteristic of the processor.

balanced or an unbalanced type of microphone input. The former can be quite useful since by having both microphone leads ungrounded, many problems with noise pickup, rf pickup, etc. on the microphone leads are automatically avoided. If the usual type of unbalanced input is used, however, it is connected to pin 5 of the SL630 via a 1 μ F capacitor. Pin 6 is then left unconnected. The capacitor between pins 3 and 4 of the SL630 provides a high-frequency rolloff characteristic. The values shown provide a rolloff starting at 3 kHz, but this can be changed, if desired, by experimenting with the capacitor value.

The output is taken from pin 1 of the SL630 via the two 3 μ F coupling capacitors. Part of this output is coupled to pin 1 of the SL620 IC via the 0.5 μ F capacitor. The SL620 IC uses this voltage to generate an agc voltage which is eventually available at pin 2 of the SL620. From there it is coupled to pin 8 of the SL630 to control the gain of the latter IC. What these two little ICs can accomplish is shown nicely by Fig. 2. The upper curve shows a varying speech input, while the second curve shows how the audio output appears after processing. Notice that when the speech input either rises rapidly or falls rapidly the output remains essentially constant. Noise bursts, because of their much shorter time duration, are recognized separately by the unit. The noise burst shown occurring during speech, although much higher in amplitude than the speech level, produces practically no increase in output. An automatic squelch feature is also provided.

When there is a pause in speech, the output is disabled to prevent the background noise buildup common to most simple compressors. The pause time before the output is disabled is about 1 second and can be changed, if desired, by varying the value of the capacitor from pin 6 of the SL620 to ground.

The control range of the unit is illustrated by Fig. 3. Only a very slight change in agc voltage is necessary to control the output over a 60 dB range. In practice, the input can change over a 35 dB range and the output level will remain between 70 and 87 mV.

Construction

The photograph shows how the author constructed a unit on perforated board stock. The parts layout is in no way critical and is just a matter of convenience. The photograph of the underside of the board is just shown to illustrate how easily the unit could be adapted for etched PC board construction as a club project since only one wire crossover is necessary and even that can probably be eliminated by experimenting with the parts layout.

The units will operate equally well with a 6 or 12V dc supply and draw up to about 15 mA. The operating voltage can be borrowed from a well filtered point in a transmitter or a battery supply used. In the latter case, a usual 9V battery is ideal to use. There are no controls to the unit and so it may be housed easily inside a transmitter, avoiding only any location near high rf fields.

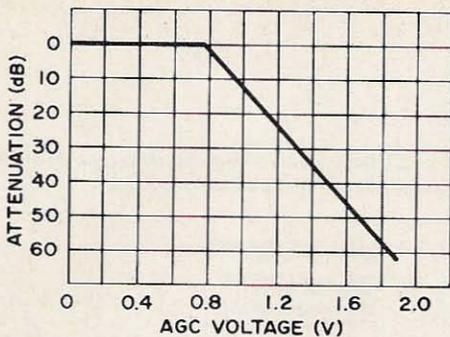


Fig. 3. Control range of the unit exceeds 60 dB. The graph illustrates the control of the input signal by the SL630 with agc voltage supplied by the SL620.

Operating Results

I compared operation of the unit to several types of conventional audio compressors. In every case, the unit described exhibited a much smoother compression action without pops, clicks, etc. It simply sounded more like the type of quality speech processing found on commercial circuits rather than the usual harsh, noisy compressor type action, which usually has to be disabled for local contacts because the inherent distortion then becomes so noticeable. The squelch and noise immunity features added also a great deal to the cleanliness of the speech output and should be particularly useful in a mobile type situation where a great deal of extraneous background noise can exist.

The IC Internals

The circuitry of the SL630 audio amplifier is not too different from that of many IC audio amplifiers, except that it includes provision for agc control of its output over a wide range. The input is coupled to a differential amplifier directly without the use of coupling capacitors for a balanced input. The agc voltage (pin 8) controls the emitter current flow return for the differential amplifier via the transistor whose base goes to pin 8 and a 3.6 k Ω resistor. The 750 Ω resistor between base and collector acts as a "linearizing" element to give the smooth control range shown in Fig. 3. The rest of the unit continues to provide


amplification (40 dB overall), ending in a series-connected output pair, which can provide an output up to 250 mW if the unit were used as solely a power amplifier device. Unlike many ICS, however, the necessary bias resistors and capacitors to suppress parasitic oscillations are all included in the unit, thus saving many external components. Pin 7, marked "muting," can be switched to ground to disable the audio output. If manual control of the gain of the unit were desired (instead of by the SL620 unit), a potentiometer can be connected between pins 9 and 2 with the wiper arm going to pin 8.

The circuitry of the SL620 unit, on the other hand, is quite different than most ICs because of its specialized functions. T1 through T4 are the input af amplifiers. The af output is coupled to a dc output amplifier (T16-T19) by means of two detectors (T14 and T15). T14 in conjunction with C1 has a short rise and fall time constant. T15 in conjunction with C2 has a long rise and fall time constant. Thus, any input signal will rapidly initiate agc action via T14 (in 20 ms), but after a longer time (200 ms) T15 takes over to control the agc. The effect is rapid initial agc response but not false agc response to sudden peaks after the speech input has started. T6-T8 form a trigger circuit which detects sudden peak inputs above 4 mV, such as noise bursts. When such a burst occurs during a pause in input it prevents via T10 and T13 the output from being turned on.

T9 in conjunction with C3 forms a sort of memory circuit having a time constant of about 1 second. So long as a speech input is present, it does not act but during a pause exceeding one second, C3 discharges to turn on T12 via T11 and turn off the audio output of the SL630/SL620 combination. The capacitors mentioned above for the various time constants, C1, C2, and C3, are external to the IC and their value can be experimentally changed to suit individual preferences. W2EY■

**If units are not available locally, write to Plessey Microelectronics, 170 Finn Street, Farmingdale, L.I., NY for location of nearest distributor.*

Brand new
 from
 Henry

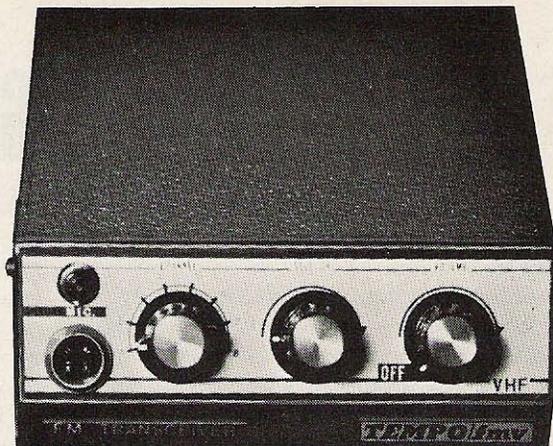

TEMPO-fmv

FM-V PERFORMANCE SPECIFICATIONS

setting
 new highs in
 performance
 and value!

\$249.00

Microphone included

OVERALL

Frequency Range: 146-148 MHz
 No. Channels: 8
 Power Supply Requirements:
 12-15 VDC at 2A

Dimensions:

2.36 in. high
 5.9 in. wide
 7.66 in. deep

Weight: 4.5 lb

Active Devices:

Transistors - 26
 Integrated Circuits - 2
 Diodes - 15

RECEIVER

I-Fs:
 First - 10.7 MHz
 Second - 455 kHz

Freq. Stability:

$f_o \times 0.00001$

Sensitivity:

For 20 dB quieting - 0.6 μ V
 Usable threshold - 0.3 μ V

Selectivity (at full quieting):

-6 dB at ± 6 kHz
 -70 dB at ± 15 kHz

Audio out:

1.0W

TRANSMITTER

RF output: 12W
 Multiplication factor: 12
 Spurious:
 Better than -60 dB

Freq. stability:

$f_o \times 0.00001$

Deviation:

Adjustable, 5-15 kHz

EXTRA FEATURES

● METERING TEST SOCKET

A built-in test socket can be used with any 50-100 μ A meter to monitor all transmitter and receiver stages, including DISCRIMINATOR (for zeroing to frequency).

● OPERATION/MAINTENANCE MANUAL

A large manual includes photos and schematics as well as complete instructions for checkout, adjustment, and alignment of the transceiver.

● OPTIONAL TEST SET ACCESSORY

An attractive test set is available as an optional add-on accessory. The test set mates with the built-in test socket, and includes a sensitive microammeter that can be switched to monitor transmitter oscillator, multiplier and driver stages as well as first and second local oscillator stages of the receiver and discriminator current. **\$29.00**

● STANDARD HENRY WARRANTY

The FM-V is backed by Henry's standard warranty that is your assurance of excellence in quality of equipment, both mechanical and electrical.

★ Tempo is proud to announce the development of a complete line of the world's most advanced amateur two meter FM equipment.
 ★ In addition to the Tempo-fmv we now offer
 ★ the fmp, a superb 3 watt portable transceiver,

the fma 25 watt transceiver and an advanced design two meter amplifier line in the 45 to 100 watt range. Available at Henry Radio and other select dealers. Write or watch for more detailed information. ★

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064

213/477-6701

931 N. Euclid, Anaheim, Calif. 92801 714/772-9200

Butler, Missouri 64730

816/679-3127

The Tempo/fmv is also available at other selected distributors in different areas of the U.S. Or you can order direct and we will ship... across the street or around the world. Call or write for specifications and terms.

"World's Largest Distributor of Amateur Radio Equipment"

AUDIO SIGNAL GENERATOR

An audio signal generator is a handy item when checking audio gear, and an af oscillator is a lot more consistent than whistling into the mike — especially if you're snacking on peanut butter sandwiches. The oscillator described here is the answer. It's inexpensive, simple, and can operate from subaudio to rf.

The oscillator basically is a modified Wien bridge using complementary FET and bipolar transistors. Analysis of the Wien bridge of Fig. 1 shows the bridge is balanced when

$$f = \frac{1}{2\pi\sqrt{R_1R_2C_1C_2}} \text{ and } C_2/C_1 = R_3/r - R_1/R_2.$$

When $C_1 = C_2$ and $R_1 = R_2$ and the frequency is such that $R = X_C$, the imped-

$$\text{ance } Z_2 = \frac{R}{\sqrt{2}} \angle -45^\circ \text{ and } Z_1 = R \sqrt{2} \angle 45^\circ.$$

Consequently, a third of the voltage applied to the bridge between points A and D appears across Z_2 . When $R_3 = 2r$, one third of the voltage applied to the bridge appears across r , so there is no difference of potential between points B and C, and the bridge is balanced.

In the actual oscillator shown in Fig. 2, R_4 and R_5 in parallel make the resistance r of Fig. 1 for ac. The reactance of C_3 must be less than 10Ω at the frequency of oscillation. R_5 is the resistance of a 6W 120V lamp whose positive temperature coefficient regulates the output of the oscillator and insures that signals within the oscillator are not clipped or limited.

A typical 6W 120V lamp has a resistance of 200Ω when the voltage across it is 0.1V rms, and about 550Ω when the voltage is 3V rms. A good operating point is about 0.5V, or a resistance of about 300Ω . The actual operating point is determined by R_3 and the particular lamp's characteristics. The larger R_3 , the higher the lamp operating voltage.

R_3 is chosen to be slightly greater than twice the lamp's resistance when the voltage across the lamp is about 0.5V rms, and a value of 680 is about right. Initially, then, the bridge is unbalanced, and oscillations will start when power is applied. The ac voltage across the lamp increases the lamp resistance and brings the bridge toward balance. The bridge is brought to the balance point, which produces a bridge attenuation exactly equal to the amplifier's gain. The attenuation, the ratio of applied voltage (A to D) to output voltage (B to C), is infinite at true balance, and an infinity-gain amplifier would be required. Therefore, the oscillator must operate with some unbalance.

The match of R_1 and R_2 and C_1 and C_2 is very important and, although the circuit given can handle 5% tolerance components, a closer match is desired so that greater variations in lamp, amplifier gain, and loading can be tolerated. Loads heavier than $1\text{ k}\Omega$ can best be accommodated by adding an emitter-follower buffer on the output of the oscillator.

Matching C_1 and C_2 can present an interesting problem if you don't have access to a good bridge. The technique I used was slow, but it was a starting point. First, I matched a pair of resistors in the

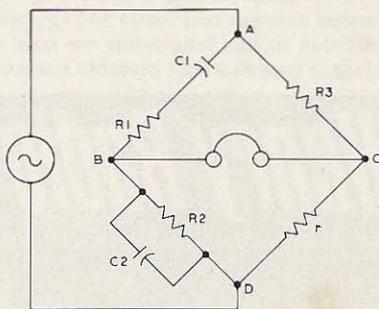


Fig. 1. The basic Wien bridge.

EXTEND YOUR COUNTER or RECEIVER up to 500 MHz with our DIVIDE-BY-TEN FREQUENCY SCALERS

Size:
5-3/4" x
4" x 2"



MAX. FREQ.	MODEL	PRICE
100 MHz	FS-100	\$ 99.50 ppd.
160 MHz	FS-160	\$129.50 ppd.
200 MHz	FS-200	\$149.50 ppd.
350 MHz	FS-350	\$249.50 ppd.
500 MHz	FS-500	\$349.50 ppd.

NOTE: Most units exceed max. frequency by 5-10%.

- Divides-by-ten using ultra-high speed binary circuits. Requires no tuning or adjustments.
- Accuracy is absolute and is determined solely by your frequency counter or radio receiver.
- Two or more units can be cascaded for division by 100, 1,000, 10,000 etc.
- Scaling is synchronized with input and does not depend on a time base.
- Built-in wide band amplifier boosts sensitivity to better than 20 mv. Amplifier can be used alone to increase your counter's sensitivity or as a receiver pre-amp up to 500 MHz. 50 ohms input and output.
- Contains a precision regulated power supply to assure trouble-free operation regardless of line voltage fluctuations. Operates from 100-130 v, 50-100 Hz, or 8-16 v.D.C.
- Ideal for use in frequency synthesizers. Divides VHF oscillators down to a range easily handled by phase-locked loops.
- Can be used with radio receivers as well as counters. Example: You can read a 146 MHz signal at 14.6 MHz on your receiver without using a converter. If your receiver is accurately calibrated you can save the cost of a frequency counter and measure frequencies up to 500 MHz directly on your receiver dial by using one or more scalars.
- High quality construction with top brand components, glass-epoxy circuit board, all IC's mounted in sockets, heavy gauge aluminum case, schematic, tested and guaranteed.

HOW TO ORDER: Mail your order direct to our factory in Hollis N.Y. Include remittance in full plus sales tax if you reside in N.Y. State. Orders may be picked up at our factory if you phone in advance and bring cash. Open from 9 A.M. to 4:30 P.M. Monday thru Friday except holidays.

VANGUARD LABS Dept. H 196-23 Jamaica Ave. Hollis NY 11423

Freq. kHz	C1, C2 μ F	R1, R2, k Ω
.250	.01	63.4
.400	.01	39.2
1.0	.01	15.8
1.8	.001	88.7
2.5	.001	63.4
10	.001	15.8

range of 270 k Ω with an ohmmeter and used them in the bridge shown in Fig. 3 to match the .01 μ F capacitors. At the start, you won't know which of the capacitors is smaller, so shunt one of them and note whether the balance improves. Add to the one that improves the null, and try to balance within 2%. In matching the .001 μ F, the bridge resistors should be in the order of 2.7 M Ω and a VTVM is essential for detecting the null.

Values of R1 and R2 between 2 k Ω and 1 M Ω and values of C1 and C2 above 470 pF are convenient. Within these bounds, these combinations are available:

The same general circuit approach can be used to make a wide-range variable frequency oscillator. In the variable oscillator, fixed resistors R1 and R2 are replaced with sections of a dual pot. If the tracking of the pot sections is within 5%, the circuit could be used directly, and a 100:1 tuning range could be achieved, but it isn't very likely that you will find such close tracking.

There are two possible solutions to the difficulty. One reduces the tuning range by adding fixed resistance in series with the variable resistances to reduce the percent-

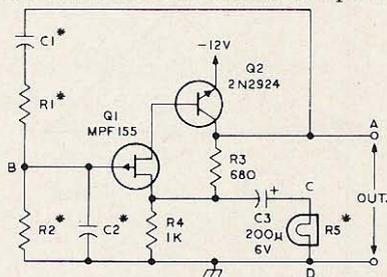


Fig. 2. Fixed frequency oscillator. All resistors 10% $\frac{1}{4}$ W. *See text for values and tolerance.

age tracking error, and the other increases the gain of the amplifier so the unavoidable unbalance can be tolerated. In the oscillator shown in Fig. 4, both solutions are used. R_{ab} adds about 2.5 k Ω in series with each of the 100 k Ω pot sections and reduces the tuning range, and Q3 makes a higher voltage gain possible from Q2. The oscillator tunes from about 150 Hz to 6 kHz for the values given.

The pot R_{ab} is adjusted to minimize the percentage difference between $R_1 + R_a$ and $R_2 + R_b$ as the dual pot is rotated fully clockwise. The power supply for the oscillator is not critical, and any voltage from 12–24V will do for the fixed-frequency oscillator, but the variable frequency oscillator should have a supply above 18V. The current required for the fixed oscillator is about 5 mA without a buffer, and the variable oscillator requires about 18 mA.

The layout of the oscillator is not particularly critical for audio frequencies, but care should be taken to shield the high-impedance sections from power-line pickup. If an external power supply or batteries are used, the normal enclosure will be sufficient. The variable oscillator of Fig. 4 will fit in a minibox if an external power supply is used. The heft will be improved if you bolt a chunk of scrap steel into the bottom of the box.

If you prefer, you can change the polarity of the unit by making these direct substitutions: MPF 155 to MPF 104; 2N2925 to MPF 6518; 2N3638 to 2N2923. Don't forget to change the polarity of the electrolytics. The heavy negative

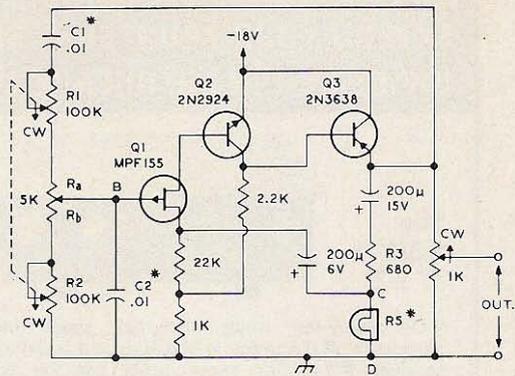


Fig. 4. Variable frequency oscillator. All resistors 10% 1/4W. *See text for tolerance.

feedback makes the circuit very tolerable of component variations, but the following table of DC voltages may be comforting when you turn the oscillator on for the first time:

Fixed Osc.	Emitter (Source)	Base (Gate)	Collector (Drain)
Q1	-4.5	0	-11.4
Q2	-12V	11.4	-7.5
Var. Osc.	Emitter (Source)	Base (Gate)	Collector (Drain)
Q1	-4.5	0	-17.4
Q2	-18.	-17.4	-14.4
Q3	-18.8	-14.4	-18

An evening or two and a few bucks for parts are all that are needed to build the oscillator. If your junkbox is like mine, full of everything except what you need, it will cost you under \$6 to buy all new parts for the fixed oscillator. A pair of these little gems operating at 400 Hz and 1.8 kHz are ideal for generating the signals for adjusting the SSB rig, and you can enjoy your peanut butter sandwich too. . . .W3SGV■

Reference:

Edson, William A: Vacuum-Tube Oscillators, New York, John Wiley & Sons, Inc., pp. 128, 138 to 142, 1953.

Terman, Frederick Emmons, Sc.D: Measurements in Radio Engineering, 1st ed., New York, McGraw-Hill Book Co., Inc., pp. 46, 47, 1935.

The MPF155 (\$1.30), 2N2924/HEP 724 (95¢), and 2N3638 (50¢) are available from: Circuit Specialists Co., Box 3047, Scottsdale AZ 85257. Please include 25¢ for shipping.


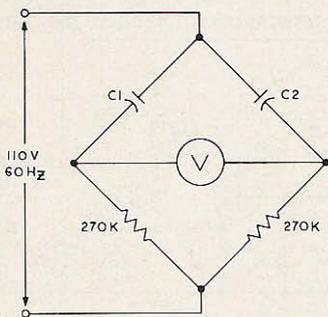


Fig. 3. Capacitor comparison bridge.

NCX-1000

THE 1000 WATT TRANSCEIVER of the 70'S

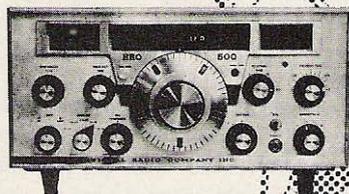

HRO-500 \$1995.00



NCX-1000 \$899.00




HRO-600/601 \$3380.00

- 5 BANDS
- 4 MODES
- SOLID STATE DESIGN

89 WASHINGTON STREET, MELROSE, MASSACHUSETTS 02176
TEL: 617-662-7700

TWX: 617-665-5032

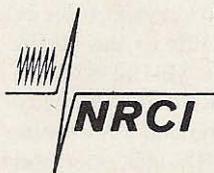

Write for Specifications!

Excellence in Communications Since 1914

NATIONAL RADIO CO., INC.

questions questions questions

Herbert S. Brier W9EGQ
385 Johnson Street
Gary IN 46402

We do not normally devote as much space to answer one question as we give to our first question this month. But telling anyone how to protect himself and his visitors from the dangers of uncontrolled electrical currents is important enough to command additional space.

I am almost afraid to touch two pieces of equipment in my electronics shack at the same time, because doing so is almost like playing Russian Roulette. One time, I get a nasty shock; the next time, nothing. And when I disconnect or connect an antenna or piece of equipment, sparks often fly, even though all power switches are shut off. Are these things dangerous? How do I correct the trouble? Yes. The conditions you outline are dangerous. Almost any electrical shock can kill under the proper circumstances. Fortunately, however, eliminating the hazards is not difficult. The basic problem is that the primary circuits of virtually all electronic devices operated from the commercial power lines are bypassed to their metal chassis and cabinets through capacitors. Consequently, the cabinets are effectively coupled to the power line via the bypass capacitors. If the cabinets are grounded, however, the resulting alternating currents are harmlessly drained off into the ground. But if the ground is omitted, and you simultaneously touch a cabinet and a grounded object, your body becomes the ground path. Depending on the capacitance of the bypass capacitor and whether it is leaky or shorted, the result may be a slight tingle or a truly shocking experience. The sparking that occurs when you connect your antenna to your equipment is a probable indication that the antenna is grounded somewhere either by design or by accident. Conversely, many a technician has had his teeth loosened by a shock while working on an ungrounded antenna left connected

to a receiver, transmitter, or transceiver. Incidentally, an actual ground connection is not needed to get a shock between two pieces of electronic equipment. Suppose that only one side of the power line is bypassed to the chassis in either unit (a common condition), depending on how the power plugs are inserted into the ac power sockets, one bypass capacitor may be on the "hot" side of the power line, and the other capacitor may be on the "ground" side of the line. As a result, there will be a voltage difference between the cabinets of the two units.

To solve the problem, connect all metal cabinets to a low-resistance ground with heavy flexible wire. The best ground for this purpose is the ground post used by the utility company in your home. In addition to the ground straps, always make certain that the equipment is completely disconnected from the power lines before connecting or disconnecting anything (including grounds) from it. Usually the easiest way to insure this is to pull the power plug from the power socket. The worst way is to depend on the power switch in the unit.

Can I change the crystal filter in my Heathkit HW-100, amateur SSB transceiver to the Heathkit SSB crystal filter? If possible, what would I gain from the exchange? The filters are interchangeable. In fact, if you purchase a new Heathkit HW-100 kit and return its crystal filter in its unopened box with \$20 to the Heath Company, and order the SB-102 SSB filter — part number 404-283 — the company will ship you the new filter and a few cents change. Replacing the HW-100, 4-crystal filter in the HW-100 with the SB-102, 6-crystal, SSB filter makes the HW-100 SSB selectivity equal to the SB-102 SSB selectivity. An SB-102 filter without a trade-in costs \$37, by the way.

I acquired a bargain bag of transistors, some good and some bad. How can I weed out the bad ones without a transistor tester? An ohmmeter that develops no more than 1.5V across its open test leads and allows a maximum of 1.0 milliamperes to flow between the test leads when they are shorted together will identify open and shorted transistors, but higher voltage or current may damage a delicate, low-power transistor. The procedure: Measure the resistance between the transistor base and collector; then reverse the ohmmeter test leads and repeat the measurement. Note the difference between the two readings. Next, make a similar pair of measurements between the transistor base and emitter. If either pair of readings show a very low meter reading that does not vary when the ohmmeter test leads are reversed, that junction is shorted. Conversely, if the reading is high and unchanging, the junction is open. In either event, the transistor is defective. But if there is a difference between the readings in each pair, the chances are good that the transistor is usable. Some power transistors, especially

germanium types, may show fairly low leakage resistances; but, as long as there is a perceptible difference in readings when the ohmmeter leads are reversed, the transistor should be usable. Do not leave the ohmmeter connected to the transistor any longer than necessary to obtain a meter reading.

My old, old shortwave receiver from the Goodwill shop brings in the stronger overseas shortwave broadcast stations, but it is not sensitive enough to bring in the weaker ones clearly. Is there any attachment I could get to bring in these weaker signals? A preamplifier between the antenna and the receiver antenna terminal should amplify weak signals three or four S-units. If you don't want to build your own preamplifier, look up the AMECO PCL-P, all-band preamp.

Your questions will be answered here to the limit of the space available. Send them to: Questions, 73 Magazine, P.O. Box 678, Gary IN 46401.

...W9EGQ■

Dipper Thing

Walt Pinner WB4MYL
7304 Lorenzo Ln.
Louisville KY 40228

Have you ever wished your grid dip meter were more accurate at higher frequencies or had the capability of going lower in frequency than the 3 MHz range that seems to be so popular on most units?

For some time I have been using a simple detector lead in conjunction with an rf generator for grid dip purposes. The probe is inexpensive and easy to construct and use. It utilizes an inexpensive movement which is available from most mail order houses under the title of "light meter movement." The cost is usually about a buck and a half and is typically a 45 μ A (basic sensitivity) meter. The sensitivity is not critical; however, something in this range is necessary for an indication which is easily seen. A VOM or other similar indicator can also be substituted at some sacrifice in compactness and operating con-

venience.

In place of the standard rf generator lead, which usually incorporates a 50 Ω or 75 Ω terminating resistor, connect the detector lead shown below.

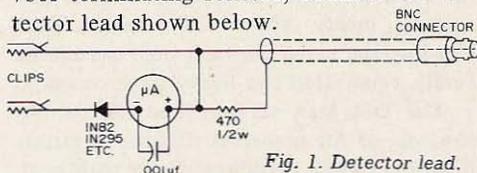


Fig. 1. Detector lead.


My probe has a BNC connector on one end and miniature alligator clips on the other. The components are mounted on the rear of the meter and this assembly is secured to the clip end of the lead with a good cement such as GE's RTV compound. Direct connections may be made to the circuit or a two-turn loop may be connected at the clips for inductive coupling to the circuits to be dipped.

You may now dip circuits whose low frequency limitation is governed by the output of the particular rf generator and the meter sensitivity. No problem has been encountered using the third harmonic of 48.3 to tune circuits in the 145 MHz range.

...WB4MYL■

A Filter Box for CW Ops.

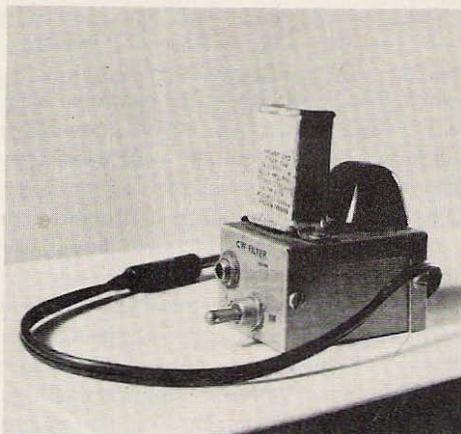Dennis J. Lazar K8TSQ
3494 Tullamore Road
University Hts. OH 44118



The kid knew, long before entering the shack, that the Old Man was working on 80 CW. Halfway down 73rd Street his transistor radio had begun to thump rhythmically. A few irate neighbors — audiophiles no doubt — could be seen glaring from windows or standing about on front porches muttering ominously as radios whined and hissed in stereo behind them.

The young Novice entered through the side door, cautiously making his way down the open wooden stairs. He descended into a dim, musty abyss. The feeble light invading the cellar through high casements barely penetrated the heavy tobacco smog.

The Old Man sat hunched before the controls of his powerful station. Dextrous fingers skillfully manipulated the paddle of an electronic keyer while the sweet music of The Code filled the basement gloom.

The kid stood watching in awed silence as dits and dahs followed fast upon each other's heels in machine gun staccato. The OM was truly a master of the ether, spanning thousands of miles with the controlled lightning at his command.

At last, with a crisp "dah dit dah," the OM "turned it over" to his distant contact. He sat back, puffing hard on his pipe, as the phones came alive. The distant station op was no slouch. His fist was crisp and clean. Moreover, there was little background noise and virtually no QRM. The signal had a clear, bell-like ring to it, quite

unlike anything the kid had ever heard before. Thus, he knew instinctively that the OM had added something to his gear. But what?

He hopped up onto a high stool beside the bench and gave the equipment a quick onceover. The receiver was as he had seen it last. No preselector or Q-multiplier was in evidence.

Then his roving eyes stopped, fixed upon a tiny box placed at the end of the table. It was connected by a length of cord to the receiver's earphone output. Mounted on the box was a jack into which the OM had plugged his earphones. "What... why... how...?" The kid began, nudging the OM and pointing.

"Shhhhhh, wait a minute, George is turning it over to me." Relays clicked, transformers hummed as the big rig went on the air.

Not able to copy at 30 wpm, the kid picked up little of the ensuing conversation. He did, however, catch the 73 and the SK. The QSO was over.

"Ok, what is it?" he demanded.

"What is what?" The OM turned to face his young companion and would-be protégé.

"That little box you're plugged into," the kid replied, pointing. "What is it?"

"Oh, why, that's an audio filter. For CW, you know."

"What does it do?"

"Well, let me show you." The OM

unplugged the filter from the receiver's earphone jack. He then plugged the phones directly into the receiver and tuned to the 40 meter Novice band. A bedlam of sound cascaded from the headset.

"Put on the cans and tune in a station," the OM instructed.

Obediently, the kid sat down putting the phones to his ears. He soon found a medium strength KN7 amid a multitude of stations vying for the frequency. "Okay," he said. "What now?"

"I simply insert the filter into the line like so." The OM inserted the proper plugs into the proper jacks. "Now, what do you hear?"

"Wow!" the kid exclaimed after a moment. "There's only one signal in there. All the others are much weaker."

"Ha - now watch this!" The OM flipped a toggle on the box.

The kid tuned the receiver slightly. "This is terrific. All I hear is the KN7, and nothing else!"

"Whenever you tune a CW station so that the beat note is a 750 Hz audio tone, the filter will let it through. All other tones will be blocked."

"Fantastic!" The kid eyed the tiny box. "What's inside?"

"Oh, just a couple of coils, a few capacitors, and an amplifier module."

"But what makes it tick?"

"Why, resonance, of course. It's a simple tank circuit, but resonant at an audio frequency instead of rf."

"I know a tank circuit is what you tune when adjusting a transmitter, but I don't really see the tie-in. I guess I really don't understand how a tank works."

"Okay," the OM sighed, "make yourself comfortable and let me begin at the beginning."

"Tank circuit is a term used to describe a parallel resonant circuit. These circuits are composed of two elements, an inductor (a coil) and a capacitor. Resonance in a tank circuit is possible due to certain properties of coils and capacitors."

"You mean inductance and capacitance, right?"

"Right. Now, do you know the differ-

ence between voltage and current?"

"Sure," the kid exclaimed, "I did pass the Novice exam, didn't I?"

"Okay," the OM smiled, "tell me about it."

"Well, er - current is the flow of electrons through a wire and voltage is the force pushing it. It's like water in a pipe; the amount of water in gallons running through the pipe each second would be the current and the pressure in pounds pushing it would be the voltage. . .right?"

"Fine, now we can get into explaining resonance. First, let's talk about inductance."

Inductance

When current flows through a coil of wire, it produces magnetic lines of force surrounding the coil. As long as current flows, the magnetic field remains constant. But, when input flow ceases, the field collapses. This collapsing magnetic field cuts across the windings of the coil causing a new current to flow. This induced current flows in a direction opposite to that of the input current.

When alternating current (Fig. 1) flows through a coil, a magnetic field builds and collapses with each change of polarity. When ac is initially applied, voltage and current flow in each turn of the coil. A magnetic field builds up around that turn, inducing voltage in the following turn. The induced voltage is in opposition to the input voltage. Thus, as voltage builds during the first alternation of the ac cycle (ABC) the coil tends to oppose the flow of current.

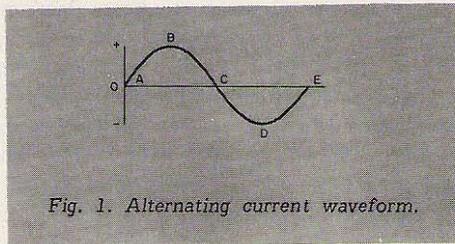


Fig. 1. Alternating current waveform.

As shown in Fig. 1, current reaches its peak at B and begins to decline. The magnetic field collapses, inducing a voltage in the coil. This voltage is in opposition to the voltage of the second alternation (CDE) and will thus resist current flow.

Resistance to change of current flow in a coil is called inductance. The effect was first described by German physicist Heinrich Lenz (1804-65). Lenz states: "Whenever a current is set up by a change of magnetic flux through a coil, the direction of the induced current will be such as to oppose the current which produced it."

Inductive reactance is the value in ohms of a coil's ability to oppose alternating current.

Capacitance

A capacitor consists of two conductors, or plates, separated by an insulator, the dielectric. Materials commonly used as plates in capacitors are metal foil and solid metal plates. Dielectric materials include air, ceramic, mica, and impregnated paper.

Capacitors function as storehouses for electricity. In Fig. 2, a battery is shown charging a capacitor through a switch. When the switch is closed, electrons flow from the negative battery terminal to capacitor plate A. At the same time, electrons flow from plate B to the positive battery terminal. As electrons gather on plate A it becomes negatively charged. The shortage of electrons on plate B causes it to become positively charged.

In the first instant following the closing of the switch, a heavy current flows, with electrons rushing to plate A and away from plate B. Little voltage is needed to force current through the circuit. Plate A soon becomes crowded with electrons and the electron supply at plate B becomes depleted. Current flow slows. More voltage now becomes necessary to keep electrons moving. With decreasing voltage drop across the capacitor due to decreasing current flow, circuit voltage increases. A point is reached at which capacitor voltage equals applied battery voltage. Current flow ceases. The capacitor now is fully charged. If the battery were removed, the capacitor would retain a portion of its charge for hours, or even days. The capacitor may be discharged by shorting across its terminals with a conductor. Current will flow from the negative to the positive terminal until both plates have an equal electron supply.

If ac voltage were applied to a capacitor, the first alternation would charge the capacitor as shown in Fig. 2. The next alternation would discharge the capacitor, recharging it in the reverse direction.

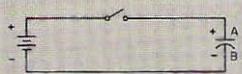


Fig. 2. Capacitor charged by battery.

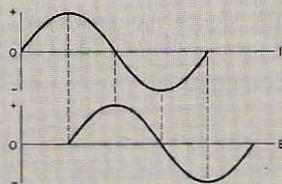


Fig. 3. Current lags voltage by 90° in an inductor.

Electron flow is to plate A and away from plate B during the first half-cycle (AB, Fig.1). The capacitor holds this charge until the second half-cycle (CD) causes electrons to flow to plate B and away from plate A.

With alternating current applied, a capacitor appears to be a closed circuit. Current flows in the circuit as if it were actually passing through the capacitor.

The amount of current that a capacitor can store is determined by its size, nature of its plate area, distance between plates, and the type of dielectric used. The capacitor thus limits or opposes current flow in a circuit. This phenomenon is called capacitive reactance and is measured in ohms.

Reactance

In a resistor, current is opposed by the material of which the resistor is composed. Power is dissipated as heat and thus is lost from the circuit.

Capacitive and inductive reactance also represent opposition to current; however, they consume no power.

Inductance of a coil is measured in *henrys*. Capacity of a capacitor is measured in *farads*. In both cases, the value of re-

actance (the ability to oppose the flow of alternating current) is measured in *ohms*.

Because alternating current flow in a coil causes an induced voltage which opposes current change, there is a phase difference between current and voltage, with current lagging. (Fig. 3). If the coil were pure inductance (having no resistance), current would lag voltage by 90 degrees. Resistance of the wire causes this phase difference to be smaller.

Capacitors also cause a phase difference between voltage and current. This is due to the reversal of polarity across the capacitor with reversals of the alternating current. In a capacitor, the current leads the voltage by 90 degrees. (Fig. 3). This phase angle would also be diminished by resistance.

It can be seen from Fig. 3, that while an inductance tends to oppose a change in current, a capacitance tends to oppose a change in voltage.

In any circuit containing both inductance and capacitance, the total effect on the circuit of these two influences will be the difference between their values.

Resonance

When inductive and capacitive reactance become equal in a circuit, a condition of resonance is said to exist. Resonant circuits can be designed to select or reject a certain frequency or group of frequencies.

Resonant circuits can be constructed in either of two configurations: series or parallel. A tank circuit is a parallel resonant circuit.

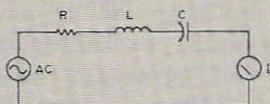


Fig. 4. Series LCR circuit

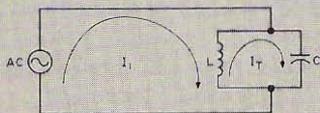


Fig. 5. Parallel LC circuit.

Series Resonance

To facilitate ease of understanding, let us look first at series resonance as shown in Fig. 4. At a given frequency, ac voltage in the circuit causes L and C each to have a reactance according to its value. If we change the input frequency, reactance values of L and C also will change. The value of R (pure resistance in the circuit) always remains constant. The difference in reactance between L and C thus represents an opposition to current flowing in the circuit. By adding this reactance value to the value of pure resistance, we arrive at the total circuit opposition to alternating current at a particular frequency. This value is called *impedance* (Z).

Assuming L and C to be some fixed value, we can find a frequency at which inductive and capacitive reactances will be equal. At this frequency the reactances, being opposite in nature, will cancel each other. Current flow in the circuit will be opposed only by R.

Looking at the circuit in Fig. 4, it can be seen that at the resonant frequency, the ammeter (I) would read a maximum current flow. At all other frequencies the reading would be lower. The circuit, in effect, allows current at one frequency to pass while impeding current of all other frequencies.

Parallel Resonance

When a capacitor and coil are wired in parallel (Fig. 5), the combination will be resonant at a frequency determined by the values of L and C. With the circuit at resonance, little signal current flows. This is because at resonance, a parallel LC circuit acts as a storage device (hence the name tank circuit). Signal energy is interchanged between capacitor and coil at a rate equal to the signal frequency. The interchange of energy, once initiated, continues nearly independent of additional signal current. The capacitor, charged by the signal, discharges into the coil. The collapsing magnetic field of the coil generates a reverse voltage which recharges the capacitor. Since the input signal established the initial charge on the capacitor, the

circuit will accept little additional signal current. Thus, at resonance, signal current is very low while tank current is very high.

A parallel LC circuit at resonance, then, acts in a manner opposite to that of a series resonance circuit. At the resonant frequency, impedance for the signal current is very high, allowing little current to flow in the circuit. For all other frequencies, the impedance is very low. Thus, at resonance, a parallel LC circuit represents a large voltage drop. Current flowing through a high impedance creates a large voltage drop across that impedance. A signal current flowing in a circuit containing an LC circuit at resonance would thus result in a signal voltage appearing across the LC tank. If the signal was not at the tank's resonant frequency, little signal voltage would be dropped across the tank. In this way, a tank circuit acts as a filter, allowing a voltage output only when a signal at the resonant frequency is applied.

"So there you have it," said the Old Man. "Capacitance, inductance, reactance, resonance, the whole bit." He stretched and began to rise.

"Say, wait a minute," the kid blurted, coming out of a semi-doze, "you forgot something, didn't you? What about the box?"

"Oh yes, the filter."

"From the lecture you just gave me I assume there are coils and capacitors inside. But how did you manage to squeeze in all the components and how does the IC tie in?"

"All right," the OM sighed, "let's start by opening the box and also by looking at the schematic."

CW Audio Filter

As most hams know only too well, CW operators, especially those using the Novice band segments, are a long-suffering lot. There are QRN and foreign broadcast interference to contend with, to say nothing of adjacent-station QRM due to crowded bands. Rarely is a contact completed without at least one station issuing a strident CQ only a few cycles from the frequency in use. Many a good QSO has

ended in frustration, fading away into this constant background din.

There is a simple and inexpensive solution to problems brought on as a result of too many stations occupying too little band space. An audio filter, selective enough to single out a discrete audio note, can make a nearly impossible snarl sound like code practice.

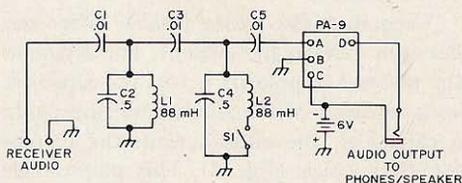


Fig. 6. Schematic of CW Audio Filter.

The Circuit

The audio filter is based upon three major components: A pair of toroidal coils which combine small size and high inductance, and a solid-state audio amplifier module.

Receiver audio, consisting of CW signals of many different audio frequencies, enters the filter through coupling capacitor C1 (Fig. 6). Capacitor C2 and coil L1 comprise a tank circuit resonant at 758 Hz. This tank will shunt to ground signals that are not at the resonant frequency. A 758 Hz signal will cause signal voltage to be developed across the tank. This signal is coupled through C3 to the top of tank circuit C4-L2. If switch S1 is closed, off-resonance signals are further attenuated. With S1 open, the second filter circuit is disabled and the signal passes directly to C5. The function of S1 is to provide two levels of selectivity for ease of tuning.

From C5, the filtered signal enters module PA-9 where it is amplified to drive headphones or speaker. Volume of the input audio from the receiver determines output volume of the amplifier.

Filter output frequency may be changed to suit the ear of the individual. Some may desire a lower tone, some a higher pitch note. By changing the value of C or L, the

STEP UP TO TELREX

Professionally Engineered Antenna Systems

Single transmission line "TRI-BAND® ARRAY"

By the only test that means anything . . . on the air comparison . . . this array continues to outperform all competition . . . and has for two decades. Here's why . . . Telrex uses a unique trap design employing 20 HiQ 7500V ceramic condensers per antenna. Telrex uses 3 optimum-spaced, optimum-tuned reflectors to provide maximum gain and true F/B Tri-band performance.

ONLY TELREX GIVES YOU ALL THESE FEATURES . . .

- Power rating 4 KW PEP . . . rain or shine
- Wind rating survival 110 MPH
- Patented broad-band coaxial Balun
- Heavy-duty steel gusset mounting plate
- Aluminum boom 2 in., 2½ in. O.D. x 18 ft.
- Large diameter, .058 wall taper-swaged dural elements for minimum

weight and exceptional strength to weight ratio

- Stainless steel electrical hardware

With a Telrex Tri-band Array you get 49 lbs. of educated aluminum engineered and built to provide many, many years of performance unmatched around the world by any other make. Longest element 36 ft. Turning radius 20 ft. Shipping weight 65 lbs. Shipping container 13 in. x 5 in. x 13 ft.

Note: If not available from your dealer, order direct. You'll get fast, personal service.

Telrex Labs are design engineers, innovators and manufacturers of the world's finest ¾ to 160 meter communication systems and accessories priced from \$25 to \$25,000.

For technical data and prices on complete Telrex line, write for Catalog PL 71.

TB5EM **\$395**

Other
Multi-Band
Arrays Available


Elements shortened to show details.



BALUN



TRAP

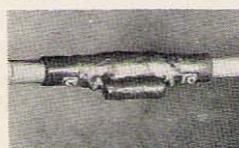

TYPICAL TELREX "MONO-BAND" ANTENNAS

15M317	- "Monarch", 10 DBD, 3 El., 4 KWP, 2-1/2" O.D., 17' boom	\$175.00
20M326	- "Monarch", 10 DBD, 3 El., 8 KWP, 3-1/2" O.D., 26' boom	\$355.00
2M609	- "Monarch", 14 DBD, 6 El., 6 KWP, 1" O.D., 9' boom	\$ 39.95
2M814	- "Monarch", 16 DBD, 8 El., .8 KWP, 1.375" O.D., 14' boom	\$ 59.00
6M516	- "Monarch", 13 DBD, 5 El., .8 KWP, 1.5" O.D., 16' boom	\$ 63.95

and ----- many, many more! send for PL-71 Dept. C

telrex LABORATORIES

TV And Communications Antennas Since 1921
Asbury Park, New Jersey 07712 201-775-7252

resonant frequency of the filter may be altered.

Components

Voltage ratings of the components are not important in this circuit. Receiver audio voltage never will approach usual component ratings. Capacitors may be disk ceramic or any other type found in the junkbox or surplus electronics store. If size is no object, an economical substitute for the two $0.5\mu\text{F}$ capacitors is a surplus double oil-filled type. Most have flanges for chassis mounting.

Coils are toroids, available through many sources. You may come across them advertised for sale in the classified section of this magazine. Toroids often are used in Teletype equipment as filters to differentiate between two audio tones that carry RTTY information.

PA-9 is a "public address amplifier module" available through Lafayette Radio Electronics Corp., either locally or by mail order (\$3.50). Address of the company is Box 88, Syosset, LI, NY 11791. Higher powered, higher priced modules are readily available from many sources where more audio output power is desired.

The battery may be of any type, considerations being size versus life.

Your preference is the rule here.

Construction

A minibox, a few terminal lugs or strips, a soldering iron, drill, and a screwdriver will get you through this project in fine form. The device, however, need not be built in a minibox. You can breadboard it or even build it right into your receiver.

Toroids are sold centertapped with these leads open. You must solder them together before installation. The coils may be mounted one above the other with a bolt running through the centers. You can, however, mount them in any way that will best fit the space available.

Mounting the module should present no problem even though it has absolutely no provisions for mounting. A few rubber grommets glued to the bottom of the module and then glued to the minibox will

hold nicely. Leads should be covered with "spaghetti" tubing and run through a rubber grommet placed in a hole in the box under the module.

"Sounds great," said the kid. "How do you operate it?"

"Listen to this." The Old Man picked up the headphones. He switched the filter to its *out* position. With only one filter in operation, a few signals sounded in the phones. . . still nothing like the bedlam really existing on the band.

"You have to zero in on the filter's resonant frequency," he explained. "Tune the receiver's main tuning or bfo tuning control to adjust the beat note to the proper frequency."

"Wow, that signal really popped up there." The kid moved in closer, taking hold of the receiver dial. He tuned back and forth. "The strength of this one station comes through at least ten times louder when you hit the resonant frequency."

"That's right. Now let's flip in that second tank." The switch clicked and only one signal remained beeping in the phones. Adjacent signals could no longer be heard at all.

"There's that ringing sound," said the kid. "Makes it a little hard to copy."

"When the Q of a circuit (its selectivity) gets very high, the circuit begins to resonate," the OM explained. "That's the ringing effect you hear. Still, though, it's a small enough price to pay for not having to contend with a pile of other signals."

"You know," the kid grinned hopefully, "you really ought to build one of these for me. It would be a real lifesaver on 40 meters."

"What?" the OM demanded. "Do you mean to tell me that after sitting here and listening to this whole monolog, you don't think you can build one yourself?"

"Well," replied the kid, "the way I see it, if I spent all the time it would take me to build a filter, I wouldn't have time to learn the code well enough to use it."

The kid ducked as a box of screws sailed past his head.

...K8TSQ

NEW 12 vhf-fm channels all solid state

AGC circuit at the front end
3 TRANSMITTING POWER positions.
REAR panel has provision for 25w unit,
TONE squelch, and MULTIPLIER unit.
CHANNEL SELECTION by diode switch.

Remote control possible

34/94, 94/94, MIKE included.

~~\$289.95~~

NOW ONLY:

249.95



6m and 2m models

NEW REGULATED DC POWER SUPPLY
OVER 3 AMPS FULL LOAD
RIPPLE CONTENT 1.5 mv P-P.
AND EQUIPPED WITH SHORT
CIRCUIT PROTECTION!

ONLY \$29.50

ACCESSORIES:

2 meter & 6 meter preamplifier.
Standby beep OSC unit.

TELECOMM ELECTRONICS
P.O. BOX 461. CUPERTINO, CA. 95014

DUALS

J. K. Bach WB2PAP
Ivy Hill Road
Walden NY 12586

*Electronics is filled with
dual-role phenomena
All you have to do is look. . .*

The electrical art in general has one very helpful feature, though this is little realized or appreciated, and that is the dual or reversible nature of many of its instruments. In mechanics, a steam engine may be driven by another engine and make a pretty good compressor. Mechanics has few of these cases, however, while electronics has several. This by no means doubles the student's knowledge without effort on his part, but it really does help. After all, if you knew one half of a Siamese twin to speak to, you could hardly avoid knowing the other half too.

Suppose you bought a new-fangled fringe-area TV antenna — which way would you point it? The way everyone else points his, of course. But the new one is different from theirs — which is the front and which is the back on the doggone thing? I couldn't tell you without seeing it, and maybe not even then. But let's examine highly directional antennas a moment:

One of the most directional, and highest gain antennas is the parabolic reflector type. These can have gains of around 40 dB (depending on frequency, size), which means that they transmit and receive 10,000 times the signal that a nondirective antenna would.

These antennas are usually called "bowls" and you often see them out in the country and on top of buildings. The bowl is actually a reflector, while the actual antenna is a little noodle of a thing in the former's focus. In Fig. 1, the transmitter T

sends the signal to the antenna A, and the radio waves bounce off the bowl and are focused on the receiving bowl to the right, many miles away. Here the waves are focused on the receiving antenna A, run down the transmission line into the receiver R. Just look at a bowl and you can see without any difficulty which way it is aimed.

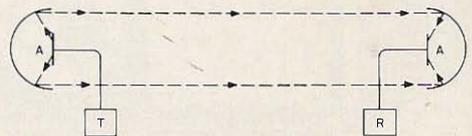


Fig. 1. The parabolic antenna concentrates virtually all the radiation into fairly tight beam.

Now consider the yagi antenna in Fig. 2. The longest element, or dipole, is at the left end and is called the reflector. The next element is the actual antenna, which is connected to the transmitter, or receiver, often switched back and forth alternately between them. In general, TV antennas are of this type. The arrow *usually* points in the direction in which the antenna transmits best — in the ideal case, toward the distant receiving antenna. At the same time, if it is used as a receiving antenna, the arrow points in the direction *from* which the best signal will arrive. You do not need to turn the antenna end-for-end when changing it from transmit to receive; this would be a clumsy expedient if it were necessary.

from those wonderful people that gave
you Amateur narrow band FM



NOW PRESENTS model FM 3601

**AMATEUR—2 meters
TRANSMITTER-RECEIVER**

(from 144 to 148 MHz)

- 8 to 10 WATTS
- SOLID STATE
- 8 CHANNELS
- HIGH PERFORMANCE RECEIVER



Professional Quality for the Professional Amateur!



The Finest Printed Circuit Materials and Exclusive Design Techniques Provide the Best in Professional Quality and Performance

- ▶ 8 Channels with Instant Push Button switching
- ▶ Solid State. Finest quality silicon transistors
- ▶ Netting trimmer for each receive and transmit crystal
- ▶ High quality mechanical filter for adjacent channel rejection
- ▶ Military-grade, glass-epoxy printed circuits
- ▶ Rugged, serviceable design, compact construction
- ▶ Diode protected Dual-gate FET mixer
- ▶ 25 transistors, 1 IC, 1 MosFet, 16 Diodes
- ▶ Overload protected receiver R.F. stage

\$29995

Complete with microphone, mobile mounting tray and 2 pair of crystals, (146.94T/146.94R and 146.34T/146.94R)
Model PS-2923 AC Regulation Power Supply . . . \$39.95

SPECIFICATIONS

Frequency Coverage: 144—148 MHz
Dimensions: 6¾"W x 2½"H x 9"D without tray
Weight: 5 lbs.
Microphone: Controlled Magnetic
Antenna Impedance: 50 ohms

RECEIVER
Sensitivity: At least 0.5 μ V for 20 db Quieting,
0.35 μ V for 12 db Sinad
Selectivity: 16 KHz @ 3 db
Freq. Tolerance: .001% from —30°C to 60°C
Spurious Rejection: At least 60 db
Audio Power: 2 W. w/less than 10% distortion
Squelch Range: 0.2—0.8 μ V
Intermediate Freq.: 10.7 MHz & 455 KHz

TRANSMITTER
Emission: 16F3 (Frequency-Modulated)
Freq. Tolerance: .0005% from —30°C to 60°C
RF Power Output: 8 to 10 Watts
Spurious & Harmonic Attenuation:
More than 50 db below RF carrier
Deviation: Internally adjustable 0—10 KHz

POWER REQUIREMENTS
Receive: Squelch standby: 0.175 Amp.
Maximum audio: 0.500 Amp.
Transmit: 1.90 Amperes
Voltage: 13.8 VDC—Neg. Ground only

315

SONAR RADIO CORPORATION
73 Wortman Ave., Brooklyn, N. Y. 11207

Please send information on Model FM 3601.

Name..... Dept.....
Address.....
City..... State..... Zip.....

NUVISTOR LOW NOISE PREAMPLIFIER



MODELS PV 27, 28, 50,
144 and 220

For 27 (CB), 28, 50, 144 or 220 MC. (Also available for 150-170 MCS)

Add this Ameco Nuvistor Preamplifier to your receiver (or converter) to improve the sensitivity and noise figure. Two tuned circuits also improve rejection of image and spurious frequencies. Compact, easily connected and low power requirements, wired and tested with tube.

Ideal for improving performance of surplus FM Two-Way equipment for "NET" operation on the 2 and 6 meter bands.

Write for details on 150-170 mcs and others



P.O. Box 6527 Raleigh, North Carolina 27608

The same holds true for the rhombic and quad antennas in the same figure. In fact, it holds true for *any* directional antenna.

Now consider the vacuum tube; sometimes it has a simple function, as in a straight uncomplicated audio amplifier. But it is entirely capable of serving half a dozen functions at one and the same time. In a superheterodyne the same tube usually serves as a heterodyning oscillator and a frequency changing modulator at the same time. A simple regenerator, such as the type your grandpop used, is a regenerative detector and more often than not operated as a zero-beating oscillator at the same time — hence all the squealing you heard when they were tuned across a broadcast carrier. Not only that, but you could put an ordinary carbon microphone in the ground lead of one of these receivers and transmit your voice over it. This worked only for short distances, but it used the same tubes and antenna for both, and required no switching — it was completely

automatic send and receive.

Or look at these toy-like walkie-talkies that children and fools abuse to the consternation of the FCC: They one and all rewire themselves at the touch of a thumb-button so that the loudspeaker becomes the microphone, the first transistor becomes a transmitting element, and the audio amplifier is turned end-for-end. Dual? It surely is.

Years before the telephone was invented, kids used to play with string-and-can intercoms. They would punch a small hole in the bottom of an ordinary tin can — empty, of course — insert a string of thread and knot it, then stretch the string to a similar outfit in the next room or out in the yard. As long as the string was fairly taut and didn't rub on anything, it would

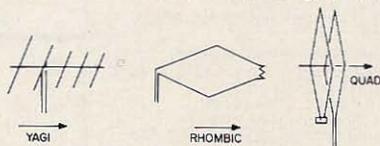


Fig. 2. Directional antennas must be pointed toward the station you're communicating with.

From Allied Radio Shack . . .
**The First First-Class Listening Post
 At a Really Affordable Price!**



**ACCESSORIES INCLUDED
 AT NO EXTRA COST!**

External
 Speaker
 Reg.
 7.95



Headphones Reg.
 2.49



Shortwave
 Antenna

Reg.
 1.98



SWL
 Guide


Reg.
 2.25

Save a Total of \$14.67!

the one with GUTS!

3-Gang Tuning
 Capacitor

PC Board
 Construction

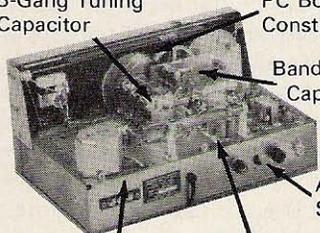

Bandspread
 Capacitor

AC/DC
 Switch

Heavy-Duty
 Power Transformer

Loopstick
 Antenna

Available NOW
 at 950 stores
 Nationwide!

119⁹⁵

**Realistic DX-150A—The Communications
 Receiver That Changed The Industry**

Hams, SW, Single-Sideband, CW—from here, from there, from everywhere! EVERY FEATURE for superior reception of 535 kHz to 30 MHz. Four-FET cascade RF stage, mechanical filter, variable BFO, product detector, 160-10 meter bandspread, "S" meter, fast and slow AVC, 11 front panel controls. Solid-state? You bet! Power? 12 VDC, 8 "D" cells or 117 VAC! See it at our store near you. Or you may order by mail—it costs no more!

There's a Store Near You. See the Yellow Pages

ALLIED RADIO SHACK

Dept. 73-1

A TANDY CORPORATION COMPANY

2725 W. 7th Street, Fort Worth, Texas 76107

Rush me the DX-150A Outfit postpaid. I enclose
 check money order for 119.95.

Name _____

Street _____

Apt. _____ Route _____ Box _____

City _____ State _____ Zip

talk pretty good. This was acoustic duality; you had to holler into the can and poke one ear into it alternately. At the transmitting end, sound waves vibrated the string, and at the receiver, the string vibrated the diaphragm, which was the bottom of the can, making sound waves again.

To get back to aiming your TV antenna: One of the very best methods is to run a pair of wires up to your roof, with an ordinary head receiver, or pair of receivers at each end. No batteries, no amplifiers, just "Whoop and holler!" Actually, you don't have to talk all that loud; it works surprisingly well.

The theory is simple. The sound of your voice vibrates the diaphragm of the headphone (left unit in Fig. 3) which varies the air gap and consequently the magnetic flux in the headphone winding, which generates a current — you know, just like Lenz's law. Anyway, this current flows to the end of the wire and — Lenz's law again, backwards — vibrates the diaphragm and makes sound again.

Faraday himself knew that an electric current could produce motion through electromagnetism, and that the latter could generate a current by reverse action. When the electric motor was invented, it was realized at once that driving this motor with, say, a steam engine would generate current provided the field was magnetized, even slightly. A few years ago, when automobiles still had generators, the voltage regulator would occasionally fail and connect the generator directly across the battery which would instantly run the generator as a motor until the battery itself ran down. If the generator could not turn the engine over, this happened pretty quickly!

Of course, not all instruments are dual. While a telephone receiver, or loudspeaker, may transmit very clearly when sound strikes it, the current generated is weak. But send a current through a carbon microphone and the only sound you will get out of it is a sizzling, frying noise as it burns up, if you push it that far. But with normal current through it, it will transmit

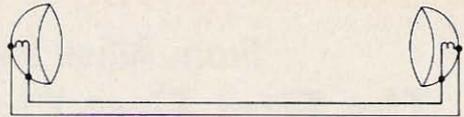


Fig. 3. Sound-powered phones are an electrical equivalent of the once-popular string and can.

very well — more efficiently than any other type. It just isn't dual. Not all motors are, either.

Technicians have a little trick for finding hidden microphones. They induce a heavy signal into the general area by methods that are kept as secret as possible, and the microphones "squeal" like tiny loudspeakers. These are not magnetic types, but crystal microphones.

Another type of crystal is the quartz oscillating crystal. These are tiny squares cut from a quartz crystal, something like minuscule soda crackers in proportion. Now quartz is one of the most elastic substances extant (no kidding, it really is!) and these tiny squares will ring like a bell, except that you can't hear them, because the frequency is millions of vibrations per second. In fact, this is the actual physical vibration that keeps the broadcast transmitter exactly on frequency. It rings better — far better than a steel tuning fork, and is more stable. But more than that, it is self-exciting.

Marie Curie's husband Pierre discovered that if you strike certain crystals, they gave off electric shocks, and if you shocked them, they were distorted out of true. The distortion was infinitesimal, but the voltage generated was considerable. A quite recent ignition system for small engines squeezes a crystal to make the ignition spark — simple and reliable. To get back to the oscillating type, when the crystal oscillator was first tuned on, the voltage twisted the crystal a tiny amount, until it went as far as it would go. Then the crystal untwisted, generating a voltage of its own, which was amplified by tube or transistor and reapplied to the crystal which distorted again. This process is much like the operation of an ordinary doorbell, and results in a very pure vibration of the crystal, of very

precisely determined frequency, so long as the voltage is applied to the oscillator. But you need that twist-to-volts and volts-to-twist action to make the crystal oscillate in the first place. And these crystals have to be sliced and ground and etched from a piece of quartz crystal.

How about transformers? Take a filament transformer, for example: Put in 120V in the primary, and get 6.3V in the secondary. Or with 6.3V in the same winding, you will certainly get 120V in the other winding. The transformer doesn't know or care which way it steps, up or down, so long as you give it the right voltage and frequency. Pretty dual, I'd say.

A meter is a kind of dc motor. Will it generate electricity, too? Certainly! In fact, we can demonstrate this principle in a very useful test. Sometimes the meter is connected to the wrong points in a circuit and you wonder if it has been burned out. Or you see a nice microammeter in surplus, all dirty but apparently nearly new. Is it burned out? Or is it well worth the buck-fifty the man asks? You haven't any kind of test instrument to check it — all you have is your hands.

With the meter in your hand, see where the needle rests. (Fig. 4.) The zero adjustment may be a little off, but no matter. Suppose it is right on zero: now twist the meter to the left with a quick but not violent wrist-motion. The needle should swing 10 or 15 degrees upscale for a moment. This checks hair-spring and pivot, which must also be working okay. Now with a paper-clip, bit of wire, tie-clasp, or even a coin, short-circuit the terminals of the meter and try the twist again. This time, if the meter coil is all right, the needle should swing *much less* than before — perhaps only 5 degrees or so.

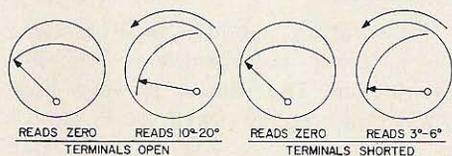


Fig. 4. A simple test can tell you a lot about a questionable meter.

When the meter terminals were open-circuited and the meter was twisted to make the needle swing, a voltage was generated by the coil moving in the magnetic field. But since no current could flow, no power was generated. But when the terminals were shorted, current *did* flow, power *was* generated, and dissipated in the winding itself, resisting the mechanical force that generated it by trying to drive the needle to the left. This is called "damping." Sensitive portable meters have a switch operated by the cover of the instrument, which shorts the meter coil when the cover is on. This prevents bending the needle due to carrying and shipping accidents, though if you drop it off a building you can kiss it goodbye.


Come to think of it, this duality business started before radio or wireless itself did. Maxwell deduced from the behavior of light that it was a kind of electromagnetic radiation, and that there should be others as yet undiscovered.

Hertz set out to find the undiscovered radiation. He used a spark coil of the same general type that Henry Ford used in his Model T ignition system. Connected to a battery, this gave a continuous series of sparks across a gap between two brass balls.

How to detect radiation from this? Sparks were disembodied electricity, so to speak; there was something magic about them. He took a brass rod about a yard long, put brass balls on the ends, and bent it into a circle or hoop, about a foot in diameter. If the gap between the balls was tiny enough, if the room was dark enough, if the loop was close enough, if the orientation was near enough, if anything like resonance was obtained, he should see a tiny spark in his loop. History tells us that he did, but you can't tell me this was accomplished all that easily. It probably took him quite a long time to try all the various positions and gaps and other variables until he hit on the one combination that would work. He had discovered hertzian waves, using a transmitter and receiver which were essentially duals of each other. More, he discovered hertzian waves with the most insensitive receiver ever built!

WB2PAP■

A MINIATURE Add-on Oscillator for 2m FM

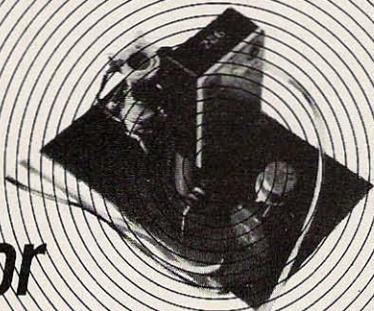

In my past experiments with FM transmitters, I built up a simple crystal oscillator that is easy to reproduce and uses a minimum of components. The unit uses about 400 mW of power to an RCA 40080 NPN silicon transistor. This transistor is low in cost because of its wide usage commercially. This oscillator operates in the 6–8 MHz region with the tuned circuit described here, but should work well throughout the high-frequency spectrum.

This oscillator's first application was in an FM transmitter designed for 2 meters. The circuit layout as it is in this article was used as a crystal oscillator that was used to control the frequency of a receiver. When old AM receivers are used with VHF converters there is often a problem with frequency drift. The MARS or net operation is necessary, a drifting receiver can be a real headache. This oscillator can be built for only a few dollars, with a good junkbox. With a little study this oscillator can be used with almost any receiver to end the need for searching for the frequency each time and never being sure that no one is calling you. Of course, the oscillator can also be used as part of a transmitter, for a frequency spotter, crystal checker, an extra-frequency deck for an FM unit, or

just an interesting little project to pass the afternoon.

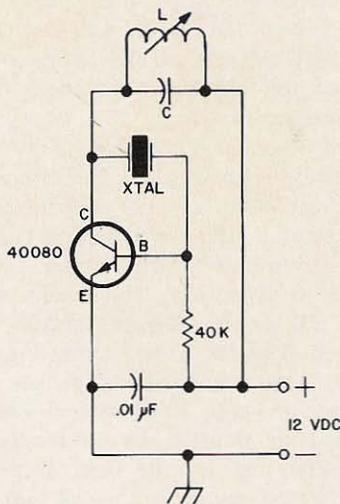


Fig. 1. Schematic diagram of simple oscillator.

Construction

The oscillator was built on a PC board and a layout is provided to simplify construction. The circuit is very non-critical, and can be wired up in almost any layout, but if you build a large number of projects and buy PC materials in large quantities, you will find that it is less expensive, much easier, and neater

than you think it might be. Ferric chloride is used for etching the copper and can be obtained from chemical supply houses in gallon sizes for that very purpose. PC board material can be obtained from electronics suppliers or by mail-order from dealers such as Allied in Chicago. The resist can be almost any kind of good enamel paint that is applied to the clean copper side of the board where the conductors are to remain. The board is then soaked in warm ferric chloride solution for ten minutes or so, until the desired action has taken place.

The board is cleaned, drilled, and the components soldered in place. The crystal socket used required slots instead of holes for mounting. The coil, mounted in a hole on one end of the board, is made from turns of 30-gage enamel wire on a 1/4 in. diameter slug tuned form. The capacitor across the coil (C) is 275 pF, a dipped mica type. The tuned circuit should be approximately tuned to the desired frequency with a grid dip meter before applying it to the transistor. Any type of L or C can be used if it is tunable to the crystal frequency desired.

Operation

Plug a crystal into the socket after L and C have been determined with the grid dip meter. If a low-impedance power supply is to be used (batteries) a resistor should be placed in series with the power supply for safety reasons. The oscillator current will be 20–40 mA. If it is working properly, removing the crystal and tuning L and C will change the current. Tune for maximum output, not for maximum current. It will key better with a load attached. Because of the minimal circuitry, the oscillator tuning and operation may exhibit some strange characteristics, but it has never failed to give a strong clean signal. The output of the oscillator can be taken from the collector of the transistor with a small capacitor, or if more voltage is required, a secondary can be wound on L to provide higher output.

In the receiver used, power was easily taken from the cathode of the audio

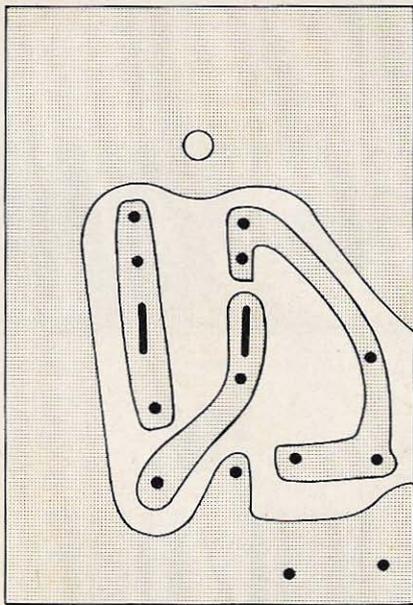


Fig. 2. 42% printed circuit layout; refer to the schematic and picture for parts placement.

output tube. This will only work when a class A output stage is used. Since the tube itself limits the current obtained from the cathode bias, no resistor is needed to protect the transistor. The transistor runs slightly warm because of the power it is dissipating, and should not be placed in an extremely warm environment.

The simple bias circuit used will not protect the transistor. A switch was wired into the receiver to short the grid of the receiver oscillator and turn on the crystal oscillator. The place and amount of oscillator injection must be determined by experiment. If not enough signal is available from the oscillator, it might be injected into the first rf stage of the receiver. This article assumes that the reader is familiar with how his own receiver operates, and will experiment to find best results.

Regardless of how this project is approached, it can fill a practical use or provide an afternoon's amusement at low cost.

The 40080 \$1.30 is available from Circuit Specialists Co., Box 3047, Scottsdale AZ 85257. Add 15¢ for shipping.

...WB6BIH

GAIN ANTENNA

for VHF/UHF REPEATERS

*... Quadruples your repeater
output power and will
bring in solid those
marginal mobiles
in the fringe areas.*

Ken W. Sessions, Jr. K6MVH

Probably the most popular antenna in the amateur repeater world is the omnidirectional collinear coaxial stack, although it is seldom called by that name. Versions of this antenna are manufactured by such companies as Prodelin, Phelps Dodge (Communications Products), and several other firms that build antennas specifically for the commercial bands.

Two of the reasons the collinear antenna is so popular are that it can be made to exhibit a great deal of omnidirectional gain at a very low angle of radiation and it takes up very little space. In its manufactured form, it resembles a long fishing pole with a pair of crossed fins at the base.

In spite of the fact that a great deal of painstaking effort is required to make the antenna and get it just right, the operation is surprisingly simple. And what makes it even more attractive to the amateur, it is remarkably inexpensive. About all you need is a good-sized hunk of 50Ω foam-dielectric coaxial cable and some polyvinyl-chloride (PVC) pipe. For 2 meters, the pipe should be between 20 and 21 ft in length; for 450 MHz, an 8 ft length will do fine. The total omnidirectional gain (as compared with a reference dipole) will be 6 dB (actually 5.8 dB, but who's counting?).

Building the Antenna

Ignoring the structural aspects, the antenna itself is nothing more than a series of precise lengths of coaxial cable soldered in an alternate phase-reversal configuration as shown in Fig. 1. A quarter-wave whip at the antenna's tip shorts the inner and outer conductors of the coax and becomes the terminal radiating element. At the lower end of the antenna, the last coax section

Invitation to transmit

*Ina L. Thurmond
1040 Meadows End Drive
Calabasas CA 91302*

I knew before we were married that he was a ham. He even told me. His mother used to give him books about electricity instead of letting him read comics.

I remember soon after we were married, he brought me a large paper bag. His eyes were shining, and he had the most lovable smile. I was ecstatic! He had actually gone out and bought something for our little home.

He did, but I actually didn't know quite what to say. In the bag was an aluminum box, with a few tubes and some wires.

"What is it"

"Two meters."

"Oh"

"A radio."

Suddenly, I had the overwhelming feeling that our marriage had just been invaded.

There was that one evening I sat in the livingroom alone, watching snow fall lightly outside, while he was up in the attic calling CQ, and thoroughly enjoying himself.

The time had come! I gathered all my courage, put on my winter jacket, and rehearsed my speech as I climbed those stairs. It was freezing up there! The air was drifting snow in one window and blowing dust out the other (through the cracks, of course).

It was very dark, except for the immediate area lit by the bulb dangling over his desk. He pointed to a box and motioned for me to sit down. He was holding the mike with his gloves on, and his breath fogged each time he spoke. I pulled up the wooden box close to the light bulb and sat.

When he finished talking to the other voice, I asked something that made me feel part of the action: "Why don't we set this up downstairs?"

He didn't think it was such a good idea. He didn't want to mess up the place with bits and pieces of solder. I nodded my head in agreement, since the place really wasn't ours to begin with. Well, I went downstairs, and began to read the Radio Amateur's Handbook. I figured I might as well start at the beginning of things to understand such an interest.

It has been three houses and six thousand miles later, and we still have all the stuff, and some new stuff; but at least the main antenna we have now doesn't oscillate when the wind blows, and it doesn't run down the middle of the house through the bedroom closet.

At present, we have a four-shelf bookcase pertaining to amateur radio and electronics.

Once in a great while, the pile of magazines for article cutting gets high, and he gets down on the floor with a pair of scissors and begins to leaf through all his books. It is amazing the effort and devotion one goes into.

"Hey, don't throw that out!" he shouts.

"Why not?"

"I haven't seen it."

"Woman's Day?"

"Oh."

If you are the wife of a ham, or the husband of one, don't despair. Amateur radio is a scientific hobby, and hobbies are a part of life just like golf, hunting, boating or cooking. A hobby is an interest to which one gives his spare time, that's all.

...Thurmond■

AT LAST!

GET YOURSELF "A PERFECT FIST" EASILY WITH A...

CODETYPER

NO MORE... HAND BUG ELECTRONIC

THE PUSHBUTTON WAY TO PRECISION MORSE.
WHY GO PART WAY WITH AN ELECTRONIC KEYS?
CODETYPERS are now in use all over the world:

- For learning code without a teacher
- For fatigue-free operation

Characters form the instant a button is pressed momentarily, automatically locking out all other buttons until characters and spaces are transmitted... prevents overlapping

- Speed is continuously variable from 5 to 55 wpm
- Built-in monitor speaker with 1000 cycle tone burst
- Built-in keying relay
- Completely solid-state—21 transistors
- Rechargeable battery operated

SEND 25% Deposit With Any C.O.D. Orders

- *Batteries: 12 volt NiCad \$25.20
- 6 volt NiCad \$ 6.40
- 1.2 volt NiCad \$ 2.28

PRICE COMPLETE WITH BATTERIES \$195.88

SEND FOR FREE TECHNICAL BROCHURE #

4

MODEL 400



Net \$160
*Less batteries

COMPUTRONICS
ENGINEERING

World Headquarters

4949 Hollywood Blvd. Los Angeles, California 90027
Dial (213) 660-0550

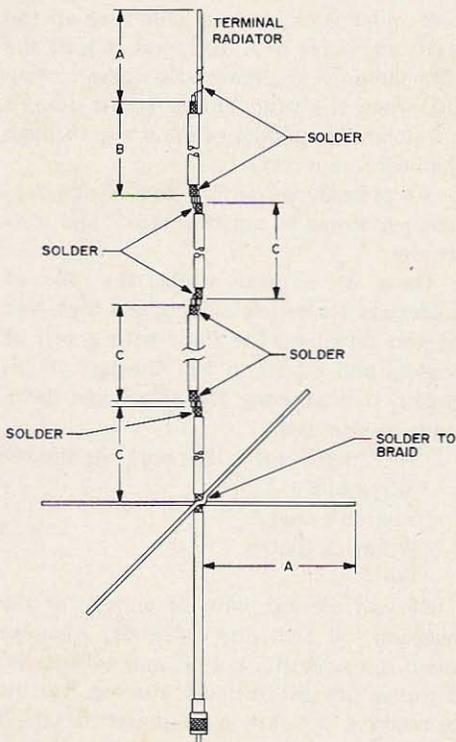


Fig. 1. The collinear gain antenna is made up of coaxial sections connected in a phase-reversal configuration. The bottom section (from the radials to the first joint) and the upper section (which joins the antenna to the shorted radiator) are half the size of all other sections.

actually becomes the feedline itself, whose length, incidentally, is not critical as long as the dimensions are followed with religious fanaticism.

A number of amateurs have managed to build antennas of this type, and diagrams have never been scarce. But few have handled the project successfully. Getting the antenna together is no big deal. The problems start to happen when it's time to turn the soldered-together pieces of coax into a structurally sound antenna. Applying wet epoxy, as in a fiber-glassing scheme, doesn't work out. I have yet to determine whether the problems are attributable to some chemical interaction between the wet epoxy and the coax dielectric (changing the dielectric constant of the line) or because the hardened epoxy doesn't allow any flexing of the coax braid. In any event, sealing the antenna with

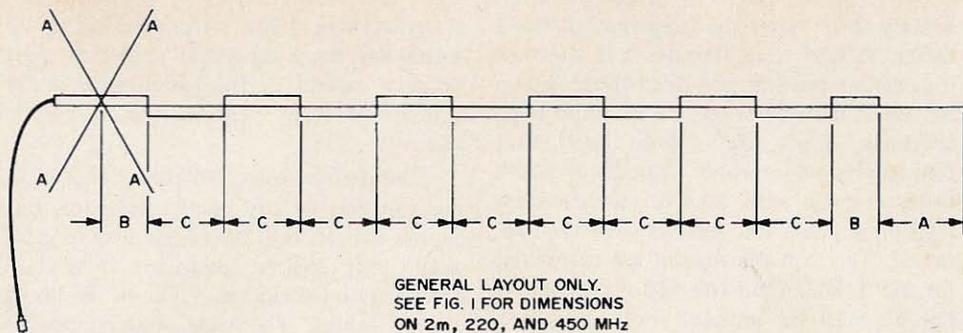


Fig. 2. Layout and dimensions of collinear gain antenna. The 2 meter dimensions are for a frequency of 147 MHz; the 450 MHz dimensions are for 442 MHz exactly. The 220 dimensions are for 220.5, just half the 450 frequency. The antenna is broadbanded enough to yield a low vswr on any frequency within a megahertz of that shown.

epoxy is ultrabad news. When the antenna is rigid and looks great, you'll measure a very disappointingly high standing wave ratio and you'll discover with much lament that your old groundplane worked better.

The commercial antenna people use fiber glass, but they do not use it to seal the antenna. Instead, they use an inert and flexible sealer, then encase the whole business within a preformed fiber-glass tubular envelope. At least one of the commercial suppliers uses beeswax as the inert sealer. Actually, there is no real need to immobilize the antenna once it has been placed inside the PVC pipe. The most important point in the construction process is to make the thing water-tight. Water drops

inside a hunk of coax do bad things to antennas and feedlines; and once the water gets inside, you're better off changing antennas than trying to ignore the problems.

The dimensional details of the antenna are shown in Fig. 2. Lengths have been calculated in the decimal system to the nearest hundredth of an inch. Of course, you'll not be able to maintain this accuracy, but the system did simplify the computations. The 2 meter figures are based on an operating frequency of 147 MHz. The antenna is broadbanded enough to give an swr of close to unity regardless of the FM channel of operation. The 450 MHz frequency of operation is 441 MHz,

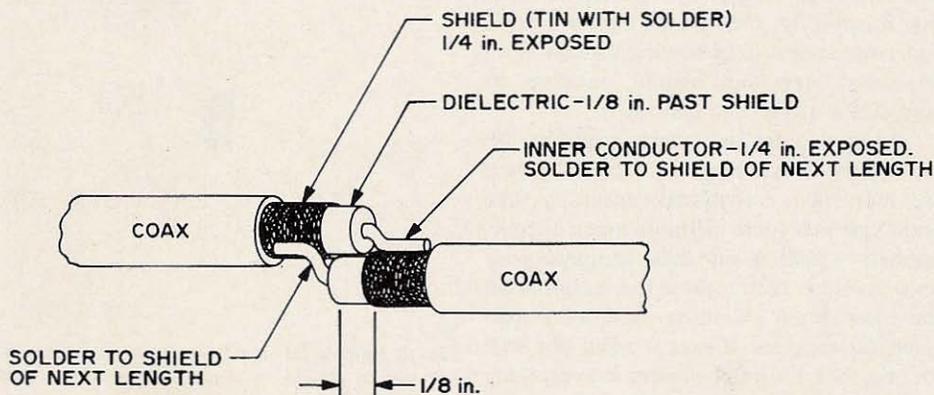


Fig. 3. The coaxial lengths should be soldered as shown. Keep the braid trimmed evenly all the way around and make sure the braid from one section doesn't make contact with the braid of the next section. If conductors are well tinned, problems will be minimized. Coax lengths are measured individually from braid end to braid end.

exactly three times the frequency of the 2 meter version. You'll note that the 450 dimensions are just one-third those shown for the 2 meter version. If you build both antennas, don't select those two exact frequencies for repeater channels or you'll likely end up with your 2 meter system triggering your 450 receiver – it *has* happened. The 220 dimensions are calculated for 220.5 MHz (half the 450 frequency). I haven't built the antenna for 220 because I've never had the occasion to use that band except when getting into W6ZJU's private repeater. But if 450 continues its trend of increasing population, there should be a general turning to 220 MHz for repeater control in the not-too-distant offing.

To begin construction, cut eight lengths of coax from the reel. Each piece should be cut about an inch oversize, then trimmed down later so that all pieces are of exactly the same length. The dimensions given are end-of-braid to end-of-braid for any given length. (See closeup detail in Fig. 3.) The braid-to-braid distance should be approximately the same as the distance between the inner and the outer conductor of the coax you're using, or approximately 1/8 in. This dimension is the only one that does not change with operating frequency or band.

When all the lengths have been cut and trimmed to the precise lengths, and you are sure they will fit together as shown, study Fig. 3 carefully, then tin all exposed braid and conductors. This tinning process is an important step and should be done as completely as you can manage it.

As you solder the lengths together, use care to avoid handling the soldered pieces any more than is absolutely necessary. The braid can pull loose without much encouragement – and when that happens your only recourse is to replace the section with the loose braid. Winding each joint with electrical tape has always worked out well for me, but I always wonder if everything is okay under that tape. Once the tape is applied, you'll just have to guess about the condition of the hidden joint. The best approach would probably be to make all joints first, then inspect the whole antenna.

If everything looks shipshape, then go ahead and wrap the joints with tape. Just be very careful in the handling until the antenna is safely stuffed into its plastic pipe.

The quarter-wave radiator that goes at the top can be any good conductor, but copper is best. And the easiest way to get a good, stiff copper conductor is to buy some narrow-diameter (1/8 in. is ideal) copper tubing. The same material can be used for the radials at the base of the antenna. I *have* used type TW soft-drawn copper wire (10-gage), but it has proved too flexible for applications involving remote mounting – such as at distant repeater sites. The tubing offers a great deal better stability. If you have a heavy-wattage soldering iron or gun, you'll have excellent results soldering the tubing, too – even though you'll probably have to file or scrape the parts where solder is to be applied.

Ground Radials

There is nothing sacred about the manner in which the radials are attached to the antenna. Figure 4 shows the system I used, which worked but had a rather ugly look about it. K6VBT built one and used an arrangement of his own that looked


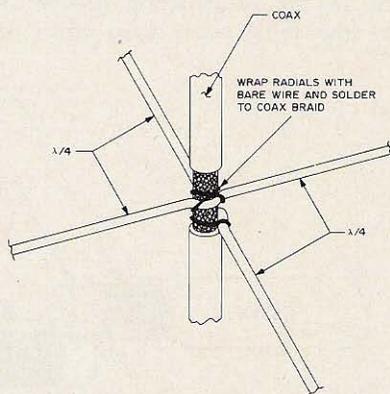


Fig. 4. Radials, of narrow-diameter copper tubing, should be cut to slightly longer than a half wavelength. The center should be bent to conform to the rounded shape of the coax braid so that on each radial a quarter-wave length extends outward from the coaxial braid. Tin the braid first. After wire-wrapping and soldering, wrap the joint well with electrical tape.

**IF YOU'VE
EVER
USED
A
REPEATER,**

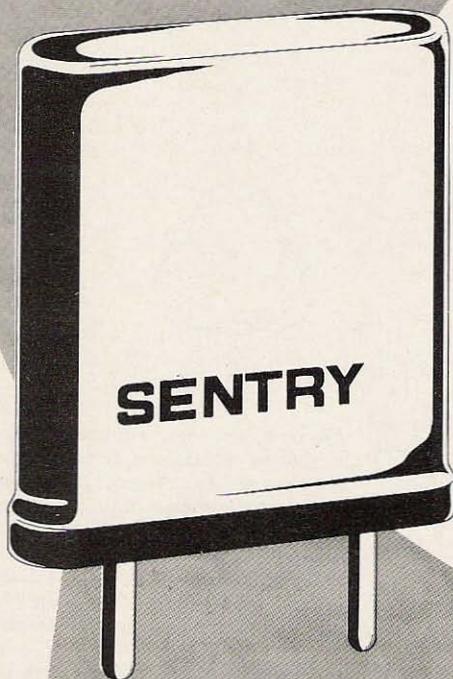

**YOU'VE USED A
SENTRY CRYSTAL**

If you haven't
already received
a copy of our **NEW**
1971 Catalog of Precision
Quartz Crystals & Electronics
for the Communications Industry,
SEND FOR YOUR COPY TODAY!

Somewhere along the line, in virtually every ham repeater in the world, you'll find a couple of Sentry crystals.

Repeater owners and FM "old-timers" don't take chances with frequency—they can't afford to. A lot of repeater users depend on a receiver to be on frequency, rock stable...in the dead of winter or the middle of July. The repeater crowd took a tip from the commercial "pros" a long time ago—and went the Sentry Route.

That's one of the reasons you can depend on your local repeater to be there (precisely there) when you're ready to use it. FM'ers use the repeater output as a frequency standard. And for accuracy, crystals by Sentry are THE standard.

**IF YOU WANT THE BEST,
SPECIFY SENTRY CRYSTALS.**

*"Ask the Hams and Pros
Who Build Repeaters!"*



SENTRY MANUFACTURING COMPANY
Crystal Park, Chickasha, Oklahoma 73018

PHONE: (405) 224-6780
TWX-910-830-6425

much more professional – but his required a lot more work and some rather precision drill work in the PVC pipe. The idea is to get four 19 in. radials extending equilaterally away from the antenna while maintaining some structural integrity. If the concept of Fig. 4 is adopted, the slot arrangement of Fig. 5 will hold things together satisfactorily.

The slots (Fig. 5) are cut lengthwise into the bottom of the PVC pipe so that the radials can be held in place when the PVC is inserted into the mounting pipe (made of heavy metal). The metal pipe is notched gently to seat the radials. Before

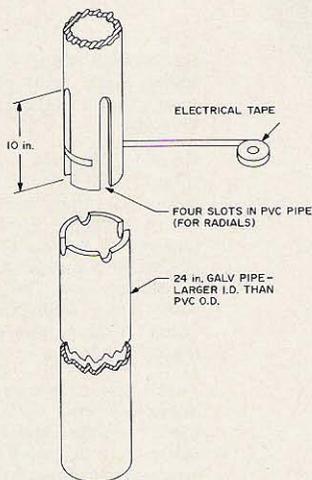


Fig. 5. Long slots in the PVC pipe will hold the radials in place with the antenna inserted. Wrap the bottom well with electrical tape after the antenna is installed in the fiber tube. Notch four matching places on a 2 ft length of galvanized pipe to seat, and try for a snug fit.

inserting the PVC into the larger pipe, the slots on the PVC should be taped up (after the antenna is installed in the PVC sheath, of course).

Building your own gain antenna is a lot of trouble, as you can readily see. But it looks pretty attractive when you start pricing the commercial equivalents. And there is an almost indescribable satisfaction that comes with putting out a good "commercial quality" signal from a homebrew antenna.

One Last Note

If your repeater doesn't give omnidirectional

coverage, or if you'd rather have a definite preplanned radiation pattern, you can get considerably more gain than the 5.8 dB already promised by merely spacing the antenna a prescribed number of quarter wavelengths from the tower. Of course this means that your antenna will have to be side-mounted rather than top-mounted. If you space the antenna one quarter-wave from the tower, you'll get a major lobe in the same direction as the antenna is from the tower mass, as shown in Fig. 6A. Each additional quarter-wave essentially adds a lobe that exceeds the 5.8 dB omnidirectional reference point.

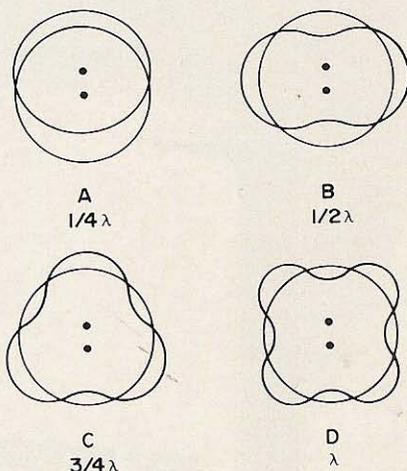


Fig. 6. By spacing the antenna the proper number of quarter wavelengths, some interesting radiation patterns can be obtained. In the patterns shown, the circles represent the 5.8 dB omnidirectional gain achieved by top-mounting. The asymmetrical overlays represent the patterns obtained by side-mounting. Note that even though signal loss occurs in some directions, significant gain improvement is realized in other areas.

Playing around with antenna-to-tower spacing can help you spend a jolly afternoon at your repeater site – which can be great fun when compared with painting the fence or fixing the wife's vacuum cleaner. So grab yourself a hunk of coax or two and get started on the antenna. Then take a good look at a map of your area and see if you can't improve your repeater's efficiency by some selective mounting techniques.

...K6MVH■

DIRECTORY OF FM SUPPLIERS, MANUFACTURERS, DEALERS

The number in parentheses following listings in bold-face type is the page of this issue on which the company's ad appears.

ANTENNAS

- Antenna Specialists
12435 Euclid Ave.
Cleveland OH 44106
Mobile
- Avanti Research & Dev.
33-35 West Fullerton
Addison IL 60101
- ComProd (Phelps Dodge)
Route 79
Marlboro NJ 07746
Mobile & Base
- Cush Craft
621 Hayward St.
Manchester NH 03103
Mobile & Base
- Decibel Products
Mobile & Base
- Dy Comm (Dynamic Communications, Inc.)**
301 Broadway
Riviera Beach FL 33404
Base (65)
- Gam Electronics
191 Varney St
Manchester NH 03301
Mobile & Base
- Gilian & Co.
105 Orchard St
Watertown MA 02172
Base
- Gotham
1805 Purdy
Miami Beach FL 33139
- Hy-Gain Electronics
8406 N.E. Highway 6
Lincoln NB 68501
Base
- Larsen Electronics
11611 N.E. 50th Ave.
Vancouver WA 98665
Mobile
- Mosley Electronics
Bridgeton MO 63044
Mobile
- Motorola, Inc. (Cover III)**
Semiconductor Prod. Div.
P.O. Box 20924
Phoenix AZ 85001
Mobile
- New-Tronics Corp.
15800 Commerce Park Dr.
Brook Park OH 44142
Mobile

- Prodelin
Hightstown NJ 08520
Base
- Shakespeare
Jefferson Square
Box 246
Columbia SC 29202
Mobile
- Swan Antenna Co.
646 N. Union St.
P.O. Box 1122
Stockton CA 95201
Base
- Telrex (31)**
Asbury Park NJ 07712
Base

CRYSTALS

- American Crystal Co. (76)**
1623 Central Ave.
Kansas City KS 66102
Amateur
- Bomar Crystal Co.
201 Blackford Ave.
Middlesex NJ 08846
Amateur
- International Crystal*
10 N. Lee
Oklahoma City OK 73102
Commercial & Amateur
- Jan Crystals (82)**
2400 Crystal Dr.
Fort Myers FL 33901
Amateur
- K-W Industries*
Box 508
Prague OK 74864
Amateur
- Midwest Crystal
1516 Parkwood Rd.
Cleveland OH 44107
Amateur
- Savoy Electronics
Box 7127
Fort Lauderdale FL 33304
Amateur
- Sentry Manufacturing* (Cover II)**
Crystal Park
Chickasha OK 73018
Commercial & Amateur

*Specializing in crystals for amateur/commercial FM units.

Shepherd Industries Inc.
8106 Santa Fe Dr.
Overland Park KS 66202
Texas Crystals
1000 Crystal Dr.
Fort Myers FL 33901
Commercial & Amateur

CAVITIES/DIPLEXERS

Decibel Products
Sinclair Radio Labs
Box 23
Tonawanda NY 14150

PUBLICATIONS

Radio Amateur's FM Repeater Hdbk
Howard W. Sams & Co.
4300 W. 62nd St.
Indianapolis IN 46268
FM Repeater Circuits Manual (70)
73 Magazine
An Introduction to FM (70)
73 Magazine
FM Anthology (Vol. I) (70)
73 Magazine
The Best of FM (Anth. Vol. II) (70)
73 Magazine
Repeater Atlas (70)
73 Magazine
FM Schematic Digest (92)
Sherman Wolf Two-Way Engineers
1100 Tremont St.
Boston MA 02120
GE Schematic Digest
General Electric Co.
Schenectady NY

PREAMPS

Crawford Electronics (87)
301 West Main St.
Genoa IL 60135
K-N Electronics, Inc.
107 Moorewood Ave.
Avon Lake OH 44012
Topeka FM Engineering
3501 Croco Road
Topeka KS 66605
Vanguard Labs (21-74-81)
196-23 Jamaica Ave.
Hollis NY 11423

REPEATER ID UNITS

Curtis Electro Devices
Box 4090
Mountain View CA 94040

Hal Devices (76-86)
P.O. Box 365A
Urbana IL 51801

RF AMPLIFIERS

Dy Comm (Dynamic Communications, Inc.)
301 Broadway
Riviera Beach FL 33404 (53)
Erickson Electronics
4657 N. Ravenswood Ave.
Chicago IL 60640
Galaxy Electronics
10 South 34th St.
Council Bluffs IA 51501
Newsome Electronics
19675 Allen Road
Trenton MI 48183
Scientific Radio Systems
401 Lyell Ave.
Rochester NY 14606
Varitronics Inc. (54-55)
4109 No. 39th St.
Phoenix AZ 85018

SCANNERS

Aerotron Inc. (36)
P.O. Box 6527
Raleigh NC 27608
Electra Corp. (61)
Cumberland IN 46229
Gonset, A Div. of Aerotron Inc.
P.O. Box 6527
Raleigh NC 27608
George D. Griffin
322 W. State St.
Ithaca NY 14850
Kris, Inc.
1026 B S. Washington Ave.
Cedarburg WI 53012
Regency Electronics, Inc. (47)
7900 Radio Row
Indianapolis IN 46226
Unimetrics Inc.
23 West Mall
Plainview NY 11803

SURPLUS

C & A Enterprises
2529 East Carson St.
Long Beach CA 90810
DuPage FM
Box 1
Lombard IL 60148
FM Ham Sales
Box 1574
Fort Worth TX 76101
Fair Radio Sales (92)
Box 105
Lima OH 45802



Standard's New High Flying "826"

Standard Communications, the world's largest manufacturer of VHF marine equipment, has developed a professional quality VHF/FM 2 metre transceiver especially for amateur use. The "826" is so compact that it makes mobile installations practical in almost any airplane, boat or car, and it becomes fully portable with Standard's battery pack. When used in conjunction with the AC power accessory, it also makes an ideal, low cost base station unit. Enjoy the fun of amateur radio communication wherever you go for just \$339.95



**STANDARD
COMMUNICATIONS CORP.**

P.O. Box 325, Wilmington,
Calif. 90744 (213) 775-6284

The world's largest manufacturer of marine VHF equipment.

Gregory Electronics Corp.
249 Route 46
Saddle Brook NJ 07662
Mann Communications (57)
18669 Ventura Blvd.
Tarzana CA 91356
Newsome Electronics
19675 Allen Road
Trenton MI 48183
Spectronics Inc.
1009 Garfield St.
Oak Park IL 60304

TEST EQUIPMENT

Cush Craft
621 Hayward St.
Manchester NH 03103
Gertsch (The Singer Co.)
3211 So. La Cienega Blvd.
Los Angeles CA 90016
Heath Company (79)
Benton Harbor MI 49022
Hewlett-Packard
Lampkin Laboratories, Inc.
8400 Ninth Ave. N.W.
Bradenton FL 33505
Measurements
Motorola Inc. (Cover III)
Semiconductor Prod.Div.
P.O. Box 10924
Phoenix AZ 85001
Pathcom Inc.
24049 S. Frampton Ave.
Harbor City CA 90710
Perfection Elect. Products
404 E. Harrison
Royal Oak MI 48067

TONE ENCODERS/DECODERS


Alpha Electronic Serv. (62)
8431 Monroe Ave.
Stanton CA 90680
Communication Specialists
P.O. Box 293
Brea CA 92621
Digitone (81)
Box 116
Portsmouth OH 45662
Federal Sign & Signal Corp.
136th & Western Ave.
Blue Island IL 60406
Mann Communications (Silent Sentry) (57)
18669 Ventura Blvd.
Tarzana CA 91356
Riggins Electronic Sales
2331 San Anselme
Long Beach CA 90815
Ross & White Co.
50 West Dundee Road
Wheeling IL 60090

TRANSCIVERS

Aerotron Inc. (36)
P.O. Box 6527
Raleigh NC 27608
Canadian Marconi Co.
Marine & Land Com. Div.
2442 Trenton Ave.
Montreal 16 P.Q. Canada
E. T. Clegg Associates, Inc. (69)
Littell Road
E. Hanover NJ 07936
Communication Company, Inc.
P.O. Box 520
Coral Gables FL 33134
R. L. Drake Co. (Cover IV)
540 Richard St.
Miamisburg OH 45342
Dumont Communications
78 Hammarlund Drive
Mars Hill NC 28754
Galaxy Electronics
10 South 34th St.
Council Bluffs IA 51501
Henry Radio (Tempo) (19)
11240 W. Olympic Blvd.
Box 64398
Los Angeles CA 90064
931 No. Euclid
Anaheim CA 92801
Butler MO 64730
New York area: J. Richardt W2WIY
Houston area: J. Carman W5SBX
E. E. Johnson Co.
Waseca MN 56093
Kaar Electronics Corp.
2250 Charleston Road
Mountain View CA 94040
Radio Corp. of America
Mobile Com. Prod.
Front & Cooper St., Bldg 2-3
Camden NJ 08102
Regency Electronics, Inc. (47)
7900 Radio Row
Indianapolis IN 46226
Sideband Engineers
Simpson Electronics
2293 N.W. 14th St.
Miami FL 33125
Sonar Radio (35)
73 Wertman Ave.
Brooklyn NY 11207
Standard Communications (51)
640 E. 219 St.
Torrance CA 90502
Swan Electronics Corp.
305 Airport Road
Oceanside CA 92054
Telecomm Electronics (33)
Box 461
Cupertino CA 95014
Varitronics Inc. (54-55)
4109 No. 39th St.
Phoenix AZ 85018

NOW!

at last:

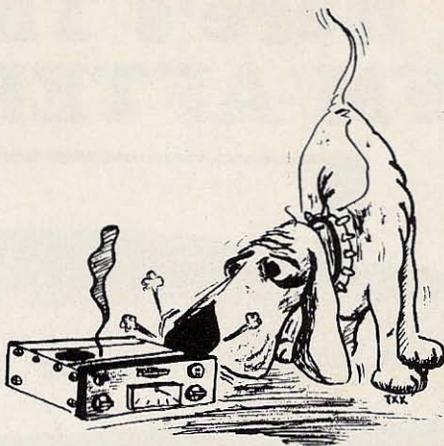


Dycomm offers the most useful trouble shooting tool since the SIMPSON 260; The Dycomm RF "SNIFF-IT". "If you can smell RF you got it licked!"

This item enables anyone to follow the RF PATH in a multiplier chain or other RF source.

Just plug it into your present multimeter and trace RF from BC to UHF. The SNIFF-IT will display relative RF (from 1 mW to 250 W) output on your VOM, in volts.

Use it to trace RF in:

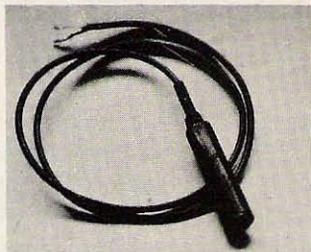- Multipliers
- I. F. Strips
- Tune to peak transmitters
- Relative RF output power
- Antenna loading/field strength



Have you ever wanted to peak up your 1.8 through 450 MHz transmitter without a wattmeter:

The Dycomm "SNIFF-IT" enables you to "DO-IT". Just place the "SNIFF-IT" near the RF source and where it stops is where the trouble is. When tuning for maximum power into a load just tune for max reading on your VOM.


The "SNIFF-IT" does not appreciably load the circuit even if placed in a tuned circuit.

Price only \$5.00 cash, check or money order.

Same day order in - shipment out. Guaranteed to work or your money back.

DYCOMM PO BOX 10116 RIVIERA BEACH FLA.

Here's The Mobile FM AFTERBURNER

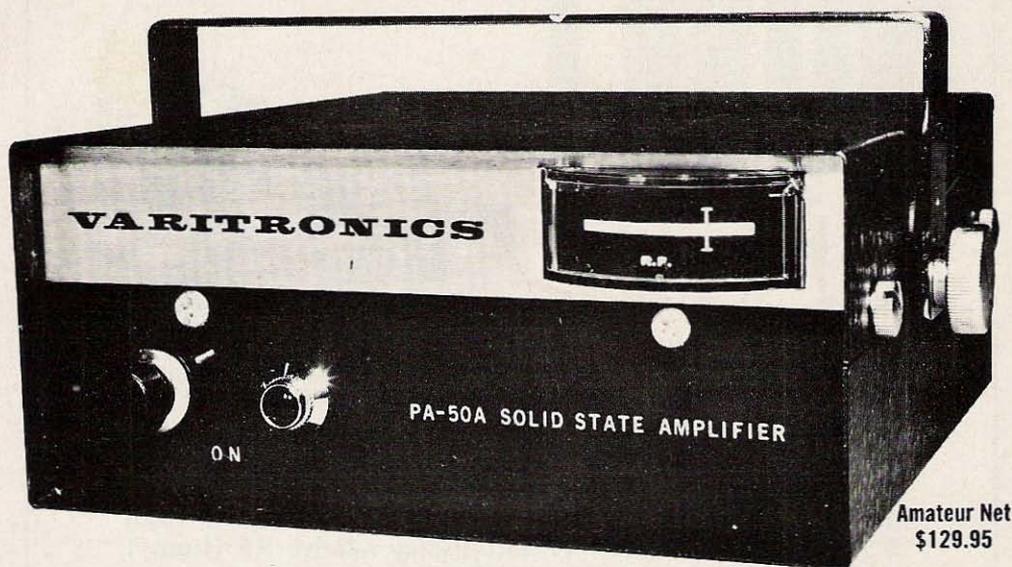

Delivers 50 Watts of Punch on 2 Meter FM

The Varitronics PA-50A is a completely solid state Class C RF amplifier designed specifically for use in mobile amateur FM applications. Internal RF switching makes the PA-50A useable with any amateur FM transceiver with 10 watts* output. Balanced emitter devices are employed which are completely insensitive to high VSWR or even no load conditions at its output. This handsome and ruggedly built amplifier is styled like the IC-2F transceiver, features a calibrated output meter and is supplied with mobile mounting bracket and DC cord. For the big signal on FM, try it!

SPECIFICATIONS

*Drive Requirements . . .	12 Watts Maximum 5 Watts Minimum
RF Output	50 Watts - Less with lower drive or input voltage
Power Requirements . . .	13.5 VDC @ 5Amps
Impedance	50 Ohms In/Out
Frequency	Any Portion of Amateur 2 Meter Band
Spurious Products	50DB Down
Dimensions	6" X 7" X 2"

Manufactured by Varitronics . . . still the leaders in quality amateur FM equipment.

See it at your dealers.

VARITRONICS INCORPORATED

2321 EAST UNIVERSITY DRIVE • PHOENIX, ARIZONA

WHAT'S BLACK AND GREY, WEIGHS TWO POUNDS AND TALKS IN AN ELEVATOR SHAFT?

An HT-2!

Varitronics' new 2 meter FM walkie-talkie •
Works anywhere • Super hot receiver • 1.6 or
more watts out • Ni-cads and charger sup-
plied • Only \$249.95


See it at your dealer

VARITRONICS INCORPORATED

2321 E. University Dr. • Phoenix, Arizona 85034

DESKTOP BASE STATION

from MOTOROLA G STRIPS

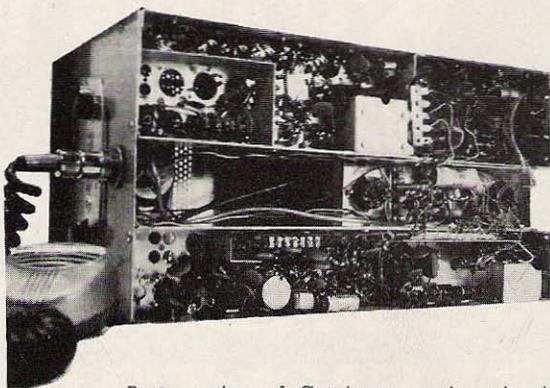

Chuck Klawitter W9VZR
4627 North Bartlett Ave.
Milwaukee WI 53211

Bottom view of G-stripper, receiver chassis at the top, conversion chassis in the middle, transmitter chassis at the bottom. Note the compactness of the unit; it makes a neat 15 x 7 $\frac{3}{4}$ x 5 $\frac{1}{4}$ in. station.


There have been a large number of manufacturers making equipment for the 2 meter FM enthusiast; but a lot of interest has also been generated on 6 meters and 10 meters. Yet, there is no newly manufactured equipment specifically designed for these frequencies. The only logical route for amateur radio operators is commercial surplus low-band equipment. (Low-band FM gear generally covers 25–50 MHz.)

After having tried several different types of equipment and methods of conversion, I will report to you my results with constructing 6- and 10-meter base stations. My concern for this equipment was compact size so that it would be compatible with my present SSB exciter and would fit comfortably on my desk. And the equipment had to be attractive enough so that my wife wouldn't try to get rid of it every time I left the house.

Receiver sensitivity and transmitter output should be compatible with present-day standards. The units should be flexible enough in design to allow multi-frequency operation, remote control, and tone operation. Finally, it must be inexpensive.

How was this vast list of specifications finally filled? With "G" strips — those

compact units which made possible such units as Motorola's T41GGV or U51GGT. These units are only 15 in. long and around 3 in. wide. They have become available separately, as strips rather than mobile units, through Mann Communications* at a combined price of \$28. Considering that surplus base stations using these strips are not available for less than \$150, this seems to make these strips a good deal for the amateur with a little time and an old TV power transformer for an ac power supply.

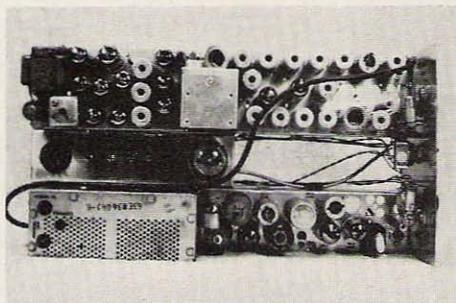

Top view of G-stripper; receiver chassis is at the top. Note the placement of components on the conversion chassis—from left to right, octal power plug, speaker jack, and voltage regulator for the transmitter oscillator.

*Mann Communications, 18669 Ventura Blvd.,
Tarzana CA 91356.

NEW!

120 WATTS FM MOBILE

AS-IS IN ORIGINAL FACTORY CARTON
120 WATTS OUTPUT 148-174 MHz
CAPABLE OF UP TO 6 FREQ OPERATION
FULLY SOLID STATE EXCEPT 8624 FINAL
STANDBY BATTERY DRAIN 0.25 AMPS.
FULLY NARROW BANDED

These units are KAAR Model DT 76 and are sold as-is less crystal and crystal oven. Manuals will be included. No factory warranty.

This mobile unit is a must for the power conscious amateur who wants a brand new 2 meter rig. All units are sold on a first-come-first-served basis. Don't be shut out; order now while they last.

Kaar Model DT 76 complete with accessories\$349
6 Freq kit (less xtals and ovens)\$ 39

We also handle clean used equipment. Write for free catalog.

Mann Guarantee

Money refunded without question if equipment is returned within seven days from shipment, undamaged, freight prepaid.

Conditions of Sale

Unless otherwise specified, equipment is used, and is sold as-is. All items shipped FOB Tarzana, California. Crystals, ovens, antennas not included unless specifically stated in catalog. All equipment is sold on a first-come, first-served basis.

Mann COMMUNICATIONS

18669 Ventura Blvd.
Box 138 Tarzana, CA 91356
(213) 342-8297

2837 North 24th Street
Phoenix, Ariz 85008
(602) 955-4570

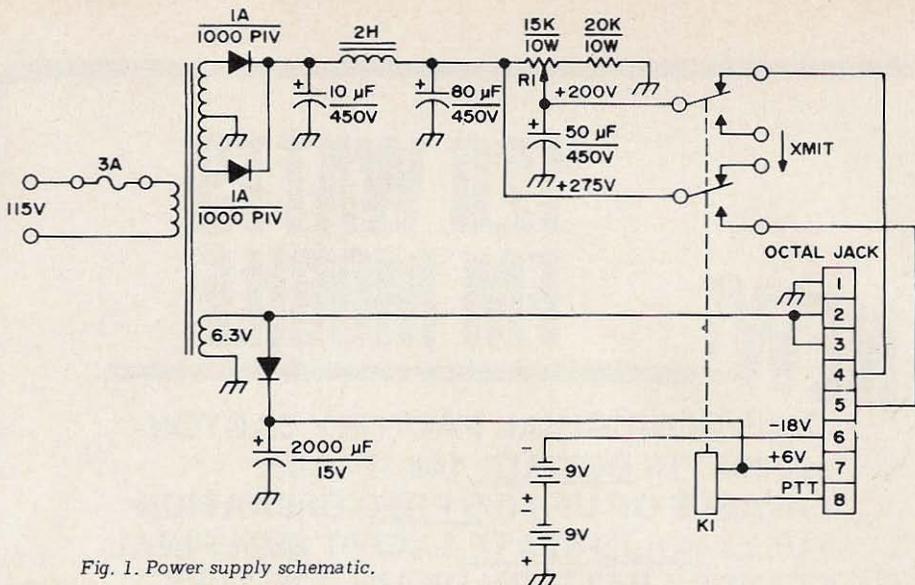


Fig. 1. Power supply schematic.

The power supply (Fig. 1) can be constructed on a separate $2\frac{1}{2} \times 5 \times 13$ in. aluminum chassis so it can be placed remotely. This helps keep the desktop package compact and eliminates a lot of unnecessary heat in the transceiver cabinet. The power supply contains the TV power transformer, high-voltage rectifying and filtering components, bias supply, filament supply, transmit-receive relay, and control voltages. Layout of this chas-

sis is not difficult; work for best mechanical design and easy wiring.

The conversion chassis (Fig. 2) is placed between the receiver and transmitter. It replaces the old mobile power supply. This chassis contains tie points for connecting various receiver and transmitter functions, a standard phone jack for the speaker, voltage regulator tube, octal power plug, and accompanying components. Four groups of 6-32 hardware

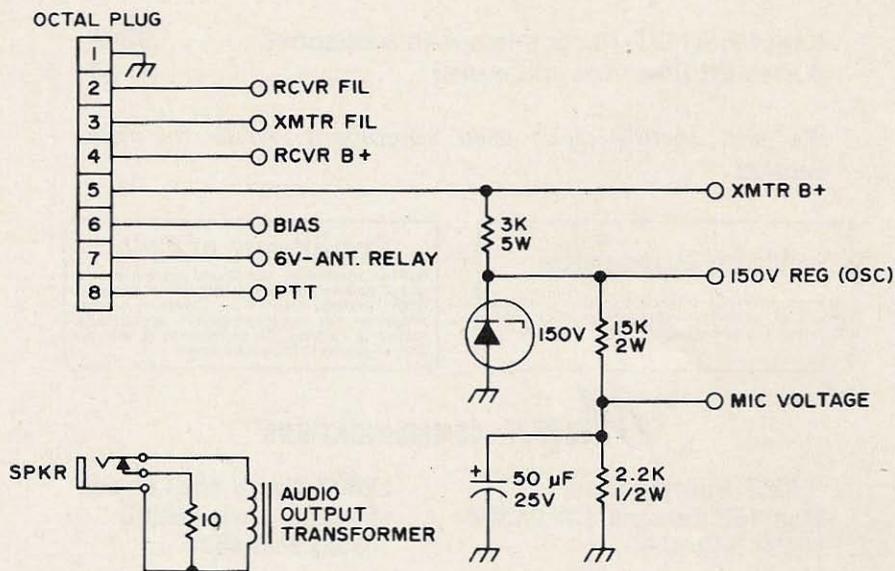


Fig. 2. Conversion chassis schematic

are used to hold the three chassis together. The conversion chassis was made of scrap aluminum about 1/16 in. thick. The mechanical layout for this chassis is shown in Fig. 3.

The front panel is also constructed from scrap aluminum. The front panel layout is shown in Fig. 4. An escutcheon from a Motorola control head will dress up the unit considerably and the components from the control head can be used in the front panel. The front panel is easily mounted because the fronts of the strips are drilled and tapped for 6-32 hardware. Four 6-32 binder head screws will securely attach the front panel to both the transmitter and receiver strips also adding a great deal of mechanical stability. The schematic for the panel elements is shown in Fig. 5.

Electrical Considerations

Fortunately, schematic diagrams are easily available for these units. The *FM Schematic Digest** not only contains the schematics for this equipment, but other helpful information for servicing, alignment, and ordering the proper crystals.


The power supply is built around an old TV power transformer which has been a fine choice in that the price is right and



Simple U-shaped cabinet is made of scrap aluminum. The speaker is mounted behind the perforated part of the cabinet at the top front of the cabinet. Choose your own color combinations, and refinish mike to match unit.


the power supply is very flexible. I have built three of these units and have used a different transformer each time with excellent results. In reference to Fig. 1, note that R1 can be adjusted to deliver 200V under load to the receiver.

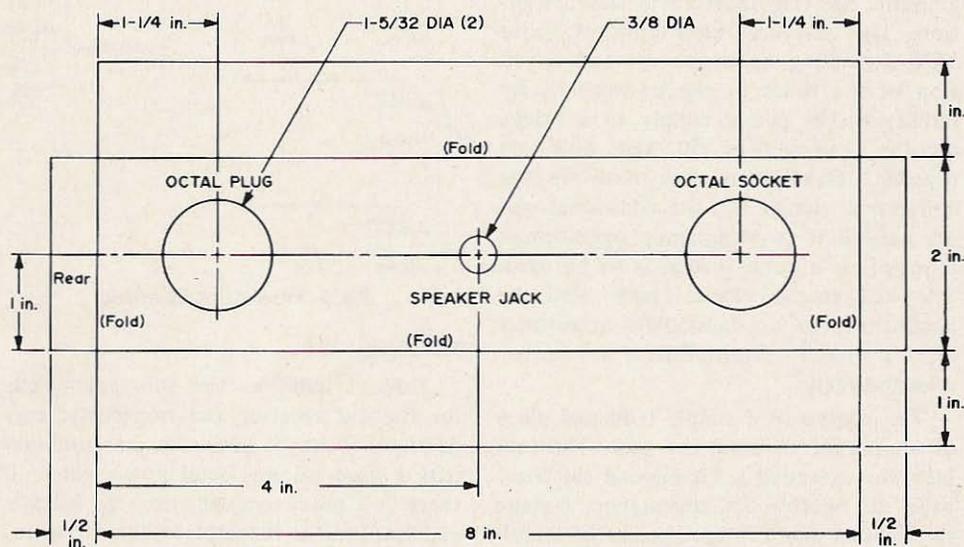The conversion chassis is primarily needed because when these strips were in their original mobile unit, the receiver and transmitter were not connected by plugs, but were wired together in manufacture. The conversion chassis serves as a place to connect the cut ends of the strips and a



*Sherman Wolf, Two-Way Radio Engineers, 1100 Tremont St., Boston MA 02120.

Fig. 3. Conversion chassis flat pattern layout.

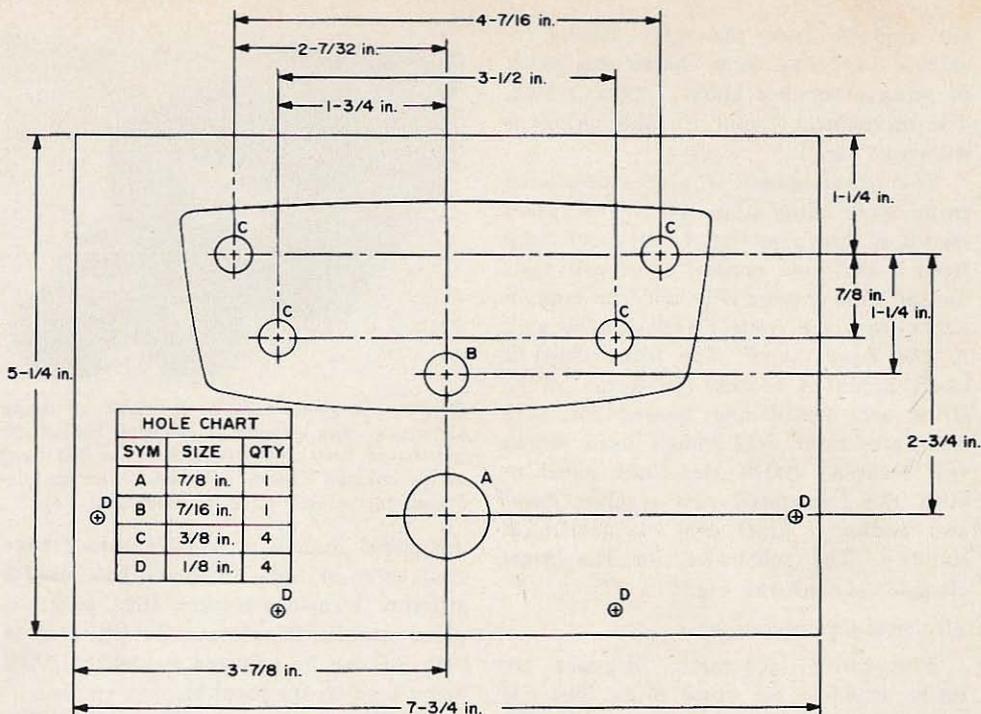

NOTE: POSITION OF "D" HOLES MAY VARY WITH DIFFERENT STRIPS.

Fig. 4. Front panel layout.

place for the power plug and speaker jack. The screen and plate of the final amplifier are tied together in this conversion. This produces an output of about 15W depending upon the age and condition of the tubes in the transmitter. By modifying the power supply to a bridge rectifier, outputs of 50 and 60W are possible. There is enough room in the conversion chassis for the additional wiring needed if two-frequency operation is required or a tone system is to be used. The conversion chassis may also be lengthened to accommodate accessories like a mike preamplifier or carrier-operated relay.

The cabinet is a simple U-shaped piece of aluminum covering the unit. The cabinet was extended a bit beyond the front panel to improve its appearance. I made the cabinet out of three pieces of aluminum bolted together. I used solid pieces for the sides and a perforated piece for the top.

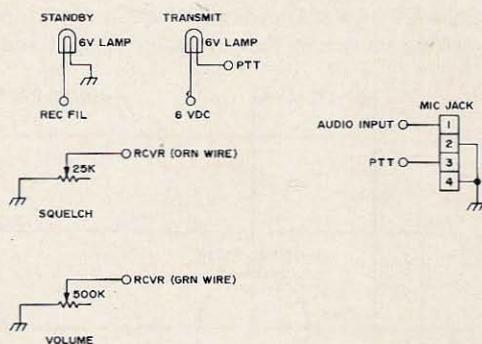


Fig. 5. Front panel schematic.

Miscellany

Table I indicates the wire color code for the cut receiver and transmitter connections. Table II gives the pin functions that I used on my octal power cable. If there is a heavy enough wire, the receiver and transmitter filament leads can be tied together. This will give you an extra connection for an additional function. An 11-pin socket can be used for more

HEAR ALL THE REPEATERS ALL THE TIME!



9" wide x 4" high
Patent No. 3,531,724

on the  **BEARCAT**
FIRST AND FINEST
Scanning Monitor Receiver

Continuously scans from 1 to 8 FM channels you select.
You can hear the local repeaters
As well as

POLICE • SHERIFF • WEATHER • CIVIL DEFENSE
FIRE • BUSINESS • UTILITY • MARINE • ETC.

The Bearcat takes you where the action is! Just turn it on and it searches for the first active channel . . . stops for any transmission . . . then resumes search. Red lights flash as channels are scanned . . . steady light indicates active channel. Switches let you select channels of greatest interest. Transistorized circuitry with plug-in crystals. Front-mounted speaker makes it ideal for table, desk, bedside, car or boat. U.S. made. Full one-year warranty. Get the original. Get the Bearcat.

AM Aircraft Band Model Also Available


FROM **\$139.95** PLUS CRYSTALS @ **\$5.00** EACH

AT BETTER DEALERS EVERYWHERE

ELECTRA CORPORATION • CUMBERLAND IND 46229

NEW... SUB-AUDIBLE TONE ENCODER

THE ALPHA QT-5

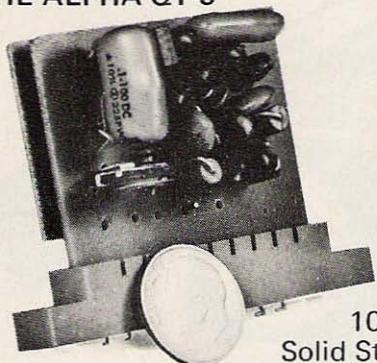

100%
Solid State
No Reeds Required

The ALPHA QT-5 Sub-Audible Continuous tone encoder comes complete with IC Frequency Network, and Installation Instruction Book.

When ordering specify tone frequency desired (67.0 to 203.5 cps) and the radio model to be used.

QT-5 ASSEMBLED \$63.60
QT-5 KIT FORM \$46.40

ALPHA Sub-Audible Tone Products are the most widely used add on tone accessories in the world.

ALSO AVAILABLE FROM ALPHA...


QT-10 Encoder/decoder
RCP-760 Multi-tone panels
PA-100 UHF 100 Watt Amplifier



ALPHA ELECTRONIC SERVICES

8431 Monroe Ave., Stanton Cal. 90680
714 - 821-4400

radio amateur callbook

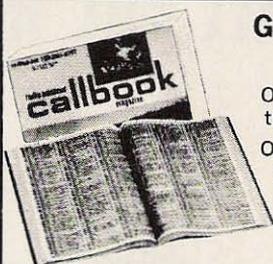

**GET YOUR NEW
ISSUES NOW!**

Over 285,000 QTHs in
the U.S. edition **\$8.95**

Over 165,000 QTHs in
the DX edition **\$6.95**

**NEW EDITION EVERY:
MARCH 1 - SEPT. 1
JUNE 1 - DEC. 1**

These valuable EXTRA features included in both editions!

- QSL Managers Around the World!
- Census of Radio Amateurs throughout the world!
- Radio Amateurs' License Class!
- World Prefix Map!
- International Radio Amateur Prefixes
- Prefixes by Countries!
- Zips on all QTH's!
- A.R.R.L. Phonetic Alphabet!
- Where To Buy!
- Great Circle Bearings!
- International Postal Information!
- Plus much more!

See your favorite dealer or order direct (add 25¢ for mailing in U.S., Possessions & Canada. Elsewhere add 50¢).

**WRITE FOR
FREE
BROCHURE!**

RADIO AMATEUR



callbook INC.

Dept. B 925 Sherwood Drive
Lake Bluff, Ill. 60044

flexibility and control of power functions.

Table I - Lead Identification Connections

Function	Color Code
6.3V ac Filament	Brown
Rcvr fil return-ground	Green with yellow stripe
Rcvr + 200V	Red
Rcvr audio control	Green
Squelch control	Orange
Xmtr audio and shield	Green shielded cable
Mike dc	Green with white stripe
Xmtr 150V dc	Red with black stripe
Xmtr 275V dc	Red with yellow stripe
PA screen	Orange
PA plate	Red with blue stripe
Bias	Green with red stripe
Xmtr fil return-ground	Brown with yellow stripe

Table II - Power Cord Connections

Pin Number	Function
1	Common-Chassis ground
2	Receiver Filament
3	Transmitter Filament
4	Receiver B+
5	Transmitter B+
6	Bias
7	6 or 12V dc
8	Control-push to talk

Some of the strips I have worked with have a disease called "hardening of the insulation." In case this should cause you any problems, it will be helpful to replace the wiring from the transmitter and receiver tie strips to their respective tie points in the conversion chassis. Carefully check wires in the strips that run tight against the chassis for shorts. . . .W9VZR■

Jack Taylor W4CWB
2400 N. Quantico St.
Arlington VA

CAMOUFLAGE EXTRA CLASS

This article is dedicated to K9AZG* and all hams who desire to improve the state of the art but must cope with XYL-itis in erecting beam antennas. The plans that follow are foolproof and allow you to assume control. However, the author assumes no responsibility for their success because his XYL won't let him.

Plan I.

Jack threw the big switch. Between the QRN from an impending storm and the impotent signal generated by his attic antenna it had been a most frustrating evening.

"I just can't get out," he mused.

The lone QSL card from W2NSD/1, obtained "eyeball" at the '58 ARRL Convention, some samples from printers, and an SWL card from a boy scout on the next block bore mute testimony of the fact.

"Damned females and their sense of esthetics, if only I could put up a beam,"

*See article by K9AZG entitled "Camouflage" October 1970 issue of 73

and as an afterthought, "and still keep peace with the XYL."

A rumble of distant thunder heralded the arrival of the storm. Quickly he made a phone call, yawned most audibly and to the XYL upstairs he called, "Nancy, let's turn in, I'm bushed."

The storm broke — successive flashes of light penetrated the shuttered darkness of the bedroom. Each flash being followed by a sharp clap of thunder that rattled and reverberated throughout the house.

"A thousand and one, a thousand and . . ."

"Jack, stop that," cried Nancy, "I'm scared enough as it is." "Did you turn off that dumb radio?" "Yeah, yeah," responded Jack, giving her a reassuring hug, "now try to get some sleep."

Jack awoke the next morning to streamers of sunlight stealing through the blinds, the aroma of breakfast coffee and a loud resounding knock on the front door. Nancy answered it. A man with a charred brick in his outstretched hand framed the entrance way.

"Good morning, m'am, some storm we had last night," he said in way of introduction. "I've been surveying the neighborhood for storm damage - it's my business, you know - lightning protection. You folks had a narrow escape, only lost a brick from your chimney - lucky! Could have been worse."

Jack had heard enough. He stormed toward the door shouting, "I don't believe it - I've heard about you fellows faking damage." He turned to Nancy and said, "I'm going up on the roof and see if a brick really is missing. However, when I get down, I suspect our caller will be the only thing missing."

Nancy appeared embarrassed. The caller appeared hurt but replied, "I'll wait." Ten minutes later a somber Jack faced Nancy.

"The man's right, Honey, a brick is missing!"

To the man: "Come in, Sir, and tell us what we need in the way of lightning protection!"

The man stayed about fifteen minutes - time for his sales pitch, a signed contract and a cup of coffee. After he had gone, they both sighed in nervous relief.

"To think," said Nancy, "we almost lost our house to lightning, when full protection can be had by a decorative flagpole lightning arrestor in the back yard!"

"I feel guilty too, Honey," said Jack, "now that I know my attic antenna contributed to the danger - I'll take it down." He lowered his head. The XYL was responsive, "Don't feel badly, Dear, remember the man said you could put an antenna on the flagpole and it would even increase our protection," she paused - "if you don't mind."

Some weeks later Jack was in QSO:

"K4SGO, this is W4CWB, how copy Marv?"

"W4CWB, this is K4SGO, Q5 S9+20, but cheapskate, when are you going to return the brick I used from my patio fireplace?"

Plan II

Plan II is tailored for a certain breed of impatient hams that will rush to the corner drug store to buy a tube on Sunday night

rather than honorably scrounging same, or who can't wait for the proper climatic conditions to execute plan I. Fortunately, this plan is also foolproof and the XYL can be conned as easily as with the flagpole routine.

Seriously, have you ever seen an XYL that wouldn't like to have a better picture on the "boob tube." Of course you haven't!

And what is the average TV antenna installation? One driven element, fed with cheap 2¢-a-foot transmission line (and one parasitic element). Point out its ugly appearance on the roof! Exercise pride.

Take down this eyesore. Restore the graceful and clean architecture of your home. In extreme cases you can even cut the grass to impress on the XYL your sincerity for the "house beautiful."

Now that this blemish has been removed, buy the largest TV antenna you can find. Some of them are really massive. Be sure to assemble it in the living room, where it must remain (under any pretext) for at least 24 hours. This is important because you are psychologically conditioning the XYL to size. Be sure that the carton identifying the monstrosity as a TV antenna remains there, too.

Next, install the antenna on a tower that will later also support your beam. Be sure to mount the TV antenna at suitable height for good reception (but reserve the top spot for you-know-what!); then feed the antenna with high grade transmission line. The XYL will be both amazed and proud of her improved TV picture. Your image will improve too. She may even tell her mother that maybe her marriage wasn't a mistake after all.

Now for the ultimate camouflage! On the chosen day encourage the XYL to go on a little shopping spree. Now do your thing! Upon her return she will voice little or no opposition to your beam which incidentally will appear smaller (than hers) on top of the tower!

Plan III

Truly, this is for desperate cases, so upon request we will mail in plain brown wrapper . . .

...W4CWB■

Notice to all FMers:

Your DYCOMM BOOSTER is compatible with all available FM rigs.

IT INCREASES YOUR EFFECTIVE COMMUNICATIONS RANGE

JUST INSERT BETWEEN
TRANSCIVER AND ANTENNA
AND APPLY 12-14VDC.

101-500C
"FM BOOSTER"
4-12W IN,
12-30W OUT!




SIZE: 3 x 4 x 4"

\$59.95

101-500D
"BLOCK BOOSTER"
5-15W IN,
30-55W OUT!
SIZE: 3 x 4 x 6"

\$89.95

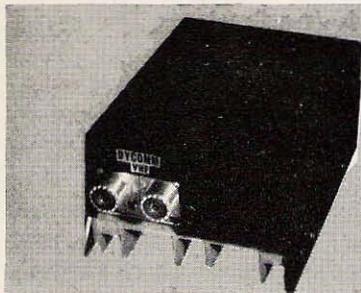


101-500E
"BRICK BOOSTER"
1-3.5W IN,
10-30W OUT!
SPECIAL



\$69.95

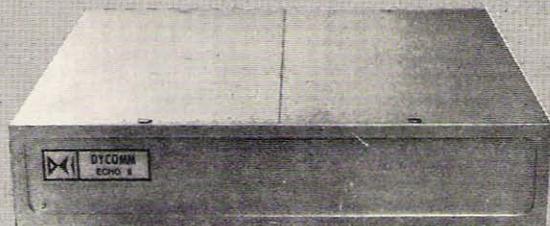INTRODUCING THE
DYCOMM 100 SIZE: 4 x 5 x 8"
"TEN-0" \$185.00
8-10W IN, 12-13V
100-150W OUT!!
NOTHING LIKE IT ANYWHERE
(Allow 3-4 weeks delivery.)



DYCOMM ECHO II repeater

*Then there's our NEW
4-channel
100-150W
remote-controllable
2-meter transmitter:*

COMPLETE, WITH MIKE,
CABLING, CRYSTALS,
12V OPERATION
5 x 8 x 12"
Delivery 2-3 weeks

\$325


Dynamic Communications, Inc.

948-A Avenue E
Riviera Beach FL 33404
(305) 844-1323

FILE BOX

Transistor Beta Tester

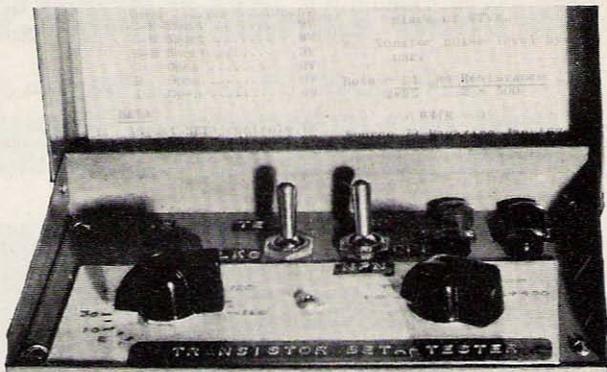Samuel C. Milbourne WB4ITN
4624 Daugette Drive N.W.
Huntsville AL 33805



Previous articles described two test units in a line of "file box" test equipment, so called because they all are housed in metal file boxes sold to hold 4 x 6 in. file cards.

This month, we have a convenient *transistor beta tester*. As Thorp¹ describes it, the main tests required to determine the adequacy of a transistor are:

1. Determine if NPN or PNP type.
2. Check for short between collector and emitter, collector and base, or base and emitter.
3. Look for open collector, base, or emitter.
4. Check the relative leakage of the transistor.
5. Determine the transistor beta (current gain).
6. Monitor the relative noise level by ear.

Previous design allowed testing of beta to 150. However, higher scale readings were noted and a range switch of plus 100, 200, 300, and 400 was added. By using this equation a fairly accurate tester will result (Fig. 1).

$$\beta = \frac{R4}{2 \times R5}$$

$$R4 = 150 \text{ k}\Omega$$

$$R5 = 500 \Omega$$

Let us assume that we will vary R4 until the dc voltage V_e equals 2V. The resulting

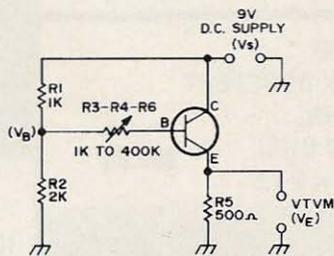


Fig. 1. Simplified Beta Test Circuit

resistance of R4 when divided by 1 k Ω (2 x R5) will result in the transistor current gain (in kilohms).

For example, after setting V_e at 2V for a specific transistor, by adjusting R4, you may have a total of 130 k Ω across R4. This is the direct equivalent of a beta of 130. You will be surprised how much several transistors of the same type will vary in beta. Now, you can determine which are the "hot" ones in a handful of transistors, all of the same type.

Look at Fig. 1 again. This is a simplified circuit. It is a common-emitter type. The two resistors (R1 and R2) form a voltage divider across the 9V power supply. The point V_b will measure 6V to ground. Thus, with the variable resistance set at minimum, the transistor base-to-ground voltage will be 6V. There will be a drop of 0.3V (germanium) to 0.7V (silicon) across from base to emitter of the transistor. The remainder of the 6V will appear across

¹Thorpe, Darrel, 73, Jan. 1967, p. 38.

Radio

Expo '71

LAKE COUNTY ILLINOIS FAIR GROUNDS
JULY 10 & 11, 1971 - 8 am to 6 pm

THE LARGEST MEETING OF
RADIO ENTHUSIASTS IN THE MIDWEST

Displays - Technical Motion Pictures - Reserved
Space for Indoor Flea Market - Indian
Village and Dances - Amusement Rides
for the Kids - Practical Door Prizes
Camping Area - And Lots More

Halfway between Chicago and Milwaukee - Rts. 45 and 120

Tickets - \$3.50 for both days

Advance Sales - \$3.00 (Children under 12 - No Charge)

For advance sales, write to:

RADIO EXPO '71

Box 271

Northbrook, Illinois 60062

sponsored by the

CHICAGO FM CLUB



emitter resistor R5 (approximately 5.5V). By adding the 5.5 and 0.5V we get 6V, or 3V from base to collector.

If we change the variable resistor, we can change the ratio of resistance between the base and emitter resistors. By arbitrarily pegging R5 at 500Ω the beta will conform to the formula above. In practice, the variable resistor will be calibrated, with an accurate ohmmeter, to show beta.


Figure 2 shows the actual transistor beta tester. You will see that either a collector-to-base, or a collector-to-emitter short will show a full power supply (9V) reading.

A base-to-emitter short will read 2V if the variable resistor is at minimum. Under this condition, R1 and R5 will then be a voltage divider across 6V, with 4V across R1 and 2V across R5. An open collector will produce the same reading. If either the base or the emitter is open, no voltage will result across R5.

A leakage test is performed by opening the supply voltage at R1. There will always be a small leakage which will result in no reading or a small reading. The lower the leakage, the lower the reading.

Whether the transistor under test is a PNP or an NPN type is easily determined by throwing the toggle switch to the position which results in a forward reading of the VTVM.

Fig. 2. Transistor Beta Tester

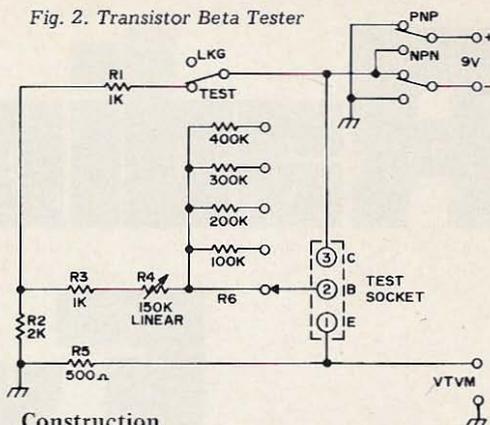

Construction


The first thing to do is to collect the necessary parts, as follows:

File box:

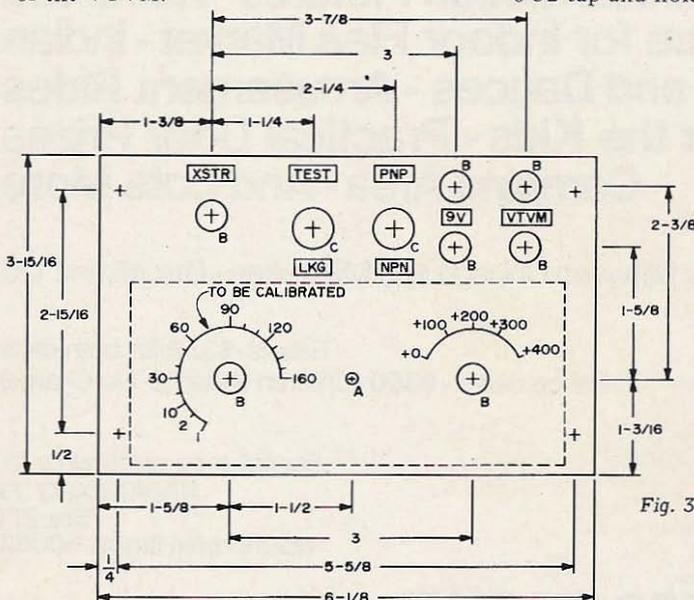- (1) File Box 4 x 6 x 4 1/2 in. Ohio Art Co. or equivalent.
- (2) pcs. 1/2 x 1/2 x 1/16 x 4 in. of aluminum angle bracket. (Reynolds Aluminum #2406, old number #161, or equivalent.)
- (4) Rubber feet with 6-32 mounting screws and nuts.
- (1) Panel, aluminum, 6 1/8 x 3 15/16 x .030 in.
- (8) Machine screws 6-32 x 1/4 in.

Miscellaneous tools and materials:

- Twist drills (#25 and #35).
6-32 tap and holder.



HOLE CHART		
LTR	SIZE	QTY
A	NO. 25	1
B	3/8	6
C	1/2	2

Fig. 3. Front panel dimensions and markings.

Fine steel wool.

Alcohol (for panel cleaning, not internal comfort).

Zinc-chromate spray

Lacquer spray, RCA 222627

Tape embosser and tape.

Transistor Beta Tester:

(1) Switch, 1 Pole, 5 position

(1) Potentiometer, 150 k Ω

(2) Knobs

(1) Switch, spdt

(1) Switch, dpdt

(2) Resistors, 1 k Ω

(1 each) Resistors, 500 Ω , 2 k Ω , 100 k Ω ,
200 k Ω , 300 k Ω , and 400 k Ω

(1) Socket, transistor

(1) Banana jack, red, with panel insulator

(3) Banana jack, black, with panel insulator

(1) Standoff, insulated lug

Assemble the file box by mounting feet 1/2 in. in from each corner. Mount the angles inside the box. Position them just below the top edge of the box and at each end. Detailed instructions on this and other construction can be obtained from the previous articles. The holes for the screws in the sides are 2 in. apart and centered. The tapped screw holes for the panel are positioned 3 in. apart and centered. The holes in the side are made with a #25 drill. Those in the bracket tops are made with a #35 drill and then tapped using a 6-32 tap. The panel is laid out and drilled or punched as shown in Fig. 3. Note that the 9V battery is shown as external to the unit. It can be mounted internally, but unless test units are to be used regularly, it is better to keep the battery external. You may also note that the picture showing the finished unit does not indicate the use of a transistor socket. The original idea was to provide several sockets in another case, but this proved cumbersome.

Before drilling or punching, always check your own parts to see that the required holes agree with those given here.

After drilling the panel, prepare it for painting and spray it as recommended in previous articles. Prepare the tapes as indicated by the picture and Fig. 3, and affix them as shown in Fig. 3. Take an index card cut to 2 3/8 x 4 1/4 in. and layout as

IF YOU WORK 2 METERS



YOU NEED THE *Clegg* T/R BOOSTER

IF your antenna feed line is longer than 40 feet some of the signals you hear are less than Q5 the other fellows hear more than you do your present 2 meter receiver lacks gain or sensitivity

Regardless of how big your 2 meter antenna is —
Regardless of how good your 2 meter antenna is —
The T/R BOOSTER is guaranteed to improve your "hearing power" if you have more than 3 dB of feed line loss!

Ask your local Clegg Dealer or write to us today for full details on this remarkable \$47.50 gadget that establishes your receiving capability up at the antenna where it counts.

e.t. Clegg associates, inc.

LITTELL RD., EAST HANOVER, N. J. 07936

NEW! SSB-1000 Linear

- 1000 Watts CW-RTTY
- To 1500 Watts PEP
- Popular 3-500 Z tube



Heavy duty construction throughout. Coasts along at full power 10 to 80 meters. A full KW in one compact cabinet at a bargain price.


- Vernier Dials
- Gray Metallic Finish
- 14 3/4" wide, 14" deep, 8 1/2" high
- Weight 58 lbs.
- 115 or 220 Volt
- Price \$275.00 FOB

MURCH ELECTRONICS

Box 35, Franklin, Maine 04634

Phone: 207-565-3312

Want to know more about Repeaters?

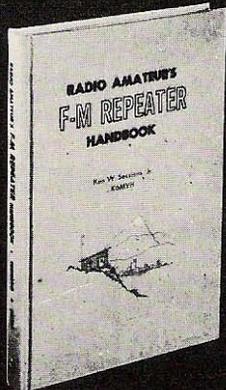

\$6.95

Want to build a repeater?
Want to improve your existing repeater?

Whether you're a newcomer or an oldtimer, you'll find "The Radio Amateur's FM Handbook" to be the most valuable repeater aid you can get.

FOR THE OLDTIMER

- the Handbook tells . . .
- how to defeat desensitization
 - how to calculate attenuation according to frequency spacing, antenna separation
 - how to build sophisticated control systems, using ICs, timers, relays, steppers, or Touchtone
 - how to build automatic logging and identification devices
 - how to build automatic phone patches

FOR THE NEWCOMER

- the Handbook tells . . .
- how to prepare for a repeater
 - how to get a repeater site
 - how to build a repeater
 - how to keep a repeater on the air
 - how to determine a prospective repeater's range
 - how to get your repeater license

The Handbook contains 208 pages of useful, hard-to-come-by information, and it's written in an interesting, personal view by Ken W. Sessions, Jr. (K6MVH) former editor of FM Journal, now managing editor of 73.

Order from:

73, Inc.

Peterborough NH 03458

Order From: 73 MAGAZINE, INC.
Peterborough NH 03458

Name _____

Address _____

Zip _____ Call _____

- FMB1 IFM
 FMJ2 Repeater Handbook

FROM 73's FM LIBRARY

FM BULLETIN (VOL. I)

Contains those rare copies of the Bulletin that nobody seems able to find any more. From the first issue of FM Bulletin to Feb 1968! Printed in chronological sequence as edited by Mike Van Den Branden (WA8UTB). 8½ x 11 in.
FMB1 \$3



THE BEST OF FM (VOL. II)

HOT OFF THE PRESS

Contains articles from the modernized FM Journal. Includes those "great," never-before-reprinted articles, complete with photos. An impressive and valuable collection of FM data. Edited by Ken Sessions (K6MVH). 6 x 9 in. Covers period from Mar 1968 to June 1969. 73's hottest selling book at Dayton Hamvention.
FMJ2 \$4.95




AN INTRODUCTION TO AMATEUR FM



by Ken W. Sessions, Jr. 96 pages of information, including current standards of deviation, tone frequencies, and operating channels. Includes an updated FM repeater directory, a catalog section of ALL FM MANUFACTURERS and dealers. Plus:

A complete bibliography listing all articles published since 1968 in FM Anthologies (Vols. I and II), 73, HR, QST, and CQ.

IFM \$1.50

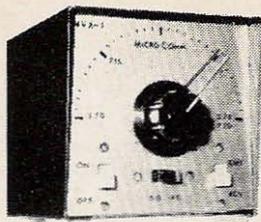

NOVICE DECLARATION OF INDEPENDENCE

We the People of MicroComm,
recognizing the inalienable right to qsy,
freedom to work DX and independance
to throw your crystals away, do ordain and
establish the Novice NVX-1 Variable Crystal
Oscillators. Fully approved by the Constitut-
ion and the F.C.C.

Works like a V.F.O. with your XMTR.

Coverage: 3702 - 3748 KHz

7152 - 7198 KHz

Declare your Independance and order today at the Intro-
ductory Price \$39.75, p.p.d., wired. Guaranteed and certified
for one full year.

shown in Fig. 3. Use india ink or press-on numbers. The left-hand control will have to be calibrated by placing the card on the panel, attaching the pot and knob, and then, with an ohmmeter, mark out the kilohms.

Mount all the parts on the panel, including the insulated lug. Wire the unit, swinging the resistors between points as required. Before the tester is finalized, the white card on the panel may be sprayed with clear acrylic. Draw up the schematic and mount it under the unit on the box bottom. Use tape with adhesive on both sides or glue.

Finally, type or cut out the following and paste onto a 4 x 6 card and install it in the file-box top.

QUALITY

1. Set PNP-NPN switch to proper position.
2. Set *BETA* controls to zero.
3. Set *LKG-TEST* switch to TEST
4. Approx. VTVM Readings:

Good	5.5 v.
C-E Short	9.0 v

C-B Short	9.0 v.
B-E Short	2.0 v.
C Open	2.0 v.
B Open	0 v.
E Open	0 v.

BETA

1. Adjust *BETA* controls to a VTVM reading of 2.0 v.
2. Read beta directly by adding calibrated and switch control reading.

LEAKAGE

1. Reset *BETA* controls to zero.
2. Set *LKG-TEST* switch to *LKG*.
3. Observe VTVM reading.

NOISE CHECK

1. Connect headphones in place of VTVM.
2. Monitor noise level by ear.

$$\begin{aligned} \text{Beta} &= \frac{R4}{2 \times R5} \\ &= \frac{R4}{2 \times 500} \\ &= R4 \text{ in Kilohms} \end{aligned}$$

FEDERAL COMMUNICATIONS COMMISSION
WASHINGTON, D. C. 20540

May 3, 1971

7524

Mr. James D. Shaddon
MicroComm, Inc.
P. O. Box 381
Hermosa Beach, California 90254

Dear Mr. Shaddon:

This is in reply to your letter of January 29, 1971, in which you included a detailed case report on the performance of your proposed variable crystal controlled transmitters for Novice Class amateur radio operation.

On the basis of the conclusive test results submitted regarding the operation of the NVX-1 and NVX-2 Novice Class amateur variable crystal controlled transmitters, the equipment appears to be acceptable for licensing in compliance with Section 97.101(c) of the Commission's Rules. Acceptability is limited to factory assembled equipment operating in the 80 and 40 meter Novice Class segments of the amateur band and each transmitter produced shall carry on the chassis the warning forbidding unauthorized tampering with the unit.

Sincerely yours,

J. E. Barr
James E. Barr
Chief, Safety and Special
Radio Services Bureau

Available ONLY from

MicroComm

"... the birthplace of new ideas
in Novice Communications"

BOX 373

CUPERTINO, CALIF.

95014

Mark Hurwich WA2ITE
48 Manetto Hill Road
Plainview NY 11803

Postage Rates Double?



That's the word. The rates for mailing magazines is scheduled to double during the next year. Does this mean subscription rates will double? Well, not quite. But they will have to go up, obviously.

When you consider that a 5¢ hot dog today costs 45¢ a \$3.00 subscription for \$6.00 is a worthy deal. Even at \$7.00 or \$8.00 this is beating inflation.

It would seem prudent to take advantage of the inertia built into subscription departments by subscribing at the present low rates instead of waiting for the inevitable increase that must and will come.

PRESENT SUBSCRIPTION RATES:

1 year \$ 6.00 (add \$1 overseas)
2 years \$11.00
3 years \$15.00

POSSIBLE NEW SUB RATES:

1 year \$10.00
2 years \$19.00
3 years \$27.00

Why take a chance? These rates may change without notice. This offer valid until August 1, 1971, at least:

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

New subscription Renewal or extension
— \$ 6 1 year — \$11 two years
— \$15 three years — +\$1 foreign

73 Magazine • Peterborough NH 03458

Call Sign Plaque

During my own rather short amateur career, I have met very few other hams who were not proud of being a radio amateur. To show the world their hard won prize, many invest a fair amount of money in some device which displays their call sign. Call sign plaques can often be expensive, but they need not be. You can make your own with very little effort and for a cost of only \$2.50 (or even less).

To start, I purchased six "house letters" (the letters printed on a gold-anodized aluminum sheet, with an adhesive backing). These were 25¢ each, for the largest size (3½ in. high). A piece of ¼ in. plywood with a walnut veneer was obtained from the local lumber yard for 75¢, about 6 in. wide and 2 ft long. To leave a 1¼ in. border, slightly longer on the ends, it was then cut to 20 in. The corners were rounded, edges sanded, and finally the face was gently sanded (use fine paper — the veneer's only 1/32 in. thick!).

I chose to finish the surface "antique oil" (wax or shellac could do just as fine). The surface is waxed, shined, and then left to harden. A finish such as *Minwax Antique Oil Finish* is then applied over the wax, to be wiped off two hours later and buffed. This results in a beautiful soft finish, which completely dries in 24 hours.


The edges are next dyed the color of the veneer using (brown) shoe polish. The last step is merely to draw a centering line and mount the letters.

By the way, the same finish on a "hunk" of walnut makes a fantastic key base!

... WA2ITE ■

PAGE SEVENTY THREE

ACTION COUPON

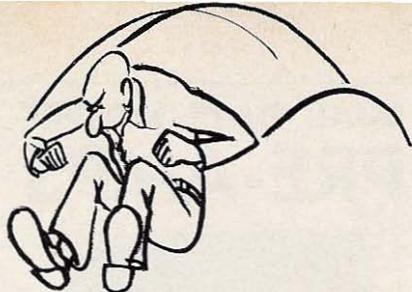

73 CONSUMER TESTING SERVICE

Have you invested in a piece of equipment that is really great and that you can recommend without reservation? Perhaps your gear has mixed blessings. Or maybe it is a 'lemon' and you'd like everyone to know what happened to you!

We here at 73 Magazine want to know your experience with new equipment. We want to be able to pass this along to the rest of the readers. We want to be able to talk with the manufacturers and get them to overcome problems. We want to be able to solve servicing difficulties.

YOU CAN HELP!

Send in the below form, or send the information on a card or letter to our Consumer Testing Department. As soon as we have enough data to get a rounded view of new gear we will publish the reader experiences, good and bad.

Send to 73 Magazine, Peterborough, NH 03458

Consumer Testing

Date: _____

73 Magazine

Peterborough, N.H. 03458

Manufacturer _____ Model _____ Type of Equip. _____ Price paid _____


Distributor _____ or other source _____

Your evaluation _____

Servicing problems? _____

Your recommendation: High Okay Poor Very Bad Or? _____

DUAL GATE MOSFET PRE-AMPS

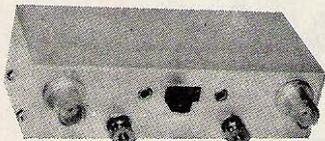


to 175 MHz. \$21.95 ppd.
to 300 MHz. \$25.95 ppd.

- Available from 5 MHz. to 300 MHz. Bandwidth is approximately 3% of frequency.
 - Voltage gain 30 to 40 DB depending on frequency.
 - Two Dual Gate MOSFET amplifier stages with each having a tuned input and tuned output. Each Dual Gate MOSFET is actually an integrated cascode circuit thus giving you 2 cascode circuits equivalent to 4 triodes.
 - Exceptionally low noise (2.5 DB at 175 MHz.), greatly reduced cross modulation and 10 times the dynamic range (signal handling capability) of the best bi-polar transistors. Also superior to preamps using junction FETs and Single Gate MOSFETs.
 - Panel mounted manual gain control.
 - Type BNC input and output receptacles for minimum loss at UHF. Standard Impedance is 50-75 ohms.
 - Carefully tuned at our laboratory with sweep generator and oscilloscope for the best bandpass characteristic.
 - Full wave UHF diodes protect input transistor.
 - Operates on 6 to 16 volts DC, 5 to 15 Ma.
- New York City and State residents add local sales tax.

VANGUARD LABS

Dept. H
196-23 Jamaica Ave., Hollis, NY 11423

ANTENNA HARDWARE MOUNTING KITS

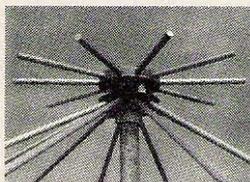

Rugged, corrosion resistant aluminum castings, for ham and CB antenna construction.

BM-1. Mounts up to five RM-75 loading coils on Hustler 4BTV vertical for 250 kHz bandwidth.

BM-2. Foundation for 21-144 kHz ground-planes, using standard aluminum tubing. Also as "spider" for Quads.

BM-3. Foundation for building broad-band Discone antennas in 50 to 1,000 mHz range using standard 3/8" rod; complete with SO-259 coax connector. (Illustrated)

Send postcard for complete brochure and price list.
Available by mail order only from ...

PAL Marketing P.O. BOX 5187
SANTA MONICA, CALIF. 90405

The best loud-speaker for
your product is SEVENTY-
THREE MAGAZINE!

ZERO BEAT

Wm. Bruce Cameron
324 So. Riverhills Dr.
Temple Terrace FL 33617

Anyone who has ever operated in a net has complained about other stations being off frequency. Crystal control by itself does not help, both because of fine differences in crystals and gross differences in rigs. When you suggest adding padders to the rig some guys rebel for fear of hurting resale value, and others because there is just not enough room.

The easiest answer I have found is to attach a small ceramic padder directly to a FT 243 case, using a longer screw through one of the upper holes in the body and cover plate, as shown in the drawing. If you are issuing crystals to a net, you can prefabricate these little assemblies so all the operator needs to do is apply a screwdriver. If he is a genuine appliance operator you may also have to supply the screwdriver. When the crystal is changed to another rig, it can be readjusted to suit.

This method works so well I have also

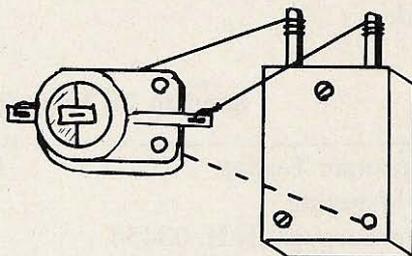


Fig. 1. Zero beat.

used it on one of my 2 meter FM rigs, which has socket provisions for only one crystal but which I like to operate on several frequencies. I removed the padder which was on the chassis and have a separate one mounted on each crystal. To the modern pushbutton set this may seem pretty strange, but for us old boys who used plug-in coils both in transmitters and receivers it seems merely a bit nostalgic.

...WA4UZM

Semiconductor Supermart

• HEP • FAIRCHILD • RCA • MOTOROLA • NATIONAL

MOTOROLA HEP SEMICONDUCTORS

NEW FUNCTIONAL ICs
 C6004 1-W Audio Power Amp \$2.60
 C6010 W'band Amp-RF-IF-Audio \$1.59
 C6001 FM IF Diff. Amp \$2.09

JUNCTION FETS
 HEP-802 N-channel RF \$1.59
 HEP-801 N-channel Audio \$1.59

DUAL-GATE FETS
 F2004 VHF RF Amp-Mixer \$2.50
 F2007 VHF RF Amp-Mixer;
 Diode Protected LOW-
 NOISE 2.6 dB at 200 MHz \$1.65

HEK-3 RADIO AMATEUR KIT
 Contains (2) HEP-590, (1) HEP-570 plus
 book w/10 Ham Projects. \$5.95

HEK-2 FET EXPERIMENTERS KIT
 Contains HEP-801, HEP-802, HEP-50,
 HEP-51 and Instructions for 9 Projects
 \$3.95

MOST MOTOROLA, RCA, & FAIRCHILD LINEAR IC's AVAILABLE
 ... WRITE US WITH YOUR NEEDS.

POPULAR IC's

MC1550G \$1.80
 CA3028A \$1.77
 CA3020 \$3.07
 CA3020A \$3.92
 MC1306P 1/2 W hi-gain audio power Amplifier \$1.10
 MC1350P IF amp, hi-gain 50 dB power gain at 60 MHz more at lower freq. \$1.15
 MC1351P FM IF amp quadrature detector \$1.70
 μ A703 RF amp \$2.00
 μ A723 Voltage regulator \$2.50
 MC1496 μ A796 Doubly balanced mod/demod \$3.50

TRANSISTORS

MPF102 \$.75
 MPF105/2N5459 \$.96
 MPF107/2N5486 \$1.26
 MPF121 \$.85
 3N140 \$1.95
 3N141 \$1.86
 MFE 3007 (replaces most dual gate FETs) \$1.98

MOST 2N, MPS AND OTHER MOTOROLA AND FAIRCHILD TRANSISTORS AND FETS AVAILABLE.

TTL BARGAINS

FACTORY FRESH - BRAND NEW
 7400P Quad 2-input gate \$.45
 7441AP BCD to Dec decoder driver \$2.75
 7490P Decade Counter \$1.90
 7475P Quad Latch \$1.50

ZENER DIODE BUY

1N757A 9-volt 5% zener \$.50
 1N759A 12-volt 5% zener \$.50

OPERATIONAL AMPLIFIER

709 Op amp \$.95

All the above devices are brand new factory tested devices... no rejects, fall-outs or such. All are guaranteed new.

*Please include 35¢ for shipping
 All orders shipped Air Mail*

CIRCUIT SPECIALISTS CO.

Box 3047, Scottsdale, AZ 85257
 FACTORY AUTHORIZED
 HEP-CIRCUIT-STIK
 DISTRIBUTOR

IS IT EASY TO LEARN THE CODE?

Frankly, no. Neither was it easy to learn how to read without two things: Proper instruction, and practice. CODEMASTER tapes, proven in over five years of sales of thousands of tapes all over the world, give you that essential instruction. No other teaching system offers you a more proven method, more accurate sending, more complete guidance. Select your CODEMASTER tapes below!



CM-1: For the beginner. A complete course of instruction is on the tape. Practice material at 5, 7, 9 WPM. Prepares you for Novice exam. Includes code groups and punctuation.

CM-1½: An intermediate tape, especially for General Class exam study. No instruction; just practice. ½ hr 11 WPM; 1 hr 14 WPM; ½ hr at 17 WPM. Includes coded groups and straight text.

CM-2: For Extra-Class license study. Mostly straight text, some code groups. 1 hour at 20 WPM, ½ hour each at 25 and 30 WPM. For real QRQ, play this tape at twice speed!

CODEMASTER tapes are 2-track monaural; available in two styles: 7 inch reel (3¼ IPS) and cassette. Be sure to specify both the program (CM-1, etc) and the style (reel or cassette). Any tape, \$6.95 postpaid USA 4th class. Any two tapes, \$13.00; all three, \$17.00 PPD. For air shipment in USA add 50¢ per cassette or 80¢ per reel. Immediate delivery. Mastercharge and BankAmericard honored; give us your account number. CODEMASTER tapes are made only by Pickering Radio Company, P O Box 29A, Portsmouth, RI 02871. See your dealer or order direct. Satisfaction guaranteed.

PICKERING RADIO CO.
 Post Office Box 29A
 Portsmouth, RI 02871



SPACE-AGE TV CAMERA KITS & PLANS



BE A PIONEER IN HOME TELECASTING! Build your own TV CAMERA. Model XT-1A, Series D, \$116.95 pp. Solid-State. Step-by-step construction manual. High quality. Connects to any TV without modification. Ideal for hams, experimenters, education, industry, etc.

PHONE or WRITE for CATALOG.
 DIAL 402-987-3771

Many other kits, parts and plans available including starter kits, focus/defl. coils, vidicon tubes, const. plans, etc.

1301 N. BROADWAY ATV Research DAKOTA CITY, NEBR. 68731

SLOW SCAN TV



SSTV MONITOR \$298 FSS CAMERA \$298

SPECIAL PRICE: Camera & Monitor \$549

If you like to build yourself, then try one of our kits.

KIT 1 P.C. Board only (2 req) ea. \$ 9.95
 KIT 2 P.C. Boards (Both) & all parts (unwired) \$ 80.00
 KIT 3 P.C. Boards Wired & tested \$125.00
 Power Supply Kit - No chassis \$ 54.95

All kits tube type with instructions
 CRTs, Power Supplies, and cabinets not included in kits

E.K.Y. VIDEO VISION CO.
BOX 15, STOCKHOLM NJ 07460

AMERICAN CRYSTAL CO.

1623 Central Ave., Kansas City KS 66102 Tel. 913-342-5493
 Mfg. Crystals for most communication Equip.

For use in:
 TWO WAY
 SCANNERS
 MONITORS
 TRANSMITTERS
 C.B. SYNTHESIZERS
 REPEATERS



Crystal prices @ .002%
FUNDAMENTALS
 2 to 14.9Mhz. \$5.25
 15 to 19.9Mhz. 6.10
THIRD MODE
 10 to 44.9Mhz. 5.35
 45 to 55.9Mhz. 6.10

ELEMENTAL CRYSTALS .0005%
 (channel freq. changed in customer's element) 15.00
 C.B. (Class D Single channel) 2.75
 AMATEUR NOVICE, HC6/U 3.00

Extras: Oven use \$1.50, Subminiature 25¢, .093 pins 10¢
 Postage 1/2 crystals 2 ozs. each additional 1/3 crystals 1 oz.
 Write for quantity discount

**HELP STAMP OUT
 MENTAL HEALTH
 SUBSCRIBE TO 73
 NOW**

HAL DEVICES

**HAL ID-1 REPEATER
 IDENTIFIER**

\$70⁰⁰

Kit Form

TTL logic. Power line frequency counter for 3 minute or less timing and control. Easily reprogrammable diode ROM uses only 27 diodes (depending on call) to send DE "any call". Low impedance audio with volume and tone control. All circuitry including PS on small G10 glass PC board. Write for full details, HAL DEVICES, BOX 365, URBANA, ILLINOIS 61801

Fabulous DX Map of the World



SHOW VISITORS DX YOU'VE WORKED

- ONLY \$1.00 POSTPAID USA**
- Wall sized (23" x 31")
 - Shipped flat in mailing tube
 - Suitable for framing
 - Most complete map available
 - Up-to-date world prefixes shown
 - Color in countries as worked
 - Shows islands, reefs, rare DX spots
 - Use colored map pins for different bands
 - Dresses up the DX shack

MADE ESPECIALLY FOR DX'ERS

Buy lavishly! Order today from:
73 MAP, Peterborough NH 03458



**Radio Amateurs
 Reference Library
 of Maps and Atlas**

WORLD PREFIX MAP - Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables postpaid \$1.25

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD - from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. postpaid \$1.25

RADIO AMATEURS MAP OF NORTH AMERICA! Full color, 30" x 25" - includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus informative information on each of the 50 United States and other Countries. postpaid \$1.25

WORLD ATLAS - Only atlas compiled for radio amateurs. Packed with world-wide information - includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica - a complete set of maps of the world. 20 pages, size 8 3/4" x 12" postpaid \$2.00

Complete reference library of maps - set of 4 as listed above postpaid \$3.50
 See your favorite dealer or order direct.

**WRITE FOR
 FREE
 BROCHURE!**

**RADIO AMATEUR
 callbook INC.**



Dept. B 925 Sherwood Drive
 Lake Bluff, Ill. 60044



2 kW from Heath

The first amateur kilowatt transmitter I ever saw was 6 ft tall and weighed over a quarter of a ton. The SB-220 is 8 in. high and weighs less than 50 lb. The first kilowatt rig I ever built, around 1947, was 5 ft across and took four of us to lift onto the operating table. The SB-220 is only 15 in. wide and can be carried under one arm. We've gone a long way, guys, to get where we are today.

In the last few years, I've looked over all the popular linear amplifiers on the market and have wished many times that one was sitting on my desk. Until recently they were all out of reach; shoes and food for my five have first priority. I even made plans to build my own, but getting parts and finding time to build crossed that idea off my list. Then I saw the Heathkit linear and couldn't resist.

It took the truck lines over two weeks to get the SB-220 kit from Michigan to my location out here in the Mojave Desert in California. All this time they did their best to bust up the two cartons. They didn't get the job done, due to good Heath packing.

It sure was a happy day when my kit

arrived. I canceled all plans for the weekend and spent the evening checking the parts list.

The electrical design follows what has almost become an amateur standard: broadband input, grounded grid, and pi-tuned output. You can get all the specifications and other good information from the Heathkit advertisements.

The mechanical design of this kit has been well planned. To get the power supply (which takes up one-third of the space) and the rf section in one little cabinet took a lot of careful planning. But they did it.

The assembly manual lives up to the Heathkit reputation of being the best in the business. One section in the manual that is very helpful consists of chassis photographs. I only wish a person could get real glossy prints so the details could be seen much clearer.

Safety is not left out. This high voltage could prove fatal. Not only do they provide a warning decal, but they designed an automatic discharge interlock that operates when the inside top panel is removed.

Bands: 80, 40, 20, 10m
Driving power: 100W
Duty cycle: Continuous
3rd order distortion: -30 dB
Output impedance: 50-75 Ω unbal.
Power required: 120V at 20A or
240V at 10A, 50-60Hz
Cabinet size: 14 7/8 x 8 1/4 x 14 1/2 in.
Net weight: 47 lbs.
Heath Model Number: SB-220

Basic specifications

Construction was started on a folding card table and was all the space needed. Three muffin pans and a couple of cigar boxes, plus the packing boxes the kit came in held all the parts for easy accessibility. All the chassis photographs were removed from the manual and hung up for easy and quick reference. This helps in understanding the layout and detail drawings. No special tools are needed; I did use a pencil-type soldering iron with a small and large tip.

Carefully following the step-by-step assembly section of the manual, it took just under 20 hours to complete. Along with coffee and rest breaks, the weekend went by very fast. The "test and final assembly" section took another three hours. I ran into a few problems and made a list of things I would do differently next time. I had a chance to use this list when a doctor friend of mine asked me to put his together. It sure helped. I gave this list to a retired friend, and it saved him time and trouble the first time. (The list is available on receipt of SASE.)

Now came the problem that many of us have, and one of the reasons many amateurs feel a linear of this size is out of the question: ac power. The SB-220 will work on 120V, but requires a maximum of 20A. This is the most a 12-gage wired circuit can handle. What could be done is to operate the linear on one house circuit and bring an extension cord in from another house circuit to run the rest of the station. I live in a rented house, and this is what I did at first. I later ran a special extension cord to the clothes dryer outlet in the kitchen and

picked up my 240V from there. We don't use a dryer here in the desert, so this made a good source of power. Keeping the cord out of the way required a few holes in the walls. Maybe an article on ac house wiring for amateurs would be a good thing to write about next.


We moved to a new house since constructing the SB-220, and this time we had to wire in a new 240V line to the operating position. That cost over 40 bucks just in materials. The SB-220 runs best on 240V, and you fellows that have it in your shack or can have it wired in have no problem. If you wire it yourself, make sure the local electrical code is followed to the letter, for your own protection. My 80 and 40 meter inverted-V antennas worked fine on low power; but for this high power, I added insulators at the ends where the high voltage could cause trouble. This proved to be a good move, and it didn't change the loading a bit. The loading control knob on the SB-220 seems to be very broad, no matter which antenna is being used. Guess I'll have to get a Heath scope to make my tuning more precise. The only real trouble I've had in using the linear has been of my own making. I sometimes forget to change the bandswitch when I go from band to band. This hasn't hurt the linear, but it sure makes the output meter pointer swing wild.

I enjoy working barefoot, but there come times during net operations or running a phone patch that a linear makes operating pure pleasure. I don't go looking for DX, but when a distant station answers the first time, man that's living! I've had no trouble running it on reduced power for RTTY 15-20 minutes at a time - this beats their specs by 100%.

The only dislikes that I have are purely personal. To ship the SB-220, it must be packed in a special shipping box. The other is the size; in this area, it doesn't match the other SB pieces of equipment.

All in all, this unit is a wonderful buy, at 17½ cents a watt! Heath sells many of these kits. Buy yours now, before the price of materials make the kit price go up. I like my SB-220 - I'm sure you'll like yours.

...W6BMK■

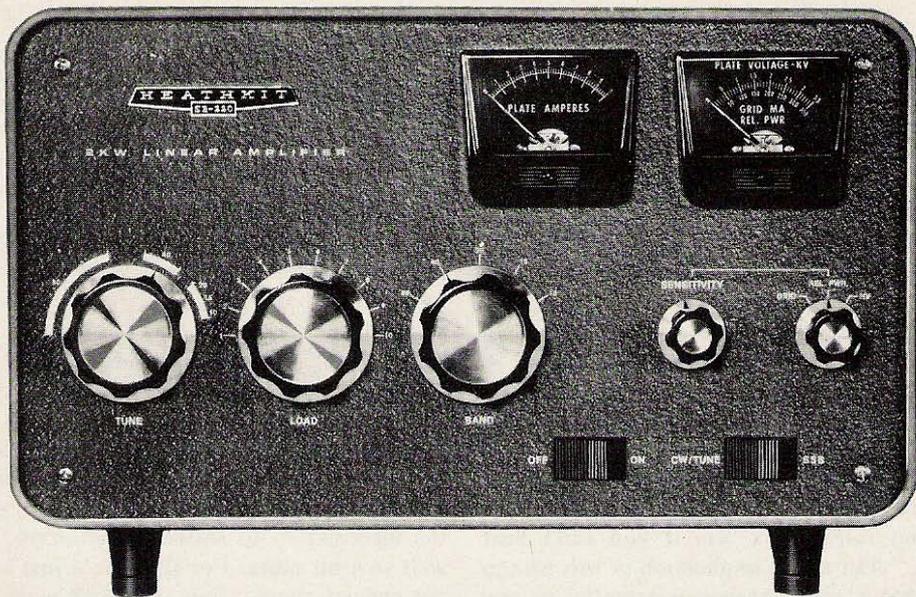

Turn on your Benton Harbor maxi-rig!

Heathkit® SB-220

Business end of the Maxi-Rig! Gives your signal the authority it takes to punch through those pile-ups (or start one yourself). And keeps you operating under conditions that drive the other guys QRT.

A pair of conservatively rated Eimac 3-500Z's provide up to 2000 watts PEP SSB input . . . 1000 watts on CW and RTTY. Requires only 100 watts PEP drive. Pretuned broad band pi-input coils deliver maximum efficiency and low distortion on the 80-10 meter bands.

The built-in solid-state power supply can be wired for either 120 or 240 VAC and switched back again in minutes if your power requirements change. Circuit breakers provide added protection and eliminate costly fuse changing. And for cooler operation and extended tube life, idling plate current is reduced by Zener diode regulated bias.

The layout of the new "220" is designed for fast, high volume air flow with a husky, quiet fan in the PA compartment doing the job. Result: the "220" actually runs cooler than most excitors.

Other features include two front panel meters for continuous monitoring of Ip plus switch-selected monitoring of Rel. Pwr., Ep & Ig . . . ALC output to reduce over-driving and distortion . . . safety interlocked cover . . . easy 15-hour assembly and handsome Heathkit SB-Series styling.

Tired of stumbling barefoot through the QRM? Order the shoes for your Maxi-Rig now . . . the new "220" . . . another hot one from the Hams at Heath.

- Full 2 kW PEP input on SSB . . . 1 kW on CW and RTTY • Boardband pi-input on 80 through 10 meters
- Two Eimac 3-500Z tubes • 120 or 240 VAC wiring options • Zener diode regulated operating bias for reduced idling plate current, longer tube life, cooler operation • Double shielded to reduce stray radiation
- Solid-state power supply • Two front panel meters for continuous monitoring of plate current, plus switch selected monitoring of Rel. Pwr., plate high voltage and grid current • Quiet, high volume fan for cool running • ALC output • Easy 15 hour assembly.

Kit SB-220, 55 lbs. \$349.95*

SB-220 SPECIFICATIONS — Band coverage: 80, 40, 20, 15 and 10 meter amateur bands. **Driving power required:** 100 watts. **Maximum power input:** SSB: 2000 watts P.E.P. CW: 1000 watts. RTTY: 1000 watts. **Duty cycle:** SSB: Continuous voice modulation. CW: Continuous (maximum key-down 10 minutes). RTTY: 50% (maximum transmit time 10 minutes). **Third order distortion:** —30 dB or better. **Input impedance:** 52 ohm unbalanced. **Output impedance:** 50 ohm to 75 ohm unbalanced; SWR 2:1 or less. **Front panel controls:** Tune, Load, Band, Sensitivity, Meter switch, Power CW/Tune — SSB, Plate meter, Multi-meter (Grid mA, Relative Power, and High Voltage). **Rear Panel:** Line card, Circuit breakers (two 10 A). Antenna Relay (phono), ALC (phono), RF Input (SO-239). Ground post. RF output (SO-239). **Tubes:** Two Eimac 3-500Z. **Power required:** 120 VAC, 50/60 cycles, at 20 amperes maximum. 240 VAC, 50/60 cycles at 10 amperes. **Cabinet size:** 14 1/4" W x 8 1/4" H x 14 1/2" D. **Net weight:** 48 lbs.



FREE '71 CATALOG

Describes these and over 300 other Heathkits. Save up to 50% by building them yourself. Use coupon and send for your FREE copy!

HEATH COMPANY, Dept. 11-7
Benton Harbor, Michigan 49022

Enclosed is \$ _____, plus shipping.

Please send model (s) _____

Please send FREE Heathkit Catalog.

Name _____

Address _____

City _____

State _____

Zip _____

Prices & specifications subject to change without notice.

*Mail order prices; F.O.B. factory.



a Schlumberger company

AM-246

STUDY GUIDE

GENERAL CLASS LICENSE

Part X: The Listening Post

One of the oldest sayings in radio (attributed by some to Signor G. Marconi in the years preceding 1900) is, "You can't work 'em if you can't hear 'em." The direct implication of this maxim is that a good receiver is essential to any ham station.

Not only is a good receiver essential, but the FCC requires that any aspirant for the General class license have some knowledge of what goes on inside that receiver. While only three questions on the official study list of questions to help in preparation for the license exam involve receivers, those three between them manage to require a fairly complete knowledge of receiver theory.

In this chapter we're going to tackle those receiver questions, and while we're at it we'll take up SSB (single sideband). This isn't as farfetched as it might sound, because the generation of an SSB signal is mighty like the reception of just about any kind of signal.

The FCC study list questions we will deal with are:

40. List the basic stages of a conventional superheterodyne receiver and tell what function each stage performs.

44. What are the basic stages of a single sideband (SSB) receiver and transmitter and what purpose does each serve?

46. What are "images" in a receiver?

For a start, how about "What kinds of receivers exist?" The answers to this will help put the requirements of the FCC questions into perspective, as well as pro-

viding groundwork for several parts of the detailed discussion later. Then we can look at "What makes up a superhet?" and get the information to answer question 40, as well as a bit more. For SSB, we'll just ask the general query "How does SSB work?" and get the required block diagrams of transmitters and receivers along with a view of how SSB fits into the general communications picture. Finally, we'll try to determine "How is receiver performance rated?"

This question might easily be considered first, but the ratings make more sense when the attributes being rated have some meaning.

We're biting off quite a mouthful for this chapter, so let's get right to chewing it up. If you're ready, let's go.

What Kinds of Receivers Exist?

The earliest kind of radio receiver on record was a device which today would startle almost anyone involved with electronics. It was "a circle which could be rotated within itself... made of copper wire 1 mm thick, and had a diameter of only 7.5 cm. One end of the wire carried a polished brass sphere a few millimeters in diameter; the other end was pointed and could be brought up, by means of a fine screw insulated from the wire, to within an exceedingly short distance from the brass sphere."

This receiver was used in 1888 by 31-year-old Heinrich Rudolph Hertz (the man for whom the unit of frequency is named) to demonstrate the existence of

"distinct rays of electric force" carried without wires, through space. The quotations are from his own description of the experiments, published in December 1888. The copper-wire loop was the complete receiver; the accompanying transmitter was a sparkgap arrangement, and the maximum distance between transmitter and receiver was limited to about 5 ft (when everything was working perfectly, amazing DX of 6 ft could be achieved).

After Hertz' experiments demonstrated the existence of radio waves, Marconi developed a communication system around them. The Marconi system used a "coherer" as the main part of the receiver; this was much more sensitive than Hertz' loop-and-sparkgap, but still nothing compared to today's apparatus.


By the time amateur radio began to become popular, the coherer was on its way out, having been replaced by the much-more-sensitive galena crystal. This was a first cousin to today's semiconductor crystal diodes, and operated in essentially the same fashion (but for more than 20 years no one suspected as much). Finally, during World War I, the vacuum tube came into use for radio reception, and a young Signal Corps major named E. H. Armstrong invented, in order, the regenerative receiver, the superregenerative receiver, and finally the superheterodyne circuit. The superhet is still the standard receiver circuit, although transistors and integrated-circuit chips are replacing the vacuum tubes Armstrong knew.

Despite the almost universal use of the superhet for serious communications today, the diode, regenerative, and superregen circuits are still very much with us. The popular "Twoer" and "Sixer" transceivers from Heath use superregen receivers, and most superhets include at their core at least one diode detector which is a direct descendant of the ancient "crystal set." Regenerative circuits are popular for beginners' construction projects and can deliver amazing performance with a minimum of components.

All these receiver types so far are for AM reception. For CW, the regenerative

THE BEST 2 METER CONVERTER

Model 407
\$42.95
ppd.

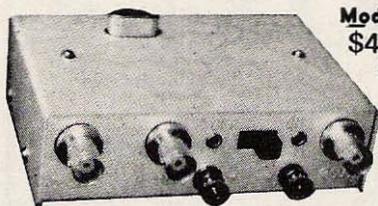

144-146 MHz in. 28-30 MHz out
or 146-148 MHz with a second crystal
Available at \$5.95 each.

A full description of this fantastic converter would fill this page, but you can take our word for it (or those of thousands of satisfied users) that it's the best. The reason is simple—we use three RCA dual gate MOSFETs, one bipolar, and 3 diodes in the best circuit ever. Still not convinced? Then send for our free catalog and get the full description, plus photos and even the schematic.


Can't wait? Then send us a postal money order for \$42.95 and we'll rush the 407 out to you. NOTE: The Model 407 is also available in any frequency combination up to 450 MHz (some at higher prices) as listed in our catalog.

*New York City and State residents add local sales tax.

VANGUARD LABS

Dept. H, 196-23 Jamaica Ave., Hollis, N.Y. 11423

LEARN RADIO CODE

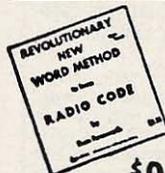

\$9.95

Album contains three 12" LP's 2 1/2 hr. instruction

THE EASY WAY!

- No Books To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn

Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in LESS THAN HALF THE TIME!

Available on magnetic tape, \$9.95 - Cassette, \$10.95

EPSILON [E] RECORDS


508 East Washington St., Arcola, Illinois 61910

TONE CONTROL DEVICES

Decoders, Encoders, Logic Processors; Autopatch, COR Compact, solid-state, plug-in modules. Reasonably priced. Write for free Application Notes & Catalog


DIGITONE BOX 73 BELLBROOK, OH 45305

VIBROPLEX

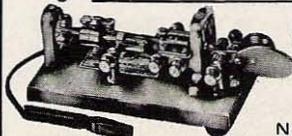

ENJOY EASY,
RESTFUL KEYING
\$21.95 to \$43.95
THE VIBROPLEX
CO., INC.
833 Broadway,
New York, NY 10003

NEED CRYSTALS?

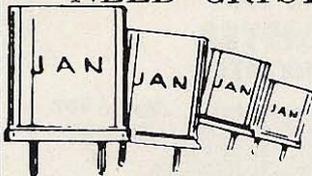

We can supply crystals from 2KHz to 80 MHz in many types of holders.

SPECIALS

Color TV crystal (3579, 545KHz) wire leads	\$1.60 4 for 5.00
100 KHz frequency standard crystal (HC 13/U)	4.50
1000 KHz frequency standard (HC6/U)	4.50
Any CB crystal, trans. or rec. (except synthesizer crystals)	2.50
Any amateur band crystal in FT-243 holders (except 80-160 meters)	1.50 4 for 5.00
80 meter crystals in FT-243 holders	2.50

We have in stock over six million crystals which include types CR1A/AR, FT243, FT241, MC7, HC6/U, HC13/U, etc. Send 10¢ for our 1970 catalog with oscillator circuits, listing thousands of frequencies in stock for immediate delivery. (Add 10¢ per crystal to above prices for shipment 1st class mail; 15¢ each for air mail.)



ORDER DIRECT

with check or money order to

Special Quantity Prices
to Jobbers and Dealers

2400B Crystal Dr., Ft. Myers, Fla. 33901

180 MHZ! ELECTRONIC COUNTER

5 DIGIT READOUT WITH 8 DIGIT CAPABILITY - .0005% ACCURACY - PORTABLE

Thru-Line operation for transmitters, direct input for signal generators. Frequency range: 1 khz to 180 mhz. Level range: 1 milliwatt to 100 watts. Get "on channel" with this solid state counter which can be operated from 115 vac or your car lighter socket. Four ranges with self test and 1 mhz output jack. RCA Numitron readouts. Shipped postpaid. Model 5-VHF.

Introductory price, only\$325

 **PAGEL ELECTRONICS**

6742C Tampa Ave., Reseda, Calif. 91335

EXPERT REPAIR AND CALIBRATION SERVICE

Specializing in repair and calibration of test, amateur, CB, and business FM equipment. Prompt attention by highly qualified personnel. All technicians hold both FCC amateur and commercial licenses. Write for shipping instructions.

SOUTHWEST RADIO-METRICS

290 Alamosa Road, Albuquerque, N. Mex. 87107
Telephone 505-345-0768 505-762-2224

Receiver Repair Specialists Equipment Broker-Dealer

We Sell (SASE) ● We Buy (Write)
201-366-0388 (First) 201-743-5705 (Second)

PARADD ENGINEERING SERVICE

Lawrence Rd. (Randolph) Dover, N.J. 07801
Paul A. Reveal - W2ADD

and superhet circuits work nicely. The diode circuit and the superregen do not produce easily audible output from CW signals; the crystal set worked on the CW of its day only because the output of a sparkgap transmitter was not a clean CW signal, but instead was a raucous buzz (or smooth whine if the gap was driven by an alternator or used a rotary gap arrangement, as some of the large commercial installations did).

Almost all FM receivers are of the superhet variety, although a superregen will operate nicely on FM and even a diode circuit can perform creditably.

The modern standard, as we said, is the superhet. These come in several types, and we'll find out more about them in the next section.

What Makes Up a Superhet?

Before we can get very far in finding out what goes into a superhet circuit, we must look at receiver circuits in general. This, in turn, is going to take us back in places to the subject matter of our previous chapter, modulation.

For now, incidentally, we'll only be examining receivers for AM signals. Once we have them down cold we can proceed to the features required for other types of modulation.

The simplest practical receiver for today's signals is the diode detector, shown stripped to its basics in Fig. 1. It will work

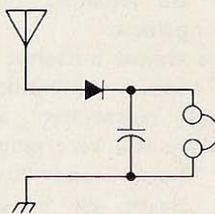


Fig. 1. Simplest radio receiver consists only of antenna, ground, diode, capacitor, and earphone connected as shown.

just this way, too, if you care to try it. Incoming rf picked up by the antenna must pass through the diode and the capacitor (the inductance of the headphones acts as a choke) to reach ground. The diode, how-

ever, permits current flow in only one direction and blocks any reverse current flow. This results in production of a charge across the capacitor which follows the *peak* values of the radio-signal envelope waveform. The headphones are operated by this voltage. Fig. 2 shows the waveforms and

sensitive (cannot pick up weak signals), has poor selectivity (cannot separate a single signal from all the rest), and has low output (earphones only, and no control of volume).

Selectivity was improved in crystal-set days by adding tuning circuits between

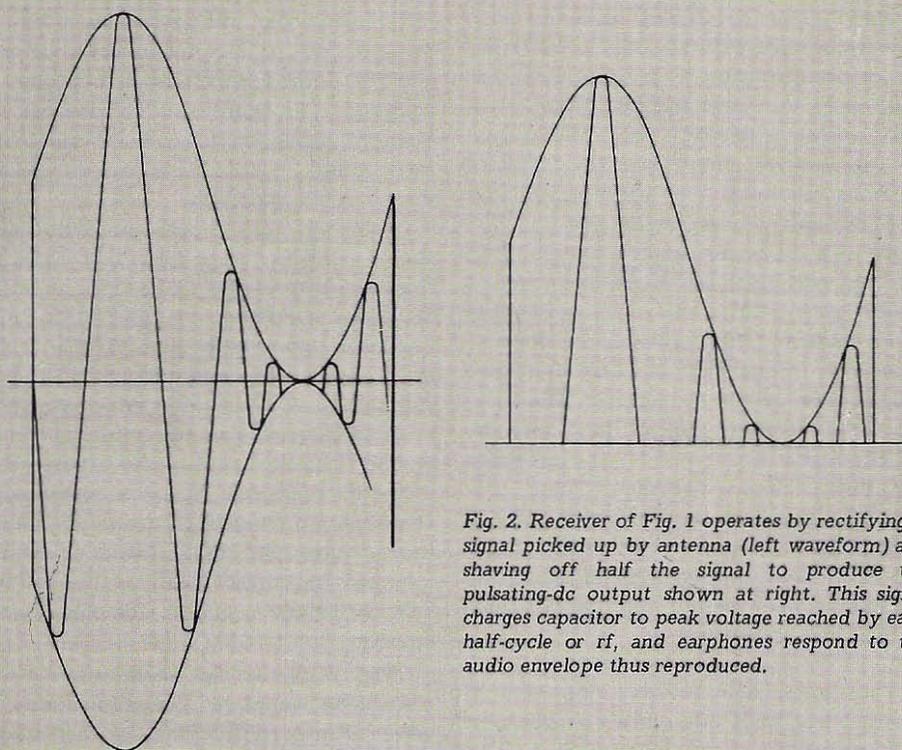


Fig. 2. Receiver of Fig. 1 operates by rectifying rf signal picked up by antenna (left waveform) and shaving off half the signal to produce the pulsating-dc output shown at right. This signal charges capacitor to peak voltage reached by each half-cycle or rf, and earphones respond to the audio envelope thus reproduced.

brings out how the rectifying action of the diode causes the modulation envelope to be reproduced across the capacitor.

Such a receiver as this will have little or no selectivity. That is, it will receive *all* radio signals which reach it. Most will not produce enough power across the capacitor to operate the phones, so if you try it you probably will get only the strongest broadcast station in your area (and if you live more than 15 to 20 miles from the transmitter, you may not get even that). Some degree of tuning is provided by the antenna, but that's the only control over what you get.

Obviously, this simple circuit suffers from three major problems. It is not very

antenna and detector. As many as three or four separate tuned circuits were found in the fancier sets, and they helped to shave reception down to the desired signal. However, they could not produce enough selectivity to separate two signals only a few kHz apart — and they did nothing for sensitivity or output.

It took the vacuum tube to do much for receiver performance in the areas of sensitivity and output volume. The amplification made possible by the tube could be used at either radio frequency, to provide added sensitivity by producing a stronger signal to the detector than the antenna alone could produce, or audio frequency following the detector, to provide louder

output. Normally it was used both places — and still is.

Early vacuum tubes were expensive, and experiments were hard-pressed to obtain more than one at a time. Ingenious circuits were devised to permit this one tube to amplify the signal at rf, then detect it, and amplify the resulting audio some more, all in the same stage.

Then Major Armstrong came up with the regenerative detector, which made use of positive feedback to produce both exceptionally high gain and very sharp selectivity within a one-tube stage. For years, the regenerative circuit was the standard for both amateurs who could afford the tube, and commercial installations.

By this time researchers had realized that the particular set of problems represented by a radio receiver had no simple direct solution. Radio communications require high frequencies, but amplifiers give greatest gain at low frequencies. Similarly, selectivity requires sharp tuned circuits, but the higher the frequency the less sharp any tuned circuit becomes. These problems, as much as anything else, limited early radio to frequencies below the upper end of today's broadcast band. Available receivers simply would not operate properly at higher frequencies.

The regenerative receiver amounted to an oscillator with not quite enough feedback provided to sustain oscillation. This gave extreme gain and excellent selectivity. By this time, CW transmitters were replacing the noisy sparkgaps, and the regenerative receiver also turned out to be excellent for receiving CW signals (which the diode detector simply could not detect). All that was necessary was to push the receiver just over the line into oscillation; the oscillating receiver was then tuned to a frequency just a few hundred cycles off from that of the transmitter. The receiver's own rf mixed with the incoming rf from the transmitter to give a "beat note" or "heterodyne" signal equal to the difference between receiver and transmitter frequencies, and this pure tone was easy copy. This technique was known as "heterodyne reception".

While serving overseas during World War I, Major Armstrong had what was probably his most important of many new ideas. He saw how to eliminate all the problems of reception by applying the heterodyne principle in a new way. Rather than offsetting local and received frequencies by an amount in the audio range as was done for heterodyne reception, why not make the difference come out in the lower end of the rf range, at a point where good gain and the desired selectivity could easily be achieved. The resulting "intermediate frequency" signal could then be redetected into audio, after being amplified and shaved down as desired.

That was the "superheterodyne" idea, and it's still in use in essentially the same form its inventor first conceived. A superhet today will have, as a minimum, a local oscillator to provide the offsetting frequency, a mixer stage to combine the local and signal frequencies into the intermediate frequency or i-f, an i-f amplifier, a second detector, and audio stages. Most will also have one or more stages of rf amplification preceding the mixer (sometimes called the first detector), and if intended for communications use, will provide heterodyne action for the second detector.

Fig. 3 shows the stages of a single-conversion superhet communications receiver. The purpose served by each stage is described in the following paragraphs.

The rf amplifier's primary purpose in superhets operating below the VHF range is to isolate the local oscillator from the antenna and thus prevent interference by the receiver to other receivers. At VHF, the rf amplifier serves primarily to boost the signal strength and thus help overcome noise problems, but at HF and lower frequencies ample gain is available in later stages.

The local oscillator provides the "offset frequency" signal and thus controls the receiver's tuning. The receiver will pick up only signals which are separated from the local-oscillator frequency by the amount of the i-f frequency, and so changing the frequency of the local oscillator changes

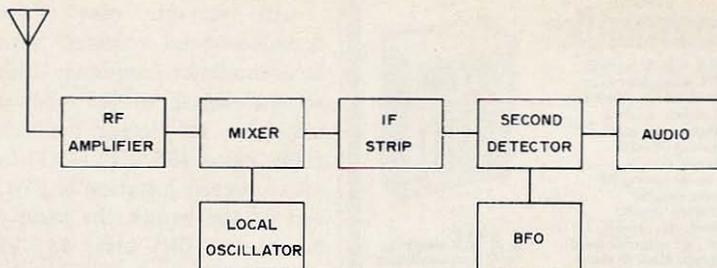


Fig. 3. Basic stages of a conventional superheterodyne receiver are shown here and described in text. Rf amplifier and bfo are not normally included in non-communications superhets for entertainment use, but are considered essential in quality communications receivers.

the frequency to which the receiver is tuned. The local oscillator must be stable; that is, its frequency must remain constant once set. Otherwise the receiver will "drift" off frequency and will require frequent retuning.

The mixer or "first detector" operates in the same manner as the amplitude modulator we examined in the last chapter, combining two input signals at different frequencies to produce four output signals which are at the two original frequencies, their sum, and their difference. Most often only the difference frequency is of interest. The mixer actually gets many more signals in, and produces many more out, because all the signals which make it through the rf amplifier stage are acted upon by the mixer. The relative frequency difference between different signals is much greater at the output than at the input, however, because the mixer essentially subtracts a constant (the local oscillator frequency) from each of its input signals.

The i-f strip is the heart of the superhet receiver. This block consists of one or more stages of rf amplification, operating at a fixed and relatively low frequency. For many purposes, the standard intermediate frequency is 455 kHz. At this low frequency, very sharp selectivity may be attained, yet good gain is still possible. The i-f amplifiers are set to one frequency and left there (a process called "alignment"), and thus the receiver's gain and selectivity are the same at any frequency within its tuning range. Because of its selectivity, the i-f strip accepts only one of the many signals appearing at the mixer output; all

the rest are eliminated, but the one signal accepted goes on through and is amplified to respectable strength before reaching the second detector.

The second detector is essentially the same as the simple diode detector of Fig. 1; since both sensitivity and selectivity have been provided by the preceding stages, the only function of this stage is to convert the i-f signal into audio.

For reception of CW and SSB signals, a beat frequency oscillator (bfo) may be provided. This oscillator produces a signal offset from the i-f by a difference within the audio range; normally, it includes a "pitch control" which adjusts its output frequency to fall either side of the i-f. The bfo output is fed to the second detector along with the i-f when heterodyne reception is desired. In more recent designs, the bfo is sometimes included as part of a separate "product detector" circuit which is switched in to replace the second detector for heterodyne reception. We'll look at this more closely in the next section.

Once the incoming signal is converted to audio by the second detector or its equivalent, the audio is then amplified to drive a loudspeaker (if desired) by the audio section.

Everything has a price, and the performance of the superhet is no exception. Since the basic principle is that of converting an incoming signal to an intermediate frequency by mixing action, which produces both a sum and a difference signal, it's possible to receive two different signals simultaneously with a superhet. Such action is called "image" reception.

oscillator/monitor ^{mark 2}

- makes an audible tone to monitor the RF of any CW transmitter from 10Mw to 1 Kw & 100Kc to 1000Mc, using only an 8' pickup antenna.
- can be self-triggered for code practice or the testing of solid state components and circuits.
- aids in tuning up & testing RF oscillator and power circuits.
- A transistor, 2 diode circuit, speaker, tone adjust, AA pencil, test tips, 8" ant., & magnetic base.
- cabinet is 16 gauge black & clear anodized aluminum, 3.4 x 2.3 x 1.2" US made & guaranteed for 1 year.



14.95 complete,
ppd usa & can.
send a check or m.o.
sold by mail only

James Research company, dep't: AR-M
20 willits road, glen cove n.y. 11542

HAL DEVICES

TTL INTEGRATED CIRCUITS

HAL is now stocking NEW 7400 series TTL IC's. Available are 7400, 7401, 7402, 7404, 7405, 7410, 7420, 7430, 7440, 7441, 7442, 7473, 7475, 7490, and 7493. Write for prices and complete catalog. **HAL DEVICES BOX 365L, URBANA, ILLINOIS 61801**

HAL DEVICES

Hot Carrier Diodes: HP2800 90¢ 12/\$10.00 Matched by HAL 4/\$4.25
IC's: 1 μ L 900, 914 60¢ 1 μ L 923 90¢
MRTL MC790P, MC890P \$2.00, 10/\$19.50
MC724P, MC789P, MC792P, MC725P \$1.05, 10/\$9.50
Also available: MC723P, MC788P, MC880P, MC767P, MC9760P.
OP AMP: SN72709N (DIP), SN72709L (TO-5) \$1.25
TOROIDS: Indiana General CF102-06, CF102-01, CF101-02 50¢
CINCH IC sockets, 14-DIP, 8-ICS 60¢ **HAL DEVICES**
Add 50¢ Postage, send for complete list. **Box 365 L, Urbana, Illinois 61801**



radio amateur

callbook

Radio Amateur Emblems engraved with your call letters.



Charm

- Gold
 Rhodium
call letters
\$6.00 Ea.



Tie Bar

- Gold
 Rhodium
call letters
\$6.00 Ea.



All illustrations are actual size.

Lapel Pin

- Gold
 Rhodium
call letters
\$6.00 Ea.

Two or more emblems at the same time \$5.00 each.

Rush Order To: RADIO AMATEUR CALLBOOK, Inc.

Dept. B 925 Sherwood Drive, Lake Bluff, Ill. 60044

An example may make it clearer. Broadcast-band receivers usually have the local-oscillator frequency higher than that of the signal to be received (partly to minimize the image problem), and normally use a 455 kHz i-f. Thus when one is set to receive a station at 610 kHz (the low end of the band), the local oscillator will be set to 1065 kHz, 455 kHz higher, in order to produce a difference frequency of 455 kHz.

Unfortunately, with the oscillator at 1065 kHz, any incoming signal at 1520 kHz which happens to reach the mixer stage will also produce a 455 kHz output (1520 - 1065), which the i-f stage will not be able to distinguish from the desired signal. Thus the 1520 kHz signal can and will interfere with the desired one at 610 kHz.

The characteristic of image reception is that the undesired signal is always separated from the desired one by twice the i-f, and is on the other side of the local-oscillator frequency.

Another aspect of the image problem, which shows up on many inexpensive ham receivers, is the possibility of tuning the same signal in at two places on the dial. To reverse our previous example, you could tune in the 1520 kHz station either at its true frequency of 1520 kHz, or at the image point 910 kHz lower, 610.

As the signal frequency gets higher, with a constant i-f, the separation between true and image points becomes proportionately smaller. In the 40 meter band, for instance, 8 MHz commercial signals show up on top of 7 MHz ham signals, and the ham signals themselves can also be tuned in around 6 MHz if you like. By the time you get to the 10 meter region, ham signals at 29.5 MHz can be causing interference with other ham signals around 28.59 MHz.

Since the separation between true and image points is always twice the i-f, one solution to the image problem is simply to use a higher i-f. If the i-f is raised to 1600 kHz, for instance, the true and image points will be separated by 3.2 MHz, and then a single rf stage ahead of the mixer normally will reduce the image response to the point that it is not objectionable.

Unfortunately, the higher the i-f, the poorer the sensitivity and selectivity of the receiver.

One of the more ingenious solutions to this problem was the invention of the "double superhet" or "double conversion" system. This is essentially two superhets end to end, with the mixer of the second taking the place of the second detector of the first as shown in Fig. 4.


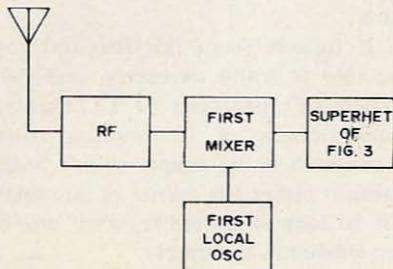


Fig. 4. Double-conversion superhet duplicates "front-end" circuitry of single-conversion superhet, then uses entire single-conversion superhet at output of first-mixer. Resulting composite circuit has two local oscillators, two mixers, and two i-f strips (rf stage of single-conversion receiver becomes first i-f of double-conversion circuit). Advantage is improved image rejection because first i-f can be relatively high frequency, while maintaining selectivity and gain with low-frequency second i-f.


The first i-f is picked for best image rejection, while the second is chosen for gain and selectivity. One popular receiver using the double-conversion principle used 1825 kHz as the first i-f, and converted this down to 85 kHz for the second to achieve high selectivity.

When double conversion is used, either the first or the second conversion oscillators may be tuned. Use of a VHF converter ahead of a tunable communications receiver is an example of double conversion with the second oscillator being tuned; the converter produces an i-f between 14 and 18 MHz, for instance, and the receiver then tunes over this band. Many high-performance receivers now make use of double conversion with tunable second oscillators in order to achieve high stability in frequency, and to get the same tuning rate on each band covered (since the tuning is always the same).

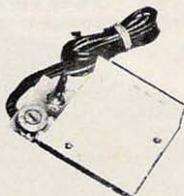AT LAST -- A SPEECH COMPRESSOR THAT REALLY WORKS!



RPC-3,3U Internal Unit
(\$24.95)

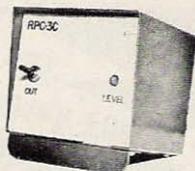

RPC-3C Cabinet Model
(\$34.95)

- Low distortion circuit.
- Fully wired & tested. NOT A KIT
- Works with phone patch.
- Internal units & modules work mobile.
- FULL WARRANTY — ONE YEAR
- INTRODUCTORY LOW PRICES
(Illinois residents add 5% Sales Tax)



RPC-3M Module
(ONLY \$22.50)

Write for specifications and information sheets (Free). Demonstration Tape (cassette) available (\$2.00 deposit).

RP ELECTRONICS

Box 1201 B Champaign, Ill. 61820

A 2M PREAMPLIFIER

12 vdc powered.
27 db gain (approximately)
noise figure 2.5
will take Regency HR-2
or Motorola to 0.1 μ v sensitivity
without appreciable noise.

Metal case. ONLY \$17.95 ppd

CRAWFORD ELECTRONICS

302 West Main, Genoa IL 60135

OOPS!

ABSOLUTELY CORRECT ADDRESS

EPSILON RECORDS

508 EAST WASHINGTON ST.
ARCOLA - ILL. 61910



TRANSKEY (TM)

\$34.95

Postpaid
Electronic
Keyer and
Monitor

W6PHA — GLOBAL IMPORT CO.
BOX 246, EL TORO, CALIF. 92630

**MORE RANGE . . .
with NO NOISE**

**FOR ALL
MOBILE UNITS**




ESTES ENGINEERING COMPANY
ELECTRO-SHIELD

**CUSTOM SYSTEMS
KITS • ACCESSORIES**

**ELIMINATE IGNITION NOISE
ELECTRO-SHIELD®
YOUR ENGINE**

FROM \$44.95

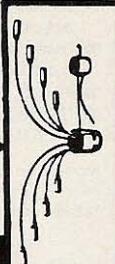

ESTES ENGINEERING CO.
543 W. 184th St., Gardena, Calif. 90247

VHF CONVERTERS

We manufacture a complete line of converters for 50 through 432 MHz. Models to suit all needs — DX, FM, ATV, MARS, etc. A postcard will bring our new FREE CATALOG with pictures, schematics, specifications and prices.

JANEL LABORATORIES P.O. Box 112
Succasunna, N. J. 07876
TEL: 201-584-6521

HOT WEATHER SPECIAL

BW COAXIAL SWITCH Model 550A-2
was \$14.40 **NOW ONLY \$7.43**

BARKER & WILLIAMSON, INC.
Canal Street, Bristol, Pennsylvania 19007

ARNOLD'S ENGRAVING
Personalized

ELECTRIC ON-THE-AIR SIGN WITH CALL



Works on 110 VAC \$12.95



WA2ZHA

Metallex Lapel Bar - \$1.50 Metallex Tie Clip - \$2.25

ARNOLD'S ENGRAVING
2041 Linden St. Ridgewood, N.Y. 11227

How Does SSB Work?

In the preceding chapter we made the acquaintance of "sidebands" and found that sidebands are necessary in any kind of modulated signal — in fact, that sidebands carry the information which composes the "modulation" of that signal.

We also saw that any modulated signal has two sidebands, one on either side of the carrier, which are mirror images of each other.

It follows from this that only one of the two is really necessary, and that the carrier isn't necessary at all. That is, the same amount of information could be transmitted if we simply didn't bother to transmit either the carrier or one sideband, just so long as we did transmit one of the two sidebands accurately.

Since with AM modulation the limit of 100% modulation is reached (with sine-wave signals) when the modulating signal has half as much power as the carrier wave, and since this modulating signal's energy is split between the two sidebands, that means that 3/4 of the power transmitted from an AM station is useless; all of the information can be recovered properly from one sideband, which represents only 250W of the power transmitted from a 1 kW transmitter.

That's what SSB is all about — the technique of taking advantage of these facts, to achieve that 4-to-1 power advantage by concentrating all the transmitted power in the only meaningful part of the signal, and simultaneously to conserve space in the rf spectrum by holding the bandwidth of the signal down to half that of a conventional AM transmission.

Unfortunately, doing so is not so simple as we may have just implied. Getting rid of the carrier and one sideband requires special circuitry in the transmitter, and in addition SSB signals cannot be received as simply as can those from ordinary AM stations. The missing carrier must be put back into the signal at the receiver in order to recover the audio, and that's a bit of a job.

SSB has been in use since 1927, but until 1948 was applied only to commercial

telephone communications. The first ham station to use SSB was apparently W6YT, the Stanford University club station, but within a matter of weeks after W6YT appeared with SSB a number of other stations followed suit. Today, SSB is rapidly approaching the state of being the "standard" means of voice communication on HF ham bands.

A number of factors combined to produce the 21-year delay between first use of SSB and hams' acceptance of the technique. Most of them boiled down to the fact that at first, it was simply not simple enough to be practical for the vast majority of hams. Costly installations and special equipment were required. The advances in radio technique during World War II changed this situation and made it practical for hams to take up SSB operation.

Still, SSB is nowhere near as simple as ordinary AM, either to generate for transmission, or to receive. In addition to all the functions of a normal AM transmitter, the SSB transmitter must include facilities for removing the carrier and unwanted sideband from the signal. These normally operate properly only at low signal levels, and once the signal is converted into SSB it cannot be amplified by normal rf power amplifiers (which would introduce distortion). This introduces the requirement for linear amplifiers, which are more difficult and critical to adjust than are ordinary class C stages.

Once the signal is generated and transmitted, it must be received. Frequency stability is necessary in an SSB receiver, because a drift in receiver tuning of as little as 20 Hz is noticeable, and a 100 Hz drift renders the signal unreadable in most cases. The receiver must, in addition to having high stability, include provisions for putting the carrier back into the signal for detection, and this means that heterodyne reception is necessary.

Let's look at the requirements for both generation and reception of SSB signals, now that we have a general idea of how they differ from conventional AM techniques. We'll take the transmitter first.

Figure 5 shows a block diagram of a



CAMP ALBERT BUTLER RADIO SESSION 12th YEAR — 600 GRADUATES

Courses Taught: General Theory and Code
Advanced Theory and Code
Amateur Extra Theory and Code

Golf privileges at New River Country Club; also fishing

TRULY A VACATION WITH A PURPOSE!!!

People attended from the following states and areas:

North Carolina, South Carolina, Missouri, Tennessee, Utah, Florida, Oklahoma, West Virginia, Alabama, New Hampshire, Iowa, District of Columbia, Vermont, Arizona, Indiana, Ohio, New Jersey, New York, Massachusetts, Maryland, Virginia, Illinois, Michigan, Georgia, Kansas, Mississippi, Nebraska, Maine, Kentucky, California, New Mexico, Arkansas, Texas, Wisconsin, Louisiana, Oregon, Connecticut, Minnesota, Pennsylvania.

OUT OF STATE:

Puerto Rico; Saskatchewan, Canada; Ontario, Canada; Quebec, Canada; Granada, Spain; London, England; Geneva, Switzerland; Netherland, Antilles; St. Croix, Virgin Islands

C.L. Peters, K4DNJ, General Secretary
Gilvin Roth Y.M.C.A., Elkin, North Carolina

Please send me the Booklet and Application Blank for the Camp Albert Butler Radio Session.

Name _____ Call _____

Address _____

City/State/Zip _____

HILLTOPPERS
INSTANT ERECTING
3 EL 6M . . . \$14.95
8 EL 2M . . . \$16.95

We also make Saturn 6 Halos - 6 & 2 M Beams
HI-PAR PROD. BOX 88 FITCH. MA 01420

WORLD QSL BUREAU
5200 Panama Ave., Richmond CA USA 94804
NO POSTAL INCREASE

QSLs forwarded to anywhere
Only 4¢ each

FRECK RADIO SUPPLY

38 Biltmore Ave., Asheville, N.C. 28801
(704) 254-9551

Serving the amateurs for 43 years
(Established 1928)

Send for our free list of used equipment. Over 300 pieces to choose from. Also new in stock
● Collins ● Drake ● Kenwood ● Galaxy
● Tempo ● Signal 1 ● Swan ● "Factory Direct Prices on Swan"

"WE TRADE HIGH" TRY US

Bank Americard - Master Charge

Tenny Freck W4WL — Sandy Jackson Mgr.
Harvey Nations W4VOV

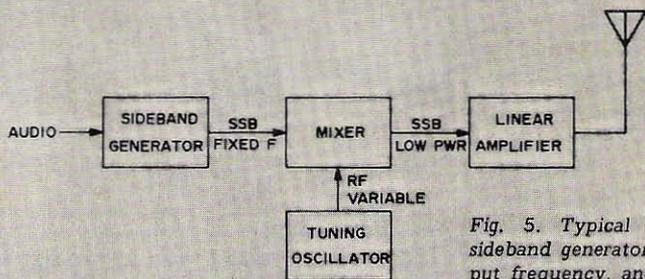


Fig. 5. Typical SSB transmitter consists of sideband generator, provisions for changing output frequency, and linear amplifiers. See Figs. 6 and 7 for details of sideband generators.

typical SSB transmitter, contrasted with that of a typical AM transmitter. The difference in complexity is obvious.

In the SSB transmitter, the audio is applied to a sideband generator stage where it is converted to an rf signal which reproduces the audio at some radio frequency. This is done by a variation of the normal AM process, but the carrier and unwanted sideband are removed before the signal gets out of the sideband generator. Output of the sideband generator is an SSB signal, but is not necessarily at the desired signal frequency because it turns out to be much simpler to always generate the SSB signal at the same frequency, and then translate it by a mixing operation to the desired frequency for transmission.

Sideband generator output, therefore, is applied to a mixer stage, and an output-frequency tuning signal is applied to the mixer's other input. This output tuning signal may be obtained either from a fixed-frequency oscillator such as a crystal circuit, or from a stable vfo. The mixer's output includes an SSB signal at the desired output frequency, which is selected and amplified to the output power level by means of linear amplifiers.

The sideband generator stage is the heart of the SSB transmitter, and warrants additional examination. At least three different techniques for sideband generation are known, but only two of these are used in practice. They are known as the "filter method" and the "phasing method."

Both the filter and phasing methods make use of "balanced modulator" circuits, which are special types of mixers

which eliminate one of the two input signals from their outputs. These balanced mixers are usually set up to eliminate the carrier signal, because the audio signal (at a far different frequency) can easily be rejected by tuned circuits. Output of an SSB balanced modulator, then, usually consists only of the two mirror-imaged sidebands which result from the mixing process.

Figure 6 shows a block diagram of a filter-method sideband generator. Incoming audio and the rf carrier signal are applied

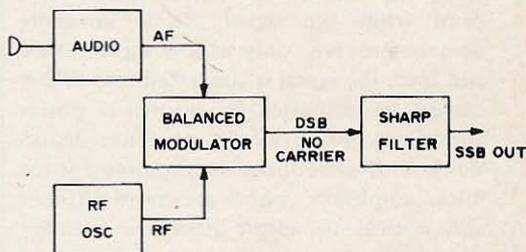


Fig. 6. Filter-method sideband generator converts audio and fixed-frequency rf into double-sideband suppressed carrier signal using balanced modulator, then filters away one sideband to produce SSB. Filter may use crystals or mechanical technique, and may operate at frequencies from 17 kHz up to 9 MHz.

to a balanced modulator, where the original signals disappear. Output of the balanced modulator is a double-sideband (DSB) signal with both carrier and audio suppressed. This DSB signal is then passed through an extremely sharp filter, which shaves off one of the two sidebands, and passes the other relatively unaffected. Output of the filter, therefore, is the desired single sideband signal.

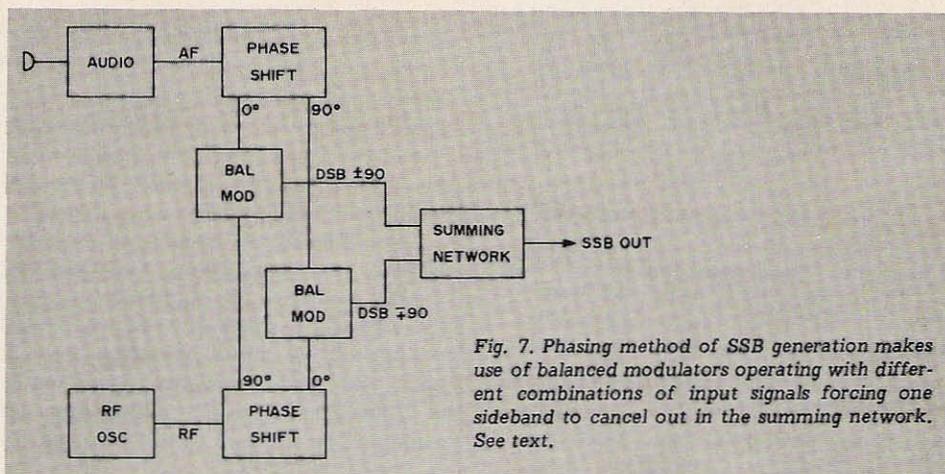


Fig. 7. Phasing method of SSB generation makes use of balanced modulators operating with different combinations of input signals forcing one sideband to cancel out in the summing network. See text.

The phasing method (Fig. 7) is more complex, but eliminates the need for the sharp (and costly) filter. Incoming signals, both audio and rf, are applied to phase-shifting networks. The phase shift networks produce pairs of outputs, which are identical except that they differ from each other in phase by 90 degrees.

One audio-rf pair is applied to one balanced modulator, and the other pair goes to a second balanced modulator. Outputs of these two balanced modulators are double sideband signals.

The balanced-modulator outputs differ from each other in phase, however. Because of the phase shift introduced into the signals before mixing, one sideband (either the upper or the lower one) will have the same phase in both modulator outputs, while the other sideband will have a 180-degree phase difference between one modulator output and the other.

The two outputs are combined in a summing network, where the sideband with no phase difference survives while the one with 180-degree phase difference cancels itself out. The output of the summing network is, therefore, the desired single sideband signal.

Both the filter method and the phasing method have advantages and disadvantages. The filter is simpler in concept, but requires components which are usually more costly. On the other hand, phasing is less expensive but requires more critical adjust-

ments. Either technique is capable of producing outstanding results — or garbage, depending upon the skill and care of the operator.

Once the sideband generator produces an SSB signal, regardless of the method used to obtain it, the mixer (Fig. 5) translates it to desired output frequency and its power level is determined by linear amplifiers.

Now that we understand how SSB is generated and transmitted, let's look at how it is received:

Almost any receiver capable of copying CW signals *can* be used for SSB reception, but for generally satisfactory results an SSB receiver should have high frequency stability, a slow tuning rate, and sharp selectivity. We've already seen why stability is required. The tuning rate goes right along with it; when a 20 Hz error causes distortion, you want to be able to make fine tuning adjustments slowly.

The selectivity is required in order to take maximum advantage of SSB's narrower bandwidth. Best use is made of a signal if the receiver bandwidth exactly matches that of the signal, because if the receiver covers a wider band than the signal occupies, the leftover space will contribute noise to the receiver's input and thus degrade total performance.

The receiver must be capable of heterodyne reception to recover the audio from the SSB signal. Detection, like modulation,

GATEWAY ELECTRONICS

6150 DELMAR BLVD., ST. LOUIS, MO 63112
314-726-6116

6 MFD. - 5000 VDC CAPACITOR 11x4 1/2x3 3/4	
Ship Wt. 10 lb.	\$15.00
12 VDC - 5 Ma MINIATURE RELAY - 3 AMP Contacts SDPT - Size 1/2" cubed.	
Ship Wt. 1/4 lb.	1.50
6 VDC - 5 Ma MINIATURE RELAY - 3 AMP Contacts SPDT - Size 1/2" cubed.	
Ship Wt. 1/4 lb.	1.50
24 VOLT CENTER TAPPED TRANSFORMER - 1 AMP 2 1/2 x 2 x 2	
Ship Wt. 1 lb.	2.00
36 VOLT CENTER TAPPED TRANSFORMER - 2 1/2 AMP 2 3/4" Square	
Ship Wt. 2 lb.	2.00
12 VOLT CENTER TAPPED TRANSFORMER - 1/2 AMP 2" Square	
Ship Wt. 1/2 lb.	1.25
DIODES - 100 PIV - 1 AMP TOP HAT	
Ship wt. 1/8 lb.	12/1.00
MC-718 IC-DUAL 3 Input Nor Gate	.60
MC-719 IC-DUAL 4 Input Nor Gate	.60
MC-724 IC-QUAD 2 Input Nor Gate	.60
MC-798 IC-DUAL 2 Input Buffer	.60
SN15862 Triple 3 Input Nand/Nor Gate	.60

Write for catalog - See last month's ad for other I C Prices. Stop in and see us when you're in St. Louis.

FM Schematic Digest

A COLLECTION OF
MOTOROLA SCHEMATICS
Alignment, Crystal, and Technical Notes
covering 1947-1960
136 pages 11 1/2" x 17" ppd \$6.50

S. Wolf
1100 Tremont Street
Boston, Massachusetts 02120

F.M. MOTOROLA GOVERNMENT SURPLUS



Also - Power Supplies,
Amplifiers, Modules, etc.
Write - Dept. 73

	Used: Recond.:
R-394 RECEIVER	152-172 MC... \$14.95 \$22.50
T-278 TRANSMITTER	152-172 MC... 18.95 24.95
R-257 RECEIVER	25-50 MC... 19.95
T-208 TRANSMITTER	25-50 MC... 29.95
CY-938 CABINET	7.95 9.95
C-847 CONTROL BOX	8.95 12.95

Send For Our BIG CATALOG No. 71

FAIR RADIO SALES
1016 E. EUREKA · Box 1105 · LIMA, OHIO · 45802

is actually a mixing process. In a conventional AM detector, the sidebands are mixed with the carrier, and the difference frequency (which is the audio involved) is taken as output. Since the SSB signal has no carrier to mix against, an external carrier must be supplied.

SSB forced recognition of the basic identity of modulation, detection, and mixing - and led to improved techniques for detection when the principles long established for mixer operation were applied. The resulting circuits are now known as "product detectors" and provide outstanding performance for both CW and SSB signals.

A good agc system is convenient to have in an SSB receiver, because the signal strength varies widely and rapidly. This creates some problems, because conventional AM receivers drive their agc (sometimes called avc) systems with a signal derived from the carrier strength (the same signal drives the S-meter), and SSB has no carrier. The problems have been solved in many different ways, and again CW operators as well as SSB users have benefited.

The block diagram of a typical single-conversion selectable sideband receiver intended for AM/SSB/CW operation is shown in Fig. 8. The circuit may be compared with Fig. 3, which shows the conventional version of a similar receiver. You can see that the sideband receiver contains all the functions required for ordinary reception, and merely adds a few new ones to handle SSB.

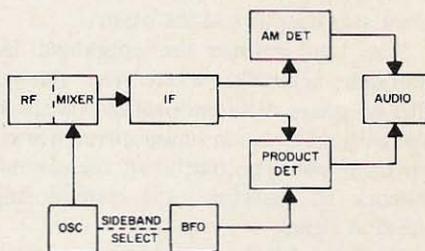


Fig. 8. Selectable sideband receiver shows great similarity to ordinary receiver (Fig. 3), but with added extras to facilitate SSB reception. Actually, any receiver capable of receiving CW can tune in SSB, but extra features shown here are needed for extended use.

The purposes served by these added functions have been indicated in the preceding paragraphs. Naturally, many more functions *could* be added. For instance, most selectable sideband receivers involve double-conversion techniques to achieve sideband selection. For this, add the features of Fig. 4.

How Is Receiver Performance Rated?

Now that we know all that we need to at this stage about both receivers and SSB operation, let's look at the factors by which various receivers are rated and compared with each other.

We've been using some of these factors all the way through without bothering to specifically define them. This is the point at which we will remedy that situation and provide definitions.

The three major performance points involved in rating receivers are (1) sensitivity, (2) selectivity, and (3) stability.

Sensitivity is a measure of how weak a signal can be received, or to put it another way, of how strong a signal must be in order for the receiver to pick it up. Different techniques for measuring sensitivity are used in different parts of the frequency spectrum. In the normal ham bands, a measurement of signal level in microvolts (μV) is about as frequently encountered as is any other rating. The smaller the rating, the more sensitive the receiver. That is, a receiver rated at $1 \mu\text{V}$ sensitivity is ten times as sensitive as one rated at $10 \mu\text{V}$, all other conditions remaining equal.

It's necessary to be cautious in comparing receiver sensitivity ratings, though, because the "microvolt" rating is meaningful only when the impedance across which this voltage is to be measured is specified. For instance, a receiver rated at $10 \mu\text{V}$ across 300Ω does *not* have the same sensitivity as one rated at $10 \mu\text{V}$ across 75Ω . The first receiver is four times as sensitive as the second, because when impedance is stepped down so is the voltage, and $10 \mu\text{V}$ at 300Ω is equivalent to $2.5 \mu\text{V}$ at 75Ω .

Selectivity measures the receiver's abil-

CLOSEOUT! OVERHAULED & CERTIFIED COUNTERS

Solid-State 220 MHz: CMC 737CU, 7 nixies, plus 525A & B. Light and compact	575.00
510 MHz: Substitute 525C for 525B, add	150.00
10 Hz-15 GHz: Read freq. on 7 DCU's, no algebra: Beckman 7370/7580 combo	750.00
1 MHz Universal, 6 DCU's, Beck. or H.P.	149.50
1 MHz Universal, 6 Nixies, Hewl-Pack	195.00
2 MHz Universal, 6 DCU's, Beckman	195.00
Solid-State 5 Nixie 3 MHz, H.P. 5223L	275.00
Solid-State 6 Nixie 2 MHz, H.P. 5233L	395.00
Solid-State Preset & Freq., H.P. 5214L	275.00
8 lb 20 MHz solid-state, Simpson #2725	250.00
#2590A Hewl-Pack 15 GHz Transfer Osc	420.00

BRAND-NEW SOLID STATE SCOPE BARGAINS:

We are now the Distributor for Leader Instr. Corp. **QUALITY-CONTROLLED** imports. See their ad inside back cover. Warranty is 2 years on parts, 6 mos on labor. We pay the shipping to your door.

20-LB NAVY PORTABLE 4 Mhz SCOPE

AN/USM-32: 10 Hz to 4 MHz ± 2 db. Line 118v, 50-400 Hz. 3WP1 CR tube with rectangular mask & graticule. Sensit. 40 mv rms/cm & up, and includes calibrator, 350 nsec video delay line. Input 1 meg, 28 pf. Sweep triggered by signal, 3/4 usec/cm & up. 5 choices Z-axis Markers for exact calib. With schem. dwg. & op. instruct.

Good used \$129.50

(OHC at cost if desired, grtd not over \$50.)

TEKT' & HEWLETT-PACKARD SCOPE BARGAINS:

See our June ad for listing. ADD: Tekt. 515A at \$395 and 543B at \$695, both exc. cond., and 661 with 4S1 and 5T3 already overhauled & calib. at only \$1090.

REDUCED SUMMER RADIO-RECEIVER PRICES!

Take advantage of the usual summer sales slump and some real good buys we made. Start a Christmas Lay-Away purchase if you wish . . . we will hold them at no charge for holding. Every receiver put through a VERY competent shop, aligned, grtd 199% perfect, and clean. SP-600-JX, double-conversion 540 KHz continuous to 54 MHz, plus crystal control, if you wish, for your 6 most-favorite stations. In cabinet, \$299.50. Less cabinet but with top & bottom covers, \$275.00. R390/URR, triple-conversion, 500 KHz to 52 MHz with precision digital tuning and crystal zero-beat and corrector each 100 KHz . . . only \$595.00. R390A/URR adds the sharper CW selectivity of mechanical filters, only \$795.00. Dual-Diversity TTY converter AN/URA-8 in very exc. cond. grtd 100% OK only \$275.00.

If you don't see it here, ask for it!

Or ask for the *KIND of material you want. But don't ask for a general catalog . . . we believe that is nonsense in surplus . . . we get new things in almost every day! WE ALSO BUY!* So tell us what you have, condition, and your asking price.

R. E. GOODHEART CO., INC.
Box 1220-GC, Beverly Hills, Calif. 90213
Phones: Area Code 213, Office 272-5707

*Tell Our Advertisers
You Saw It in 73*

Even if you didn't.


**WE PAY CASH
FOR TUBES**

Lewispaul Electronics, Inc.
303 West Crescent Avenue
Allandale, New Jersey 07401

NEW G&G CATALOG! MILITARY ELECTRONICS

24 PAGES, crammed with Gov't Surplus Electronic Gear — the Biggest Bargain Buys in America! It will pay you to **SEND 25¢** for your copy — Refunded with your first order.

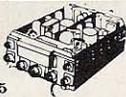BC-645 TRANSCEIVER 15 tubes, 435 to 500 Mc, Easily adapted for 2 way voice or code on Ham, Mobile, Television Experimental, and Citizens Bands. With tubes, less power supply in factory carton, BRAND NEW... \$16.95



SPECIAL PACKAGE OFFER: BC-645 Transceiver. Dynamotor and all accessories, including mounting. UHF Antenna Assemblies, control box, complete set of connectors and plugs. Brand New \$26.95

SCR-274-N, ARC-5 COMMAND SET HQ!

Freq. Range	Type Complete with Tubes	Exc. Used	Like New	BRAND NEW
RECEIVERS				
190-550 Kc	BC-453	\$16.95	\$23.50	\$27.50
6-9.1 Mc.	BC-455	\$14.95	\$17.95	\$21.50
1.5-3 Mc.	R-25		\$19.50	\$21.50

ARC-R11A Modern Q-5 Receiver 190-550 Khz \$10.95
ARC-R22 540-1600 Khz Receiver with tuning graph \$15.95
R-4 ARR-2 Receiver 234-258 MHz, 11 tubes, NEW... \$8.95

AN/APR - 4Y FM & AM RECEIVER "FB"

for Satellite Tracking!

High precision lab instrument, for monitoring and measuring frequency and relative signal strength, 38 to 4000 Mc, in 5 tuning ranges. For 110 v 60 cycle AC. Built-in power supply. Original circuit diagram included. Checked out, Perfect. LIKE NEW \$88.50
All tuning units available for above.



HEADSET Low impedance. With large chamois ear cushions. 4-ft. cord and plug. Reg. \$12.50. OUR SPECIAL PRICE \$2.95
Less Ear Cushions \$1.95
High impedance adaptor for above \$69¢



TG-34A CODE KEYS, self-contained, automatic, reproduces code practice signals from paper tape. 5 to 12 WPM. Built-in speaker. Brand new with tech manual, takeup reel and AC line cord \$24.50
Code practice tapes for above P. U. R.



TERMS: 25% Deposit with order, balance C.O.D. -or- Remittance in full. Minimum order \$5.00 F.O.B. NYC. Subject to prior sale and price change.

G&G RADIO ELECTRONICS COMPANY

47 Warren St. (2nd Fl) NYC, NY 10007 Ph 212-267-4605

WE PAY HIGHEST CASH PRICE

for Electron Tubes & Semiconductors
Immediate Payment on Unused Tubes
H & L ASSOCIATES

Elizabethport Industrial Park
Elizabeth, New Jersey 07206
(201) 351-4200

SURPLUS TEST EQUIPMENT

Electronic Parts, Tubes, Radios
New & Used Amateur Gear.

Send 25¢ for flyer listing hundreds of bargains, and we'll add your name to our permanent mailing list.

JEFF-TRONICS

4252 Pearl Rd. Cleveland, Ohio 44109

ity to separate signals which are close to each other in the spectrum. Again, there are many different ways to rate this ability. The normal way is to specify a bandwidth, or two bandwidths, together with a rejection level. If only a bandwidth is given, the rejection level is normally understood to be 3 dB or 70% voltage (half power).

Thus a 10 kHz bandwidth rating for selectivity does not mean that a signal 11 kHz away will be totally rejected. It means only that signals 10 kHz from the frequency to which the receiver is tuned will be reduced in strength to 70% voltage or half power.

If 6 dB bandwidth is rated at 6 kHz and 60 dB bandwidth is rated at 12 kHz, though, excellent selectivity is indicated. This says that signals 6 kHz away from center frequency will be cut to half voltage, and those just twice that far away will be trimmed to 1/1,000,000 their voltage level. This amounts to complete rejection, in most cases.

Another facet of selectivity has to do with "image rejection." This is a quality unique to superhet circuits, which we met earlier. Image rejection is usually rated in dB, and refers to the amount of rejection of the unwanted or "image" frequency which is achieved. Anything better than 60 dB is excellent; many good receivers do not exceed 35 dB image rejection.

Stability, the final major performance point, refers to the receiver's ability to stay tuned to one spot over a period of time as the equipment heats up during use. Stability is often rated in terms of frequency drift, which in turn is usually quoted as so many cycles per unit of time. For instance, some receivers are rated for frequency stability "better than 20 Hz per hour," which says that this receiver will remain within 20 Hz of the spot to which it is tuned for at least an hour without readjustment of the tuning controls.

Less major performance points, but still important rating factors, include such items as the frequency coverage of the receiver, its power requirements, nature and level of audio outputs, etc.

Communications receivers usually come in one of four main categories with respect

COUNTING SYSTEM

3 PC. KIT

\$5.95



Includes SN7490 decade counter, SN7441 BCD decoder-driver, SN7475 quad latch with hookup instructions

FAIRCHILD IC "AMP"

Any 3 10% Discount!

Type	Description	Each
<input type="checkbox"/>	709 Operational	.88
<input type="checkbox"/>	710 Hi Speed Diff.	.88
<input type="checkbox"/>	711 Dual Comparator	.88
<input type="checkbox"/>	723 V. Regulator	1.19
<input type="checkbox"/>	741 Freq. Comp 709	1.50
<input type="checkbox"/>	2809 Dual 709	1.50
<input type="checkbox"/>	2747 Dual 711	1.98

LIGHT EMITTING DIODES

\$1.50 Any 2 for \$2.69

- Visible LED "brite red"
- Visible "brite red" sensor*
- Invisible infra-red LED
- Invisible infra-red sensor*



* With built-in Darlington amplifiers

10¢ Catalog on Fiber Optics, 'ICs', Semis, Parts

Terms: add postage. Rated: net 30, cod's 25%

Phone Orders: Wakefield, Mass. (617) 245-3829

Retail: 211 Albion, St., Wakefield, Mass.

POLY PAKS

P.O. BOX 942 A
Lynnfield, Mass.
01940

GENERAL ELECTRIC 3-WATT AUDIO AMP

Any 3
10%
Discount!



\$3.95

3 for \$10

Lowest Prices

Brand New!

Delivers 3.5 watts continuous, 10 watts peak. With heat sinks; micro-mini size: 3/4 x 1/2 x 1/2". 9 to 30V supply. High sensitivity. 8 to 16 ohm. For mono & Stereo phonos, tape, FM, AM, TV, servo.

SPRAGUE- IC's 6 AMP FULL

Your Choice

3 for \$1

- 908 Full Adder
- 909 Buffer
- 912 Half Adder
- 913 Shift Register



PIV	SALE
50	\$0.88
100	.99
200	1.25
400	1.50
600	1.75
800	1.95
1000	2.25

WAVE
BRIDGE
RECTS

12

AMP
1000
PIV



2
for
\$1

HIGH VOLTAGE EPOXY RECTIFIERS

1 AMP EPOXY

PIV	SALE
<input type="checkbox"/> 2000°	1.00
<input type="checkbox"/> 3000	1.35
<input type="checkbox"/> 4000	1.65
<input type="checkbox"/> 5000	2.25
<input type="checkbox"/> 6000	2.96
<input type="checkbox"/> 8000	3.50
<input type="checkbox"/> 10000	3.95



SILICON
RECTIFIERS



SILICON

PIV	1Amp*	2Amp	3Amp
50	\$.05	\$.05	\$.08
100	.06	.06	.12
200	.07	.07	.15
400	.09	.09	.22
600	.12	.12	.28
800	.16	.16	.39
1000	.22	.22	.59

*microminiature

to frequency coverage. Commercial users often employ fixed-frequency receivers, which are permanently tuned to a single frequency. These find little use in ham work except for the VHF FM nets operating on a basis similar to police or taxicab radio dispatch networks.

In addition to the fixed-frequency group, receivers may be "general-coverage," "continuous coverage," or "ham band only." Inexpensive receivers are often general-coverage types, enabling reception of SW bands other than ham bands. The ham-band-only receiver, being designed to cover a smaller frequency range, often gives more performance per dollar since the design need make fewer compromises. Price is usually higher, however, because of limited demand for these units in comparison to the market for general entertainment receivers. Continuous coverage receivers are seldom seen; they provide complete coverage of their portions of the rf spectrum with no omitted regions. Normally these are laboratory instruments. Some military receivers, however, are of the continuous coverage type, and occa-

T-3 has a powdered iron core and is built like a TV fly back transformer. Operates at about 800 CPS. 12V DC Pri. using 2N442's or equivalent. DC output of V/DBLR 475 volts 90 watts. C/T feed back winding for 2N442's \$2.75 ea. -2 for \$5.00.
P-7 117 VAC Pri. Sec. # 1 185 VAC @ 120 ma. Sec. # 2 6.3 VAC @ 4A. Double Half Shell Metal Box Type. SX 146 type. \$2.75 ea. -2 for \$5.00.

SEE MARCH ISSUE FOR SUPER VALUES

TOWER COMMUNICATIONS
1220-22 Villa St., Racine, WI 53403

Thousands of Parts

ELECTRONIC PARTS & EQUIPMENTS

See us U Builders for Bargains (no fliers)

DOW TRADING CO. INC.

1829 E. Huntington Drive
Duarte CA 91010 - 213-357-3763

sionally appear in surplus and so reach the ham market.

Rating for power requirements and audio output is self-explanatory. These ratings must be compatible with your desires, or the receiver won't do you much good. It's worth noting that most better receivers do not provide a loudspeaker as standard equipment; it's an extra-cost option, because for many communications uses the speaker is unnecessary — and when it is, its characteristics may vary from job to job.

...Staff ■

73 Reader Service Coupon

Now we don't say that every single reader must buy every last product advertised in 73. We believe that, but we don't say it. The very least every reader can do is put on a show of interest in the products herein advertised. To make this a simple task, even for the laziest reader (now there is a contest for you!), we have cleverly arranged the advertising index to double as a reader's service coupon. All you have to do is tear it out (or photocopy it) and send it in with the appropriate boxes marked. (We have a prize for the most boxes marked... a silent prayer of thanks from the publisher). We'll accept postcards, slips of paper, or almost anything else that lists the companies you want to hear from and your address.

No one likes to go into a store without buying something, right? It is the same with these information requests. You will be expected to buy something. Oh, it doesn't have to be a \$50,000 antenna system, but it should be something modest... a transceiver... a linear... you know. We'll leave the decision up to you, knowing that we can trust you to do the right thing.

And we are definitely not saying that the use of this service coupon has any curative powers, but we cannot but notice that many readers report remarkable relief from simple backache, headaches, lumbago, and acid indigestion after sending in their coupon. Why take any chances?

ADVERTISER INDEX

- | | |
|---|--|
| <input type="checkbox"/> Allied 37 | <input type="checkbox"/> Janel 88 |
| <input type="checkbox"/> Alpha 62 | <input type="checkbox"/> Lewispal 93 |
| <input type="checkbox"/> Ameco 36 | <input type="checkbox"/> Mann 57 |
| <input type="checkbox"/> American Crystal 76 | <input type="checkbox"/> Micro Communications 71 |
| <input type="checkbox"/> Arnold 88 | <input type="checkbox"/> Motorola Cover III |
| <input type="checkbox"/> ATV 75 | <input type="checkbox"/> Murch 69 |
| <input type="checkbox"/> B&W 88 | <input type="checkbox"/> National 23 |
| <input type="checkbox"/> Callbook 62, 76, 86 | <input type="checkbox"/> Page 82 |
| <input type="checkbox"/> Camp Albert Butler 89 | <input type="checkbox"/> Pal 74 |
| <input type="checkbox"/> Circuit Specialists 75 | <input type="checkbox"/> Paradd 82 |
| <input type="checkbox"/> Clegg 69 | <input type="checkbox"/> Pickering 75 |
| <input type="checkbox"/> Computronics 44 | <input type="checkbox"/> Poly Paks 95 |
| <input type="checkbox"/> Crawford 87 | <input type="checkbox"/> Regency Cover II |
| <input type="checkbox"/> Digitone 81 | <input type="checkbox"/> RP Electronics 87 |
| <input type="checkbox"/> Dow 95 | <input type="checkbox"/> Sentry 47 |
| <input type="checkbox"/> Drake Cover IV | <input type="checkbox"/> Sonar 35 |
| <input type="checkbox"/> DyComm 53, 65 | <input type="checkbox"/> Standard 51 |
| <input type="checkbox"/> EKY Video Vision 76 | <input type="checkbox"/> Southwest Radio 82 |
| <input type="checkbox"/> Electra 61 | <input type="checkbox"/> Telecom 33 |
| <input type="checkbox"/> Epsilon 81, 87 | <input type="checkbox"/> Telrex 31 |
| <input type="checkbox"/> Estes 88 | <input type="checkbox"/> Tower 95 |
| <input type="checkbox"/> Fair 92 | <input type="checkbox"/> Vanguard 21, 74, 81 |
| <input type="checkbox"/> Freck 89 | <input type="checkbox"/> Varitronics 54, 55 |
| <input type="checkbox"/> Gateway 92 | <input type="checkbox"/> Vibroplex 81 |
| <input type="checkbox"/> G&G 94 | <input type="checkbox"/> Wolf 92 |
| <input type="checkbox"/> Global 87 | <input type="checkbox"/> World QSL 89 |
| <input type="checkbox"/> Goodheart 93 | |
| <input type="checkbox"/> Hal 76, 86 | <input type="checkbox"/> 73 Stuff |
| <input type="checkbox"/> Heath 79 | <input type="checkbox"/> 73 FM Books 70 |
| <input type="checkbox"/> Henry 19 | <input type="checkbox"/> Repeater Handbook 70 |
| <input type="checkbox"/> Hi Par 89 | <input type="checkbox"/> Radio Bookshop 14, 15 |
| <input type="checkbox"/> H&L 94 | <input type="checkbox"/> 73 Subscriptions 72 |
| <input type="checkbox"/> James 86 | <input type="checkbox"/> 73 Special 73 |
| <input type="checkbox"/> Jan Crystals 82 | <input type="checkbox"/> DX Map 76 |

Mail to: 73 INC., PETERBOROUGH NH 03458

Name _____

Call _____

Address _____

Zip _____

PROPAGATION CHART J. H. Nelson

Good: Open/Fair: O/Poor:

July 1971

SUN	MON	TUES	WED	THUR	FRI	SAT
				①	②	③
4	5	6	7	8	9	⑩
⑪	⑫	13	14	15	16	17
⑱	⑲	⑳	㉑	㉒	㉓	㉔
25	26	27	28	29	③①	31

EASTERN UNITED STATES TO:

GMT: 00 02 04 06 08 10 12 14 16 18 20 22

ALASKA	14	14	14	7A	7	7	7	7	7A	14	14	14
ARGENTINA	14	14	14	14	7	7	14	14	21	21	21	14
AUSTRALIA	14A	14	14	7A	7B	7B	7	7	7B	14	14	14
CANAL ZONE	21	14	14	14	7	7	14	14	14	14	21	21
ENGLAND	14	7	7	7	7	14	14	14	14A	14A	14	14
HAWAII	14	14	14	7A	7	7	7	7B	14	14	14	14
INDIA	14	14	7B	7B	7B	7B	14	14	14	14	14	14
JAPAN	14	14	7A	7	7	7	7	14	14	14	14	14
MEXICO	14	14	14	7A	7	7	7	7	14	14	14	14
PHILIPPINES	14	14	7A	7B	7B	7B	7B	7B	14	14	14	14
PUERTO RICO	14	14	7	7	7	7	7	14	14	14	14	14
SOUTH AFRICA	7B	7B	7	7	7B	14	14	14	14A	14A	14	14
U. S. S. R.	14	7	7	7	7B	14	14	14	14A	14A	14	14
WEST COAST	14	14	14	7	7	7	7	14	14	14	14	14

CENTRAL UNITED STATES TO:

ALASKA	14	14	14	7A	7	7	7	7	7A	14	14	14
ARGENTINA	21	14	14	14	7	7	14	14	14	21	21	21
AUSTRALIA	14	14A	14	14	7B	7B	7	7	7B	14	14	14
CANAL ZONE	21	14	14	14	7	7	14	14	14	14	21	21
ENGLAND	14	7A	7	7	7	7	7A	14	14	14	14	14
HAWAII	14A	14	14	7A	7	7	7	14	14	14	14	14
INDIA	14	14	14	7B	7B	7B	7B	7B	14	14	14	14
JAPAN	14	14	7A	7	7	7	7	7	14	14	14	14
MEXICO	14	14	7A	7	7	7	7	7A	14	14	14	14
PHILIPPINES	14	14	14	7B	7B	7B	7B	7B	14	14	14	14
PUERTO RICO	14	14	14	7	7	7	7	14	14	14	14	14
SOUTH AFRICA	7B	7B	7	7	7B	7B	14	14	14	14	14	14
U. S. S. R.	14	7B	7	7	7	7	7A	14	14	14	14	14

WESTERN UNITED STATES TO:

ALASKA	14	14	14	7	7	7	7	7	7A	14	14	14
ARGENTINA	21	14	14	14	7	7	7	14	14	14	21	21
AUSTRALIA	21	21	21	14	14	14	7	7	7	7B	14	21
CANAL ZONE	14	14	14	14	7	7	7	14	14	14	14A	14A
ENGLAND	14	7A	7	7	7	7	7	7A	14	14	14	14
HAWAII	21	21	21	14	14	14	7	7	14	14	14	14A
INDIA	14	14	14	14	7B	7B	7B	7B	14	14	14	14
JAPAN	14	14	14	14	7A	7	7	7	14	14	14	14
MEXICO	14	14	7A	7	7	7	7	7	14	14	14	14
PHILIPPINES	14	14	14	14	7A	7B	7B	7B	14	14	14	14
PUERTO RICO	14	14	14	7	7	7	7	14	14	14	14	14
SOUTH AFRICA	7B	7B	7	7	7B	7B	7B	7B	14	14	14	14
U. S. S. R.	14	7B	7B	7	7	7	7	7B	14	14	14	14
EAST COAST	14	14	14	7	7	7	7	14	14	14	14	14

A = Next higher frequency may be useful also.
B = Difficult circuit this period.