December 1980 \$2.95

MAGAZINE FOR RADIO AMATEURS

HERE IN 1902 NATHAN B. STUBBLEFIELD 1860 – 1928 INVENTOR OF RADIO-BROADCAST AND RECEIVED THE HUMAN VOICE BY WIRELESS HE MADE EXPERIMENTS 10 YEARS EARLIER HIS HOME WAS 100 FEET WEST.

Who Really Invented Radio?

tempo does it again THE WORLD'S FIRST **440 MHz SYNTHESIZED** HAND HELD RADIO

Tempo was the first with a synthesized hand held for amateur use, first with a 220 MHz synthesized hand held, first with a 5 watt output synthesized hand held...and once again first in the 440 MHz range with the S-4, a fully synthesized hand held radio. Not only does Tempo offer the broadest line of synthesized hand helds, but its standards of reliability are unsurpassed ... reliability proven through millions of hours of operation. No other hand held has been so

thoroughly field tested, is so simple to operate or offers so much value. The Tempo S-4 offers the opportunity to get on 440 MHz from where ever you may be. With the addition of a touch tone pad and matching power amplifier its versatility is also unsurpassed.

The S-4...\$349.00

With 12 button touch tone pad...\$399.00 With 16 button touch tone pad...\$419.00 S-40 matching 40 watt output 13.8 VDC power amplifier...\$149.00



Tempo S-I

The first and most thoroughly field tested hand held synthesized radio available today. Many thousands are now in use and the letters of praise still pour in. The S-1 is the most simple radio to operate and is built to provide years of dependable service. Despite its light weight and small size it is built to withstand rough handling and hard use. Its heavy duty battery pack allows more operating time between charges and its new lower price makes it even more affordable.

Specifications:

Frequency Coverage: 440 to 449.995 MHz Channel Spacing: 30 KHz minimum Power Requirements: 9.6 VDC Current Drain: 17 ma-standby 400 ma-transmit (1 amp high power) Antenna Impedance: 50 ohms

Tempo S4

Tempo S-5

Offers the same field proven reliability, features and specifications as the S-1 except that the S-5 provides a big 5 watt output (or 1 watt low power operation). They both have external microphone capability and can be operated with matching solid state power amplifiers (30 watt or 80 watt output). Allows your hand held to double as a powerful mobile or base radio. S-30...\$89.00*

S-80...\$149.00*

*For use with S-1 and S-5

Tempo S-2



With an S-2 in your car or pocket you can use 220 MHz repeaters throughout the U.S. It offers all the advanced engineering, premium quality components and features of the S-1 and S-5. The S-2 offers 1000 channels in an extremely lightweight but rugged case. If you're not on 220 this is the perfect way to get started. With the addition of the S-20 Tempo solid state amplifier it becomes a

powerful mobile or base station. If you have a 220 MHz station, the S-2 will add tremendous versatility. Price...\$349.00 (With touch tone pad installed...\$399.00) S-20...\$89.00

Please note, as of Dec. 1, 1980 we will occupy our new world headquarters building with a new Los Angeles address and phone number.

Sensitivity: Better than .5 microvolts nominal for 20 db Supplied Accessories: Rubber flex antenna 450 ma ni-cad battery pack, charger and earphone RF output Power: Nominal 3 watts high or 1 watt low power Repeater Offset: ± 5 MHz

Optional Accessories for all models

12 button touch tone pad (not installed): \$39 • 16 button touch tone pad (not installed): \$48 • Tone burst generator: \$29.95 CTCSS sub-audible tone control: \$29.95
 Leather holster: \$20 • Cigarette lighter plug mobile charging unit: \$6

TEMPO VHF & UHF SOLID STATE POWER AMPLIFIERS

Boost your signal. . . give it the range and clarity of a high powered base station. VHF (135 to 175 MHz)

Drive Power	Output	Model No.	Price
2W	130W	130A02	\$209
10W	130W	130A10	\$189
30W	130W	130A30	\$199
2W	80W	80A02	\$169
10W	80W	80A10	\$149
30W	80W	80A30	\$159
2W	50W	50A02	\$129
2W	30W	30A02	\$ 89

UHF (400 to 512 MHz) models, lower power and FCC type accepted models also available.



2050 S. Bundy Dr., Los Angeles, CA 90025 931 N. Euclid, Anaheim, CA 92801 Butler, Missouri 64730

(213) 820-1234 (714) 772-9200 (816) 679-3127

TOLL FREE ORDER NUMBER: (800) 421-6631 For all states except California. Calif. residents please call collect on our regular numbers. Prices subject to change without notice.

A LIFETIME GUARANTEE AND 11 OTHER REASONS TO BUY AN "OPTOELECTRONICS" FREQUENCY COUNTER

1. SENSITIVITY: Superb amplifier circuitry with performance that can't be matched at twice the price. Average sensitivity of better than 15 mV from 10 Hz to 500 MHz on every model and better than 30 mV from 500 MHz to 1.1 GHz on the Series 8010A and 8013.

2. RESOLUTION: 0.1 Hz to 12 MHz, 1 Hz to 50 MHz, 10 Hz over 50 MHz.

3. ALL METAL CASES: Not only are the heavy gauge aluminum cases rugged and attractive, they provide the RF shielding and minimize RFI so necessary in many user environments.

4. EXTERNAL CLOCK INPUT/OUTPUT: Standard on the 8010/ 8013 series and optional on the 7010 series is a buffered 10 MHz clock time base input/output port on the rear panel. Numerous uses include phase comparison of counter time base with WWVB (U.S. National Bureau of Standards). Standardize calibration of all counters at a facility with a common 10 MHz external clock signal, calibrate scopes and other test equipment with the output from precision time base in counter, etc., etc.

5. ACCURACY: A choice of precision to ultra precision time base oscillators. Our ± 1 PPM TCXO (temperature compensated xtal oscillator) and ± 0.1 PPM TCXO are sealed units tested over 20-40°C. They contain voltage regulation circuitry for immunity to power variations in main instrument power supply, a 10 turn (50 PPM) calibration adjustment for easy, accurate setability and a heavily buffered output prevents circuit loads from affecting oscillator. Available in the 8010 and 8013 series is our new ultra precision micro power proportional oven oscillator. With $\pm .05$ PPM typical stability over 10-45°C, this new time base incorporates all of the advantages of our TCXO's and virtually none of the disadvantages of the traditional ovenized oscillator: Requires less than 4 minutes warm-up time, small physical size and has a peak current drain of less than 100 ma.

6. RAPID DISPLAY UPDATE: Internal housekeeping functions require only .2 seconds between any gate or sample time MODEL 7010A 600 MHz period. At a 1 second gate time the counter will display a new count every 1.2 seconds, on a 10 second gate time a new count is displayed every 10.2 seconds. (10.2 seconds is the maximum time required between display updates for any resolution on any model listed).

7. PORTABILITY: All models are delivered with a 115 VAC adapter, a 12 VDC cord with plug and may be equipped with an optional ni-cad rechargeable battery pack installed within its case. The optional Ni-Cad pack may be recharged with 12 VDC or the AC adapter provided.

8. COMPACT SIZES: State-of-the-Art circuitry and external AC adapters allowed design of compact easy to use and transport instruments.

Series 8010/8013: 3" H x 7-1/2" W x 6-1/2" D Series 7010: 1-3/4" H x 4-1/4" W x 5-1/4" D

 MADE IN U.S.A.: All models are designed and manufactured at our modern 13,000 square foot facility at Ft. Lauderdale, Florida.

10. CERTIFIED CALIBRATION: All models meet FCC specs for frequency measurement and provided with each model is a certificate of NBS traceable calibration.

11. LIFE TIME GUARANTEE: Using the latest State-of-the-Art LSI circuitry, parts count is kept to a minimum and internal case temperature is only a few degrees above ambient resulting in long component life and reliable operation. (No custom IC's are used.) To demonstrate our confidence in these designs, all parts (excluding batteries) and service labor are 100% guaranteed for life to the original purchaser.

(Transportation expense not covered).

12. PRICE: Whether you choose a series 7010 600 MHz counter or a series 8013 1.3 GHz instrument it will compete at twice its price for comparable quality and performance.

MODEL 8010A/8013 1.1 GHz/1.3 GHz

I GH2 FREQUENCY COUNTER



MODEL	RANGE	10 M	10 MHz TIME BASE		AVG. SENSITIVITY		AVG. SENSITIVITY		GATE	RE	RESOLUTION		EXT. CLOCK	SENSITIVITY	NI-CAD
	(From 10 Hz)	STABILITY	AGING	DESIGN	10 Hz to 500 MHz	500 MHz to 1.1 GHz	TIMES	TIMES 12 MHz	60 MHz	Max. Freq.	INPUTIOUTPUT	CONTROL E	BATTERY PACK		
7010A	600 MHz	±1 PPM	<1 PPM/VR	TCXO.	15 mV	N/A	(3)	1 Hz	1 Hz	10 Hz	YES	NO	YES		
7010.1A	000 11112	± 0.1 PPM	STEEMATE IS	STATISTICS IS	TTTT MATTER	TONO	151014		1. 1. 10 sec.			(600 MHZ)	OPTIONAL		OPTIONAL
8010A		±1PPM	<1 PPM/YR TCXO*	TCXO.			141			10 Hz	YES		YES		
8010.1A	1.1 GHz	± 0.1 PPM		<1 PPM/YR	<1 PPM/YR	15 mV	30 mV	.01. 1, 1, 10 sec.	.01. 1. 1. 10 sec. 1 H.	,1 Hz	1.Hz	(1.1 GHz)	STANDARD	YES	OPTIONAL
8010.05A		±.05 PPM													
8013.1	± 0.1 PPM	± 0.1 PPM		TCXO.	15 mV	30 mV	(4)	1Hz	1.87	10 Hz	YES	YES	YES		
8013.05		± 05 PPM	STITIMOTO.	ocxo	13 1114	Variot	01, .1, 1, 10 sec.		-	(1.3 GHz)	STANDARD	100	OPTIONAL		

TCXO = Temperature Compensated Xtal Oscillator

SERIES 8010A/8013

**OCXO = Proportional Oven Controlled Xtal Oscillator

SERIES 7010A

#7010A	600 MHz Counter - 1 PPM TCXO	\$199.95	
#7010.1A	600 MHz Counter - 0.1 PPM TCXO	\$249.95	
OPTIONS:			
#70-H	Handle/Till Bail (not shown)	\$2.95	
#NI-Cad-701	Ni-Gad Battery Pack & Charging		
	Circuitry Installed Inside Unit	\$19.95	
#EC-70	External Clock Input/Output	\$35.00	
#CC-70	Carry Case - Padded Black Vinyl	\$9.95	

#8010A	1.1 GHz Counter - 1 PPM TCXO	\$399.00
#8010.1A	1.1 GHz Counter - 0.1 PPM TCXO	\$450.00
#8010.05A	1.3 GHz Counter05 PPM Oven	\$499.00
#8013.1	1.3 GHz Counter - 0.1 PPM TCXO	\$550.00
#8013.05	1.3 GHz Counter05 PPM Oven	\$599.00
OPTIONS		
#NI-Cad-80	Ni/Cad Battery Pack & Charging	\$49.95
	Circuitry Installed Inside Unit	
#CC-80	Carry Case - Padded Black Vinyl	\$ 9.95

ACCESSORIES

#TA-100	Telescope antenna with	
	right angle BNC	\$ 9.95
#P-100	Probe, 50 Ohm, 1X	\$13.95
#P-101	Probe, Lo-Pass	
	Audio Usage	\$16.95
#P-102	Probe, Hi-Z	
	General Purpose	\$16,95
#LFM 1110	Low Frequency Multiplier	
	X 10, X 100, X1000	\$119.95
	For High Resolution of Audio Freq.	

1 55

5821 N.E. 14th Avenue, Fort Lauderdale, Florida 33334

TERMS: Orders to U.S. and Canada, add 5% for shipping, handling and insurance to a maximum of \$10.00. All other orders add 15% C.O.D. collection fee \$2.00. Florida orders add 4% state tax. Personal checks must clear before goods are shipped

1-800-327-5912 FROM FLORIDA (305) 771-2051/2

INFO

Manuscripts

Contributions in the form of manuscripts with drawings and/or photographs are welcome and will be considered for possible publication. We can assume no responsibility for loss or damage to any material. Please enclose a stamped, self-addressed envelope with each submission. Payment for the use of any unsolicited material will be made upon acceptance. All contributions should be directed to the 73 editorial offices. "How to Write for 73" guidelines are available upon request.

Editorial Offices:

Pine Street Peterborough NH 03458 Phone: 603-924-3873, 924-3874

Advertising Offices:

Elm Street Peterborough NH 03458 Phone: 603-924-7138

Circulation Offices:

Elm Street Peterborough NH 03458 Phone: 603-924-7296

Subscription Rates

In the United States and Possessions: One Year (12 issues) \$25.00 Two Years (24 issues) \$38.00 Three Years (36 issues) \$53.00

Now, upgrade faster! Here's 30 easy ways.

Satisfaction guaranteed or return in 10 days for full refund!

All cassettes 60 minutes.

Theory Tapes

Designed with an instructive, interviewstyle format, Kantronics Study Tapes are great supportive theory material for the latest exams.

Novice Study Tape - \$4.95

General Study Tape set - (two) \$8.95

General Q & A Tape - Questions similar to those on the FCC exam with good possible answers by Extra-class John Lenahan, KØRW, \$6.95

The New Advanced Study Tapes - (two) \$11.95

The New Extra Study Tape - \$6.95

Gradient Series

Push yourself gradually with slowly increasing code generated by computer to exact Morse specifications. Tape transcripts included.

□ Novice Gradient - 4 to 9 WPM \$6.95 General Gradient - 7 to 15 WPM \$6.95 Extra Gradient - 13 to 23 WPM \$6.95 High-Speed Gradient - 18 to 30 WPM \$6.95

QSO Tape Series

Simulated "on-the-air" conversations designed for the new-style FCC tests. Tape transcripts and multi-choice exams included.

OSO Tape - 7.5, 10, 13 and 15 WPM \$4.95 OSO-2 Tape - another hour of OSOs at 7.5,

Gold Label

- The Mysterious lonosphere By Jim Gray, W1XU. Learn how to take advantage of the ionized layers that make long-distance communication possible, \$6.95
- Sounds of Shortwave By Bob Grove. WA4PYQ. Listen to and hear explanations of mysterious signals heard across the radio spectrum, \$6.95
- Ins and Outs of Running Your Own Ham Station - By Paul Passman, WBØBBC, A twotape set that lets you in on the protocol used by experienced hams, \$11,95
- Choosing the Best Antenna By Jim Gray. W1XU. Find out how the right antenna can dramatically increase your station's abilities. \$6.95

Super Tapes

Kantronics' Super tapes generate characters sent at higher speeds with longer spaces for easier copying. Great for learning code and breaking copying barriers! Transcripts included.

- Super 5 WPM Instructor teaches code from characters to words and sentences. \$4.95
- Super 050 13 050 format with enhanced code at 13 WPM S4 95



Elsewhere:

Canada-\$27.00/1 year only, U.S. funds. Foreign surface mail-\$35.00/1 year only, U.S. funds. Foreign air mail-\$62.00/1 year only, U.S. funds.

To subscribe, renew or change an address:

Write to 73 Magazine, Subscription Department, PO Box 931, Farmingdale NY 11737. For renewals and changes of address, include the address label from your most recent issue of 73. For gift subscriptions, include your name and address as well as those of gift recipients. Postmaster: Send form #3579 to 73 Magazine, Subscription Services, P.O. Box 931, Farmingdale, NY 11737.

Subscription problem or question:

Write to 73 Magazine, Subscription Department, PO Box 931, Farmingdale NY 11737. Please include an address label.

73 Magazine (ISSN 0098-9010) is published monthly by 73, Inc., 80 Pine Street, Peterborough NH 03458. Second class postage paid at Peterborough NH 03458 and at additional mailing offices. Copyright (c) 1980 by 73, Inc. All rights reserved. No part of this publication may be reprinted or otherwise reproduced without written permission from the publisher. Microfilm Edition-University Microfilm, Ann Arbor MI 48106.

10, 13 and 15 WPM \$4.95 **OSO-13 Tape** - all 13 WPM \$4.95

OXX Tapes

'On-the-air' format at Extra-class speeds. Tape transcripts included.

- OXX Tape 20, 23 and 26 WPM with exam \$4.95
- QXX-2 Tape another hour of QSOs at 20. 23 and 26 WPM \$4.95
- O-Signals and Short Words Learn to hear groups of letters as units at high speed, 22, 33 and 40 WPM \$4.95

Radio Game

A fun and educational board game based on answering amateur radio license questions. Includes board, die, markers, questions and answers.

Amateur Upgrade - \$3.95

S

URDER

Random letters, numbers and punctuation generated by computer in groups of five. Transcripts included for self-testing.

Novice Random - \$4.95 General Random - \$4.95 Extra Random - \$4.95

Bookshelf

- Novice-Class Amateur Radio License Manual - By Phil Anderson, WØXI, \$3.95
- General-Class Amateur License Study Guide - By Phil Anderson, WØXI, \$6.50 Federal Frequency Directory - \$12.95

Combos

□ Novice - Includes Novice manual, Super 5 WPM tape, Novice Study Tape and OSO Tape. \$14.95

General - Includes General manual, General Study Tape set and QSO-2 Tape, \$19.95

1202 E. 23rd Street

Lawrence, Kansas 66044

Yes, I want to upgrade faster!

City		State	Zip
D Master Charge Card no.	D Visa	Check	
Signature		Expi	ration date
clude \$1 shipping / handlin	ng for single	tapes and manua	ls or \$2 for other orders.
			na statu z stat interior

Who Really Invented Radio? - the twisted tale of Nathan B. Stubblefield	
In Search of the Elusive SES WB2NEL	36
-track solar activity with this simple VLF receiver	
	42
An Even Better IC Timer	
-better than what?	46
-part II: constructing the facsimile recorder	
WB8DQT	52
de	c. 80

B MAGAZINE





A 600-MHz Universal Counter	
-you'll freq out over this one	58
Top-Banding the DX-60B	
-part II: a companion vfo WB1ASL	64
An Amp for QRPp Addicts	
-build this resistive step attenuator for low, low	
power work	68
The Center-Fed Bizarre	
-would you believe an indoor antenna for 80?	
N6RY	72
Clean Sweep for the FT-221	
-don't miss the action	82
A New Frontier	
-weekends were made for 10 FM! K4TWJ	84
Scanner Magic for Heath's 2036	
-grab your October '79 issue for part I of this	
project WA4BZP	88

Teletext and Viewdata: Are You Ready fo Information Boom?	r the
-coming soon to a living room near you: video	
data servicesWB9KPT	120
Double-Duty CW Keyboard	
-helps you on receive as well as transmit	
	126
Sixteen Channels of Digital Delight	
1 - do-it-yourself data acquisition	
WB4UHY	132
A Computer-Controlled Talking Repeater	
I — part III: interfacing to the	
microcomputer WA6AXX	138
Make a Microcomputerist Smile	
I — build him this EPROM eraser	
AL7G	148
Build a Talking Digital IDer	
-K2OAW redesigns his IDer at last K2OAW	162

Never Say Die – 6, Looking West – 12, DX – 14, Contests – 16, RTTY Loop – 18, Awards – 20, Leaky Lines – 22, Letters – 24, Fun! – 26, OSCAR Orbits – 28, New Products – 32, Social Events – 78, Ham Help – 79, 179, Corrections – 175, 1980 Index – 176, Review – 181, Dealer Directory – 225, Propagation – 225

Who?-36

W2NSD/1 NEVER SAY DIE editorial by Wayne Green

SHADES OF THE PAST!

The year was 1950 and Wayne Green, not very long out of college, was fresh from a job in Dallas as a television producer-director (the damned station went from live productions to all film, throwing the entire production crew out of work). I was looking for something temporary to tide me over until I could find work in television again.

Having a first class ticket and experience as an announcer, I put an ad in *Broadcasting*, looking for a combination spot: engineer-announcer. There was a big need for that kind of experience at that time and I was soon sitting there sorting out telegrams from over 50 broadcast stations with good jobs open. One of the best bets was from WSPB in Sarasota, Florida. ville was published. He's had a peck of best sellers down through the years. McKinley would come by the station occasionally with Bandel and we'd talk. I think the thing I enjoyed the most about both of them was their sense of humor.

McKinley did a number on Bandel one time. He went out and bought an enormous number of old books from a defunct used book store. He had a stamp made up which said, "If found, please return to Bandel Linn"...etc., along with Linn's address. McKinley traveled a lot and would drop off these books in stores everywhere he went. Bandel was soon up to here in returned books, arriving with every mail from all over the country...or people driving up to bring them back personally. When I decided to start a ham magazine in 1960, I got in touch with Bandel, who in addition to being a great radio personality was also a nationally known cartoonist, and got him to do the cover for issue #1. Bandel is still cartooning and broadcasting, holding forth from Pensacola these days. I get to see him every now and then when I get down to Mobile for the reunion of my old submarine crew. There are a few people I've known who have really been enjoyable to talk with...such as Jean Shepherd, John Campbell, and Linn. All are hams, oddly enough, though I seldom talked hamming with any of them. John is gone now, but he left a raft of admirers. I'm sure it was his editorials in Astounding Science Fiction . . . and later in Analog...which got me started writing long editorials. I enjoyed them for years and it just never occurred to me that an editor

would do anything other than write long editorials. I don't think I gave it much thought until a couple of months ago when it suddenly dawned on me that I'm probably the *only* editor writing these damned things.

Of course the pressures of writing editorials for three big magazines a month, plus a fourth just for the microcomputer industry, and the shadow of two more magazines getting started all helped to focus my awareness on a good thing overdone. Now, with a month-long trip coming up to Asia, the managing editors are pushing me to write a month ahead. Hells bells, I can hardly get 'em done for one month, much less two. of 605. The reception is not prohibited, only the use of the information. What are you going to do about this, FCC?

SAROC SHOOTS SELF IN FOOT

The pitiful shreds of what was once a halfway decent hamfest will be aired again in January. This, I believe, is a commercial exploitation of hams for the personal gain of one chap, who the last I heard was disavowed by all ham clubs which had ever tried to work with him. At the last of these hamfests I attended, the technical sessions were a joke and the exhibits few. The advanced registration for this disaster is \$16, if you are that eager to throw your money away.

The hamfest has been bounced from one hotel to another, presumably for some good reason. Now it is at the Dunes and filling a date obviously unwanted by any sane group: January 1. Bring playing cards, if you are so totally desperate on New Years Day as to go to this silly thing...so at least you'll have *something* to do.

One of the major ham dealers tried exhibiting at the show not long ago and went away totally disgusted. Other than some free booze courtesy of *Ham Radio* magazine, apparently out to help create more alcoholics, the dealer felt ripped off.

I loaded my ham gear into my old 1941 Ford...NBFM kilowatt for all bands, dipole antenna, SX-28A receiver...and drove down to Sarasota, the "Air Conditioned City." It was pleasant there temperaturewise, but the mosquitos were worse than those in New Jersey or the swamps of Brooklyn.

It didn't take long before I settled into a comfortable routine, opening the station mornings, lying on the beach afternoons, and hamming evenings. One of the chaps who popped in to do a radio show daily was Bandel Linn, also a ham. We hit it off right away. Linn lived nearby on one of the keys and his mailbox said, "Corporal Bandel Linn." This was in retaliation for all the other mailboxes with retired colonels, generals, and such.

One of Bandel's best friends was a little known writer, McKinley Cantor. He became better known after his book, AndersonWe've got a series of cartoons by Bandel starting in the magazine. I hope you enjoy his humor as much as I do.

THAT ARKANSAS WARHEAD

Those of you who read the fine print on the silo explosion in Arkansas may have noticed that the newspapers were able to print a transcript of a tape-recorded Air Force radio conversation about the search for the warhead. Some chap has receivers tuned to Air Force and other channels with recorders ready in case of any emergency... then he is able to sell the information to the papers. If ever there was a case where the FCC rules in Section 605 regarding the privacy of radio transmissions was being broken, it is here. If the FCC lets this go untouched, they are turning their heads when their rules are clearly being broken.

It is against the law to sell information gotten over the air from anything other than broadcast stations. This is the heart If you are absolutely desperate to go to Vegas, wait a couple days and catch the Winter Consumer Electronics Show, starting January 8th. Then, if you still have time on your hands, why not come up to Vail for the ham industry convention January 10–17th?

NARA EVAPORATED

A couple of months ago, I wrote about what appeared to be a scam to fleece hams, with the only action I could see coming from a chap with a bad record...convicted of conning hams. If there was anyone who did not get his money back from NARA, I'd like to hear from them.

I first heard of this one while at a hamfest in Wiesbaden, Germany, last May. A chap there had just come from the Dayton Hamvention and mentioned that NARA was there, taking memberships. I was at a loss to understand how a group could get started without being in touch with me...if they were legiti-



TRIO-KENWOOD COMMUNICATIONS INC. 1111 WEST WALNUT / COMPTON, CA 90220

Small wonder.



Processor, N/W switch, IF shift, DFC option

TS-130S

An incredibly compact, full-featured, all solidstate HF SSB/CW transceiver for both mobile and fixed operation. It covers 3.5 to 29.7 MHz (including the three new Amateur bands!) and is loaded with optimum operating features such as digital display, IF shift, speech processor, narrow/wide filter selection (on both SSB and CW), and optional DFC-230 digital frequency controller. The TS-130S runs high power and the TS-130V is a low-power version for QRP applications.

TS-130 SERIES FEATURES:

80-10 meters, including three new bands

Covers all Amateur bands from 3.5 to 29.7 MHz. including the new 10, 18, and 24-MHz bands. Receives WWV on 10 MHz. VFO covers more than 50 kHz above and below each 500-kHz band.

 Two power versions . . . easy operation TS-130S runs 200 W PEP/160 W DC input on 80 -15 meters and 160 W PEP/140 W DC on 12 and 10 meters. TS-130V runs 25 W PEP/20 W DC input on all bands. Solid-state, wideband final amplifier eliminates transmitter tuning, and receiver wideband RF amplifiers eliminate preselector peaking.

Built-in speech processor

Increases audio punch and average SSB output power, while suppressing sideband splatter.

CW narrow/wide selection

"N-W" switch allows selection of wide and narrow bandwidths. Wide CW and SSB bandwidths are the same. Optional YK-88C (500 Hz) or YK-88CN (270 Hz) filter may be installed for narrow CW.

SSB narrow selection

"N-W" switch allows selection of narrow SSB bandwidth to eliminate QRM, when optional YK-88SN (1.8 kHz) filter is installed. (CW filter may still be selected in CW mode.)

Sideband mode selected automatically

LSB is selected on 40 meters and below, and USB on 30 meters and above. SSB REVERSE position is provided on the MODE switch.

Built-in digital display

Six-digit green fluorescent tube display indicates actual operating frequency to 100 Hz. Also indicates external VFO or fixed-channel frequency, RIT shift, and CW transmit/receive shifts. Also analog subdial for backup frequency indication.

IF shift

Allows IF passband to be moved away from interfering signals and sideband splatter.

- Single-conversion PLL system Improves stability as well as transmit and receive spurious characteristics.
- Built-in RF attenuator For optimum rejection of intermodulation distortion_
- Built-in VOX

For convenient SSB operation, as well as semibreak-in CW with sidetone.

Effective noise blanker

Eliminates pulse-type interference such as ignition noise.

Built-in 25-kHz marker

Accurate frequency reference for calibration.

Compact and lightweight

Measures only 3-3/4 inches high, 9-1/2 inches wide, and 11-9/16 inches deep, and weighs only 12.3 pounds. It is styled to enhance the appearance of any fixed or mobile station.



Optional DFC-230 Digital Frequency Controller

Allows frequency control in 20-Hz steps with UP/ DOWN microphone (supplied with DFC-230). Includes four memories (handy for split-frequency operation) and digital display. Covers 100 kHz above and below each 500-kHz band. Very compact.

Ask your Authorized Kenwood Dealer about the compact, full-featured, all solid-state TS-130 Series.

NOTE: Price, specifications subject to change without notice and obligation.

MATCHING ACCESSORIES FOR FIXED-STATION OPERATION:

- PS-30 base-station power supply (remotely switchable on and off with TS-130S power switch).
- SP-120 external speaker VFO-120 remote VFO
- microphone

Other accessories not shown:

- YK-88C (500 Hz) and YK-88CN (270 Hz) CW filters
- YK-88SN (1.8 kHz) narrow SSB filter
- AT-130 compact antenna tuner (80-10 m, including 3 new bands)
- MB-100 mobile mounting bracket
- MC-50 50kΩ/500Ω desk
- MC-30S and MC-35S
 - noise cancelling hand microphones PC-1 phone patch

 - TL-922A linear amplifier
 - HS-5 and HS-4 headphones HC-10 world digital clock
 - PS-20 base-station power
 - supply for TS-130V

 SP-40 compact mobile speaker

 VFO-230 digital VFO with five memories

STAFF

PUBLISHER/EDITOR Wayne Green W2NSD/1 EXECUTIVE VICE PRESIDENT Sherry Smythe ASSISTANT PUBLISHER/EDITOR Jeff DeTray WB8BTH ASSOCIATE PUBLISHER/DIRECTOR

OF PUBLICATIONS Edward Ferman WA1UFY

> MANAGING EDITOR John Burnett

ASST. MANAGING EDITOR Susan Philbrick

NEWS EDITOR Gene Smarte WB6TOV

EDITORIAL ASSISTANTS Nancy Noyd Richard Phenix

CONTRIBUTING EDITORS Chris Brown N1AUI Paul Grupp KBØNV/1

ADMINISTRATIVE ASSISTANTS Suzy Clyne Pat Graham

ASSOCIATES Robert Baker WB2GFE Jim Cain K1TN Bill Gosney WB7BFK Sanger Green Dave Ingram K4TWJ Larry Kahaner WB2NEL Joe Kasser G32CZ Dr. Marc Leavey WA3AJR Dave Mann K2AGZ Bill Pasternak WA6ITF John Schultz W4FA Peter Stark K2OAW

MANUFACTURING MANAGER Noel Self WB1ARP

PRODUCTION MANAGER/ PUBLICATIONS Nancy Salmon

ASST. PRODUCTION MANAGER/PUBLICATIONS mate. The story of a group of ten hams putting up \$35,000 each in seed money didn't ring true either. I know many of the hams with a spare \$35,000 and I can't believe they would put out that kind of loot without checking with me.

Then, I found out who the chap was behind the whole thing and remembered his previous record. Ask the ARRL about it; QST ran his ads which brought about the troubles and the conviction. But if something like this was afoot, why no word from the ARRL? They certainly couldn't say they didn't hear about it...or that they didn't know the chap. I have no explanation for this.

Once my editorial piece appeared, NARA seemed to disappear. I got a letter from a ham who had joined, saying he had gotten his \$10 back and that the NARA telephone number had been disconnected, with no forwarding number. He did some

sleuthing and found that the chap had moved to Virginia and was now operating under the name of Keswick Sales, with ads in the yellow sheets. The report went on to say that over two hundred orders had been received with payments, but nothing had been shipped and no payments had been returned. No explanation by mail to the customers. It appears that the FTC rules on back orders has already been broken. Will he move on again, leaving mulcted hams in his wake?

ELECTRONIC DESIGN BUNK

I really hate it when I see another magazine print a letter from some uninformed person and it puts down amateur radio. Thanks to W5IFH for sending me a clipping from the September 13th issue of *Electronic Design*, wherein is a letter from a Collins man, a program engineer named Roe. He fears that amateurs now are "nothing more than hobbyists and gadgeteers, lacking the inquisitive and inventive spirit which made the early days of amateur radio so productive. Now, the only innovations come from the R&D labs of the amateur equipment manufacturers."

Amateur radio needs this type of hogwash like another Incentive Licensing attack. The facts are quite otherwise, as Roe would know if he were a reader of 73. It is true that the FCC has been doing all in its power to prohibit amateurs from experimenting and pursuing the FCC's own regulations (see 97.1c), but despite this, amateurs have been building more than ever before in history and have been developing new circuits and modes of communications.

In case you think that hams are not building...and I get that crap a lot from old-timers who

Continued on page 189



Michael Murphy ART DIRECTOR **Diana Shonk** PRODUCTION William Anderson III Steve Baldwin Pati Burr Tedd Cluff Linda Drew **Robert Drew** Bruce Hedin Kenneth Jackson Ross Kenyon Maryann Metevier **Dion Owens Robert Sawyer** Patrice Scribner Susan Symonds PHOTOGRAPHY William Heydolph Terrie Anderson TYPESETTING Barbara Latti Sara Bedell Mary Kinzell Linda Locke Michele DesRochers CORPORATE CONTROLLER Charles Garniss, Jr. **EXECUTIVE ASSISTANT** Leatrice O'Nell ACCOUNTING MANAGER Knud Keller KV4GG/1 CIRCULATION MANAGER Debra Boudrieau CIRCULATION Doris Day 603-924-7296 **Pauline Johnstone BULK SALES MANAGER** Ginnie Boudrieau **ADVERTISING** 603-924-7138 Jim Gray W1XU, Mgr. Nancy Ciampa, Asst. Mgr.



"I live next door and I came over to thank you for those little squiggles and lines on my TV—They're very interesting!"

2 A VERSCITIFY 10 Options Guaranteed to Make the Extremely Popular 2A and 2AT Even More Popular!









A fresh idea!

Our new crop of tone equipment is the freshest thing growing in the encoder/decoder field today. All tones are instantly programmable by setting a dip switch; no counter is required. Frequency accuracy is an astonishing $\pm .1$ Hz over all temperature extremes. Multiple tone frequency operation is a snap since the dip switch may be remoted. Our SS-32 encode only model is programmed for all 32 CTCSS tones or all test tones,

touch-tones and burst-tones. And, of course, there's no need to mention our 1 day delivery and 1 year warranty.

TS-32



SS-32

TS-32 Encoder-Decoder

- Size: 1.25" x 2.0" x .40"
- High-pass tone filter included that may be muted
- Meets all new RS-220-A specifications
- Available in all 32 EIA standard CTCSS tones

SS-32 Encoder

- Size: .9" x 1.3" x .40"
- · Available with either Group A or Group B tones

Frequencies Available:

Group A				
67.0 XZ	91.5 ZZ	118.8 2B	156.7 5A	
71.9 XA	94.8 ZA	123.0 3Z	162.2 5B	
74.4 WA	97.4 ZB	127.3 3A	167.9 6Z	
77.0 XB	100.0 1Z	131.8 3B	173.8 6A	
79.7 SP	103.5 1A	136.5 4Z	179.9 6B	
82.5 YZ	107.2 1B	141.3 4A	186.2 7Z	
85.4 YA	110.9 2Z	146.2 4B	192.8 7A	
88.5 YB	114.8 2A	151.4 5Z	203.5 MI	

• Frequency accuracy, ±.1 Hz maximum - 40°C to + 85°C

· Frequencies to 250 Hz available on special order

Continuous tone

		Group B	3		human	in
TEST-TONES:	TOUCH	-TONES:	В	URST-	TONE	S:
600 1000 1500 2175 2805	697 770 852 941	1209 1336 1477 1633	1600 1650 1700 1750 1800	1850 1900 1950 2000 2100	2150 2200 2250 2300 2350	2400 2450 2500 2550

• Frequency accuracy, ±1 Hz maximum - 40°C to +85°C

 Tone length approximately 300 ms. May be lengthened, shortened or eliminated by changing value of resistor

Wired and tested: TS-32 \$59.95, SS-32 \$29.95





426 West Taft Avenue, Orange, California 92667 (800) 854-0547 / California: (714) 998-3021





Bill Pasternak WA6ITF 24854-C Newhall Ave. Newhall CA 91321

OPEN REPEATERS DON'T EXIST DEPARTMENT

There is no such thing as an "open" repeater-at least not in the eyes of the Federal Communications Commission. This came about as the final result of a well-intentioned rulemaking request filed some three years ago by a Texas amateur. Jones Talley W5TJE had requested that closed and private repeater operation be outlawed. In addition, Mr. Talley felt that much on-channel interference between repeaters could be eliminated by lowering all repeater power levels.

I recently interviewed Mr. Talley for Westlink and found him to be a most delightful person. Moreover, he is a very dedicated amateur. He told me that the reasoning behind his twin petitions (There were two, but the FCC elected to combine both into one rulemaking action.) was that he and many others felt that repeater operations that required membership in an organization were not in the spirit of the amateur service. Further, that with the large number of repeaters currently operating, there was precious little spectrum left for new operations. By lowering the power levels, there would be less chance of on-channel interference as new systems came into being. I should add that Mr. Talley is a broadcast engineer with many years of experience behind him. He understands very well the many technical aspects of radio communication. So, Mr. Talley elected to file his petitions to lower maximum power levels for repeater operation and also to gain acknowledgement for the concept of the open repeater, a concept that we as amateurs have understood for years. For many moons, things sat quiet in Washington-not a peep on the topic. Most amateurs, including me, had all but forgotten that such a rulemaking request was on file with the Commission.

blockbuster. It was all but unnoticed by most hams since it was merely a dismissal order on two rulemaking requests, one of which belonged to Mr. Talley. It was only after reading the order several times that the implications came to light, that in the eyes of the FCC, no such thing as an open repeater existed. In fact, the text you are about to read is that of the order itself. I suggest that you pay close attention to the first portion of Section 2, because this may well set a precedent.

Before the Federal Communications Commission Washington, D.C. 20554 PR FCC 80-351 27525

In the Matter of

Rulemaking petitions requesting "open" repeaters; and, to require license endorsement authorizing repeater operation. RM-2844 and RM-3461

ORDER

that closed repeaters violate the spirit of Amateur radio communications.

2. With respect to the matter of forbidding a station in repeater operation to be closed to anyone, we do not agree that such a stance is desirable. The control operator of the station must be in a position to deny access to any person who is violating our rules. Any other view would be construed as our approval of unlawful acts. Moreover, a fundamental principle is at stake here. At all times, the control operator of a station in repeater operation is responsible for the proper operation of the station. Open repeaters would militate against that basic operator accountability. Further, we do not concur in Mr. Talley's suggestion to lower the maximum power levels for repeaters. The maximum power levels specified in the present rules are not mandatory. Less power may always be used. In fact, we expect Amateur radio operators to take appropriate means to avoid interfering with each other's transmissions. Amateur radio licensees have always been known for selfdisciplining and a cooperative spirit in the use of Amateur radio frequencies. There is no reason to believe that they have relinquished working together to solve mutual usage problems.

5. Accordingly, in view of the reasons herein given, it appears that the public interest would best be served by dismissing the instant petitions. Therefore, IT IS ORDERED, That RM-2844 and RM-3461 ARE DISMISSED and that these proceedings ARE TERMINATED. For further information, contact Maurice J. DePont, 2025 M Street, N.W., Washington, D.C. 20554, (202)-254-6884.

> FEDERAL COMMUNICATIONS COMMISSION William J. Tricarico Secretary

Now, before you run out and

regulations were *that* restrictive. They also were not needed—the problems had been solved.

For a number of years, amateurs from all over the nation worked hard to try to initiate some relief from the restrictions of 18803. Among these was Capt. Richard McKay K6VGP. Dick owned a "private" category repeater located in Palos Verdes and was able to obtain "Special Temporary Authority" to operate his repeater without 24-houra-day, full-time control operators on hand.

The success of this experiment on WR6AAD convinced the Commission to issue another "Special Temporary Authority" to the Palisades Amateur Radio Club of Culver City, California, for a similar experiment. After a year's time and many filings with the Commission detailing progress of the experiments, a petition was filed to permit what was termed "automatic remote control" over amateur repeaters.

One of the first actions taken in the deregulatory process was the adoption of two control standards based upon the classification a repeater operated under. A closed or private repeater could operate under the doctrine of "fully automatic re-

Then, in late July, came the

Adopted: June 17, 1980;

Released: July 2, 1980

By the Commission:

1. Rulemaking petition RM-2844, submitted by Jones P. Talley (W5TJE), of Dallas, Texas, proposed that Section 97.85 of the Amateur Radio Service rules be amended by adding a provision that no repeater be operated as a "closed" repeater. In support of his petition, Mr. Talley offered these reasons. He said that, in the majority of the country, there are no longer any available frequencies for new repeaters. Further, according to the petitioner, no one, in the history of the Amateur Radio Service, has ever had an assigned or a closed frequency. Mr. Talley feels that the Amateur Radio Service should remain open and clear for all properly licensed Amateur radio operators. In addition, petitioner suggested that Section 97.67 of the Commission's Rules be amended to lower the maximum amount of power that Amateur radio stations in repeater operation could use. For example, on frequency bands above 52 MHz, the power would be 50 Watts, rather than 100 Watts, where the antenna height above average terrain is below 100 feet. His reason for the proposal is that he believes that most repeaters are covering more area than just the local area, thereby causing interference between repeaters in surrounding areas. This, in turn, he alleges, is why the surrounding areas have no available frequencies. Mr. Talley says that lower maximum power levels will correct this problem. Only one comment was filed in RM-2844. The Amateur Radio Club of the Veterans Administration Medical Center, Montrose, New York, supported the petition saying tell all your users that they must immediately purchase some form of CTCSS generator if they intend to continue operating on your repeater, sit back a moment and permit me to point out why this is not necessary. We must go back into the archives a bit, but I think you will enjoy the trip, especially if you are a newcomer to FM.

In the late 1960s, amateur radio FM and repeater operation took off like the proverbial bat out of you know where. After a while, some amateurs who just could not leave well enough alone decided that what repeaters needed were rules, and a number of petitions were sent to the FCC requesting these. As usual, time went by, and in the interim, the problems inherent to the implementation of anything new were solved. In this case, the solution took the form of individuals and groups providing voluntary coordination for repeater operations. Then, with the arrival of the 1970s, came something known as Docket 18803. 18803's implementation brought FM relay growth to a screeching halt. The

mote control," while open repeaters were given limited relief in the form of "semi-automatic remote control." I won't go into the details of each at this time; it would take pages to do so. An exact account of the entire deregulatory process can be found by going through back issues of 73 containing this column. We lived it and we reported on each step in the long process.

What is important is the contention that this first step in deregulation of amateur relay activity initially gave FCC recognition of both open and closed/private repeater operation. This being the case, the report and dismissal order on RM-2844 is a direct contradiction of what has been stated in the past. Additionally, while we in amateur radio have developed our own definitions concerning relay system operation categorization, the FCC never has done likewise. You and I know what constitutes an open, closed, or private repeater, but the Commission has never seen fit to offer any definitions of their own.

Continued on page 192

SUPER RIG

NEW TEN-TEC OMNI-C 9 Band Transceiver + HERCULES Solid-State KW Linear

TEN-TEC SUPER RIG IS READY. For every band, every band condition. With the latest in solid-state hf technology, the latest in features. To make communications easier, more reliable — super.

HERCULES

Amateur Radio's first full break-in solid-state kW linear amplifier. With the reliability you'd expect from the pioneer in high-power solid-state

HERCULES 444 Linear Amplifier

OMNI-C

The new model in this famous series. With new coverage and new features to make it better than ever!

All 9 HF Bands. From 160 through 10 meters, including the new 10, 18 and 24.5 MHz bands. Coverage you can live with—for years and years.

3-Mode, 2-Range Offset Tuning. Offset the receiver section or the transmitter section or the entire transceiver! In 2 ranges: ± 500 Hz or ± 4 kHz. For complete flexibility in fine tuning, a DX work, or net operations.

Seven Response Curves. Four for SSB, three for CW. With new switching to select the standard 2.4 kHz filter, optional 1.8 kHz SSB filter, 500 Hz or 250 Hz CW filters, and standard 450 and 150 Hz CW active audio filters. Up to 16 poles of i-f filtering plus audio filtering to handle any situation.

Built-In Notch Filter and Noise Blanker. Notch is variable from 200 Hz to 3.5 kHz with a depth of more than 50 dB. New noise blanker reduces ignition and line noise. Both standard equipment.

"Hang" AGC. New, smoother operation.

Super Specs. Optimized sensitivity —a balance between dynamic range and sensitivity (2 μ V on 160 to 0.3 μ V on 10 meters) Greater dynamic range: better than 90 dB. And a PIN diode switchable 18 dB attenuator. 200 watts input on all bands! 100% duty cycle on all bands for up to 20 minutes.

Super Convenient. Built-In VOX with 3 up-front controls. Built-In PTT control at front and rear jacks. Built-In Zero-Beat switch puts you on exact frequency. Built-In Adjustable Sidetone with variable pitch and level. Adjustable ALC for full control from low power to full output. 2-Speed Break-In, fast or slow speeds to fit operating conditions. Built-In Speaker eliminates desk clutter. Automatic Sideband Selection—reversible.

Super Design. All Solid-State and Broadbanded—from the pioneer, Ten-Tec. Modular plug-in circuit boards. Functional Styling with convenient controls, full shielding, easy-to-use size (5¾"h x 14¼"w x 14"d).

Super Hercules Companion. Styled to match, plus separate receiving antenna capability, plus transceiver front panel control of linear's bandswitching (one knob does it all).

Full Accessory Line including filters, remote VFO, power supplies, keyers, microphones, speech processors, antenna tuners—all in matching color.

Model 546 OMNI-Series C.... \$1189.

technology-TEN-TEC.

All Solid-State. No tubes. Instead, HERCULES uses two 500-watt push-pull solid-state amplifier modules with an output combiner. Super solid.

Broadband Design. No knobs, no tuning. From the pioneer, TEN-TEC. For fast, effortless changing of bands. Super easy.

Automatic Bandswitching when used with OMNI (the OMNI bandswitch also controls HERCULES bandswitching through a motor driven stepping switch). Super convenient.

Full Break-In. HERCULES puts the conversation back into high power CW operation—you can hear between every character you send.

Full Coverage. 160 through 15 meters plus four "AUX" positions for 10-meter conversion by owner and future band additions.

Full Gallon. 1000 watts input on *all* bands, 600 watts output, typical. Built-in forced-air cooling. Driving power: 50 watts, typical. Adjustable negative ALC voltage. 100% duty cycle for SSB voice modulation; 50% duty cycle for CW/RTTY (keydown time: 5 minutes max.) Continuous carrier operation at reduced output.

Full Protection. Six LED status indicators continuously monitor operating conditions and shut down the amplifier whenever any one exceeds set limits (the exciter automatically bypasses the amplifier under amplifier shut-down for barefoot operation). The six parameters monitored are: 1) overdrive; 2) improper control switch setting; 3) heat sink temp.; 4) SWR; 5) overvoltage/over-current; 6) rf output balance. *Two meters* monitor collector current, voltage, and forward/reverse power. And a highly efficient automatic line voltage correction circuit (patent applied for) eliminates the need for selecting transformer taps, prevents applying too high a voltage to final amplifier devices, becomes operative under low line conditions.

Super Power Supply. Provides approximately 45 VDC @ 24 amperes, operates on 105/125 VAC or 210/250 VAC. Tape wound transformer and choke reduce weight (50 lbs.) and size (7½"h x 15¾"w x 13½"d). Separate enclosure.

Super Styling. Designed to match OMNI, the HERCULES has the same height as OMNI, plus matching bail and matching colors. The front panel is simplicity in itself with two push-button switches (power and mode) plus two knobs (meter and bandswitch), and a "black-out" monitor panel (when unit is off, meters are unobtrusive). Amplifier size is 5¾"h x 16"w x 15½"d.

Model 444, HERCULES amplifier & power supply.... \$1575.



Experience SUPER RIG at your TEN-TEC dealer, or write for full details.





Jim Cain K1TN 306 Vernon Avenue Vernon CT 06066

THE NEW BREED

Comments made here the past few months have brought some interesting letters, most reinforcing our own attitudes about DXing today compared to a decade or more ago. As very little of life in 1980 is like life in 1960, it comes as no particular surprise that amateur radio in general and DXing specifically often leave many old-timers somewhat cold.

For example, the FCC has just announced that the CW portion of their exams is changing again, with the exams to be only ten questions, fill-in-the-blank instead of multiple choice, and a passing grade will be only seventy percent instead of eighty. This is a test? On the same sheet where we read that FCC news was the story of a Conditional class amateur who was traversing the court system because he had not, for some obscure reason, been grandfathered to General class. The FCC had called him in to take a 13-wpm code test and he refused. Obviously, he doesn't know the code, probably cheated on his original Conditional test (with the aid of another amateur, sorry to say), and that's that. Aside from the FCC making it possible for people to operate kilowatt transmitters on the HF bands with little or no knowledge of what are recognized as basic radio techniques, the actual styles of operating today often add to the confusion and lowering of standards on the bands. Here's a case:

code! True, but his methods frustrated many who also know the code. Operating split, this DXer listened up in frequency, often as much as 50 kHz. In addition, he immediately moved his receiving vfo after each contact, making it nigh impossible for the good operators to ply their trade of finding his last contact, zeroing the frequency, and making one short call on his known listening frequency-not "tailending," mind you, but just being where the DX is listening is operating at its best. It was not to be in this case.

It used to be that when the neophyte DXer discovered he could not always crack the pileups with a hundred Watts and a dipole, pennies began going into the bank for an amplifier, and a safety belt was purchased for future antenna work. Learning to trust the belt, lean back, and use both hands on the tower was part of the process whereby one became a "real ham," a "true DXer," or whatever. It was simple: If you couldn't get through to the station you wanted, either your signal was too weak or your operating technique was not appropriate. And the solutions were equally straightforward: Build a better station, practice operating, and be patient. As a result, the bands continually witnessed new crops of hams who became proficient by their own efforts. (Made it without using the word "bootstraps!") Now that this hole has been dug, I might as well just climb on in. Today's saviors of the bands have found new solutions to the devastating blow of not being able to work your favorite DX station. Those solutions are called "nets" and "lists." They have ruined DXing for what it once was: the second most competitive aspect of amateur radio (after contesting). It seems unlikely that anyone reading this column does not know the net and list style; either one uses it or hates it or, occasionally, both. Let's look at the implications of this new breed of operator and the possible future in store if the trends continue.

The list and net operator (L/N) will tell us that the new style enables the weaker stations to work through to the DX, that L/N maintains order on the bands, that it gives everyone a fair shake, and, hoo-boy, here it comes, that new DX operators are spared the massive pileups which had previously driven a few of them into other pursuits, such as stamp collecting. We are sure to hear from some of you with other justifications, such as that there are just too many hams on the bands now when compared to 1960 and new techniques are consequently required, or that maybe not everyone can afford a second vfo in order to operate split.

Of course, it will be said that if an operator wishes to use L/N because he is an inexperienced amateur on Island X (which everyone needs), it is his own decision and those who don't like it can lump it. Those who play his game will be rewarded with a contact (often despite the fact that they can't hear him). Those who refuse to play the game will go away empty-handed.

A parallel: The US national speed limit is now 55 mph, on highways designed for 70 mph + driving. This was instituted in 1974 to "save gas," and was later further justified by a contrived set of statistics "proving" the reduced speeds resulted in fewer highway accident deaths. Voilà! The temporary law becomes permanent. The fact is that L/N has driven off more avid DXers in a couple of years than pileups ever did in forty years. L/N has raised a cacophony of tooth grinding by those with beams, amplifiers, and savvy. L/N is what brought the "frequency policemen" and catcallers to their heyday, as they trash the frequencies in anger at their inability to just jump in there and call until they work what they want. In fact, highway deaths have not gone down, particularly on the limited-access interstates. As for fuel consumption, guzzlers do use less fuel at 55 than at 70; so do, for that matter, all autos. Now here's the point: Say you are driving, oh, a diesel Rabbit at 50 mpg and are restrained to 55 mph so the Cadillacs can produce 18 instead of 15 mpg. You have gone the full mile to conserve fuel; you have reacted to the situation in the most efficient, intelligent manner. Yet, you are punished because you are in the minority.

Back to the new DX station on the band. You wrenched your back getting that new beam up, smelled up the entire house smoke-testing your new amplifier, but now you're LOUD. Further, you have practiced your ham radio hobby, not expecting to set the world on fire your first couple of years on the bands, but now you're a "good operator." Now you've found that DX station, but they've already taken calls from your call area and you might just as well turn off your radios. So mail your postcard to the list taker for the next time, take down your beam, and sell your amplifier, because when your turn comes, you won't need them. You won't need your brain, either.

What's coming in the future? Unfortunately, probably more of the same, as mediocrity breeds mediocrity. As more and more new DXers come to know no operating style other than L/N, they will demand, verily, that L/N becomes the norm. New, inexperienced operators may be easily enticed into the rut, during that period of time when they need a sheet to determine whether it is the plate current or the output that is supposed to be peaked. As L/N grows, additional DXers will be driven from the bands only to be replaced by still more L/N operators. Make no mistake about it! It already is happening, and the pace is accelerating. Blame it on the lax FCC exams, on the Welfare State, on the "Me Decade," on the weather, on the Democrats, the Republicans, the hippies. The only ones who can reverse the trend and make DXing what it once was-a competitive activity-are you and me. DXing was never supposed to be easy, from the first time Hiram Percy Maxim used a relay in Windsor Locks to work from Hartford to Massachusetts. DXing has been the true spirit of amateur radio. If it ceases to be so, many will find new hobbies and hamming will be the less for their loss. One thing L/N has done is given amateur radio column writers and bulletin editors some cannon fodder, as they stake their claims on one side of the issue or the other. You may disagree violently with this column's

An American operated last autumn from Africa, on CW only, from a fairly rare country. Great, you say, at least he knows the

Continued on page 182

ICOM Quality and Performance in the Most Compact and Economical Hand-Held Designed for Ham Radio.

rezzaiolen.



FEATURES YOU'VE WANTED

- Touch Tone® Pad
- 800 T/R Channels. Synthesized.
- 1.5 Watt Output High/ Low Power Battery Saving Switch to .15 Watt.
- Separate built in Speaker & Mic. Excellent audio quality.
- Compact. About the size of a dollar bill.
- Variable size NiCd Power Pack, 3 sizes available to suit your needs. (250 MA standard). Makes the IC-2AT the most compact synthesized Hand-Held on the market. **ICOM level Receiver** Performance-ICOM Quality Receiver in a compact package (.2uv/20db typical) **Optional Leather Case**, Mobile Charge Cord, Desk Charger, Speaker/Mic available. With slip on/slip off Bottom NiCd Pack, you can vary the size of the Hand-Held from about 116 mm high to 175 mm high. Easy to carry extra Snap-on packs packs with you for extended trips. Complete with BP3 NiCd Pak, wall charger, flexible antenna and belt clip.



BACK VIEW 600 khz offset simplex/duplex Hi/lo power



TOP VIEW BNC antenna connector "Rubber Duckie" standard transmit indicator squelch

volume

control

Dut the ICOM IC-2AT in the palm of your hand.

3

6

9

4

Picco

P

Ð

B

0

A

7

 Image: Contract of the second selection

 Speaker/mic jack

ICOM AMERICA, INC.

2112 - 116th Avenue NE Bellevue, WA 98004

3331 Towerwood Dr., Suite 307 Dallas, TX 75234

CONTESTS



Robert Baker WB2GFE 15 Windsor Dr. Atco NJ 08004

CONNECTICUT QSO PARTY Starts: 2000 GMT December 6 Ends: 0200 GMT December 8 Rest period: 0500 to 1200 GMT December 7

Sponsored by the Candlewood Amateur Radio Association (CARA). Phone and CW are considered to be the same contest. Stations may be worked once on each band and each mode. Out-of-state portables and mobiles operating in Connecticut are requested to identify themselves as such as are Connecticut mobiles operating sum of ARRL sections and provinces. Additional DX contacts count for QSO points, but only one DX multiplier overall is allowed. W1QI, the club station, will be operating CW on the odd hours and SSB on the even hours, and counts as 5 points on each band and mode. Novice contacts count as 2 points each and OSCAR contacts count 3 points each.

FREQUENCIES:

CW-40 kHz up from the bottom of each band.

SSB-3927, 7250, 14295, 21370, 28540.

Novice—3725, 7125, 21125, 28125.

ENTRIES & AWARDS:

A Worked All Connecticut Counties certificate will be awarded to each station working all Connecticut counties. Other awards given as usual, minimum of 5 QSO points! Logs must show category, date/time (GMT), stations, numbers, bands, QSO points, and claimed scores. Enclose a large SASE for results. Logs must be postmarked by January 2nd and sent to: CARA, c/o Steve Grouse KA1ECL, 3 Queens Court, Danbury CT 06810. Use all bands from 160 to 2 meters, CW and phone combined, and everybody works everybody. Classes of entry include: single-operator, all band; singleoperator, single-band; and multi-operator, single-transmitter, all band. All contacts with amateur stations are valid. The same station may be worked twice on each band: once on CW and once on phone. No crossmode contacts and no CW contacts in the phone bands allowed.

EXCHANGE:

Signal report and consecutive serial number starting with 001. VE1 stations will also send their province (NS, NB, PEI).

SCORING:

10 points for each contact with Canada, 1 point for each contact with others. 10 bonus points for each contact with any CARF official news station using the suffix TCA or VCA. Multipliers are the number of Canadian provinces/territories worked on each band and mode (12 provinces/territories × 8 bands × 2 modes for a maximum of 192 possible multipliers).

FREQUENCIES (as applicable):

Phone-1810, 3770, 3900, 7070, 7230, 14150, 14300, 21200, 21400, 28500, 50100, 146520.

CW-1810, 3525, 7025, 14025, 21025, 28025, 50100, 144100.

Suggest phone on the even hours (GMT), CW on the odd hours.

AWARDS:

The CARF Canada Contest Trophy will be awarded to the highest scoring single-operator entry. Certificates will be awarded to the highest score in each entry class in each province/territory, USA call area, and DX country, to the highest score from a Canadian non-advanced amateur (no phone on 3.5-21 MHz), and where participation warrants.

ENTRIES

A valid entry must contain log sheets, dupe sheets, and a summary sheet showing a chart of multipliers per band/mode and score calculation. Send your entry with comments to: Canadian Amateur Radio Federation, 203-1946 York Avenue, Van-

Continued on page 182



in other counties.

EXCHANGE:

Send QSO number, RS(T), and ARRL section or Connecticut county.

SCORING:

Out-of-state stations multiply total QSOs by the number of Connecticut counties worked (8 maximum). Connecticut stations multiply total QSOs by the

CANADA CONTEST Starts: 0001 GMT December 28 Ends: 2359 GMT December 28

Sponsored by the Canadian Amateur Radio Federation, the contest is open to all amateurs.

CALENDAR

Dec 6-7	ARRL 160-Meter Contest
Dec 6-8	Connecticut QSO Party
Dec 13-14	ARRL 10-Meter Contest
Dec 28	Canada Contest
Jan 3-5	Zero District QSO Party
Jan 10-11	Hunting Lions in the Air
Jan 17-18	73's International 160-Meter Phone Contes
Jan 17-18	Michigan QRP Club CW Contest
Jan 17-19	QRP SSB QSO Party
Jan 18	FRACAP Worldwide Contest
Mar 7-8	1981 SSTV Contest
Mar 21-22	Bermuda Contest
Aug 8-9	European DX Contest-CW
Sep 12-13	European DX Contest—Phone
Nov 14-15	European DX Contest—RTTY

VEDAFID

BERMUDA	CONTEST 1980	GI4ELQ	102,600		
RE	SULTS	GI4ISR	72,080		
		G3TKF	56,140		
West	Germany	G2FXQ	16,290		
DK9WB	383,295	G4FJT	13,910		
DK5EZ	343,600	G4HQN	7,370		
DL7SU	113,220	G4GFH	5,680		
DF6UO	109,410				
DF9ZP	78,715	Cana	ida		
DK8OP	32,065	VE5RA	100,270		
DF6JX	22,100	VE3HGZ	99,000		
DF1JI	19,450	VE1AIH	72,450		
DF6AT	15,795	VE3NE	45,560		
DL2OY	14,740	VE2NL	43,520		
		VE3DJX	13,870		
	USA	VE3KK	8,550		
W3MA	128,975	VE4ADS	2,520		
N1ZZ	125,775				
KB8JF	71,225	Berm	uda		
K3DH	39,600	VP9IB	3,025,000		
WA2RUX	31,510	VP9IX	1,128,245		
W3HNK	25,415	VP9IW	557,230		
K6SVL	16,260	VP9JQ	68,370		
KA1EP	15,900				
W9RE	14,880	Check	Logs		
W2FFQ	12,500	DEOHX	VP9CP		
		DIQIK	VP9HI		
United	d Kingdom	HI3DJP/W2	VP9II		
G4DSE	532 740	VE3PE/VP9	VP91.1		
G3VPW	484,560	VETVX	VP9KI		
G3VOF	267,930	VP9AD	W3ARK		

Louis N. Anciaux, WB6NMT stands behind every product he makes at Lunar Electronics.

All Lunar products are designed and manufactured under the direct supervision of Louis Anciaux, head of Lunar Electronics. While Lunar maintains a complete QA department, Louis controls the final check-out. If it's not right, it's not shipped.

That's why, in amps, pre-amps, and transverter modules, Lunar is considered the standard of the industry. As in all ham products, you get what you pay for...that's why Lunar is your best buy.



LUNAR LINEARIZED AMPLIFIERS

One reason our Linearized amp/pre-amp combos are the best selling amps in the amateur market is the superior linearity our units exhibit in the SSB mode. To be "Linear," the amplifier's output signal must be an exact reproduction of the input signal, with only the power level changed.

Lunar is the originator of the LINEAR-IZED process, and all of our amps exhibit this by the very small amount of side-splatter produced. Others may attempt to copy us. But, why buy a copy when you can have the original.

2 Meter Amps

40 to 160 watt power output. From 1124#

For 220 MHz

25 to 140 watt power output. From \$159%

For 6 Meters

50 to 120 watts. From \$19990 Commercial and other special frequencies available.

LUNAR TRANSVERTER MODULES

The addition of Lunar Transverter Modules to your present transceiver in various combinations expands your station's coverage from HF through UHF.

FOR COMMUNICATION CAPABILITY

Adding Lunar Transverter Modules to your present transceiver allows you to include working Oscar Phase III, exploring 220MHz SSB, or many other present and future uses of amateur radio.

FOR AMATEUR TV (ATV)

Special Lunar Transverter Modules can allow you to transmit/receive 440 MHz ATV signals from/to Channel 3 I.F.

AMATEUR RADIO ASTRONOMY

Lunar can provide you with modules for receiving noise from the sky (make your own sky noise chart), or from the sun (plot occurances of flares). We even have modules that receive the weather satellite transmissions (they can be connected to your home computer for a weather map print-out on your CRT display).

LUNAR RECEIVING PRE-AMPLIFIERS

These ultra-performance receiving pre-amps are suitable to the most demanding needs where low noise figure is important. Uses include all types of weak signal work such as EME, Tropo, Iono and Meteor Scatter, Satellite Communications, Radio Astronomy, weak, etc. Absolutely the highest quality construction and components.

Models for all amateur bands through 1296 priced from \$35%



2785 Kurtz Street #10 San Diego, CA 92110 (714) 299-9740 TELEX: 181 747



Marc I. Leavey, M.D. WA3AJR 4006 Winlee Road Randallstown MD 21133

December would be a bleak month indeed, if it were not for the holidays at the end. Whether you celebrate Christmas or Hanukkah, or just enjoy exchanging gifts, the season provides a warm flicker in the middle of winter. This month, we will look at some gift ideas for the amateur involved in RTTY. Perhaps this will give you an excuse to let this copy of 73 sit around where someone else can see it!

At the outset, let me make it clear that I am not describing expensive or exotic items. Most of these will be under ten dollars, and many far less than that. Several of them are not even exclusively amateur radio items, which will make it that much easier for the spouse or child to find. Above all, I have tried to compile a list of unique gift ideas that are affordable, useful, and obtainable, any one of which would delight the heart of the recipient. For hard usage, heavily inked cotton ribbons, specifically made for teleprinter applications, are best, and these may often be found at larger office supply houses.

What do we type on but paper, and this is another item often in short supply in the shack. I have found that standard roll paper, 8.5 inches wide, is available from most business form suppliers at a fairly reasonable price. Look in the Yellow Pages for a supplier near you and check several out. While you are asking, check on the availability of 11/32-inch paper tape. This is another perpetual "need" of the teleprintophile, especially one who is involved with RTTY art or traffic, both of which are quite popular this time of year. Although hamfests are usually the most economical places to stock up on these paper goods, they can be had, albeit at list price, from dealers in most areas.

Maintenance items for the mechanical teleprinter are often overlooked and fall into the "make-do" category. How about a big can of grease for the type bars? Lubriplate is one popular make and is available at most large hardware stores. Don't forget the oil for the felts. I use automobile oil; get something expensive for snob appeal-it goes a long way! Is the print all mucked up? Get back to the stationery store for some type cleaner. All kinds of products are available, from liquids to gobs of sticky stuff to press into the type. The kind I have found most useful is a sheet designed to be placed into the machine, like a piece of paper, with the ribbon off. Run all the characters a few times on tape and the type is clean! A sure winner for anyone.

Perhaps the ham is interested in keeping the shack looking tiptop (obviously never saw mine!). Black wrinkle finishes, such as are found on many kinds of RTTY equipment, perk up nicely under a coat of black liquid shoe polish. When you're getting a bottle, pick up some paste wax, the old-fashioned kind, for other equipment finishes around the shack. A bottle of spray-on glass cleaner would round out a "spic-and-span" gift package.

Another item, the need for which is obvious to anyone who ever worked on a teleprinter away from running water, is a box of pre-moistened hand wipes, like "Wash-n-Dry." Certainly not expensive, but throw it into any of the above packages, or by itself, and it will be appreciated the first time something breaks down.

For the RTTYer who is using a computer, consider a supply of cassettes or diskettes. Neither is very expensive, but they come in handy when you need to make a record of something. Diskette cases, which are now stocked by many office supply houses, come in useful for organizing the disk-based shack; cassette racks, which are available in a wide variety of styles at audio and discount houses, do the same for the taper. Consider reading material. Subscriptions to 73 Magazine, RTTY Journal, or other amateur radio publications may be just the ticket. If computers are involved, try Kilobaud Microcomputing, 80 Microcomputing (for the TRS-80 addict), 68 Micro Journal, or any of the other computer magazines. Look through the 73 Bookshop ad in the back of this magazine for many titles of interest to the RTTYer, computerist, and ham in general. There is surely one there to delight any ham. In the realm of reading material that may be more difficult to come by, is there a set of manuals to the RTTY machine in your life? The Teletype Corporation put out extensive manuals on the Model 15, Model 19, Model 28, and other Teletype

machines in common use. If you, or your ham, do not have them, check the ads for suppliers who may. Finding them may be difficult, but there will be real joy in the eyes when they detail the way to deal with a problem.

Want to spend a little more money? How about a low-priced demodulator? Monitors are available for those computer nuts who are still using converted TV sets. Other kinds of gizmos are out there, any of which would be eagerly received by a hungry ham. Logic probes, breadboard kits, and gift certificates at a local emporium on up to hundred-dollar counters, single-board computers, and disk drives, there is something to delight the ham's heart from pennies up. I hope these suggestions help.

Now let's pick up a letter from Wayne Hall WB4OGM from Colorado. Wayne writes that he has acquired a MITS 680b microcomputer, which has all of 1K of RAM in it, and wonders if there is any way to add more memory. For those who are not familiar with the 680b, this was a machine that MITS, whose first machine, the Altair 8800, started this computer craze, brought out to exploit the then-new Motorola 6800. Although it used the same CPU as the more-successful Southwest Tech 6800 machine, it used a bus unique to itself. Thus, neither S-100 boards nor SS-50 boards will fit. Well, this problem was tackled in an article in Kilobaud (that's all it was called then!) in its third issue, March, 1977. In fact, there are two articles on the 680b in that issue. The first, by Anthony R. Curtis, describes building the 680b and is a sketchy review of the box. The other article, entitled "Make Your 680b Smarter," describes the efforts of Stu Mitchell and Phil Poole to design and build an S-100 adapter that fits inside the 680b case. This allows the use of S-100 memory. Although an 8K board was considered hot stuff back in 1977 (my, how time flies), you can get quite a bit more on a board now. The article includes a printed circuit layout of the board and full details on implementing the augmentation. More reviews on the way, with whatever I can lay my hands on as the target. Reader questions and more fun, here in RTTY Loop in eighty-one!

As any of us in RTTY know, it is the little things that mean a lot. A trip to any stationery store will turn up many items useful to the RTTYer. Ribbons are always needed by the hard-copy devotee. There is no need to look far and wide for Teletype® ribbons; standard Underwood typewriter ribbons are a perfect fit and are usually much more available.

7500 SALES OPPORTUNITIES FOR YOUR COMPANY

Be part of the ROCHESTER SHOW MAY 15-16. Largest show in NORTH-EAST and CANADA.

Call or write HAROLD SMITH

716-424-1100

P.O. Box 1388 Rochester, NY 14603





There are those who will only be satisfied with the finest.

For these perfectionists HAL Communications is pleased to offer the DS 3100 Automatic Send-Receive ASCII, Baudot and Morse Terminal. We cordially invite you to request our catalog.



J 345

HAL COMMUNICATIONS CORP. Box 365, Urbana, IL 61801, (217) 367-7373

For our European customers, contact: Richter & Co. D 3000 Hannover 1 • Transradio SA, 6816 Bissone/Lugano • Radio Shack, Ltd., London NW6 3AY • Erik Torpdahl Telecom, DK 3660, Stenlose, Denmark

AWARDS

Bill Gosney WB7BFK 2665 North 1250 East Whidbey Island Oak Harbor WA 98277

FORT WAYNE RADIO CLUB AWARD

This week, I was pleased to receive a very nice letter from Bernard Holm K9JDF, who is the Communications Manager for the Fort Wayne Radio Club out of Fort Wayne, Indiana. In his letter, Bernard provided details of an awards program sponsored by their club station, W9TE. Here are the award program details.

To qualify for the Fort Wayne Radio Club Award, applicants within Allen County, Indiana, must work 25 individual members of the Fort Wayne Radio Club. Applicants located elsewhere in the United States must work a minimum of 5 Fort Wayne Radio Club members. There are no band or mode restrictions, but all contacts must be made after January 1, 1979, to be valid.

To apply, prepare a list of claimed contacts in order by callsign. Include the name of the station operator, the date and time worked in GMT, and the mode and band of operation. Have this list verified by at least two other amateurs or by a radio club official, stating that QSL cards were in your possession at the time verification was made. to: Fort Wayne Radio Club, Inc., PO Box 15127, Fort Wayne IN 46885.

Last month, I featured a couple of awards from our amateur friends in Brazil. Not realizing the popularity of these programs, I received two more that I would like to share with you now.

GPCW AWARD FROM BRAZIL

Sponsored by the Grupo Praiano de CW, this award is made available to amateur operators throughout the world.

To qualify for the GPCW award, applicants must establish two-way contacts with at least 5 members of the Group. These contacts must have been made after November 5, 1973, to be valid. All authorized amateur bands may be utilized, but only CW contacts with a minimum report of 338 may be claimed.

To apply, prepare your list of contacts, listing the usual logbook information, and have it authenticated by a local radio club or at least two fellow amateurs. Enclose your application with at least 5 IRCs to: GPCW, Box 556, 11100 - Santos, Brasil, South America.

AN OPEN LETTER TO CLUBS AND ORGANIZATIONS

Each year, literally thousands in our fraternity of radio amateurs seek ultimate recognition by accomplishing the many levels of operating excellence. And, thus, "award hunting" has become a unique aspect in amateur radio operation.

To achieve the many goals established by them, amateurs rely almost entirely on publications such as 73 Magazine to inform them of the various award incentives. Each month, I dedicate a special multi-page Awards column to over 150,000 readers throughout the world. With every edition, this figure grows.

Should your own organization have an awards program, I would like to extend a personal invitation for you to share its contents with our many readers. What an excellent opportunity this will be for you to gain worldwide recognition at absolutely no cost to you whatsoever!

To obtain this free service, please forward 1) rules for each award being offered and 2) a sample copy of each award certificate.

Perhaps your organization doesn't have an awards program yet? Allow me to encourage your officers to consider such an endeavor. Not only will it bring immediate recognition, but it can serve as a reliable source of revenue for your organization.

Good luck and my sincere thanks for your dedicated support!—Bill Gosney WB7BFK

PPC AWARD FROM BRAZIL

Radio amateurs the world over are invited to become eligible for the PPC Award, sometimes referred to as the "Carioca Woodpecker's Award."

To qualify, applicants are required to establish two-way CW contact with different PPC members. Brazilian amateurs must make 10 contacts, while amateur operators located outside the country of Brazil must conduct 5 individual QSOs on the CW bands. PY6HL, PY7CGV (YL), and the following list of Silent Keys: PY1AIF (1966), PY1BXO (1968), PY1DB (1977), PY1TC (1977), and PY1DNN (1977).

Traveling abroad, we learn of a very challenging award from Sardinia. At least from a DXer's standpoint on the west coast of the states, this one ain't easy, my friend!

Enclose your application with an award fee of \$1.00 or 2 IRCs GPCW members who qualify as contacts are: PY2ARX, BBO, BKT, BOP, CE, CJW, CSI, CYE, CZL, DBU, DHP (YL), DYX, EQR, EW, EWB, FYF, EXD, FDO, FNB, FPE, FRW, GUN, GYJ, RG, TT, YON, ZY, and PY1DG/2.



To be valid, all contacts must be made after March 1, 1965, which is hailed as Rio de Janeiro's 4th centenary. A minimum signal report of 338 must have been logged for each claimed contact.

To apply for the PPC Award, have your contacts verified by at least two fellow amateurs or by a radio club official. Enclose this list along with an award fee of 5 IRCs addressed to: PPC Bureau, PO Box 2675, 20000 Rio de Janeiro, RJ, Brazil, South America.

This award also may be earned by SWLs and the same rules apply.

PPC members are: PY1AFA, ARS, AVV, AZ, BHO, BIR, BLG, BOA, CBW, CC, CCE, CFS, CIP, CMT, CTP, DDI, DMZ, DNL, DNS, DOG, DUB, DUJ (YL), EFX, EHF (YL), EHN, EIR, HO, JN, KO, LA, LG, MB, RJ, SJ (YL), PY2EW, PY2FWT, PY2RG, PY4CZ,

GOLD SARDINIA AWARD

Sponsored by the URS Club of Sassari, Sardinia, the Gold Sardinia Award is granted to any licensed amateur or shortwave listener who has made contact with or heard stations in Sardinia since January 1, 1976.

To qualify, European applicants must accumulate a total of 20 points, while amateurs outside Europe must gather 15 points total. The points are figured this way: Each contact with a URS Club member counts 4 points on HF and 5 points on the VHF bands. A contact with ISØLYN counts 6 points regardless of the band. All other Sardinian contacts count 1 point on the HF bands and 2 points on the VHF bands. The same station may be worked on the same band on different days or the same day on different bands for award credit. For example, should you be fortunate enough to work ISOLYN on all three

Continued on page 183

Count on DSI Frequency Counters to deliver. 1.2 GHZ for only \$189.95 Accuracy Sensitivity High Resolution and Reliability Meeting All FCC Regulations Accuracy Sensitivity High

Checking a 960 MHz transmitter; Servicing a TV tuner; VTR; Calibrating instrumentation; Measuring PLL signals; Reading a PL or audio signal to 1/1000th of a Hz(Models C1200, 5700 only) - Whatever your needs -DSI's 1.2 GHz Models 5700, C1200 or 1 GHz Model 5510 or 512 MHz Model 5500 are sure to provide the accuracy, sensitivity and flexibility required to meet your most stringent criteria. All C1200 counters include 1/1000th Hz capability and a variable sensitivity control. (Resolve 1/1000th of a Hz with your 5700 by adding option AM57 - Audio Multiplier.) The 5500 series are compact and portable and use a TCXO time base, while the 5700 and C1200 offer laboratory standard oven time base oscillators. Portability is improved on all models with the addition of the rechargeable NiCad battery pack which includes AC batt eliminator/AC9. All DSI models will operate on 8 to 14.5 VDC, and include 50 ohm and 1 Meg BNC inputs. Join the growing ranks of tens of thousands of satisfied customers who have discovered that DSI offers the best price to quality features ratio in the industry.



MODEL C1200 \$269.95 BUILT-IN AUDIO MULTIPLIER 1/1000 Hz RESOLUTION ON AUDIO 50 Hz - 1.2 GHz



MODEL 5500 50 Hz - 512 MHz \$119.95

MODEL 5510 50 Hz to 1.0 GHz \$139.95

1		
	Ant-How Pepiloci Louista	
	5 10 0 2 0 9 9	
		6
PL	ATTIL TON THE REAL PROPERTY AND ADDRESS OF THE REAL PROPERTY ADDRESS OF THE	

MODEL 5700 50 Hz - 1.2 GHz 189.95

..... 34.95 34.95

..... 8.95

..... 8.95

Foreign Dealers

Centro Instrumental Electronico SA

AVDA Independencia 1956

1225 Buenos Aires

San Juan P.R. 00903

Vancouver, Canada BC 6P6E3

West Germany (089) 7144065

New Zealand & Australia

810 SW Marine Dr.

Southern Cross EI.

West Garmany

Heighof Str. 5

4006 Erkrath 2

MCR Electronics

1420 Brane L'Alleud

West Germany

Dynatrade

Belgium

Belgium

26 Sauthern Cross Rd.

Keithley Instruments

Schimmelbusch Str. 25

Chaussee De Nivelies 100

8000 Munchen 70

Kohmarma Auckland NZ

Argentina

Argentina

Canada

Dollard

Puerto Rico

Redio Comm.

P.O. Box 1832

..... 8.95

	FREQ.		and in some		SEN	SITIVITY	YP.		RESO	UTION	
MODEL		FREQ.	TYP. OF	ACCURAC	ATURE	100 Hz to	25 MHz to -	250 MHz to -	NO. OF	AUDIO FREQ.	50 Hz to
		OSC.	20º - 35° C	0° - 40° C	25 MHz	250 MHz	512 MHz	DIGITS	USING SCALER	50 MHz	1.2 GHz
5500	50 Hz to 512 MHz	тсхо	± 1 ppm	±3 ppm	15 25 My	15 	20 - 75 Mv	8	N/A	1 Hz	10 Hz
5700	50 Hz to 1.2 GHz	oven	±.2 ppm	± 1 ppm	10 	10 20 My	15 50 Mv	9	SAME AS C1200 WITH OPT. AM57	.1 Hz	10Hz
C1200	50 Hz to 1.2 GHz	oven	± 1 ppm	±.5 ppm	10 	10 	15 50 Mv	9	.001 Hz Std.	.1 Hz	10 Hz

NOTE: 9th Digit-Overflow 1

NOTE: Prices and/or specifications are subject to change without notice or obligation by DSI Instruments, Inc. Please add 10% to a maximum of \$10.00 for shipping, handling and insurance. Orders outside of U.S.A. & Canada, please add an additional \$20.00 to cover air shipment. California residents add 6% sales tax.

To Order Call



5500 BAC	139.95 AM57	
5700	19.95 BA-57	
C1200	269.95 A C-9 T-600	

Toll Free 800-854-2049 DSI INSTRUMENTS INC. 9550 Chesapeake Dr. San Diego, CA 92123 • (714) 565-8402

See Your Local Authorized DS/ Dealer

West Indies Sales

Hialeah, FL 33010

Com-Tec Assoc.

305-267-6453

Britt's 2-Way

Georgia

215 Hopkins Ave. (US1)

Titusville FL 32780

2508 Atlanta Street

Smyrna, GA 30080

Ack Radio Supply

Atlanta, GA 30309.

Honolulu HI 96814

Ross Distributing

Preston, ID 83263

Gardner Electronics

Orleans, Indiana 47452

5456 N. Milwaukee Av.

404-351-6340

808-521-1227

78 S. State

208-852-0830

204 Wesley St

812-865-2459

312-631-5181

312-631-5181

Erickson Comm.

Chicago: IL 60630

Floyd Electronics

Collinsville IL 62234

2213 Vandalia St.

Spectronics, Inc.

Oak Park IL 60304

Audas Radio Electronics

1009 Garfield St.

312-848-6777

Kansas City, KS

307 McLean Ave

502-886-4534

Cohoon Ama Supply

P.I. Burks Company

Hopkinsville, KY 42240

Kansas

Kentucky

Hawaii

Idaho

Indiana

Illinois

554 Deering Rd. NW

Van's CB Radio Supply

1352 'D' So Beretama St.

690 West 28th St

20

Alabama

Amatronics Route 1 Box 1039 Millbrook AL 36054 205-285-3033

Ack Radio Supply 3101 4th Ave. South Birmingham AL 35233 205-322-0588

Arizona Arizona Radio Comm 2245 No. 7th St. Phoenix, AZ 85006 602-257-8559

California Base Station 2101 Pacheco Concord CA 94520 415-685-7368

Cal-Pine Elec 1950 Lake Tahoe Blvd. South Lake Tahoe. CA 95731 918-541-3777

Center Comm. 455 Auzerias San Jose, CA 95126 406-297-2581 408-297-2530

Cut Rate Elec t074 S. Brawley Fresna CA 93706 209-264-9952

Jun's Elec. 11656 E. Pico Blvd West Los Angeles, CA 90064 213-477-1824

University Ave San Diego 714-463-1886 **Omega Radio Elec.** 7094 Miramar Rd 101 San Diego, CA 92121

714-578-3324 Henry Radio 11240 W. Olympic Blvd Los Angeles, CA 90081 213-477-6701

Henry Radio **B31 N. Euclid Ave** Anaheim, CA 92801 714-172-9200

Hobbytronics 1378 S. Bascom Ave. San Jose, CA 95128

408-998-1103 C & A Roberts, Inc. 2559 East 220th St. Long Beach, CA 90810 213-835-9221

Estero Comm. 573 Manunita St. Los Osos CA 93402

Tele-Com 15460 Union Ave San Jose, CA 95124

Cherokee Elect. & Comm. 6119 Graystone. Citrus Heights: CA 95610 916-969-1339 Sacramento 305-888-1676

Colorado Comm. Unlimited 6210 East 6th Ave. Denver, CO 80220

Delaware Amateur Adv Comm.

3208 Cnord Pk Rt 202 Wiimington, DE 19803 302-478-2757 Delaware Ama Sup.

71 Meadow Road New Castle, DE 19720 302-328-7728

Florida Amateur Elec. Sup. 521 Commonwealth Ave. Orlando FL 32803

A.G.L. Electronic 1898 Drew St. Ciearwater, FL 33515 461-4267 Hialeah Comm.

612 East 9th Street Hialean FL 33010 305-805-9929 Hollister & Claytor

1747-1749 Pearl St. Jacksonville, FL 32206 904-353-7898 Lakeland Spec. Elec.

37424 Swindell Road Lakeland, FL 33801 813-688-4181

N & G Distributing 7285 NW 12th Street Mam. FL 33126 305-592-9685

Quad Electronics 2251 North E St Pensacola, FL 32501

904-438-3319 Ray's Amat Radio. 1590 US 19 South Clearwater FL 33516

813-535-1418 Tymms Elec. Ser. 14714 NW 7th Ave

Miam. FL 33168 305-681-8544 Amat Radio Center 2805 NE 2nd Ave

Miami, FL 33137

Halean, FL 33012

305-573-8383

305-887-3203

AB Comm.

842 South 7th Street Louisville, KY 40203 502-589-3960

Maine 1660 West 32nd St. Place

Downeast Hamshack 206 Northriver Rd Auburn, ME 04210 207-782-8642

Maryland Com Center 24 Fort Mead Road Laurei, MD 20810

301-792-0600

Elec. Int. Svc. Corp. 11305 Elkin St. Wheaton, MD 20902 301-946-1088

Mississippi Hooper Elec. Sup. 495 Rodenburg Ave Biloxi, MS 39531

601-432-0584 Michigan. Purchase Radio

327 E. Hoover Ave. Ann Arbor, MJ 48104 313-668-8696 313-668-8262 Minnesota

P.T.I. 10201 103rd St. No: Stillwater, MN 55082

612-429-2975 Pal Electronics 3452 Fremont Ave. N Minneapolis, MN 55412

612-521-4662 Missouri

Mid-Com 2506 S. Brentwn St. Louis, MO 63144 314-961-9990

9807 View Cove Dr. Parkville, MO 64152

Roberts Rx Elec. 405 E 19th Ave N. Kansas City, MD 64116 816-471-4149

Saturn Elec. #9 Country Lane Florissant, MO 63033 314-831-1449 Massachusetts Norbill's Elec. 2097 Riverdale St.

W. Springfield, MA 01089 Tuft's Radio & Elec. 209 Mystic Ave. Medlord, MA 02155 800-225-4428 617-395-8280

TL-Comm 675 Great Rd. Rf. 119 Littleton: MA 01460 517-486-3040

New Jersey Summit Radio Sup. 1008 Teaneck Rd. Teaneck, NJ 07666 201-837-3644

New York

Barry Electronics 512 Broadway New York, NY 10012 212-925-7000

Comm. Tech. Group 488 Merrick Rd. Oceanside, NY 11572 516-536-5724

Cavaliere Elec. 2536 14th Street Astoria, NY 11102

Grand Cen. Radio 124 E. 44th St. New York, NY 10015

JR'S Amateurradio 1185 Scottsville Rd. Rochester, NY 14624

Radio World 605 Beech Street Rome, NY 13440

North Carolina Georgetown Comm. 1074 Patton Ave Asheville, NC 28806

704-252-9815 Vicker's Elec. 500 East Main Street Durham, NC 27701 919-683-1597

Ohio Amateur Elect. Sup. 28940 Euclid Ave. Missouri Comm Systems Inc. Wickliffe, OH 44092 216-585-7388

800-362-0290 Queen City Elec.

7404 Hamilton Ave. Cincinnati, OH 45231

Universal Amateur 1260 Aida Drive Reynoldsburg, OH 43068 614-373-4987

Marietta Radio & TV 1028 E. Green Marietta, OH 45750 614-373-4987

Srepco Elect. 314 Leo St. Dayton, OH 45404

Oklahoma Brodie Elec. 2537 Edgewood Dr Moore, OK 73160 405-794-0406

Derrick Elec. 714 W. Kenosha Broken Arrow, OK 74012 918-251-9923

Nebraska

402-346-5530

Omaha Amat Center Sere-Rose-Spencer 2565 Dodge Street Omaha, NE 68131

Nevede

Amateur Elec. Sup. 1072 N. Rancho Dr. Las Vegas, NV 89106

702-647-3114 New Hampshire

Evan's Radio, Inc. Rt. 3A Box 893 Bow Junc

Concord, NH 03301 603-224-9961 Oregon Siskiyou Radio

586 N. Main Ashland, OR 97520 503-482-4555

Oregon Ham Sales 401 W. 1st Ave. Albany, OR 97321 503-926-4591

Pennsylvania Inc "Ham" Buerger 68 North York Road

Willow Grove, PA 19090 215-659-5900 Hamtronics

4033 Brownsville Rd. Trevose, PA 19047 800-523-8998

Rhode Island D & N Communications

1854 Smith St. No. Providence, RI 401-231-6653

South Carolina **A & G Electronics** Route 3 Ayersdale Dr. Taylors, SC 29687

803-268-3330 **Radio Com-Charles**

100 B Farm Road Goose Creek, SC 29445 Giamo Comm.

2305 Cherry Rd. Rockhill, SC 29730 803-366-7157

Tennessee ARSON.

615 S. Gallatin D. Madison, TN 37115 615-868-4956

Rush Electronics 1315 Bluff City Hwy. Bristol, TN 37620 615-764-0831 800-251-0264

1465 Wells Station Memphis, TN 38117 901-683-9125

Toxas Amateur & Comm. Elec. 5691 W. Creek Dr

Ft. Worth, TX 76133 817-294-1801

Kennedy Assoc. 2618 Rigsby San Antonio, TX 78222 512-333-6110

Leak Proof Seal Red Bird Airport #8 Daltas, TX 75232 214-337-4346

Madison Elec. 1508 McKinley Houston, TX 77002 713-658-0268

Omega Electronics Rt. 1-10 Climer Dr. Amarillo, TX 79106 806-352-8251

Alpha Tronics 3713 Cranston Ct. East. Irving, TX 75062 214-255-8583

B & T Electronics 10457 Seawood El Paso, TX 79925

Virginia Elec.Equip. Bank 516 Mill St. NE Vienna, VA 22180 703-938-3350

> Radio Comm 311 Shenandoah Av. NW Roanoke, VA 24016 703-342-8513

Harrisonburg, VA 22801

ABC Communications

17550 15th St. NE

Seattle, WA 98154

Amateur Elec. Sup.

Milwaukee, WI 53216

4828 W. Fon Du Lac Ave.

Highland Spring, VA 23075

Virginia, Elec. Com

702 E. Nine Mile Rd

The Tuned Circuit

789 E. Market St.

804-737-5100

206-364-8300

414-442-4200

Ranger Elec.

La Crosse, WI

608-452-3230

Wisconsin

Weshington

LEAKY LINES



Dave Mann K2AGZ 3 Daniel Lane Kinnelon NJ 07405

Tired of knocking your brains out in DX pileups? Frustrated by the sheer idiocy of self-appointed monitors and vigilantes who congregate on the DX station's exact frequency and QRM the action with bickering and other abuse? Turned off by selfish operators who either refuse to abide by the DX station's instructions or who don't bother to listen to them in the first place?

If any or all of these examples fit your present frame of mind toward DX chasing, I may have a solution for you. It may not put you on the Honor Roll, but it will afford you the satisfaction which comes from genuine accomplishment. But let me tell you of the circumstances which led to the idea. When I finally made the coveted Honor Roll after years of dedicated effort, I was faced with a gloomy prospect. I'd grown so used to chasing DX that I'd become bored with other facets of the hobby. DX had become the ne plus ultra, and it was all I thought about in connection with ham radio. This feeling of dreariness devolved out of the realization that only four countries remained on my want list, and while there did exist some slight possibilities that those four would eventually be activated, this did not appear likely in the immediate future.

tions. Mind you, I do not criticize them. But they are just not my cup of tea.

I had never enjoyed participation in traffic nets, and with the exception of a few years of MARS activity, I was not overly attracted to the prospect. (I believe that my distaste was inspired by one of those simulated emergencies back in the 50s, when, as part of an AREC group which I'd joined, I observed one of my colleagues calling Net Control with the astonishing news that Yonkers, New York, had been hit simultaneously with a devastating nuclear attack and a cholera epidemic. I threw up my hands.)

No! The sudden and abrupt realization that DX was about to become a thing of the past for me was a shock. And I could not find a way to cope with it.

Then one day an inspiration hit me like a bolt out of the blue. I was idly thumbing through the Callbook, and my eye was suddenly captured by one of those special entries; you know the sort I mean...the listing was separated from all the others and printed in bold type. And this particular callsign had the same suffix as my own. I had never worked anyone with my own suffix, and I thought it might be nice to hook up with a few and to exchange QSLs. I began writing down in my notebook the prefixes of the various AGZ stations, and I started listening for them on the air. Eventually I latched on to a couple. The first was KØAGZ, and others followed after a few months. I even ran into a few foreign ones, and this prompted me to investigate the possibility of writing to several and proposing on-the-air schedules. They were all over the map, in all countries. For the most part, they showed up at the suggested time and frequency; we established contact and ultimately exchanged cards. In some cases, we have continued to meet on a regular basis ever since the first contact. To shorten the story, I now have over 75 AGZ cards, and I'm sure that I will eventually have 100 of them.

The best part of this, of course, is that notwithstanding the fact that all the other AGZ stations are desirable from my point of view, there is absolutely no competition from anyone else. I don't have to worry about pileups or the loonies who have begun to make a shambles and fiasco out of DX. I can chase AGZs to my heart's content, and there's not another soul who's going to give me a hard time. Others with my suffix seem just as desirous of working me, and there hasn't been a single instance of QSL difficulty: The cards generally arrive by the quickest route.

Some are in Europe, some are in South America; there are many in Canada and in the Antipodes. I have quite a few from the West Indies and from Africa. And, as I mentioned, it's my own game and I can play it to my heart's content. The only limits are dictated by my own energy and willingness to exert myself.

I found that whenever I mentioned this activity, it seemed to elicit interest among others. And the thought occurred that this might be a new and different radio-sport that could be adopted by others who may have become bored with the awards program can be managed at minimal cost, it cannot be done for peanuts. Perhaps the applicants themselves would be willing to help to underwrite these costs by paying a moderate fee of, say, five dollars or some equally modest sum. No one would get rich on the proceeds, that is certain. But no one would go broke either.

What to call the award? How about WYOS, Work Your Own Suffix? Not too bad. But perhaps it would be better if the initials formed an acronym such as do VISTA, Volunteers In Service To America, or NOW, the National Organization for Women. Unfortunately, my background as a professional songwriter and creator of comedy material invariably bubbles to the surface, and I find that every acronym that occurs to my mind turns out to be a four-letter word of questionable taste. Amateur Suffix Society, Callsign Radio Amateur...oh, well, you get the idea, I'm sure. Out there in the vastness of ham radio land, there are enterprising and creative minds; there must be someone who can come up with a unique name in keeping with the spirit of the thing.

But please, I beg you, don't send in your suggestions at this time. And don't send in any applications or money. If and when the program is inaugurated, an appropriate announcement will be made in this space. In the meantime, I urge you to try chasing your own suffix in the same way that I do...on your own and at your own pace. There's no reason why you should have to wait for this activity to be organized. In fact, it might be better if it remained an off-the-cuff thing without all the hoopla of certificates and competition of standings and listings. Since there is no competition in it now, why introduce it anyway? And if it happens that some of you should happen to amass a total which you think unusually high, you might let me know about it. I'll be happy to mention it here so that you can gain the recognition that the achievement deserves. But let me warn you: Despite the lack of competition, it is not the easiest thing in the world to accomplish. It will take dedication and persistence.

I had to find some new interest to take the place of DX; this was clear.

Never much of a constructor, I couldn't envision starting to build at this late date. That possibility was out.

Slow scan television and moonbounce had never "put bubbles in my blood," nor had amateur satellite communicausual and commonplace and are looking for a novel and unique pursuit.

I thought: Suppose the game could be organized, with certificates, endorsements, annual listings, and the like? Suppose it were possible to send out a computer printout of every applicant's callsign counterparts throughout the world, together with mailing addresses? And suppose there were a quarterly newsletter listing standings, profiles of the top contenders, and the like? And suppose there were special awards for multiband and multi-mode?

The idea began to feel exciting. In sounding out friends, I found more than casual interest. I had the feeling that perhaps it might meet with general enthusiasm, both here and abroad. Why not?

The only fly in the ointment, of course, is that if all these supplementary adjuncts were to be incorporated in the game, it would cost some initial money to get the thing off the ground. The printing of a suitable certificate would be costly, and the computer readout would cost several bucks as well. While an

Go to it, and the very best of luck to you all.

THE GIANT A ZDE COMPANY **REVOLUTIONIZES THE STATE OF THE ART** AWE AND AZDEN. INTRODUCE THE BRILLIANT NEW PCS-2000

NOT \$550.00 FALL SALE 259000

REG. \$369.00

MICROCOMPUTER CONTROLLED SUPERIOR COMMERCIAL GRADE 2 METER FM TRANSCEIVER

NOT \$550.00 FALL SALE 25900

REG. \$369.00



COMPARE THESE FEATURES WITH ANY UNIT AT ANY PRICE



- FREQUENCY RANGE: Receive and transmit: 144.00 to 147.995 MHz, 5Khz steps + MARS-CAP CAPABILITY BUILT IN (142-149.995 MHz).
- ALL SOLID STATE-CMOS PL DIGITAL SYNTHESIZED.
- . SIZE: UNBELIEVABLE! ONLY 6 3/4" x 2 3/8" x 9 3/4". COMPARE!
- MICROCOMPUTER CONTROLLED: All scanning and frequency-control functions are performed by microcomputer.
- DETACHABLE HEAD: The control head may be separated from the radio for use in limited spaces and for security purposes.
- SIX-CHANNEL MEMORY: Each memory is re-programmable. Memory is retained even when the unit is turned off.
- MEMORY SCAN: The six channels may be scanned in either the "busy" or "vacant" modes for quick, easy location of an occupied or unoccupied frequency. AUTO RESUME. <u>COMPARE!</u>
- FULL-BAND SCAN: All channels may be scanned in either "busy" or "vacant" mode. This is especially useful for locating repeater frequencies in an unfamiliar area. AUTO RESUME. COMPARE!
- INSTANT MEMORY-1 RECALL: By pressing a button on the microphone or front panel, memory channel 1 may be recalled for immediate use.
- MIC-CONTROLLED VOLUME AND SQUELCH: Volume and squelch can be adjusted from the microphone for convenience in mobile operation.
- ADDITIONAL OFFSETS: Provides three additional offset values: +0.4 MHz, +1 MHz and +1.6 MHz. Other offsets may also be obtained.
- · 25 WATTS OUTPUT: Also 5 watts low power for short-distance commun-

15

ication.

- DIGITAL S/RF METER: LEDS indicate signal strength and power output. No more mechanical meter movements to fall apart!
- LARGE ½-INCH LED DISPLAY: Easy-to-read frequency display minimizes "eyes-off-the-road" time.
- PUSHBUTTON FREQUENCY CONTROL FROM MIC OR FRONT PANEL: Any frequency may be selected by pressing a microphone or front-panel switch.
- SUPERIOR RECEIVER SENSITIVITY: 0.28 uV for 20-dB quieting. The squelch sensitivity is superb requiring less than 0.1 uV to open. The receiver radio circuits are designed and built to exacting specifications, resulting in unsurpassed received-signal intelligibility.
- TRUE FM, NOT PHASE MODULATION: Transmitted audio quality is optimized by the same high standard of design and construction as is found in the receiver. The microphone amplifier and compression circuits offer intelligibility second to none.
- OTHER FEATURES: Dynamic Microphone, built in speaker, mobile mounting bracket, external remote speaker jack (head and radio) and much, much more: All cords, plugs, fuses, microphone hanger, etc. included. Weight: 6 lbs.
- ACCESSORIES: 15' REMOTE CABLE....\$ 35.00 CS-6R A/C POWER SUPPLY....\$49.95. TOUCHTONE MIC. KIT....\$39.95. EXTERNAL SPEAKER....\$18.00.

-800-327-302

AMATEUR-WHOLESALE ELECTRONICS ORDER NOW TOLL FREE

8817 S.W. 129th Terrace, Miami, Florida 33176 Telephone (305) 233-3631 • Telex: 80-3356

Hours: 9-5 MonFri.	
--------------------	--

U.S. DISTRIBUTOR

DEALER INQUIRIES INVITED

LETTERS

LEARNING THE CODE

I just wanted to drop you a quick note to say how much your 73 code course helped me. I have sporadically attempted to get my ticket for seven years now. The theory is no problem (I have a commercial 1st phone and have worked in RF for five years), but that code practice would get me every time. I tried manuals and the ARRL code course, but I would memorize the code sent on the cassettes, or, with the manuals, I'd stay on the first few pages and never move on, until I lost interest.

I honestly can't say this about the 73 cassette. I couldn't memorize the code groups, and it introduced new characters so fast and furious that before I knew it, I was through the whole alphabet.

Anyway, I passed the exam for my Tech ticket yesterday, after practicing with the cassette for two weeks! Before, I'd have practiced for a month or so before losing faith. Your code course is great. Now I'll work on my Advanced ticket in my spare time. Tnx again! have heard them all.

I found that after a month and a half with your tapes, I could copy plain English code at better than 25 wpm. Considering that a year and a half ago I didn't know a dit from a dah, I've made pretty good progress.

I believe in giving credit where credit is due; therefore, thank you for helping me to enjoy a great hobby. By the way, your ad states, "...you'll almost fall asleep copying the FCC stuff..." This was not exactly the case, but your point is well taken. Thanks again.

Steve Lewis KF8G Rossford OH

CHRISTMAS DX

The Clark County Amateur Radio Club (Jeffersonville IN) will go on a DXpedition to Bethlehem IN from 1700 UTC December 13th until 1700 UTC December 14, 1980. Using the callsign W9WWI/9, they will operate phone on 3.900, 7.235, 14.285, 21.360, 28.510, and 147.300 simplex. Special Christmas season cards will be sent to all stations and the envelopes will be stamped with the unique Bethlehem IN postal stamps consisting of the Three Wise Men and the Star of David. QSL (with SASE) to Clark County Amateur Radio Club, PO Box 352, Jeffersonville IN 47130.

quently remarked on the quality of the magazine and its editorial standards in the past few years.

Likewise, I was amazed by the quality of the photo reproduction. The negatives are, of course, close to 40 years old. The prints I made late one night, a Sunday, of course, when I could not get paper and had only a few odds and ends of various grades left.

In all, I am pleased (and I know that you will accept this in the proper light) that 73 printed the article...payment aside. It is a source of real satisfaction to an author when everything comes out right.

It may also interest you to know that I've received two letters from old friends who learned of my whereabouts from the piece.

Julian N. Jablin W9IWI Skokie IL

It's nice to have someone notice the superb job Jack has been doing with the editing and production of the magazine... thanks for the bouquet. By the way, it's good to get an article from one of the old guard in New York. I remember contacts and seeing you at radio clubs 30 years ago.—Wayne. one in a higher echelon of the government decides that "excessive" travel must come to a halt. And the result? Many people will be denied the opportunity of obtaining or upgrading an FCC license whether it be amateur or commercial. It's a damn shame! These same people are the ones putting their lives on the line defending this country and ensuring the preservation of peace. As Colonel Potter of M*A*S*H would say, "horse hockey!"

Before I go any further, let's go back to the basics. One of the first things we all learned in our study of amateur radio was its basis and purpose. This can be found in Section 97.1 of Subpart A of Part 97. Listed there are "five" principles of our radio service. To print them here would use too much valuable space, so I will extract some of the finer points for you. Principle number one talks about the recognition and advancement of the Amateur Radio Service and emergency communications. Numbers two and three contain key words such as encouragement, improvement, and advancing skills. Expansion of the existing reservoir of trained operators, technicians, and electronics experts is outlined in number four. And, finally, principle number five mentions our unique ability to enhance international goodwill. This drastic measure taken by the FCC will impede the exercise of these very principles! It's simple arithmetic. As for us here in Germany, look under the "Delta Alpha" callsigns in the latest edition of the DX Callbook. You will find approximately 600 amateurs, of which 85% are Americans. Isn't this enough "clout" to warrant resumption of FCC testing? The number 600 may not seem like much, but with our current problem of a stagnant growth rate, the FCC's policy could show adverse affects. With dwindling numbers and no encouragement from or improvement in the operations of our governing body, the FCC, how are "we" supposed to expand, become "encouraged" and "improved"? We are a public service, dammit! When a natural disaster strikes, hams are usually the first ones on the scene ready to help. And when we do, we are praised and glorified...sometimes. But

Grant Howes Jackson MI

Grant, you should have started with the 13 per...it's no more difficult to learn the code at that speed than at 5 wpm, so why horse around and extend the agony?—Wayne.

BUT THEY WORK

I wish to congratulate you and your staff on a job well done regarding your 73 code cassettes. They are indeed the most mindboggling, frustrating, teethgnashing, high-blood-pressurecausing pieces of recorded material I have ever purchased...but they work!

I used your 21 wpm tape most recently to help me achieve the elusive Amateur Extra class ticket. I don't know how many times I have personally told others of the virtues of your cassettes, but I firmly believe yours are the best on the market, and I

John W. Shean N9TV Jeffersonville IN

SATISFACTION

On my return from an extended vacation, I found the August issue of 73 Magazine in the mail, with my article ("Over There") on page 86.

I must compliment whoever was involved for some very fine editorial work. It is not uncommon these days for a writer, in looking at the printed version of his work, to wonder, "Why did they slip those commas in there?" or "What happened to the last two words of that sentence?" or even "Don't the damn fools know that 'the' is spelled 't-h-e?'" But then, I have fre-

NOT ONE?

GOOD LORD!! Wayne Green in Mensa for 20 years?? It's strange I haven't agreed with one 73 editorial. (Congrats.)

Robert Roither WD0FDK Florissant MO

All of which goes to prove that brains and common sense are not necessarily parallel endowments.—Wayne.

HORSE HOCKEY

At the present time I am stationed with the military in West Germany, where we have the largest American population outside the United States. In the past, the FCC has dispatched examiners to Germany twice a year and many individuals have taken advantage of this. They've traveled from all over Germany and its neighboring countries ... they came by plane, by train, and by car. Examination rooms were jam-packed with more people than you could shake a stick at. Now, all of a sudden, some-

Continued on page 193



Model TE-284

Self-completing dots and deshes

· Ismbic Keying with any squeeze

· Both dot and deah memory

Epert, volume, tone, tune

Low current drain CMOS

battery operation portable

Deluxe quarter mch secks for

and weight controls Sidetone and speaker

PLUS

peddle ●5-50 = p.m

\$89.95

Features:

·State-of the Art CMOS Circuitry -Three choices of Messege Storage

- A. Two (50 character each) message storage -8. Four (25 character each)
- message storage
- ·C. One 50 character and two 25 character message
- storage

Palomar Engineers

1520G Industrial Avenue, Escondido, CA 92025 Telephone (714) 747-3363



VIS4

\$349.95

R-X NOISE BRIDGE \$55.00

- Learn the truth about your antenna.
- Find its resonant frequency.
- Adjust it to your operating frequency quickly and easily.

If there is one place in your station where you cannot risk uncertain results, it is in your antenna.

ANTENNA BALUNS

- Model 1K \$32.50 1 Kw CW, 3 Kw PEP input. Model 2K \$42.50
- 2 Kw CW, 6 Kw PEP input.

ANTENNA TUNER **New Low Profile Design**

Here is a new tuner that puts more power into your antenna, works from 160 through 10 meters, handles full legal power and then some, and works with coax, single wire and balanced lines. And it lets you tune up without going on the air!

IC KEYER \$117.50

All the desirable features are built into this compact self-contained unit. Sends manual, semi-automatic, dot memory, squeeze, and iambic. Speeds 5-50 wpm. Built-in sidetone, speaker, speed and volume controls.

VLF CONVERTER \$59.95

- New device open up the world of Very Low Frequency radio.
- Gives reception of the 1750 band at 160-190 KHz meter where transmitters of one watt power can be operated without FCC license. Also covers the navigation radiobeacon band, standard frequency broadcasts, ship-to-shore communications, and the European low frequency broadcast band.



Beam Balum \$47.50 2 Kw CW, 6 Kw PEP input. Adjustable U bolt for mounting on rotary beams.

Palomar Engineers

1750 Mater Transmitter

0

.

1750 METER XMTR \$145.00

- Main transmitter assembly factory wired and tested.
- Antenna tuning assembly can be wired and mounted on your breadboard in less than an hour.
- Meets all F.C.C. requirements.
- For use in U.S.A. only. Not for Canada.

LOOP ANTENNA

- Low noise reception.
- Nulls out interference.
- Accurate direction finder.
- Rotates 360° in azimuth. Tilts ±90° in elevation.
- Superb nulls.

NEW!

Loop amplifier connects to your receiver or to your VLF converter.

Plug-in loops available for: 1600-5000 KHz (160/80 meter amateur bands) 550-1600 KHz (Broadcast Band) 150-550 KHz (VLF, 1750 meter band) 40-150 KHz (WWVB, Loran) 10-40 KHz (Omega) 5-15 MHz (Model HF-1) Loop Amplifier \$67.50; Plug-in Loop Antenna \$47.50 each.

These items are stocked for Christmas delivery. Order today direct or from your favorite dealer. Include \$3 shipping/handling (\$4 for IC Keyer, \$10 for Antenna Tuner). Add sales tax in Calif. Free catalog on request



John Edwards WB2IBE 78-56 86th Street Glendale NY 11385

ELEMENT 1-CROSSWORD PUZZLE

Across

- 1 A microcomputer memory (abbr.)
- 4 RTTY machine
- 9 Radio users (abbr.)
- 10 Greenland prefix
- 11 Cable prefix
- 14 Something to chew
- 15 Scientific test
- 19 A prosign
- 20 Teletype (abbr.)
- 22 Automatic Picture Retransmission (abbr.)
- 23 What a signal usually carries (abbr.)
- 24 Keyboard Send-Receive (abbr.)
- 26 Soviet space satellite (abbr.)
- 27 A Model 15 is extreme in this
- 29 HW____?
- 30 A display medium
- 33 Sudanese prefix
- 35 Moonbounce (abbr.)

Down

- 1 RTTY Read-Only (abbr.)
- 2 Vertex
- 3 Meteor scatter (abbr.)
- 4 Transmitter-distributor (abbr.)
- 5 Opposite of Hi
- 6 Proficient hams
- 7 Public Relations Assistant (abbr.)
- 8 Code of Ethics laid one
- 12 Morse "from"
- 13 Code Chuckle
- 14 Radioteletype (abbr.)
- 15 Specialized modes require lots of this
- 16 RTTY tape unit
- 17 Radio Corporation of America (abbr.)
- 18 Crystal use
- 21 Soft hams (abbr.)
- 25 "Ears" (abbr.)
- 26 RTTY test string
- 27 Amateur television (abbr.)

SPECIALIZED MODES

Have you ever been accused of being an "appliance operator"? Are you a complete blockhead when it comes to doing anything more technical than shouting into a microphone or tapping a key? When the other guys talk about slow-scan television, do you think they're referring to the instant replays on last Sunday's football broadcast? If so, this month's puzzles are for you.

While RTTY, SSTV, ATV, EME, ASCII, and MSTV may just sound like a bowl of alphabet soup to many of us, there's a whole class of fellow amateurs out there who consider these modes to be the *real* amateur radio—a place for experimenting, not just communicating. So, for those of you not yet hooked on an exotic operating mode, and even for those who are, grab a pencil and see how much you know about ham radio's other side.

ELEMENT 2—MATCHING

Match the specialized mode in Column A with the appropriate equipment in Column B.

Column A

- 1) Slow-scan television
- 2) Meteor scatter
- 3) Digital communication
- 4) Fast-scan television
- 5) Facsimile
- 6) Satellite communication
- 7) Moonbounce
- Microwave communication
- 9) Radioteletype
- 10) Medium-scan television

Column B

- A) Horn antenna
- B) Murphy receiver
- C) Stylus
- D) Keyer (CW)
- E) Model 33
- F) Wideband 10-meter receiver
- G) Steerable dish antenna
- H) 2-meter transmitter/10meter receiver
- I) Stock Robot 400
- J) Model 15
- K) Commercial TV set and converter

ELEMENT 3-TRUE-FALSE

True False

 Eleven meters was the first amateur band opened to slow-scan television.

- 36 Tough WAS state (abbr.)
- 37 Formal shack title (abbr.)
- 38 Old repeater prefix
- 41 Pakistani prefix
- 42 "Idiot Box" or fast scan (abbr.)
- 43 Pictures via radio
- 28 Past of "get"
- 31 Ham salutation (abbr.)
- 32 What most specialized
- modes are
- 34 Recording or paper (mylar, too)
- 39 Transmitter power (abbr.)
- 40 FCC country (abbr.)
- 41 Familiar battery (abbr.)
- 3 5 6 2 11 10 9 13 12 14 18 16 17 15 19 20 21 22 23 24 25 26 29 27 28 33 34 30 31 32 35 36 37 39 40 41 38 42 43
- One of the inventors of the teleprinter was Joy Morton, owner of the Morton Salt Company.
- AF2M is the official FCC designation for frequency-shift telegraphy.
- The Geminids are a December meteor shower.
- 5) The ARRL sponsors both RTTY and SSTV DXCC awards.
- 6) Amateur 10-GHz signals have spanned the English Channel.
- Most moonbounce activity takes place on 144 and 432 MHz.
- The facsimile DX record is from New York, N.Y., to Seattle, Wash.
- Medium-scan television's frame rate is 2 per second.
- 10) To operate a mode not permitted under amateur rules, one can request an "STA" from the FCC.
- 11) Most RTTY enthusiasts gain their WAS awards from "cards" printed on their Teletype.
- 12) Maximum radioteletype shift is 900 kHz.
- "NBVM" stands for Negative Bias Voltmeter.
- 14) ASCII is permissible on 160 meters.
- 15) FSK is allowed on all CW bands, even Novice.
- 16) Many amateurs call moonbounce "EME" in honor of the late K6EME.

Continued on page 180

PRICES F.O.B. HOUSTON

PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

ITEMS SUBJECT TO PRIOR SALE

> ORDER YOUR **KWM 380 NOW! OLD PRICE & FREE GOODS**

BRENWOOD PACKAGE



You simply can't buy better reliability, performance and reputation than the 520 series from Kenwood, and the TS520 SE is no exception. This is a just plain good radio at a tremendous. savings, when you consider the free CW filter (YK-88) and microphone (MC-50) too.

629.95 **TS 520 SE** our gift MC-50 MIC YK-88 CW FILTER TOTAL 629.95



Electronics Supply



SANTEC HT 1200

SUGGESTED LIST \$379.95

> CALL FOR QUOTE



synthesized hf transceiving system

master charg

V45

VISA

continuous coverage



continuous coverage reception no gaps no range crystals required

Amateur Band transmission, including **GO-JO**_{Meters} capability for MARS, Embassy, Government, and future band expansions

> PASSBAND TUNNING R. I. T.

INDEPENDENT RECEIVE SELECTIVITY WILL HANDLE WARC BAND **EXPANSIONS**

CALL FOR QUOTE

ALL BAND COVERAGE!

ASTRO 103

ET CETERA

Cubic-Swan 102BXA	\$999.00
Astro 150	779.00
Astro 100MXA	499.00
Mirage B23 1 watt-30 Watt amp	89.95
DSI 5600A w/Ant/Ac	185.00
Cushcraft A3 Tribander	169.00
Bird 43, Slugs	. Stock
CDE Ham-4 Rotor	169.00
Ham-X	239.00
FDK Palm 2 Handie with BP/AC	149.00
Cetron, GE 572 B	34.00
GE 61468	9.95
Fig. W	

Fits Kenwood Yaesu

Kenwood Service Manuals

Stock	10.00 ea
Telrex TB5EM	. 425.00
Telrex TB6EM	. 540.00
Telrex Monobanders	. Stock
Adel Nibbling Tool	8.95
Janel QSA5	41.95
Sprague 100MFD/450V Cap	2.00
Rohn Tower 20% c	off deale
Alliance HD73 Rotor	. 109.9
Amphenol Silverplate PL259	1.00
ICOM 255A 2M Synthesized	. 319.00
ICOM 260A 2M SSB/FM/CW	. 429.00
Kenwood TS1805/DFC/SSB	Cal
ICOM IC2AT/TTP/NICAD	. 229.00
New-Icom IC720 w/AC/mike	Ca
Bearcat 220 - \$299.00 3	00-399.0

160 THROUGH 10, INCLUDING WARC **9 BANDS FULLY OPERATING**

Professional Grade HF/SSB Transceiver

100 WATTS ALL BANDS ALL MODES

AGC DYNAMIC RANGE GREATER THAN 100 dB

SELECTIVITY 16 POLE CRYSTAL FILTER 2.7 kHz at - 6dB; 3.78 kHz at - 100 dB

\$1395.00 SUGGESTED LIST CALL FOR QUOTE



MEMORY EYER BREAK-**THROUGH!**



The remarkable AEA Morsematic memory keyer has 35 fantastic features including two AEA designed microcomputers, up to 2,000 character memory, automatic serial number, beacon mode. and automatic morse trainer mode

199.00

Brings you the **Breakthrough!**

713-658-0268

RG8/u

RG8/u

CALL FOR QUOTES

1508 McKINNEY HOUSTON, TEXAS 77010



Courtesy of AMSAT

Any satellite placed into a near-Earth orbit suffers from the cumulative effects of atmospheric drag. The much publicized descent of the Skylab space station was a graphic demonstration of these effects.

The OSCAR satellites are subject to atmospheric drag, of course, and the present period of intense solar activity has accentuated the problem. During this period, our sun has been expelling huge numbers of charged particles, some of which find their way into the Earth's upper atmosphere, increasing the density (and thus the drag) there. It is through this region that the OSCARs must pass. OSCAR 8, in a lower orbit than OSCAR 7, is the more seriously affected of the two.

If the drag factor is not considered when OSCAR calculations are performed, long-range orbital projections will be in error. For example, by the end of 1979, OSCAR 8 was more than 20 minutes ahead of some published schedules. The nature of orbital mechanics is such that extra drag on a satellite causes it to move into a lower orbit, resulting in a shorter orbital period. Thus, the satellite arrives above a given Earthbound location earlier than predicted.

Using data supplied to us by Dr. Thomas A. Clark W3IWI of AM-SAT, the equatorial crossing tables shown here were generated with the aid of a TRS-80TM microcomputer. The tables take into account the effects of atmospheric drag and should be in error by a few seconds at most.

The listed data tells you the time and place that OSCAR 7 and OSCAR 8 cross the equator in an ascending orbit for the first time each day. To calculate successive OSCAR 7 orbits, make a list of the first orbit number and the next twelve orbits for that day. List the time of the first orbit. Each successive orbit is 115 minutes later (two hours less five minutes). The chart gives the longitude of the day's first ascending (northbound) equatorial crossing. Add 29° for each succeeding orbit. When OSCAR is ascending on the other side of the world from you, it will descend over you. To find the equatorial descending longitude, subtract 166° from the ascending longitude. To find the time OSCAR 7 passes the North Pole, add 29 minutes to the time it passes the equator. You should be able to hear OSCAR 7 when it is within 45 degrees of you. The easiest way to determine if OSCAR is above the horizon (and thus within range) at your location is to take a globe and draw a circle with a radius of 2450 miles (4000 kilometers) from your QTH. If OSCAR passes above that circle, you should be able to hear it. If it passes right overhead, you should hear it for about 24 minutes total. OSCAR 7 will pass an imaginary line drawn from San Francisco to Norfolk about 12 minutes after passing the equator. Add about a minute for each 200 miles that you live north of this line. If OSCAR passes 15° east or west of you, add another minute; at 30°, three minutes; at 45°, ten minutes. Mode A: 145.85-.95 MHz uplink, 29.4-29.5 MHz downlink, beacon at 29.502 MHz. Mode B: 432.125-.175 MHz uplink, 145.975-.925 MHz downlink, beacon at 145.972 MHz.

At press time, OSCAR 7 was scheduled to be in Mode A on odd numbered days of the year and in Mode B on even numbered days. Monday is QRP day on OSCAR 7, while Wednesdays are set aside for experiments and are not available for use.

OSCAR 8 calculations are similar to those for OSCAR 7, with some important exceptions. Instead of making 13 orbits each day, OSCAR 8 makes 14 orbits during each 24-hour period. The orbital period of OSCAR 8 is therefore somewhat shorter: 103 minutes.

To calculate successive OSCAR 8 orbits, make a list of the first orbit number (from the OSCAR 8 chart) and the next thirteen orbits for that day. List the time of the first orbit. Each successive orbit is then 103 minutes later. The chart gives the longitude of the day's first ascending equatorial crossing. Add 26° for each succeeding orbit. To find the time OSCAR 8 passes the North Pole, add 26 minutes to the time it crosses the equator. OSCAR 8 will cross the imaginary San Francisco-to-Norfolk line about 11 minutes after crossing the equator. Mode A: 145.85-.95 MHz uplink, 29.4-29.50 MHz downlink, beacon at 29.40 MHz. Mode J: 145.90-146.00 MHz uplink, 435.20-435.10 MHz downlink, beacon on 435.090 MHz.

OSCAR 8 is in Mode A on Mondays and Thursdays, Mode J on Saturdays and Sundays, and both modes simultaneously on Tuesdays and Fridays. As with OSCAR 7, Wednesdays are reserved for experiments.

OSCAR 7 ORBIT	AL INFORMATION I	FOR DECEMBER	OSCAR # OR	BITAL INFORMA	TION FOR DECEMBER	OSCAR 7 0	RBITAL IN	PORMATION P	OR JANUARY	OSCAR 8 08	BITAL IN	FORMATION	FOR JANUARY
ORBIT # D	ATE TIME (GRT)	EQ. CROSSING (DEGREES WEST)	ORBIT #	DATE TIN	E EQ. CROSSING	ORBIT .	DATE	TIME (CMT)	EQ. CROSSING (DEGREES WEST)	ORBIT #	DATE	TIME (GMT)	EQ. CROSSING (DEGREES WEST)

27653	1	2218:49	79.8	13969	1	2813:32	39.6	28842	1	#131:#5	98.7	14482	1	8857143	71.5
27666	2	0113:04	93.4	13983	2	0018:18	8,86	28854	2	0030:23	83.5	14416	2	0102:28	72.7
27678	3	8012:22	78.3	13997	3	8823:84	62.1	28867	3	0124:38	97.1	14438	3	0107:12	73.9
27691		0106:36	51.9	14011	14	0027:50	63.3	28879	4	0023+56	82.0	14444	4	@111:57	75.2
27783	4	0005-54	76.7	34825		8832135	64.5	20092	5	8118-18	95.6	14458	E.	0116+41	76.4
27716	6	20-10-10-10	1.80	14830		8832+21	65.7	26184	*	2217+28	80.4	14472	2	8121.26	77.6
27720	7	0154-23	103.4	74053	14	6042+86	66 0	20117		0111.42	0.4 .0	14496	10	0126.18	70.0
277.43		0053.43	80.3	24057	201	0042100	60.1	20117		8833-88	78.0	14500		8128-65	60.0
22254		00003201	100.1	14007		0040102	1.80	48.1.42	0	0011100	07 4	14588	0	0130133	00.0
27724	3.	0147150	184.3	14581	3	0021138	09.4	28142		8183514	92.4	14014	3	0133133	84.4.4
21100	1.0	8047:14	87+2	14895	10	0056123	70.6	28154	10	0004:32	11.3	14528	10	0240:23	82+4
27779	11	0141:28	100.0	14109	11	0101:09	71.8	28167	11	8058:46	98.9	14541	11	0001:26	57.8
27791	12	8848:46	85.6	14123	12	0105:54	73.0	28180	12	0153:01	104.5	14555	12	0005:40	59.1
27884	13	0135:00	9912	14137	13	0110:39	7.4.2	28192	13	0052:18	89.3	14569	13	0011:25	60.3
27816	34	0034:18	84.0	14151	14	0115:25	75.4	28205	14	0146:33	102.9	14583	14	0016:09	61.5
27829	15	0128:33	97.6	14165	15	0120:10	76.7	28217	15	0045:51	87.7	14597	15	0820:53	62.7
27841	16	0027:51	62.5	14179	16	0124:55	77.9	28230	16	0140:05	101.3	14611	16	0025:37	63.9
27.854	17	0122:05	96.1	14193	17	8129:48	79.1	28242	17	8839:23	86.2	14625	17	0030:21	\$5.1
27866	18	0021:23	00.9	14207	1.6	0134:26	80.3	28255	18	0133:37	99.8	14639	18	0035:05	66.3
27879	19	0115:37	94.5	14221	19	8139:11	81.5	28267	19	8832:55	84.6	14653	19	8839:49	67.5
27891	28	0014:55	79.3	14234	-28	2088:44	56.9	28288	28	0127:09	98.2	14667	28	0044:33	68.8
27904	21	0109:10	92.9	14248	21	8885:29	58.2	28292	23	0026:27	83.0	14681	21	0049:17	79.0
27916	22	0008:28	77.8	14262	22	##10:14	59.4	283#5	22	8128:41	96.6	14695	22	0054:01	71.2
27929	23	#1#2:42	91.4	14276	23	8814:59	60.6	28317	23	0019:59	81.5	14789	23	##58:45	72.4
27941	2.4	8882:00	76.2	14290	24	8819:44	61.8	28330	24	0214:13	95.1	14723	24	#1#3:29	73.6
27954	25	8856:14	89.8	14384	25	8824:29	63.8	28342	25	0011:31	79.9	14737	25	61#8+13	74.8
27967	26	#15#:29	103.4	14318	26	8829:14	64.2	28355	76	0207:45	93.5	14751	25	0112:57	76.8
27979	27	8849+47	88.5	14332	27	0033-59	65.4	28367	27	0007-01	78.4	14765	22	8117+48	77.5
27992	28	8144-81	181.8	14346	28	0038+44	66.7	26388	28	0101-17	01.0	14770	28	#137.24	70 4
28884	24	8843-39	-86.7	14368	29	0843.29	67.9	20300	20	0008-35	75 8	14762	20	0127-02	70.7
28817	30	6137-33	100.3	14374	3.0	8848-11	69.1	20405	24	0854.49	0.0	14087	3.0	0121-51	00.0
28829	31	8836+51	85.1	143.98	- 33	2052+50	78.3	20465	31	8140-84	104 0	14007	31	0136+35	00.7
10013	2.5	0030131	83.1	14300	22	0032130	1010	29470	54	8743184	704.8	14041	31	8130133	86.1



28 73 Magazine • December, 1980



DELUXE 12-BUTTON TOUCHTONE ENCODER KIT utilizing the new ICM 7206 chip. Provides both VISUAL AND AUDIO indications! Comes with its own two tone anodized aluminum cabinet. Measures only 2 3/4 × 3 3/4" Complete with Touch-Tone pad, board, crystal, chip and all necessary components to finish the kit.



PRICED AT......\$14.95

ACCUKEYER - MEMORY OFTION KIT THIS ACCUKEYER MEMORY KIT PRO-VIDES A SIMPLE, LOW COST METHOD OF ADDING MEMORY CAPABILITY TO THE WB4VVF ACCUKEYER. WHILE DESIGNED FOR DIRECT ATTACH-MENT TO THE ABOVE ACCUKEYER, IT CAN ALSO BE ATTACHED TO ANY STANDARD ACCUKEYER BOARD WITH LITTLE DIFFICULTY. \$16.95

ACCUKEYER (KIT) THIS ACCUKEYER IS A REVISED VERSION OF THE VERY POPULAR WB4VVF ACCUKEYER ORIGINALLY DESCRIBED BY JAMES GAR-RETT, IN QST MAGAZINE AND THE 1975 RADIO AMATEURS HANDBOOK. \$16.95

6-DIGIT CLOCK • 12/24 HOUR

COMPLETE KIT CONSISTING OF 2 PC G10 PRE-DRILLED PC BOARDS, 1 CLOCK CHIP, 6 FND 359 READOUTS, 13 TRANSISTORS, 3 CAPS, 9 RESISTORS, 5 DIODES, 3 PUSH-BUTTON SWITCHES, POWER TRANSFORMER AND INSTRUCTIONS.

DON'T BE FOOLED BY PARTIAL KITS WHERE YOU HAVE TO BUY EVERYTHING EXTRA.

PRICED AT\$12.95

CLOCK CASE Available and will fit any one of the above clocks. Regular Price ... \$6.50 But Only \$4.50 when bought with clock

SIX-DIGIT ALARM CLOCK KIT for home, camper, RV, or field-day use. Operates on 12-volt AC or DC, and has its own 60-Hz time base on the board. Complete with all electronic components and two-piece, pre-drilled PC boards. Board size 4" x 3". Complete with speaker and switches. If operated on DC, there is nothing more to buy."

Twelve-volt AC line cord for those who wish to operate the clock from 110-volt AC. \$2.95

SHIPPING INFORMATION

ORDERS OVER \$20.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$20.00 PLEASE INCLUDE ADDITIONAL \$1.50 FOR HANDLING AND MAILING CHARGES. SEND SASE FOR FREE FLYER.



A 60-MINUTE CASSETTE IDENTIFIES THOSE STRANGE SOUNDS: TELEMETRY, MULTI-PLEX JAMMING, SPY TRANSMISSIONS, SWEEPERS, TELETYPE, MANY MORE. EXPLAINS IN EASY-TO-LISTEN TERMS: HOW TO BUY A RECEIVER, PLANNING THE PROPER ANTENNA, COPING WITH INTERFERENCE, WHEN AND HOW TO LISTEN, CHOOSING ACCESSORIES.

> \$39.95 (Plus \$2.00 del.chg.)

\$5.95

(Plus .50

FINALLY, A DIRECTIONAL ANTENNA MADE ESPECIALLY FOR SCANNERS. PICK UP THOSE WEAK DISTANT STATIONS WITH EASE. OPTIMIZED FOR 108 - 174 AND 406 - 512 MHz AIRCRAFT, LAND MOBILE, AND AMATEUR SERVICES. ALSO RECEIVES 30 - 50 MHz (non-directional). MATCHING TRANSFORMER AND MOUNTING HARDWARE INCLUDED.







Model 1528 Drake L7 Continuous Duty 160-15* Meters 2kW Linear Amplifier

Temperature-controlled design for "key-down" operation over a wide frequency range.

2 kW PEP, 1 kW cw, RTTY, SSTV operation—all modes full rated input, continuous duty cycle.

160-15* meter amateur band coverage, plus expanded ranges for any future hf band expansions or additions within FCC rules. These ranges also include increased coverage for MARS, embassy, government, or other such services.

The Drake L7 utilizes a pair of Eimac 3-500 Z triodes for rugged use, and lower replacement cost compared to equivalent ceramic types.



Model 1539

Drake Matching Networks MN7 and MN2700 Models 1538 and 1539

- · Frequency Coverage: 1.8 30 MHz
- Antenna Choice: Matches antennas fed with coax, balanced line (use optional B-1000 Balun), or random wire.
- Antenna/By-Pass Switching: Allows matching unit by-pass regardless of antenna in use, and selects various antennas.
- Extra Harmonic Reduction: Employs "pi-network" low pass filter type circuitry for maximum harmonic rejection.

Accurate built-in rf wattmeter, with forward/reverse readings, is switch selected. Calibrated 300/3000 watt scales.

Temperature controlled two speed fan is a high volume low noise type and offers optimum cooling.

Adjustable exciter agc feedback circuitry permits drive power to be automatically controlled at proper levels to prevent peak clipping and cw overdrive. Front panel control.

By-pass switching is included for straight through, low power operation without having to turn off amplifier.

Bandpass tuned input circuitry for low distortion and 50 ohm input impedance.

Amplifier is comprised of two units-rf deck for desk top and separate power supply.

Operates from 120/240 V-ac, 50/60 Hz primary line voltage.

DRAKE L7 SPECIFICATIONS

 Frequency Coverage*: Ham bands 160 through 15 meters*. Nonamateur frequencies between 6.5 and 21.5 MHz may be covered with some modification of the input circuit. . Plate Power Input: 2000 watts PEP on ssb and a-m. 1000 watts dc on cw, RTTY, and SSTV. . Drive Power Requirements: 100 watts PEP on ssb and 75 watts on cw, a-m, RTTY, and SSTV. . Input Impedance: 50 ohms. (Bandpass tuned input) Output Impedance: Adjustable pi-network matches 50 ohm line with SWR not to exceed 2:1. . Intermodulation Distortion Products: In excess of - 33 dB. · Wattmeter Accuracy: 300 watts forward and reflected, ± (5% of reading + 3 watts). 3000 watts forward, ± (5% of reading + 30 watts). • Power Requirements: 240 volts 50-60 hertz 15 amperes, or 120 volts 50-60 hertz 30 amperes. . Tube Complement: Two of 3-500Z or 8802/3-500Z or 3-400Z. • Dimensions: Amplifier 13.69"W x 6.75"H x 14.25"D (34.8 x 17.1 x 36.2 cm). Power Supply 6.75"W x 7.88"H x 11"D (17 x 20 x 28 cm). • Weight: Amplifier 27 lbs (12.25 kg), Power Supply 42.5 lbs (19.3 kg).

- Built-in Metering: Accurate Rf Wattmeter and VSWR Reading, pushbutton controlled from front panel.
- Input Impedance: 50 ohms resistive.
- Power Capability: MN7—250 watts average continuous duty (0-300 W scale). MN2700—1000 watts average continuous duty (2000 watts PEP). (0-200 or 0-2000 W scale).
- Dimensions: MN7—13.1"W x 4.53"H x 8.5"D excluding knobs and connectors (33.26 x 11.5 x 21.6 cm). MN2700— 13.1"W x4.53"H x 13"D excluding knobs and connectors (33.26 x 11.5 x 33 cm).
- Weight: MN7—10 lbs (4.5 kg). MN2700—11 lbs (5 kg).

Drake MN7 and MN2700 Specifications

 Frequency Coverage: 1.8 to 30 MHz. Band Switch marked for 160, 80, 40, 20, 15, and 10 meter amateur bands; however, frequency coverage between amateur bands is possible by using the nearest band positions with a small reduction in matching capability. . Input Impedance: 50 ohms (resistive). . Load Impedance: 50 ohm coaxial with VSWR of 5:1 or less at any phase angle (3:1 on 10 meters). 75 ohm coaxial at a lower VSWR can be used. • Balanced Feedlines: With the Drake B-1000 accessory balun, which mounts on rear panel, tunes feed point impedances of 40 to 1000 ohms, or 5:1 VSWR referenced to 200 ohms (3:1 on 10 meters). • Long-Wire Antennas: Feed point impedances up to 5:1 VSWR referenced to 50 ohms. Also, 5:1 referenced to 200 ohms. with the Drake B-1000 accessory balun (3:1 on 10 meters). . Meter: Reads VSWR or forward power. . Wattmeter Accuracy: ±5% of reading ± 1% of full scale. • Insertion Loss: 0.5 dB or less on each band after tuning. . Front Panel Controls: Provide for the adjustment of resistive and reactive tuning, antenna switching, band switching, VSWR calibration, and selection of watts or VSWR calibration, and selection of watts or VSWR functions of the meter. • Rear Panel Connectors: The rear panel has four type SO-239 connectors (one for input and 3 for outputs), three screw terminal connections (for long-wire and open-wire feeder systems), and a ground post.

* Export model includes coverage of the 10-meter Ham Band.

Specifications, availability and prices subject to change without notice or obligation.





540 Richard St., Miamisburg, Ohio 45342, USA Phone: (513) 866-2421 • Telex: 288-017

30 73 Magazine • December, 1980

Model 7077 Dynamic Desk Microphone

Audio and level characteristics custom designed to match the transmit audio requirements of the Drake TR7.
Features both VOX and PTT operation without modification.
High Impedance • Includes coil cord and plug wired for direct connection to the Drake TR7.
Style and color provide a beautiful match to the Drake 7-line • Size 4.3"W x 5.8"D x 9.3"H (10.9 x 14.7 x 23.6 cm). Weight 1 lb 7 oz (650 g).

Model 1553 C SP75 Speech Processor

Provides an increase in average power/ readability of a single sideband voice signal during weak signal, high interference conditions. The SP75 is connected between the microphone and microphone input of the ssb transmitter, requiring no modification of existing transmitter or transceiver. A front panel switch allows the processor to be switched in or bypassed. Two additional inputs, such as a tape player or phone patch, may be front panel selected.

ACCESSORIES

C

Model 1535 E CS7 Coax Switch

DRAKE 7-Line Family

B

A

 Switches up to five coax-fed antennas via one main feed line.
 Allows selection of up to five radios at other end of main feed line.

 Minimizes amount of coax needed for multiantenna installation.
 Grounds unused inputs (both local and remote).

DRAKE CS7 SPECIFICATIONS • Maximum Input Power: 2000 watts PEP • Frequency Range: Up to 30 MHz, insertion of Switch changes VSWR no more than 1.05:1. From 30 MHz to 150 MHz, insertion changes VSWR no more than 1.5:1 (both switches). • Operating Temperature Range: - 40 °F. to 150 °F. • Supply Voltage: 120 V-ac or 240 V-ac selectable, 50/60 Hz, 50 watts. • Dimensions & Weight: Console -5.25"H x 6.81"W, 7.06" cabinet depth (13.3 x 17.3 x 17.9 cm); 4.33 lbs (1.96 kg); Remote Antenna Switch-7.13"H x 5.88"W x 4.39"D (18.1 x 15.0 x 11.1 cm). 8.19" (20.8 cm) center to center mounting; 5 lbs (2.27 kg).

Model 1531 B MS7 Matching Speaker



D

WH7 Directional Rf Wattmeter

E

Model 1514

Directional, in-line wattmeter.
 Removable coupler provides remote metering.
 Three calibrated scales (0-20, 0-200, and 0-2000 watts.
 Fourth scale provides direct reading VSWR.

SPECIFICATIONS: • Frequency Coverage:
1.8-30 MHz. • Line Impedance: 50 ohm resistive. • Power Capability: 2000 W
continuous. • Jacks, Removable Coupler: Two SO-239 input and output connectors. • Semiconductors: Two power meter rectifiers.
• Accuracy: ± (5% of reading + 1% of full scale). • VSWR Insertion: Insertion of wattmeter in line changes VSWR no more than
1.05:1. • Shipping Weight: 3 lbs (1.4 kg).
• Dimensions: 5.3"H x 6.9"W x 7.5"D (13.5 x 17.5 x 19 cm).

LA7 Line Amplifier

Rf envelope clipping adjustable between zero and twenty decibels. LED indicates proper audio input level.

Muting circuitry reduces gain during speech pauses, allowing VOX operation with the processor on.

SPECIFICATIONS . Processing Type:

Preclipping audio compression followed by rf envelope clipping at the processor intermediate frequency. . Rf Clipping Range: Adjustable 0 to 20 dB from front panel control. . Input Level (Microphone Input): 3.5 mV minimum for full processing. Gain adjustable to accommodate up to 300 mV maximum. . Input Level (Tape and Patch Inputs): 15 mV minimum for full processing. 30 mV maximum. . Input Impedance (Microphone): 1 megohm. . Input Impedance (Tape and Patch): 50 kilohm. Output Level w/Processing: 0-50 mV adjustable into 50 kilohm load. . Output Impedance: 50 kilohm. . Muting (Microphone Input Only): 10 to 20 dB attenuation during speech pauses. . Frequency Response: 400-6000 Hz@6 dB. • Distortion: Less than 5% T.H.D.@1kHz, 20 dB clipping. . Power: 11-16 V-dc@95 mA. • Size: 7"L x 61/4 "W x 21/4 "H (17.3 x 15.9 x 5.4 cm). • Weight: 1.4 lbs. (.63 kg).

D P75 Phone Patch

Hybrid Phone Patch for use with 7-line or other receiver/transmitter combination. • In/out Switching • Adjustable TX and RX level controls.

Size: 7.5"D x 6.9"W x 4.6"H excluding feet (19 x 17.5 x 11.6 cm).
 Weight: 2.5 lbs (1.13 kg).

"Dry" Dummy Loads —no oil required



Model 1551 Drake DL-1000

 1000 watts for 30 seconds, with derating curve to 5 minutes. Accepts Drake FA7 cooling fan for extended high power operation.
 VSWR of 1.5:1 max. 0-30 MHz
 SO-239 coax connector
 Rubber feet for desk or bench use
 Size 14" x 3.6" (35.6 x 9.1 cm). Weight: 2 lbs (910 g).

Model 1550 Drake DL-300

 300 watts for 30 seconds, with derating curve to 5 minutes.
 Built-in PL-259 coax connector for direct connection to rear of transceiver or transmitter—no jumper coax necessary.
 VSWR of 1.1:1 max. 0-30 MHz 1.5 max 30-160 MHz
 Ideal as bench test device for amateur or commercial hf and vhf gear.

 Small size fits conveniently in any field service tool box. 6.7" x 2.08" (17.0 x 5.3 cm).
 Weight: 11 oz (310 g).

Specifications, availability and prices subject to change without notice or obligation.

R.L. DRAKE COMPANY



19

540 Richard St., Miamisburg, Ohio 45342, USA Phone: (513) 866-2421 • Telex: 288-017

✓ Reader Service—see page 226

Line output, 1 mW nominal into 600 ohm balanced, adjustable by internal pre-set level control.

TV Interference Filters

High Pass Filters for TV Sets

More than 40 dB attenuation at 52 MHz and lower. Protect the TV set from amateur transmitters 6-160 meters.



Model No. 1603 Drake TV-300-HP

For 300 ohm twin lead. New terminals for easy installation.

Model No. 1610 Drake TV-75-HP

For 75 ohm TV coaxial cable; TV type "F" connectors installed.

Low Pass Filters for Transmitters



Four pi sections for sharp cut off above the hf amateur bands and to attenuate transmitter harmonics falling in any TV channel and fm band. 52 ohm. SO-239 connectors built in.

Model No. 1608 Drake TV-3300-LP

1000 watts max. below 30 MHz. Attenuation better than 80 dB above 41 MHz. Helps TV i-f interference, as well as harmonic interference.

Model No. 1605 Drake TV-42-LP

A four section filter designed with 43.2 MHz cutoff and extremely high attenuation in all TV channels for transmitters operating at 30 MHz and lower. Rated 100 watts input.

NEW PRODUCTS

AEA'S MODEL CK-1 ELECTRONIC KEYER

The new AEA Model CK-1 iambic electronic keyer incorporates virtually all of the features of the renowned AEA MorseMatic, with the exception of the trainer and beacon modes. The CK-1 keyer also has two preset speeds for fast recall and a stepped variable speed control for fast contest operation. The speed range is 1- to 99-wpm in one-wpm increments. The unit operates from 12 volts dc (plus or minus 3 volts dc) for maximum DXpedition flexibility. An optional ac adapter is available from AEA.

The keyer offers the contest operator a competitive edge with a flexible automatic serial number generator. The memory has a storage capability of approximately 500 Morse characters. AEA's exclusive soft partitioningTM of the memory means that all of the memory can be allotted to one message or divided up into as many as ten separate

the 500 characters. If you make a mistake loading the message, it can be easily corrected by using exclusive AEA editing. The edit mode can save the CW operator time and frustration, especially in loading a long message. The CK-1 memory can be loaded in the automatic word/ character space load for easy flawless memory loading or in the real-time load mode. In either case, memory load does not initiate until the first character is sent so that there is no undesirable delay in playback. The memory playback can be halted in the middle of a message for manual keying by tapping the paddle and resumed where interrupted, or from the beginning. When loading memory, a significant drop in sidetone frequency signals a "memory full" condition.

The CK-1 keyer features a serial number generator that was designed after analyzing suggestions from many successful contest winners. The serial number automatically increments each time a mes-



Jameco's desk-top enclosures.

sage preprogrammed with a serial number is sent. The serial number can even be repeated several times (in another message) if the exchange was not made the first time. The serial number is not restricted to the same position in a message. It can be placed anywhere within a message and as many times as desired, and it does not increment until a message is repeated. Any new serial number may be selected in less than three seconds. The serial number can be loaded with as little as one character space between it and the preceding character. Like all other keyers in the AEA computerized electronic keyer line, the CK-1 features independent dot and dash ratio adjustment (full weighting). Also, dot and dash memories can be independently turned on or off. For the operator who enjoys operating with a bug, the CK-1 features semi-automatic operation. In the semi-auto bug mode, an operator can even load the message memories. The CK-1 will key any modern transceiver and features a single output jack (RCA phono type) for keying either plus or minus keyjack voltages to ground. The CK-1 also features an automatic tune mode which can be halted by tapping any keypad button, or the paddle.

"shake out" component failures. Mating power and paddle connectors are provided.

The CK-1 is easy to learn and easy to use, providing the operator the maximum amount of enjoyment with CW.

For further information, contact Advanced Electronic Applications, Inc., PO Box 2160, Bldg. O&P, 2006-196th SW, Lynnwood WA 98036; (206)-775-7373/524-7374.

NEW DESK-TOP ELECTRONIC ENCLOSURES

Jameco Electronics has an-

messages of varying length as long as the total is no more than



AEA's CK-1 electronic keyer.

The CK-1 is packaged in a high-impact plastic case, ideal for placing next to the keyer paddle without wasting valuable operating desk space. AEA engineering has provided maximum rf protection to avoid frustrating false keying. All ICs are socketed and, like all AEA products, each unit is fully tested and burned in at 50° C to nounced a new Designer Series of desk-top enclosures to accommodate electronic equipment. These stylish enclosures are designed to blend and complement today's modern computer equipment and can be used in both industry and home.

The unique four-piece construction of the series enables easy access for servicing while providing strong protection. The end pieces are precision-molded high-strength epoxy with an internal slot (all around) to accept both top and bottom panels. The aluminum panels (.080" thick) are fastened to ¼"thick mounting tabs inside the end pieces to provide maximum rigidity. For service, the rear/bottom panel slides backward on slotted guide tracks.

The aluminum panels are coated with an alodine type 1200 finish for best paint adhesion. The molded end pieces are mocha brown, matte finish, but can be painted to match any color scheme.

The Designer Series enclosures are available in three

Continued on page 186

Yesterday you could admire all-band digital tuning in a short wave receiver.* Today you can afford it.



Tune in the Panasonic Command Series[™] top-of-the-line RF-4900. Everything you want in short wave at a surprisingly affordable price. Like fluorescent all-band readout with a five-digit

frequency display. It's so accurate (within 1 kHz, to be exact), you can tune in a station even before it's broadcasting. And with the RF-4900's eight short wave bands, you can choose any broadcast between 1.6 and 31 MHz. That's all short wave bands. That's Panasonic.



And what you see on the

outside is just a small part of what Panasonic gives you inside. There's a double superheterodyne system for sharp reception stability and selectivity as well as image rejection. An input-tuned RF amplifier with a 3-ganged variable tuning capacitor for excellent sensitivity and frequency linearity. Ladder-type ceramic filters to reduce frequency interference. And even an antenna trimmer that changes the front-end capacitance for reception of weak broadcast signals.

To help you control all that sophisticated circuitry, Panasonic's RF-4900 gives you all these sophisticated controls. Like an all-gear-drive tuning control to prevent "backlash." Separate wide/narrow bandwidth selectors for crisp reception even in crowded conditions. Adjustable calibration for easy tuning to exact frequencies. A BFO pitch

> control. RF-gain control for improved reception in strong signal areas. An ANL switch. Even separate bass and treble controls.

And if all that short wave isn't enough. There's more. Like SSB (single sideband) amateur radio. All 40 CB channels. Ship to shore. Even Morse communications. AC/DC operation. And with

Panasonic's 4" full-range speaker, the big sound of AM and FM will really sound big. There's also the Panasonic RF-2900. It has most of the features of the RF-4900, but it costs a lot less.

The Command Series from Panasonic. If you had short wave receivers as good. You wouldn't still be reading. You'd be listening.

*Short wave reception will vary with antenna, weather conditions, operator's geographic location and other factors. An outside antenna may be required for maximum short wave reception.

Panasonic. * 380 just slightly ahead of our time.

PRODUCT

exciting new ideas from the world's leading manufacturer of amateur radio accessories

NEW MFJ/BENCHER Keyer-Paddle Combo — "The Pacesetter"



The best of all CW worlds - a deluxe MFJ keyer in a compact configuration that fits right on the BENCHER iambic paddle! And you can buy the combination or just the keyer to fit on your BENCHER. New MFJ keyer - small in size, big in. features. Curtis 8044 IC, adjustable weight and tone, front panel volume and speed controls (8-50 wpm), built-in dot-dash memories, speaker, sidetone, and pushbutton selection of semi-automatic/tune or automatic modes. Ultra-reliable solid-state keying: gridblock, cathode and solid-state transmitters (-300 V, 10 mA max; +300 V, 100 mA max). Fully shielded. Uses 9 V battery or optional AC adapter (\$7.95 + \$2) Beautiful functional engineering. The keyer mounts on the paddle base to form a small (41/8Wx25/8H x 51/2"L) attractive combination that's a pleasure to look at and use. The BENCHER paddle is a best seller. Fully adjustable; gold-plated silver contacts; lucite paddles; chrome plated brass; heavy steel base with non-skid feet.

NEW MFJ 4 & 8-Band Mobile Shortwave Converters



pleasure.

"World Explorer I' (MFJ-304) offers com- with your automotive receiver. plete 19, 25, 31 and 49 meter coverage (the capabilities at various times of the day and year). Hear countries from Europe, Africa, Middle East, Asia, the Islands, North and South America. The 8-band "World Explorer II" (MFJ-308 adds 13, 16, 41, and 60 meter bands) for even greater listening Listen to the world on the road. Get the variety.

Another MFJ "first," these low cost measures just 51/4W x 11/4H x 4"D to fit mobile SWL converters provide new excite- anywhere in your vehicle (the 8-band version ment and variety for your driving/listening is just 1" wider and 1" deeper). Two dual-gate MOSFETS give these converters excellent Two models to choose from. The 4-band sensitivity and selectivity when combined

MFJ-308

FJ WORLD EXPLORER 11

Easy to use, easy to install. Push a converter most popular HF bands due to their distance button to choose the band, tune in stations with your regular car radio. To install, just plug the car antenna into the converter and insert the converter cable into your car radio antenna jack; connect the power lead to 12 VDC.

new MFJ mobile SWL converters - "World

Compact and sensitive. The 4-band model Explorers I & II."

NEW MFJ Active CW/SSB/Notch Filters



Two new super-selective filters. The new MFJ-722 "Optimizer" offers razor sharp, but less notch; MFJ-720, \$39.95, like 723 no-ring CW filtering with switch-selectable but less notch. bandwidths (80, 110, 150, 180 Hz centered Versatile, all models plug into the phone on 750 Hz), steep-skirted SSB filtering, and a jack, provide 2 watts for speaker or can be 300-3000 Hz tunable 70 dB notch filter.

is optimized for reduced sideband splatter and less QRM (375 Hz highpass cutoff plus selectable lowpass cutoffs at 2.5, 2.0, and 1.5 kHz, 36 dB/octave rolloff). Size: 5x2x6". New model MFJ-723 is similar to the 722 but is for CW only, has a 60 dB notch tunable from 300-1200 Hz, and measures 2x4x6". Other models: MFJ-721. \$59.95, like 722 used with headphones. All require 9-18 The 8-pole (4-stage) active IC filter gives VDC, 300 mA max (or 110 VAC with

CW performance no tunable filter can match. optional AC adapter at \$7.95 + \$2). (80 Hz bandwidth gives -60 dB response Enjoy pleasant listening and improved one octave from center and up to 15 dB noise readability with one of these new MFJ reduction). The 8-pole SSB audio bandwidth filters.

NEW MFJ "Dry" 300W & 1KW Dummy Loads



in perforated metal housings with SO-239 21/2x21/2x7"; MFJ-262 (1kW) is 3x3x13".

connectors; both rated to full load for 30 seconds; de-rating curves to 5 minutes included. Just right for tests and fast tune up. Low VSWR. 300W: 1.1:1 max to 30 MHz, 1.5:1 max. 30-160 MHz. 1 kW: 1.5:1 max to Air Cooled, non-inductive 50-ohm resistors 30 MHz. MFJ-260 (300W) is just

NEW MFJ Shortwave Accessories



MFJ-1040 Receiver Preselector

Boosts weak signals, rejects out of band signals, reduces images. Covers 1.8-54 MHz with up to 20 dB gain from low noise MOSFET circuitry. Works with 2 antennas and 2 receivers (even XCVRS to 350W input).

overload. Also includes auto-bypass, delay or 110 VAC, with optional AC adapter at control, PTT jack. Operates on 9 V battery, \$7.95 + \$2. 5x2x6".

9-18 VDC, or 110 VAC with optional AC adapter, \$7.95 +\$2.

Model MFJ-1045, \$69.95, is the same less attenuator, bypass, delay, PTT, 1 antenna & I receiver.

MFJ-1020 Indoor Active Antenna

"World grabber," rivaling or exceeding reception of outside long wires.

Unique tuned circuitry with amplification minimizes intermod distortion, improves selectivity, reduces noise outside the tuned band, even functions as a preselector with an external antenna. Covers 0,3-30 MHz in 5 bands. Telescoping ant.; tune, band, gain, Built-in 20 dB attenuator prevents receiver on-off-bypass; Uses 9 V battery, 9-18 VDC,



For tech. info., order or repair status, or calls outside continental U.S. and inside Miss., call 601-323-5869.

- All MFJ products unconditionally guaranteed for one year (except as noted)
- Products ordered from MFJ are returnable within 30 days for full refund (less shipping)
- Add shipping & handling charges in amounts shown in parentheses

Write for FREE catalog, over 60 products



Box 494; Mississippi State, MS 39762

300 W Versa Tuners—Versatile Bargains





MFJ 941C Versa Tuner II

SWR + dual range wattmeter, 300 & 30 watts full scale, forward & reflected power. Sensitive meter measures SWR down to 5 W output.

6-position antenna switch selects 2 coax lines, direct or through tuner, random/ balanced line, or bypass for dummy load.

12-position airwound inductor, built-in balun.

Matches everything from 160-10M, dipoles, vees, randoms, verticals, mobile whips, beams.

Easy to use anywhere. Coax conn., binding posts, size 8x2x6" in eggshell white, walnut-grained sides. Mobile bracket, \$3.





MFJ 949B Versa Tuner II

Matches everything from 1.8-30MHz, coax, randoms, bala ced lines, up to 300 W output, solid-state or tubes.

Tunes out SWR on dipoles, vees, long wires, verticals, whips, beams, quads. Built-in 4:1 balun; 200w, 50-ohm dummy load; SWR meter and 2-range wattmeter

(300w & 30w).

6-position antenna switch, 12-position air-wound inductor; coax connectors, binding posts, black and beige case 10x3x7". 4 Other 300W Models: MFJ-940, \$79.95, (+\$4), like 941C less balun. MFJ-945, \$79.95, (+\$4) like 941C less ant. switch. MFJ-944, \$79.95, (+\$4) like 945, less SWR/Wattmeter MFJ-943, \$69.95, (+\$4) like 944, less ant. switch.

World leader in Antenna Tuner/ 15 Models to choose from

Other MFJ Shack Favorites



NEW 12/24 Hour Digital Clock/ID Timer Switch from 12 hr. to GMT, to "seconds" readout, ID timer or elapsed timer. WWV sync, solid-state, blue 0.6" digits, reg. alarm +indicators. 110 VAC, 60 Hz, 6x2x3".



MFJ Grandmaster Memory Keyer has up to twelve 25 ch. messages plus 100, 75, 50 or 25 ch. messages (4096 bits) that repeat continuously or in adjustable pauses (to 2 min.); full controls; 8-50wpm; solid state keying; 12-15 VDC or 110VAC with adapter (\$7.95 + \$2).

200 W Economy Tuners do the job for less





Works with any transceiver, solid-state or tube type.

Increases antenna bandwidth to operate all bands. SO-239 + binding post; 5x2x6". 2 OTHER 200W MODELS:

MFJ-901, \$54.95, (+\$4) like 900 but includes 4:1 balun for use with balanced lines.

MFJ-900 — improved but still low cost. Matches coax, random wires 1.8-30 MHz. Handles up to 200 watts output; efficient airwound inductor gives more watts out.

MFJ-16010, \$34.95, (+\$4) for random wires only. Great for apartment, motel, camping, operation. Tunes 1.8-30 MHz.

1.5 KW Versa Tuners III — low cost power handlers

MFJ 962 VERSA Tuner III

Run up to 1.5 KW PEP, match any feed line from 1.8-30 MHz.

Built-in SWR/Wattmeter has 2000 and 200 watt ranges, forward and reflected. 6-position antenna switch handles 2 coax lines, direct or through tuner, plus wire and balanced lines.

Built-in 4:1 ferrite balun; 250 pf 6 kV capacitors; 12 pos. inductor; ceramic switches; black cabinet and panel.



ANOTHER 1.5 KW MODEL MFJ 961, \$179.95, (+\$10) similar but less the SWR/Wattmeter.



MFJ Dual Tunable SSB/CW Filter; primary filter has peak, notch, lowpass and highpass; aux. filter notches to 70 dB or peaks to 40 Hz; both tune 300-3000 Hz with bandwidth from 40 Hz to flat; constant output; noise limiter; 2 inputs; 9-18 VDC 300 mA; or 110VAC with adapter (\$7.95 +\$2) 10x2x6".

3 KW Deluxe Antenna Tuners — MFJ's best



MFJ-984 \$29995 (+\$10)

MFJ 984 Versa Tuner IV

Up to 3 kW PEP and it matches any feedline, 1.8-30 MHz, coax, balanced or random.

Exclusive 10 amp RF ammeter assures maximum power at minimum SWR.

Separate SWR/Wattmeter, forward and reflected, with 2000 and 200 watt ranges. 18-position dual inductor, ceramic switch. 7-position antenna switch handles 3 coax lines through tuner and 1 coax through or direct to antenna, random wire, balanced line, and dummy load.

Built-in 200 watt, 50 ohm dummy load. Built-in 4:1 ferrite balun; 250 pf 6 kV capacitors; 5x14x14" black & aluminum. Compare this MFJ deluxe 3 kW tuner with any! You'll agree MFJ gives you more.

3 MORE 3 KW MODELS

MFJ 981, \$199.95, (+\$10) similar to 984 but less the 7-position antenna switch and 10 amp. RF ammeter. MFJ 982, \$199.95, (+\$10) similar to 984 but less 10 amp. RF ammeter and dual range SWR/Wattmeter. MFJ-980, \$169.95, (+\$10) similar to 984 but less antenna switch, RF ammeter and SWR/Wattmeter.



For tech. info., order or repair status, or calls outside continental U.S. and inside Miss., call 601-323-5869.

- All MFJ products unconditionally guaranteed for one year (except as noted)
- Products ordered from MFJ are returnable within 30 days for full refund (less shipping)
- Add shipping & handling charges in amounts shown in parentheses

Write for FREE catalog, over 60 products



Who Really Invented Radio? — the twisted tale of Nathan B. Stubblefield

Larry Kahaner WB2NEL 73 Associate Editor decided to buy the \$3-aday collision insurance for my Avis rent-a-car. It might be that kind of assignment.

When they send you to

unravel the twisted tale of Nathan B. Stubblefield who Murray, Kentucky, residents insist invented radio while Marconi was just a lad—you're bound to run

into trouble.

As I neared town, I first heard it on the AM radio. The country-western station played, appropriately enough, "Stand By Your



Photo A. Family and friends gathered (date unknown) at the home of Nathan B. Stubblefield on North 16th Street, Murray, Kentucky. From left, Sam Stubblefield, the black man, and then, identified by numbers, (1) Mr. John P. McElrath; (2) Mrs. John P. McElrath; (3) O. T. Hale; (4) John H. Keys; (5) Mrs. John H. Keys; (6) James M. Cole; (7) Solon Higgins; (8) Mrs. Solon Higgins; (9) O. J. Jennings; (10) Mrs. Ella Hale Woodruff; and then, (1) Pattie Stubblefield; (2) Helen Gould Stubblefield; (3) Oliver Stubblefield; (4) Victoria Stubblefield; (5) Mrs. Hattie Keys Beale; (6) Bernard Stubblefield; (7) Isaac W. Keys; (8) James H. Coleman; (9) Abe Thompson; (10) Ben B. Keys; (11) George Gatlin; (12) Tip Wilcox; (13) Nathan B. Stubblefield, and (14) Mrs. Nathan B. Stubblefield. (Photo courtesy of Murray State University.)

36 73 Magazine • December, 1980




Man," and its call letters were WNBS: Nathan B. Stubblefield. These folks were serious.

When I arrived in Murray and called the motel, I saw it in the phone book. Right there on page III was a photo of Nathan B. standing in the woods, head cocked to one side, holding the wireless device to his ear. The text called him the inventor of the radio. to halt the controversy and contradictions surrounding this eccentric genius?

It was frustrating enough to make me aim my silver Chevette for the nearest telephone pole and take advantage of that \$3-a-day coverage.



Photo C. Ronnie Outland, 22, lives next to the private cemetery where Stubblefield is buried. "Until recent years the grave was not kept up. There were weeds all around and I used to play here when I was younger. There was a big controversy about whether he invented radio. Now they think he did."



Add to that the granite monument in front of his homesite and the state highway market pinpointing his birthplace, and there was little doubt left.

Murrayites meant business.

Who was that man with the bowler hat and handlebar moustache? And why, if he invented radio, has he been largely ignored outside of Murray? And why, if he had willing financial backers for his invention, did he die a pauper, found locked in his cabin outside of Murray where a pet cat seeking moisture had licked out his dried eyes? And why was it that the hundreds of articles written about Stubblefield, a PhD thesis, and a play about his work failed

Instead, I headed for Murray State University where Dr. Keith Heim, head of special collections, had gathered a respectable file of information. Unfortunately, most of it was secondary source material.

In the journalism biz, information is divided into primary and secondary sources. Primary sources are best because they include government documents, photographs, taped and transcribed interviews with people who witnessed an event, and so on. Secondary sources include magazine, newspaper, and other pieces written about an event. They are not as reliable as primary sources because they are secondhand information. Primary sources are the writers' mother lode.

MSU's Stubblefield files contained materials (even from highly touted publications) that contradicted

Photo D. Gravestone in Photo C located behind the Watson home, Route 8, about a mile north of Murray.

each other. I saw differences in simple items such as names, dates, spellings, and attribution. Even Stubblefield's middle name was argued. Smart money is on Beverly, but some pieces list it as Bowman (his mother's maiden name) or Bedford. Each additional article I read only muddled the issue.

In addition, it appeared that much of what has been written about Stubblefield was based on the research of two prominent Murray citizens who are less than unbiased about the role of the farmer/inventor in radio's early days.

It was not an auspicious beginning.

Some things are certain, however. Few disagree that Stubblefield was born in 1860 in Murray, the son of Victoria and William Stubblefield. He was a loner and had few friends besides Duncan Holt, a boyhood chum.

As they grew up, they became fascinated by the work of Nikola Tesla and Heinrich Rudolf Hertz. They read all they could about the burgeoning interest in this new concept of electrical waves and com-

UNITED STATES PATENT OFFICE.

NATHAN 8. STUBBLEFIELD, OF MURRAY, KENTUCKY, ASSIGNOR OF TWELVE AND ONE-HALF ONE-HUNDREDTRS TO CONN LINN, FIVE ONE-HUNDREDTRS TO R. DOWNS, FIVE ONE-HUNDREDTHS TO B. F. SCHROADER, FIVE ONE-RUNDREDTHS TO GEDRGE C. McLARIN, FIVE ONE-HUNDREDTHS TO JOHN F MCKLRATH, TWO AND ONE HALF ONE-HUNDREDTHS TO JEFF D. BOULETT, AND ONE-TWENTIETH TO SAMUEL E. BYNUM, ALL OF MURRAY, KENTUCKY.

WIRELESS TELEPHONE.

No. 887,257.

Specification of Letters Patent. Patented May 12, 1908.

Application filed April 5, 1907. Serial No. 588,544.

To all whom it may concern:

FIELD, & citizen of the United States, resulting at Murray, in the county of Calloway and

a State of Kentucky, have invented a new and useful Wireless Telephone, of which the following is a specification.

The present invention relates to means for electrically transmitting signals from one 10 point to another without the use of connect-

ing wires, and more particularly compre-hending means for securing telephonic communication between moving vehicles and way stations.

15 The principal object of the invention is to provide simple and practical means of a novel nature whereby clear and audible communication can be established, said means being simple and of a character that will per-20 mit certain of the station mechanisms to be

small and compact. In the accompanying drawings --- Figure 1

is a perspective view, showing means for es- An outfit similar to the above, is located on

in which is placed a conducting wire com-Be it known that I. NATHAN B. STURBLE- prising a plurality of convolutions 13, each of which is insulated from the other. The terminals 14 of this coil extend to a suitable \$5 way-station, and at the station is located a powerful source of electrical energy 15, to which is connected by a suitable wire 16 an electrically operated transmitter 17. The battery or other source of electricity has a so connection 18 with one of the leads 14. A receiver 19 of the ordinary type has a con-nection with the same lead 14, to which the battery is connected, and both the receiver and transmitter have connections 21 with 65 the contacts of a switch 22. This switch has suitable means, as for instance, a spring 23, which normally maintains the receiver in circuit with the coil 11, as will be evident by reference to Fig. 1, but if the switch is 70 thrown to break the circuit, it will then cut in the source of electrical energy 15 and the transmitter 17.

tablishing communication between a vessel | the vehicle or boat 9, but the coil 24 thereof, 75 25 and a shore station. Fig. 2 is a diagrammatic view of the mechaniam mounted on the boat. Fig. 3 is a cross sectional view on mounted on the boat, consists of a transan enlarged scale of the shore coil. Fig. 4 is mitter 25, and a battery or other source of

30 system for establishing communication between road vehicles and a way-station, the latter being illustrated diagrammatically Fig. 5 is a detail view of a vehicle equipped with one of the instruments, which is shown

35 diagrammatically. Fig. 6 is a perspective view showing the system applied to a railway for establishing communication between a moving train and a way-station. Fig. 7 is a sectional view through a car abox-40 ing in diagram the car mechanism illustrated

in Fig. 6.

Similar reference numerals designate corresponding parts in all the figures of the drawings.

Referring to the embodiment illustrated in 45 Figs. 1, 2 and 3, a water-way 8 is disclosed, upon which a vessel 9 operates. Surrounding the path of travel of the vessel, and pref- therefore the operator at the shore-station

in Fig. 3, consists of an outer casing 12, with- | ing through the coil of great magnitude 11,

23

887,887

will be induced in the coil 24, and the speech | construction, operation, and many advanor other sounds will thus be transmitted to | tages of the herein described invention will the operator on the boat. By reversing the be apparent to those skilled in the art, with-arrangement, speech may be transmitted out further description, and it will be underfrom the boat to the shore station.

shown in Fig. 2, is much smaller. As further illustrated in said figure, the mechanism a perspective view of a road-way, showing a electrical energy 26 electrically connected, as so shown at 27 and having a connection 28 with one of the leads of the coil. The receiver 29. also has a connection 30 with said lead. A switch 31 is connected to the other lead, and is normally held in a position by a spring 32 88 to maintain a closed circuit through the receiver 29 and the coil, though it may be moved to cut out said receiver and close the circuit through the coil, the source of electrical energy and the transmitter.

In this system, if it is desired to transmit from one station, as for instance, the shorestation, the switch 22 is moved downwardly to cut out the receiver and throw in the transnuitter and source of electrical energy, while 95 the operator upon the boat or vehicle leaving the mechanism in the condition shown in Fig. 2, holds the receiver 29 to his ear. If scably elevated on poles 10, is a coil 11 of uses the transmitter in the ordinary manner, 100 50 considerable magnitude. This coil, as shown a varying current corresponding to that pass-

stood that various changes in the size, shape, 70



- 32 Fig.3

munication. They spent hours reading magazines, Scientific American being a favorite.

Stubblefield and his wife had several children, but only their son Bernard took a fancy to his father's tinkering, and he later became a trusted cohort.

Another man, Rainey T. Wells, who went on to found Murray State Teachers College, figured heavily



Photo E. Monument erected by L. J. Hortin and others to mark the home (since torn down) of Stubblefield. The massive stone was established at the edge of the Murray State University campus in the 1930s.

in the inventor's life and was allegedly present when Stubblefield demonstrated his wireless invention in 1892. Before that, though, Stubblefield supposedly told Holt of his discovery in 1885. However, it was not until January 1, 1902, that he gave the first documented public demonstration of his device in Murray's town square.

The instruments he and his son exhibited by the courthouse consisted of a transmitter and receiver-200 feet apart-and metal rods thrust into the ground connected by wire to both devices. Coils spread all over the walkway.

In an interview with a St. Louis Post-Dispatch reporter ten days after the demonstration, Stubblefield was quoted as saying: "I had been working on this ten or twelve years before I heard

of Marconi's efforts (Marconi successfully sent radiotelegraphy in 1896, but not voice) or the efforts of others to solve the problem of transmission of messages through space without wires. I have solved the problem of telephoning without wires through the earth as Signor Marconi has of sending signals through space. But I can also telephone without wires through space as well as earth because my medium is everywhere."

He never said what that medium was.

Stubblefield demonstrated his wireless voice device on his farm to the reporter. Bernard stayed in the house while his father and the reporter walked to a cornfield about 500 yards away.

The reporter wrote: "The transmitting apparatus is concealed in a box. Two

The use of coils for both stations, each coil | consisting of a plurality of convolutions has been found by experience to be of the utmost value, and furthermore experience has dem-

- 10 onstrated that the employment of coils of different magnitudes is of great importance, for it has been found that while two small coils can be used to transmit but a short distance, if one large coil of the character set forth is emi-
- 15 ployed, the other may be very small, and speech or sounds can be transmitted comparatively great distances from one to the other. These sounds are clearly audible.
- The structure disclosed in Figs. 4 and 5 is so of the same general character. A road-way 32 is disclosed surrounded by a coil 33 of great magnitude that is supported on suit-able poles 34. The way-station 35 consists of a transmitter 36, a source of electrical en-
- af ergy 37 connected thereto, a receiver 38, and a switch 39, whereby the receiver or the transmitter and source of electrical energy can be thrown into circuit with the coil 33 The vehicles 40, which operate on the road-
- so way, are provided with smaller coils 41 and instruments consisting of receivers 42, transmitters 43, sources of electrical energy 44 and switches 45 all arranged in the manner gready described. In a system of this kind,
- as it will be evident that the occupant of one vehicle may telephone to the home or waystation, and the message can be transmitted to another vehicle. Thus it will be evident that communication can be established be-40 tween two moving vehicles or between a way-
- station and any vehicle desired which is

proportion, and minor details of construction, may be resorted to without departing from the spirit or sacrificing any of the advantages of the invention.

Having thus fully described my invention, 75 what I claim as new, and desire to secure by Letters Patent, is:-

1. In a system of the character described, the combination with a vehicle, of a comparatively small coil of conducting material so mounted thereon, electrical transmitting and receiving mechanism including a source of electrical energy connected to the small coil and carried by the vehicle, a stationary aerial coil of much greater magnitude than the as small coil having its opposite stretches or sides extending along the opposite sides of the path of travel of the vehicle and elevated above the same and above the vehicle coil, and electrical transmitting and receiving 90 mechanism connected to the greater coil and including a source of heavy electrical current. 2. In a system of the character described, the combination with a vehicle, of a coil of conducting material mounted thereon, elec- 95 trical transmitting mechanism, a source of electrical energy connected thereto, receiving mechanism, means for connecting either the transmitting mechanism and source of electrical energy or the receiving mechanism 100 to the coil, a stationary coil of greater magnitude surrounding the path of travel of the vehicle and comprising a plurality of convolutions of conducting material, the different convolutions being insulated one from the 105 other, means for supporting the coil in an within the range of the home-or way-station. elevated position, electrical transmitting

The system is also capable of use in connec- | mechanism, a source of great electrical ention with railways, and in Figs. 6 and 7, such

45 a system is disclosed in connection therewith. A comparatively great coil 46 is sup-ported on opposite sides of the railway 47 by poles 48 and a station 49 has a receiver 50 and a transmitter 51, a source of electrical energy

50 52 and a switch 53, the last mentioned being employed for throwing either the receiver or the transmitter and source of electrical energy into closed circuit with the coil 46. One or more cars of a railway train is equipped 55 with an outfit consisting of a coil 54, a receiver

55, a transmitter 56, a source of electrical energy 57, and a switch 58 for throwing either the receiver or the transmitter and source of electrical energy into circuit with so the coil 54. It will be evident that the operation of these two last described systems are substantially the same as that first set forth, and no extended description thereof is believed to be necessary.

ergy connected to said transmitting mechanism, electrical receiving mechanism, and 110 means for electrically connecting either the transmitting mechanism and source of electrical energy or the receiving mechanism to the said coil of greater magnitude.

3. Means for communicating between a 115 plurality of stations which consists of an aerial electrical coil of great magnitude, means for supporting the said coil, a station electrically connected to the great coil and comprising transmitting and receiving mech- 120 aniam that includes a source of heavy electrical energy, and a plurality of other separate stations simultaneously in coacting relation with the aerial coil, each of said latter stations comprising a coil of conducting ma- 125 terial spaced from but in coacting relation with said great coil and below the same, and transmitting and receiving mechanism connected to said other coil and including a 130

From the foregoing, it is thought that the | source of electrical energy.

887,357

4. Means for communicating between a and transmitting and receiving mechanism plurality of stations which consists of an mounted on each vehicle and including a aerial coil of conducting material of great 'source of electrical energy, magnitude, transmitting and receiving merh-5 anism connected to said aerial coil and in- as my own, I have hereto affixed my signa- 15 cluding a source of heavy electrical energy, ture in the presence of two witnesses, a plurality of vehicles movable between the NATHAN B STUBBLEFIELD. a plurality of vehicles movable between the opposite sides or stretches of the great coil, coils carried by said vehicles and disposed to within the field of action of the actial coil,

a

In testimony, that I claim the foregoing

Witness

J. P. MCELBATH. J. H. COLEMAN.



Fig.6.





wires of the thickness of a lead pencil coil from its corners and disappear through the walls of the room and enter the ground outside. On top of the box is an ordinary telephone transmitter and a telephone switch. This is the machine through which the voice of the sender is passed into the ground to be transmitted by the Earth's electrical waves to the ear of the person who has an instrument capable of receiving and reproducing it.

"We went into the cornfield back of the house. After walking five hundred yards, we came to the experimental station the inventor has used for several months. It is a dry goods box fastened to the top of a stump. A roof to shed the rain has been placed on top of it; one side is hinged for a door, and the wires con-

nected with the ground on both sides run into it and are attached to a pair of telephone receivers. The box was built as a shelter from the weather and as a protection to the receivers. I took a seat in the box and Mr. Stubblefield shouted 'hello' to the house. This was a signal to his son to begin sending messages. I placed the receiver to my ear and listened. Presently, there came with extraordinary distinctness several spasmodic buzzings and then a voice which said: 'Hello, can you hear me? Now I will count to ten. One-two-three-four-five-sixseven-eight-nine-ten. Did you hear that? Now I will whisper.""

The demonstration continued with the reporter and Stubblefield walking about a mile from the house, the reporter placing

the rods anywhere he wished and hearing Bernard talk as clearly as when they were 500 yards away.

The reporter quoted Stubblefield: "The earth, the air, the water, all the universe as we know it is permeated with the remarkable fluid which we call

electricity, the most wonderful of God's gifts to the world and capable of the most inestimable benefits when it is mastered by man. For years I have been trying to make the bare earth do the work of the wires. I know now I have conquered it."



Photo F. The back of the monument in Photo E.

73 Magazine • December, 1980 39



Photo G. This sign, erected by the state of Kentucky, marks Stubblefield's birthplace. Ironically, it is almost directly opposite the tower of radio station WNBS.

Stubblefield claimed his invention would work for any distance. He also said that eventually he would invent a tuning apparatus so that many conversations could go on at the same time without interference. And, he said it wasn't necessary to use the ground rods.

The father and son team demonstrated the wireless device in Philadelphia, New York, and Washington, D.C. Newspapers and magazines documented the events and Stubblefield's fame grew. The March 20, 1902, experiment was particularly unique in that Stubblefield transmitted from the ship Bartholdi on the Potomac River, and it was billed as the "First Marine Wireless Telephone Demonstration." He transmitted about ³/₄ of a mile. During all his demonstrations, Stubblefield employed what he called "an earth battery." Although no one knows for sure what it was, Stubblefield claimed the cell, which he placed in the ground, converted the earth's natural current into electricity. That, in turn, transmitted his voice.

(Stubblefield received patent #600,457, March 8, 1898, for a "primary battery" consisting of a bare iron wire and insulated copper wire wound helically on an iron core. The patent claimed this construction increased the output of the couple, using water as an electrolyte. A couple is two dissimilar metals touching. He proposed placing the battery in moist earth, but it was never proven to be the one used in his voice transmission experiments, although it probably was.)

bute the poor performance to the hard, dry bedrock in the area.

Around this time, Stubblefield became quite well known. Scientific American printed an article about his work, and a coterie of sharp financiers took notice. They saw his system as a moneymaker. A group of New York businessmen formed The Wireless Telephone Company of America to promote the still unpatented device. Several Murray men owned stock. But, for some reason, Stubblefield shied away from the operation after it got underway. It's rumored that he turned down a half million dollars for his invention.

He finally applied for a patent on April 5, 1907, and received it May 12, 1908. He also obtained foreign patents.

Then, for some unknown reason, Stubblefield retreated to his home, disillusioned, distant, and despondent.

Some say his invention

wrote: "...he had been dead for some time. I wouldn't know, but he was pretty stiff and all. Rigor mortis has set in. That cat had licked out his entire eyeball sockets. That's what the cat was doing."

One question still remains amid all the conjecture, weird tales, and questionable articles. Did Nathan B. Stubblefield invent radio? Are the people of Murray correct; did hometown boy make good?

It all depends on how you look at it and who you ask.

L. J. Hortin, one-time chairman of the Murray State University journalism school, spent 50 years studying Stubblefield. He has written hundreds of articles about the man and his work and is responsible for raising most of the money for a monument at Murray State University honoring Stubblefield.

But, like Stubblefield, Hortin appears distant and bitter about the whole affair, and although he claims to possess documents, affidavits, and photos attesting to Stubblefield's inventions, he refuses to let anyone see them. "I've been giving it out free for years," Hortin said. "I'm tired of people making fun of him and getting their information wrong. I've decided to put it all together and write a book. "Pardon my vehemence," he continued, "but I've been doing this for 50 years. "I say he invented radio about 1890, but I don't think anyone really knows. When someone questions me, I say, 'Let's see what you have. Who do you think did it?' That usually quiets them down.

Interestingly enough, his Philadelphia experiments as well as his Washington showings were successful, but his New York trip was a bust. Some observers attri-

"Be it resolved by the General Assembly of the Commonwealth of Kentucky: That the General Assembly of the Commonwealth of Kentucky hereby publicly recognizes Nathan B. Stubblefield, who was a native of the city of Murray, Calloway County, Ky., as the true inventor of the radio, and it is the sentiment of the General Assembly that said Nathan B. Stubblefield is entitled to the highest honor and respect at the hands of the people of this Commonwealth and of this nation for his outstanding service."

> -Resolution by the Kentucky Legislature, 1944.

was stolen. Others say he became angry at his backers' greed. Still others contend he went mad.

After a Washington trip in 1912, Stubblefield told his friends and associates to withdraw their investments, go away, and leave him alone. That same year his house burned to the ground.

Later, his wife and children left him and he built a cabin about six miles north of Murray. There he continued to tinker, and apocraphyl stories abounded about his strange experiments which supposedly involved drawing energy from the earth for lighting.

He died March 28, 1928, of natural causes, and two days later Horace Churchill, country coroner, and his son, Ronald, broke down the door to Stubblefield's cabin. He was dead on the floor.

In his report, Churchill

"Radio is a device that transmits and receives voice over considerable distance without connecting wires," Hortin said. "Stubblefield invented, manufactured, and demonstrated such a device and did so before anyone else on this planet. That's my claim." He described "considerable distance" as several miles.

James L. Johnson is another unabashed Stubblefield booster. In a 1961 speech, the former executive secretary of the Murray chamber of commerce told the annual convention of The Kentucky Broadcaster Association in Louisville: "'Hello Rainey...Hello Rainey.' These four words, highly insignificant in themselves, were the gateway that opened a fabulous industry in the late 19th and early 20th century. These were the first words ever broadcast by radio. These four words put you people in business."

Following the address, the association presented the chamber of commerce a plaque recognizing Nathan B. Stubblefield as the inventor of broadcast radio.

But Riley Kaye W4LMF holds a different view of the Stubblefield story. "I think Stubblefield invented the induction telephone. He used loops above the ground. There appeared to be no carrier. He used audio frequencies, and that's where the challenge comes in," said the man who worked for 7 years as chief instructor at RCA and high-frequency development engineer for Western Electric in Chicago. "There is no proof that he used radiation. There's no proof he used resonant circuits. That would be radio." Kaye, 9DKN during sparkgap days, added: "Nobody can challenge that he didn't invent the wireless telephone and that he was the first to transmit voice without wires. He deserves a lot of credit and Murray can be proud of him."

er look. "It's not a private system, but it is cheap. It has a range of about five miles and seems perfect for community civil defense and emergencies. That avenue has not been pursued."

(Note that in Stubblefield's patent the ground rods are missing. In his early work, he employed a conduction system of telephony using the earth, but he later switched to an induction system. Evidently, Stubblefield confused the two media, thinking his voice traveled through both of them in a similar fashion.)

Another local ham takes issue with the Stubblefield saga. William Call KJ4W is vice-president and trustee of the Murray State University Amateur Radio Club. "It may have been magnetic induction," he said. "But you won't find that opinion around here much because it offends people. They want to believe he invented radio. On what I've seen," the school's electrical engineer said, "I don't believe he invented radio, but one thing almost everyone agrees on is that Stubblefield was a genius."



Photo H. Built in 1948, radio station WNBS was the first broadcast station in Murray. Its call letters were chosen to honor Nathan B. Stubblefield.

Despite its limitations, Kaye believes that Stubblefield's system needs a closThat he was.

Assaults on his claims of inventing radio have drawn attention from Stubblefield's other brilliant inventions. In 1888, he patented the first mechanical telephone, and he linked Murray with the system. It worked well until Bell introduced his electrical telephone which was superior in voice quality and reliability. He also invented a new type of primary battery, previously mentioned, whose revolutionary design stepped up dry-cell technology many notches.

So, if Stubblefield didn't invent radio-and it appears from his patent that he really didn't-who did? According to many ex-

perts, another relatively unknown inventor, Reginald Aubrey Fessenden, on December 11, 1906, gave the first public demonstration of voice transmission using Hertzian waves-radio as we know it.

The exhibition by the one-time chief chemist of Thomas Edison's lab took place at Brant Rock, Massachusetts. He reportedly told a journalist in 1915 that he had been toying with the invention for some time and perfected it in December, 1900. He gradually increased the transmission range until, in 1904, he could cover 25 miles. Then he offered it to the Navy for development.

Fessenden was born October 6, 1866, in East Bolton, Quebec, and died July 23, 1932, in Bermuda.

So, it appears that although Stubblefield didn't invent radio, he was indeed

the first person to send wireless voice transmission and suggest that it be employed in a moving vehicle such as a boat or horseless carriage.

But he holds another title, too. He was the first to transmit wireless voice from a ship.

In a 1971 thesis paper for Florida State University titled "The Contribution of Nathan B. Stubblefield to the Invention of Wireless Voice Transmission," author T. Morgan wrote: "Nathan B. Stubblefield was not the father of radio broadcasting. Stubblefield was the first man to successfully transmit and receive the human voice without wires. Therefore, let him be called the father of wireless voice transmission, for this title is truly his."

Perhaps I should drive to East Bolton and see if the residents there agree.

Carl M. Chernan WA3UER 1135 Constitution Drive Tarentum PA 15084

In Search of the Elusive SES – track solar activity with this simple VLF receiver

With the continuing and growing interest in solar flare activity, in-

cluding the predictions for Cycle 21, radio amateurs and experimenters alike are searching for methods to follow and record this fascinating phenomenon.



Photo A. Finished package with the fine-tune control added.

The SES (Sudden Enhancement of Signal) receiver that I am going to describe in this article provides a simple answer.

When a solar flare occurs on the sun, there is a major emission of X-rays. This has the effect of increasing the electron density of the D layer, immediately enhancing the storm noise (or the transmitted signal) to levels about twice normal. The effect is very prominent in the LF and VLF ranges. This enhancement, though it has a rather rapid rise time as seen from the recordings in Fig. 1, has a slow decay time as the D layer reestablishes its normal condition which can take from 30 minutes up to an hour.

Heat generated by the sun in the daytime periods expands the gas in the D layer, lowering its efficiency for radio propagation

42 73 Magazine • December, 1980



Photo B. Prototype receiver - front view.

during the day. Similarly, the cooling of the layer allows the gas to contract, increasing its efficiency; this, of course, is the reason that AM radio stations are received at greater distances at night. There also are seasonal effects which occur as the Earth heats or cools, depending upon the angle of the sunlight as it strikes the Earth.

Receivers used to record

Sudden Enhancement of Atmospherics. The second type is tuned to a transmitted signal in the VLF range, and is the SES receiver — referred to above. SES receivers are easier to tune, and you do not have to be an expert to interpret the recording charts.

Building the SES Receiver

A proven circuit for building a tunable SES receiver is shown in Fig. 2. It is basically a high-gain amplifier which is tunable from 17.8 to 35 kHz. If you use the exact components shown on the schematic,



Photo C. Prototype receiver – rear view, showing the shielding method used.

the frequency range will be from 17.8 to 23 kHz. This circuitry is then followed by a detector and integrator and finally by a dc amplifier which brings the dc signalrelated current up to a proper level to operate an analog meter or a recording device.

The recorder recommended is a model 288 Rustrak (0-100 uA) with a chart speed of 1" per hour, although I have used Esterline Angus 0-1-mA chart recorders successfully. The receiver has more than enough gain to peg a 0-1-mA meter.

All of the parts used in the construction of the receiver are standard, with the exception of the inductor coils. These inductor coils (Miller 6319) are high-Q types and are Litz-wire wound. They can be obtained from Bell Industries, J. W. Miller Division, 19070 Reyes Avenue, PO Box 5825, Compton CA 80224.

these enhancements come in two categories. The first is an SEA receiver that is tuned to an unused frequency spectrum in the VLF range—hence the name,

Wiring of the circuit is not critical; however, I suggest that a socket be used to mount the IC amplifier. A



Fig. 1. Actual recordings showing characteristic fast rise/slow decay times.



Photo D. Shield removed to show coils, L1, L2, and gain pot.

substitution for the RCA CA3035 amplifier array is the more-readily-available Sylvania ECG-785. Both wideband amplifier arrays are made up of three individual ultrahigh-gain amplifiers. These amplifiers have low noise characteristics, can be operated either independently or in cascade, and have excellent high cascade voltage gain-129 dB at 40 kHz. The output transistor (RCA SK3019) can be replaced with either a Sylvania ECG-108 or a GE-214. Power supply requirements are 9.3 V dc for optimum operation, but any well-regulated 12-volt power supply can be used. The higher the voltage, the "choppier" the trace will become on the recording.

Initial Tuning Procedure

Run the cores of L1 and L2 completely in. Proceed to turn the gain control (R1) 1/4 turn clockwise. Connect the antenna (preferably an 18-foot vertical or an 8-foot CB whip) to the receiver input jack. Ground the receiver using a good earth ground. Connect an oscilloscope (using the vertical input) to the test-point jack on the receiver. Turn out L1 one full turn. A large sine wave will appear on the screen, showing a prominent "hump."

not be used in solar flare studies, so continue to turn the core of L1 out. The 17.8-kHz signal should drop out and a small hump will, appear. This will be 18.6 kHz-NAA's 1-megawatt station. If the signal has good strength, by all means record it. If the signal is weak, as in my case, continue with the turning by opening the core of L1 until it's almost fully open or until a large signal reappears on the screen.

This signal will be 21.4 kHz (NSS) radiating a 200-kW signal. This station is an excellent choice for flare propagation recording for a number of reasons. First, it is easy to access (you cannot mistake the signal) and tuning is straightforward. Second, my records, along with the records at the AAVSO (American Association of Variable Star Observers) show that a lot of small flares are recorded at this frequency while they are often completely missed at other low frequencies.

scope or tuning meter and place a recorder at the designated terminals. Turn up gain control R1 to give you a mid-scale reading of either 50 uA or close to 1 mA if you are using a 0-1-mA recorder. By turning L1 in and out a few threads, peak the signal. Fine-tune the signal with 5-6 turns of L2. In some cases, it will show a prominent increase; in others, it will not. (Since all coils are not the same, the tuning of L2 may vary.) To test for oscillation, disconnect the antenna; the signal on the recorder should drop to zero or almost to zero. When the ground is disconnected, the signal definitely should drop to zero.

Other Hints and Correlation Ideas

The receiver itself can be housed in any standard metal or wood enclosure, but be sure to make use of adequate shielding around the inductor coils to ensure proper mixing. I use small,

If you have used the components specified in the schematic, this will be a signal coming from 17.8 kHz (NAA, Coutler, Maine). The format of this transmitted signal is such that it canIf an oscilloscope is not available for tuning, the receiver can be tuned with a 0-200 uA meter placed across the receiver's recorder output terminals. When coil L1 is turned, a prominent peak will indicate that you have tuned the signal.

Final Tuning Procedure Disconnect the oscillo-



Fig. 2. Circuit for a tunable SES receiver.

Good correlation on an official basis for flare recording and verification may be obtained by sending for a weekly solar data bulletin (free) printed by the government. Write to the Space Environment Services Center, Space Environment Laboratory ERL, NOAA, Boulder CO 80302. Ask for the preliminary report and forecast of solar geophysical data.

Circuit boards for building the receiver are available from me for \$8.00 each, plus postage.

For those further interested in solar flares and flare recording, my Handbook of Solar Flare Monitoring and Propagation Forecasting is available from Tab Books.





- Tells the date and year.
- Up-timer to 60 minutes, 59 seconds with pause.
- Alarm to ring at the same time everyday.
- Daily appointment sets appointments for the next 23 hours, 59 minutes.
- Future appointments up to one year.
- Dimmer switch for display.
- Memory will hold up to 30 appointments.
- Lithium power cell to retain memory during power outage.
- Appointments entered out of chronological order will be stored in chronological order.
- Colon flashes once each second.
- A.M./P.M. indicator.
- Plugs into any wall outlet.
- Easy to read vacuum fluorescent display.
- Extremely accurate quartz crystal clock.

EFFICIENT. REMARKABLE.

TimeTrac sold and distributed by HAL-TRONIX. Dealers welcome.

Send 15¢ stamp or S.A.S.E. for information and flyer on other HAL-TRONIX products. To order by phone: 1-313-285-1782.



HAL-TRONIX ×31 P.O. Box 1101

Southgate, MI 48195

SHIPPING INFORMATION:

"HAL" HAROLD C. NOWLAND

W8ZXH

ORDERS OVER \$20.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$20.00 PLEASE INCLUDE ADDITION-AL \$1.50 FOR HANDLING AND MAILING CHARGES.

IU-/S HEAVY-ROTATOR

with exclusive Dual-Speed Control!

For antennas up to 10.7 sq. ft. of wind load area. Mast support bracket design permits easy centering and offers a positive drive no-slip option. Automatic brake action cushions stops to reduce inertia stresses. Unique control unit features DUAL-SPEED rotation with one five-position switch. SPECIFICATIONS: Max. wind load bending moment-10,000 in.-Ibs. (side-thrust overturning); Starting torque - 400 in.-Ibs.; Hardened steel drive gears; Bearings -100-3/8" diameter (hardened); Meter - D'Arsonval, taut band (backlighted). There's much, much more — so get the whole story!

Mail this coupon for complete details! ~314

Send	me	соп	plete	det	ails	on the I	HD-73!
Give	me	the	name	of	my	nearest	dealer!

NAME

STATE

ADDRESS

CITY

ZIP

ker of the famous Antenna Rotator . . . Alliance Tenna-Rotor® . . . "TV's Better Color Getter!"

The ALLIANCE Manufacturing Co., Inc., Alliance, Ohio 44601

A NORTH AMERICAN PHILIPS COMPANY

C 1978 The Alliance Mfg. Co., Inc.

Don Inbody WA0PBQ 8413 Riggs Overland Park KS 66212

An Even Better IC Timer - better than what?

Photos by Joe Woelfel



his project is a good example of the use of elaborate means to accomplish a simple task. Having become hopelessly hooked on the fun and logic of TTL devices, I was intrigued by an article by Kenneth Williams WB3ELV, in 73, September, 1978. He had designed a circuit board for a 10-minute ID timer described by Ken Henry K3VTZ in a May, 1977, 73 article. His timer used a single 7-segment readout and cycled through 10-minute intervals. After reading most of the series of 73 articles on how to use ICs, by Alexander McLean WA2SUT, I decided it would be more fun to have a timer which indicated minutes and seconds. I had a 10-minute timer working on the breadboard when I found another 73 article, "Build a Unique Timer," by Marc Leavey WA3AJR (August, 1977). His timer, built for darkroom use, will time to either 99 seconds or 99 minutes and used a 555 as the timebase. That article exposed me to the 7485 comparator chip and

This is the front of the timer. Three 7-segment LEDs are behind a red plastic filter mounted in the upper left section. One digit is to the left of the letters; two are on the right. Discrete LEDs behind the H-M and M-S indicate whether the timer is in the hours/minutes or minutes/seconds mode. They are controlled by the toggle in the upper center. Thumbwheel switches are in the upper right section. The white frame is a piece of plastic covering a mistake made when cutting the hole. Lying on top of the timer is the remote switch box connected by a 4-wire cable. Woodgrain contact vinyl was used to cover the bare aluminum of the Radio Shack cabinet. Labels are dry transfer letters. thumbwheel switches. My timer grew out of all these, along with some basic design concepts from The TTL Cookbook.

My timer will do everything these will do and more. It will run to any userselected time up to 9 minutes, 59 seconds by seconds or it will run from 1 minute to 9 hours, 59 minutes by minutes. At the end of the selected interval, an alarm may be sounded and a 115-V ac appliance may be turned on or turned off. The timing sequence may be interrupted by a manual reset. The timer may also be used as a stopwatch or an elapsed-time recorder. It may be stopped and restarted with or without resetting to zero.

The block diagram, Fig. 1, shows the general operation of the timer. A waveshaper converts 60-Hz sinewave current from the transformer secondary into the square wave required by TTL. A gate, controlled by a start/stop flip-flop, routes these pulses to the divider chain which divides by 60 twice to produce one pulse per second and one pulse per minute. These, as selected by the mode switch, go to the counter/ driver/display section which shows minutes and seconds or hours and minutes. The output of the counters is compared with the settings of external thumbwheel switches. When these match, an alarm sounds and all dividers and counters are reset to zero. The wave-shaper consists of two resistors, a diode, and a Schmitt trigger circuit using two inverters on U1. I have seen circuits which used only a diode to clip the sine-wave output, but I did not get dependable triggering until I included the trigger. Most TTL devices require negative-going pulses and tend to get confused unless they see very

fast high-to-low switching. The circuit shown does not produce a 50% duty cycle square wave, but the negative-going pulses follow each other at a 60-Hz rate. Switching time is very short—on the order of a few nanoseconds.

The shaper output goes to the divider chain through a gate on U2 controlled by the start/stop flip-flops. U3 and U4 divide by 6 and 10 and produce one pulse per











Interior view showing the inside of the front panel and part of the main circuit board. Displays are upper right; thumbwheel switches are at the left. The 7447 display drivers and segment current-limiting resistors are in the lower center. Below them are the 7490 and 7492 decoders. The unorthodox wire connections to two of the drivers were added to correct errors on the circuit board. Because of omitted foil connections, wires were forced into the sockets beside IC pins.

second. This is further divided by 6 and 10 by U5 and U6 to produce one pulse per minute.

one-per-minute pulses, as selected by the mode switch, S5, are fed to the divider chain consisting of U9, U10, and U11. Each of these feeds a 7447 driver and a 7-segment LED readout. The outputs of U9, U10, and U11 are compared with the settings of three BCD thumbwheel switches by U15, U16, and U17. When those outputs match, pin 6 of U17 goes high, resets all counters to zero, sets off an alarm, and trips an SPDT relay which switches one 115-V ac outlet on and another off. U7 is wired to form two interconnected R-S flipflops. One is used to start and stop the timer by operating a gate on U2 which controls the 60-Hz pulse to the divider chain. This permits stopping and restarting the timer without resetting the counters to zero. Interrupting the count at this point introduces a mini-

mum of error. The other flip-flop is used to control the reset line to all dividers and counters. When pin 6 of The one-per-second or U17 goes high, pins 3 and 4 of U7 and the reset line go high. This stops all counting and resets the dividers and counters to zero. The reset line stays high until the start button is pushed, which drives the reset line low and permits the counters and dividers to operate. Closing the start switch also sets the reset flip-flop so that it is ready to accept a new pulse from U17. The reset line also can be driven high manually by S3. U10, a 7492, needed some special treatment. To show tens of seconds (or minutes), the counter has to count to 5 and reset to zero on the sixth count. On the sixth count, a negative-going pulse must be provided to the input of U11, the minutes (or hours) counter. Pin 9 of the 7492 goes high on the fourth count and low on the sixth count. U11 ignores the positive-going pulse and is triggered by the negative-going pulse. However,



Rear view showing placement of tone duration and volume pots, voltage regulator, and external connections. The fourhole socket at the left is for the remote switch box. At the right are two 115 V ac sockets, "THEN" is hot at the end of the pre-set timing period. "NOW" is hot during the timing period.

if left to proceed through its normal count cycle, the pin 9 output would remain low for 10 more counts, triggering U11 only every second minute (or hour).

There is a solution, though. Pin 8 goes high on the sixth count, so that output can be used to reset the counter to zero, and U11 is triggered every sixth count. Connecting pin 8 of U10 directly to its reset pins, 6 and 7, interfered with the operation of the system-reset from U2. A diode between pins 7 and 8, blocking the system-reset pulse from U2, solved the problem. The 7447 BCD drivers provide leading-zero blanking. When pin 5 of the most significant digit is grounded and pin 4 is connected to less significant digits, the readouts will not display meaningless zeros. I connected pin 5 of U14 to the reset line instead of to ground; thus, leading zeros are blanked only when the timer is counting. This gives a visual indication of the state of the timer. I also wanted visual indication of whether the timer was in the hours/minutes or

minutes/seconds mode. The obvious solution was to use discrete LEDs as indicators. Also, in the hours/minutes mode, the readout changes only once per minute. To provide assurance that something was really happening, I made one of the readout decimal points blink at a 1-Hz rate. Switching all those functions would be simple with a 3-pole, 2-position switch. However, switches are expensive; ICs are cheap. With the use of gates on U2 and inverters on U1, the hours/minutes and minutes/seconds timing pulses, the LED indicators, and a pulsing decimal point for hours/minutes are all switched with an SPDT toggle, S5. When S5 is in the minutes/seconds position, pin 10 of U2 is high, allowing the 1-Hz pulses to reach the counter chain. Also, pin 5 of U1 is high and pin 6 is low, providing a ground for the minutes/seconds indicator LED. In the hours/minutes position of S5, pin 13 of U2 is high and one pulse reaches the counter each minute; pin 4 of U1 is low, providing a ground for the

indicator, and pin 4 of U2 is high, passing one pulse per second to the decimal point of the units readout.

All this switching caused a small problem. I discovered that in the hours/minutes mode, the timer indicated 1 minute after 48 seconds had elapsed. Just a little examination of the 7490 logic table revealed the reason. Pin 11 of a 7490 is low for 8 counts, high for 2 counts, then goes low. That negative-going pulse triggers other devices. However, I had routed the pulses through a 7400 gate and inverted everything. Thus, the positive-going pulse at the eighth count of U6 was seen at the input of U9 as a negative-going pulse. Of course, each succeeding "minute" was 60 seconds long. The problem was corrected by running the minutes output from U6 through an inverter on U1.

The same inaccuracy exists with the 1-Hz output from U4. The first "second" is only .8 second long. I decided to live with that error, because no more inverters were available without adding another IC. By now I realized that the whole problem (and some others) could have been avoided by using a 7408 for U2 instead of a 7400. I did not have a 7408, and my circuit board was already laid out. Oh, well. Next time! S4, an SPST toggle, was added to increase the versatility of the timer. When it is closed, the reset and start push-buttons are shorted together. Pressing either switch resets everything to zero and immediately starts a new timing sequence. The alarm still sounds at the end of the selected interval, but it is not possible to stop and restart the count without returning to zero. This mode also effectively disables the 115-V ac switching function as the stop-reset-start sequence is so fast that the relay does not trip. I called

the closed position of S4 "auto" and the open position "manual." The strange location of the switch happened because this feature was not installed until the project was complete. With a little forethought, the switch could have been located in a better place.

Two 115-V ac sockets are provided for the operation of external appliances such as lights, radio, TV, etc. An SPDT relay with a 6-V coil switches the outlets on or off. One is on and one is off during the timing sequence. This is reversed at the end of the selected interval. Pin 1 of U7 is high during the timing period, so that output was used to make a 2N2222A transistor switch 5 V dc to the relay. A 1N914 diode across the relay coil reduces voltage spikes which occur when the coil is switched out.

The alarm circuit is built around a 556 timer. This is a dual 555 with one part serv-



Interior view of the timer. The power supply and ac switching relay are on the left. Displays are at lower left; thumbwheel switches are at lower right. The 7485 comparators and 7405 inverters are on a small circuit board mounted vertically at the right. The unorthodox wires on the ICs in the upper right and lower left were used to correct circuit board mistakes. Some foil connections were omitted, so wires were forced into the sockets beside the IC pins.

be used.

The switch input to the 7485 comparators requires a BCD complement. I have read that complement mode switches are available, but I could locate only straight BCD switches. A couple of 7405 hex inverters were used to generate the complements of the selected numbers.

could be used. A 10-uF tantalum capacitor from the output of the 7805 to ground is necessary to prevent oscillation and should be mounted as close to the output terminal as possible. De-spiking is provided by several .01-uF disc capacitors. These are not shown on the schematic, but were placed at various locations where the +5-V dc lines were near ground buses. Good TTL design calls for one de-spiking capacitor for every 3 ICs, and one at every place the supply line enters a circuit board.

ing as an oscillator to produce a tone and the other as a timer to set the duration of the tone. Pin 6 must be low to trigger the multivibrator, so the high output from pin 6 of U17 is inverted through U1. The pitch of the alarm tone may be adjusted with a 100k pot mounted on the circuit board. The duration of the alarm tone may be varied from a fraction of a second to several seconds with a 50k pot mounted on the rear of the cabinet. I placed a 2.2k resistor in series with the pot so that there would be some tone when the pot was at minimum resistance. The volume of the alarm tone may be adjusted with a 1k pot on the rear of the cabinet. The alarm can be completely disabled with a toggle switch mounted on the front of the cabinet. I included an LED to indicate when the alarm is enabled. If the indicator were omitted, an SPST switch could

The power supply as shown in Fig. 3 is conventional. A 12.6-V, 1-A transformer was used because it was on hand. Anything that will produce at least 7.5 V at .5 A should work. I used a 7805 regulator and mounted it on the rear of the cabinet. Any +5-V regulator capable of handling .5 A

To make the timer more useful for timing games, for use as a stopwatch, and to generally improve portabil-



73 Magazine • December, 1980 49



Interior view of the timer showing the speaker mounted on the top of the cabinet. The power supply components and 115 V ac connections are shown on the left side. The small board at the right was added after the project had been designed and the main circuit board etched. With better planning, the 2 ICs could have been mounted on the main board.

ity, I installed 3 push-button switches in a small box and connected them in parallel with the front-mounted start, stop, and reset buttons. I used a 4-pin socket on the cabinet back and a piece of 4-wire cable from the junk box. ground connections instead of +5 V dc.

All parts were readily available at local Radio Shack stores and from firms advertising in 73. There is considerable variation of prices, so it pays to do some comparison shopping.

Parts List Diodes 2 1N914 or 1N4148 3 1N4001 Capacitors 6 .01-uF ceramic disc 1 10-uF tantalum 1 10-uF 16-V electrolytic 1 22-uF 16-V electrolytic 1 2200-uF 16-V electrolytic Integrated Circuits 1 U1-SN7404 1 U2-SN7400 3 U3, U5, U10-SN7492 4 U4, U6, U9, U11-SN7490 1 U7-SN7402 1 U8-NE556 3 U12, U13, U14-SN7447 3 U15, U16, U17-SN7485 2 U18, U19-SN7405 1 U20-7805 regulator LEDs 3.2" discrete LEDs 3 FND-510 displays Resistors (all 1/4 Watt) 7 330 Ohm 23 470 Ohm 3 2.2k Ohm 1 6.8k Ohm 1 10k Ohm 1 1k linear pot 1 50k linear pot 1 100k PC-board pot Sockets 2 ac sockets (Radio Shack 270-642) 13 14-pin IC sockets

I used FND-510s for the readouts. They are large (.5") and can be bought for \$1.00 or less. The 510 is a common-anode device. Almost any 7-segment LED could be used. Commoncathode devices would require 7446 drivers and



Fig. 4. Supply connections.

I used circuit board construction. Perfboard or wire-wrap probably would have worked, but I wanted the neater appearance of circuit boards. I ended up with 4 boards. The FND-510s, the hours/minutes, and the minutes/seconds LEDs were on one. Because of the many interconnections with other ICs, it seemed simpler to mount the 7485s and 7405s on a separate board. After the main board was etched, I made a design change which required the addition of the 7404 hex inverter and different connections to the 7400 NAND gate. A separate small board was made for those two ICs. They could have been included on the main board with proper planning. The 7805 regulator, alarm volume control, alarm dura-

Switches
3 NO push-buttons (S1,S2,S3)
1 SPST miniature toggle (S4)
1 SPDT miniature toggle (S5)
1 DPST miniature toggle (S6)
1 SPST standard toggle (S10)
3 * BCD thumbwheel switches (S7,S8,S9)
Other
Cabinet (Radio Shack 270-269)
Relay-SPDT, 6-V coil (Calectro D1-066)
Speaker-8-Ohm, 2-inch
Transformer-12.6-V c-t, 1 A
Transistor-2N2222A
*Thumbwheel switches are available from
Jameco. This installation required:
3 SR21 BCD switches
1 SRBB blank body
1 pr. SREP end plates

tion pot, 115-V ac sockets, and the remote-control socket were all mounted on the rear of the cabinet. All other components were mounted on the main circuit board except the frontmounted switches. There is nothing especially critical about parts placement, although a little care and planning are needed to reduce the need for jumpers. Supply connections are

6 16-pin IC sockets

not shown on the schematic, Fig. 2. Ground and +5-V dc connections must be provided to all ICs, as shown in Fig. 4.

This project has been a lot of fun. In it, as my first attempt to design a project, or at least to make major modifications to others' projects, I have learned a great deal about TTL. And, the completed timer has even proven useful! I have actually used it as an ID reminder when rag chewing on 15 meters. My family enjoys a variety of games which have time limits varying from a few seconds to several minutes. The timer works well for them. One son is supposed to practice on the organ for 30 minutes. Sometimes he has to interrupt that practice for more important business such as petting the dog, going to the bathroom, etc. Now the rule is that he has to set the timer for 30 minutes, stop it whenever one of those diversions occurs, restart it when returning to the organ, and continue until 30 minutes of actual practice have been completed.

If you build this timer, you will no doubt want to make changes. Some variations have already occurred to me. I have already mentioned the use of a 7408 for U2. The timer limit could easily be extended to 99

minutes or 99 hours. The counter/driver/comparator chain could easily be expanded by adding another 7490, 7485, 7447, readout, and thumbwheel switch. The timer could be made to display tenths of seconds by feeding the counters from the output of U3. No doubt there are also more efficient or effective ways to accomplish some of the same functions. I will be interested in hearing about your results.

Incidentally, etched and drilled circuit boards and parts kits are not available. You are on your own! You will probably want to make modifications to suit your own needs. Anyway, getting there is at least half the fun.

My thanks to my colleague, Joe Woelfel, for the photography, and to those mentioned in the opening paragraphs who got me into this.

NOW, ADJUST YOUR D104 WITH ONE FINCER

The Fingertip Volume Control makes it simple - without screwdrivers, nail files or special tools.

NO DRILLING! NO SOLDERING! NO CUTTING!

Remove the stock bottom plate, screw on the Fingertip Volume Control, adjust with one finger, and talk. It's that simple!

THE QUALITY UNIT!

Rugged black Cycolac with aluminum look dial is both durable and attractive. No-scratch rubber feet protect fine furniture.

FITS THEM ALL!

The Fingertip Volume Control fits all TUG8, TUG9, and TUP9 D104 microphones, including the Golden Eagle, Silver Eagle, and Blackfoot models. Complete instructions and hardware included.

SATISFACTION GUARANT

URBAN ENGINEERING, INC. × 387 P.O. Box 571052 Miami, Florida 33157

Fingertip Volume Control(s) at \$7.95 plus 80 cents Yes, please send me. postage and handling each (Florida residents add 4% tax). I understand that if I am not completely satisfied. I can return the unit(s) within ten days for a full refund.

Name (please print)

Address

City/State/Zip

My check is enclosed, please ship within 14 days

I have enclosed a money order for immediate shipping

Charge my credit card: Visa Master Charge

Card No. Exp. Date

ANNOUNCEMENT FROM THE

WORLD'S LARGEST SPECIALISTS IN THE DESIGNING, DEVELOPING AND MANUFACTURING OF "NO COIL, NO TRAP" ANTENNA SYSTEMS.

NO TRAPS, NO CAPACITORS, (Not to Scale) (80-10HD) NO COILS, NO STUBS DRGAI

EXCLUSIVE 66 FOOT,75-10 METER DIPOLES

negligible effect on performance.

VERY IMPORT

- Fabricated from highstrength 40% breaking strength.
- Stainless steel hardware.
- Completely assembled and pre-tuned. No cutting or measuring necessary.
- 1-year limited warranty.
- · Patented linear phase loading principle eliminates need for traps, loading coils or stubs.

Mor-Gain 2200 T South 4th Street P.O. Box 329 T Leavenworth, Kansas 66048 (913) 682-3142 Monday - Friday: 9AM-5PM CST

- May be installed as inverted vee with
 Engineering design and manufacturing is backed by our more than 15 years experience.
 - copperweld wire over 500 pounds . Professional grade design Amateur models are identical to those we produce for commercial/industrial systems.
 - · No antenna tuner required for operation within stated specifications.
 - · Re-tuneable by the user to accomodate site proximity effcts.
 - · HD/A models have female coax connector. Other models have lugs at center insulator.





MODEL	BAND L	ENGTH	I PRICE
	(Meters)	(feet)	
40-20 HD	40/20	36	S 69.25
40-20 HD/A	40/20	36	\$ 75.50
75-10 HD	75/40/20/15/10	66	\$112.25
75-10 HD/A	75/40/20/15/10	66	S118.50
75-10 HD(SP)	75/40/20/15/10	66	\$112.25
75-10 HD(SP)A	75/40/20/15/10	66	\$118.50
75-20 HD	75/40/20	66	S 95.50
75-20 HD/A	75/40/20	66	\$101.75
75-20 HD(SP)	75/40/20	66	\$ 95.50
75-20 HD(SP)A	75/40/20	66	\$101.75
75-40 HD	75/40	66	\$ 81.00
75-40 HD/A	75/40	66	\$ 87.25
75-40 HD(SP)	75/40	66	S 81.00
75-40 HD(SP)A	75/40	66	\$ 87.25
80-10 HD	80/40/20/15/10	69	\$117.25
80-10 HD/A	80/40/20/15/10	69	\$123.50
80-10 HD(NT)	80/40/20/15/10	69	\$117.25
50-10 HD(NT)A	80/40/20/15/10	69	\$123.50
50-40 HD	80/40/15	60	5 85.75
50-40 HD/A	80/40/15	60	\$ 92.00
0-40 HD(NT)	00/40/15	60	5 85.75
50-40 MU(NT)A	80/40/15	03	5 92.00

Please include \$3.00 for shipping and insurance

N/T series are models specifically optimized for novice band opertors.



Please write for fully descriptive 5 page brochure. Contact your favorite dealer or order direct from Mor-Gain.

Dr. Ralph E. Taggart WB8DQT 602 South Jefferson Mason MI 48854

Direct Printing FAX — part II: constructing the facsimile recorder

n part II of this three-part article, I will cover construction of the facsimile recorder. Construction is probably the most critical part of the project, as considerable mechanical tinkering is involved and the various parts must function

of additional assembly work is required to get the assembly ready for operation. The cost for this package is \$500 plus shipping. This is more than you will pay for the home-built alternative but does eliminate virtually all of the work associated with the mechanical part of the project, and you also get circuit boards for the electronics. The second approach is to build the mechanics yourself. To this end, I have documented a modified (and improved) version of the fax mechanics described in the first edition of the Weather Satellite Handbook. This assembly will do an excellent job, but you will have to build it and do considerable fine-tuning to get it operating properly. Once it is set up, it should require very little ongoing maintenance. The Drum. The drum (Fig. 2) is fabricated from a plastic rolling pin-a "Pastry Pin" manufactured by the Housewares Division of the Foley Manufacturing Company of Minneapolis. This item is sold in housewares departments and discount stores across the country and costs between \$1.60

and \$2.00 depending upon the source. The drum is just over 2 inches (5 cm) in diameter and is perfect for this application. Other materials may be used for the drum, but you should stick close to this figure for the diameter to avoid distor-

grounding paper. This means that the ground return must be provided from the paper surface. This is accomplished via an aluminum foil strip attached to the drum surface and connected to the drum shaft for grounding. Drill a #2 pilot hole at the right end of the drum and place the small end of the angled piece of foil over this hole. Use a small sheet-metal screw to attach a small solder lug so that it is in contact with the foil strip. The 7-inch length of foil is folded in half lengthwise along the dotted line and laid along the precise center line of the drum so that the right end of the strip is in contact with the piece of foil already in place. A long piece of transparent tape is then used to attach the lower side of the folded tape to the drum surface. The upper folded side must be free so that the paper can be inserted under it when it is fastened to the drum. The transparent tape should extend all the way to the back of the fold so that the entire lower half of the foil strip is covered, and should be wide enough to extend past the foil on three sides as indicated in the

smoothly in relation to one another if quality results are to be obtained.

Recorder Mechanics

The easiest approach is to use the FX-2E minikit available from METSAT Products, Box 142, Mason MI 48854. This kit contains drilled and plated circuit boards for the electronics circuits and a complete set of parts, most fully assembled, for the fax mechanics. The mechanical assembly, illustrated in Fig. 1, is made up of a series of parts machined out of brass, aluminum, and stainless steel and it is built like a battleship. It is quite heavy and massive and provides the rigidity and precision required for a smoothly operating system. The parts are drilled and tapped to permit assembly and disassembly with machine screws, and the kit includes all of the mechanics components including the motors. About 15 minutes

tion of the image aspect ratio.

The plastic handles of the rolling pin are twisted off and the shaft removed. A fine saw is used to cut the drum down to a length of 8 inches. True the cut end by using a fine file or sandpaper, and insert the end piece removed from the short length that was cut from the drum. The steel shaft should be cut down to 11.25 inches (save the piece you cut off as we will use it for the stylus). Deburr the ends with a fine file, and use steel wool or emery cloth to remove any corrosion from the steel shaft. Use a cyanoacrylate adhesive (Super GlueTM, Eastman 910TM, or other brands) to cement the shaft into place as indicated in Fig. 2.

Now comes the part which is harder to describe than it is to do. The paper we will use is a frontfigure. Additional tape then can be used to cover the exposed parts of the angled piece of foil so that it will not pull loose.

Next, break two brass inserts out of standard plastic panel knobs. Set one of these aside for stylus construction and slide the other over the right end of the drum shaft, using its set screw to secure it up against the right end of the drum. Prior to this step, however, you should solder a short length of hookup wire to the outside of the brass insert. When the insert is locked in place, cut and strip the wire and solder it to the small solder lug mounted previously. Do this operation quickly to avoid melting the plastic of the drum. A small magnet should be cemented to the drum as indicated in the figure. This completes the drum assembly. It should be set aside carefully to avoid spoiling your handiwork. Motors. The drum and traverse motors which are recommended are manufactured by the Hurst Manufacturing Company of Princeton IN. Other synchronous motors of identical speed and similar power rating or torque may be substituted. Motors of other speeds might also be usable if suitable gearing is provided to produce the proper speed at the output shaft of the gearing assembly. The drum motor is a 240-rpm type-GA motor, rated at 10 W, with 600-inch-oz. torque at 1 rpm. This speed is not a normally stocked option, but can be obtained on special order with a lead time of 4-6 weeks. The traverse motor selection is based on the class of service for which the recorder is intended. For GOES WEFAX, you should obtain a 40-rpm type-CA motor. This selection also will work well for



Fig. 1. A photograph showing the METSAT version of the facsimile mechanics. The homebuilt version described here operates on the same principles, but some features have been changed to facilitate home construction. In the METSAT version, the base and backplate are 1/2" aluminum with 1/8" aluminum side plates. The motors are to the left and the stylus carriage and the stylus itself are visible. In the illustrated version, the machined brass carriage base plate rides on two brass rails. The drum shows the foil grounding strip, magnet, and grounding wire and shaft collar. The magnetic reed switch that helps control WEFAX phasing is shown on the right end plate.

METEOR display. TIROS N display will require a 20-rpm type-CA motor. Both the 40- and 20-rpm motors are available as stock items. It should be noted that all of the motor speed ratings given are referenced to 60-Hz ac drive. In 50-Hz countries, you should obtain motors designed to operate from 50-Hz mains. Do not do this for the drum motor as the sync system is designed to provide 60-Hz drive, and if you use a 240-rpm motor designed for 50 Hz, the drum will be too fast. The motor wiring should be followed carefully, or the motors may not turn in the proper direction-something that will lead to some rather unusual pictures.

Mechanics Assembly. Fig. 3 shows some general views of the relationship of parts for the home-built version of the fax mechanics. Precise measurements are



Fig. 2. (1) General drum configuration. (A) 1/4" steel shaft. (B) Drum. (C) Small solder lug. (D) Piece of insulated hookup wire soldered to C and E. (E) Brass insert from a 1/4" control knob secured to the drum shaft with its setscrew. (2) Layout of aluminum foil strips (crosshatched) and transparent tape (stippled) on the drum. (F) is the small magnet attached to the drum surface with double-sided adhesive foam tape. (3) Dimensions of aluminum foil strips (see text for assembly).



Fig. 3. The facsimile recorder mechanical assembly. A - Drum motor; B - traverse motor; C - motor mounting plateangle bracket; <math>D - motor mounting plate; E - rubber-tubing shaft coupling; F - drive-rod support plate angle bracket; G - drive-rod support plate; H - 3/8'' panel bushing; I - drum support bracket; J - carriage track bracket; K - glass-platetrack surface; L - 1/4-20 threaded drive rod; M - drum assembly; N - stylus-carriage base; O - stylus support; P - carriage-drive washer, and <math>Q - 1/4-20 carriage-drive nut.



Fig. 4. Stylus holder details. (A) 3-1/4" piece of 1/4" steel rod stock (left over after the drum shaft has been cut to size). (B) 3/4" piece of 3/8" o.d. plastic tube stock. (C) 1/2" piece of 1/16" tube stock (stylus holder). (D) length of hookup wire soldered to one end of (C). (E) Wire stylus inserted into (C). num angle stock cut to the width of the motor mounting plate. The hole for the motor shaft bushing is drilled so that the motor shaft will line up precisely with the drum shaft when the plate/bracket assembly is screwed to the plywood base.

Once the shaft bushing hole has been drilled cortioned to provide a smooth sliding fit for the carriage base piece. It should be tight enough to eliminate any shifting of the base but no so tight that it binds. Once the second track rail has been mounted, you should measure the track width (between the rails) and have a piece of window glass cut to fit between the rails. It should be epoxied in place. The next job is to prepare the support plates for the 1/4-20 threaded drive rod. The rod must run down the center of the track at a height that will place it about 1/2'' above the top surface of the carriage base. The rod is supported by two 3/8" bushings in small plates of G-10 board stock or metal secured to the base with strips of aluminum angle stock. Drill the plates so that the 3/8" holes are at exactly the same height. Install the bushings and secure the plates to the base so that the rod runs down the center of the track. The traverse motor mounting arrangements are essentially identical to those of the drum motor, with alignment and mounting adjusted to keep the traverse drive shaft in alignment with the threaded

of little use since the details of layout will depend upon the locally available materials. I will, however, provide some general notes, trusting in your ability to improvise.

The base of the unit is best made with a piece of 3/4" plywood. The surface should be covered with formica, masonite, or some other smooth material. The recorder will produce some fine black ash that accumulates after a time and needs to be wiped off the surface. This is quite difficult if the natural rough wood porous surface is retained. The recorder mechanics utilize standard 3/8" panel bushings for 1/4" control shafts as bearings for the drum and drive rod. The drum is supported by two such bushings mounted at the top of the upright

section of two standard steel or brass right-angle brackets available from local hardware stores. The brackets should have the standard screw holes enlarged to 3/8" to accommodate the bushings.

Mount the right bracket to the base with wood screws and orient the left bracket so that the drum will turn freely when the bracket is screwed in place. Occasionally, these brackets are not completely true so that some bending with a pair of heavy pliers may be required after mounting to true up the bushings so that the drum will turn freely. The drum motor is mounted to a plate of G-10 fiberglass board stock, 1/8" aluminum sheet stock, or other rigid material. This mounting plate is secured to the base with a piece of 1/2" alumirectly, you can mark and drill the holes for the motor mounting lugs. Final positioning and securing of the mounting plate to the base is done while checking the alignment of the motor and drum shafts. The motor and drum are coupled with a piece of thick-walled tubing of the type used for vacuum lines in laboratories or automobile engines.

The stylus carriage is assembled from hardwood. The base piece should be about 3 inches square, and the vertical upright should be cut so that it is at or slightly above the centerline of the drum. A long piece of aluminum angle bracket is laid out parallel to and about an inch out from the drum face to define one edge of the carriage track. The positioning of the other edge is based on the width of your carriage base piece. The second rail should be posi-

drive rod.

A 3/8" hole should be drilled in the vertical member of the carriage assembly so that the carriage can be moved along the length of the track without coming in contact with the drive rod. Remove the carriage and paint it with several coats of epoxy paint or other oil-resistant finish. While the carriage is drying, take a 1/4-20 nut and drill a small hole part way through one of the flat faces on the edge of the nut. Solder a 3/4" wire brad or nail into this hole.

A small quantity of talcum powder should be sprinkled onto the track to serve as a dry lubricant. Place the carriage at the center of the track and thread the drive rod through the left support bushing, continuing to extend the rod until the right end protrudes through the hole drilled in the vertical carriage member. Slide the 1/2" flat washer over the exposed end of the drive rod and thread the prepared nut over the end of the rod. Run the nut down the rod (to the left) while extending the rod until it passes through the support bushing on the right end of the track. Couple the right end of the threaded drive rod to the traverse motor shaft using another piece of thickwalled rubber tubing. Rotate the drive nut until the brad is horizontal, and move the carriage up against the drive nut/washer assembly. Note that if the drive rod is rotated in either direction, the nut will rotate until the brad comes into contact with the carriage base. At this point the nut can no longer rotate and must move along the shaft. If the shaft is rotated in a counterclockwise direction (viewed from the front of the traverse motor), the nut will move away from the carriage and toward the motor. This is

Pin Function

1 Ground

3

5

- 2 Phase sensor reed switch (S203)
 - Stylus
- 4 M2 black lead (both)
 - M1 white lead
- 6 M1 black lead
- 7 M2 red lead
- 8 M2 white lead

Table 1.

what will occur when you are resetting the recorder. If the shaft is rotated in a clockwise direction, the nut will move away from the motor, pushing the carriage ahead of it. Misalignment or wobble in the shaft will cause the nut to slide around in contact with the washer but will not result in axial movements of the carriage; the only motion transferred to the carriage is a smooth push down the length of the carriage track. This particular drive system is much superior to systems where the nut is directly attached to the carriage assembly.

The final step in the assembly of the main mechanics package is to fabricate a small aluminum bracket that will attach to the right drum-mounting bracket and hold the magnetic reed switch above the



Fig. 5. Stylus support details. (A) 1" brass angle bracket. (B) 1" piece of 1/4" (o.d.) brass tubing soldered to the top of the vertical leg of the angle bracket. (C) 1-3/4" piece of 3/16" (o.d.) brass tube soldered at one end to the side of the brass insert from a 1/4" control knob (D). (E) 3/16" (i.d.) wheel collar. (F) 5/16" piece of 1/4" (o.d.) brass tube stock soldered to (C) so that the latter extends beyond (F) on the right side.

right end of the drum. Wire leads should be soldered to the switch terminals and a covering of electrical tape placed over the entire switch assembly. The aluminum support bracket and the attachment of the switch assembly to this bracket should be adjusted so that the small magnet on the drum will close the switch once during each drum revolution. This can be checked with an ohmmeter connected to the switch leads. Although aluminum is specified for the switch mounting assembly, almost any non-ferrous

metal can be used. Steel should be avoided as it will gradually become magnetized in the field of the drum magnet, exerting a pull on the switch elements that will gradually make the switch less sensitive.

Stylus Assembly. The details of the stylus assembly are shown in Figs. 4 and 5. The stylus holder is made up from the scrap piece of 1/4" steel rod cut from the drum shaft. To insulate the stylus from the support arm, a small piece of plastic tubing is cemented to the end of the steel rod, using cyanoacrylate glue. A small



Fig. 6. Stylus pivot and stylus arm assemblies. The stylus support bracket and pivot assembly are shown to the left, while the stylus arm is on the right.

piece of 1/16" brass tubing (this and other sizes of brass tubing are available in your local hobby shop) serves to hold the small, steel stylus wire. A piece of lightweight hookup wire is soldered to one end of the brass tube which then is mounted in a hole drilled in the plastic end piece and secured with cyanoacrylate cement.

For the stylus wire, you will need one of the small wire brushes designed to operate in an electric drill. (We will get to that during final checkout.) The stylus arm is supported by a brass pivot/bearing assembly formed of small pieces of brass tubing. The bearing assembly is soldered to a small brass angle bracket screwed to the vertical support of the carriage assembly. The precise size of the various pieces of tubing used for the bearing assembly is unimportant as long as the pieces nest smoothly.

The second brass knob insert, which you had set aside earlier, is soldered to the long piece of tubing (C) which serves as the axle of the support structure for the stylus arm. The bearing for the support of this axle (B) is soldered at the top of the vertical extension of the brass angle bracket. An aluminum "wheel collar," available from the same hobby shop where you get the tubing, serves as a stop at the brass insert end of the shaft, while a small piece of tubing (F) is slipped over the shaft and soldered at the outside end to provide the second stop. The tubing pieces should be deburred and the ends filed true prior to assembly. When completed, the inserted knob should rotate very freely but with no excess play in any other axis. Fig. 6 shows the assembled stylus parts to give you some idea how they look when assembled.

The stylus pivot assembly is mounted to the carriage upright using wood screws. It should be oriented with the bearing tube facing the drum. The free end of the stylus arm is inserted in the brass knob insert, and the support arm is oriented so that the protruding brass tube is facing directly down at the top center of the drum. The set screw of the insert then can be tightened to secure the stylus arm. The small brass tube used to hold the wire stylus should now be resting in contact with the top of the drum along the centerline. The weight of the stylus arm will supply the needed stylus pressure. You should be able to lift the stylus arm, folding it back away from the drum, and there should be no binding in the pivot assembly.

The connection between the control electronics and the mechanics assembly is

via an 8-conductor cable. The cable is anchored to the base of the mechanics assembly and is equipped with an 8-conductor plug (P3) that mates with an 8-conductor socket on the rear apron of the electronics cabinet. The P2 and P3 pin assignments, as indicated in the schematics, are shown in Table 1.

Heat-shrink tubing, tape, or other insulating steps should be taken for all connections (including the M1 starting capacitor, C301) to eliminate the possibility of shorting leads or creating a shock hazard.

If you've managed to get the electronics constructed and working already, completing this mechanical phase should keep you busy until part III of this article arrives. In part III, we'll put the whole system together, test and calibrate it, and (hopefully) enjoy the results.



New Lower Prices





WHY GET ON FAST SCAN ATV ?

- You can send broadcast quality video of home movies, video tapes, computer games, the shack, etc., at a cost that is less than slowscan. Requires only a technican class or higher.
- Really aids public service communications for parades, RACES, CAP searches, weather watch, marathons, etc.
- DX is about the same as 2 meter simplex 15 to 100 miles.
- ATV uses broadcast standards. No special converters needed. Receive full color and sound on a regular TV set.

TC-1 TRANSMITTER/CONVERTER



Plug in any closed circuit camera, antenna, mic., and TV set and you are on the air. Contains the basic four modules, AC supply, and T/R switch. Full color and sound. Specify xmtr freq and TV ch 2 or 3.

ALL IN ONE BOX READY TO OPERATE \$399 delivered U.S.

GET A BUDDY ON SPECIAL 2 for	\$ 750 ppd
HITACHI HV62U CAMERA B & W	\$ 239 ppd
GP-4D COLOR CAMERA	\$ 839 ppd

Build Your Own System with The Basic Four Modules



TXA5-4 ATV EXCITER/MODULATOR \$89 ppd This wired and tested module is designed to drive the Motorola MHW-710 module in the PA5 10 watt linear amp. The crystal in the 100 mHz region keeps harmonics out of two meters for talk back. The video modulator is full 8 mHz for computer graphics and color. Requires 13.8 vdc reg @ 70 ma. Tuned with xtal on 439.25, 434.0, or 426.25 mHz. Two Freq \$ 115 ppd.









2. PA5 10 WATT ATV POWER MODULE\$79 ppd

The PA5 will put out 10 watts RMS power on the sync tips when driven with 80 mw by the TXA5 exciter. 50 ohms in and out, plus bandwidth for the whole band with good linearity for color and sound. Requires 13.8 vdc regulated @ 3 amps.

3. FMA5 AUDIO SUBCARRIER GENERATOR \$ 29 ppd

Puts audio on with your camera video just as broadcast TV does at 4.5 mHz. Puts out up to 1 v p-p to drive the TXA5 or VM-2, 3, or 4 modulators. Requires low Z mic (150 to 600 ohms), and +12 to 18 vdc @ 25 ma. Works with any xmtr with 5 mHz video bandwidth.

4. TVC-2 ATV DOWNCONVERTER \$55 ppd Very sensitive stripline MRF901 (1.7 db NF) preamp and double balanced mixer module digs out the weak ones but resists intermods and overload. Connects between uhf antenna and TV set tuned to channel 2 or 3. Tunes 420 to 450 mHz. Requires +12 to18 vdc @ 20 ma. Super sensitive TVC-2L with NE64535 preamp (.9 db NF) preamp \$ 79 ppd.

TVC-4 ATV DOWNCONVERTER\$89 ppd This is a packaged version of the TVC-2 converter with internal power supply. Has BNC input and F output connectors. Also available with the NE64535 for \$115 ppd. Size 5¼ x 2½ x 7 inches.

PACKAGE SPECIALS TXA5-4, PA5, FMA5, and TVC-2 BASIC MODULE PACKAGE \$ 239 ppd OPTIONS:

NE64535 low noise downconverter . add \$ 30 Packaged TVC-4 downconverter ... add \$ 34

SEND SELF ADDRESSED STAMPED ENVELOPE FOR COMPLETE CATALOG AND ATV INFO. We have all your ATV needs: Antennas, Cameras, Repeaters, Video Monitors, Preamp, Linears, Test Equipment, and more. 19 years in ATV. Check, Money Order or Credit Card by mail. Credit Card orders call (213) 447-4565



A 600-MHz Universal Counter - you'll freq out over this one

	Function	Digit
Function Input	Frequency	Da
Pin 3	Period	D,
	Frequency Ratio	D,
	Time Interval	D,
	Unit Counter	D,
	Oscillator Frequency	D ₂
Range Input	0.01 s/1 cycle	D.
Pin 14	0.1 s/10 cycles	D,
	1 s/100 cycles	D,

E. E. Buffington W4VGZ 2736 Woodbury Drive Burlington NC 27215

This is truly a one-chip counter. The Intersil ICM7216 BIPI counter chip does it all. It is a frequency counter, period counter, frequency ratio counter,

time interval counter, or a

totalizing counter. It uses a

1- or 10-MHz timebase and

has facilities for an external

timebase input. For period

and time interval, the 10-

MHz timebase gives 0.1-mi-

the frequency mode, the user can select accumulation times of 0.01, 0.1, 1, and 10 seconds. With a 10-second accumulation time, the frequency can be displayed to a resolution of 0.1 Hz in the least significant digit. There is 0.2 seconds between measurements in all ranges.



Table 1.



Fig. 1. Counter section part of main board.

This universal counter chip has a high-frequency oscillator, a decade timebase divider, 8-decade data counter with latches, a 7-segment decoder, digit multiplexers, and 8-segment and 8-digit drivers which can directly drive large LED displays. The counter has a maximum input of 10 megahertz and, with the prescaler, this is extended to over 600 megahertz.

Intersil has an excellent 16-page data brochure describing this and other counters in a series. I have quoted from this brochure in many instances in this article. The A, C, and D versions of this counter have other characteristics and require a different circuit board layout, so beware.

Signal Conditioning

Front-end design is a

thorny problem since not enough gain means that there are many instances where a measurement cannot be made. Too much gain and you will be counting 60 Hertz, 120 Hertz, the local radio station, and whatever trash is there. I think the front end given here is a good compromise, with 50- to 100-millivolt rms sensitivity. The low frequency end has coverage to less than 5 Hz.

Multiplexed Inputs

The function, range, control, and external decimal point inputs are time-multiplexed to select the input function desired. This is achieved by connecting the appropriate digit driver output to the inputs. The input function, range, and control inputs must be stable during the last half of each digit output (typically 125 μ s). The multiplex inputs are active low for the common cathode ICM7216B.

Table 1 shows the functions selected by each digit



for the multiplexed inputs. You will note that some possible functions are not implemented in my circuit board.

Control Input Functions

Display Test—All segments are enabled continuously, giving a display of all 8s with decimal points. The display will be blanked if Display Off is selected at the same time.

Display Off-To enable the Display Off mode, it is necessary to input D3 to the control input and have the HOLD input at V+. The chip will remain in the Display Off mode until HOLD is switched back to V-While in the Display Off mode, the segment and digit driver outputs are open. During Display Off, the oscillator continues to run with a typical supply current of 1.5 mA with 10-MHz crystal and no measurements are made. In addi-



FUNCTION SI



tion, inputs to the multiplexed inputs will have no effect. A new measurement is initiated when the HOLD input is switched to V-. The Display Off feature is not implemented in my circuit board layout.

BIN

+5V

HOLD

AIN

FUNCTION IN

1-MHz Select — The 1-MHz select mode allows use of a 1-MHz crystal with the same digit multiplex rate and time between measurements as with a 10-MHz crystal. The decimal point is also shifted one digit to the right in period and time interval, since the least



RATIO-A78 (DI)

COUNT A (03)

OSCILLATOR FRED (D2)

INTERVAL A+B (D4)



significant digit will be in microsecond increments rather than 0.1-µs increments.

External Oscillator Enable - In this mode, the external oscillator input is used instead of the on-chip oscillator for timebase input and main counter input in period and time interval modes. The on-chip oscillator will



Fig. 5. Prescaler. This divide-by-one-hundred prescaler has a grounded-base input stage and gives good performance to over 450 MHz.

continue to function when the external oscillator is selected. The external oscillator input frequency must be greater than 100 kHz or the chip will reset itself to enable the on-chip oscillator.

Hold Input-When the hold input is at V+, any

measurement in progress is stopped, the main counter is reset, and the chip is held ready to initiate a new measurement. The latches which hold the main counter data are not updated, so the last complete measurement is displayed. When hold is changed to V-, a new measurement is initiated.

Reset Input—The reset input is the same as a hold input, except that the latches for the main counter are enabled, resulting in an output of all zeros.



Range Input – The range input selects whether the measurement is made for 1, 10, 100, or 1000 counts of the reference counter. In all functional modes except unit counter, a change in the range input will stop the measurement in progress without updating the display and then initiate a new measurement. This prevents an erroneous first reading after the range input is changed.

Display Considerations

The display is multiplexed at a 500-Hz rate with a digit time of 244 µs. An interdigit blanking time of 6 µs is used to prevent ghosting between digits. The decimal point and leading zero blanking have been implemented for right-hand decimal point displays. Any zeros following the decimal point will not be blanked. Also, the leading zero blanking will be disabled when the main counter overflows.

The ICM7216B is de-

Fig. 6(a). Main counter board.



Fig. 6(b). Component layout, main counter board.

signed to drive common cathode displays at peak current of 15 mA/segment using displays with $V_f = 1.8$ V at 15 mA. Resistors can be added in series with the segment drivers to limit the display current in very efficient displays if required.

To get additional brightness out of the displays, V + may be increased up to 6.0 V. However, care should be taken to see that maximum power and current ratings are not exceeded.

The display consists of 8 digits of multiplexed, common-cathode LEDs. A circuit board for the popular MAN 74 is given. Calculator displays are available at super savings — 8 or 9 digits on a circuit board for a dollar. You can't beat that!.

Crystal Characteristics

The circuit board has facilities for HC-33 or HC-18 crystal holders. The oscillator is implemented as a

high-gain complementary MOS inverter. An external 10- or 22-megohm resistor is used for biasing. The oscillator is designed to work with a parallel resonance, 10-megahertz crystal calibrated with 22 pF and having a series resistance of less than 35 Ohms. You should not try to save money here since the accuracy of your counter is directly dependent upon the accuracy of this oscillator. You should specify: A-T cut, optimum angle, and commercial quality and accuracy.

Prescaler

The prescaler uses a grounded-base amplifier driving an 11C90 600-MHz divide-by-ten followed by a 74196 divide-by-ten, resulting in a divide-by-100 circuit. The grounded-base amplifier yields a sensitivity of 20- to 50-millivolts rms and will respond to a 1-Watt handie-talkie several yards away with a quarter-wave antenna connected to the prescale input jack. Slightly better frequency response from the 74196 was obtained by using 5.7 volts. The voltage is reduced to 5 V for the 11C90 by the silicon diode. The prescaler draws about 200 mA from the 5.7-volt supply.



Fig. 7(a). Prescaler board.

Fig. 7(b). Component layout.



all six functions or all four ranges; this would simplify the front panel. The use of rainbow or ribbon wire will simplify the segment, digit, function, and range wiring.

Conclusion

Fig. 8. Display board.

were constructed, and good results were obtained with both. This is a fun project with little chance for problems. Circuit boards can be obtained from O. C. Stafford, 427 S. Benbow Road, Greensboro NC 27401. Write Ozzie at that address for a price list of both circuit boards and any other parts you're having trouble finding.

I will gladly correspond if you will send an SASE with your questions. I hate to be this way, but: no SASE, no reply!

Power Supply

As the total current is only 300 mA or so, the simple power supply shown will be OK. Turning off the prescaler results in a savings of 200 mA, so battery power is a reasonable option by using a 9-volt transistor radio battery for portable use.

Construction

This is where the satisfaction of home-brew electronics really comes forth. Your workmanship will be there for all to see, so a few dollars spent for a good-looking box will buy much as far as satisfaction goes. You may not want to implement Two of these counters

	Parts	s List	
Main Board		Prescaler	
Resistors	Qty.	Resistors	Qty.
100 Ω, ¼ W	2	100 Ω, ¼ W	1
3k Ω, 1/4 W	2	150 Ω, ¼ W	1
4.7k Ω, ¼ W	4	470 Ω, 1/4 W	1
10k Ω, 1/4 W	3	680 Ω, ¼ W	1
100k Ω, 1/4 W	5	Capacitors	
1 megohm, 1/4 W	2	.01-uF disc	5
10 megohm, 1/4 W	1	10-µF tantalum	1
5k (TO-5) pot	2	Other Parts	
Canacitore		1N4001	1
6 8 nF disc	2	2N5179	1
39-pF disc NPO	1	11C90DC	1
100-nF disc	2	SN74196	1
01-vE disc	4	4.7-uH coil	1
0.1-µF disc or tantalum	2	Country	
4.7-uF tantalum	2	Counter	
47-uF tantalum	2	Common-cathode display	(see text)
47-uF axial tantalum	1	Function switch	1P6T
50-pF variable	1	Range switch	1P4T
an printerio		Prescale switch	2P2T
Semiconductors		Hold switch	1P-NO
1N914	7	Reset switch	1P-NO
2N2222	2	1 MHz En. switch	1P1T
2N3823	2	Ext. osc. en. switch	1P1T
SN7413	1	Display test switch	1P-NO
ICM7216 BIPI	1	Coax jack (BNC)	4 each
10-MHz crystal	(see text)	Power supply	(see text)

SCR1000VHF—SCR4000UHF For Your New Repeater or Link System, Or, to Replace



2 Mtr. 220 MHz 450 MHz

• 30W Output.

- Low Noise/Wide Dynamic Range Front End for Excellent Sensitivity & IM Rejection.
- Sensitivity: 0.3uV Typ.
- 12 Pole IF Filter, & 8 Pole Front End Filter.
- Full Metering, Lighted Status Indicators/Control Push-buttons, Btry. Power Input, AC Pwr. Supply, CW IDer, etc. etc.

O

63

If you plan to install a new Repeater or VHF/UHF Link System (with or w/o Autopatch), you'll find that you can't find better quality, more reliable equipment, with all of the features and options you want at anywhere near our prices—if you can find it at all!

Your Old "Klunker"

Go With Spec Comm!

For many years now, we have specialized specifically in the field of VHF/UHF Repeaters, Links, Transceivers and all of the accessories to makeup a complete system. We now have hundreds of repeater and link systems operating successfully all over the world!

When you buy Spec Comm gear, you get the benefit of all of these years of experience—you get the best! And, years from now, you'll still be glad you went with Spec Comm!

Shown in Optional Cabinet



SCR1000

& SCR4000

ARE FCC TYPE

ACCEPTED

for Commercial

Services

30 or 70 WATTS on 2 Mtrs.!

Available just the way you want it—with Full Autopatch/Reverse Patch/Land-Line Control; Touch Tone Control of various repeater functions; "PL", "Emergency Pwr. I.D."; various Tone & Timer Units, etc. PLUS—the finest Duplexers, Cabinets, Antennas, Cables, etc. Our Repeaters are sold factory direct only, or through Foreign Sales Reps. Get your order in A.S.A.P.!

SPECIAUM

Commercial Business Radio Dealer Inquiries Invited

180 Day Warranty Call or write today and get the details!



UNIT FOR DEPERTED

Export Orders - Contact our International Dept.

1055 W. Germantown Pk., Dept. S10

COMMERCIAL MOBILE & **BASE TRANSCEIVERS** "" Spec Comm "Professional Communications Line"

136-174 MHz

Features

6 channels. 0.35 uV Rcvr. 8 Pole Crystal Fltr. Beautiful Audio—RX + TX. Provision for CTCSS. Very Reasonable Price!

PCL250 30 Wt. **Mobile Unit**

 "Super Rugged" Housing Solid 1/8" Thk. Aircraft Aluminum! 220-240 MHZ (Commercial Export and Amateur)

Very attractive woodgrain housing.

 Built-in AC Power Supply. Front Panel Status Indicator Lights. Optional Rcvr. Scanning Function Available.

PCL300 30 Wt. **Base Station**

FCC TYPE ACCEPTED - PARTS 21, 81, 90

SPEC COMM REPEATER BOARDS & SUB-ASSEMBLIES

These are Professional "Commercial Grade" Units-Designed for Extreme Environments (- 30 to + 60° C). All equipment assembled & tested. For 2M, 220 MHz & New 450 MHz!

SCR450

BOARD

SCR100 VHF Receiver Board

- Wide dynamic range! Reduces overload. 'desense', and IM
- Sens, 0.3 uV/12dB SINAD typ.
- Sel. 6dB @ ± 6.5 KHz. 110dB @ ± 30KHz. (8) Pole Crystal Fitr.)



FL-6 Rcvr. Front-End Preselector

- 6 Hi Q Resonators with Lo-Noise Transistor Amp (2M or 220 MHz).
- · Provides tremendous rejection of "out-of-band" signals w/out the usual loss! Can often be used instead of large, expensive cavity filters. Extremely helpful at sites with many nearby VHF transmiters to "filter-out" these 'out-of-band' signals. Voltage Gain: apx. 10 dB.

SCT410 XMTR. ASSY.

SCT110 VHF Xmtr/Exciter Board

- 7 or 10 Wts. Output. 100% Duty Cycle!
- Infinite VSWR proof
- True FM for exc. audio quality New Design—specifically for continuous rptr. service Very low in "white noise" Spurious – 70 dB. Harmonics – 60 dB. With .0005% xtal. BA-10 30 Wt. Amp board & Heat Sink, 3 sec. L.P. Filter & rel. pwr. sensor.

- 'S Meter' Output.
- Exc. audio quality! Fast squelch! w/0.0005% Crystal.

SCR100 Receiver Assembly

- SCR100 mounted in shielded housing
- Same as used on SCR1000
- Completely asmbid. w/F.T. caps, SO239 conn., AF GAIN POT, etc.

SCR450 UHF Receiver Bd. or Assy.

- Similar to SCR100, except with 12 Pole IF Fltr. & 8 Resonator Front End Fltr.!
- Discriminator & Deviation Mtr. Outputs
- Totally New Advanced Design!





SCAP Autopatch Board

- Provides all basic autopatch functions.
- 3 Digit Access; 1 Aux. On/Off function, Audio AGC; Built-in Timers; etc.
- 0/1 Inhibit bd. also available.
- Write/call for details and a data sheet.

RPCM Board

- Used w/SCAP board to provide "Reverse Patch" and Land-Line Control of Repeater
- Includes land line "answering" circuitry

 Selectivity: -20 dB @ ±2.0 MHz; -60 dB @ ±6 MHz (typ.).

ID1000 Automatic Base **Station CW Identifier**



- For Repeaters, Base Xmtrs., etc.
- Fully Automatic ID timing & xmtr. keying.
- Convenient Front Panel Controls. Many Deluxe Features!
- AC or DC powered
- Easy to install! 19" Rack Mount
- Reasonable Price! Ask for Data Sheet

PSM-1 Repeater Power Supply Mod Kit

- For SCR-1000 or SCR-4000
- Replaces Darlington Pass Tr.-for improved reliability
- Includes new overvoltage "Crowbar" shutdown circuit.
- Complete kit, w/assembled PC board. \$19.50 + \$2.50 SH.

ID250 CW ID & Audio Mixer Board

- Adjustable ID tone, speed, level, timing cycle.
- 4 Input AF Mixer & Local Mic amp.
- COR input & xmtr. hold circuits.
- CMOS logic; PROM memory—250 bits/channel.
- Up to 4 different ID channels!
- Many other features Factory Programmed

SCT110 Transmitter Assembly

- SCT110 mounted in shielded housing
- Same as used on SCR1000
- Completely assmbld. w/F.T. caps, SO239 conn.
- 7, 10 or 30 Wt. unit.

SCT410 UHF Transmitter Bd. or Assy.

- Similar to SCT110, 8-10 Wts.
- Avail. w/ or w/o OS-18 Super High Stability Crystal Osc./Oven.
- BA-40 30W. min. UHF Amp. Bd. & Heat Sink.

TTC100 Touchtone

Control Board

- 3 digit ON, 3 digit OFF control of a single repeater function. Or, (optional) 2 functions (2 digits ON/OFF each).
- Can be used to pull in a relay, trigger logic, etc.
- Typically used for Rptr. ON/OFF, HI/LO Pwr. P.L. ON/OFF, Patch Inhibit/Reset, etc.
- Stable, anti-falsing design. 5s Limit on access.
- For Add'l Function(s)—Add a "Partial TTC" Board.

COMMUNICATIONS CORP. Send for **Data Sheets!** ✓ 68

Norristown, PA 19401 (215) 631-1710 -



Richard C. Force WB1ASL Box 78 Greenfield NH 03047

Top-Banding the DX-60B – part II: a companion vfo

Part I of WB1ASL's 160-meter conversion for the DX-60B appeared on page 44 of the July 1980 issue of 73.

recently converted the Heathkit® DX-60B to 160 meters. The transmitter works fine on that band, with one drawback: It is crystal controlled. This fact adds inconvenience to the operation even though there are four crystal positions provided. The ability to move at will around your allocated portion of the band not only eases operation, but also cuts down on operator frustration caused by unanswered responses to CQ calls. With many operators using transceivers nowadays, they do not bother to tune after a call, but expect a response only on their own frequency. After many such unanswered calls, I decided to add a vfo to my newly-converted rig. The DX-60B transmitter was originally designed to be used with the Heathkit HG-10B vfo on 80-10 meters. In fact, the unit comes with a vfo accessory power socket provided on the back, as well as a vfo input and a vfo position on the crystal switch. The accessory socket has pins for ground, 6.3 volts ac, 300 volts, keying bias, and a 110-volt ac line for powering a relay for antenna change-over.

power and switching circuits provided.

Because the HG-10B is a vacuum tube vfo, it seemed only reasonable to use vacuum tubes in the new design. The tubes I selected are, however, very easy to obtain even in this age of solid state.



Photo A. Front view of the vfo showing use of the ARC-5 cabinet. The front is covered by a coppercial plate for appearance's sake and for dial mounting.

With these facts in mind, I decided to use the existing provisions and design a vfo similar to the HG-10B to be used with the DX-60B on 160 meters. This vfo would be compatible with the

The circuit is straightforward and operates on the fundamental frequency of 1.8-2 MHz. The 6AU6 tube operates as a Hartley oscillator on this fundamental frequency. Grid-block keying is used, with the keying bias provided from the accessory socket of the DX-60B. The bias, which is applied to the grid of the 6AU6 through the NE-2 neon lamp and R2, is sufficient to cut off the oscillator during standby. When this bias is removed through keying the transmitter, the oscillator resumes oscillation.

The 6C4 tube acts as a buffer. This tube, by the way, can be replaced by one-half of a 12AU7 or 12AT7 or even by a 6J6 if the 6C4 cannot be found. The circuit helps to maintain the stability of the oscillator by establishing a fixed load for the oscillator output.

Of course, the 0A2 tube is a voltage regulator to ensure that the voltage to the vfo remains at 150 volts.

As can be seen from the photographs, I made use of a surplus ARC-5 transmitter. I used the chassis, cabinet, and the coil form from the oscillator section. The coil form was used for L1 in the new vfo. All frequency range models of the ARC-5 use the same coil forms, so any ARC-5 unit will have the needed form.

This coil form is made of ceramic, which is a very good material for the winding of oscillator coils. Another coil form and chassis can, of course, be substituted if you do not have a surplus ARC-5 transmitter lying around the house. (They're getting rarer all the time, but are still available from some surplus outlets-although at a cost much too prohibitive for an oscillator coil and a cabinet.) Be very selective about the coil form material to ensure stability in the transmitter. Ceramic is best, but whatever material you use for the form, make sure the wire is wound tightly over the form and cemented in place with Q-Dope. Avoid toroid cores! They are very susceptible to frequency drift, especially in vacuum tube environments where there can be a high degree of change in the ambient temperature. Also avoid slug-adjustable core forms. If you must change the diameter of the coil, experiment with the number of turns until you get the right resonant frequency range. You also can resort to a coil chart or coil design formula, but in all cases keep the coil Q quite high.

of extra space in the ARC-5, so a different chassis and cabinet could actually reduce the size considerably.

Mechanical stability in construction as well as heat shielding are, of course, of paramount importance as they are in all oscillator construction. By mounting the coil below the chassis, it is shielded from drafts and variations in temperature after initial warm-up.

A sturdy bracket was fabricated for the mounting of capacitor C3. This helps ensure that an accidental jarring of the cabinet will not change the frequency of the oscillator. Also, keep component leads as short as possible for the same reason and to cut down on lead inductance.

All frequency-determining capacitors should be either silver mica or polyester types for stability.

The inclusion of the 0A2 regulator keeps the voltage to the oscillator rock steady, which is needed for stability purposes.



Photo B. Top view of the vfo. The copperclad board is used to cover holes in the chassis and to mount vfo parts. The 6AU6 tube is in the front, the 6C4 is in the center, and the 0A2 is in the rear.

zero beat. The amount of drift is infinitesimal.

After constructing the vfo, tune-up and testing are simple matters. First, check all your wiring to make sure it is correct. Especially check to see that the power connections are wired to the power plug correctly. If you are like most of us, you probably haven't used octal sockets in years and the numbering of the pins might not be fresh in your mind. Check, and check again. Tubes are expensive, and they don't like to have 110 or 300 volts on their filaments.

ment can be made before the vfo is connected to the DX-60B. If a grid-dip oscillator is available, the vfo tuned circuit can be dipped to the 160-meter band. Do this by setting the main vfo tuning capacitor, C3, to the center of its range. Set the grid-dip oscillator to 1.9 MHz. With the grid-dip oscillator coil coupled to L1, tune trimmer capacitor C2 for a dip on the meter. Now the oscillator is tuned for approximately the center of the 160-meter band. (If you do not have a grid-dip oscillator, an alternative method follows.)

As for the chassis, you can see from the photographs that there is plenty By following these good construction practices, I can, after initial warm-up, zero-beat the vfo to a stable receiver and come back an hour later and still be on

One preliminary adjust-

After all is checked out,



Fig. 1. Vfo schematic.



Photo C. Bottom view of the vfo, showing coil L1 at the left center and C3 mounted on the bracket at the left. As can be seen, there is an excess of space.

plug the vfo power cord into the DX-60B power-accessory socket and the rf output from the vfo into the vfo input socket on the back.

Turn the Function switch to "Standby," check to see that the tubes in the vfo are lighting, and let the unit warm up for at least onehalf hour.

Set the controls on the front of the DX-60B as follows: Drive Level to 0, Xtal to vfo, Drive Tune to 1, and Band to 80 (which is now the 160-meter position). the center of the 160-meter band. Run a wire from the receiver's antenna terminal to a point near the vfo to ensure the receiver will pick up the signal from the vfo.

Now, turn the Function switch to the "Tune" position. Tune the vfo main tuning capacitor, C3, through its range while listening for the signal in the receiver.

If the signal is not heard and the receiver is a general coverage receiver, leave the vfo capacitor set to the center of its range and tune the receiver both above and below the 160-meter band until the signal is found. If the signal is higher than the band, capacitor C2 will have to be adjusted to add more capacitance to the circuit to bring the oscillator within the band. If the signal is below the band, C2 will have to be adjusted to decrease the capacitance.

If the signal is not heard and the receiver only covers the 160-meter band, set capacitor C3 to the center of its range and the receiver to 1.9 MHz. Adjust capacitor C2 until the signal is heard. If it is still not heard, keep alternating capacitor adjustments on C2 and C3 until it is heard.

If the signal cannot be found at all, either the oscillator is not oscillating or its frequency range is completely out of the range of the receiver. Check all components and voltages. If an absorption wavemeter is available, use it to determine if the oscillator is oscillating. Once it is determined that the oscillator is functioning outside the desired frequency range, a few minor changes will have to be made to the oscillator to bring it into line. This will entail either increasing the amount of capacitance in the tuned circuit by adding a small silver mica capacitor across C1 to lower the frequency, or by removing turns from coil L1 to raise the frequency. This situation should occur only if L1 was redesigned incorrectly because of the use of a different coil form. After the signal is found, one way or another, listen to the signal for purity of tone (no hum or hash). Turn the vfo off and on by turning the Function switch to "Standby" and then to "Tune" again several times to make sure oscillation begins immediately. After these observations, check for drift by zero-beating the signal on the receiver (with the receiver vfo turned on) and letting the oscillator sit for awhile to see how far it drifts from zero beat. A better alternative method to check drift would be to use a frequency counter. If excessive drift occurs, a bad capacitor or L1 may be the cause. Check voltage stability and drafts also.

If all checks out all right, you may then proceed to the next step, that of calibration. Set the main tuning capacitor, C3, to maximum capacitance. Tune the receiver to the bottom of the 160-meter band. Using trimmer capacitor C2 only, zero-beat the oscillator to the receiver. Mark the dial. Now, by tuning the receiver up the band to set intervals and adjusting the main vfo tuning capacitor, C3, to zero beat and then marking the dial, the vfo can be calibrated.

After calibration, final testing is at hand. With the antenna output of the DX-60B fed into a dummy load, set the vfo to an allocated part of the band. Proceed to tune up the DX-60B. If you do not get enough grid drive, check the buffer stage in the vfo.

If all is operating correct-

The next step will need the services of a good, accurate communications receiver which covers the 160-meter band. Set the receiver, after warm-up, to

Parts List

C1—270-pF polystyrene or silver mica
C2—3-30-pF mica trimmer
C3—30-pF air variable (Hammarlund HF-30)
C4—100-pF polystyrene or silver mica
C5, C6, C8, C9, C1102-uF disc ceramic
C7001 uF
C10-150 pF
L1-35 turns #18 AWG enamel on a 1-3/8"
ceramic form (see text)
R1-47k, 1/2 W
R2, R4-150k, 1/2 W
R3-33k, 1/2 W
R5-1000, 1/2 W
R6-2700, 1/2 W
B7-10k, 1/2 W
B8-5.6k, 7 Watt
BEC1-2.5-mH rf choke
NF-2-Neon Jamp
HEL HOOH MINP

ly, you should have no trouble tuning up the DX-60B. It should tune exactly as it did when it was crystal-controlled.

To zero-beat a signal or to locate your frequency, simply turn the Function switch to "Tune" with the Drive Level control turned down and use the vfo main tuning capacitor to zerobeat the signal.

With the use of the vfo, your number of QSOs should increase dramatically. No longer will the other guy have to look for you. You'll be right there on frequency with your DX-60B.

This completes the second phase of my conversion of the DX-60B to 160 meters. It has been great fun doing the conversion and operating on the "top band." I hope these two pieces will give many an opportunity to operate on this interesting segment of the amateur spectrum.

DOUBLE YOUR PLEASURE

Versatility Plus . . . Work Both 2 and ¾ Meters With Yaesu's New FT-720R

The FT-720R series is a compact VHF/UHF mobile transceiver that harnesses the incredible power of the microprocessor to bring you top-operating flexibility. Start with the FT-720R Control Head, then add either the 10 watt FT-720RU 440 MHz or 25 watt FT-720RVH 2 meter RF Deck. You can clamp the Control and RF Deck together or use an optional remote cable to hide the RF Deck. The best news is still to come! By using the optional S-72 Switching Box and two remote cables, you can use a single Control Head for operation with both the 440 MHz and 2 meter decks, giving you a high-performance two band FM station for your car or home. Compare the features below, then ask your dealer for a demonstration of the fabulous FT-720R series. . . another winner from the performance leader . . . Yaesu.

- Four simplex/repeater memory channels, plus receive-only memory channel.
- Scanning controls on microphone with search for busy or clear channel.
- Optional 32 tone CTCSS module for accessing private repeaters.
- Colorful, easy-to-read LED power output/S meter.
- Built-in 1800 Hz tone generator.

- Priority channel with search-back feature.
- Pause feature that holds, then restarts scan, on busy or clear channels.

* YAESU

- Digital display of last four digits of operating frequency.
- Single Control Head may be used for operation on both 440 MHz and 2 meters via optional switching box and remote cables.
- Extremely compact size, light weight.

Specifications	FT-720RU
Frequency Coverage	440.00-449.975 MHz
Synthesizer Steps	25 kHz
Power Output	10 watts
Sensitivity	0.5 uV for 20 dB
	quieting
Selectivity	±12 kHz (6dB)
	±24 kHz (-60 dB)
NOC.	
	Specifications Frequency Coverage Synthesizer Steps Power Output Sensitivity Selectivity

Price And Specifications Surject To . Change Wittesur Nation GR Oblighton

> YAESU ELECTRONICS CORP., 8851 Walthall Way, Paramount, CA 90723 @ (213) 633-4007 YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246

Mark Oman WAØRBR 528 Deines Ct. Ft. Collins CO 80525

An Amp for QRPp Addicts - build this resistive step attenuator for low, low power work



Internal view of QRP Amp showing switches and connections.

fter having enjoyed QRP operation and its 2-Watt world for a period of time, it was decided that a new frontier was needed for a challenge. An amplifier was designed and constructed which provided 25 Watts on 160 through 10 meters. Increased signal reports did result, but just about anything you can work on 25 Watts can be worked on 2 Watts. So I felt that a new and somewhat different kind of challenge was still needed-why not an amplifier (an "inverse amplifier')? Rather than increasing the input signal. it "inversely amplifies," or decreases, the input (in a logarithmic manner).

The QRP Amp definitely re-instills the challenge into the sometimes repetitious world of ham radio. It also can be used to allow QRP/ QRPp operation with medium-powered transceivers. Better yet, it can be constructed and in use in a few hours with locally purchased parts, for \$15 or less. If you have slide or toggle switches in the junk box, then the price is reduced even further. It requires no tune-up or adjustment and is nearly guaranteed to work the first time.

The Amp is actually a step attenuator which provides from 3 to 39 dB of attenuation to your already low-power signal. What this means is that your 2-Watt signal, after passing through the QRP Amp, now becomes anywhere from 1 Watt down to about 200 microwatts! Twenty milliwatts of output power can and does produce plenty of solid contacts, and it opens up a whole new world to ham radio.

Since the QRP Amp is a resistive step attenuator, it requires no tuned circuits, no active circuits, and works on any mode. Referring to Fig. 1, it can be seen that four switches are used



View of QRP Amp shown with 10 dB of attenuation and switched IN.

in conjunction with half-Watt standard value carbon resistors to produce the necessary attenuation. The double-pole, double-throw switches are set up to produce 3, 6, 10, and 20 dB of attenuation by either switching in the resistors or bypassing them. These switches can be miniature toggle type or, to reduce costs, miniature slide switches. The desired attenuation is selected in an "additive" manner. To select 13 dB of attenuation, for example, switch in the 3-dB and 10-dB switches. A DPDT 12-V relay purchased at Radio Shack is used to automatically switch the attenuator out during receive. It is controlled by the transceiver driving the Amp. Switch S1 is used to bypass the Amp, if desired. The Amp can be built in just about any enclosure available to the builder. Small coax (RG-174/U) is used for rf runs between connectors, the relay, and the switches. The resistors should be soldered directly to the switch contacts with their leads kept short to minimize their inductance. Spray paint and dry transfer lettering add a final touch to the simple project.

tained from the driving transceiver. Run a lead from the control side of the transceiver relay to a plug to mate with J1. Verify that K1 closes when your transceiver is in transmit and S1 is in the IN position. Actual attenuation values were verified to be within .5 dB of the calculated values with a Hewlett-Packard 180 oscilloscope. After you have verified that K1 and S1 are operational, apply drive to the box (with dummy load attached). With no switches IN (no attenuation), you should see the same output power as input power. Switch in 3 dB and the output should be decreased by one-half. Remember that most, if not all, power meters become



View of QRP Amp shown with 13 dB of attenuation and switched IN.

inaccurate below 1 Watt and are usually unreadable below 100 mW, so don't fret when the needle doesn't budge with 10 dB or more of attenuation switched in.

If problems arise, about the only things that can be wrong are soldered connections or misplaced resistors. Also, recheck all wiring between switches, connectors, and relay. For those who want to use a 200-Watt transceiver, an additional 20-dB attenuator is needed to prevent damage. Use high wattage (20 Watts or more) resistors

in that portion of the attenuator.

Operation

Operating the QRP station, a portion of which was described in the December, 1978, issue of Ham Radio, has been greatly enhanced using this project. Before describing the results you can expect, you will be interested in a few observations concerning milliwatt operation. Assuming you are using a 2-Watt transmitter to drive the Amp and have switched in 20 dB attenuation, your output will

The only setup required is to supply +12 V and a relay control. Both can be ob-



Fig. 1. Schematic, QRP Amp. QRP Amp is a classic pi-type step attenuator using four switches to provide from 3 to 39 dB of attenuation. With switches as shown, 16 dB of attenuation would exist when S1 is switched to "IN" and the transmitter is keyed. J1, J2-SO-239 rf connector. J3, J4-Phone or phone jack. K1-DPDT 12-V relay. S1-SPST miniature. S2-S5 - DPDT miniature slide or toggle. All resistors 1/2 Watt or greater.

DEAL WITH #1!

CARLOAD INVENTORIES • ROCK BOTTOM PRICES 24-HOUR SERVICE

LINES:

AEA A AVANTI B ASTRON B ALLIANCE B

ALPHA CUSHCRA BEARCAT COLLINS BIRD CDE BENCHER DRAKE

CUSHCRAFT DENTRON COLLINS HY GAIN CDE HUSTLER DRAKE ICOM KLM MOR GAIN KENWOOD MIRAGE MICROLOG MFJ MINI-PRODUCTS NYE

PALOMAR ENG. REGENCY SWAN TEN TEC UNIVERSAL UNARCO-ROHN VIBROPLEX



HesterCord 1754

1 52

be 20 mW. This power level is 30 mW below the FCC specification for total harmonic radiation. Furthermore, a typical SSB transceiver running 200 Watts output might have 40 to 50 dB attenuation of carrier and opposite sideband. The carrier output will then be 2 to 20 mW, the power used with the Amp to make contacts.

A quick calculation re-



Fig. 2. 20-dB attenuator to enable 100-200-Watt transceiver to be used with QRP Amp. Resistors should be 20 Watts for 50-Watt output, 40-50 Watts for 100-Watt output, and 80-100 Watts for 200-Watt output. Use parallel combinations of smaller wattage resistors to reach these wattage ratings. veals that if you can obtain an S9 report with a 2-Watt signal (easy!), then, theoretically, assuming no noise or QRM, an S1 signal would be produced by less than a 200-microwatt signal. This is my present goal with the QRP Amp.

Naturally, the purist will balk at the idea of wasting energy by dissipating power in a resistor, but it is the only practical way of generating QRPp levels. Single transistor rigs which would normally generate these levels are subject to chirp, FMing, drift, and a lack of convenience. With the Amp and your normal QRP transceiver, you retain those conveniences and avoid the aforementioned maladies. It also considerably reduces the expense of QRP operation if you already own a regular transceiver.

Both SSB and CW modes are used at my station, with SSB slightly preferred because an in-depth explanation can be made of the low-power experiments. This way, the other station invariably becomes enthused and he, too, wants to see at just what level of power he can hear you.

Contacts have been made, however, with stations who become indignant when told that your power level is 10 mW. Apparently, this pricks their conscience about that shiny, expensive linear sitting in front of them!

During the past three months, 10 states have been worked in casual operation, mostly on 10 meters, using 10 mW of output. A number of contacts have been made in Japan, Hawaii, Canada, and Mexico using 100 mW output. 100 mW on 10 meters provides plenty of in-USA contacts. Even 20 meters can be used for 10- to 20-mW CW contacts. Incidentally, the antennas used at my station are a dipole on 80/40 meters and a 2-element quad on 10-20 meters.

As with any QRP operation, patience is the key word. Not every station called will answer, with the ratio becoming worse as output power is reduced. With a little practice, you'll become familiar with the conditions and signals that will produce a solid contact.

The QRP Amp has provided the challenge that was sought. When you contact a station that is using a linear amplifier, you can reply that your newest homebrew accessory is a logarithmic de-amplifier, built for less than \$15. That should make for plenty of interesting conversation! Plus, there is fun in working across the continent on a power level most rigs use to generate spurious harmonics!



....on inexpensive paper too. Our latest addition, the MICROLOG companion printer for the ATR-6800, plugs in directly for easy 'hard copy' of your QSO's, messages, programs, etc. When the tape interface isn't enough, our printer is ready on keyboard command. Complete system for CW/RTTY: ATR-6800, video and printer \$2,445, without printer \$1995, printer alone \$495. We're always up to something new here at MICROLOG CORPORATION, 4 Professional Drive, Suite 119, Gaithersburg, Maryland 20760. Telephone (301) 948-5307.



1 51

Innovators in Digital Communications

Terry Conboy N6RY 2631 S.W. Orchard Hill Place Lake Oswego OR 97034

The Center-Fed Bizarre — would you believe an indoor antenna for 80?

More and more of us find that the acreage for that dream antenna farm with phased verticals, rhombics, and giant monoband yagis just isn't available on a lot size within the bounds of our meager earnings. Even when a tidy home on a reasonably roomy lot is found at an attractive price, city ordinances or deed restrictions may make it impossible to erect tall towers or any outside antennas at all. My situation falls into the second category. Not even TV antennas are permitted in my area.

After two years at this address, I finally decided that operating only on two meters with a magneticmount mobile antenna in a window wasn't my idea of the ultimate ham station. I grew up as a ham on the 80-meter band and wanted to keep in touch with the friends that I had made over the years. I did have access to the club station at my place of business, but





Fig. 1. A common configuration for a VLF antenna using the guy wires for top-loading capacitance.

72 73 Magazine • December, 1980


that often proved to be an inconvenient arrangement.

There seemed to be three reasonable alternatives. Put up an inconspicuous outside antenna, load up a flagpole, or try to put something in the attic. The outside antenna was ruled out, since a leading figure in the local homeowners association was my next-door neighbor. Decent flagpoles aren't cheap, and I was advised by a lawyer that I still might be subject to legal action in which it would cost me hard-earned dollars to prove that it was a flagpole. So I crawled up my ladder and made friends with the spiders and the insulation.

Mobile Attenuators

I had acquired a wellrespected mobile antenna with a 75-meter loading coil a few years ago, but never used it. As a result, my first attempt at an indoor antenna was to erect it in the center of the attic. Several wires were run around the rafters for a ground system. I was pleased when the swr meter read 1-to-1 near the frequency of interest. I was not at all pleased when most of the stations that I tried to work were barely capable of moving my normally hyperactive S-meter and seldom able to copy me. Some rough calculations showed that I really couldn't expect more than 2% efficiency, since the radiation resistance of the antenna had to be less than 1 Ohm and the other 49 Ohms came from the resistance in the loading coil. I was generally leery of vertically-polarized antennas in the attic anyway. There were a large number of metal vent pipes and chimneys that were nearby. Most of them had friction joints which could certainly create harmonics or at least be lossy, further soaking up the meager radiated energy.



Fig. 3. Measured impedance of the attic antenna. Reference impedance for the Smith chart is 50 Ohms.

Taking a Lesson from the VLF Boys

Compact antennas are nothing new in high-power transmitting installations for use below 100 kHz. A quarter wavelength is well over 2000 feet in this part of the spectrum. Looking at the types of antennas used showed the popularity of top loading. This is no surprise. Placing the loading away from the feedpoint helps keep the base impedance up to reasonable values.

As a rough rule of thumb, the radiation resistance of a base-loaded antenna

changes as the square of its length, when the antenna is less than a quarter-wavelength tall (for a vertical). For top-loaded antennas, it changes almost directly in proportion to the length. For example, if the antenna is one-fifth of full size, the base-loaded antenna impedance will look like about one twenty-fifth of its full-size impedance, or about 2 Ohms. The toploaded antenna will be about 10 Ohms. For very short antennas, this can give a significant increase in efficiency and bandwidth.

One popular configura-

tion for a VLF vertical antenna is shown in Fig. 1. The top guy wires are used as a capacity hat to increase the electrical length of the radiator. I saw no reason why this configuration couldn't be adapted to a balanced horizontal arrangement, since I wanted to avoid vertical radiators.

Wire Everywhere

My attic is about 24 feet wide across the highest part, which is where I wanted to place the main radiating portion of the antenna. The loading wires were bent back at about a 55 degree angle from the



Fig. 4. Schematic of the impedance-matching network used to feed the antenna. This network is at the transmitter end of about 100 feet of RG-8 cable.

flat-top section. I didn't want to run them at right angles, since the walls of my house are stucco and contain wire mesh that could create problems.

As a starting point, I used a total of a half-wavelength of wire. I had to bend the ends of the loading wires back toward the feedpoint to get it to fit. The final configuration is shown in Fig. 2. As you can see, the total length of the wire exceeds a half-wavelength by about one-third. It is resonant near the center of the 80-meter band.

It should now be obvious why this antenna received its name. When I first put it on the air, I tried in vain to explain its configuration to W7ZUL. When it became apparent that he couldn't understand it without a picture, I told him that it was too bizarre to explain. He naturally replied, "Oh, so you're using a center-fed bizarre."

The wire used in the antenna was plastic-insulated #18 with stranded conductors. Three of these wires were laboriously braided together to increase the apparent conductor diameter in an attempt to reduce resistive losses and to help broadband the antenna. The three wires were kept separate everywhere but at the feedpoint. There are three joints at the ends of the radiating portion where the loading wires connect.

Single-wire conductors could have been used just as well, the larger the better. I used what I had available.

Care and Feeding

Upon first inspection of the antenna, I was somewhat alarmed at the magnitude of the feedpoint impedance. Using a noise bridge that was capable of measuring resistance and reactance through a known length of RG-8 coax, I found 5 Ohms of radiation resistance. That's right, the swr was 10 to 1. The Smith chart in Fig. 3 shows the results of my measurements.

The actual impedance of the antenna may be even less than 5 Ohms. I did not take into account the loss of the feedline when the measurements were made. I had predicted that the radiation resistance would be closer to 10 Ohms, but the effect of nearby household electrical wiring and the fact that the antenna was only about 0.1 wavelengths above ground could easily lower the impedance. Since the loading wires do not run at a 90-degree angle to the radiating wire, a partial cancellation of the field also results in a lower antenna impedance. In an antenna of this type, a high impedance is sure to indicate undesirable losses.

No one would think of trying to feed such a mismatch directly from the output of his transmitter. Almost any of the "universal transmatches" will reduce this to an acceptable level.

The matching network I use is shown in Fig. 4. The capacitors are from old ARC-5 equipment. They are adequate for power levels up to 400 Watts PEP or CW input. By the use of a logging scale on the capacitor dials, I can rapidly QSY anywhere within the 80-meter band and still present a 50-Ohm load to my transmitter.

A second method of matching may appeal to those of you who are squeamish about high swrs. There are several nice wideband impedance step-up transformers available that are designed for use with mobile antennas. Using one of them will raise the impedance to nearly 50 Ohms so that the main feedline operates with a reasonably low swr. The catch is that this will only allow operation over a narrow band of frequencies, since the antenna has a fairly high Q.

ATTENTION MOBILE HAMS IS METER MOBILE TRANSCEIVER CW & USB NCG 15SB



THE QRP RIG WITH THE **BIG RIG SOUND** ACTIVE NOISE BLANKER—RF GAIN—CW SWITCH— SQUELCH—MIC GAIN—DIGITAL FREQUENCY DISPLAY—HI/LO POWER SWITCH—13.8 VDC 5A POSITIVE OR NEGATIVE GROUND.

See your dealer for a demonstration.

DEALER INQUIRY INVITED.

NEW 438 to 450 MHz PLL mobile Memory-Scan 1275 N. GROVE ST. ANAHEIM, CALIF. 92806 (714) 630-4541

There certainly are hams who consider a 10-to-1 swr unthinkable. There is salvation for you, but first give thought to this: At 4 MHz, 100 feet of RG-8 (or RG-213) has a loss of about 0.3 dB and the additional loss caused by a 10-to-1 swr is 1.0 dB. A total of 1.3 dB or about 25% of your power is lost in the coax. Foam dielectric coax will be about 1.2 dB, and shorter lengths give proportionately less loss.

On the Air

Just because it looks funny, it doesn't mean that it works that way. Stations report respectable signals. Comparisons were made with one local station whose transmitter power is about 3 dB below mine. He uses a normal inverted vee about 40 feet high. No perceptible differences were noted in signal strength, both on close-in (30-mile) and longer-haul (1000-mile) paths. I found this hard to believe at first, too. However, repeated comparisons and several months of successful operation bear out the solid reliability of this indoor radiator.



AUTOMATIC SWR & PEAK READINGHF POWER METERMODEL APM-1H\$99.95Frequency Coverage:1.8 - 60 MHzInput Impedance:50 - 52 ohmsPower Range:0 - 200, 1000, 2000W

SWR Range:	1:1 - 10:1
Power Modes:	Average & PEP
Accuracy:	±10%
Power Requirements:	117 VAC 60 Hz



AUTOMATIC SWR & PEAK READING VHF POWER METER MODEL APM-1V \$99.95

Frequency Coverage:	50 - 150 MHz
Input Impedance:	50 - 52 ohms
Power Range:	0 - 20, 200W
SWR Range:	1:1 - 10:1
Power Modes:	Average & PEP
Accuracy:	±10%
Power Requirements:	117 VAC 60 Hz



SWR & POWER METER FOR HF/VHF MODEL PM-3HV \$54.95

Frequency Coverage: 3 - 150 MHzInput Impedance: 50 - 52 ohmsPower Range: 0 - 20, 200, 1000WSWR Range: 1:1 - 5:1Accuracy: $\pm 10\%$ Power Requirements: 12 VDCIlluminated meters for mobile operator





SWR & POWER METER FOR HF/VHF MODEL PM-4HV \$44.95

Frequency Coverage:3 - 150 MHzInput Impedance:50 - 52 ohmsPower Range:0 - 20, 200, 1000WSWR Range:1:1 - 3:1Accuracy: $\pm 10\%$ Power Requirements:NoneVelcro for mobile mounting



MIKE COMPRESSOR WITH LINEAR AMPLIFIER MODEL MCLA-1 \$89.95 Compressor Section Frequency Range: 100 – 10000 Hz Distortion: Within 0.4% Linear Amplifier Section Frequency Range: 300 – 10000 Hz Gain: 25 dB (12V) Power Requirements: 9 VDC



FLAT RESPONSE SWR & POWER METER FOR HF MODEL PM-2H \$89.95

1.8 - 60 MHz
50 - 52 ohms
0-200, 1000, 2000
1:1 - 3:1
±10%
None



FLAT RESPONSE SI	WR & POWER METER
MODEL PM-2V	\$89.95
Frequency Coverage:	50 - 150 MHz
Input Impedance:	50 - 52 ohms
Power Range:	0 - 20, 200W
SWR Bange:	1:1 - 3:1

Accuracy: ±10% Power Requirements: None

AKIGRIUR 1d By:

Manufactured By: AKIGAWA ELECTRONICS CORPORATION

Distributed Exclusively By: MACAW ELECTRONICS INCORPORATED P.O. Box 66, Carlsbad, Calif, 92008 Phone (714) - 434-1078 Telex 181743 MACAW CSBD



SWR & POWER MET	ER FOR MOBILE
MODEL PM-5H (HF)	\$49.95
MODEL PM-5V (VHF	=) \$49.95
Frequency Coverage:	1.8 - 30 MHz (PM-5H)
	50 - 150 MHz (PM-5V)
Input Impedance:	50 - 52 ohms
Power Range:	0 - 20, 200 W ±10%
Power Requirements:	12V DC
Complete with directi	onal coupler unit

(Prices are suggested list and are subject to change without notice.)



ACTIVE AUDIO FIL	TER
MODEL AAF-1	\$89.95
Filters:	Band Pass+Notch
Center Frequency	
Shift Width:	200 - 2500 Hz
Input Impedance:	8 - 600 ohms
Output Impedance:	8 ohms
Output Power:	1W max.
Power Requirements:	9 VDC 150 mA



PRESELECTOR MODEL PR-1	\$109.95
Frequency Coverage: Gain:	3 – 30 MHz 20 dB at 7 MHz, Variable
RF Attenuation: Input/Output	-20 dB & -10 dB
Impedance: Relay Power	50 – 75 ohms
Capability: Power Requirements:	200W CW 117 VAC 60 Hz

✓ Reader Service—see page 226

Signalcrafters Presents The Most Advanced Automatic Computing Power Meters In Amateur Radio!



MODELS 31 and 32*

Our portable Models 31 and 32 feature the same state-of-the-art technology that is incorporated in their Big Brother, the Model 30. Never again will you have to bother with SWR "calibrate" controls and switches! Signalcrafters' custom integrated circuit makes power and SWR measurement a "handsoff" operation by automatically computing SWR. The result is unparalleled accuracy and ease of operation.

FEATURES:

 CUSTOM IC—Computes SWR from the level sensed on the transmission line independent of the power level. This analog computer operates over a range of only one watt to the full scale of the meter with unequaled accuracy.

SCANNERS:

Introducing a scanner for the ICOM IC2AT. KENWOODTR7400A, TR7600, & TR7625, TEMPO (51, 51A, 52, 55), KDK 2015R, KDK 2016A, ICOM IC22S, MIDLAND 13-510,13-513, CLEGG FM-28, COMTRONIX, YAESU FT227R

AED continues to expand its line of quality scanners.

All of AED's scanners are custom designed to install completely inside of their respective rios.

Installation is simple. Unlike other competitive products all AED scanners are designed so that it is totally unnecessary to cut any wires inside your rig during installation.

All P.C.B.s are silk-screened and tin plated for easier and more effective soldering

• The kit comes complete with all parts and a detailed instruction manual including schematics.

In the scanner OFF mode the rig operates normally. In the scanner ON mode the scanner locks on an occupied frequency, pauses for a preset time (about 5 sec.) and then resumes scanning (except 225).

The frequency being scanned is displayed on the digital readout (except 225) ICZAT and lempo).

This gives you the ability to eavesdrop all over the band without lifting a finger. When you hear something interesting, you flip the switch to the LOCK mode and the rig is ready to transmit.

KIT PRICE	39.95
PREASSEMBLED, REG	59.95
SPECIAL, NOW	49.95

10 METER FM -THE NEW FRONTIER The AED FM ADAPTER is now available

The AED adapter converts existing HF transceivers to transmit on 10 meter FM.

To use the adapter you are required to have an HF SSB transceiver and a 2 M FM transceiver or receiver

The AED kit consists of 2 P.C. boards. Both boards are designed to fit entirely inside your HF rig. (Each board measures $1'' \times 2''$.)

One board serves as the modulator which FM's your existing HF transceiver's VFO.

The second board is a receiver adapter which converts your HF transceivers I.F. to a 2M frequency. This will allow you to receive noise free 10H FM on your 2M transceiver

This modification can be disabled with the on-off switch supplied with the kit.

The kit comes complete with all parts and a detailed instruction manual (crystal not included)



- RUGGED TAUT-BAND METERS— Provide accuracy and readability that must be seen to be appreciated.
- HEAVY DUTY CABINETS—Handsome heavy duty metal cabinets complement virtually every transceiver on the market today.
- TWO MODES-PEAK OR AVER-AGE-The amateur may choose between either peak or average power readings.
- POWER REQUIREMENTS—Due to the advanced low current design, battery life is truly outstanding, making this meter a natural for portable or field day operation. Uses standard 9 volt battery or 120V AC with optional AC adaptor.
- ATTRACTIVE AFFORDABLE PRICING *Model 31A (0 to 200w) 31B (0 to 20w)only \$149.00 Model 32A (0 to 200w, 0 to 2000w) 32B (0 to 20w, 0 to 200w) V 66 only \$169.00

SIGNALCRAFTERS, INC. **5460 BUENA VISTA DRIVE** SHAWNEE MISSION, KANSAS 66205 913/262-6565; TELEX 42-4171

All Signalcrafters products are designed, engineered, and produced in the U.S.A. Prices include shipping to all U.S.A. VISA and Master Charge accepted Kansas Residents please add 3½ percent.

V 82 **The UDT 170** 4,5 \$10 165 UD1170 SPECIAL SPECIAL Prom Ident Prom CW Ident Prom

The SMART TU for RTTY & MORSE

MAITEX CORR

The UDT 170 Universal Data Transceiver will instantly convert any ASCII or Baudot teletype or video terminal into a multiple baud rate data transceiver for ASCII, Baudot or Morse operation. It features ...

- 170/850 HZ Shift
- Dual 6 pole active filters for weak signal operation
- ASCII/Baudot Regeneration with multiple baud rates
- CW Auto Ident (optional)
- 1-150 WPM Morse with Auto-track

Price, Complete and Assembled \$4

Bank Americand



Price subject to change without notice

- Computes & Displays WPM copy rate & Buffer Status
- Selectable line length from 40 to 80 characters
- Metal Enclosure 12"x7 1/4"x3 1/2"

For more information write or phone

XITEX CORP. 9861 Chartwell Drive Dallas, Texas 75243 (214) 349-2490





TRS-80'/RTTY The Crowning Touch ROM-116

Amateur RTTY Operating System

00 ROM-110 2

* MODES: RTTY (ASCII or BAUDOT) *

 REAL-TIME CLOCK: 24 hour clock * Automatic updating * Time display includes day, month and year.

 SPLIT-SCREEN VIDEO: 12 lines receive text * 3 lines transmit text or pre-typing a message * 1 line display, realtime clock * Status displayed continuously * Word-wrapping.

 TWO SERIAL PORTS PROVIDED: Port "A" -Interfaces to internal or external terminal unit * RS-232, TTL and 60 ma. * ASCII/BAUDOT *



Supports any 8-level serial printer or modem * Baud rate keyboard selectable * Expansion interface not required for operation of serial printer or modem.

 BUFFERS: 7.5K Main text buffer * Pre-typed messages up to 7.5K possible. * 2.5K general purpose buffer *

 AUTOMATIC CW/ID: At the start/end of each transmission * Every 10 minutes * Provision for quick break (no ID).

 TRANSMITTER CONTROL: Transmitter turns on/off automatically via software control * Provisions made for quick break.

 SOFTWARE PROVIDED: 2 RTTY Programs (Cassette/Disk version) * ASCII/BAUDOT Driver routines (permits use of "LLIST" and "LPRINT" commands from basic) * CW send/receive program.

 HARDWARE REQUIREMENTS: TRS-80 with 16K RAM * External terminal unit recommended (Flesher TU-170, ST-6 etc) * AFSK/FSK unit.

INTRODUCTORY \$300

less cabinet

P. O. Box 892

Marysville, Washington 98270 206-659-4279 / 206-659-9512 *A Trademark of The Tandy Corp.

MODEL	BANDS	LENGTH	PRIC HI-Q	E WITH BALUN	WITH HI-Q CENTER INSULATOR
D-80	8	0.75	130	\$28.95	\$24.95
D-40	4(0,15	66	25.95	21.95
D-20		20	33	24.95	20.95
D-15		15	22	23.95	19.95
D-10		10	16	22.95	18.95
Shortened d	lipoles				
SD-80	SD-80 80.75 90 31		31.95	27.95	
SD-40		40	45	28.95	24.95
Parallel dipo	les				
PD-8010	80,40,	20,10,15	130	39.95	35.95
PD-4010	40,20	0,10,15	66	33.95	29.95
PD-8040	80,	40,15	130	35.95	31.95
PD-4020	40,	20,15	66	29.95	25.95
Dipole short	eners - only	r, same as in	cluded in	sD model	Is
S-80	80	0,75			\$11.95 pr
S-40		40			\$10.95 pr
Antenna Nylon gu Ceramic i SO-239 cr	accessor y rope 45 (Dogbone	les—availa 0# test 100 Type) ant ectors	able wi) feet enna ir	th anteni nsulators	na orders \$3.49 .70 pr
Available	e at your	All prid favorite de	ces are aler or	postpaid order di	d USA 48 rect from
Vai	ord	Dealer I	Inqui	ries In	vited
E	ng	ine	eı	rin	g
BOX 3	21305,	S. EUCL	.ID, (DHIO 4	4121

SOCIAL EVENTS

Listings in this column are provided free of charge on a space-available basis. The following information should be included in every announcement: sponsor, event, date, time, place, city, state, admission charge (if any), features, talk-in frequencies, and the name of whom to contact for further information. Announcements must be received two months prior to the month in which the event takes place. They should be sent directly to Editorial Offices, 73 Magazine, Pine Street, Peterborough NH 03458, Attn: Social Events.

FARIBAULT MN DEC 6

The Handi-Ham System will hold its annual winter hamfest on Saturday, December 6, 1980, at the Eagles Club, Faribault MN. There will be a flea market, a dinner at noon, a program, and a prize drawing.

OAK PARK MI JAN 11

The Oak Park ARC will hold its annual indoor Swap & Shop on January 11, 1981, at the Oak Park High School, Oak Park Boulevard (91/2 miles west of Coolidge Highway), Oak Park MI. Doors will be open from 8:00 am to 3:00 pm and admission is \$2.00 per person. Features will include an ARRL table, a door prize, a YLRL table, food, refreshments, and free parking. Talk-in on 146.04/.64 and 146.52. For more information, send an SASE to Rob Numerick, 23737 Couzens, Hazel Park MI 48030, or call (313)-398-3189.

CHESTERFIELD VA JAN 11

The Richmond Amateur Telecommunications Society will hold Frostfest 1981 on Sunday, January 11, 1981, at the Chesterfield County Fairgrounds, Chesterfield VA, from 8:00 am to 4:00 pm. New and large facilities include spacious aisles, and plenty of on-site parking, with charter buses welcome. Admission is \$3.00 for each four-footlong flea market table, and \$2.00 for each tailgating vehicle. Features will include commercial exhibitors, a flea market, an auction, and prizes consisting of a color TV, a Bird Wattmeter with slug, a digital VOM, and many more. Talk-in on 146.34/.94 and 146.28/.88. For further information, contact the Richmond Amateur Telecommunications Society, PO Box 1070, Richmond VA 23208.

LIVONIA MI FEB 22

The Livonia Amateur Radio Club will hold its 11th annual LARC Swap 'n Shop on Sunday, February 22, 1981, from 8:00 am to 4:00 pm, at Churchill High School, Livonia MI. There will be plenty of tables available. Other features include door prizes, refreshments, and free parking. Talk-in on 146.52. For further information, send an SASBE (4" x 9") to Neil Coffin WA8GWL, c/o Livonia Amateur Radio Club, PO Box 2111, Livonia MI 48150.

VERO BEACH FL FEB 21-22

The Treasure Coast Hamfest will be held on February 21-22, 1981, at the Vero Beach Community Center. Admission is \$3.00 per family, in advance, and \$4.00 at the door. Features will include prizes, drawings, and a QCWA luncheon. Talk-in on 146.13/.73, 146.52/.52, 146.04/.64, and 222.34/223.94. For information, write PO Box 3088, Beach Station, Vero Beach FL 32960.

DAVENPORT IA MAR 1

The Davenport Radio Amateur Club will hold its tenth annual hamfest on Sunday, March 1, 1981, at the Davenport Masonic Temple, Highway 61 (Brady Street) and 7th Street, Davenport IA, from 8:00 am to 4:00 pm. Tickets are \$2.00 in advance and \$3.00 at the door. For advance tickets and table reservations, write Dave Johannsen WBØFBP, 2131 Myrtle, Davenport IA 52804.

close encounter



Dateline Dayton Hamvention...

To demonstrate the selectivity of our Mark 3CR repeater we keyed a transmitter 15 KHz off frequency and set it directly against the receiver input. Our Mark 3CR didn't even notice the close encounter.

Sure the Mark 3CR can withstand severe interference.. it uses both crystal filtering and double conversion. And that's just the beginning. Its performance continues with a transmitter that meets commercial specs plus a microprocessor controller that gives you 39 functions and 13 Morse messages. For peak performance have your own close encounter with a Mark 3CR / Repeater or Mark 3C Controller.

call or write for specifications 49 MICRO CONTROL SPECIALTIES 23 Elm Park, Groveland, Ma. 01834 (617) 372-3442



I need schematics/owner's manual for an Eico model 625 tube tester. I will pay the postage, copy, and return all material.

Also, I need any modifications for the Globe V-10 vfo. I recently purchased one at a hamfest and the 6CB6 plate circuit doesn't match the schematics. It has a very low output (approximately 0.5 V p-p).

I'm awaiting my Novice ticket; that's why there's no call in my address.

Tim Cook 4536 Knoll Drive Woodbridge VA 22193

I recently obtained an Allied SX-190 reciever at a local hamfest, but I did not receive an operating manual. If anyone could supply me with a manual or a xerox copy of one (I believe the manual for the AX-190 ham receiver is the same), I would be happy to pay for it. The receivers were produced by Allied/Radio Shack in the early 70s. Thanks! the Kenwood TS-820S has an i-f output at 8.83 MHz, and I would be interested in any modification which will accommodate the higher frequency.

J.O. Dickinson 1408 Monmouth Court West Richmond VA 23233

I'm looking for a schematic or instruction manual for a Knight model KG-642-A ultrasonic intrusion alarm, circa 1970, and a schematic for a function generator using the XR-205 chip. I would be happy to pay for an original or a copy. Thanks.

> Gene Smarte WB6TOV Nubanusit Road Hancock NH 03449

I need circuit diagrams and/or books, as well as information on a vfo and mods, for a Conar 400 transmitter and 500 receiver. I will pay for copies.

> Nate Bushnell KA0DGN 7175 S. Grant St. Littleton CO 80122

SIGNAL GENERATORS OVERHAULED AND LAB CALIBRATED

AN/URM-25, RANGE 10 KHZ THRU 50 MHZ, AM/CW, MODULATION 400 & 1 KHZ, RF OUTPUT O-2V OR O-,1 V, PRECISION 50 OHM STOP ATTENUATOR, PERFECT FOR AMA-TS-510/U, RANGE 10 MHZ THRU 420 MHZ OUTPUT VOLTAGE .5V TO 1V, MODULATION TS-497/URR, RANGE 2 MHZ THRU 50 MHZ, OUTPUT VOLTAGE 0-100,000 MV, 400 CYCLE MODULATION, AM/CW MILITARY VERSION OF THE MEASUREMENTS MODEL 225.00 80 SG-3/U FM RANGE 50 THRU 400 MHZ IN 3 BANDS, METERED RF OUTPUT O-1V, METERED FM DEVIATION O-150 KHZ, VARIABLE 50 OHM ATTENUATOR, EXCELLENT FOR HIGHBAND SG-12/U FM RANGE 20 MHZ THRU 100 MHZ IN 5 RANGES, METERED OUTPUT AND DEVI-ATION, PERFECT FOR LOW BAND FM MILITARY AND COMMERCIAL RADIOS. 185.00 MEASUREMENTS 560 FM RANGE 25 THRU 54 MHZ, 130 THRU 174 MHZ, 400 THRU 4/0 MHZ AND 890 MHZ IN 6 BANDS, VARIABLE OUTPUT 100,000 MV TO 0.1 MV, 1000 CYCLE MODULATION, VARIABLE DEVIATION O-16 KCS, METERED OUTPUT AND DEVIA-TION, A FINE COMMERCIAL GENERATOR. 450.00 SG-13/U VOR/ILS, RANGE 108 THRU 135.9 MHZ AND 329.3 TO 335 MHZ, OUTPUT SIG-NALS INCLUDE VOR, LOC. GLIDESCOPE AND 1000 CPS, OPERATES FROM 115V/60HZ, SAME AS COLLINS 479T-2, PERFECT TO REPAIR AIRCRAFT RADIOS. 285.00 TS-418/URM-49, RANGE 400 THRU 1000 MHZ, AM, CW, OR PULSE, METERED OUTPUT, PRECISION ATTENUATOR 165.00 TS-1379/U SPECTRUM ANALYZER, RANGE 2 THRU 31.5 MHZ, 5" CRT DISPLAY USED TO DE-TERMINE RESIDUAL CARRIER LEVEL, THE LEVEL OF HUM SIDEBANDS, AND INTERMODULA-TION DISTORTION, PERFECT FOR TESTING SSB TRANSMITTER. USED ON ALL NAVY COMM FOB OTTO, N.C., SATISFACTION GUARANTEED OR MONEY REFUNDED, SEND CHECK, VISA OR M/C. PHONE BILL SLEP 704-524-7519. ₩ 367 **Slep Electronics** Company

> P. O. BOX 100, HWY 441, DEPT. 73 OTTO, NORTH CAROLINA 28763

Gary Toncre WA4FYZ 13764 SW 54th Lane Miami FL 33175

I would be interested in communicating with anyone who has used the Heathkit SB-610 and SB-620 at i-f frequencies higher than 6 MHz. For example,

(303)-794-6956

I need all the information I can get on converting a J.C. Penney's Pinto SSB rig to 10m.

> John Lynn 1456 Cheyenne Street W. Fargo ND 58078

I need operating manuals and schematics for a Collins 75A transmitter and 75A-2 receiver. Can someone help? I will pay for copies.

Electronic

Distributors

Bill Morehouse PO Box 214 Waukesha WI 53187 Does anyone have any information or a schematic for a Motorola T71GJT-1100? I will buy a manual for the above or pay for a copy. Thank you.

> Fred Martin 16 Reid Street South River NJ 08882



University Microfilms International

300 North Zeeb Road Dept. P.R. Ann Arbor, MI 48106 U.S.A. 18 Bedford Row Dept. P.R. London, WC1R 4EJ England

STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION (Required by 39 U.S.C. 3685), 1. Title of publication, 73 Magazine, 2. Date of filling, Oct. 1, 1980. 3 Frequency of issue, Monthly A. No. of issues published annually, 12 B. Annual subscription price, \$25.00.4. Location of known office of publication (Street, City, County, State and ZIP Code) (Not printers), 80 Pine Street, Peterborough, Hillsboro County, N.H. 03458, 5. Location of the headquarters or general business offices of the publishers (Not printers), 80 Pine Street, Peterborough, Hillsboro County, N.H. 03458. 6. Names and complete addresses of publisher, editor and managing editor Publisher (Name and Address), Wayne Green, Peterborough, N.H. 03458. Editor (Name and Address), Wayne Green, Peterborough, N.H. 03458. Managing Editor (Name and Address), Jack Burnett, 12-C Granite St., Peterborough, N.H. 03458. 7. Owner (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual must be given. If the publication is published by a nonprofit organization, its name and address must be stated.) Name, 73, Inc., Peterborough, N.H. 03458, Wayne Green, Peterborough, N.H. 03458.8. Known bondholders, mortgagees and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages or other securities (If there are none, so state) Name, none. 9. For completion by nonprofit organizations authorized to mail at special rates (Section 132.122, PSM) The purpose, function and nonprofit status of this organization and the exempt status for Federal income tax purposes (Check one) Not applicable, 10. Extent and nature of circulation. (X) Average No. copies each issue during preceding 12 months. (Y) Actual No. copies of single issue published nearest to filing date. A. Total No. of copies printed (Net Press Run) (X) 76,953 (Y) 73,695 B. Paid circulation 1. Sales. through dealers and carriers, street vendors and counter sales, (X) 10,779 (Y) 9,950. 2 Mail subscriptions (X) 60,132 (Y) 55,279 C. Total paid circulation (Sum of 10B1 and 10B2) (X) 70,911 (Y) 65,229. D. Free distribution by mail, carrier or other means samples, complimentary, and other free copies (X) 220 (Y) 284. E. Total distribution (Sum of C and D) (X) 71,131 (Y) 85,513. F. Copies not distributed 1. Office use, left over, unaccounted, spoiled after printing (X) 1,040 (Y) 1,040. 2. Returns from news agents (X) 4.782 (Y) 7.142. G Total (Sum of E, F1 and 2-should equal net press run shown in A) (X) 76,953 (Y) 73,695, 11. I certify that the statements made by me above are correct and complete. Signature and title of editor, publisher, business manager. or owner. Debra Boudrieau. Business Manager.





One-Stop Component Center ^{III} This is a partial listing of over 500 items available from authorized Jim-pak Distributors:

2

		-	m	-		Т	TL		-			1	
7400		12	1		8	. 2/.85	7490 .	-		1	1	3	.85
7402			1		2	. 2/.85	7493 .	1	- 53		2		.85
7404						. 2/.85	74100.						.2.25
7406		18	3		12	.2/1.19	74109	2			3	3	2/1.19
7407		3	0		8	2/1 19	74121	8	3	1	÷.	1	69
7408		1	•			2/ 89	74123	•			•		.00
7410		8	9		85.	2/ 85	74150		1			- 53	1 05
7410	•	1	1		1	. 2/.05	74150.		5		•	*	1.95
7414			•			2/1 10	74104.	•				•	.1.95
7417	*	1	1		1	. 2/1.10	74107.			18	*	1	1.10
7420	•					. 2/.85	/4101.	•		•	٠	•	.1.19
1441			*	1		1.19	/4164.		•				. 1.59
1414	18	12			15	69	74174.			(\mathbf{z})			.1.59
7475						79	74175.						.1.49
7476		2				69	74192.	2		14			.1.19
7485						1.19	74193.						.1.19
7486			-			.2/1.19	74367.		-	-	-	-	.99
7489		2	14		2	. 2.99	74393.	1	- 23	8	8	2	.1.95

POTENTIOMETERS

	830P 100K 7318 1 2 3
att @ 70°C Slotted Shaft near Taper	3/4 Watt @ 7 15 Turn Po Linear Tape
5K 10K 50K 100K	100Ω 500Ω 5K 10K 100K 500K 1





REGULATED POWER SUPPLY KIT

Uses LM309K. Heat Sink provided. PC board construction. Provides a solid 1 amp @ 5 volts. Can supply up to ±5V, ±9V and ±12V with JE205 Adapter, Includes compo-



4LS02. 4LS04. 4LS08. 4LS10. 4LS14. 4LS30. 4LS32. 4LS38. 4LS47. 4LS47. 4LS73. 4LS75. 4LS75. 4LS85. 4LS90.		* * * * * * * * * * * * * * * *	*************	*************	.55 .69 .55 .55 1.09 .55 .69 1.49 1.49 1.49 1.79 .79 .99 1.95 1.09	74LS123 1.95 74LS138 1.49 74LS139 1.49 74LS154 2.49 74LS154 2.49 74LS157 1.49 74LS161 1.79 74LS174 1.79 74LS192 1.89 74LS193 1.89 74LS193 1.89 74LS193 1.89 74LS193 1.29 74LS245 3.49 74LS367 1.29 74LS374 2.49 81LS97 2.49
Lov pin L pin L pin L pin L pin L pin L pin L	VP PP PP PP P	Pr	01	file	e 2/.59 2/.69 2/.79 2/.89 2/.99 2/.99 2/.99	KETS Wire Wrap 14 pin WW tin .75 14 pin WW gold 1.09 16 pin WW gold 1.09 16 pin WW gold 1.19 24 pin WW gold 1.69 40 pin WW gold 2.75

LS Schottky

2 Watt @ 70°C 3/4 Watt @ 70°C 7/8" Slotted Shaft 15 Turn Pot.	nents, hardware and instructions.	28 pin LP
Linear Taper Linear Taper 1K 5K 10K 25K 50K 100K 1 Meg 100K 500Ω 1K 1 Meg 100K 500K 1Meg	JE200 \$14.95 DESK TOP ENCLOSURES	DIODES & TRANSISTORS 1N751 2/.59 2N2219A2/1.19 1N757 2/.59 2N2222A 2/.89 1N1188 2.69 2N2907A 2/.89 1N3600 5/.99 2N305599 1N4001 4/.59 2N3772 2.25 1N4004 4/.69 2N3904 2/.69
CMU\$2.95 830P\$1.79		IN40074/.79 2N39062/.69 IN414810/.99 2N44012/.79 IN47332/.69 2N44032/.79 IN47342/.69 2N51292/.69 IN47352/.69 2N51392/.69 IN47422/.69 2N52102/.79 IN47442/.69 2N52102/.79
4002 .69 4044 1.39 4006 1.95 4046 2.49 4009 .89 4047 2.75 4010 .85 4049 .89 4011 .69 4050 .89 4013 .85 4051 1.95 4016 .85 4066 1.19 4017 1.49 4069 .79	DTE-8 (Pictured) \$31.95 DTE-11 (Pictured) 34.95 DTE-14 36.95 DTE-HK (Case for JE600) 47.95 DTE-AK (Case for JE610) (Pictured) 52.95	CAPACITORS Dipped Tantalum ELECTROLYTIC .1mfd@35V 2/.89 1mfd@50V 3/.69 .47mfd@35V 2/.89 4.7mfd@50V 2/.59 1mfd@35V 2/.89 10mfd@50V 2/.59 1mfd@35V 2/.89 10mfd@50V 2/.69 2.2mfd@25V 2/1.09 22mfd@50V 2/.79 3.3mfd@25V 2/1.19 47mfd@50V 2/.89
4020 2.19 4071 79 4023 49 4081 69 4024 1.29 4093 1.19 4027 89 4511 1.95	VIDEO CONTROLLER Ideal for all video	4.7mfd@25V 2/1.39 100mfd@50V .59 10mfd@25V 1.19 220mfd@50V .69 33mfd@25V 3.95 1000mfd@25V 1.19 100V MYLAR 2200mfd@16V 1.39 .00101mfd 4/.79 50V CERAMIC .022mfd 4/.89 10pf022mfd 4/.59 .047mfd 4/.99 047mfd 4/.69
DB25P D-Subminiature Plug 3.95 DB25S D-Subminiature Socket 4.95 DB51226 Cover for DB25P/S 2.25 22/44SE P.C. Edge 2.95 UG88/U BNC Plug 2.19 UG89/U BNC Jack 3.95 UG175/U UHF Adapter 59 SO239 UHF Panel Recp. 1.49 PL258 UHF Adapter 1.95 PL259 UHF Plug 1.95 UG260/U BNC Plug 2.39 UG1094/U BNC Bulkhead Recp. 1.49	Front Inside View Inside JVC-40 \$5.95 each	.04/mind 47.99 .04/mind 47.69 .1mfd 4/1.19 .1mfd 4/.79 .22mfd 4/1.29 4/1.29 4/.79 MICROPROCESSORS Z80A CPU (4MHz) 14.95 MC6800 8 Bit MPU 14.95 8080A CPU 7.95 8212 8 Bit I/O Port 3.95 8216 Bi-Directional Bus Driver 4.49 2513/2140 Character Generator 12.95 8T97 Tri-State Hex Buffer 2.25 AY-5-1013 30K Baud UART 6.95 AY-5-2376 88-Key Keyboard Encoder 13.95 2114-3 4K Static RAM (300ns) 9.49 MK4116 16K Dynamic RAM (250ns) 9.95 2708 8K EPROM 10.95 2716 16K EPROM (+5V) 19.95
LINEAR LM301N. .59 LM7805T 1.75 LM305H. 1.39 LM7812T 1.75 LM307N. .75 LM7815T 1.75 LM308N. 1.19 LM380N. 1.49 LM309K. 2.25 LM384N. 2.49 LM310N. 2.69 LM555N. .69 LM311N. 1.49 LM556N. 1.49 LM311N. 2.69 LM555N. .69 LM311N. 1.49 LM556N. 1.49 LM319N. 2.29 LM565N. 1.95 LM318N. 2.95 LM566N. 1.95 LM319N. 2.95 LM566N. 1.95 LM319N. 2.95 LM723N. .79 LM7905T 1.75 LM741N. .65 LM7912T 1.75 LM1458N. .99 LM323K. 5.95 LM1488N. 1.59 LM324N. 1.29 LM1489N. 1.59 LM339N. 1.29 LM1480N.	Discount ONE DOLLAR DOLLAR Discount Coupon OFFER EXPIRES DECEMBER 31, 1980 Redeemable at participating JIM-PAK Distributors for \$1.00 discount on purchases of JIM-PAK components exceeding \$1.00	Coupon GOOD FOR GOOD FOR ONE DOLLAR DISCOUNT On purchase of any JIM-PAK PRODUCTS at participating Distributors Mr. Distributor: Jim-Pak will accept this coupon for one dollar credit when returned to us with your regular orders.

80 73 Magazine • December, 1980

73 Magazine • December, 1980 81

-
0
-
-
U
-
3
Ct I
1
-
2
5
-
0
=
12.00
-
3
-
0
¥.
2
-
2
m
<u> </u>
0
\leq
3
<
2
-
T
D
0
0
115
-
0
3
õ
2
3
0
3
5
-
N
5
-
>
2
-
~
·@
0
1.3
00
G
55
55
55 0
55 S
55 Sh
55 Sho
55 Shor
55 Shore
55 Shorev
55 Shorew
55 Shorewa
55 Shoreway
55 Shoreway
55 Shoreway
55 Shoreway R
55 Shoreway Ru
55 Shoreway Ro.
55 Shoreway Roa
55 Shoreway Road
55 Shoreway Road,
55 Shoreway Road,
55 Shoreway Road, B
55 Shoreway Road, Be
55 Shoreway Road, Bel
55 Shoreway Road, Belr
55 Shoreway Road, Belm
55 Shoreway Road, Belmo
55 Shoreway Road, Belmo
55 Shoreway Road, Belmon
55 Shoreway Road, Belmont
55 Shoreway Road, Belmont,
55 Shoreway Road, Belmont, (
55 Shoreway Road, Belmont, C
55 Shoreway Road, Belmont, C/
55 Shoreway Road, Belmont, CA
55 Shoreway Road, Belmont, CA !
55 Shoreway Road, Belmont, CA 9
55 Shoreway Road, Belmont, CA 94
55 Shoreway Road, Belmont, CA 940
55 Shoreway Road, Belmont, CA 940
55 Shoreway Road, Belmont, CA 9400
55 Shoreway Road, Belmont, CA 94002
55 Shoreway Road, Belmont, CA 94002
55 Shoreway Road, Belmont, CA 94002
55 Shoreway Road, Belmont, CA 94002 (
55 Shoreway Road, Belmont, CA 94002 (4
55 Shoreway Road, Belmont, CA 94002 (41
55 Shoreway Road, Belmont, CA 94002 (41)
55 Shoreway Road, Belmont, CA 94002 (415
55 Shoreway Road, Belmont, CA 94002 (415)
55 Shoreway Road, Belmont, CA 94002 (415) (
55 Shoreway Road, Belmont, CA 94002 (415) 5
55 Shoreway Road, Belmont, CA 94002 (415) 59
55 Shoreway Road, Belmont, CA 94002 (415) 595
55 Shoreway Road, Belmont, CA 94002 (415) 595
55 Shoreway Road, Belmont, CA 94002 (415) 595-t
55 Shoreway Road, Belmont, CA 94002 (415) 595-5
55 Shoreway Road, Belmont, CA 94002 (415) 595-59
55 Shoreway Road, Belmont, CA 94002 (415) 595-593
55 Shoreway Road, Belmont, CA 94002 (415) 595-593(
55 Shoreway Road, Belmont, CA 94002 (415) 595-5936
55 Shoreway Road, Belmont, CA 94002 (415) 595-5936

Pensacola	Oakland Park	Miami	Lakeland	Hialeah	Ft. Laudardala Geineville	Ft. Laudardale	FLORIDA	Wilmington	Newark	New Castle	Westport	New Haven	Avon	Denver	Denver	Colorado Spring	Aurora	Woodland Hills	Whittier	Whittier	Westminster	Van Nuvs	Tustin	Torrance	Torrance	South Lake Ial	South Gate	Santa Rosa	Santa Maria	Santa Fa Spring	Santa Barbara	San Rafael	San Luis Obisp	San Jose	San Inco	San Fernando	San Diego	San Carlos	Salinas	Sacramento	Sacramento	Raddina	Paso Robles	Pasadena	Palo Alto	Palmdale	Contain
Southeast Micro-Date Corp. Grice Electronics Inc.	Lafayette Radio	Herman Electronics	Lakeland Specialty Electronics	Heathkit Electronic Canter	Lafayette Radio Electronics	Computers For You	ACT Elements	Wholesale Electronics Inc.	Computerland	Delaware Amateur Supply	Computerworks	Customized Computer Systems	Heathkit Electronics Center	Micro World Electronics	Mt. Coin Distributing Co.	rs Centennial Electronics Inc.	Aurora Electronics	Heathkit Electronic Center	Whittier Electronics Co.	D&S Electronics	JK Electronics	Thrifty Electronics Supply Inc.	A-B&B Electronics	Torrance Electronics	SE Electronics	Calline Electronics	Mac's Electronics	Electronics Inc.	Cap's Communications	Industrial Electronics	Lombard Electronics	Electronics Plus	o Mid-State Electronic Supply	United Radio & TV Supply	Panineula Electronic Supply Inc	San Fernando Electronics	Radio Shack A.S.C. Mira Mesa	J&H Outlet Store	Salinas Radio	Zackit	Calif Radio & Television Supply	HeathKit Electronic Center	Mission Electronics	Dow Radio Inc.	Zack Electronics	Radio Shack A.S.C. Paimdale	
Grand Rapids Grand Rapids	Grand Rapida	Garden City	Flint	Oxford	Detroit R	Detroit	Clawson R	Canton	Battle Creek	Ann Arbor	Adrian Dark	MICHIGAN	West Springfield	Wellesley	Waltham	Pittsfield	Peabody	MASSACHUSE	Whearon	Towson	Towson	Towson	Silver Spring	Rockville	La Vale	Clan Burnia	Damascus	Churchville -	Baltimore	Baltimore	Baltimore	Annapolis	Annapolis	MARYLAND	Shravanort	Lake Charles	Lake Charles	Kenner	Baton Rouge	Baton Rouge	Baton Rouge	IOUISIANA	Louisville Pee	Lexington R	KENTUCKY	Salina	
T&W Electronics Warren Radio Co.	Radio Parts Inc.	Computer Center	Shand Electronics Inc.	Oxford Software Co.	adio Supply & Engineering Co.	Heathkit Electronic Center	adio Supply & Engineering Co.	The Electronic Connection	Warren Radio Co.	Wedemeyer Electronic Supply	E&B Electronics Inc.	and a manual of man of some	AM Electronics Inc.	Heathkit Electronic Center	Computer Mart Inc.	Pittsfield Radio Co. Inc.	Heathkit Electronic Center	15 Tol Com Int	Computer Grafters	Heathkit Electronic Center	Computers Unlimited	Daynesville Electronic Inc.	Computers Etc.	Heathkit Electronic Center	J&M Electronics	Frederick Computers	Damascus CB	Churchville Electronics	Trittonics, Inc.	Every ming Electronic	American Distributing Co.	J&M Electronics Inc.	Computers Etc.	Fiddan Automates Internatio	Industrial Electronic Supply Co.	Wholesale Hadio & Equipment	Gult Power & Controls	Heathkit Electronic Center	Pelican Electronics	Menard Electronics Inc.	Davis Electronics Supply Co.	Medison County Electronics	riess Electronic Equipment Co.	tadio Electronic Equipment Co.	Andteur navio equipinent vo.	Ametain Dadio Fauloment Co	interest and and a second and
Eugene Portland	Corvallis	Albany	OREGON	Oklahoma City	OKLAHOMA	Youngstown	Toledo	Toledo	Fremont	Dover	Cleveland	Cincinnati	Cincinnati	Fargo	NORTH DAKO	Raleigh	NORTH CARO	Wappingers half	Unica	Utica	Troy	Rochester	Poughkeepsie	Peekstill	Orchard Park	New York City	New York City	Newburgh	Middleton	Kinaston	Jericho	Jamestown	Ithaca	Ithaca	Endual	Buttalo	Amberst	Albany	Albany	Albany	NEW YORK	Vineland	Ramsey	Pompton Lakes	Pennsauken	Fair Lawn	DODARDING
Eugene Amateur Radio Supply Portland Radio Supply	Zero-Gee	Oregon Ham Sales	Trice Wholesale Electronics	Heathkit Electronic Center	Bire Butse & Minne	Ross Radio Company	Warren Radio	Heathkit Electronic Center	Terra Tech College Bookstore	T. V. Specialties	Heathkit Electronic Center	Micro-Solution	Heathkit Electronic Center	S&S Electronics	TA	Byte Shop of Raleigh	LINA The Computer Conner	Action Audio Inc.	Central Electronics	Am-Com Electronics	Trojan Electronics	Heathkit Electronic Center	Greylock Electronics	Action Audio Inc.	Radio Equipment Corp.	Taft Electronice AS Com	Aristo Craft	Action Audio Inc.	Action Audio Inc.	Graving Flortranics	Heathkit Electronic Center	Warren Radio	Rad-Tronics	Action Audio Inc.	Computer Tree Inc.	Hadio Equipment Corp.	Heathkit Electronic Center	Greylock Electronics	Fort Orange Electronics	Action Audio Inc.	Latayette nadio electronica	Lataverte Radio Electronics	Typetronic Computer Store	Computer Corner	Lafaverte Radio	Heathkit Electronic Center	eratepinonueu
Port of Spain, 1	Stockholm	SINGAPORE	SINGAPORE	GUATEMALA	ENGLAND	GUAM	Ontario:	Calgary	CANADA			Chevenne	Wheeling	Morgantown	Morgantown	Fairmont	VECT VIDCIA	Tacoma	Spokane	Spokane	Seattle	Seattle	Richland	Pasco	Longview	Kennewick	Everett	Bellevue	WASHINGTO	Warrenton	Virginia Beach	Vienna	Roanoke	Richmond	Nortoik	Norfolk	McLean	Hopewell	Hampton	Falls Church	Charlottacville	Arlington	Annadale	Alexandria	Alexandria	Essex Junction	I ALCONOLA A
Trinidad The Hobby Centre	LSI Electronics HB	Sys-Tech	Applied Digital System	Electronica Pan-Americana	NewRear Computing Store	Marianas Electronics	United Company	CompuShop Alberta Ltd.				Computer Concepts	Lafayette Radio Associate Store	Electro Distributing Co. Inc.	The Computer Corner	TPS Electronics Inc.	Northwest Hadio Supply	C&G Electronics	Personal Computers	Don's Stereo Center	Amateur nadio Supply	ABC Communications	C&J Electronics	Riverview Electronics	Progress electronics	C&J Electronics Inc.	ABC Communications	ABC Communications	N Priginia milito Systems	Madio Shack	Heathkit Electronic Center	Electronic Equipment Bank	Avec Electronics Corp.	Avec Electronics Com	Electronics Linimited	Avec Electronics Corp.	Tyson's Computer Emporium	B&G Electronics	Electronic Sales Inc.	Crossroad Electronics	Gravet Electronics	Arlington Electronic Wholesalers	Arcade Electronics	Heathkit Electronic Center	Computers Plus Inc.	Latayette Hadio	

Inchorage RIZONA lagstaff ireen Valley ierra Vista LABAM ASKA LIFORNIA eley na Park na Park na Park la Vista Bay nal City Ige eim adero City Gity avette acific J.L.S. Electronic Inc. Micrologic Inc. trial Electronic Supply W&W Electronics rette Radio Electronics Radio Parts Inc. triaf Buff's Electro Carson Electro ic Radio Exchany Newood Electronics A.B.C. Electronic A.B.C. Electronic Int Electronic Cente Int Electronic Cente Int Electronic Cente Inter Electronic A.B.C. Electronic Electro Coast Electron Willy's Electron Electronic Cen nic Center Electronics Electronic Electronic Electronic ectronics Co. tereo Repair Radio Shack Electronics Electronic City Electronics ic Company TV Mart

Indianapolis Muncie South Bend South Bend IOWA Davenport Des Moines Des Moines Ces Moines KANSAS Hutchinson Hutchinson Kansas City Rockford Schaumburg Skokie Skokie Skokie Skokie Villa Park Villa Park Villa Park Villa Park NDIANA Bloomington Chesterton Chesterton Chesterton Chesterton Chesterton Chesterton Chesterton tone Mo AWAII EORGIA LINOIS chondali ORID HO eva reland nt Pro ton ontini AME Giff Heathkit Electronic Center Microcomputer Center Inc. Heathkit Electronic Center Microcomputer Systems Electronic Supply Inc. Memory Bank ford Brown Incorporated Radio Trade Supply Co. Computer Atlanta Computer Mart CompuShop leathkit Electronic Center Radio Wholesale Coleman's Electronics Tri-State E Stansifer Radio Co. Inc. Chesterton Electronics Acro Electronics Corp. Hutch & Son Inc. Iurnet Electronic Supply athkit Electronic Supply Pierce Electronics Radio Distributing Inc. Television Supply Co. Hutchinson Electronics Electronic Surplus Sales Picks Electronics Howard Electronic Sales Olson Electronics ri State Electronic Corp. Melvin Electronics Moyer Electronics ri State Electronic Corp. Dom Electror Custom Electronics A-Gem Supply Inc. ated Circuit Supply 0.S.K. Electronics Computer Land - Land of Peoria arren Radio Co. are of Rockford of Schaumburg ipute Computer ipute Computer ivin Electronics

Livonia Radio Supply & Engli Madison Heights Wa ADA mazoo Falls ASKA SIPPI SOTA JRI olis Northwest Radio of Duluth Inc. Heathkit Electronic Center Pal Electronics Heathkit Electronic Center Hiawatha Electronics Inc. Scott Elect Cott Elect Heathk Computronia C&S Electron Olso ott Elect Fulton Radio : Lafay H.R. Electronic Niles Radio Suppl Electronic Suppl Radio Electronics Ind Electronic Mar Bell Electronic Mar Bell Electronic Heath Customer Cente Electronic Work City Electronic Suppl Olson Electronic V Ra Forsy the Computers Beckreen Electronics Computer Country Country (Downtown) Conley ic Servi Fulton M Es Inputer System ranic Supply In a & Hobby Sha hic Supply Corp west Compu-ic Supply Arts Electronics afayette Ra vest Elec-Radio Si Warren I lio Supply nics Man on Electr pply Col pnic Cent Century 23 ic Supp Co. adio

PENNSYLVANIA Braddock Chambersburg Drexel Hill Drums ridge llahoma EXAS umont vnsville HODE ISLAND anston wrtucket arwick eNNESSEE bokeville bokeville mphis emphis emphis Sen AH rt Worth Hand Uston Uston Uston Uston Uston Antonio Antonio Antonio lladelphia lladelphia penixville tsburgh tsburgh kes Barre rk REGON Lake City cer Eddie Electro-Hut George's Electronics Mart Heathkit Electronic Center Ram Micro Systems The Ingenuity Concept Tinker Tronics Inc. Heathkit Electronic Center Interactive Computers Carlos Franco Electronics Carlos Franco Electronics Carlos Franco Electronics Cak Electronics Inc. C&K Electronics Inc. Heathkit Electronic Center L&M Wholesale Electronics Wagnon's Stereo Center hields Electronics Supply Inc. Bluff City Electronics e-Rose & Spencer Electronics Warren Radio Company ddie Warner's Parts Company Electra Distributing Co. National Electronics H&H Electronics Co. Inc. Leff Electronics Sunrise Electronics Distributors Mr. D's Digital Electronics Marren Radio Heathkit Electronic Center Heathkit Electronic Center Resco Electronics Stevens Electronics Heathkit Electronics South Hills Electronics Hamline Electronics Heathkit Electronic Center Alpine Electronic Supply Co. Best Distributing Computerland of Salt Lake abbour Electronics City abbour Electronics City athkit Electronic Center 8 ŝ

. ne-Stop P 9 ompone

electronic components Λ. 384

UTHORIZED DIST 30 55 ORS ente



Fred Gerken WBØLLP 7009 Knight Drive Box 91910 Lewisville TX 75056

Clean Sweep for the FT-221 - don't miss the action

C SB on two meters is be-Coming more popular in my area, and activity centers around the national calling frequency of 144.200 MHz. So, whenever I am in the shack, I turn on my FT-221 and position the vfo on that frequency. Several times I have listened for hours to the rush of the receiver, not hearing a peep, only to move the vfo dial when passing the rig on the way to the 807 locker and find a QSO in progress a few kHz away. This half-hearted monitoring causes me to miss much of the local activity. In order to solve this problem, I have added a clarifier sweeper to the rig. This allows me to monitor 144.200 \pm 8 kHz in a sweeping mode. The Yaesu FT-221 has a broad clarifier which uses a varactor diode in the local oscillator module. By varying the voltage on the varactor from one to eight volts, the clarifier has over \pm 8 kHz of tuning range. The circuit in Fig. 1 provides an inexpensive pseudo-triangle wave generator with an output of one to eight volts, and a sweep time of one complete sweep approximately every four seconds.

generator, and R1C1 forms an integrator which converts the square wave into a triangular wave. See Fig. 2. For the purist, an op-amp integrator could be substituted for R1C1. See Fig. 3.

Once the sweeper is assembled, check the output voltage. The output should swing slowly towards Vcc and then slowly back to about 1.0 volt and start over again.

Installing the sweeper in

switch for the original pot. See Fig. 5. This method is my choice. Only the new pot and two diodes need to be added. When the clarifier knob is rotated fully until the switch clicks, the sweep mode is engaged. When the clarifier knob is in any other position, it functions normally.



The circuit itself is very small and mounts anywhere room is available. However, there is a good spot just in front of the crystal deck. The eight volts dc to run the sweeper is easily obtained from the clarifier pot itself. See Fig. 5.

Happy sweeping!

The circuit is designed to be both small and inexpensive. The 555 timer is wired as an astable square-wave the FT-221 is a matter of preference. A simple toggle switch could be used to control the sweeper, as shown in Fig. 4. If you are the type who hates to cut holes in a \$600 rig, you might try substituting a new clarifier pot and SPST



Fig. 2. Waveform from square-wave generator and R1C1 integrator.



Fig. 4. Hookup using toggle switch.











CUBIC'S ALL BAND ASTRO-103

A new name, a new look, and a new standard of performance in ham radio!

(and you don't have to be a computer expert to use it!)

ALL BANDS INS AND OPERATIN 160 thru 10 including WARC	STALLED IG! bands	DUAL ultra stabl PTO's	Fast break-in (QSK)	RTTY VOX	Jack for separate receive antenna	Fully variable AGC decay	Dual 8-pole filters. 1.4:1 shape factor -6 to -100dB	True Passband Tuning with width and position indicators
Built-in VSWR meter	CW out pulse sh — hard	put naping or soft	Sophisticated Noise Blanker	Speech Processor	r Noise Flo 3rd order	al Dynamics or -132dBm intercept +15dBn	RF/IF Gain Controls	Optional CW Narrow Crystal Filter





KEY/MIC

CUBIC

The Cubic ASTRO-103 expands on the highly acclaimed ASTRO-102BXA with the addition of the most asked for features — RTTY, an input connector for a separate receive antenna, and of course, ALL BAND coverage from 160 through 10 meters, including the new bands at 10, 18, and 24.5 MHz. All bands are operating *now*, nothing to buy later, and of course WWV is covered.

With the optional 400Hz crystal filter installed, which cascades with one of the 8-pole I.F. filters and can be moved through the passband, along with QSK provisions, the ASTRO-103 is the CW operator's dream!

Performance under high cross mod conditions found in todays' crowded bands is second to none. With dual independent high stability PTO's for split band DX and all its other features, the ASTRO-103 is the result of American Technology and American Quality combined to bring the best to the American Amateur. See your dealer for a demonstration you won't leave the store without one!

CUBIC — Success Built on Excellence

Cubic Corporation with over 3,500 employees world-wide, including more than 1200 scientists, engineers and technicians, has more than one million square feet under roof.

Established in 1951 the company has grown and expanded in high technology fields, including computer based automatic fare collection systems, electronic countermeasures, supersonic pilot training and other defense and space systems, electronic positioning devices and, of course, communications. New Cubic Amateur products reflect this heritage of excellence and is your assurance of the strength and resources to support your purchase in the years to come.



Another member of the ASTRO family, the ASTRO-150, has been highly acclaimed as the ideal Mobile/Base station. With microprocessor control, VRS tuning and microphone scanning, the ASTRO-150A led the way for competitive radios now appearing on the market.



The ASTRO-102BXA provides basically all the fine performance of the ASTRO-103 at a lower cost, but less the WARC bands, which of course may be added later if desired.



305 Airport Road, Oceanside, CA 92054 (714) 757-7525 Dave Ingram K4TWJ Eastwood Village, #1201 South Route 11, Box 499 Birmingham AL 35210

A New Frontier - weekends were made for . . . 10 FM!

During recent years, FM has become one of amateur radio's most popular and widely accepted modes of UHF communication. The convenience and flexibility of channelized, squelch-muted equipment continuously appeals to numerous amateurs. braces a unique pleasure which all amateurs cherish -a thrill as old and irreplaceable as ham radio itself. Wouldn't it be interesting to combine these

two modes and enjoy intercontinental FM operations? Imagine an ample supply of remote-base setups and repeaters capable of practically worldwide communication in this vision and you have an accurate description of 10-meter FM—a frontier which is presently blowing wide open with excitement.

The excitement of lowband DXing, however, em-



Photo A. Recipe for mountaintopping fun with 10 FM includes (left to right) a Cushcraft 10-meter FM Ringo, an MFJ antenna tuner with knapsack full of loose and long wires, Comtronix FM-80, and a 2-meter hand-held talkie.

Although FM communications have been taking place on the high end of our 10-meter band for several years, this mode only recently gained widespread popularity. Two of the prime reasons for this upsurge are the increasing sunspot activity and the availability of commercially-manufactured 10meter FM equipment. The introduction of Yaesu's FT-901DM all-mode 160through 10-meter deluxe transceiver and the Comtronix FM-80 10-meter FM transceiver substantially promoted 10-FM activity. During the period of a few

84 73 Magazine • December, 1980

Repeater Inputs	International Direct Frequency	Repeater Outputs
29,520 kHz		29,620 kHz
29,540 kHz	29,600 kHz	29,640 kHz
29,560 kHz		29,660 kHz
29,580 kHz		29,680 kHz

Table 1. Ten-meter FM band plan. "Direct" operation on repeater output frequencies is acceptable provided deliberate interference isn't created.

months, 10 FM actually came alive with worldwide FM operations. This activity continues to grow each day, as innovative-minded amateurs clamor to join the fun.

Overview of 10-FM Operations

Although a number of inband repeaters are operational on 10 FM, most of the activity is "direct" communications on the International Direct Frequency of 29,600 kHz or the repeater output frequencies of 29,620, 29,640, 29,660, or 29,680 kHz. Thus far, the use of direct communications on repeater output frequencies has proven quite acceptable on 10 FM, provided it doesn't interfere with the normal repeater activities on that channel. Due to the limited spectrum allocation for 10 FM, a tight-fitting and conscientiously adhered-to band plan is necessary. As this is being written, 29,600 kHz is being used for brief QSOs and as an international calling frequency with resultant additional communications being carried out on 29,620, 29,640, and 29,660 kHz. 10 FMers realize the long-distance propagation effects of this band, and during such times their gentlemanly procedures are generally beyond reproach. Several repeater groups are presently investigating ways of improving the 10-meter FM band plan, but it appears that the one shown in Table 1 will be retained for many more moons.

and evening, this band's most exciting times usually occur during weekends. The fun starts early each Friday afternoon and continues full bore until the band closes each Sunday night. During these times, signals from European, South American, and Japanese amateurs have been heard working various stations through repeaters in the northwestern United States, and New Zealand stations have been heard transmitting through repeaters in the California area. It's not extremely unusual, either, to hear two or three European amateurs communicating with each other through a US-based



Photo B. Receiver section of WR6BDG, the 29, 620-kHz FM repeater in Sierra Madre, California. This repeater is maintained by David Findley N6DF and John Portune WB6ZCT. During weekends, Dave and John occasionally switch this machine to straight COR function for "open" access. The

While 10 FM is alive and active almost every day repeater during a weekend on 10 FM—and this situation should also exist in reverse in the near future.

All of the US-based repeaters on 10 FM employ PLTM tone encoding to prevent unwarranted in-band interference. Right now, the most common PL frequency in use on 10 FM is 107.2 Hz. When the control operator is monitoring a system during the weekend, however, some repeaters switch to straight COR control to permit various forms of DX operations through their machine.

An uncounted number of remote base setups are operational on 10 FM. Some of these systems are permanent arrangements used by many amateurs, while other remote bases are private systems created by interconnecting one's 10- and 2-meter FM units as desired. Another possibility for the near future is that of mobile remotes, produced transmitter of WR6BDC is approximately one mile away, at the QTH of WB6ZCT.

by interconnecting one's 10- and 2-meter mobile FM rigs. These units can be used separately while mobile, or the 10-meter unit can be 2-meter-accessed by the operator's HT when he leaves the car. An in-car rubber ducky 2-meter antenna will restrict the 2-meter access range of this system.

Equipment

As previously mentioned, the introduction of Yaesu's FT-901 series transceivers and Comtronix's FM-80 units has been a contributing factor in the recent growth of 10 FM. Prior to this evolution, the bulk of 10-FM equipment consisted of converted low-band (30 to 40 MHz) business radios. Both the Yaesu and the Comtronix are superb performers on 10 FM. FM capability is standard on the FT-901DM and an available option on the FT-901D and DE transceivers. Power output is approximately 20 Watts in the FM mode. The unit's memory is perfect for programming repeater "splits," and its squelch circuit operates very smoothly.

The Comtronix operates 80 discrete channels of 10 FM, and the standard 10-FM repeater offset of 100 kHz is accomplished by a switch on the unit's squelch control. The rig's front-panel meter reads S-units on receive and relative output power on transmit. Additionally, a front-panel LED varies in intensity according to transmitted modulation, while another LED (bipolar) lights green during receive and red during transmit. Power output of the

Comtronix is 10 Watts (high power) or 1 Watt (low power). The low power of both the Yaesu and the Comtronix is synonymous with 10 FM. 50-Watt stations are considered high power, and 250-Watt signals are "super power" and usually are unnecessary.

Commercially-manufactured antennas for 10 FM also are beginning to gain in polularity. Cushcraft recently introduced a 10-FM Ringo which looks very similar to their 2-meter Ringo except that it's much larger (17 feet tall—and it's great!).

Newtronics recently introduced their HOT 10 trunk-lip-mounted, centerloaded mobile antenna for 10 FM.

There are a number of antenna tuners which the 10-FM enthusiast will find beneficial when tuning a beam or random length of wire for operation on $29,600 \pm \text{kHz}$. MFJ Enterprises manufactures a full line of these items, and any of their tuners that I've tried have worked extremely well.

Finally, there are a large number of CB sets which may easily be converted for 10-meter FM operation. Basically, this conversion involves three steps: Move the unit up approximately 2.5 MHz in rf range, replace the AM modulation with an FM modulator, and change the receiver's AM detector to an FM counterpart. Several articles concerning CBto-10-FM conversions have been published in amateur magazines recently.

Getting Started On 10 FM

Joining the fun of 10 FM will probably bear a striking resemblance to the time you first became involved with 2-meter FM. You'll probably locate and convert a business radio for 10 FM, convert a CB set to 10 FM, or purchase a Yaesu or Comtronix for 10 FM. Operating techniques may seem different from 10meter SSB activity, but you'll get the hang of it within a couple of days and wonder why you didn't try 10 FM sooner.

Remember to keep your transmissions short when there's any possibility of interfering with distant QSOs, and never conduct lengthy direct communications on a repeater input frequency. As with any new mode of communications, the prime key to successful operation involves listening extensively to learn the techniques of that mode. 10 FM doesn't hold a money-back guarantee of fun, but you can feel relatively confident that there will be numerous amateurs waiting to purchase your used 10-FM gear should you decide to

sell out and return to SSBonly activities.

Conclusion

The amateur frontier of 10 FM is growing at a fantastic rate, and this mode has an extremely promising future. Long-distance communication via FM is a unique experience-and this aspect blends perfectly with today's frantic lifestyle and mobile operating techniques. This band is much smaller in rf spectrum than other FM bands, so considerate and sophisticated operating techniques are a vitally important consideration.

All aspects considered, 10 FM should prove an exciting experience for the progressive-minded amateur. Its DXing, casual operating, and mountaintopping pleasures add new life to an amateur's interests. Here's listening for you on twenty-nine six!

× 323



SIMPLY THE BEST! FOX TANGO FILTERS YAESU-KENWOOD-DRAKE-COLLINS-HEATH

Whether your SSB rig is old or new, there is no easier or essentially less expensive way to significantly upgrade its performance than by improv-

ing its IF passband filtering. FOX-TANGO filters are made of speciallytreated high-Q quartz crystals, affording excellent shape factors and ultimate rejection exceeding 80 dB. They are custom made for drop-in installation, matching perfectly, both physically and electronically. Our Diode Switching Boards make possible (now or in the future) the addition of a variety of switch-selectable filters affording superior variable bandwidth without the need to buy an expensive new model. If you want the best for less, you'll buy FOX-TANGO. Just tell us the bandwidth(s) desired for your make and model.

*DIODE SWITCHING BOARDS available to permit 1, 2 or more filters than those for which manufacturer provides room. SPECIFY make and model.

> Single-filter type: \$12 Airmail postpaid worldwide. Dual-filter type: \$21 Airmail postpaid worldwide. Florida residents add 4% (sales tax) (FOREIGN ADD \$5 per filter)



Dealer Inquiries Welcomed Visa/MC welcomed. Money back if not satisfied.



GIFT CERTIFICATES AVAILABLE

BROCHURE ON REQUEST

FOX-TANGO CORP.

8-POLE FILTER BANDWIDTHS IN STOCK

GRYSTAL FILTER			CW	(Hz)				SSB-	AM (I	kHz)	
107 24 W 10 WE - 5019260	125	250	400	500	600	800	1.8	2.1	2.4	6.0	8.0
YAESU					\$5	5 EA	СН			-M-	
*FT-101/F/FR-101	ſ	~		-	~		~	11	2	1	
*FT-301/FT-7B/620		~		~			1	1	~	1	
*FT-901/101ZD/107		~		~			1		1	-	
FT-401/560/570		1		-			1	1			
FT-200/TEMPO 1				~			~	-			
KENWOOD				Mun.20	\$5	5 EA	СН		1	112-112	311-77
*TS-520/R-599		~	1				~	~	• 21	d IF S	125
*TS-820/R-820		~	~	1			~	10	for	R-820	only
HEATH			ii m		\$5	5 EA	СН	-	- and		
ALL HF		1	1				1	1			
DRAKE	1		an 1	FOR	PRIC	ES S	SEE N	OTE	S		Rive"
R-4C GUF-	1 Bro	ad 1st	IF S	uperio	r Sha	pe Fa	ctor/	Ult Re	\$65	2	1
GUF-	2 Nar	row 1	st IF		~	1	+	pcb w	SW F	elays	\$90
NEW 2nd I	F			-	Plug i	n typ	8 1	12			\$55
GUD	Produ	ict De	tector	p	cb w	relay	doub	le bala	inced	type	\$30
COLLINS:	T			SPEC	IAL	\$125	EAC	н		181	-
75S-38/C	T	V		EQUA	LS OR	EXC	ELS S	100 CO	LLIN	S UNI	T

Box 15944S, West Palm Beach, FL 33406

SAVE \$ SAVE \$ SAVE CALL TOLL FREE 1-800-228-4097 We Offer The Lowest Prices In The Country

HAM RADIOS

ALLIANCE AVANTI BEARCAT B&W BENCHER CDE CUSHCRAFT DENTRON DRAKE ENCOMM ETO HUSTLER HY-GAIN ICOM KENWOOD LARSEN MIRAGE MOSLEY SHURE SHURE TELEX TEMPO TRAC YAESU

COMPUTERS

APPLE ATARI BASE 2 CENTRONICS COMMODORE DC HAYES MAXELL MOUNTAIN HDWR NEC PAPER TIGER PET VERBATIM

IN STOCK NOW! VIDEO DISC PLAYERS Call for Discount Prices

Communications Center



1840 'O' St., Lincoln, Ne., 68508 In Ne. Call (402) 476-7331

VISA'

Tom French WA4BZP All Systems Go PO Box 915 Winter Garden FL 32787

Scanner Magic for Heath's 2036 – grab your October '79 issue for part I of this project

	Parts List
R1	90k (value varies, depending on level of threshold
	signal-see text)
R2, R3	1 meg
R4	1k

n the October, 1979, issue of 73, an article entitled, "An LED Display for the HW-2036" really excited a number of Heathkit® 2036 and 2036A users. As mentioned in the article, a scan board circuit could be piggybacked to the 2036-DB Display Board. Below are a few hints on how to build this board and check it out.

Acquire a 2"×3" piece of perforated board and mount it for sizing on the forward 21/4" screw above the 2036-DB. With the board piggyback on the 2036-DB, position all three 74LS163 chips and also the NE555; don't forget to leave a little bit of room for Q1 and R1 through R3. After marking the parts locations, remove the board. The components then can be inserted, leads bent, and all required connections made with wire-wrap as shown in Fig. 1. R1 is a threshold-setting resistor and its value is dependent on what signal strength you wish the scanner to lock. The higher its value, the more signal is required to lock the scanner on a carrier. A trimpot here would make adjustment easier. Clock Out from the NE555 will go to the new scan operate switch (0/5 kHz), to provide a strobe pulse for the SN74LS298s. Install the push-to-scan switch on your mike at some place convenient (best location is on top) and use one of the extra wires in



OPERATE +5 VDC 2036-SB CLOCK 2036-DB STROBE ER4 Q213 2036-MB STROBE START LOCATED ON MIC SCANNING 01 ZERO VDC 2036-DB SCAN-PIN +5 VDC SCAN POSI n +5 VDC +5 VDC +5 VDC 16 LOCATED ON REC BOARD 15. IC1 102 103 IN 2036 74LS163 74L5163 74L5163 ti the S. 13 8 Λ^{*} 0 'Δ' PIN PIN 9 7 PIN PIN PIN 9 9 4 -41 TO 1C7 TO 1C6 TO 105 +5 VDC IC4 NE-555 R2 R3 CLOCK OUT TO SCAN-OP SWITCH CI OINF.

Fig. 1. 2036-SB Scan Board schematic diagram.

88

the mike cable for the signal back to the 2036-SB.

Next, install the respective wires to IC5 through IC7 from the 2036-DB to the 2036-SB (see Fig. 2). Remove the scan bridge on your 2036-DB and solder in the wire from the scan operate switch. Reassemble your unit and apply power. Throwing the scan operate switch to Scan should cause the display to count from .000 to .999 and cycle again. If this does not occur, check the 2036-SB to verify that the scan clock is active. Also read the signal at the 2036-DB on pin 10 of IC4 through IC7; these should also toggle.

To scan 147.000 to 147.999, key in 7-7-7-7, then switch to scan. The switch should be toggled slowly. This scan modification is used to enable the user to locate new repeaters in a new city, and by no means is it competitive with professional scanners.





If your synthesizer is not locking on frequency in the scan mode, it is recommended that the scan clock be slowed down. This is accomplished by increasing the value of the two 1-megohm resistors, R2 and R3 (see Fig. 1).



Organize your shack with a **CLUTTERFREE MODULAR CONSOLE \$179.95**

- Large, 42" H x 57" W x 29"D
- Strong groove-construction
- · Mar-resistant wood grain finish
- · Options, drawers & face plate
- · For ham or home computer
- · Visa and Master Charge

CLUTTERFREE MODULAR CONSOLES

P.O. Box 5103 Tacoma, WA 98405 (206) 759-1611 ~ 89

ſ	Poly Paks	Juality E 58 For	Electronics Less !
	200-PRECISION RESISTORS, 19W, 13, axial [=2428]	400 for \$3	
_	10-QUAD PHONO JACKS, 4 RCA jacks on 2 x 11/2 Bakelite strip, (#6249) 2.99	20 for \$3	
	25-RCA PHONO PLUGS, popular audio/speaker plugs, 100% material, (=3293) 2.99	50 for \$3	
	25 SLIDE SWITCHES, various shapes, sizes, and types 2004 2726 2.99	50 for \$3	
	50-TRANSISTOR ELECTROLYTICS, epoxy encapsulated, asst. values, =2747 2.99	100 for \$3	
	175 HALF WATTERS, 100%, color coded resistors, asst. values, (*3046)	350 for \$3	
	20-SLIDE VOLUME CONTROLS, various values & types, for Hi Fi, etc. (#3057) 2.99	40 for \$3	
	20-PANEL SWITCHES, assorted rotary, micro, slide, etc. (6629) 2.99	40 for \$3	
	20-PAIRS-RCA PLUGS & JACKS, popular for Hi-Fi, speakers, etc. -6630	40 for \$3	
	60-IN914 SWITCHING DIODES, 4 nsec. axial, glass, untested, (+6632) 2.99	120 for \$3 Bi	uv One \$2,99er.
	4-2N3055 NPN TRANSISTORS, 115 watts, 15 amps, TO 3, 1001 material, (6633) 2.99	8 for \$3	.,
	250 CERAMIC CAPS sest tubulars NPO's temo coefficient etc	500 for \$3	Get 2nd
	SO-THERMISTORS, various types & styles, neg. coefficient, 100%, 4089	100 for \$3	Got Lind
	30-INSTRUMENT KNOBS. for half round shafts, some w/pointers, 1-6498 2.99	60 for \$3	same cat. no.)
	10-LINE CORDS, heavy-duty, 18 gauge, 6, molded plug, 2 cond. 6499 2.99	20 for \$3	
	10-2N3055 MDBBT TRANSISTORS, manuf. fallout, TO 3, U test, 16624	200 for 53 FO	or 1 Penny More!
	35-STEREO INDICATORS, tiny red 1.5V bulbs, for Hi Fi replacement, 6244 2.99	70 far \$3	
	40-800V 1A RECTIFIERS, type IN4006, epoxy, axial leads, 6245	80 for \$3	ORDERING
	9-DIGIT READOUTS, flat pak w/bubble mag. 120 high, 14 pin, 1+5558	18 for \$3	INSTRUCTIONS
	20 NE-2 BUILES W/RESISTOR mean mines right into 110 VAC (6630) 2.99	40 for \$3	INSTRUCTIONS
	15-RCA PHONO JACKS, popular Hi-Fi Jack on a Bakelit strip, =6230	30 fer \$3 @ C	check boxes in front of i
	200-HI-QUALITY RESISTORS, asst. carbons, some metallic, some Sters. (+6627) 2.99	400 for \$3	2 99ers desired
	150 "4000" RECTIFIERS, IN4000 series, may include: 50 to 1000V, 2417 2.99	300 for \$3	ndicate OTY Desired On
	3 SWIFL DED AUDIO CARLES 3 could with DCA plugs at each and (6412) 2.99	100 for \$3 0 1	Ling To Lott Of Box
	200-PC-SEMICON SPECIAL, assorted semis of all types, Untested material, 3300 2.99	400 for \$3	Line to Left Of Box
	200-PRE-FORMED 1/2 WATTERS, popular values, some 5 & 10%ers, 16246 2.99	400 for \$3 .	complete coupon section
	30-SCRs & TRIACS, assorted values, 10 Amp TO 220, untested, (6337) 2.99	60 for 53 0 (Cut out ad along dotted
	40 FDCF CONNECTORS used A & 6 min 2 sided or leads (#6385)	50 for \$3	line and mail to:
	6-MINI-MOTORS, Type RE56, 1.5-6 VDC, color-coded wire leads, 1=6718	12 for \$3	mie and man to.
	24-MINI BULBS, asst. voltages & base styles, some colored, (#6757)	48 for \$3	Olu Ook (P)
	40-STRAIN RELIEFS, asst. types, styles, & sizes. (#6756)	80 for \$3	OIU PORJ
	3. NEAVY DUTY AUTO CHOKE, fulters 12 VDC (54 open frame, (6750) 2.99	6 for \$3	
121	10-5K CONTROLS, thumbwheel type, single-turn, vert. mt. #6705] 2.99	20 for 53 D (BOX 042 72 12
	4-CHROME PLATED ALARM SWITCH, spst, N.C. momentary, (#6742) 2.99	8 for \$3	. DON 342 13 12
	8-LED LAMPS, 2V red LED in chrome-colored assembly, w/hardware, 15702 2.99	16 for 33 SC	UTH LYNNFIELD
	A TAPF NEADS record/play stores & mono w/plues 11 leads (\$973) 2.99	H for \$3	144 01040
1	10-RESISTOR LEDS, asst. red. green, & yellow jumbos, 5V. =6761	20 for \$3	MA. 01940
Ser Feat	nd For Our FREE Catalog Today! Total Amount Please Add St uring sensational savings on Computer	of Order \$ 3 for Postage &	Handling
Peri	pherals, Speakers, Transformers, Solar Pro-		

ducts, Fans, Stereo Equipment, Relays, and a wide variety of other diverse electronic components. Take advantage of our 25 years as America's foremost supplier of discount electronics.

For Faster Service

1-617-245-3828

Order By Phone

VISA





International's TV-4300 is a high performance satellite receiver that tunes all channels within the 3.7 — 4.2 GHz band. Standard dual audio output provided at 6.2 and 6.8 MHz. Others available. The TV-4300 is a fully packaged and assembled receiver complete with a built-in LNA power supply, built-in AFC,' tuner, control circuitry and power cable. All output levels compatible with video monitor and VTR input. Easy to use! Simple tuning!

ATTENTION HAMS! Earn a "FREE" Antenna, Tower or BOTH!

If you are employed by a company that could use a high lift work platform, as shown below, you may earn a new antenna system FREE.





Select These Options . . .

2
FINE TUNE
6
Faleflite Romote
PPP
HOF
CHANNEL

Remote tuning control \$99.50 Six frequency, crystal control, audio with stereo output. (Factory installed 6.2 and 6.8 MHz crystals supplied) \$89.50 Other audio frequency crystals \$9.50 ea. Model TV-4300A . . . supplied with remote control and six frequency, crystal control, audio with stereo output \$1,149.00

-36

Write for information.



INTERNATIONAL CRYSTAL MANUFACTURING CO., INC. 10 N. Lee, Oklahoma City, Oklahoma 73102, 405-236-3741 With today's inflationary times, this may be the perfect opportunity to upgrade your station with no drain on the family budget.

Contact Jerry Flatt at WILSON SYSTEMS for the details on this offer ... call Toll Free (800) 634-6898.



For your TRS-80 . send & receive CW/RTTY MACROTRONICS, inc. FEATURES M80 Software, PC Board, Manual \$149 Auto Send & Receive RTTY & CW CM80 As above in Cabinet \$279 Connects to TRS-80 User Port TM80 As above plus demodulator & AFSK \$499 & Key head phone jacks M800 Adds advanced RTTY to M80 / CM80 / TM80 \$99 10 message memories 255 char. ea Uses builtin PLL or external TU DISK BASED RTT Includes hardware: cassette & manual Morse tutorial-10 lessons-corrects mistakes * DISK BASED - MAILBOX - ANY STONO simplest, fastest way to learn the code tor the TRS-80 Morse practice-random 5 letter words. Leove o messoge in o molibox (on dox Auto numbering contest keyer Interactive graphics custom PIX Hood any message from als Autotransmitter control PTT Requires Level II Basic & 16K RAM me system instruction List current colls in molibor nized with your Nome & Collision TRS-80 is a recognized trademark of Tandy Corporation And much much more 150 Write or call Custor for complete catalog (\$100 with M800 "Trade-in") Write or call for ordening information. Requires M80 MACROTRONICS, inc. ® CMBO or TMBO plus 32K TRSBO Disk System 1125 N. Golden State Blvd. / Suite G Turlock, CA 95380 (S) V 44 (209) 667-2888 / 634-8888 We are experiencing telephone difficulties, please keep trying. California residents add 6% to

• HEAVY DUTY • HIGH QUALITY • RUGGED • RELIABLE •



SPECIAL FEATURES

- SOLID STATE ELECTRONICALLY REGULATED
- FOLD-BACK CURRENT LIMITING Protects Power Supply from excessive current & continuous shorted output.
- CROWBAR OVER VOLTAGE PROTECTION on Models RS-7A.
 RS-12A, RS-20A, RS-35A, RS-20M & RS-35M
- · MAINTAIN REGULATION & LOW RIPPLE at low line input Voltage.
- HEAVY DUTY HEAT SINK . CHASSIS MOUNT FUSE
- THREE CONDUCTOR POWER CORD
- ONE YEAR WARRANTY . MADE IN U.S.A.
- VOLT & AMP METER ON MODELS RS-20M & RS-35M

PERFORMANCE SPECIFICATIONS

- INPUT VOLTAGE: 105 125 VAC
- OUTPUT VOLTAGE: 13.8 VDC ±0.05 volts (Internally Adjustable: 11-15 VDC)
- · RIPPLE: Less than 5mv peak to peak (full load & low line)
- REGULATION: ± 05 volts no load to full load & low line to high line Pri
 Other popular POWER SUPPLIES also available: (Same features and specifications as above)

Model	Continuous Duty (amps)	ICS* (amps)	Size (in.) H X W X D	Shipping Wt. (lbs.)	Price
RS-35M	25	35	5 X 11 X 11	29	\$167.95
RS-35A	25	35	5 X 11 X 11	29	\$149.95
RS-20A	16	20	5 X 9 X 101/2	20	\$99.95
RS-12A	9	12	41/2 X 8 X 9	13	\$74.95
RS-7A	5	7	3¾ X 6½ X 9	8	\$54.95
RS-4A	3	4	3¾ X 6½ X 9	5	\$39.95

*ICS — Intermittent Communication Service (50% Duty Cycle) If not available at your local dealer, please contact us directly.





ASTRON 20 AMP REGULATED POWER SUPPLY Model RS-20M

16 Amps continuous 20 Amps ICS* 5" (H) \times 9" (W) \times 10.5" (D) Shipping Weight 20 Ibs. Price\$117.95



Inside View - RS-12A

2852 Walnut Unit E Tustin, CA 92680 (714) 835-0682 / 358 World-famous Radio Amateur Callbooks, the most respected and complete listing of radio amateurs. Lists calls, license classes, address information. Loaded with special features such as call changes, prefixes of the world,standard time charts,world-wide QSL bureaus, and more. The U.S.Edition features over 400,000 listings, with over 100,000 changes from last year. The Foreign Edition has over 300,000 listings, over 90,000 changes. The new 1981 Callbooks will be available on December 1, 1980. Place your order now.

	Each	Shipping	Total
US Callbook	\$17.95	\$2.55	\$20.50
Callbook	\$16.95	\$2.55	\$19.50
Order both t \$37.45 includ	books at the	e same	time for
Order from y the publisher for shipping.	All direct of Illinois re	or dire orders a sidents	ctly from idd \$2.55 add 5%
Sales lan. S	PECIAL LI	MITED	OFFER!
(AL		Amateu	ir Radio
AL AL		Emble	m Patch
AMATEUR RADIO	only s	52.50 p	ostpaid
Pegasus on blu	le field, red le	ttering.	3 " wide x
3" high. Great	on jackets an	d caps.	Sorry, no
call letters.		ORDE	R TODAY!
✓ 61			
P 61			
P 61 RADIO AMA		ook	INC.
P 61 RADIO AMA	Dept. B	ook	INC.
P 61	Dept. B 925 Sherw		INC. ve

Steven D. Katz WB2WIK 24 Louis Drive Budd Lake NJ 07828

HV Power Rectifiers – amplifier builders should read this one

ams seem to have a propensity for using general-purpose techniques in specialized applications. For example, a fellow may try to use an inch-and-aquarter TV mast to hold up his TH6DXX beam because it is the only size that fits through the bearing in his tower. Lousy reason . . . and the result will be a perfectly good antenna strewn about his yard after the first real windstorm. Another ham may use an RG-58/U feedline to connect up his kW on two meters; after all, it handled the power just fine on 75. See my point? One mistake hams nearly always seem to make is to use low-voltage technology applied to high-voltage circuits. This approach falls well in line with the mast and coax examples above. An amateur who designs his new kW plate supply using a long string of 1N4000-type plastic rectifiers is making a mistake which likely will remind him of his error just when he begins calling that FO8!

technologies currently employed by the manufacturers of silicon power rectifiers, and only a few lend themselves to high-voltage applications. The alwaysavailable "1000-piv, 1-A" plastic diodes you find at flea markets and on retailers' shelves - usually priced at 15¢ each or so-just aren't. Aren't 1000 piv or 1 A, that is. These cheapie products nearly always are high-leakage commercial devices with weak reverse "knees" (V_R/I_R characteristics) and limited surge capabilities. After all, if these diodes were so good, why wouldn't their source sell them to high-reliability industrial houses, where the demand is high and supply is short, for much higher prices? Reason is, the manufacturers of these cheapie devices know the value of their product: nearly zero. A ham may build just one kW amplifier in his lifetime; he'll look everywhere for Eimac tubes, Jennings tuning capacitors, Dow-Key relays, and the like-all high-quality products. Why endanger the usefulness of this major investment by using scrap power-supply components?

I have seen rectifiers which were marked "1500 piv, 2.5 A" for sale at a local electronics retailer priced at 6 for \$1.00. Hmmm. I looked at them: They measured 0.125" in diameter, were 0.250" long, were made of plastic (epoxy), and had plated copper leads. I purchased 12 of these gems and made a few measurements on them when I brought them home. The very best diode of the lot "broke down" (exceeded 100-uA reverse current) at slightly over 700 volts. In the forward direction, at 2.5 A, they averaged 1.3 volts forward drop. This represents 3.25 Watts of power dissipated in only one direction. Add in the 100 uA of leakage at 700 volts in the other direction (70 mW) and we find that this diode would have to dissipate 3.32 Watts minimum in a 700-V ac application - an awful lot of power for a device the size of a 1/2-Watt resistor.

When you consider that these devices are soldered together, i.e., the leads are formed like nail-heads and soldered to the metallized silicon die inside the diode, it becomes very evident that the overall reliability of a device of such small volume dissipating over three Watts of power is questionable. Have you ever touched a 1/2-Watt resistor which was actually dissipating one-half Watt? Ouch!

There are different

Another limitation of the soldered-together approach is surge current capability. Ever turn on a piece of gear which immediately blew a fuse? Often, it is the power rectifiers which blew, from surge or inrush current. In a typical power supply, the rectifiers charge a capacitor which represents a very low impedance at the operating frequency (in a line-operated system, this is 60 Hz for half-wave, 120 Hz for full-wave designs). Before the capacitor charges up to its working dc potential, it may look like a

Tomorrow's Technology – Here Today!

THE YAESU FT-207R

The "horse-and-buggy" days of crystal-controlled handies are gone! Yaesu's engineers have harnessed the power of the microprocessor, bringing you 800 channels, digital display, memory, and scanning from a hand-held package. Only with Yaesu can you get these big performance features in such a compact package.

BNC Antenna Connector

Squeich Control and Tone Squeich On/Off ~

Audio Gain Control

Condensor Mike

- · 4 bit CPU chip for frequency control.
- Keyboard entry of all frequencies
- Digital frequency display.
- 800 channels across 144-148 MHz.
- Up/Down manual scan, or auto scan for busy/clear channels. 10 kHz scanning steps.
- Five channels of memory
- Priority channel with search-back feature.
- Keyboard lock to prevent accidental frequency change.
- Memory backup
- ± 600 kHz or odd repeater splits.
- Display ON/OFF switch for battery conservation.
- Equipped with rubber flex antenna, wallmount battery charger, earphone, shoulder strap, and belt clip.
- · Switchable RF output 2.5 watts (minimum) or 200 mW
- Earphone for private listening
- · 2 Tone (Touchtone®) Input from Keyboard
- Highly reliable LED frequency display (works in cold temperatures and does not fade with age)

Clear/Busy Auto Scan Selector

- Earphone Jack

---- Repeater/Simplex Offset Switch

Remote Speaker/Mike Input

Channel Busy Lamp



YAESU ELECTRONICS CORP., 6851 Walthall Way, Paramount, CA 90723 (213) 633-4007 YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246 dead short, drawing, for the first few cycles of operation, considerably higher current than the rectifiers can withstand. In fact, it is not uncommon for (lowvoltage) computer-grade electrolytics to be such effective shorts that they attempt to draw several hundred Amperes of inrush current, limited only by the resistance of the power transformer and the saturation effects of its core. This surge current may be a hundred times the normal operating output current of the supply and can cause rectifier failures in an otherwise sound design. The problems caused by surge currents are numerous, but one may be solder fatigue in the rectifiers: The solder bonds soften as the result of prolonged high-current operation, then harden when the power is removed. This thermal cycling weakens the bonds and may cause a failure.

So much for surge currents. How about avalanche characteristics? This term describes the manner in which the silicon junction breaks down in the reverse mode (in normal line rectifier applications, this mode occurs at a 60-Hz rate) and at what voltage the junction enters breakdown. Typical double-diffused junction rectifiersthe most common type used for commercial applications, due to the inexpensive process employed—can be built easily to block 500 volts or so in the reverse direction. 1000 volts is an entirely different story and requires higher-resistivity silicon and tighter process controls. It has been my experience, after testing many lots of devices, that most "1000volt" double-diffused parts, like the 1N4007, break down well below their rated 1000 volts. What can we do? Sue the manuacturers? Nope. You see, unless one is very careful, the reversevoltage test can be destructive, and most manufacturers accept no responsibility for devices which are field-tested unless tight testing controls are employed and proven acceptable.

Where does that leave us hams? Holding the bag, I'm afraid, unless we deal exclusively with sources which have high scruples and specialize in highvoltage technology.

Even if the rectifiers used actually meet or exceed their rated reverse voltage specifications, what happens if they're not matched for this characteristic? Absolutely nothing, as long as no one diode in the string is approaching breakdown or avalanche. We can assume that even a poorly-made power rectifier in the oneto-three-Amp region probably does not exceed 10-20-uA leakage at room temperature if operated well below its rated breakdown voltage. Except in extremely high-voltage (or low current) applications, this represents such a small amount of power (e.g., 500 V \times 10 uA = 5 mW) that it is not worth worrying about. Equalizing resistors wired across every rectifier in a string are, therefore, a waste of power and money and create an additional liability in the system: A resistor could fail. By the way, the temperature coefficient of breakdown voltage for a silicon junction is positive-the hotter the junction, the higher the breakdown voltage. This is, of course, a positive feature of a silicon rectifier. An effect to consider, however, is the increase in leakage current with an increase in junction temperature. Silicon devices double in leakage about every 10° C,1 and in many power-supply applications, the junction tem-



Fig. 1.

peratures will exceed 100° C; often, power rectifiers will exceed 100-uA leakage at this temperature. At 500 volts V_R , this is 50 mW, not an insignificant value.

Matching rectifiers for forward characteristics can be important since it is in the forward-or conduction-mode that the rectifier will be dissipating real power. Fortunately, most silicon power devices built with the same technology will offer similar forward characteristics-roughly one-volt drop per junction at rated Io and 25° C. The temperature coefficient of this characteristic is negative, i.e., the hotter the junction, the lower the forward drop at a given current. Packaging also is a consideration which will determine the reliability and life of a silicon rectifier. Many inexpensive devices are cased in epoxy, a hard plastic molded around the tiny silicon die to protect and insulate it and the fragile lead bonds. Some diodes use a glass sleeve to hermetically seal out contaminants which would gradually increase surface leakage of the silicon and lead to a failure; sometimes, the glass sleeve also holds the leads on. This is not a great way to build

power semiconductors! Old-fashioned, "top hat" leaded rectifiers built in type DO-1, DO-2, and DO-3 cases are just that: oldfashioned. They rely on the thermal impedance of a soft-solder bond to just one side of the silicon die to conduct heat away from the junction; they also are "cavity" devices, whose characteristics can change as the result of mechanical shock. Not a great choice for that contest rig which gets bounced up the side of a rocky mountain. As this discussion relates primarily to ac-line-operated linear-type power supply designs (direct conversion of 60-Hz power to dc power), we have intentionally avoided the subject of switching characteristics of rectifiers. These characteristics, called forwardrecovery and reverse-recovery expressed in subsecond increments (or dv/dt expressed in volts per time interval, usually us), do not normally become important until operating frequencies far exceed 60 Hz. However, a considerable mismatch in trr (reverserecovery time) characteristics, especially if one or more diodes in a string are very slow to recover from forward saturation, can

YOU ARE LOOKING AT EVERYTHING THAT IS NOT ON SALE THIS MONTH AT HAM RADIO CENTER

FOR BEST PRICE – FAST DELIV **CALL TOLL - FREE** ARADIOCENTER - 32

8340-42 Olive Blvd. • P.O. Box 28271 • St. Louis, MO 63132



cause the fastest diode in that string to be overstressed for a lengthy enough period to cause its deterioration or destruction.² It is wise, therefore, to use at least mediumrecovery rectifiers—typically rated 2 to 5 us—in reliable 60-Hz power supply designs where the devices are used in series.

So far, we've discussed a lot of "don'ts":

1. Don't use long strings of low-voltage rectifiers.

2. Don't use cheapie devices whose ratings are nearly always overstated.

3. Don't use miniature diodes which will dissipate excessive power in your application.

 Don't use devices with limited or unknown surge current ratings.

5. Don't use "1000-V" diodes at this rating, but operate comfortably below their V_R capability when using in series.

6. Don't use equalizing resistors – they're just a cover-up for having selected the wrong semiconductors for the job.
7. Don't use power rectifiers which are built like small-signal devices, e.g., epoxy, glass-sleeved pressure-bonded, top-hat axials, etc.
6. Don't use equalizing of half the transformer's secondary; for a full-wave bridge, each rectifier must block 1.41 times the rms voltage of the transformer secondary.
To further illustrate the examples in the last paragraph, if you have a plate transformer whose secondary voltage is 2000 V

manufacturers of these assemblies are much better equipped than the average ham to select the proper devices to use and then measure the overall results.

A conscientious manufacturer will use hermetically-sealed, internal heatsink devices, which are high-temperature metallurgically bonded (not soldered) together, then screened and selected for characteristics which will allow trouble-free series operation, before assembling the finished product. This may sound like an expensive process, but manufacturers set up to build such assemblies in large quantities can do so quite economically.3

Calculate the piv requirement of the rectifier or assembly selected. For example, if the configuration is a full-wave center-tap, each rectifier has to block 2.82 times the rms voltage of half the transformer's secondary; for a full-wave block 1.41 times the rms voltage of the transformer secondary. To further illustrate the examples in the last paragraph, if you have a plate transformer whose secondary voltage is 2000 V rms and you desire to use a full-wave bridge rectifier circuit, each leg of the bridge must be capable of blocking at least 2000 × 1.41 = 2820 volts with each half cycle. This assumes a nominal ac line voltage equal to and never exceeding the primary voltage rating of the transformer; this also assumes that under no-load conditions, the rms voltage delivered by the transformer doesn't rise above its full-load voltage (transformers are typically rated at some rms voltage at some load current, like 2000 V at 500 mA). These are poor assumptions!

rated at 1 kVA (equivalent of 1-kW resistive power)say, 2000 V at 500 mA-will rise in secondary voltage under no-load conditions by about 10% or, in our example, to 2200 V. In addition, it is not uncommon for ac line voltage fluctuations to swing "upward" another 10% or so-say, from 117 V rms to 128.7 V rms-which transforms to 2420 V in our example. This would require a rectifier bridge rated at 3412 V per leg as a minimum, and even this value does not include any protection factor for short-duration transients.

So, you see that while our initial calculations led us to believe that a 2800-piv rectifier assembly might be used in each leg of the bridge described, in truth we should use at least 3500-piv assemblies as an absolute minimum; 5000piv rated assemblies would not be overkill to afford us some protection against unexpected transients.

Next, estimate surge cur-

tor in series with each ac input to a bridge as described above (2 kV rms secondary) will limit surge current to 40 Amperes maximum while dissipating only 8.75 Watts per resistor and degrading power supply regulation by about 1%. A compromise, surely, but not a bad one; surge protection may be switched "out" just a moment after turn-on if one wishes to conserve power and enhance regulation during normal operation.

Next, determine the continuous operating current requirements placed upon the rectifiers based on circuit configuration and operating habits. I always design a power supply for continuous duty unless size and weight restrictions are a consideration. AM, FM, RTTY, and SSTV are pretty much continuous-duty modes. SSB and CW may be low- or high-duty cycle modes, depending upon voice characteristics, audio processing, keying characteristics, etc. The thermal time constant of most rectifier assemblies in the low kilowatt region (say, 1/2 to 3 kW) is very short, which means the rectifiers will reach operating temperature from internal heating rapidly-probably in less than one minute of keydown time. Therefore, just because one keeps his transmissions reasonably short does not mean that the rectifiers aren't reaching their operating temperature. Most kW-region, highvoltage supplies will never have to deliver more than one Ampere dc continuous. Those folks who are fortunate enough to own a pair of 4-1000s or 8877s may wish to design a power supply capable of delivering 2 A dc, but don't brag about this on the air, lest the FCC wonder why you need such a big supply!

8. Don't use devices of unknown or poor reverserecovery characteristics, especially in a series string.

Well, what should we do? Thought you'd never ask.

When possible, use highvoltage rectifier assemblies manufactured by a reliable power rectifier house, rather than building your own assembly by wiring a string of discrete devices in series. These high-voltage assemblies are made of several rectifiers in series, of course-it is very difficult to manufacture a single junction which can block much over 1000 volts successfully and otherwise maintain the characteristics of a rectifier-but the

Normally, a transformer

rent requirements. I say "estimate" because there usually are unknown factors involved, like transformer efficiency, saturation effects of its core, and the discharged resistance of the input filter capacitor. However, one can make a worst-case surge current calculation based on transformer secondary resistance. If the resistance of your transformer secondary winding is 20 Ohms and the secondary voltage is 2000 V rms, the worstcase surge current is Epk/R (2800/20), or 140 Amperes.

Actually, the surge current will not be quite this high. If your transformer secondary winding resistance measures very low or your input filter capacitor is very large, you may wish to add some series resistance in each input leg to the rectifier bridge to act as surgecurrent limiters.

A 35-Ohm, 10-Watt resis-

In a full-wave circuit, each rectifier conducts for

CENTRAL NEW YORK'S LARGEST HAM DEALER HOLIDAY SALE DAYS

Radio World

YOU MIGHT BE ABLE TO BEAT OUR PRICES . . .

. . . BUT YOU WON'T BEAT OUR SERVICE



ICOM IC720



KENWOOD TS-830S



YAESU FT-707



ALPHA 76A

Season's Greetings From Our Staff

Warren/K2IXN Bob/WA2MSH Alan/WA2MSI Norman/K2KLV Jack/WB2LCP Chuck/WA2GJN Bev/K2TPE Val/KA2GNA





KENWOOD TS-130S



All Sales Over \$750.00 Will Entitle You To A FREE 1981 Callbook Until December 31st. OUT OF STATE CALL TOLL FREE **1-800-448-9338**

Featuring Kenwood, Yaesu, Icom, Drake, Ten-Tec, Swan, Dentron, Alpha, Robot, MFJ, Tempo, Astron, KLM, Hy Gain, Mosley, Larsen, Cushcraft, Hustler, Mini Products, Bird, Mirage, Vibroplex, Bencher, Info-Tech, Universal Towers, Callbook, ARRL, Astatic, Shure.

WE SERVICE EVERYTHING WE SELL! CALL FOR A QUOTE . . . YOU WON'T BE DISAPPOINTED



We are just a few minutes off the NYS Thruway (I-90) Exit 32



Bob

WA2MSH

Warren K2IXN ONEIDA COUNTY AIRPORT TERMINAL BUILDING ORISKANY, NEW YORK 13424

N.Y. Res. Call (315) 337-0203

only half the input wave, and therefore must handle only half the dc output current. Even a two-Amp supply can be built using rectifiers rated at one Amp Io (continuous output current), as long as the rectifier rating is compatible with its operating temperature. It is wise to assume that under some conditions the rectifier junction temperature will be at least 100° C. This may sound very hot (and it is, for human beings), but silicon power rectifiers normally work in this region and they don't mind, as long as one derates them properly. The derating curves for one popular kWlevel rectifier assembly are shown in Fig. 1.4

As you can see, the single-phase, full-wave current rating for this assembly is 500 mA from 25° C (77° F) to about 55° C (131° F); then it derates in a nearly linear fashion to zero current at 175° C (347° F). This represents a derating factor of about 4.17 mA/°C (2.31 mA/°F), calculated: [(lo @ $T_a) - (I_o @ T_{max})]/(T_{max} -$ T_a) Amps/degree, where I_o is rated output current, Ta is ambient temperature (usually 25 or 55° C) and Tmax is the maximum rated temperature of the device or assembly. At 100° C, then, the "500-mA" rectifier assembly shown is actually rated at about 312 mA; at 125° C, it is rated at about 208 mA. Operating temperature equals ambient temperature plus thermal rise from junction heating and is sometimes difficult to calculate. To allow margin for error, it is best to use assemblies rated for your actual operating current at some rather high temperature (like 100° C). It is wise to take manufacturers' data sheet ratings literally and not exceed them. Note that the temperatures expressed in Fig. 1 are ambient, for free

Type No.	Peak Inverse Voltage Per Leg	Average Rectified Current	Maximum Forward Voltage @500 mA/Leg	One Cycle Surge Current	Reverse Current/Leg @ PIV	Case Length
	55°C	55°C Mtg.	25°C	55°C	25°C	Α
	Volts	Amps	Volts	Amps	uA	Inches
SDH5KM	5 kV	1.0	7	50	1.0	3.36
SDH10KM	10 kV	1.0	14	50	1.0	3.36
SDH15KM	15 kV	1.0	20	50	1.0	4.04
*SDHC5KM	5 kV	2.0	7	50	1.0	4.72
SDHD5KM	5 kV	1.0	7	50	1.0	4.72
*SDHC10KM	10 kV	2.0	14	50	1.0	4.72
SDHD10KM	10 kV	1.0	14	50	1.0	4.72
*SDHC15KM	15 kV	2.0	20	50	1.0	6.09
SDHD15KM	15 kV	1.0	20	50	1.0	6.09

air. There is a multiplier table shown which reveals that the current rating for this assembly is substantially higher if external (oil or forced-air) cooling is introduced, as is often the case in industrial or military designs.

Another consideration is insulation resistance across high-voltage terminals or from them to ground. At working voltages normally encountered in amateur amplifiers, even big ones, this is not a real problem, since most of us are working below 5 kV. A good ruleof-thumb dimension for high-voltage spacers or standoffs used to mount rectifiers and other highvoltage components is 0.10" per 1000 volts minimum. The same rule holds true for package length of highvoltage rectifiers. Beware of a 1/4 "-long diode rated at "5 kV." The silicon junctions inside may not break down until that level is reached, but what about the package itself or the air around it? Many subminiature high-voltage rectifiers were designed to be used in dielectric oil or fluorocarbon, not in air, and should be avoided for amateur applications.

Fig. 2.

use a commercially-manufactured complete rectifier assembly (such as a fullwave center-tap) when economically feasible, since the manufacturer has used well-matched devices therein, ensuring good balance and long life. A typical fullwave center-tap high-voltage rectifier assembly data sheet is reproduced in part here (Fig. 2⁵) as an example of a readily-available industrial product and its ratings. The SDHC-prefix devices asterisked are the center-tap assemblies and are, therefore, rated at twice the dc output current; the SDH- and SDHD-prefix devices are half-wave diodes and voltage-doubler configured arrays. (A doubler is two rectifiers in series with the center anode-to-cathode connection brought out for connection to external highvoltage capacitors.) Note the V_F-forward voltagespecified for each assembly; this is a clue to the number of junctions contained in each. This discussion, lengthy as it is, leaves out much information; it is important to note that many of the rules outlined here do not apply to low-voltage, high-current designs. If there is enough interest generated by this article, I will follow up with articles on p-n power semiconductor junctions, assembly techniques, thermal impedance ratings, switching power designs, etc.

In the meantime, most amateurs who have absorbed the material presented here should have a better understanding of high-voltage power rectifiers and their applications and ratings. Next time you look inside a kW amateurband amplifier, see what type of high-voltage rectifier system is used. It can tell you a great deal about how smart the amplifier's designer was ... and how much he cared about building a reliable product.

Silicon high-voltage rectifier assemblies are available as complete centertaps and bridges as well as half-wave devices. In fact, it is a good choice indeed to

References

1. W. Shockley, "Problems Relating to p-n Junctions in Silicon," *Solid State Electronics*, vol. 2, c. 1961.

2. H.W. Henkel, "Germanium and Silicon Rectifiers," *Proceedings of the I.R.E.*, vol. 47, c. 1958.

3. Semtech Corporation, 652 Mitchell Rd., Newbury Park CA 91320. Examples of construction and design technology used here are taken from ideas used in Semtech products. Other manufacturers of high-voltage rectifier assemblies include: Edal Industries, 4 Short Beach Rd., E. Haven CT 06512; Electronic Devices, Inc., 21 Gray Oaks Ave., Yonkers NY 10710; International Rectifier, 233 Kansas St., El Segundo CA 90245; Unitrode Corp., 580 Pleasant St., Watertown MA 02172; Varo Semiconductor, PO Box 676, Garland TX 75040; and Westinghouse Electric Corp., Semiconductor Div., Youngwood PA 15697.

4. Courtesy of Semtech Corporation.

5. Courtesy of Semtech Corporation.



ANTENNA SYSTEMS 1-800-654-3231



TET, THE LEADER IN WIDEBAND ANTENNA

DESIGN, introduces another new triband antenna to provide unmatched wideband performance on the 10, 15 and 20 meter amateur bands. This radical departure from conventional triband antenna design employs TWO DRIVEN ELE · MENTS with a rigid phasing line to couple power from the radiator element to the reflector. Phase relationships have been carefully engineered to provide extremely high gain figures without neglecting the need for high front to back ratio. The two element drive system is coupled to one parasitic director on the model HB33SP; two parasitic directors on a longer boom with the model HB43SP.

FULL BAND COVERAGE is possible without the need for antenna tuners or separate CW and phone antenna adjustments. The 1.5:1 VSWR bandwidth covers the entire 20 and 15 meter amateur bands, with a little extra for MARS operation. On 10 meters, coverage is in excess of 1 MHz.

QUALITY CONSTRUCTION and repeatable performance permit TET to deliver an antenna package without need for any tuning adjustments. All tubing is cut and pre-drilled to precision tolerances. The phasing harness and feed assembly for the two driven elements are preassembled to insure ease of construction and reliable performance.



MOVE UP with the performance oriented leader in antenna technology. Order your new high performance wideband triband antenna system from TET today.

MODEL	BANDS	ELE- MENTS	MENTS PER BAND	MAX PWR	VSWR	IMPEDANCE	MAX ELEMENT LGTH	BOOM LGTH	TURN- ING RADIUS	WIND SURFACE AREA	WIND LOAD @80 mph	BOOM DIA- METER	MAST SIZE	WT
HB43SP HB33SP	14/21/28 14/21/28	4	43	2KW 2KW	BELOW 1.5 BELOW 1.5	50 Ohm 50 Ohm	27 [.] 27 [.]	19' 8'' 13' 2''	16' 9" 15'	6.62 sq.ft. 4.73 sq.ft.	131.3 lb. 102 lb.	2'' 1 9/16''	1½-2" 1½-2"	38 lb. 27 lb.

Call Factory for ANTENNA GAIN dBd and FRONT TO BACK RATIO.

TET FACTORY DIRECT PRICE

HB43SP \$219.95 HB33SP \$174.95

Call Toll Free 1-800-654-3231







425 HIGHLAND PARKWAY, NORMAN, OKLAHOMA 73069 TEL: 405-360-6410

Keith Carter WD4LWC Route 1, Box 123 Sycamore GA 31790

Cheap Connectors for Half-Inch Hardline - at your neighborhood hardware store

Vou've just become the owner of some really nice half-inch, 72-Ohm CATV hardline, but where, oh where, will you find connectors for this prize? What will you do? What will you do? To make matters worse, you know that even if you had the money to purchase commercial connectors, they would not fit anything in your shack. And what if your fellow amateurs found out that you weren't innovative enough to come up with something as simple as

a cable connector!

Don't despair; you're not alone. I found the answer after several weeks of thinking, looking, asking, and trying every harebrained idea that came along. I found it across town in the plumbing section of the local hardware store, for less than a dollar. method of solving this problem without any cash outlay. He simply strips the half-inch hardline just as you would strip RG-8. Using two pairs of standard pliers, he screws a PL-259 connector up onto the aluminum jacket and solders the center in the normal fashion. I tried this method-and tried, and tried, and tried, until I finally decided that there had to be an easier way. (The one I did get to work lasted only two weeks before Mother Nature produced a break where the 259 and aluminum jacket joined.)

My Way

Another Way

WA4VYR, a good friend and the inspiration for my original idea, has successfully used the following



Photo A. The completed connector.

After the trip up the tower to find the broken connection, I dried my eyes and resumed my quest for a better way. When you don't know where you're going, I had been told, make an outline. Just what did I need to do the job? I wanted a coupling that was compatible with the existing system, namely, with SO-239/PL-259 hardware. And the joint needed reinforcing, I decided, in the light of my previous experience. The coupling must be small and have no clamps or sharp edges. It also would be nice if it could be weatherproofed easily. And, above all, it must be simple and cheap.

As I mentioned, the solution to all this was found in the local hardware store. This particular store had a display of brass fittings used for the installation of copper gas and water lines. Among them was a half-

FORMULA FOR 2 METER FM ENJOYMENT



79.00

Holidan Special 143-149 MHz .25 uv sensitivity mobile mount & microphone included 25 Watts (variable) Provisions for non-standard splits (CAP, MARS, etc.) **Optional AC power supply available**

THAT'S CORRECT!!!

We are convinced that the FM-88 is four times more reliable than the other 2 meter rigs being offered. To prove it to you, we are supplying the FM-88 with four times more warranty than supplied with other models - One full year instead of the normally expected 90 days.

While there are radios on the market that offer lots of "gadgets" - our past experience

has been that simplicity of operation & elimination of unnecessary "Bells & Whistles" actually removes the causes of many failures being experienced with such transceivers.

If you are shopping for a new 2 meter transceiver, don't you owe it to yourself to go with a radio that has proven itself with thousands of hours of reliable, "On the Air" operation?

Phone 1 (800) 233-0250 today to order your FM-88 or to request a detailed brochure describing this fantastic transceiver & related accessories.

The FM-88 is also available with an 800 channel, programmable scanner - order model FM-88S - \$379.00







Communications Corp. 1911 Old Homestead Lane Greenfield Industrial Park East Lancaster, PA 17601 (717) 299-7221

inch brass compression coupling.

This connector is a perfect adapter. It will fit almost perfectly over the aluminum jacket of the commonly-available, half-inch CATV hardline. It consists of the five parts shown in Photo B: the main body, two brass collets-one inserted into each end of the main body, and two brass caps. These collets constrict around the tubing being joined when tightened correctly and form an airtight, firm connection. To make matters even simpler, the main body has a rim centered inside. This allows the cable to be inserted and seated properly before tightening.

So much for the history and sales pitch. Get your parts up and follow me through the simple ten-minute assembly.

Assembly

Prepare the end of the hardline as shown in Photo C. Cutting is done best with a small tubing cutter because of its smooth cutting action. Loosely assemble the brass fitting and twist one end onto the prepared end of the CATV cable. This will be simple to do correctly since the cable will stop when it contacts the inner rim inside the brass fitting. Since the main body and end caps are machined for gripping with standard wrenches, use two wrenches and tighten this end very snugly. Be careful not to strip the brass threads, but do make sure you tighten the cap enough to compress the collet around the hardline jacket. Don't worry if the union crooks slightly. I said the fit was almost perfect!

Next, it is very important to scrape all the enamel coating from the center conductor. It won't solder if you don't. Now we are ready to slip a PL-259 onto the center by screwing it onto the foam insulation and up into the brass fitting. It probably won't go far enough to seat against the inner rim, but it will be far enough to allow the collet to tighten properly. Don't overdo the insertion bit here; remember, you'll need to be able to turn the cap of the PL-259! The rest should go without further detailed description.

Solder the center in the normal fashion and trim any excess length from it afterwards. Don't tin the inner conductor before insertion because you will find they fit very closely, and it probably wouldn't fit afterwards if you do. Presto! You now are back on familiar ground. The 259 connector should be readily adaptable to most of your amateur needs.

When I showed my discovery to KA4DPF, a close friend who is an engineer for the local power company, he remarked that this connector had a very important virtue that I had overlooked. Since direct connection of dissimilar metals always produces some corrosion, the power company uses brass intermediate connectors to prevent eventual problems. Hence, this configuration should provide years of trouble-free operation, especially if taped well when installed.

Installation

By now you should have surmised that I am relatively non-technical and am far from being an expert on antenna technology. However, some remarks about matching 72-Ohm cable with a 50-Ohm system are in order. I am told by those more knowledgeable than I am that the following conditions are found in this situation. Provided the antenna is an acceptable match to the transmitter and the 72-Ohm cable is exactly a multiple of one-half wavelengths long at the operating frequency, the transmitter will effectively "see" the antenna load at the other end regardless of the characteristic impedance of the line. Further, the expected loss from this line mismatch would be only around 1.6 to 1: probably a good tradeoff relative to a long run of RG-8, especially from a receive-loss standpoint.

I matched the system at K4QT/RPT and at my home station by inserting different lengths of RG-8/X between the hardline and the transmitter until I found one that made the total cable length appear to be the proper length. The reflected power shown on a 50-Ohm Bird 43 was less than one Watt with twelve Watts out of the transmitter. The flexible jumpers are a welcome addition also when moving and installing equipment.

I am certain that this method has its faults and I would welcome any constructive advice concerning better methods. The repeater, which was constructed from an old Heathkit® HW-202, has been operating on this system for about a year now without incident. This doesn't prove anything except that a solid-state transmitter can operate well when used in the manner described. Perhaps these ideas will be of some help to you when you come across that old CATV cable someone else doesn't want or couldn't figure out how to use!



Photo B. The five-part brass adapter.



Photo C. Half-inch CATV hardline, adapter, and PL-259.

102 73 Magazine • December, 1980

ATR-6800 gets'10 dB'boost



The proven RFI proof system for RTTY/CW is now available with applications program modules. Multiply your computer power to make amateur radio a real blast. Our first plug-in module adds 10 ham oriented programs such as: SSTV Transmit, Auto-CQ/Response, Mailbox, Log Keeper, and RTTY Speed-Seeker with more modules, including BASIC to follow soon.

All utility programs permanently stored in ROM ready to execute from the keyboard. Application module number one: \$189. Interface connector mounts on rear of the ATR-6800 free with first module. ATR-6800 with 9" monitor: \$1995, with companion printer: \$2445. There's never a dull moment here at Microlog Corp., 4 Professional Drive, Suite 119, Gaithersburg, MD 20760. Telephone: (301) 948-5307.



MICROLOG

Innovators in Digital Communications









Highest prices ever on recent U.S. Military surplus, especially on Collins equipment or parts. We Pay freight. Call collect for high offer. (201) 440-8787. 35 Ruta Court, HAMS...with TRS-80* Computers **GET ON RADIOTELETYPE**

201-493-4511 EVE'S

REGENCY

N.J. RESIDENTS

ADD 5% SALES TAX

S 89

105

209

279

R804

R106

M100

M400

\$229

360

290

290

129

199



with **BIT-BYTER** Complete system includes BIT-BYTER interface AND



Now with courtesy beep and beacon capability.

REPEATERS 220 144

New and Improved Receiver and Transmitter

(Included in All Repeaters)



programmable, Fully adjustable, time out (.5-7 min.), hang time (0-1 min.), identifier (1-10 min.), tone, speed, volume, L.E.D. outputs, low current drain, CMOS logic, plugs for easy installation and removal plus much more \$99.95.

COR Identifier: All on one band,

Basic Repeater \$649.95

2M 130-175 MH/Basic Repeater for 2 meters with all the features of the Hi Pro Mk1 less the power supply and front panel controls and accessories.

Maggiore Electronic Laboratory ~46

845 Westtown Rd. West Chester, PA 1938O Phone (215) 436-6051

450 MHz also available.

OPTIONS

Duplexers Basic auto patch Matching cabinet .0005% High stability crystals

Hi Pro Mk I

144 or 220 MHz \$849.95

rt Pto Mk

PLUS SHIPPING PA Res. add 6% tax



The BEST in Code Converters THE INFO-TECH M200-F TRI-MODE CONVERTER INFO-TECH M-200F

NTE ---- S48

O.

0 CLEAR

(Baudot & ASCII) to video, and serial Baudot or ASCII for hard copy

Morse Reception: 6-55 wpm standard (simple user adjustment for higher speeds). Automatic speed tracking & word space adjustment.

RTTY/ASCII Operation: Decodes RTTY (45, 50, 57, 74, 100 Baud) and ASCII (110 & 300 Baud), Auto CR/LF, automatic threshold control, selectable unshift on space, limiter is switch selectable, solid state tuning "meter". Demodulator has 3 fixed shifts and 1 tunable shift, user selectable printer outputs in ASCII or Baudot for all modes with crystal controlled baud rate generator. RS232, TTL & isolated loop outputs. User adjustable autostart. Price S

For the best deal on •AEA•Alliance•Ameco•Apple•ASP •Avanti•Belden•Bencher•Bird•CDE •CES•Communications Specialists Collins
 Cushcraft
 Daiwa
 DenTron DrakeeHustlereHy-GainelcomeIRLeKLM Kenwood Larsen Macrotronics MFJ Midland
 Mini-Products
 Mirage
 Mosley NPC
 Newtronics
 Nye
 Panasonic Palomar Engineers
 Regency
 Robot Shure-Standard-Swan-Tempo • Ten-Tec• Transcom• Yaesu

HOLIDAY SPECIALS

KENWOOD IR-760	0
closeout	\$269
ICOM IC-255A	\$329
TEMPO S-1	\$239
with touchtone	\$260

Video Display Formats

Converts Morse

& RTTY

(User Selectable)

16 lines x 32 characters, 16 lines x 72 characters, 25 lines x 32 characters, 25 lines x 72 characters 50 or 60 Hz operation. Cursor, on or off

Built-in 115/230v power supply

or See These Dealers

A-1 Technik Blomberg 3 D-5882 Meinerzhagen 2 West Germany

Cohoon Amateur Supply 307 McLean Avenue Hopkinsville, Kentucky 42240 (502) 886-4534

Colmay Products 14903 Beachview Ave White Rock, B.C. Canada V4B1N8 (604) 536-3058

Dialta Amateur Radio Supply 212 48th Street Rapid City, South Dakota 57701 (605) 343-6127

Germantown Amateur Supply 3202 Summer Avenue Memphis, Tennessee 38112 1-800-238-6168

Gilfer Associates, Inc. 52 Park Avenue Park Ridge, New Jersey 07656 (201) 391-7887

Global Communications 606 Cocoa Isles Blvd Cocoa Beach, Florida 32931 (305) 783-3624

Ham Radio Center 8342 Olive Blvd. St. Louis, Missouri 63132 1-800-325-3636

Marcucci SPA Via F LLI Bronzetti 37 20129 Milan, Italy





1633 Wisteria Court • Englewood, Florida 33533 • 813-474-9518

N & G Distributing 7285 NW 12th Street Miami, Florida 33126 (305) 592-9685, 763-8170

Mastercharge, Visa

We accept

FOB factory

VISA

V 35

5 O 2

0

REVERSE

WICE 0

0

LIMITER

Radio World Terminal Building Oneida County Airport Oriskany, New York 13424 (315) 337-2622

Ray's Amateur Radio 1590 U.S. Highway 19 South Clearwater, Florida 33516 (813) 535-1416

Universal Amateur Radio 1280 Aida Drive Reynoldsburg, Ohio 43068 (614) 866-4267

ELECTRONIC

EQUIPMENT



KENWOOD TR-7800, **TR-9000 and TR-2400** all now in stock... Call for great Erickson prices today!

APPLE: Buy a 16k Apple II or Apple II Plus for \$1195; get 32k more memory, installed, free! Complete with disc drive, only \$1739

Apple prices include prepaid shipping within continental U.S.A.

CALL TOLL FREE (outside Illinois only)

HOURS: 9:30-5:30 Mon., Tues., Wed. & Fri. 9:30-9:00 Thursday KISA. 9:00-3:00 Saturday



Eugene F. Ruperto W3KH RD 1, Box 366 West Alexander PA 15376

The Microwave Midget - this WEFAX converter features something different - an active mixer

Several years have passed since NOAA (National Oceanic and Atmospheric Administration) graduated from VHF WEFAX (Weather Facsimile) satellites to geosynchronous microwave satellites. True, some of the polar-orbiting satellites transmitted data on S-band, besides the low-frequency product usually found on 137.5 and 137.62 MHz, but only the bravest of souls at-

tempted to track such a fast-moving target with a narrow beamwidth dish. Besides, I was content to extract weather pictures from the low-altitude polar orbiters and occasionally, for some real DX, from ATS-1 or ATS-3 parked some 22,500 miles above the equator. of Converting the SMS/ **GOES WEFAX Frequency** (1691 MHz) to the Existing APT/WEFAX Frequency (137 MHz)." This was followed up with an APT Information Note (76-W4) in September, 1976, advising all ground stations of the proposed S-band broadcasts and schedules. Clearly, the handwriting was on the wall, and many of us (some reluctantly) were dragged into the realm of microwaves. The rush to 1691 MHz was not especially spectacular, and for most of us, it resembled a slow and laborious climb. Microcomm rose to the occasion with a line of inexpensive modules, and a fine article by WB8DQT1 showed us how to use them, besides providing a wealth of data

on dishes, gain figures, path loss and margins.

The annual gathering of weather-satellite buffs at the Dayton Hamvention in 1979 unearthed several home-brew devices, but I believe none has been described in print with the exception of one produced by G8FCD. He wrote about his METEOSAT (Europe's counterpart to GOES) Earth station in recent issues of Wireless World.² The heart of my system is an active mixer-a mixer with conversion gain rather than the conversion loss associated with diode mixers. The expected groundlevel signal of -134 dBm is not exactly an S-meter needle bender, so every bit of help you can get in the way of gain in the system is to

In April, 1976, NOAA published Technical Memorandum NESS 54, by John Nagle, entitled "A Method



Photo A. The six-foot dish and feedhorn. 73 Magazine • December, 1980

106



Fig. 1. System configuration for the active-mixer converter.



Photo B. No land mass is visible in this photo of the NE quadrant. Placed above and overlapping Photo C, covering the SE quadrant, complete coverage of the eastern half of the hemisphere is obtained.

your advantage (and of benefit to your wallet) because high-gain preamps and transistors at this frequency still cost a few bucks. I was convinced of the worth of an active mixer by W6KT through correspondence and because of his success with such a device-although his differs considerably from the one about to be described. I used an almost exact copy of an active mixer described by Larkin Crutcher WA5WOW³ for 1296 MHz, with a few modifications necessary to achieve similar results.

MHz. The output signal from this cavity is coupled to an inductive link at the other end of this line. The input signal at 1691 MHz is coupled to the input cavity via a capacitive probe at one end of the line and taken off the other end of the line with a capacitive probe.



Photo C. South America's west and east coasts are visible in this picture, at lower left.

tive link of the multiplier cavity are composed of one piece of #14 wire bent into a U shape, 20 mm long with 12-mm legs. The difference signal, 137.5 MHz, is coupled to the mixer transistor by connecting a 100-pF disc ceramic capacitor from the center point (10 mm) of the U-shaped link to the base of the MRF901. The collector of this transistor uses a conventionally-tuned output circuit to the 137.5-MHz wideband FM receiver. No preamp was necessary.

The active mixer box is constructed entirely of double-sided PC board. The base is slightly longer than 88 mm \times 54 mm, and the four walls plus the center partition are made from 1-inch-high strips. The actual box dimensions are 88 mm \times 50 mm \times 25 mm. The

Circuit Description and Layout

The active mixer consists of two half-wavelength lines of #10 soft-drawn copper wire grounded at both ends of their respective cavities and tuned at their center point with 10-32 brass screws. The brass nuts are soldered inside the cavities. At one end of the multiplier cavity, a signal from the local oscillator is injected at 517.833 MHz at 5 mW, which, in turn, is multiplied by 3 to 1553.5 This probe and the induc-



Fig. 2. Schematic of the active mixer. L1, L2—#10 wire; C1, C2—10-32 nuts and bolts; L3—20 mm × 14 mm U-shaped link, #14 wire; D1—MA4882 mixer diode; L4—12 mm × 7 mm × 2 mm tab.



Photo D. NOAA product from low-altitude satellite Tiros N relayed from the ground through uplink.

center partition is slightly shorter than 88 mm to fit in the center of the box, and is notched at one end with a 13 mm × 15 mm cut out to accommodate the Ushaped link. A hole is drilled in the end wall adja#30 insulated wire to pass through and connect to the base of the transistor to provide the necessary bias. The rest of the transistor lives outside of the cavity. The low-frequency circuit for 137.5 MHz was built on a small piece of PC board and tack soldered to the back side of the baseplate for isolation. An additional one-inch strip was soldered



Photo E. Daytime infrared photo, NW guadrant.

to the baseplate parallel to the long walls and drilled for mounting on a 19-inch aluminum panel. SMA connectors were used for the input and output ports to match the Microcomm rf preamp and local oscillator, but BNC connectors should work as well. deforming the line itself downward by about 2 mm, I picked up an additional 600 microamps of collector current.

Initially, I constructed the mixer with inductive links throughout, but in actual practice ended up with more gain by cutting the input link to the signal line from ground and also the signal line portion of the U-shaped link. I accomplished this tweaking by setting the signal generator to 1691 MHz and the power to 0 dBm and turning down the calibrated attenuator. The tuning screw in the signal cavity tunes with the 10-32 screw almost all the way out with about one thread left in the cavity. The multiplier screw needed a 12-mm disk of thin brass or copper soldered to the end of its 10-32 screw to tune the line since it is too short, but the disk, with its added capacity, nicely pulls it down lower in frequency. With one 12-dB gain Microcomm preamp connected ahead of the mixer and a properly functioning output circuit attached to the MRF901, the attenuator was cranked into more than -125 dBm with plenty of

cent to the link for mounting the MRF901.

A very small hole is drilled into the baseplate near the wall for a piece of



Photo F. Back side of the active mixer.

Tune-Up and Operation

I wish I could say that everything went as smooth as silk with this project, but I traipsed with Murphy down the garden path for several months until I finally discovered that I had the collector circuit tuned to about 300 MHz. The microwave portion of the mixer apparently worked well from the start. I used a Hewlett-Packard HP-614A signal generator for a beacon/signal source for testing. Initially, I biased the MRF901 for a collector current of about 800 microamps without oscillator injection, fired up the oscillator and tuned the multiplier cavity for maximum collector current which, at this point, was 1.2 mA. By bending the Ushaped link closer to the multiplier line, squeezing the multiplier diode closer to the line, and slightly
signal showing on the receiver, so I moved everything outdoors. I attached the system to a 6-foot dish and a homemade feedhorn sporting an N connector through ten feet of RG-9 cable and picked up a fullquieting signal from SMS-GOES East. After optimizing the feedhorn for focus and polarization angle, I removed the preamp, and though the signal was a bit noisy through ten feet of cable, I think it would have made a useful picture.

Since most of the users have devised ways of mounting their converters and preamps at the antenna site, I assumed that it would be impossible to use only one preamp and expect to use the system indoors through a long run of cable. Taggart devised such a scheme using a Coleman insulated cooler and an incubator device. My dish is situated more than 25 feet from my shack and "looks" through an ancient sugar maple tree about 70 feet high with about 30 feet of leaves and branches in the way. I'm sure there is some signal absorption when the sap flows. To satisfy my curiosity, I attached another 22-foot piece of RG-9 to the existing ten-foot piece and still received a full-quieting signal! I now have the entire system indoors except for the dish, feedhorn, and thirty-two feet of RG-9 cable and one foot of RG-142/U with a total of six connectors in the line: one SMA male, four series-N males, and a double-female N "barrel" connector. (I believe I have some loss there.) The pictures shown were made with this cable configuration, but someday I hope to replace it all with one piece.

didn't use any bandpass filters in the front end because I live in a natural dish in a rural area. For a more hostile rf environment, their use probably will be necessary. The Microcomm LO is exceptionally clean, so I got away without one between it and the multiplier diode. If for some reason this localoscillator module is not available in the future, you should be able to construct one from N6TX's article4 or build your own. W6KT built a simple oscillator chain for 259 MHz and multiplied by six by replacing the multiplier diode with an MRF901.

I monitor the multiplierdiode current of the .MA4882 with a 0-15-mA meter. Nominal current is between 4 to 7 mA. The collector current of the MRF901 also is monitored with a 0-10-mA meter. By varying the bias pot, a satisfactory operating point would be from 900 microamps to about 2 mA, with some mixer noise becoming evident above this figure. The current was brought up to 7 mA without a tendency to oscillate, but the noise was objectionable and the gain started downhill. Finally, NOAA, unlike the private sector of the satellite business, welcomes the use of their service by amateurs. Bob Popham,⁵ the coordinator for the NOAA satellite service, has attended the weather satellite symposiums at Dayton for the last several years as one of the principal speakers. The weather pictures for this article were produced on a facsimile device described in my previous articles. 6,7

New Improved Adhesive Mount for the 2 Meter Avanti Mobile Antenna.

Mounts on glass – no holes!

- Receives and transmits through glass.
- Superior performance equivalent to 5/8 wave.
- Superior radiation full Omni-Directional.



It's easy to install — No holes to drill, no magnet to scratch the paint, no clamps. Uses an especially developed silicone adhesive that secures antenna to window. The capacity coupling box is simply attached with a special adhesive tape to inside of window. Worried about crimping or corroding coaxial cables? It's all inside and out of sight.

Models also available for 220 MHz and 450 MHz.

avanti" antennas

See Avanti's other new mobile and base antennas. Write for new catalog today. Send 50% for handling and postage.



10

Conclusion

For my money, the active mixer is definitely the way to go at these frequencies. I I think I'll get out my PC board and try for some converters for 1296 and 2304.

References

1. Ralph Taggart WB8DQT, "Be a Weather Genius—Eavesdrop on GOES," 73 Magazine, November, 1978. 2. Mike Christieson G8FCD, "A METEOSAT Earth Station," *Wireless World*, June and July, 1979.

3. Larkin Crutcher WA5WOW, "An Active Mixer for 1296," QST, August, 1974.

4. Paul Schuch N6TX, "A UHF Oscillator for the Purist," Ham Radio, July, 1979.

5. U.S. Department of Com-

merce, NOAA, NESS, Washington DC 20233, Attn: Popham OA/S131.

 Eugene Ruperto W3KH, "Weather Satellite Pix Printers," 73 Magazine, January, 1978.
 Eugene Ruperto W3KH, "A Satellite Receiver for the Home," Scientific American, "The Amateur Scientist," January, 1974.



Photo G. From left to right: the oscillator, active mixer, and preamp.

Jerrold A. Swank W8HXR 657 Willabar Drive Washington Court House OH 43160

The Amazing Bobtail ...Our Readers Respond - more ideas for using and modifying this easy-to-build antenna

he first week after the Bobtail article was published (May, 1980, 73 Magazine, page 44), four hams wrote me that they had built the antenna and agreed with my evaluation. The first was Jim Gray W1XU, who tried the idea which I had failed to try completely-feeding it with coax at a high-current point. He said it worked perfectly. He used 984/f, the normal quad formula, and had 34.44 feet for the separation of the top sections between verticals and 17.22 for the verticals. It was 1:1 at 14.250 MHz and 2:1 at 14.000. He planned to lengthen it a couple of inches. He worked EI2EC with a barefoot TS-820S. He then called "CQ Pacific" and landed VK1DH. He wrote, in part, "Now let the guys know that the antenna can be fed with coax-with low swr, too. It saves wear and tear on tuners and tuning. I like it, and

so does the DX." More later on the feedpoint.

Ron Chiappari N6AUV put the antenna up with three elements on 40 meters and fed it at the top with coax; he phoned me from California to tell me about it. He said it tuned up easily and was 1:1 at the design frequency. Merl W9ZSI built the antenna with voltage feed and wrote me that it was a great antenna. I then told him to try current feed, and he said it tuned up perfectly 1:1 at 14.250 MHz. He is now going to put up another complete Bobtail and phase the pair with quarter-wave spacing, driving both antennas. Bill W8YFB in Elyria, Ohio, wrote to say that he was feeding the center element voltage-fed with open-wire ladder line on 80/20/15/10 and then tied the two feeders together for a Bobtail on 40. Dave W7TO wrote me that he had talked one evening to Bob K8FN in

Troy, Ohio, who had the strongest signal from the east one night while running only 25 Watts. Of course I wrote Bob, and he said his Bobtail was suspended from three towers, and he had hung old tires at the bottom of the vertical wires so that he could mow under them. How about that? I also received a letter from "Judge" Ganzer K7SCO who has written books on antennas. He said he calls this type of current top-fed antennas "blacktop antennas" because they do not have to use buried radials in the ground. You may have guessed there are no grounds on the top-fed antennas. The center of the coax goes to the top of the vertical in the center, or at one end (as I do), and the shield goes to the flat-top horizontal section.

and that I was right about it. All agreed that it was a quiet antenna, and some wondered why. Verticals are not usually quiet.

I received a surprising number of letters from people merely telling me that they had used the antenna It is a long-range antenna and is at its best when the path exceeds 2500 miles.

This is important-when you feed it, connect the center of the coax to the vertical. I first thought I would run the coax up the center of the quarter-wave tubing and feed the top section, with the shield going to the vertical as in the case of the balun. This might work, but it would change the phasing. The three verticals are in phase because the two top sections are cancelled out when centerfed.

I am using mine with the coax to the top of the end vertical because it is more convenient. I believe that the pattern is skewed toward the west (driven) vertical and that this method is related to a full-wave longwire. I get strong reports from both the SW Pa-

cific area and the NE European area. This happens to suit me fine. I think my pattern is a four-leaf-clover pattern with the accent on the western lobes, but I cannot prove this by driving around locally with a fieldstrength meter for a pattern measurement.

Most of the hams who wrote to me used the usual formula and made the top sections 33' long and the verticals 16' 6". I used 34' at the top for each section, as Jim Gray did, and tried the verticals at 17' 3", but I had to cut the verticals back to 16' 6" to get the swr to 1:1. In the usual manner of phased verticals, I believe that the length of the top sections is uncritical, as in the spacing of phased verticals. It affects the pattern but not the resonance. The antenna is tuned to resonance with the vertical radiators.

Now you know the rest of the story. No grounds; topfed with coax; tune the vertical sections. However, Ron N6AUV said that no verticals worked well at his location in California because of poor grounds. I told him to try a method which I advised a friend in Connecticut to use one time: Lay a roll of fence wire under the antenna. He used chicken wire and it worked beautifully. No connection to the antennas -just a reflecting surface. You can buy green vinylcovered fence wire now and lay it on the grass. It blends with the grass and you can mow over it.

I noticed one thingmost of the letters were from very experienced hams, not newcomers. I hope some new people will try it and let me know, now that voltage feed is not necessary.



RAPID MOBILE CHARGER SEE THE WORKS CLOCK The DEB-TED Rapid Mobile Charger is a OUR EASIEST CLOCK TO constant voltage charger that will charge ASSEMBLE! your batteries off a 12 Volt source in 4-6 Chours. You may use the charger at all 6 Digits 12 or 24 Hour Format times, this includes transmit and receive Clock rests between two periods. It is equipped with a cigarette pieces of clear plesiglas A lighter plug on the input side and the **GREAT CONVERSATION PIECE!** appropriate charging plug on the output Kit is complete including top side. Models available now for the Kenwood TR2400, Yaesu 207R, Tempo quality PC board, all componets, pre-cut and drilled S1, S2, S5 and the Wilson Mark II and IV. Other models available also plexiglas and all hardware\$29.95 please call or write for info \$34.95. COMING SOON THE NEW AC VERSION VEHICLE INTRUSION ALARM SPECIAL An easy to assemble and install kit that offers options not normally found in other alarm systems. Hidden switch mounts under the dash. Kit has provisions for sensors and remote control switch. Programmable time delays for exit, entry and alarm periods. Basic hook-up utilizes dome light circuit activating when doors are opened. The alarm will drive a siren or pulse horn at a 1HZ rate. Not prone to false alarm do to reliable CMOS MODEL 5314 CLOCK KIT 12 or 24 hour format 6 large circuitry. No external switch required! Complete kit with easy to follow ."5 Digits. Kit is complete with all parts, pc board and instructions and diagrams \$12.95 custom designed cabinet. (Specify Whit or Black) Wired and Tested \$19.95 \$29.95 DEBCO ELECTRONICS Add 5% Shipping for U.S. Orders under \$20.00 add P.O. BOX 9169 & Canada \$1.00 handling All foreign orders add 10% Ohio residents add 4½% Tax CINCINNATI, OHIO 45209

- COD orders add \$1.25

· Master Charge and Visa

Welcome

CALL OR WRITE FOR CATALOG

× 330

Phone: (513) 731-7220

Single-Tone Paging for Wilson HTs - simple circuit should work with many rigs

Fred Studenberg W4BF 1305 E. Norfolk Tampa FL 33604

The small size of the new generation of twometer HTs permits them to be carried almost anywhere, giving instant communications capability either direct or through repeaters. In my specific aplication, my wife and I use Wilson MK IIs to keep in touch on an unused simplex frequency, and the channel can be monitored constantly for any calls to each other. Sometimes we are too far apart for reliable simplex communications, however, and must switch over to one of the local repeaters. Naturally, the wide-coverage repeaters are fairly busy, and monitoring all the repeater activity for a specific call is very distracting, especially in a business meeting or restaurant. What we each needed was a way to be alerted to an incoming call without constant attention to the HT.

this problem many years ago by the use of selective calling. Selective calling permits a receiver to monitor a frequency for calls and unsquelch only when specifically addressed. Thus, a user can go about his business without any conscious attention to the receiver and yet immediately be alerted to any incoming call. The most common form of selective calling used in commercial paging applications is some form of two-tone sequential encoding-decoding. This is accomplished by transmitting an rf carrier which is modulated by a series of two audio tones. Each paging recipient carries a receiver that responds to a particular sequence of different audio tones. The receiver remains muted until the proper tones are received, after which an audible alert tone is produced. In the case of a toneonly page, this alert tone is a signal for the paged person to perform some prearranged action, such as calling a telephone number or reporting to a specific location. For a tone and voice page, the alerting tone is followed by a voice message. The decoders in the receiver are immune to

false alarms by virtue of the sequencing requirement, decoder bandwidth, and slow response time. Typically, over 100 different codes are available on any given frequency.

Adding a suitable highperformance sequential tone decoder to an already crowded HT is not easy, unfortunately, and the problem is further complicated by the need for a compatible encoder when the signaling of another unit in the network is required.

Selective Calling

Commercial users solved



Fig. 1. Single-tone encoder-decoder for the Wilson MK II/ IV.

Single-Tone Paging

For many amateur applications, large numbers of different signaling codes on any given channel are not required and a simpler form of selective calling can be used. Encoding and decoding a single audio tone can be implemented with a minimum amount of circuitry and can provide very effective results if certain precautions are taken. As in the case of sequential tone decoding, the response time of the decoder must be slow so that voice or other momentary in-band signals do not trigger the squelch. Additionally, the frequency separation of the different tone frequencies must be compatible with low-cost decoders. Close frequency spacings allow more individual codes, but require tighter bandwidth control in the decoder and encoder, complicating the design and increasing the size and cost.

While researching this problem, I noticed that the eight frequencies used in touchtoneTM signaling (assuming 16 digits) use 10% frequency spacing for each of the 4 high-group and 4 low-group tones. Using this as a starting point, the group of tones shown in Table 1 was developed. Note that all the frequencies have a 10% offset from each adjacent frequency, except for the 1075-Hz tone. This was arbitrarily chosen to be midway from the 941-Hz and 1209-Hz touchtone frequencies. Eighteen different audio tones within the normal voice band permit up to 18 different paging networks to operate on any given channel. By using tones in the voice band, as opposed to subaudible tones, repeaters may be used as the paging transmitter since the originating tone can be transmitted by any station capable of accessing the repeater. Of course, the system will also work on simplex channels. There is no advantage in using the 8 touchtone frequencies in this plan, since in normal autopatch use any specific tone is usually transmitted for less than 1 second, and a 3-second response time on the singletone decoder allows it to effectively ignore the single tone associated with the dual-tone touchtone signal. Actually, there is some advantage to using touchtone frequencies in this tone plan since any of the 8 users of these frequencies can be paged by anyone equipped with a touchtone HT or by use of a touchtone phone on a reverse autopatch. Repeater groups might want

to assign these tones to key individuals in the organization such as members of the engineering committee or emergency coordinators.

Tone Coordination

In order for this tone plan to be successful, some form of tone coordination on any given channel is necessary. Since most repeaters are operated by well-organized groups, the 18 available tones can be assigned and their use administered in any manner that suits the group. The main consideration is to avoid duplication of tones so that users of the service are not bothered by unwanted pages.

Circuit Design

I have had excellent results using the single tone encoder-decoder shown in Fig. 1. The circuit uses an NE567 tone-decoder chip to detect one of the 18 different tones. The filter bandwidth is compatible with the 10% tone separation, and the operating frequency can be set to any of the 18 tones by the adjustment of R4. In addition, the circuit also generates the exact frequency which it decodes, permitting the encoder to alert any other receiver in the same network. The circuit is insensitive to voltage variations from 7.5 to 16 volts and varies less than 1% in frequency over the -10°-to-60°C temperature range.



Fig. 2. Full-size layout of PCB for the single-tone encoderdecoder.





urated output from Q2 in the decoder. Whenever a signal appears on frequency modulated by the correct tone, the output of U1 goes low. After about 3 seconds, as determined by C6 and R6, the collector of Q2 goes high and the MK II unsquelches. Once unsquelched, the activating tone is heard in the speaker indicating a page. The receiver squelches as soon as the rf input or tone is removed. Once the alert tone is heard, the squelch control is rotated to the normal carrier squelch position and the frequency monitored for information from the paging station, and twoway contact can be carried out if desired. If paging of

another station in the same tone network is desired, one first checks for a clear channel, identifies, and then transmits a 5-second tone by switching back to the Tone position while keying the MK II. The 5-second tone transmission allows about 2 seconds of the tone to be heard in the paged receiver.

Operation and Circuit Description

As installed in my Wilson MK II, the decoder is activated whenever the squelch control is switched to the Tone position. This tone feature was intended by Wilson to activate a subaudible tone squelch, but it works fine for this application. With the squelch control in this position, the normal carrier squelch is disabled, but the receiver remains squelched by the sat-

Construction

The entire encoderdecoder fits on one singlesided PCB. A full-size layout of the board is shown in Fig. 2 and the parts list is shown in Table 2. All the parts are available from advertisers in 73 or most Radio Shack stores. I've also made arrangements for

Tone Channel	Frequency	
1	515	
2	570	
• 3	630	
4	697	
5	770	Low group touchtone
6	852	Low-group touchtone
7	941)	
8	1075	
9	1209	
10	1336	High-group touchtone
11	1447	righ-group touchtone
12	1633 /	
13	1805	
14	1995	
15	2205	
16	2437	
17	2694	
18	2977	

Table 1.



ORBIT is the Official Journal for the Radio Amateur Satellite Corporation (AMSAT), P.O. Box 27, Washington, DC 20047. Please write for application.

For a **FREE SAMPLE COPY** please send \$1 to cover First Class Postage and handling to: Orbit, 221 Long Swamp Road, Wolcott, CT 06716.

switch contacts on the squelch control. Run a jumper from one of the switch contacts to the ground plane on the main PCB of the MK II or MK IV. Next, connect the wire from P2 to the other switch contact. Note that this wire must be routed from the backside of the PCB to the switch contact on the squelch control. The connections of each of the leads from the encoderdecoder to the MK II is shown in Fig. 1. In each case, the reference designator shown on the schematic beside each lead number refers to the connection point on the MK II. These points are best located by referring to the circuit board overlay on page 18 of the Operating and Service Manual for the MK II/MK IV.

The encoder-decoder is secured inside the radio by pressure from the top cover. Now, carefully reinstall the top and bottom covers and check for tone is transmitted.

How Does It Perform?

I can monitor a busy repeater all day and never once hear the squelch break, yet as soon as I am paged, the paging tone comes through loud and clear. I've had the opportunity to try the page feature through a number of different repeaters and it has never failed to work. When readable signals are present, the encoder-decoder works every time.

Incidentally, when switched On, the encoderdecoder adds about 6 mA of additional current drain. This is of no consequence since the average drain in the Tone position is much less than in normal squelch because battery life is directly proportional to the amount of audio coming from the speaker. With the decoder turned on, *nothing* is ever heard except the desired paging tone.

Use of Encoder-Decoder

the PCB alone, or a complete kit, to be made available from a source listed in the parts list. Mention the ST Encoder-Decoder when ordering.

All the parts are mounted as shown in Fig. 3. Note that the resistors are mounted vertically to save space. If your MK II or MK IV has the Hi-Lo power switch, it will be necessary to notch out the rear corner of the PCB to provide clearance. The solid copper area bordering the board name provides the proper guidelines for this operation. Six #26 stranded wires about 7" long are connected to the unit for testing and eventual connection to the MK II or MK IV PCB.

Testing

To avoid any extra trouble, I recommend testing the encoder-decoder externally and then connecting it to the MK II or MK IV. Referring again to Fig. 1, connect +12 volts to P1 and ground to P5. Connect a frequency counter to P4 and adjust R4 for the desired tone frequency. Then apply a 100-mV rms audio signal at the desired tone frequency to P3. Before the tone is applied, the base of Q2 should be at .7 volts. This should drop to 0 volts about 3 seconds after the tone is applied. Verify that the on/off switch works by grounding P2. The transmit output signal at P4 should disappear, and the base of Q2 will go to 0 volts. Once the board has been tested, insulate the entire bottom of the PCB with electrical or vinyl tape to prevent shorts when it is installed in the MK II or MK IV.

Installation

The first step is to remove the top and bottom covers from the MK II or MK IV to gain access to the proper operation. If you have a deviation meter, check for about 3-kHz tone deviation. This is more than adequate since the decoder will function with deviations from transmitters as low as 1.5 kHz. Have someone transmit a signal with the correct tone frequency and check for proper receiver operation. The receiver should unsquelch about 2.5 seconds after the

in Other Equipment

I haven't had the chance to investigate the use of the encoder-decoder in other equipment, but aside from physical constraints, the unit should work with most negative-ground solid state equipment. I will be glad to answer any specific questions on interfacing it with your rig if you include a copy of the schematic and an SASE.

	Parts Lis	st
R1, R5, R3	22k, 1/4 W	
R2	470, 1/4 W	
R4	25k Pot	Radio Shack 271-336
R6, R7	180k, 1/4 W	
C1, C7	10 µF, 16 V	Radio Shack 272-1411
C2, C3	0.01 ceramic	
C4	0.1 mylar TM	Radio Shack 272-1053
C5	1 µF, 35 V	Radio Shack 272-1406
C6	2.2 µF, 35 V	Radio Shack 272-1407
D1	1N4148	
D2	1N750A	
U1	NE567N	
01 02	2N2222	

A complete parts kit, including drilled and plated PCB, is available from Coggin Mfg., P.O. Box 44, Cedar Rapids IA 52404, \$15.95 (postpaid). The PCB alone is \$3.50 postpaid.

Have you ever wondered why the best ham bargains are advertised in 73?

You'll find a wider selection of ham bargains ... and lower prices in 73, because 73's readers buy far more than readers of other ham magazines.



Wayne Green

THE LEADING EDGE

That shouldn't come as a surprise to you... For twenty years we've been publishing more construction projects and articles than any other ham magazine, so it is natural for the active hams to read 73... and buy from the ads.

The readers of 73 catch the leading edge, through sideband in the early 60's, then solid state in the mid-60's, FM and repeaters in the early 70's...SSTV, ATV, RTTY and all other special modes have received more coverage in 73 than all other ham magazines combined.

ALL OF THIS IS MADE POSSIBLE BY YOU

All of this is made possible by you reading 73 and getting your friends and club members to subscribe to 73. I admit that we're not really pushing the radio relay of messages, since that is more geared to the 1920's than the 1980's and is more likely than other activities to cause troubles with foreign governments nervous about potential lost telephone revenues. We're looking toward the 1990's, with over one million hams in our country using state of the art communications techniques to keep in touch with hams worldwide.

NEXT YEAR WE'LL BE PUSHING...

In the next year or so, we'll be pushing for amateur experimentation and pioneering with new modes of communications, via computer, automatic identification, satellite, wideband techniques, synchronous detectors, time slicing. Never before was a point in time so exciting to contemplate, and with 73 you can keep up with the new ideas and changes.

We'll also be pushing for increased pressure on the FCC for better and more responsive rules, for a return to a national growth and for amateur radio development in as many of the emerging nations as possible.

YEAR 2000?

What will amateur radio be like in the year 2000? We can't really even imagine, except that we know it will be different from 1980...probably as different as amateur radio is today from what it was in 1960, when FM and repeaters were all but unknown, and AM was still going strong on our phone bands. A frequency synthesizer required over a hundred tubes and radioteletype circuits were larger than the printers. You can be sure that 73 will be in the vanguard of the developments to come...reporting on them and giving you the information so you can participate.

73 MAGAZIN	□ Bill me for one year of 73 at \$25.00 Name	New Subscription Renewal
	Address City	StateZip
The state of the second	Canadian \$27.00/1 year only, US funds Please allow 4-6 we 73 Magazine • PO Box 931	Foreign \$35.00/1 year only, US funds eeks for delivery. Farmingdale NY 11737 30DB6

WILSON SYSTEMS, INC. CHRISTMAS SPECIAL SALE SYSTEM 36



A trap loaded antenna that performs like a monobander! That's the characteristic of this six element three band beam. Through the use of wide spacing and interlacing of elements, the following is possible: three active elements on 20, three active elements on 15, and four active elements on 10 meters. No need to run separate coax feed lines for each band, as the bandswitching is automatically made via the High-Q Wilson traps. Designed to handle the maximum legal power, the traps are capped at each end to provide a weather-proof seal against rain and dust. The special High-Q traps are the strongest available in the industry today.

SPECIFICATIONS

Band MHz Maximum power input Gain (dbd)	14-21-28 Legal Limit
Impedance F/B Ratio	50 ohm 20 db or Better
Boom (O.D. x Length) No. of Elements.	. 2" x 24 '2½ "
Longest Element	28'2½"
Turning Radius	18'6"
Maximum Mast Diameter	
Surface Area	8.6 sq. ft.



Matching Method	. Beta
Wind Loading @ 80 mph 2	215 lbs.
Mfaximum Wind Survival 10	00 mph
Feed Method Balun (Su	pplied)
Assembled Weight (approx.)	53 lbs.
Shipping Weight (approx.)	62 lbs.

Compare the SY-36 & SY-33 with others...



Compare the size and strength of the boom to element clamps. See who offers the largest and heaviest duty. Which would you prefer?

Wilson Systems traps offer a larger diameter trap coil and a larger outside housing, giving excellent Q and power capabilities.

Christmas Special CALL FACTORY DIRECT 1-800-634-6898

WSI WILSON SYSTEMS, INC.

4286 S. Polaris Ave., Las Vegas, Nevada 89103

Prices and specifications subject to change without notice.

WILSON SYSTEMS INC.



Capable of handling the Legal Limit, the SYSTEM 33 is the finest compact tribander available to the amateur.

Designed and produced by one of the world's largest antenna manufacturers, the traditional quality of workmanship and materials excels with the SYSTEM 33.

The boom-to-element mount consists of two 1/8" thick formed aluminum plates that will provide more clamping and holding strength to prevent element misalignment. Superior clamping power is obtained with the use of a rugged 1/4" thick aluminum plate for boom to mast mounting.

The use of large diameter High-Q Traps in the SYSTEM 33 makes it a high performing tri-bander and at a very economical price.

A complete step-by-step illustrated instruction manual guides you to easy assembly and the lightweight antenna makes installation of the SYSTEM 33 quick and simple.

SPECIFICATIONS

Band MHz	14-21-28
Max. power input I	Legal limit
Gain (dbd)	8
VSWR at resonance.	1.2:1
Impedence	50 ohms
F/B ratio	up to 20

CW -----

Boom (O.D. x length)2" x 14'4"
No. elements 3
Longest element
Turning radius
Max. mast diameter 2" O.D.
Surface area5.7 sq. ft.
ACTUAL SWR CURVES

Wind load @ 80 mph	114 lbs
Assembled Wt	37 lbs
Shipping Wt	42 lbs
Direct 52 ohm feed	
the ball of the second s	CONTRACTOR OF A

Max wind survival ... 100 mph

REGULAR PRICE *65% SALE PRICE **\$59**5

4 BAND TRAP VERTICAL (10 - 40 METERS)

No bandswitching necessary with this vertical. An excellent low cost DX antenna with an electrical quarter wavelength on each band and low angle radiation. Advanced design provides low SWR and exceptionally flat response across the full width of each band.

Featured is the Wilson large diameter High-Q traps which will maintain resonant points with varying temperatures and humidity.

Easily assembled, the WV-1A is supplied with a base mount bracket to attach to vent pipe or to a mast driven in the ground.



Compare the size and strength of the boom to element clamps. See who offers the largest and heaviest duty. Which would you prefer? Wilson Systems traps offer a larger diameter trap coil and a larger outside housing, giving excellent Q and power capabilities.

REGULAR PRICE

*65*5

SALE PRICE

-095

ADD 40 METERS TO YOUR TRI-BAND WITH THE 33-6 MK

- IN STOCK -

Now you can have the capabilities of 40-meter operation on the SYSTEM 36 and SYSTEM 33. Using the same type high quality traps, the 40-meter addition will offer 150 KHZ of bandwidth. The 33-6 MK will fit your present SY36, SY33, or SY3 and use the same single feed line.

The 33-6 MK adds approximately 15' to the driven element of your tri-bander, increasing the tuning radius by 5 to 6 feet. This addition will offer a rotatable dipole at the same height of your beam.



4286 S. Polaris Ave., Las Vegas, Nevada 89103 Prices and specifications subject to change without notice. Prices Effective 11-1-80 thru 12-31-80 For Christmas Special Sale – Call FACTORY DIRECT 1-800-634-6898

NOTE: Radials are required for peak operation or above ground mounting. (See GR-1 below)

SPECIFICATIONS

- 19' total height
- Self supporting no guys required
- Weight 14 lbs.
- Input impedance: 50 Ω
- Powerhandling capability: Legal Limit
- Two High-Q traps with large diameter coils
- Low angle radiation
- Omnidirectional performance
- Taper swaged aluminum tubing
- Automatic bandswitching
- Mast bracket furnished
- SWR: 1.1:1 or less on all bands



The GR-1 is the complete ground radial kit for the WV 1A. It consists of 150' of 7/14 aluminum wire, heavy duty egg insulators and instructions. The GR-1 will increase the efficiency of the WV-1 by providing the correct counterpoise.



		and the second second	ATTICSMATTER
Tower	WIND L Height	OADING Sq. Ft.	Nixian
Tower	WIND L Height 69	OADING Sq. Ft.	Square
Tower ST-77B	WIND L Height 69 77	OADING Sq. Ft. 16 10	Square
Tower ST-77B	WIND L Height 69 77 53	OADING Sq. Ft. 16 10 18	Square Footage
Tower ST-77B MT-61B	WIND L Height 69 77 53 61	OADING Sq. Ft. 16 10 18 12	Square Footage Based on
Tower ST-77B MT-61B	WIND L Height 69 77 53 61 37	OADING Sq. Ft. 16 10 18 12 18	Square Footage Based on 50 MPH

SI

use on the TT-45, MT-61 and ST-77 towers.

EW-45 (TT-45) EW-61 (MT-61) EW-77 (ST-77)

-	INT. OID	10 10	
/	FB-61B	3' x 3'	5½ ′
	RB-61B	3' x 3'	5½′
5	ST-778	See Below	
	RB-77B	3½'x3½'	6'

Remote Switch . . . *2495

Wilson Systems uses a high strength carbon steel tube manufactured especially for Wilson Systems. It is 25% stronger than conventional pipe or tubing. The tubing size used is: 2" & 3½ "-.095; 4½ " & 6"-.125; 8" - 134. All tubing is hot dip galvanized. Top section is 2" O.D. for proper rotor and antenna mounting.

The TT-45B and MT-61B come complete with house bracket and hinged base plate for against-house mounting. For totally freestanding installation, use either of the tilt-over bases shown below.

The ST-77B cannot be mounted against the house and must be used with the rotating tilt-over base RB-77B shown below.

TILT-OVER BASES FOR TOWERS

FIXED BASE

The FB Series was designed to provide an economical method of moving the tower away from the house. It will support the tower in a completely free-standing vertical position, while also having the capabilities of tilting the tower over to provide an easy access to the antenna. The rotor mounts at the top of the tower in the conventional manner, and will not rotate the complete tower.

FB-45B...112 lbs...*16995 FB-61B...169 lbs...*24495

CHRISTMAS SPECIAL SALE Call Factory Direct 1-800-634-6898



The RB Series was designed for the Amateur who wants the added convenience of being able to work on the rotor from the ground position. This series of bases will give that ease plus rotate the complete tower and antenna system by the use of a heavy duty thrust bearing at the base of the tower mounting position, while still being able to tilt the tower over when desiring to make changes on the antenna system.

RB-45B...144 lbs...*234⁹⁵ RB-61B...229 lbs...*309⁹⁵ RB-77B...300 lbs...*463⁹⁵ Order the CHRISTMAS SPECIAL!

Prices Effective 11-1-80 thru 12-31-80





Tilting the tower over is a one-man task with the Wilson bases. (Shown above is the RB-61B. Rotor is not included.)



WILSON SYSTEMS, INC. PRESENTS CHRISTMAS SPECIAL THE SYSTEM 40 TRIBANDER 3 MONOBAND ANTENNAS IN ONE - EACH WITH FULL MONOBAND PERFORMANCE



- FOR THE SERIOUS DXer WHO WANTS MONOBANDERS ON 10-15-20
- FOUR FULL SIZE 20 MTR ELEMENTS WITH 10 dbd GAIN AND 25 db F/B
- FOUR WIDE SPACED 15 MTR ELEMENTS WITH 10 dbd GAIN AND 20 db F/B
- FIVE WIDE SPACED 10 MTR ELEMENTS WITH 11.5 dbd GAIN AND 20 db F/B
- ONLY ONE FEED LINE REQUIRED
- HEAVY DUTY BALUN INCLUDED
- DESIGNED WITH NO INTERACTIONS BETWEEN ELEMENTS.
- ALL DRIVEN AND DIRECTOR ELEMENTS ARE INSULATED FROM BOOM



SAME QUALITY HARDWARE AS USED IN ALL WILSON ANTENNAS -SPECIFICATIONS-

Max. Pwr. Input	Legal Lmi
VSWR @ Res	1.2:1
Impedance	50 ohr
Feed Method	Balun Supplied
Matching Method	Modified Beta
F/B Ratio	See Above
Gain	See Above

Longest Element	36'
Turning Radius	22'6"
Boom	26'
Surface Area	. 12.1 sq. ft.
Wind Loading @ 80 mph	309 lbs.
Assem. Weight	75 lbs.
Shipping Weight	99 lbs.

NETERS 22.2 21.0 21.1 113 31.4 31.1 2.0 METERS 15 16.1 10.0 14.2 14.3 14.4 14.5

WILSON SYSTEMS, INC. - 4286 S. Polaris Las Vegas, NV 89103 - (702) 739-7401

FACTORY DIRECT ORDER BLANK CHRISTMAS SPECIAL SALE

Model Description Price Description Price Shipping Oty. Model City. Shipping Remote Switch for EW SY40 10 Ele. Tribander for 10, 15, 20 Mtrs. UPS **RM-1** UPS 337.95 24.95 UPS Freestanding 45' Tubular Tower SY36 6 Ele. Tribander for 10, 15, 20 Mtrs. 199.95 TT-45B TRUCK 349.95 SY33 3 Ele. Tribander for 10, 15, 20 Mtrs. UPS **RB-45B** Rotating Base for TT-45B w/tilt over feature TRUCK 149.95 234.95 UPS 40 Mtr. Mod Kit for SY33 & SY36 33-6 MK 59.95 FB-45B Fixed Base for TT-45B w/tilt over feature TRUCK 169.95 UPS WV-1A Trap Vertical for 10, 15, 20, 40 Mtrs. MT-61B Freestanding 61 ' Tubular Tower 59.95 TRUCK 579.95 GR-1 Ground Radials for WV-1A UPS 12.95 **RB-61B** Rotating Base for MT-61B w/tilt over feature TRUCK 309.95 4 Elements on 20 Mtrs. UPS 174.95 M-420A 244.95 FB-61B Fixed Base for MT-61B w/tilt over feature TRUCK M-515A 5 Elements on 15 Mtrs. UPS 139.95 ST-77B 994.95 Freestanding 77' Tubular Tower TRUCK M-520A 5 Elements on 20 Mtrs. 224.95 TRUCK **RB-77B** Rotating Base for ST-77B w/tilt over feature TRUCK 463.95 M410A 4 Elements on 10 Mtrs. UPS 74.95 **GK-46** Guying Kit for GT-46 UPS-TRK 74.95 ACCESSORIES Guying Kit for TT-45B UPS-TRK 69.95 GK-45B T^zX Tail Twister Rotor UPS 274.95 **GK-61B** Guying Kit for MT-61B UPS-TRK 79.95 UPS 109.95 HD-73 Alliance Heavy Duty Rotor GK-77B Guying Kit for ST-77B UPS-TRK 99.95 RC-8C 8/C Rotor Cable UPS 18¢/ft. WTB-1 Thrust Bearing for Top of Rotating Towers UPS-TRK 59.95 RG-8U Foam Coaxial Cable - Ultra Flex RG-8U 28¢/ft. UPS center conductor, 11 guage UPS Wilson Electric Winch for TT-45B 249.95 EW-45

249.95

249.95

UPS

UPS

NOTE:

Wilson Electric Winch for MT-61

Wilson Electric Winch for ST-77

EW-61

EW-77

On Coaxial and Rotor Cable, minimum order is 100' and 50' multiples. Prices and specifications subject to change without notice. Ninety (90) Day Limited Warranty - Shipping Not Included in Above

Christmas Prices Effective Nov. 1-Dec. 31, 1980

Nevada Residents add Sales Tax

Toll-Free Order Number

1-800-634-6898

Ship C.O.D. Check enclosed Charge to VISA MasterCharge

Card No		Expires	Expires		
Bank No.	Signature				
Name	and a property in the	Phone	-		
Street	Renner Maria	the states	and and		
City	State	Zip			
Prices and s	pecifications subject to change v	vithout notice.			

William L. Thomas WB9KPT 3485 Bayberry Drive Northbrook IL 60062

Teletext and Viewdata: Are You Ready for the Information Boom?

- coming soon to a living room near you: video data services

S pecially equipped TV receivers are now available to provide us with current weather, sports, news headlines, tonight's television shows, local events of interest, and many other interesting bits and pieces of information. The magic word in this scenario is *information*. Almost anything of general interest, can be formatted and sent to your home by the systems to be described in this article.

In England, a set-top adapter currently available for this service is priced at \$250. The cost of the LSI integrated circuits that will form the heart of these adapters is less than \$50. I feel that there is the possibility of adapting this hardware, which will be produced in large volume for consumers, for use on the ham bands. tems broadcasting pages of information along with the normal TV signal. This information is digitally encoded and sent during the vertical-retrace interval when the scan of your TV receiver is off screen. What the viewer sees on the screen of his teletext TV is a page of characters, 40 in a row, 20 to 24 rows, 800 to 960 characters per page. These characters can be presented in eight colors, including colored backgrounds. Included in the character set are all the letters of the alphabet (both uppercase and lowercase), numbers, punctuation marks, special symbols, and graphics. The graphics can be as simple as 64 special graphic symbols, called mosaic graphics, or higher density if one is willing to pay the price. Each page is identified by a page number and typically will be displayed on the screen in less than a minute after the desired number is entered via the keypad. Several hundred pages can be transmitted in less than a minute in a serial fashion, one page after an-

other. The teletext adapter grabs the appropriate page as it comes by and immediately displays the selected page on the screen. Index pages are provided to help the consumer determine pages of interest.

Teletext is a generic term for television-based sys-



Photo A. Typical teletext hardware. Left to right: Mullard module, remote control, and Texas Instruments module.

Where does all this information come from and why does the broadcaster want to transmit it to your home? One way to answer this question is to consider teletext as a new publishing medium. As advertising supports most mass-market publishing efforts, so would it play in this one. As an interesting example, the news headlines could be brought to you by your local paper in an effort to sell you today's edition containing more details on the stories. It is expected that most pages broadcast by commercial TV stations would include such advertising.

On the public TV stations, information would be financed by the same sources that contribute to their normal program funds. Obviously, most major corporations and many government agencies have

much material that would be suitable for this system of distributing information. Many data bases already exist and are being made available to hobbyists with home computers via dialup telephone networks. Much of this information is directly presentable on teletext systems. There seems to be no lack of available material, and there are many organizations willing to finance its presentation.

Now that we have the information, how does it get from the source to your home? To begin with, the desired page is composed within the display format specification previously highlighted. If this composing is not done directly in the broadcaster's studio, it probably will be sent to him either over the telephone line or in the form of a digital cassette or floppy disk (i.e., in computer-compati-

ble form). At the station, this data is loaded into a piece of apparatus which encodes it into a digital serial data signal. This signal is appropriately filtered (bandlimited) and inserted in unused scan lines during the vertical retrace portion of the current video signal being broadcast. A decoding apparatus connected to your TV will accept this special signal and when the requested page is being transmitted, will grab it and load it into a television display memory. The pages are transmitted row by row, one page after another, and then the whole sequence is repeated. Hence, if the page you requested had just been sent, you will have to wait while all the other pages are sent-until the sequence cycles back to your page.

Since the television broadcast system deals with analog and not digital



Photo B. Prestel page. Both teletext and viewdata pages will look like this.

signals, special precautions have to be taken with both the broadcast and reception equipment. The digital signal leaving the studio encounters many places where distortion can occur. Some of these are in the studio-totransmitter link, the transmitter, in reflections caused by large objects, in your TV antenna and lead-in, and in the television receiver and decoder input circuitry. All these effects are being considered by the organizations trying to propose standards in this country.



Fig. 1. Transmission format for British teletext.



Fig. 2. Insertion of teletext signal in 625-line video signal.

Teletext: Current Systems Being Proposed for North American Use

At the present time, there is no standard for the broadcast of teletext in North America. In Europe, there are systems in place and regularly broadcasting, with the largest number of receivers in England. There currently are three major contenders for teletext standards in this part of the world: 1) British teletext, 2) French Antiope, and 3) Canadian Telidon proposals. Also, a system called Captions for the Deaf (CFD) should be mentioned since it shares some similar characteristics.

transmission format. This is likely to lead to the cheapest decoder design, which is important in the consumer product marketplace. There are two names by which these systems are identified. The British Broadcasting Corporation (BBC) has called its system Ceefax. The Independent Broadcasting Authority (IBA) calls its version Oracle.

The French system, Antiope, is based on packets of data which are efficient representations of only the displayed characters on any page. On pages sparsely covered, the Antiope system requires less time to transmit than British teletext. On full pages, this is not the case. Telidon, proposes a generalized technique for transmitting higher resolution graphics displays. As mentioned earlier, the basic graphic character set is 64 mosaic symbols. Originally, this was proposed as a way of improving the appearance of the primarily textoriented displays. However, as more experience has been gained, the graphics feature has been found to be a very useful and definitely desirable aspect of teletext.

The approach suggested

olution graphics is likely to influence system development in this country also.

Captions for the Deaf is a system intended primarily for sending captions for hearing-impaired viewers. As such, much lower data rates are adequate (about 10 times slower). As one provision of the system, called info-text, 15 lines of 32 characters can be displayed. Currently, the FCC has authorized the use of TV scan-line 21 for this purpose. All the teletext systems have provision for captioning services, including foreign language subtitles.

British Teletext: A Detailed Description

To make these systems affordable for the consumer, several LSI integrated circuits will be required. At the present, these chips are available only for the British teletext system. Several manufacturers including Mullard, Texas Instruments, and General Instruments offer chip sets for this purpose. To understand how these circuits work, a description of the page encoding scheme must be studied.

The British teletext system is probably the simplest because it has a fixed-

The Canadian system,



Photo C. Interested in a holiday? The cost of this page was .5 pence (about one cent).

by the Canadians is to transmit Picture Description Instructions (PDI). These instructions describe images in terms of basic geometrical shapes. Included are line, arc, polygon, point, and area. To describe a line, a starting point and a final displacement are sent instead of characters corresponding to each section of the line. Decoders could be built with various degrees of resolution in the display, with higher resolution being more costly. Most likely, these would have to be microprocessor based, since software algorithms would be needed to "draw" the shapes into the display memory. The minimum decoder, which would perform similarly to the 64-character mosaic approach, likely would be more expensive than a system which is tailored only for simple graphics. However, the appeal of high-res-

The standard character set is shown in Table 1. If you are familiar with ASCII coded symbols, you will notice a great similarity between the two character sets. There are several characteristics which should be noticed about this set. The 64-character, mosaic-graphic set is shown in columns 2a, 3a, 6a, and 7a. The digital code which represents these characters is the same as that for the symbols in columns 2, 3, 6, and 7.

How can this be? The answer is contained in the first two columns (0 and 1) of control characters. Each row of displayed text is assumed to be transmitted under an initial set of conditions shown in Table 1. The "alpha" control characters tell the decoder to use 2, 3, 6, and 7, or, for "graphics" characters, to use 2a, 3a, 6a, and 7a. Therefore, as an example, it is impossible to mix lowercase letters and mosaic graphics without sending a control character to switch the character set. All control characters are displayed as spaces.

In the British system, 24 rows of text are transmitted per page. The first row is special and is given the name page header. It includes 32 characters to be displayed and special page descriptors which are not displayed. All other rows have 40 characters. See Fig. 1, which shows the makeup of these rows. Each row starts with a clock run-in and framing code for hardware synchronization. Then the magazine (0-7) and row address (0-23) are sent. (The three-digit page number can be from 0 to 799 with the most significant digit being referred to as the magazine number.) Finally, 40 characters are sent. The page-header row has the page number, time code, and special control bits followed by 32 characters. The magazine, row address, page, time code, and control bits all are encoded with special protection bits forming a Hamming code. This code is made up of message and protection bits shown in Table 2. The other characters use a single bit, b8, to form parity. Parity refers to the number of bits which are equal to 1; in this case, an odd number is sent for protection purposes. From Fig. 1, you will find that there are 360 bits (or 45 bytes) per row. All these bits (one row) are transmitted on one horizontal scan line during the vertical blanking interval. As shown in Fig. 2, lines 17, 18, 330, and 331 are used by the British in their 625-line television system. Since only two lines are transmitted per field, it

-						and the second se	A REAL PROPERTY AND INCOME.	-			_						
07 b6 b	5-				***	000	°0 ₁	0	¹ 0	0,	1	100	¹ 0 ₁	1,	0	1,	4
Bits	1	03	b2	b1	Row	0	1	2	20	3	3a	4	5	6	60	7	7a
-	0	0	0	0	0	NUL®	DLE®			0		0	P			D	
	0	0	0	1	1	Alpha ⁿ Red	Graphics Red			1		A	Q	0	2	a	
	0	0	1	0	2	Alpha ⁿ Green	Graphics Green	•		2		B	R	Ь		r	
	0	0	1	1	3	Alpha ⁿ Yellow	Graphics Yellow	£		3		C	S	C	F	s	
	0	1	0	0	4	Alpha ⁿ Blue	Graphics Blue	\$		4		D	T	d		t	
	0	1	0	1	5	Alpha ⁿ Magenta	Graphics Magenta	%	J	5		E	U	e		U	
	0	1	1	0	6	Alpha ⁿ Cyan	Graphics Cyan	8		6		F	\bigtriangledown	f		V	
	0	1	1	1	7	Alpha ⁿ White	Graphics White			7		G	W	g		w	ŀ
	1	0	0	0	8	Flash	Conceal Display		C	8		Η	\mathbf{X}	h		×	•
	1	0	0	1	9	Steady	Contiguous Graphics			9		Ι	Y	i		V	•
	1	0	1	0	10	End Box	Separated Graphics	*				J	Z			Z	
	1	0	1	1	11	Start Box	ESC®	+		:		K	₽	k		14	•
	1	1	0	0	12	Normal [®] Height	Black ² Background						12				Γ



Table 1. Teletext character codes. Notice the similarity to ASCII.

takes 12 fields (6 frames) to send a page of text. To transmit 360 bits, a rate of 6.9 Mbits/sec is used. This raises compatibility questions for use in this country where we have different TV standards.

The decoder chip set functions in real time as the data is received. On each line, bit synchronization is achieved using the clock run-in, and then word synchronization is determined with the framing code. Next, the magazine and row address are grabbed and Hamming decoded. In the page header row, additional Hamming encoded data are processed. For the character bytes, the parity is checked and, if correct, the character bytes are loaded into display memory. During the display time, these characters are read out of memory and, using a color-character generator, are shown on the screen. The user specifies the desired page by punching data into the chip set via a small hand-held keyboard.

Viewdata: Telephone Systems

A similar service is possible using telephone line, two-way communications. Instead of serially broadcasting a fixed set of pages, the user asks for specific



Photo D. Visiting New York? Check out some options for your stay.

pages from a large data base. In England, there are currently over 150,000 pages on their Prestel system. (See "The Ultimate Consumer Computer," by Derfler, Kilobaud Microcomputing, October, 1979.) The main difference from teletext is that only the pages you request are sent. This gives apparent immediate access to a very large amount of information. user having a unique access code, there are also advantages such as the possibility of having a complete shopfrom-home service. With so many pages of information, a user normally would refer to a guide to locate pages of interest, or it would be possible to step through menu pages, narrowing the topic as you go. This is described as a tree searching method, where you branch into more specific areas. The hardware for teletext and viewdata is similar. In fact, viewdata adapters are based on teletext systems with the addition of a microprocessor and telephone modem. Basically, this doubles the cost of the integrated circuits (over a teletext only system).

at 1200 baud (1300 Hz for binary 1 and 2100 Hz for binary 0). The user responds at 75 baud (390 Hz for 1 and 450 Hz for 0) when the keypad is punched.

The character set is the same as that previously described in Table 1, with some additional codes. Some of these codes are cursor controls, page deliminators, and other computer symbols. Since two-way interaction occurs in this system, the keypad requires a few more buttons than the one solely for teletext. Two of these are * and #. These are used as page deliminators. As an example, if page 123 is desired, you would enter *123# directly instead of continuing with branching from page to page.

One nice feature of this system is the automatic dialing of the computer's telephone number. All you need to do is push the viewdata button and the system in the TV does the rest; when the access procedure is completed, the system is ready for your first page request. Many variations on this theme are possible, including a completely automated system that would access data in the middle of the night when phone rates are the lowest and store the information on inexpensive audio cassettes.

using the ham bands. A system similar to viewdata could be envisioned, since it uses audio bandwidth channels which we already possess. This might be implemented similarly to slow scan, where pages of information (and graphics) are sent instead of pictures. Hopefully, we all can learn quite a bit and have a good time doing it.

Since teletext and viewdata are not yet widely available in this country, getting information normally requires correspondence to Europe. However, there are two publications which I can suggest for those who are anxious to learn more.

"Consumer Text Display Systems (Teletext and Viewdata)," IEEE Transactions on Consumer Electronics, July, 1979, volume CE-25, number 3, is available for \$15 from IEEE Service Center, 445 Hoes Lane, Piscataway NJ 08854, or from your local library. It is composed of two hundred pages of general articles on the various systems. For the most part, these are not written at a high technical level. Multitext Technical Information is available for \$5, check or money order, from Signetics Corp., Publication Services-Bin 027 MTB, 811 Arques Ave., PO Box 409, Sunnyvale CA 94086. It is a fifty-page brochure describing the Mullard (Signetics) teletext and viewdata chip set and system operation. There are 35 color photographs including many sample text pages. (Only a limited quantity of these brochures is available.) I would like to thank Neal Williams for arranging the availability of the Multitext brochure and Merv Cox for his photographic work. Several figures were obtained from the Broadcast Teletext Specification, jointly published by the BBC, IBA, and BREMA.

The catch in using this system is a financial one. Since you are in direct communications with a computer, it is very easy to charge you for this information on a page-by-page basis. However, with each



Table 2. Hamming protection of four-bit binary values.

Prestel: The British Viewdata System

In England, the British Post Office controls all communications for the country. This has helped considerably in allowing them to develop both teletext and viewdata systems with similar standards. From the user's point of view, the text display looks identical for both systems.

The actual communications is accomplished using FSK modulation. The computer sends the characters

Amateur Radio: Possible Applications

Now that I have described these consumer systems, you may be asking yourself how to apply the technology from these systems towards our hobby. In all honesty, I don't have the answer. Even as this is being written, new circuits are being developed which might be applicable for use in an amateur radio system.

In the tradition of amateur radio experimentation, I expect that some pioneers will devise a way to send these pages of information







Honny Redio



IN ADDITION TO THE PRODUCTS LISTED ABOVE, WE ARE ALSO FAC-TORY AUTHORIZED DEALERS OR DISTRIBUTORS FOR **B & W, UNI-VERSAL TOWERS, BERK-TEK CABLES, BENCHER PADDLES,** THE NEW **CES DIALER** AND MANY OTHER ACCESSORIES. OUR SERVICE SHOP, STAFFED BY FIRST PHONE, EXTRA CLASS TECHNICIANS, OFFERS EXPERT SERVICE ON ALL MAKES AND MODELS AND FACTORY AU-THORIZED SERVICE ON SWAN, YAESU AND KENWOOD PRODUCTS.

SERVICE DEPARTMENT CALL 803-366-7158

ORDER TOLL FREE! 800-845-6183

Double-Duty CW Keyboard - helps you on receive as well as transmit

Robert C. Spindel K1GN Box 169 North Falmouth MA 02556

A orse code keyboards are a popular station accessory, as witnessed by the numerous designs available.¹ The beautiful, rhythmic sound of near-perfect CW is easy to achieve with these units. Merely striking the keys on a typewritertype keyboard produces perfectly formed Morse characters.

But sending flawless CW is only half the battle. You have to be able to copy it as well. And with the speed attainable with keyboard units, that means copying at higher rates.

This keyboard has a unique feature to help you receive code accurately so that you can keep up with your ability to send at high speeds. With the flip of a switch, the Morse keyboard becomes, voilà, a tireless instructor sending a continuous stream of random letters or five-letter code groups at any speed.

The Instructor-Keyboard is also the perfect device for giving new Novices code practice. Someone who does not know Morse can type to the neophyte, or he can use the Instruct mode to copy random letters. It allows practice at times when W1AW cannot be heard or when a receiver is not available. Since it sends letters randomly, there is no danger of the memorizing of practice material which often limits the usefulness of tapes and records. Needless to say, its utility is not restricted to beginners. A little time spent copying high-speed, random code groups should have you copying W1NJM's transmissions with ease.² Switch to the Keyer mode, and you can send at that speed, too. Although available keyboard designs differ in detail of execution-some employ scanned keyboards while others use diode matrices, some have character buffers and some have message memories-they all operate in the same fundamental way. A single switch closure is used to produce a logic signal. A separate switch is provided for each desired character (letter, number, punctua-



Photo A. The Instructor-Keyboard is built in a homemade case. The front panel is made of galvanized sheet metal painted with spray enamel. The keyboard keys have been relabeled with transfer letters. To the left are the Instruct/Keyer and Space switches; the speed control is in the upper center; to the right are the Tune, Sidetone on-off, and Power on-off switches.

tion, or special symbol such as AA, AS, AR, BT, etc.), and the switches are arranged in a standard typewriter format. The operator strikes a series of keys to generate a sequence of characters. The resulting logic signal is used to key a transmitter, FSK converter, sidetone oscillator, or other device. This keyboard uses a diode matrix to encode switch closures into logic signals, and in the Instruct mode it uses hard-wired CMOS digital logic elements to simulate switch closures in a random manner. Thus, the logic replaces the action of the keyboard. In fact, as will be pointed out below, it is quite simple to build the Instructor without the Keyboard, thereby yielding a simple code-practice machine.

Circuit Features

The Instructor-Keyboard has been designed without unnecessary frills. It is capable of sending all letters, digits from 0 to 9, common punctuation, and special symbols AR, SK, BT, AA, and AS. It has two-key rollover, which means that a second key can be depressed while the first is held down and, provided the first is released, two successive characters will be sent with perfect inter-character spacing. Holding a single key down will cause that character to be sent repetitively, again with perfect spacing.



Photo B. Perfboard and wire-wrap sockets are used for the two electronic boards. The diode matrix and keyer are on the lower board. The Instructor electronics are on the smaller board on the left, partially obscuring the diode matrix.

\$15 to \$20. Keyboards are available from a number of surplus dealers at reasonable cost. The digital logic for both Keyboard and Instructor is all CMOS, selected for its tolerance to power-supply variations and its high immunity to electronic noise. I have not observed any rf interference with the operation of the Keyboard even in the presence of my 1-kW linear amplifier. There are three main subsections in the Instructor-Keyboard. The first is a diode matrix for encoding a switch closure into a unique digital signal representative of the desired character. This is fed to the second subsection, the digital keyer logic, that converts it into appropriate dots and dashes. The third subsection is the Instructor itself. It automatically generates digital signals identical to those created by switch closures so that letters are sent without striking keys. They are also sent without the need for a diode matrix so that an In-

structor can be built without the keyboard-matrix combination. By the same token, the unit can be constructed without the Instructor electronics and used as a conventional keyboard. In the Instruct mode, three spacing options are provided. The Instructor-Keyboard can be set to issue a continuous stream of random letters with the proper three-element intercharacter spacing. Alternatively, random five-letter code groups can be sent with either a long or short pause between groups. Letter spacing within groups is always precisely correct for the speed being sent. As described below, the Instructor sends only letters. It was felt that sending letters only provided a costeffective realization of an automatic Morse code generator easily adaptable to many existing keyboards. The unit can be altered to allow automatic generation of numbers and punctuation in the Instruct mode at the expense of an increased

parts count.

The Diode Matrix

All characters are encoded into an eight-bit digital word by the diode matrix. The coding scheme is the same as that used by Bryant W4UX and Horowitz W1HFA. A diode is used for each dash, no diode for a dot, and a final diode to signify the end of the character. Diodes are used for dashes because there are fewer dashes than dots in Morse code, thus reducing the number of diodes needed. The first few letters and numbers are wired as shown in Fig. 1. The remaining pattern of diodes should be obvious if it is kept in mind that a diode is wired in place for a dash and also to terminate the character. The bits in the code word are labeled B1 through B8. Note that with no keys depressed, all bit lines are held high (+12 volts) by a single 10k pull-up resistor on each bit line. Depressing a key (closing a switch) causes only those bit lines connected to the switch by di-

The keyboard is completely debounced so that only a single character is sent when a key is struck even though the switches themselves may bounce open and closed for several milliseconds after being struck. Furthermore, the Instructor-Keyboard is constructed from readily-available and inexpensive components. A perusal of the back pages of 73 indicates that the CMOS logic elements should cost less than



Fig. 1. Wiring diagram for diode matrix. All diodes are general-purpose switching diodes such as 1N914s. If constructed as an Instructor only, diodes are not needed, but the 10k pull-up resistors should be connected to all bit lines.

odes to be forced to ground (0 volts). Thus, the pattern of bits appearing on B1 through B8 for the letter A will be 10011111 where we have used a 1 to denote a high voltage level and a 0 to denote a low, or zero, level. Depressing the B key will create the pattern 01110111, and a question mark will be 11001101. These are the unique digital codes that the keyer portion of the unit translates into appropriate dots and dashes. Incidentally, these are the codes that the Instructor portion of the unit also must simulate.

Detailed operation of the keyer logic can be deduced from one of the excellent manufacturer's data books on CMOS logic. The following is a brief explanation of the general sequence of events that occurs after a are filled with whatever signal is present on the serial-input (SI) line. Since this pin is grounded, as the bits are shifted through the register they are replaced by zeros at the bottom. The bit present on IC9-1 turns the dash flip-flop on and off depending on whether it is high or low, respectively. Meanwhile, IC6 constantly monitors the status of the output lines of the register in order to detect an end-ofcharacter condition. When an end-of-character occurs, the lines monitored by IC6 are all low, its output goes high, thus terminating keyboard output through IC1 and IC3b. At this time, IC9-1 will be high since a diode has been inserted at the end of each character. One more clock cycle makes this low and IC3a turns the shift register back into its parallel mode allowing it to accept a new code word, the next character. This extra clock cycle ensures that there will be a three-eleoscillator also is constructed with two inverters, and gives an approximate 700-Hz tone. The output of the sidetone oscillator is gated on and off by the keyer through IC3c and is then applied to Q1. Q2 drives a small relay to key a transmitter. S1 closes the relay for tune-up purposes. If desired, a solid-state keying circuit can be substituted for the relay; a reed relay, however, is fast enough to follow 60-wpm keying and allows the keyboard to be used with virtually any transmitter. To prevent relay sticking with those transmitter keying circuits that draw more than a few milliamps, it often is a good idea to place a 20- to 50-Ohm resistor in series with the output line.

The Instructor

A careful examination of the digital code words produced by the diode matrix for the 26 letters of the alphabet indicates that they use only bits B1 through B5. These five bits allow 32 combinations of zeros and ones. Now, a five-bit binary counter will count sequentially from 0 to 31 and in the course of doing so will present at its output every one of the 32 possible bit combinations. If we devise circuitry to select only the 26 output states corresponding to the letter codes, and then apply the output of the counter to the B1 through B5 input lines of the keyer, the counter will effectively act as a substitute for the keyboard and diode matrix. If the counter is clocked slowly, the keyer will generate a sequence of letters corresponding to the bit codes at the output of the counter and will repeat this sequence ad infinitum.

The Keyer

The heart of the keyer consists of an 8-bit parallelto-serial (P/S) shift register, IC9, dot-dash generator flipflops IC7a and IC7b, and an end-of-character recognizer, IC6. Additional logic is used to debounce the keyboard and to insert a proper space between characters. This space is exactly three code elements long (a dot is two elements long) as required in Morse code. A dash is four elements long (three on and one off). Interword spacing is seven elements in length.

key is closed.

The bit pattern, or code produced by the diode matrix, is inverted by IC5 and part of IC1 so that the letter A becomes, for example, 01100000. The shift register accepts this code on its 8 input lines and immediately transfers it to its output lines if the P/S line is high and if the A Enable (AE) line is high. When AE is low, the input lines are disabled and information present on them is ignored. This feature is used to debounce the keyboard. Now, when the P/S line is low, input data is ignored similarly, but the register is converted to its serial mode. Data stored in the register then can be clocked out by pulses applied to the CLK input.

Each positive transition of the clock signal transfers the bit pattern one step through the register. Bits at the top (IC9-1) "fall out," while the empty spaces at the bottom of the register ment space between successive characters.

Note that in its idle state the keyer logic has the code word 00000000 on the output lines of IC9. The inputs to IC6 are low; its output is therefore high. Upon striking a key, at least one of the bits at the output of IC9 goes high so that the output of IC6 goes immediately low. This triggers the oneshot, IC4, and it responds with a 2-ms pulse which is applied to the AE input of IC9. It has the effect of disabling the input lines of the register for sufficient time to allow all contact bounce to subside.

The keyer clock is a simple oscillator made of two CMOS inverters. With the parts values shown, the speed is adjustable from about 5 to 50 wpm. Variation of speed in either direction can be achieved by changing the value of the 10k resistor or the 1-uF capacitor. The sidetone

In order to generate letters in a random sequence with no repetitions, binary counter IC9 is clocked at a frequency that is high compared to keying speeds.



Fig. 2. The keyer subsection uses CMOS integrated circuits. All unused CMOS gate inputs are tied to 12 volts as recommended by the manufacturer. Q1 and Q2 are general-purpose transistors, and many substitutions will work.

NOR gates IC6a and IC6b are wired as inverters to form a CMOS oscillator running at about 700 Hz (60 wpm corresponds to about 25 Hz). Thus, a new bit code appears at the output of the counter every 1/700 of a second.

The keyer logic responds to whatever code is presented to it, generates the appropriate letter, and returns to its ready state. Because the generation of the letter is slow compared with the speed of the counter, the counter has counted from 0 to 31 many times during the time it takes for a letter to emanate from the keyer. The code present at the input of the keyer upon completion of the letter will therefore be a function of the letter length, the frequency of the counter oscil-

lator, and the frequency of the keyer oscillator. Since these are unrelated guantities, the bit code present at the counter output when the keyer is ready to generate a new letter will be independent of the bit code of the previously generated letter. Thus, random letters are generated.

Only 26 of the 32 possible counter states represent valid letters. Rather than detect these 26 states, we detect only the 6 states that are invalid and disable the Instructor output if one of these should occur. In fact, we need detect only 5 illegal states since the state 11111 corresponds to the condition of the keyer with no keys depressed and no output will ensue. Logic gates IC2, IC3, IC4, and IC1a and IC1b comprise the

unwanted-state detector. The output of IC2d goes high whenever one of the forbidden states occurs. This high is passed through IC6a and IC6b and holds the register, composed of D-type flip-flops IC10A, IC11, and IC12, in a set mode. That is, the output lines of the register are held high (11111), which is equivalent to having no keys depressed. No letter is generated. For all other combinations of B1 through B5, a letter is sent. There is no apparent pause in the output of the Instructor since new combinations of bits are created every 1/700 second.

Switch S1 in Fig. 3 allows the Instructor to be turned off by holding the register in a continuously high, or set, mode. The keyer may then be activated by the

keyboard and diode matrix. When S1 is grounded, the Instructor sends random letters in a continuous sequence. In its middle position, S1 is connected to the output of one-shot IC7. IC8 is wired as a four-bit counter that is clocked by the P/S line of the keyer. Since the P/S line goes from low to high after the generation of each letter, IC8 is clocked one count. When four letters are counted, the oneshot is triggered and its output goes high for a period of time determined by R1, R2, and C1. This high disables the D flip-flop register by setting it. The fifth letter is completed, but a new one is not generated until IC7 goes low. This period of silence can be made long, short, or nonexistent depending upon the position



Fig. 3. The electronics of the Instructor. Not all connections are shown to avoid confusion in the diagram. All points labeled Q1 to Q5 are connected together. Similarly, all those labeled Q1 to Q5 are connected together. All unused CMOS gates are tied to 12 volts.



Fig. 4. The power supply is not critical, and any voltage from 5 to 12 will work.

of S2.

Construction

Parts placement and inter-component wiring are not at all critical. I prefer to use wire-wrap techniques for digital logic circuits because it is fast and reliable. All the wiring can be completed in an evening or two. Care should be exercised in construction of the diode matrix, if it is included. With so many diodes, it is easy to make an error. However, troubleshooting, if required, can be accomplished with simple equipment. A voltmeter will indicate high or low states or an LED driven by a transistor will serve the same purpose. One of these simple tools will allow diagnosis of almost any possible problem.

The power supply is not critical. I chose to use a 12-volt regulator (Fig. 4), but anything from 5 to 12 volts will work and regulation is not necessary. It is a good idea, though, to filter the power supply adequately. Oscillators like the keyer clock have a tendency to synchronize with power supply ripple. If this occurs, speeds will appear to jump from one to another as the speed control is rotated, rather than to vary smoothly.

Variations

The Instructor portion of the circuitry can be used as is with many existing keyboards, and can be adapted simply for use with others. If the coding scheme in your keyboard uses diodes for dashes and character termination and operates from 5 to 12 volts, just connect the Instructor directly to it. If you can identify a portion of your keyboard logic that produces a lowto-high transition after each letter, connect it to IC8-1. If you cannot find such a point, leave out IC7, IC8, and IC10b. Then switch S1 to ground for continuous letter generation or to 12 volts for resumption of normal keyboard operation.

With keyboards that use other coding schemes, the illegal-logic-state detector must be modified. This should not prove to be difficult once it is understood exactly how the detector works. If, for example, your existing keyboard uses diodes for dots instead of dashes, simply reverse all $\overline{Q1}$ to $\overline{Q5}$ and Q1 to Q5leads. Other coding schemes will require similar simple changes.

As mentioned above, the Instructor-Keyboard also can be constructed without the keyboard or diode matrix and used as an Instructor alone. Simply construct keyer and instructor electronics as shown in the figures and attach 10k pull-up resistors to lines B1 to B8 of Fig. 2.

Numbers and punctuation can be added to the Instructor's vocabulary, if desired. However, this will require the addition of extensive detection circuitry to eliminate unwanted codes. In order to accommodate these additional characters, a total of 8 bits in a code word is needed. There are 256 combinations of zeros and ones in an 8-bit word. but the Instructor uses only a small number of them. Thirty-six are needed for letters and numbers. Adding a comma, question mark, and

period gives 39; special symbols will add a few more. In this case, we would have to detect 217 illegal words (ignoring special symbols which are not really needed for practice). It would undoubtedly be easier to detect the 39 legal ones, allow them to be passed through the register to the keyer, and reject all the rest. To do this, one simply would invert the output of the detector logic at IC6b. IC9 would have to be wired as a full 8-bit counter and two more D flip-flops would have to be added to the register.

References

1. Bryant, "Touchcoder II," QST, July, 1969; Horowitz, "Compucoder," QST, June, 1975; Crom, "This Station Plays Beautiful CW," 73, March, 1979; Helfrick, "An Inexpensive Morse Keyboard," QST, January, 1978. These articles contain additional references.

2. Hart, "High Speed CW, Anyone?" QST, June, 1979.

Reach Out!

just like adding a 10-watt amp to your 2-meter hand-held...

- True ⁵/₈ wave gain antenna
- Dramatically boosts reception as well as transmit range
- Individually tuned matching network
- Base spring/tuned coil protects radio as well as antenna from accidents
- Extends to 47", telescopes to only 8"
- BNC connector fits most current handheld and portable radios
- Better than 1.5:1 VSWR across the entire 144-148 MHz band
- Only \$24.95 from your dealer or postpaid from VoCom (Illinois residents please include 6% sales tax)

Ask about our 25, 50 and 100 watt amplifiers for hand-helds



QUALITY THAT SPEAKS FOR ITSELF!

Hustler fixed station two meter gain antennas.

Hustler is the choice of those who know quality. Because we're known for precision engineering and electronic expertise.

Only the finest materials are used to make a Hustler amateur antenna. And each model is the result of years of design excellence.

From easy and precise assembly to outstanding long-range transmitting and receiving, Hustler quality speaks for itself. See your dealer and find out why!



3275 North B. Ave., Kissimmee, Florida 32741

OW 2-MB 5 Cision 2-MB 5 Cision 66-144B Clearly the choice of those who know quality. Clearly the choice of those who know quality.

Sixteen Channels of Digital Delight

- do-it-yourself data acquisition

COUNTER-COMPARATOR A/D

ust his adding a 10-wait



Chris Bowick WB4UHY 1498 Holland Street Melbourne FL 32935

n my last article on A/D conversion (November, 1980), I covered some theory to help you understand the principles. Now we'll put that knowledge to work and build a complete 16-channel Data Acquisi-

Photo A. A good, low-cost 8-bit A/D made by Datel. Its output coding is in binary, it runs off 5 volts, and it has a conversion time of only 500 µs. Its current selling price is about \$8.00. (Photo courtesy of Datel)



Fig. 1. A block diagram of a complete 16-channel DAS that you can build with almost any A/D converter on the market today.

tion System (DAS-a 16-channel A/D converter).

Background

A portion of my last article dealt with the process of choosing the right A/D for a specific function. The gist of that section was that there are literally hundreds of A/D converters on the market today, and choosing the right one for your needs could be quite a difficult process if you don't know what to look for. The average hobbyist just does not need extreme accuracy or extremely fast conversion times. He is looking for an A/D which: (1) runs on common supply voltages, (2) covers the needed analog input range, and (3) has a digital output which is compatible with his interface circuitry.

There are quite a few low-cost A/D converters on the market which should satisfy most any hobbyist (see Photos A and B). But the purpose of this article is to show you how you can use that A/D to build a complete 16-channel DAS.

What is a DAS?

We know from my previous article that an A/D takes a single analog voltage and converts it to digital form. There are a lot of different conversion processes possible and a few different digital-coding techniques utilized in various A/D converters, but the end result is always the same-some kind of digital word representing the analog voltage level present at the A/D's input. This is just fine, but what if there were several different analog voltages which we wanted to digitize? Of course, if we had 16 different analog voltage levels to measure, we could go out and buy 16 A/D converters and wire



Photo B. Another Datel device which is a bit more expensive (\$34.00). It is a 12-bit binary or $3\frac{1}{2}$ -digit BCD coded A/D converter, and it runs off ± 5 volts and has a 20-ms conversion time. (Photo courtesy of Datel)



Fig. 2. The complete schematic for the 16-channel DAS utilizing the Teledyne 8700 series of A/D converters.





Photo C. This is what the big boys use for a 16-channel Data Acquisition System. The MP6812 can be had for a mere \$200.00. (Photo courtesy of Analogic)

them up in a maze of confusion. But if you're anything like me, you don't have the time or the money to throw away on such a huge project. You could, however (with a minimum of time, effort, and money), build the complete 16-channel DAS described in this article.

Fig. 1 is a block diagram of one possible candidate for a complete DAS. Basically, all we need to add to our A/D is a counter, two 8-channel multiplexers, and possibly some chip-select circuitry for the analog multiplexers. With the addition of this minimal amount of circuitry, we now can look at 16 different analog voltages without the maze of confusion mentioned above.

is really very simple. Let's assume an initial starting point for the DAS with the counter set to binary zero. In this state, the address inputs to each analog multiplexer will also be at binary zero and the chip-select line will choose only one of the multiplexers to be active. Thus, the analog voltage at switch address zero will be connected to the A/D and the conversion process will begin. When the A/D has converted the analog voltage to digital form, it outputs a pulse from "Data Valid" to clock the counter and to let the output circuitry know that the digital data at the output of the A/D is ready for use.

When the counter is clocked, it is incremented to binary 0001, and the analog voltage at switch one is now connected to the A/D for conversion. Again, the A/D performs the conversion process and outputs a pulse when it is finished, and, in this manner, all 16 analog voltages are converted to digital form in a multiplexed fashion until you tell it to stop. Another variation to this approach would be to get rid of the counter and to address the analog multiplexers directly with a microcomputer or thumbwheel switches. Therefore, any one analog channel could be accessed directly at any time and for any length of time you wish, without having to cycle through all 16 channels.

The operation of the DAS



Building the DAS

Fig. 2 is a complete schematic of a 16-channel DAS utilizing the Teledyne 8700 series of A/D converters.¹ The 8700, 8701, and 8702 are 8-, 10-, and 12-bit monolithic CMOS analog-to-digital converters, respectively, in a 24-pin DIP. Output coding is in binary, and its conversion time is fast enough for our purposes (1.8 ms for 8 bits). Its operation is exactly

Fig. 3. The PC board foil pattern for the schematic of Fig. 2. The pattern is shown from the foil side.

134 73 Magazine • December, 1980

as was explained for the block diagram in Fig. 1, so no other explanation should be necessary.

Figs. 3, 4, and 5 (which were graciously supplied by Michael Paiva, A/D Product Manager at Teledyne Semiconductor) show the foil pattern, pinout, and component layout for a singlesided PC board of the complete 16-channel DAS shown in Fig. 2.

For those of you who do not wish to make your own PC board, it is available directly from Teledyne or any of their distributors for \$5.00. Just ask for the 8700 Test Board. Of course, a PC board makes things nice and neat, but you can build your own through wirewrapping or direct wiring.

In the Parts List for the DAS, some components are marked with an asterisk. These are somewhat critical. The stability of the system is directly affected by



Photo D. Our finished product is propped up against my computer system.

stitutions could be made. For example, if an 8-bit A/D is used at room temperature, then 5% carbon resistors could be used in place of the 1% resistors because the resolution of an 8-bit A/D is only 0.4%. With a 12-bit A/D, however, these components will be very critical if full 12-bit accuracy is needed.

Following are a few suggestions that you may want to consider before building your DAS:

First, as in any project handling both digital and analog signals, keep analog signals as far away from digital signals as possible. To avoid ground loops, isolate the analog ground from the digital ground by using the system ground as the only common point between the two. Use adequate bypassing of supply voltages and, finally, make sure your reference voltage, V_{ref}, is as stable as you can make it. For example, an 8-bit A/D should require

the stability of these components. For standard hobby use, however, some sub-



Fig. 4. Component layout and edge connector pin assignments. Look carefully for all jumpers.

73 Magazine • December, 1980 135



NO MONKEY BUSINESS!

- (A) Complete Service Facilities
- (B) Good Deals on most Brands
- (C) Shipping within 24 Hours
- (D) All inquiries handled by Active Hams with over 20 years experience in ham radio

CALL TOLL FREE 1-800-238-6168

IN TENNESSEE, CALL 901-452-4276 MONDAY – SATURDAY 8:30-5:30 FOR YOUR SPECIAL.

Write: 3202 Summer Ave., Memphis, Tennessee 38112

Parts List

	Part Number	Description
1, IC2	4051	CMOS—8-channel analog switch
3	8700 type	CMOS—Teledyne A/D converter
4	4024	CMOS-7-bit binary counter
5	4011	CMOS—quad 2-input NAND gate
1	68 pF ± 10%	Low leakage mica, ceramic, etc.
2	270 pF ± 20%	Ceramic, mica, etc.
3, C4, C5	0.1 µF ± 20%	Ceramic, mylar, electrolytic, tan- talum, etc.
1	*953k ± 1%	Carbon, carbon film, metal film, etc.
2	*100k ± 10%	Trimmer resistor
3	*1 megohm ± 1%	Carbon, carbon film, metal film, etc.
4	100Ω ± 10%	Carbon resistor
5	20k ± 10%	Trimmer resistor
6	100k ± 5%	Carbon resistor
7	1k ± 5%	Carbon resistor
3	100k ± 10%	Carbon resistor
9	*20k ± 10%	Trimmer resistor
10	*243k ± 1%	Carbon, carbon film, metal film,

*See text.

IC

IC

C

C

C

R

R

R

R

R

R

R

R

R

R

0.04% voltage regulation (one-tenth of its resolution). Photo D shows my completed DAS in front of my computer system.

SQUELCH

COMMAND

Reference

1. Teledyne Semiconductor, AN-9, "Applications of the 8700 Series of CMOS A/D Converters."

close encounter



To demonstrate the selectivity of our Mark 3CR repeater we keyed a transmitter 15 KHz off frequency and set it directly against the receiver input. Our Mark 3CR didn't even notice the close encounter.

MARK 3-CR REPEATER

R

MICRO

CONTROL SPECIALTIES

Sure the Mark 3CR can withstand severe interference.. it uses both crystal filtering and double conversion. And that's just the beginning. Its performance continues with a transmitter that meets commercial specs plus a microprocessor controller that gives you 39 functions and 13 Morse messages. For peak performance have your own close encounter with a Mark 3CR / Repeater or Mark 3C Controller.

call or write for specifications <a>49

MICRO CONTROL SPECIALTIES

23 Eim Park, Groveland, Ma. 01834

(617) 372-3442





INDIVIDUAL COMPONENTS

MOS-1416	14-16 PIN MOS CMOS SAFE INSERTER	\$ 7.95
MOS-2428	24-28 PIN MOS CMOS SAFE INSERTER	\$ 7.95
MOS-40	36-40 PIN MOS CMOS SAFE INSERTER	\$ 7.95
EX-1	14-16 PIN EXTRACTOR TOOL	\$ 1.49
EX-2	24-40 PIN CMOS SAFE EXTRACTOR TOOL	\$ 7.95

MINIMUM BILLING \$25.00. ADD SHIPPING CHARGE \$2.00. NEW YORK RESIDENTS ADD APPLICABLE TAX.

OK MACHINE & TOOL CORPORATION 3455 CONNER ST., BRONX, N.Y. 10475 (212) 994-6600/TELEX 125091

Ed Ingber WA6AXX 10816 Northridge Square Cupertino CA 95014

A Computer-Controlled Talking Repeater - part III: interfacing to the microcomputer

he first two parts of this article provided an overview of the project and microcomputer hardware and software nucleus details. This final part describes interfacing of var-

ious peripheral circuits to the microcomputer.

Speech Synthesizer

The most distinctive characteristic of the repeater is its voice, provided by Telesensory Systems' S2B and S2C Mini Speech Synthesis PC boards. Each board has a vocabulary of 64 words. The S2C contains the ASCII character set and the S2B provides 64 additional words such as ten, eleven, twenty, thirty, hundred, clear, Hertz, and other useful radio-type words. The speech synthesizer is used for IDing the repeater, reading back commands, and for reading



out signal strength and frequency error measurements. The boards are perfect for countless other microcomputer-based applications including remote bases, home remotecontrol systems, and speech-response terminals. Each board is about 3"

by 3" with a 20-pin connector on one end. They contain a 40-pin LSI synthesizer chip, 24-pin ROMs containing the vocabulary, and a couple of resistors and capacitors. The internal clock frequency is controlled by an RC network, but if desired, the board can be driven by an external clock for more precise pitch control.

To generate speech, a sixbit binary code representing the desired word is applied to the board and the start input is pulsed. The busy output signal goes low, remaining low until the word is complete. The code for the next word can then

138 73 Magazine • December, 1980 be applied, the start input pulsed, etc. It couldn't be easier!

The Telesensory speech synthesizers are fundamentally different from synthesizers that have been available for hobby computers. Control requires only presenting the six-bit representation of the word desired. Other synthesizers require a complex construction of commands for each word, and it becomes a game to understand what the machine actually said. Such systems are really toys-not tools. If only a limited vocabulary is required, the Telesensory boards are the perfect solution. The voice sounds authoritative, rather than friendly like the voice of the TI Speak and SpellTM, and is more intelligible and punches through any background noise.

Synthesizer Hardware Interface

The pitch of the speech output normally is deter-



Photo B. IC-22S with interface board plugged into old diode programming board location. Molex connector on back carries all the signals.

ple interface circuit to drive ple of volts peak to peak. boards goes to the repeat-5-volt logic. The signals are Telesensory recommends a er's audio mixer circuits.

mined by the board's RC oscillator circuit. By removing the resistor and capacitor, an external clock signal can be used to eliminate the possibility of frequency drift with time or temperature and to precisely match the pitch of the two boards. The clock signal is generated by a programmable counter/timer on the Pragmatic Designs CPU-1A microcomputer board, dividing the CPU's crystalcontrolled clock frequency to 24 kHz.

The six-bit word-select code for both boards is provided by the computer's DACPORT output port, and the individual start strobes are provided by two bits of XPORT output port. To guarantee logic level compatibility, pull-up resistors to +5 volts are included for each synthesizer input line.

The synthesizers' busy output lines require a sim5-volt logic. The signals are brought into the 8085A's interrupt 5.5 and 6.5 inputs, used as an input port—not really as interrupt inputs.

The speech output is a high-impedance (10k) cou-

Telesensory recommends a filter network to shape the audio response, but we found that it sounded far better through the repeater with virtually no filtering. The audio from the two

Synthesizer Software

73 Magazine • December, 1980 139

Messages to be spoken are generally stored as strings in the microcomputer's ROM. Other messages



Fig. 1. Speech synthesizer hardware interface to microcomputer.

Table 1. Speech synthesizer control subroutine.

3204

200

1120 01401

				TOPE FITO
	FSPEECH	SYNTHESIZER CONT	TROL ROUTINE. (HL)-> CHARACTER STRING.	32C5 E630
	FCHARAC	TER STRING TERMIN	NATED BY OFFH.	3207 022833
	FCODES	20H TO SFH ARE AS	SCII. CODES 60H TO 9FH	32CA 2A2010
	FARE TE	LESENSORY *STANDA	ARD" VOCABULARY. CODES OON TO OCH	3208 78
	JARE BC	D AND STAR/POUND	(OAH NOT USED).	32CE 84
	#IF 220	SPEECH IS INTER	RUPTED, ROUTINE RETURNS WITH CY=1.	32CF CAF532
	-			32D2 DB1A
1D4C =	SPDELAY	EQU 7500	JINTER CHARACTER DELAY	32D4 E608
7530 =	SPWORDE	LAY EQU 30000	FINTER WORD DELAY	3206 CAF532
0032 =	TSPTIM	EQU 50	ISPEECH MALFUNCTION TIMER=1.3 SEC	32D9 3A4410
		and the second se		32DC OF
3250 =	TALK	EQU \$		3200 DAF532
3250 05		PUSH B		32E0 3A4510
23420321	-	1 contraction		32E3 OF
3250 =	TALK1	EQU .		32E4 DAF532
3250 F3	- Aleria	DI	IPPOTECT CRITICAL AREA	32E7 3A4D10
325F 0812		TH YPOPT	ITAKE BOTH ETROBEE HTOH	32EA OF
3260 F60C		ORT SPISTE OF R	POCTE	32EB DAF532
3262 0312		OUT XPORT		32EE 3A4E10
3264 CD4831		CALL TTREVETEST	ITALKING TO PADIO OF PUDNET	32F1 0F
3267 CA7032		JZ TALKID	LIF TO PHONE, DONT NUTE OR	32F2 D2FD32
326A DB1A		IN AUDI	IXCON RE AUDIO TO 220 YHTE	32F5 =
326C E6FD		ANI CRBRT0220	Theorem has not and the same	32F5 2A2F10
326E 0310		OUT AUDI		32F8 7D
		and house		32F9 B4
3270 =	TALKID	FOU &		32FA C2C432
3270 FB	THEORE	FI		
3271 75		HOU ANH	IGET PUADACTED	32FD =
1272 21		THY H	JUEI UNHRHUTER	JOED FT
3273 FFF0		CPT OFOH	TOHAD EDON AUTODIAL HENR	32FE DB1A
1275 047510		IC TALKIC	I UNC A DIVERSION	1300 FAF7
1278 EAGE		ANT OFH	ITE VEC. THEN HARY OFF HE BITS OF SER	1102 D314
3276 FEOF		CRT OFH	HAFT CHAPT INCH MADA OFF HS BITS SU BLU	3304 FR
327C CA1533		17 ETHTALK	IETHTOUCH TE WEG	3304 10
Serv smadda	10	JE PARTEN	FRATORED IF. TED	7705 -
327F =	TALKIC	FOU .		3303 -
327F FE20	Constraint.	CPT 20H	INOT ETHICHER, SPACE?	3305420
3281 CA3533		JZ SPACETALK	ITE YES, HIST DELAY	130A FA30
3284 FEOD		CPI ODH	LECD OR STAR /POIND?	3308 021333
3286 029932		INC TOLKIA	The an armitigne:	330B 202E10
3289 C630		ADI JOH	IVES, CONVERT TO ASTIT	130F 70
3288 FE38		CPT 3BH	ITE IT STADY	TROF BA
3280 C20232		INT TALKID	748 41 BINN	7710 000877
3290 3E24		HUT A-20H	TTE VER. HEE TELES CODE	3310 020533
States Manual			THE TEST OF TELED CODE	7717 -
3292 =	TALKIR	FOU S		3313 =
3292 FE3C	(Cestan) and	CPI 3CH	ITS IT POUNDY	3313 37
3294 C29932		JNZ TALKIA		3314 ET
3297 3E23		HUI A.23H	HUSE NUMBER (POUND)	3715 -
SHOLD BREEZE			The manager trading?	3315 51
3299 =	TALK1A	EQU \$		3313 73
3299 EE20	(completely	XRT 20H	INFUENCE BIT 5 TO MATCH TELES CODE	3310 01
329B FB		FI	THETEROL DAT D TO THICH TELED GOOL	331/ FD
3290 76		HL T	ISYNCHRONITE TO RETTS TO DUARANTEE SETUR	3318 SHUILU
3290 F3		81	TO NOTICE TO NOTIO TO DURANTEE DETUR	3318 2020
329E 0311		OUT DACPORT	LAND HOLD TIMES, ONTOUT TO SYNTH DATA	3310 7220
32A0 0632		HUI 8.50	IDELAY TO OBSERVE SETUR PEOUTPENENTS	1122 DDIA
3262 05		DCP B	TAPERT TO ABORNAL SETUP REMATKEMENTS	TTTA FIAT
3263 026333		JNZ 8-1		1724 0714
TOAL FEDA		VDT DOU	IFI TO DACK DIT &	3326 D318
3240 EE20		CRT (OH	INCLT BALK BIT D	7700
7200 PE00		INC TALKS	TABLIT OK STANDARD VOLABULARTT	3328 =
3200 0458		HUT P-COMMOTO	LARCTT, BOARD I UNICTOODE	3328 F1
TOAF DIRATE		INP. TALKT	INDETTI BUNKU I UNDIKUBE	7724 00
SENT COD432	1.1	JHIP THENS		332A CY
3282 -	TAL NO	FOU .		1128 -
3282 0AF7	Inche	MUL B. SPOUNGTR	ISTANDARD, BOARD 2 UNSTRODE	1120 51
		THE PERSON AND THE PE	A CONTRACT AND A MILLING A CONTRACTOR	0000 01

	1		
-	TALK4	FOU &	
	PILITY	PIN	ISPEECH EINTSHEDT
120		DR 20H	Tareson ranaoneer
EATO		ANT INTAS	
COORTS		W7 TALES	I THE TE DONE HORD
262010		I WER I TTREEP	1350 SOUELCH OPENY
70		HOU AN	TEEV SUGELLIN OFENT
PA		DRA H	
PACETO		IT TALKAA	IND. CONTINUE
DRIA		JE INLINA	LIVERS TALETHO TO PADIOR
5400		ANT SEPTORO	TTEST THERING TO RADIO!
CACETO		17 TALKAG	THO. CONTINUE
LAFDAZ		JE THERAH	IVER HONOLDONE HADA ANNER
384410		LDA NWAKA	TEST HUNDLUBUE WARM ANNUT
DAFETO		IC TALKAS	IVER PONTINIE
704510		I DA POTUADU	IDATCH TTHED HADNINGT
3H4310		PPC	FRICH LINCK MARITINGT
DAFETS		IC TALEAA	IVER, CONTINUE
ZAADIA		LDA DCOUED	IND. COUCO TONES
244010		LUN FLOVER	THOF LOVER TORET
UP DATE TO		MAL .	
DAF532		JC TALKAA	ATT CONTRACTOR
384110		LDW TILUVER	TTT COVER TONET
01		NKL	
D2FD32		JNC TALKABORT	
	TALK4A	EQU 4	
2A2F10		LHLD LGPT	FND, MALF TIMER TIMED OUT?
7D		HOV A+L	
B4		ORA H	
C2C432		JNZ TALK4	
	+		
=	TALKABO	RT EQU .	
F3		DI	IYES, ABORT
DB1A		IN AUD1	FXCON SPEECH AUDIO
E6F7		ANI CSPT0220	
D31A		OUT AUDI	
FB		EI	
1995 - C			
	TAL KARD	RT1 FOULS	
		PTM	
+26		DE 20H	
EA30		ANT INTAS	WATT FOR FWR OF SPEECH
021333		INT TALKABORT2	renal run env or orecon
202510		LHD LGPT	ICHECK HALF TIMER
70		HOU A-I	Toneon mer Tanen
PA		DPA H	
COARTY		INT TAL PADDETS	HORD INTEL DONE
020533	140	JNZ TALKABURTI	FLOOP UNTIL DUNE.
	TAL MADO		
all and a second se	TALKABU	RTZ EUU \$	they are not attended on the
37		STC	FSET CY FOR INTERRUPTED RETURN
E1		POP H	
-	FINTALK	EUU	
F3		DI	
C1		POP B	and the second second second second second second
FD		PUSH PSW	FRECONNECT RB AUDIO IF NECESSARY
360110		LDA MBOR	
E628		ANI SRBEN OR SR	BRON
FE28		CPI SRBEN OR SR	BROM
022833		JNZ FINTALKI	Table and the second
DBIA		IN AUDI	TRECONNECT
F602		ORI SRBRT0220	
D31A	123	OUT AUD1	
-	FINTALK	1 EQU \$	
F1		POP PSW	
FB		EI	
C9		RET	
		WARNE ST	
1(=	TALK5	EQU \$	
E1		POP H	

1284	-	TALKT	FOIL 4			and area search rannan
3284	DB12	THEAS	IN XPORT		332F =	TALKSA EQU 1
32B6	AO		ANA B		332F CD9934	CALL DEL2
3297	0312		OUT XPORT	JUNSTROBE IT	3332 C35032	JHP TALK1
3289	FB		EI			;
328A	76		HLT	IAND ALLOW DELAY OF BUSY LINE		Francisco and a second second second
328B	FB		EI			IDELAY WORD SPACE TIME
3280	76		HLT			
32BD	85		PUSH H		3335 =	SPACETALK EQU \$
328E	213200		LXI H.TSPTIM		3335 013075	LXI B.SPWORDELAY
3201	222F10		SHLD LGPT	ISTORE MALFUNCTION TIMEOUT IN	3338 C32F33	JMP TALK5A
		3		4 GENERAL PURPOSE TIMER		



Fig. 2. A/D converter hardware for reading the meters.

140 73 Magazine • December, 1980

are generated by computations made by the computer and are stored as strings in RAM. Prior to generating speech, the computer enables the synthesizer's audio mixer to the transmitter and/or phone line. The TALK subroutine expects the HL register pair to point to the character string in memory, and the string is terminated by a OFFH code. If speech to the transmitter is interrupted by a receiver squelch open, speech aborts and the subroutine returns with the carry flag set. There are certain exceptions to this rule, including timeout announcements and cover tone generation.

The TALK subroutine is

Table 2. Meter-read program extracted from the background module, TRAP interrupt module, and foreground module.

0510 E1 POP H 0511 D1 POP D 0512 C9 RET ### FOREDROUND SEQUENCE DECODE ROUTINE ### # ### BACKGROUND METER READ ### IDATA ACQUISITION. TICK COUNTER DETERMINES A CHANNEL TO BE # S-METER AND DISCRIMINATOR READ ANNOUNCEMENT. IMEASURED BY A/D CONVERTER. VALUE ENTERED INTO PROPER FLOCATION OF A/D TABLE. TABLE CONTAINS LAST 16 MEASUREMENTS OBDS -SSMETER EQU # FOF 4 CHANNELS. **OBDB 21050C** LXI H, SMETABLE #POINT TO TABLE 0103 = DATAACO EQU \$ **OBDB 110600** FADD CONSTANT LXI Dr6 01D3 DB13 IN CHPORT **ISELECT A/D CHANNEL** OBDE = SSHETER1 EQU # 0105 E6FC ANI NOT ADMASK **FCURRENT PORT VALUE** OBDE 3A0810 LDA READING FOET LAST AVERAGED VALUE 0107 47 HOV B.A 01D8 7E **OBE1 47** HOV B.A HOV A.H *ITICK COUNTER* 01D9 E603 ANI ADMASK FLS 2 BITS 0BE2 = SSHETER2 EQU # OIDS BO ORA B I OR IN A/D CHANNEL BITS OBE2 7E HOV A.H **FCORRECT VALUE?** 01DC D313 OUT CHPORT JAND SELECT OBE3 B8 CMP B OBE4 D2F40B JNC METALK FIF YES, SAY VALUE 01DE 0600 MUI B.O ISUCCESSIVE APPROXIMATION A/D CONVERSION **OBE7 19** DAD D *FIF NOT, TRY NEXT VALUE* 01E0 0E80 HVI C+BOH IB=CURRENT VALUE, C=MASK BIT **OBEB C3E20B** JHP SSMETER2 01E2 = DATA1 EQU \$ ID-METER ANNOUNCEMENT. 01E2 78 HOV A.B **JSET NEXT BIT** 01E3 A9 XRA C OBEB = DDMETER EQU \$ 01E4 47 HOV B,A **OBEB 21650C** LXI H, DMETABLE ; POINT TO TABLE 01E5 D311 FAND SEND CURRENT VALUE TO DAC OUT DACPORT **OBEE 110800** LXI D.8 FADD CONSTANT 01E7 00 NOP FALLOW OP AMP TO SLEW **OBF1 C3DE0B** JMP SSMETER1 FCONTINUE 01E8 00 NOP 01E9 00 NOP OBF4 = HETALK EQU # 01EA 00 NOP **OBF4 23** INX H **#PDINT TO FIRST CHARACTER** OIEB DB19 IN RPORT FLODK AT COMPARATOR **OBF5 E5** PUSH H **ISAVE POINTER** 01ED E680 ANI ADCOMPB **OBF6 2A0910 #WAS MIKE HELD DOWN FOR** LHLD READTIME 01EF C2F501 JNZ DATA2 **FIF HIGH, LEAVE SET OBF9 1186E5** LXI D+-(THT-20) # AT LEAST 1/2 SECOND 01F2 78 HOV A.B FIF LOW, CLEAR IT **OBFC 19** DAD D # SO HAVE VALID AVERAGE? 01F3 A9 XRA C POP H OBFD E1 **FRESTORE POINTER** 01F4 47 HOV B,A **OBFE DA4FOB** FABORT IF NO JC FINSEQ OCO1 CD3B33 CALL TALKR FSAY IT DATA2 01F5 = EQU \$ JMPFINSED # DONE 01F5 79 MOV A+C INEXT MASK 0C04+E7 RST 4 01F6 OF RRC 01F7 4F HOV C+A FS-METER TABLE OF VALUE AND SPEECH 01F8 D2E201 JNC DATA1 ICONTINUE FOR 8 POSITIONS 0005 =SHETABLE EQU \$ 01FB = DATA3 EQU \$ 0C05 825330FF00 DB 82H. '50'.0FFH.0.0 01FB 2A0610 LHLD CURRENTVALUE #A/D TABLE POINTER OCOB 845331FF00 DB B4H+ 'S1'+ OFFH+0+0 01FE 70 HOU M.B **IPUT VALUE INTO TABLE** 0C11 885332FF00 DB B8H+ 'S2', OFFH+0+0 01FF 23 INX H 0C17 905333FF00 DB 90H, 'S3', OFFH, 0, 0 SHLD CURRENTVALUE 0200 220610 0C1D 985334FF00 DB 98H+ 'S4'+ OFFH+0+0 IWRAPAROUND? 0203 7D MOV ArL DB OAOH. 'SS'. OFFH. 0.0 0C23 A05335FF00 CPI LOW FINADTABLE 0204 FEBA 0C29 A85336FF00 DB 0ABH+ 'S&'+0FFH+0+0 JNZ FIN75 0206 C2D900 ING. DONE 0C2F 805337FF00 DB OBOH, "S7" + OFFH + 0 + 0 0209 217A10 LXI H, ADTABLE IYES, WRAP AROUND TO BEDINNING 0C35 885338FF00 DB OBBH+ 'S8'+OFFH+0+0 020C 220610 SHLD CURRENTVALUE 0C3B C05339FF00 DB 0COH+ 'S9'+0FFH+0+0 020F C3D900 JHP FIN75 FNOW DONE 0C41 C85339286A DB OC8H+'S9'+PLUS+TEN+OFFH DB ODOH, 'S9', PLUS, TWENTY, OFFH OC47 D053392874 # *** TRAP ROUTINE, AVERAGE READINGS AND STORE *** DB ODBH, 'S9', PLUS, THIRTY, OFFH OC4D D853392875 OC53 E053392B76 DB OEOH, 'S9', PLUS, FORTY, OFFH OC59 E853392877 DB OE8H, 'S9', PLUS, FIFTY, OFFH 04E4 = TRAPSHET EQU \$ OC5F FF53392878 DB OFFH. 'S9' . PLUS, SIXTY, OFFH LXI B.ADTABLE ICHANNEL O (TICK 4) IS SMETER 04E4 017A10 0065 = FINSMETABLE EQU # 04E7 C3ED04 JHP AVBIT #(BC)-> START OF SMETER RAM VALUES IDISCRIMINATOR METER TABLE OF VALUE AND SPEECH 04EA = TRAPDHET EQU \$ 0065 = DHETABLE EQU # 04EA 017B10 LXI B.ADTABLE+1 ICHANNEL 3 (TICK 3) IS DMETER

0506 70

0507 320810

050A 2A2510

050B 220910

MOV A+H

LHLD LHT

STA READING

SHLD READTIME

FMS BYTE IS AVERAGE

FSTORE MONOLOGUE TIMER SO KNOW

THAT MIKE HELD DWN LONG ENOUGH

#STORE IT

				VLGD IF 2DAE 3D4B	DB IFM+MINUS+UREATERTMAN+ SK +MENTZ+OFFM+0	
04ED =	AVGIT	EQU S		0C6D 2C2D354B96	DB 2CH+MINUS+'5K'+HERTZ+OFFH+0+0	
04EB 05		PUSH D	LAUFRAGE PREUTOUS 14 PEADINGS	OC75 442D334B96	DB 44H, MINUS, '3K', HERTZ, OFFH, 0, 0	
DAFE ES		PUSH H	THE THE THEFTERS IS HEREITS	OC7D 582D324896	DB 58H, MINUS, '2K', HERTZ, OFFH, 0, 0	
04FF 210000		IXI H.O	LCUMULATTUE SUM	0C85 622D318335	DB 62H+MINUS+'1'+POINT+'5K'+HERTZ+OFFH	
0452 110000		LYT D.O	IDE-NEVT LIALUE	0C8D 6C2D314896	DB ACH. MINUS. '1K'. HERTZ. OFFH. 0.0	
0462 110000		LAI DIO	IDE-MEAT VHEUE	0095 7020387096	DR 20H+MINUS+ 'R' +HUNDRED -HERTZ+DEEH+0+0	
ALTE -	AUDITA			0090 7420367096	DR 74H. NTNUS, "A" . HUNDRED. HERTZ. OFFH. 0.0	
0453 #	90111	EMU .	LOFT HALVE	0045 7820347096	DB 704-MINIG. (A' WINDED. HERTT. DEEN. 0.0	
04F5 0A		LDAX B	FOET VALUE	0000 2020322004	DE 704-NTHUE-121-NUMBER HERT OFFICIO	
04F6 5F		MOV ETA	IDE=VALUE	0005 0470707004	DB DAW LECCTUAN (2) HUNDEED HERTZ OFFHIOTO	
04F7 19		DAD D	INEW SUM IN HL	0000 0430327070	DB BAHILEBSTHAN, 2 HUNDREDINERTZIOFFH,0,0	
04FB 03		INX B		0080 8828327098	DB BBH+PLUS+ 2 +HUNDRED+HERTZ+OFFH+0+0	
04F9 03		INX B		OCC5 BC2B347C96	DB BCH+PLUS+ 4 + HUNDRED+HERTZ+OFFH+0+0	
04FA 03		INX B		OCCD 902B367C96	DB 90H+PLUS+'6'+HUNDRED+HERTZ+OFFH+0+0	
04F8 03		INX B	INFXT UALUE	OCD5 9428387C96	DB 94H, PLUS, '8', HUNDRED, HERTZ, OFFH, 0+0	
04FC 79		HOU A.C	THE PERSON PROPERTY AND A PERSON PROPERTY A PERSON PROPERTY AND A PERSON PROPERTY AND A PERSON PROPERTY AND A	OCDD 9D2B314B96	DB 9DH+PLUS+'1K'+HERTZ+OFFH+0+0	
CAED FERA		CRT LOW ETHADT	ABLE IDONE?	OCE5 A828318335	DB OABH, PLUS, '1', POINT, '5K', HERTZ, OFFH	
DATE BAFFOA		IP AUGTTA	HOLE TOUTE (OCED BC2B324B96	DB OBCH, PLUS, '2K', HERTZ, OFFH, 0,0	
OFOO DO		JL HVOITI	INTO HOU OFT O HOD	OCF5 D42B334B96	DB 0D4H+PLUS+'3K'+HERTZ+OFFH+0+0	
0502 29		DAD H	FTESF NUW DEL & MSB	OCFD E12B354B96	DB OF1H.PLUS. '5K' HERTZ. OFFH. 0.0	
0003 29		DAD H		0D05 FF2B3F354R	DR OFFH-PLUS-ORFATERTHAN- 15K - HERTZ-OFFH-O	
0504 29		DAD H		ODOD - ETNOEN		
0505 29		DAD H	FX 16 IN HL	Prop - FINDER	CIMPLE CHU *	

listed in Table 1. Optimum selection of the synthesizer's pitch and inter-character delay is essential to achieving the best intelligibility.

Meter Read

The repeater's meterread capability allows users to request S-meter and discriminator meter readings to check signal strength and frequency error. Analog voltages from the receiver are buffered and brought to the A/D converter on the CPU-1A microcomputer board. Provisions are made for four analog channels,

although only two are used presently. The background module measures each channel every 26.6 ms, and the reading is stored with the 15 previous readings for that channel in RAM. When the proper touchtoneTM key sequence is detected by the TRAP interrupt module, the 16 readings for the appropriate channel are averaged and stored, to be retrieved by the foreground sequence-detect branch routine which speaks the meter value over the air. When a meter-read command is entered, therefore, the average reading over

the last half second is read, reducing the effect of noise and flutter.

The A/D converter consists of a DAC-08 8-bit digital-to-analog converter with a current-to-voltage converter, analog multiplexer, and comparator. The DAC is driven by DAC-PORT output port, the multiplexer by CHPORT output port, and the comparator is read through RPORT input port. A 300-µs total conversion time successive approximation algorithm is used.

The meter-read software consists of three routines in

the background, TRAP interrupt, and foreground modules. The listings of each are shown in Table 2.

Remote Base

An Icom IC-22S twometer synthesized transceiver serves as a remote base, commandable through the repeater. Command codes independently enable the remote-base receiver and transmitter, allowing monitoring only and talking over the twometer signals. The IC-22S synthesizer is under control of the CPU-1A microcomputer, allowing users to pro-

73 Magazine • December, 1980 141

Table 3. IC-22S remote-base frequency control routine. Touchtone command is decomposed and determines programming frequency.

> FREMOTE BASE FREQUENCY LOAD SEQUENCE DECODE ROUTINE. FPOINTER TO START OF COMMAND STRING ON TOP OF STACK. FINTERPRETS STRING OF FORMAT (1'S MHZ) (100'S KHZ) 1(10'S KHZ) (1'S KHZ) (1=-600KHZ,2=SIMPLEX, #3=+600KHZ XHT OFFSET) AND PROGRAMS IC-225. SAMPLE STRING FOR .34/.94 IS 69401. RBLOADP EQU # POP B (BC)-> START OF STRING LXI D.FINSEQ PUSH D **FPUT FINSED ON TOP OF STACK** LDA RBOR FRB ENABLED AND ONT ANI SRBRON DR SRBEN CPI SRBRON DR SRBEN RNZ FRETURN (TO FINSED) IF NO MOV L+C **#STRING START ADDRESS** MOV H+B SHLD TEMPAIR

SAUE ADDRESS

ARCI

087B =

OB7B C1

087F D5

OB7C 117108

OBBO 3A0110

OB8A 221310

OB83 E628

OB85 FE28

0B87 CO

OB88 69

0889 60

OBBD	0A		LDAX B	FTYP STRING=69401(FF)
OBBE	FE08		CPI 8	FCHECK FOR 145-147 MHZ
0890	DO		RNC	
0891	FE05		CPI 5	
0893	08		RC	
0894	D606		SUI 6	FSTART FORMING VALUE
0876	216803		LXI H,1000	
0899	CAA50B		JZ RBLOAD1	
OB9C	210000		LXI H.O	
OBPF	FAA50B		JH RBLOAD1	
OBAZ	210007		LXI H+2000	15-20.6-21000.7-22000
		F		
OBAS	*	RBLOAD1	EQU S	
0BA5	03	and a second second	INX B	
OBAS	0A		LDAX B	ICONVERT BCD TO 0-2999 BIN
OBA7	116400		LXI D:100	IX100 (HUNDREDS)
OBAA	-	RBL0AD2	EQU \$	
OBAA	30		DCR A	
OBAB	FAB20B		JM RELDAD3	
OBAE	19		DAD D	
OBAF	CJAAOB		JHP RBLOAD2	
		:	THE ASSESSMENT	
OBB2		REL DAD3	EQU .	
OBB2	03	CONTRACTOR OF	TNX B	
OBB3	0A		LDAX R	
OBB4	110400		LXI DelO	IXIO (TENS)
		1	Ent Priv	TALY TILIDY
OBBZ		RBI DADA	FOU &	
OBB7	30	THE OTHER	DCR A	
OBBR	FARFOR		JH RRI DADS	
OBBR	19		DAD D	
ORRC	CIRTOR		INP PRI DADA	
vepu	430790		ane nounnus	
OBRE	-	PRIDADS	EDII 6	
OBBE	0.1	NECONDO	THY B	
OBCO	0.0		LDAY B	INI CONFES
OPCI	87		ODA A	ICUMUS DE C DO E PUT
OBCI	COCHAR		UKH A	SHUDED BE O OK S KHZ
and the second se			and the second second second	

BC5	3E20		HVI A+SPACE	IS OF INSERT SPEECH SPACE
BC7	02		STAX B	
BCB	C3D00B		JMP RBLOAD6	
1000		Fine Lores	See 1	
BCB	FEAE	RECORDA	CDT 5	
BCD	FEUS		847	LTNUAL TO ERED
BCE	SE		HOU F.A	LADD ONES
BCF	19		DAD D	They unco
		4		
BDO	-	RELOADS	EQU 6	
BBDO	116202		LXI D.610	TADJUST
BD3	19		DAD D	
BD4	11F1FF		LXI D+-15	THL=0-2999+ MULTIPLE OF 5
BD7	05		PUSH B	INOW DIVIDE BY 15
RDR	0600	-	WVI B+0	
ADDA	-	PRI DADZ	COU	
RDA	19	RECORD/	DAD D	INFER SURTRACTING UNTIL DONE
BDB	04		INR B	THEN SHOTHIGTING UNTIL DURL
BDC	70		HOV A.H	INEGATIVE? IF YES ERROR
BDD	07		RLC	F (NOT MULTIPLE OF 15 KHZ)
BDE	DAESOB		JC RBLOADB	
BE1	B5		ORA L	IZERO? IF YES DONE!!!
BE2	C2DAOB		JNZ RBLOAD7	
APR.		PHI DADO		
BED	=	RELUADE	HOU E.P	
REA	C1		POP B	IVALUE TO BU TO ILZZ TH E
BET	08		RE	IRETURN IF NEG (ERROR-NOT MULT OF 15)
BEB	03		INX B	
BE9	0A		LDAX B	HGET OFFSET, 1=-600+2=SIMPLEX+3=+600
BEA	FE01		CPI 1	1-600 KHZ?
DBEC	C2FBOB		JNZ RBLOAD9	
DBEF	3E2D		HUI A.HINUS	ISAY 'MINUS'
OBF1	02		STAX B	A DESCRIPTION OF A DESC
DBFZ	78		MOV ArE	FAND PROGRMAN 600 KHZ LOWER
5-18C	0628		501 40	
DRFA	LADE		NUT D.NOT REDUP	A ISET DIPLEY A
BFB	C3100C		JHP RETALK	
	1. (1.1.1.1.1.1.1.1.1.1.1.1.1.1.1.1.1.1.		THE CONTRACT	
BFR	=	RELOADY	EGU \$	
DBFB	FE02		CPI 2	FSIMPLEXT
DBFD	C2080C		JNZ RBLOAD10	
0030	3653		HUI A, 'S'	FSAY 'S', SIMPLEX
0002	02		SIAX B	
0003	1000		IND PRIALE	
0000		1	SHIP NOTHER	
0008	=	RBLDADIG	O EQU S	
8030	FE03	100000000000000	CPI 3	14600 KHZ?
A030	CO		RNZ	FINVALID IF NOT
OCOB	3E2B		HVI A, PLUS	ISAY 'PLUS', DUPLEX B
OCOD	02		STAX B	
OCOE	16EF	4	MUI DINOT REDUP	P. and S.
		hannin		
0010	DRID	RETALK	TN AUDO	
0012	FATO		ORT REDUPA OF P	BDUPB
0014	A2		ANA D	ISET DUPLEX/SIMPLEY HODE DE TE22
0015	D31B		OUT AUD2	
0017	78		HOV ALE	
0018	2F		CHA	
0C19	320028		STA IC22FRE0	WRITE FREQ TO EC22
0010	2A1310		LHLD TEMPAIR	FORIG (HL) POINTER
OC1F	C33833		JHP TALKR	ISAY NEW FREQUENCY ON RADIO

ated switch, eight syntransmitter offset. The interface signals to thesizer frequency control the IC-22S include transmit lines, plus DUPLEX A and and receive audio, push-to-DUPLEX B control lines.

gram the frequency and talk, receive carrier-oper- The interface circuits sim- pull-down resistors in the

*5V

ply convert the 5-volt logic levels of the microcomputer to the CMOS logic levels of the IC-22S. The



Fig. 3. IC-22S remote-base hardware interface to microcomputer. This hardware replaces the diode programming board. Note: R37 common taken to +5 V, R36 taken to +5 V, and dp resistor restored to pull-down.

IC-22S are made pull-up resistors so that the open collector buffers can function properly. The IC-22S simplex/duplex switch must be kept in the simplex position. The circuit was built on a small board which plugs in directly, replacing the diode matrix board. Icom's molex[®] connector option mounts on the back to carry the signals.

The software listing is provided of the routine which programs the synthesizer's frequency and offset. The routine is executed by the foreground in response to detection of a remote-base frequency-programming command when the remote base is on. The command code consists of: (least significant MHz), (100s kHz), (10s kHz), (0 or 5 kHz), and (1 for -600-kHz offset, 2 for simplex, 3 for +600-kHz offset). For example, the 146.34/.94 pair may be selected by keying



Fig. 4. Audio delay line schematic. Audio output is delayed 50 ms from the input, with squelch tails and touchtone chopped off.

in touchtone command 69401. The routine listed decomposes the command stored in the key buffer in RAM and programs the frequency synthesizer. The frequency then is read back by the speech synthesizer.

Sequence Detector

The sequence detector is a foreground task routine. Its task-pending bit is set by the timeout of the "220 only beep timer," so the task routine executes after every 220 transmission. Usually, the sequence detector finds an empty buffer and simply cleans up and returns to the foreground nucleus. If touchtone data keys have been placed in the key buffer by the TRAP input routine, meaning that commands have been sent, the sequence detector analyzes the command and, if

valid, branches the program to the appropriate command routine.

A listing of a strippeddown sequence detector program is shown in Table 4. Since the # key can be used as a "clear" to cancel previous keys during a transmission, the routine scans down from the top of the used part of the buffer to either the bottom of the buffer or to a # key — whichever is found first. That point is the start of the command to be recognized.

The sequence detector is table driven—command routine addresses are stored in tables and are retrieved by the sequence detector to determine the branch location.

The first branch is based on the number of keys in the sequence — much information on the meaning of the command is provided by its length. For example, the remote-base frequencychange command may be the only valid five-digit command. The program can branch immediately to the remote-base frequency change routine to evaluate and act upon the command.

When the number of keys in the command does not uniquely identify the command, further processing occurs. If single-digit commands are used, the key value can be used to find its routine address in the ONETAB address table. For multiple-digit commands, a routine (COMP-SEQ) compares each digit of the command up to the last digit to a valid string stored in the program. If the command sequence is valid, one of ten command

routines is branched to based on the last digit of the command.

This approach to sequence detection is extremely flexible, easily changed, and is expandable. Special cases also can be handled easily outside the table-driven structure.

Audio Delay Line

The loudness and duration of the squelch tail in FM receivers varies, but some "chunk" exists in virtually all of them. Circuitry was built which eliminates the squelch tail and also allows total muting of touchtone command signals. By delaying the received audio on the way to the transmitter, squelch tails and touchtone can be headed off at the pass, before they go out the transmitter. The delay im-

73 Magazine • December, 1980 143

Table 4. Sequence detector foreground task. Stripped down skeleton of version used in repeater controller.

skeleton of	versi	on used in	repeater controller.	086F 218A08 0872 C34131	LXI H.ONETAB	FTABLE OF ROUTINE ADDRESSES FCOMPUTE ADDRESS AND GO THERE
	ISEQUENC	E DETECTOR FORE BUFFER AND BRAN TIVELY CLEARS P	GROUND ROUTINE, DECODES SEQUENCE CHES PROGRAM EXECUTION APPROPRIATELY. REVIOUS KEYS FROM BUFFER WHEN		EIGHT KEY COMMAND	
	SENDING	A SEQUENCE.		0875 =	EIGHTDEC EQU .	
	1	9); ***************		0875 E1	POP H	+(HL)->FIRST VALID CHAR
0800 =	FPTTSED	EQU \$		0876 111009	LXI D+LSEQ1	ITEST FOR FIRST POSSIBLE SEQUENCE
	+			0879 CD8808	CALL COMPSED	FDONT RETURN IF VALID
0800 210000		LXI H+0	FCLEAR INTERDIGIT TIMER	087C 111A09	LXI D+LSE02	FTRY SECOND, ETC
0803 222710		SHED LSENDET	TO INHIBIT TIMEOUT ROUTINE	087F CD8B08	CALL COMPSED	
0806 325010		CTA KBUP	HARD GLUDE RET BUFFER	0882 112407	CALL COMPRED	
0808 300410		LDA KRPOINT	ITS BUFFER EMPTYP (KEY BUFFER POINTER)	0000 CTAEOR	IMP EINSEG	INUST BE THUALTD
OB0E 47		HOV B+A	ISAVE	0000 034700	1	THEFT WE ANTHERE
080F 17		ORA A		0888 =	COMPSEQ EQU .	
0810 CA4F08		JZ FINSEQ	FIF YES QUIT	OBBB E5	PUSH H	ISAVE STRING LOCATION
0813 3A3D10		LDA PTTSEQ	PHONE OF RADIO COMMAND?			
0816 OF		RRC		0990 -	COMPSED1 EQU .	to defer former experience and
0817 OF		RRC		088C 1A	LDAX D	IGET EXPECTED VALUE
0818 DA2208		JC FPTTSEQ1	IDUDUE COMMAND	OBBD BE	CHP M	IDETURN TE DIEFERENT
OBID FAAO		ANT TISTER	ITOUCH TONE STILL PRESENT?	0886 025708	TNY H	LATHERWISE NEXT
081F C21808		JN7 8-4	FLOOP UNTIL END OF TONE	0892 13	INX D	FORMENTER REAL
	4	2015 (MARS)	A many sector and the contract	0893 1A	LDAX D	FLAST CHAR IN SEQUENCE?
0822 *	FPTTSE01	EQU \$		0894 B7	ORA A	
0822 215910		LXI H+KEYBUF		0895 F28C08	JP COMPSERI	
0825 58		MOV E+B		0898 EB	XCHG	IYES, NOW GET BRANCH TABLE ADDRESS
0B26 1600		MVI D+0		0899 1A	LDAX D	FA=LAST DIGIT OF SEQ
0828 19		DAD D	ICTIES TH TALE ANTAL TECHTNATOR	089A 23	INX H	
0829 3011		MDU Bal	IEND OF RUFFER	OBYR DL		
V020 40		THEY DIVE	TERO OF DUTTEN	OBYD 5A	HOU D.H	FORT ADDRESS FROM TABLE
4000 -	area			089E EB	XCHG	FINTO HL
0820 =	SEGI	EUU *	ISCAN DOWN FROM TOP TO .	089F D1	POP D	
0820 20		HOV ALL	F OR BOTTOM OF BUFFER	OBAO DI	POP D	FRESTORE STACK POINTER
082E FE58		CPI LOW KEYBUF-	1	OBA1 C34131	JMP JMPTAB	FCOMPUTE ROUTINE ADDRESS AND JUMP THERE
0830 CA3908		JZ SE02			the second se	
0833 7E		HOV A.H			FBRANCH TABLE BASED ON	NUMBER OF KEYS IN BUFFER
0834 FEOC		CPI KPOUND		0844 -	KULIAN EUU S	TAT ROUTINE: (POP RPJ-)FIRST CHAR
0836 C22C08		JNZ SERI		0844 42.08	DU ONEDEC	IT KEY, DECIDE
A070 -	*			OBAR AFOR	DH FINSEOP	12 KEYS. INVALTO
0839 23	SE04	TNX H	L(HL)-SETERST VALID CHAR	OBAA 4EOB	DW FINSERP	43 KEYS, INVALID
083A FEFF		CPI OFFH	HAS ONLY KEY A #7	OBAC 4E08	DW FINSERP	F4 KEYS, INVALID
083C C24008		JNZ SE03		08AE 310B	DW RBLOADP	15 KEYS, MAY BE REMOTE BASE FREQ LOAD
083F 2B		DEX H	POINT TO # IF YES	08B0 4E0B	DW FINSEOP	16, INVALID
	3			OBB2 4EOB	DW FINSEOP	17: INVALID
0840 =	SE03	EQU #		0884 7508	DW EIGHTDEC	18, DECIDE
0840 78		MOV A+B	TA-MUNDED OF VEVE	0000 4500	DU ETNEEDD	110- THUN TO
0841 95		SUB L	TOUER ERE DUERED OU	0000 4200	2 DW FINDENF	107 THANCID
0844 024508		INC EINSED	FUNELA FUN OVERFLUM		BRANCH TABLE FOR ONE	ENTRY BUFFER
0847 E5		PUSH H	JUNP TO BRANCH TABLE ENTRY LOCATION	OBBA =	ONETAB EDU \$	
0848 21A408		LXI H.KBLTAB	# BASED ON NUMBER OF KEYS	U088A 0000	DW KEYO	10
0848 C34131		SATANL AND	I(POP RP)->FIRST VALID CHAR, B=NBPOINT	0000 JEBON	DW KEYI	F1
	÷			UOBBE 0000	DW KEY2	12
084E =	FINSEOP	EGU \$		00000 00000	DW KET3	14
084E E1	-	POP H		100002 0000	DU PEVS	15
0045	FINDER			LIOBEA 0000	DH KEYA	10
OBAF CDALT	CTUDER.	CALL TTOPEN	IDPEN TOUCHTONE KEY BUFFER, FTC.	U08C8 0000	DW KEYZ	17
0852 AF		XRA A		U08CA 0000	DW KEYB	¥8
0853 323010		STA PTTSEO	ICLEAR PENDING BIT	U08CC 0000	DW KEY9	19
0856 37		STC	IRESYNC FOREGROUND TO BKGND	OBCE 4F08	DW FINSED	F(BLANK)
No Selector	1	Carlos Aparticipation		0000 00BDU	DW KEYSTAR	
0857 =	FINCOMPT	SEG EQU 1		U0802 0000	DW KEYPOUND	10

086D =

086D E1

DD45 75

ONEDEC EQU \$

POP H

I(HL)->FIRST VALID CHAR

INFT KEY UALLE

		FONE KEY COMMAND	
		DECIDE ON TYPE OF SEC	BUENCE BASED ON NUMBER OF CHARS
0860	HE7	RST 4	
0007	CØ3833	JMPFINSEQ	· OR RADIO
2869	COTOTA	VALIDSEDR EQU \$	1 OF BADIO
		in and the second second second	
8680	HE7	RST 4	
1892	CD4733	JMPFINSED	FIREN UN PRUNE
0862	DA6908	JC VALIDSEOR	TALE ON DURNE
0861	OF	RRC	
0680	OF	RRC	IPHONE OR RADIO COMMAND?
850	3A3D10	LDA PTTSEO	# WITH SPEECH (SAY *MARK*)
985A	217033	LXI H.VHARK	#ACKNOWLEDGE VALID SEQUENCE
185A		VALIDSEG EQU .	
857	EI	PDP H	
0.59	-	VAL TOSEOP FOU &	
0.00		ne i	
050	C0	POP N	
057	E1	POP H	

plemented was 50 ms, allowing the audio to be muted gently just prior to the squelch tail or touchtone reaching the transmitter.

Audio delays can be implemented with bucket-brigade devices—particularly short delays—but the approach used here for the relatively long delay was an Intel Codec chip plus digital shift registers. The Codec is a complete twoway data acquisition system, primarily intended for use in telephone equipment. It converts an incoming audio signal to a digital bit stream, and an incoming bit stream to an audio output signal, for a two-way pulse code modulation system. As used here, however, the digital bit stream is simply delayed through the shift registers and returned to the Codec. The audio output is therefore a delayed version of the audio input. Any delay length can be accomplished by selection of the size of the shift register, but five 1024-by-1 shift registers used here provide the desired 50-ms delay.

#1234567X BRANCH TABLE 0804 * T123TAB EQU \$ 08D4 4F08 DW FINSED \$0 08D6 4F08 DW FINSEQ 11 OBDB 4F0B DW FINSED 12 OBDA 4F08 DW FINSED \$3 **OBDC 7409** DW CWID 74 \$5 08DE 5C09 DW VOICEID **OBEO 1031** DW AUTOPATCHON 16 OBE2 4FOD DW RBRCVRON \$7 OBE4 7FOD DW RBRCVROFF 18 08E6 4F08 19 DW FINSED FLONG SEQUENCES - FIRST 7 OF 8 OF COMMAND CODE AND BRANCH TABLE ADDRESS . DB 1+2+3+4+5+6+7+0FFH 0910 0102030405LSED1: 0918 D408 DW T123TAB 091A 0706050403LSE02: DB 7+6+5+4+3+2+1+0FFH DW T765TAB U0922 0000 DB 2:3:4:5:6:7:8:0FFH 0924 0203040506LSE03: DW T234TAB U092E 0000

Audio Mixers

The various audio sources in the repeater are connected to the 220 transmitter and to the phone line under computer control. AUD1 and AUD2 output ports select one or more audio sources to be enabled into the two mixers. The audio switching is solid state and is quite simple considering that there is no detectable click or pop when switched and no detectable feedthrough in an open switch. 4053B singlepole, double-throw CMOS analog switches are used.

When the audio switch is open, the output is shunted to ground to eliminate any signal feedthrough. Good grounding and isolation of the CMOS switch power supply from the computer logic are important to keep out noise. The low-power Schottky control line buffers ensure clean logic levels to the CMOS, even in the presence of possible crosstalk on an interconnect cable.

Repeater Performance

No significant problems were encountered in bring-


Fig. 5. Audio mixer schematic. Repeater contains one eight-

enough to alter memory contents, but not always low enough to reset the CPU. The machine would occasionally clear itself and sometimes turn itself off (clear the TTOR Repeater Enabled bit). A new regulator solved the problem immediately; it was back to its old self and has performed flawlessly

AUDIO

The design and construction of the control system was a six-month part-time effort by two people. That's a lot of work, but from my viewpoint it was well worth

practical approach for a system of this complexity. The project was the most satisfying microcomputer project I've been involved in.

Sincerest thanks go to Bruce Martin WA6EQS who shared half the work of this project. Bruce is the father of the three-year old repeater and had many of the ideas for features and their implementation in the new control system.

Don Pezzolo K6OZH contributed to the project as a resource for bouncing ideas back and forth throughout the development. His continuing encouragement throughout the project was a big factor in its successful completion. Don also manages the repeater site and keeps the machine happy in its home.

Behind the repeater is the rf expert Werner Vavken WB6RAW, who, with WA6EQS and Ray Maxfield WA6VAB, is responsible for the rf portion of the machine. Bill Melody WA6YBD installed and maintains the antenna systems.

input and one four-input mixer.

ing up the control system. We were concerned about rf interference from the computer's high-speed digital logic, but since the 220 receiver is very well shielded, there were no problems. The IC-22S remote base required feedthrough capacitors to be placed on all control lines leaving the repeater cabinet to keep rf off certain two-meter frequencies. RFI is something to be concerned about, but it isn't necessarily a serious problem.

When the repeater went back on the hilltop with the new controller, it worked very well. Some minor software changes were made after eight weeks-the ROMs were simply changed.

There was one failure in the system, occurring after eleven weeks. The threeterminal regulator on the computer board became in-

termittent-probably a high resistance internal bond, definitely not thermal shutdown. The computer's supply voltage occasionally dropped low

it. Use of the computer in the controller allowed building in really useful features that would not have been possible without it. The software intensive approach was extremely educational and is the only

Parts and equipment were contributed by WA6EQS, W6LVY, W6YJL, WA6VAB, and WB6WDP.

	Standard			ASCII	
zero	forty	dollars	space	six	
one	fifty	cents	x-point	seven	K
two	sixty	pounds	quote	eight	L
three	seventy	ounces	number	nine	M
four	eighty	total	dollars	colon	N
five	ninety	please	percent	semicolon	0
six	hundred	feet	and	less than	P
seven	thousand	meters	apostrophe	equals	C
eight	plus	centimeters	left paren	greater than	R
nine	minus	volts	right paren	mark	S
ten	times	ohms	star	at	Т
eleven	over	amps	plus	A	U
twelve	equals	hertz	comma	В	V
thirteen	point	DC	minus	С	W
fourteen	overflow	AC	point	D	X
fifteen	clear	down	slash	E	Y
sixteen	percent	up	zero	F	Z
seventeen	and	go	one	G	lowercase
eighteen	seconds	stop	two	Н	tone
nineteen	degrees	tone (low)	three	1	upper case
twenty		tone (high)	four		up arrow
thirty		oh	five		control

Table 5. Telesensory Systems Mini Speech Synthesis PC boards vocabulary.

73 Magazine • December, 1980 145



Chart of UNITED STATES AMATEUR RADIO PRIVILEGES

by class of license, emission type, and frequency from 160 thru 2 meters, including provision for the new 30, 17, and 12 meter bands. This 22×28 in, twelve-color chart is the first of its kind to be both informative and decorative.

Be certain about WHO gets to do WHAT, and WHERE! Enhance your shack! Regular price \$3.00. SPECIAL INTRO-DUCTORY PRICE \$2.50. Includes postage and handling.

Larry Dennison—KB6KG 5002 Marion Avenue Torrance, California 90505

∽ 365 name	
address	and some services
city	N Trans- Is Summer
state	zip



GIGA Hz Preamp!!

Ultra-wideband 1 MHz

to 1000 MHz

The PM-5 preamp module covers the entire range from 1 MHz to 1 GHz (1000 MHz). Perfect for the new GHz counters and higher UHF bands, the tremen-



dous bandwidth of this preamp makes it so versatile you will soon depend on it whenever added gain is needed for RF measurements. Also for scopes, mW power meters, detectors, etc. Gain is 30 dB from 1 MHz to 500 MHz decreasing to 15 dB at 1 GHz. Maximum output is 1 volt p-p into 50 ohms. It is designed to work in either 50 or 75 ohm systems. The preamp is ready to use with the power adapter provided or any 7.5 to 15 volt DC supply at 50 mA. It can be "built-in" or mounted on your equipment if desired. Made with fine quality plated-thru boards, strip-line design using microwave transistors, BNC connectors.

Model PM-5 UHF Preamp (w/power adapter)......\$59.95

SENSITIZE YOUR COUNTER It's Ten Times Better with a COUNTER PREAMP

Wide band preamps with 20 to 30 dB gain. Improves performance of low price counters considerably. Probe reads oscillators without loading. Generators can be set to lower output avoiding frequent shifts. Also for scopes, meters, etc. Valuable troubleshooting aid. Powered by 3 pencells. BNC connectors. Hi Z input. Output is 200 to 400 mv rms into 50 ohms.

> Model VP-2, VHF Counter Preamp, 100 KHz to 200 MHz......\$39.95 Model UP-3: UHF Counter Preamp.

> 1 MHz to 500 MHz \$54.95

Order from PAGEL ELECTRONICS, 6742-C Tampa Ave., Reseda, CA 91335. Send check or MO for ppd. shipment via UPS when avail. Or call 213-342-2714 for COD. Foreign add 10% for airmail & handling. Calif. res. add 6% sales tax. One year warranty, money back guarantee.





RTTY Demodulators



RL PSK-500

\$229.00

700 Taylor Road

T.M. Call (614) 864-2464

Columbus, Ohio 43230

Order direct on Visa or MC

\$449.00 Ham net

....

FSK-1000 T.M.

FSK-500 T.M.

- Unparalleled selectivity achieved with sophisticated limiterless design utilizing ultrasharp active filters and decision level correction circuits
- The most flexible interface system available to computers and high voltage loops
- Built in 170 volt loop supply
- Selectable bandwidths of 55 and 100 Hz. (copies 110 Baud ASCII)
- Continuously tunable shift coverage
- Rugged construction commercial quality throughout
- Full complement of rear panel connectors for easy interface
- Keyboard activated switch for break in operation
- Individual tuning meters and LED's for quick, accurate tuning

This RTTY demodulator is designed for computer interface but is a fine stand alone unit:

- Easy computer interface with RS-232 or 5 volt logic signals
- Three shift coverage without straddle tuning
- Selectable bandwidths give you optimal Baudot or 110 Baud ASCII copy
- Input bandpass preselector using active filters
- High voltage loop keyer output
- Autostart built in
- Three shift AFSK keyer plus narrow shift CW ID
- Fully wired and tested: ready to copy!
- The FSK-500 is the best demodulator available for under \$500.00 (Except for our FSK-1000!)
- Positive tuning with meter and LED's



COMPARE the J.I.L. SX-100 Scanner to any other scanner available on the market today.

16 Channels 30-54 MHZ 140-180 MHZ 410-514 MHZ Digital Clock Date Display 110 V. AC or 12-16 V.DC 1 Year Warranty Seek Rate: Fast 10ch/sec Slow 5 ch/sec



BRIGHT GREEN 9 DIGIT FREQUENCY DISPLAY

Ext. Antenna Jack Ext. Speaker Jack Large Top Mounted Speaker Mobile Mounting Bracket Scan Rate: Fast 8 ch/sec Slow 4 ch/sec Scan delay time variable 0-4 sec.

Now you can see why it is our best selling scanner at only \$199.95 HURRY! Supply is limited.



Kenwood TR-7800

15 multi-function memory channels Extended frequency coverage 143.900-148.995 mhz Front panel keyboard and internal battery backup for all memories Priorty alert Auto scan and up/down manual scan Digital readout of both transmit and

receive frequency



Panasonic RF-4900 on sale this month. List \$549.95 Sale price this month \$369.95

Yaesu FT 207R

800 channels across 144-148 mhz Up/down scan feature 4 memories plus priority channel Keyboard entry of frequencies RF output 2.5w or 200 mw Call for Special Price Today!



Kenwood TS-520SE Cents-ability in a quality HF Transceiver Features: Coverage 160-10 meters CW wide-narrow switch RIT control Eight-pole crystal filter

HELLO WORLD!...You get it all with the ICOM 720!!!

All 9 bands and solid state Digitally synthesized tuning Two VFO's RF Speech Processor General Coverage Receiver 0.1 to 30 mhz AM, CW, SSB, and RTTY modes



We Export PRICES SUBJECT TO CHANGE AND AVAILABILITY Communications Center 1840 "O" STREET LINCOLN, NEBRASKA 68508 MasterCard

In Nebraska Call 402/476-7331

VISA°

Make a Microcomputerist Smile build him this EPROM eraser

Herbert M. Rosenthal AL7G 2941 Brandywine Anchorage AK 99502

a small fluorescent ballast to it, drilled a hole for the line cord, and included the usual 4-wire fluorescent starter switch. El Cheapo at its best, but we wondered about the safety of the device as we had heard of the potential injury to eyes and skin from exposure to ultraviolet (UV) rays. The tube used in the device was a Sylvania G8T5-remember this, as it's important. The next EPROM eraser we saw was built by someone with a much better concept. It had an all-metal case with a drawer that held

the EPROM in conductive foam. The drawer had to be in place before a switch was operated to complete the circuit. No UV leakage, no unintentional viewing of UV. This one also had a 60-minute timer built in. It appears that the bulb used by the latter device has a much stronger output, for the suggested erasing times were in the area of 20-30 minutes. The bulb has a house number and no doubt is made by or for that company and thus would not readily be available to the home constructor. The next chapter in this story comes from a 14-page General Electric manual, "Germicidal Lamps," TP-122, from their Large Lamp Department. I obtained a copy of this from the local industrial dealer for these lamps. An inquiry to them on the Sylvania number revealed that GE and others (Norelco) also make this lamp for air irradiation and other germicidal devices. We joked about the UV bulb in the electric razor at the airport (ten minutes, two bits) ... all along my friend could have erased

the EPROM while he was shaving! (Also used at the bowling alley to sterilize the rental shoes.)

But something good did come of this pursuit.

ne of my friends, who is deep into the homecomputer hobby, had a difficult time locating an eraser for his 2716 EPROM. He finally located one that was built into a plastic tapecartridge storage box and it worked fine. A quick look inside the box revealed that the manufacturer simply epoxied a pair of sockets to the edges of the box, bolted

Tube: G8T5 Nominal Watts: 8 Nominal length: 12" Tube diameter: 5/8" Approx. lamp Amps: 0.160 Approx. hours of life: 7500 Effective UV length: 81/2" UV output @ 2537 angstroms at 100 hours, Watts: 1.3 Average UV output through life: 0.98 Watts Max. intensity perpendicular to bare tube:

Watts/Square Foot at:

1 ft-0.14 8"-0.315 4"-0.86 2"-0.75

These are averages at 100 hours life; initial ratings about 20% higher, decreasing to an average of 0.75 ratings above, through life.

Fig. 1. Useful data if you "roll your own." Source: General Electric TP-122, Large Lamp Department.

73 Magazine · December, 1980 148

Whereas the electric dealer would order the bulbs only in quantities of 24 or more, we found that the local barber and beauty supply house had them in stock and would sell them at retail for about ten dollars. Click. A small 6- to 8-Watt fluorescent tube ballast and switch are another six or seven dollars; everyone has a microswitch in his junk box for the absolutely mandatory interlock switch. Click. LMB and others make metal boxes; plywood is cheap; the tube is nominally 12" long, and the EPROM should end up under the lamp, about 1" from it, centered along the bulb, and impressed in the black conductive foam it came in. Under the bulb is specified so that the UV rays and not the heat from the bulb work on the EPROM. The effective length of the UV radiation is 81/2", so cluster the EPROMs from the center of

the bulb.

Back to the GE manual. To allay any fears about the use of UV at all, I quote, "... Prolonged exposures or exposures to high intensities of ultraviolet energy can cause conjunctivitis (inflammation of the outer membrane of the eyes) and a reddening, or burns, of the skin. The glass used in conventional eyeglasses affords adequate protection. However, care should be taken that the UV energy does not enter the eyes from the side, nor is reflected into the eyes from the back side of the glass. To protect the face, clear plastic face shields are available ... General practice is to consider 0.5 microwatts per square centimeter of 2537-angstrom energy in a 7-hour period to be the maximum safe exposure without protection. An equivalent amount of exposure will be obtained from a bare 30-Watt lamp in one minute at 18 inches or in one hour at 12 feet."

Most of the rest of the manual describes the use of the family of germicidal lamps-from a 21/4" length to the largest, which is 64"; the lamps are used in everything from air cleaners to meat-cooling rooms to pharmaceutical manufacturing. But what should interest us the most is that the spectral response of these mercury vapor lamps peaks at 2537 angstroms, the exact wavelength called out for all EPROM erasures.

Fig. 1 is a compilation of data that will be of use to you if you choose to "roll your own." Fig. 2 shows typical wiring for a unit. Note in this latter drawing that the fluorescent switch, a 4-wire unit, performs the function of on-off and start, without a starter. If this



Fig. 2. Typical wiring.

switch is not available, one could use two separate ones, an SPST on-off switch and an SPST normally-open push-button for the momentary depress-to-start.

It probably wouldn't hurt to fabricate a reflector from soft cardboard and then cover it with shiny aluminum cooking foil. Place this a couple inches above the lamp; it can only increase the UV intensity to the EPROM. Provide a small hole (¼" will do) covered with milky white plastic to act as a pilot lamp. Try a one-hour ex-

posure as a beginning point. In summary, you can have an ultra EPROM eraser, violet, for about \$20, some ingenuity, and a lot of fun ... but only if you promise to observe the strict cautions from the GE manual, which suggests that all products using germicidal lamps bear a prominent, highly legible CAUTION warning that no one should look directly at a lighted lamp or work near it without adequate eye (and skin) protection. Don't forget that interlock switch, be it on a tray or door!

Andrew An	
lincoast	
Lincous	
kicoad	6/1/0
kitobaud	-
MICROCOMPUTING	3
////	UIII.
//// Mish	11111
////	1111
cent survey showed that 20% of the 73 subscr	ibers also read
and MICROCOMPUTING magazine and en arn and keep up with the rapidly developing wo	joy it. This is the best way orld of microcomputers.
e's nothing to be afraid of, you just have to rea	d an interesting
azine and you'll learn. Try a subscription to Kilo see for yourself.	baud MICKCOMPUTING
w subscription	12 issues for \$25.00
yment enclosed \$	24 issues for \$38.00
SA MC AE Bill me	□ 36 issues for \$53.00
d#In	terbank #
nature	Exp. date
ne	
ress	and the second
State	Zip
-for even faster ordering service call toll f	ree (800) 258-5473
a support of the second s	CONTRACTOR STREET
anadian: \$27, one year only, U.S. funds. Other	r foreign: 30DB6

PROFESSIONAL HEADPHONES & HEADSETS BOOM MIC HEADSETS

For the ultimate in communications convenience and efficiency select a boom mic headset. Long-time favorites of professional communications, boom mic headsets allow more personal mobility while always keeping the mic properly positioned for fast, precise voice transmission. Boom microphones are completely adjustable to allow perfect positioning. And, boom headsets leave both hands free to perform other tasks.

All modes are supplied with "close talking" microphones to limit ambient noise pick-up and provide superior intelligibility. Each model as a convenient, inline push-to-talk switch, which can be wired for either push-to-talk relay control or mic circuit interrupt for voice operated transmitters. The switch may be used as a momentary push-button or it can be locked in the down position. All models have tough, flexible, 8 foot cords which are stripped and tinned, unterminated.







CM-1320











HMC-2



Ham Clubs, field day contest operation. No more jury rigs for multiple headphones. Six ¼" phone jacks with individual volume controls, 4 foot cord with ¼" phone plug. \$14.30

CM-610 CM-1210

CM-1320-S

PC-100

HTC-2

HTC-91

MODEL	C-610	SWL-610	C-1210	C-1320	CM-610	CM-1210	CM-1320	CM-1320S	PC-100	HTC-2	HMC-2	HFC-91
Headphone Sensitivity Ref 0002 Dynes/cm ² @ 1mW input. 1kHz	103dB SPL *5dB	103dB SPL ±5dB	103dB SPL ±3dB	105dB SPL ±5dB	103dB SPL ±5dB	103dB SPL ±3dB	105dB SPL ±5dB	105dB SPL ±dB			4	
Headphone Impedance	3.2 20 ohms	2000 ohms	3.2 20 ohms	3.2 20 ohms	3.2 20 ohms	3.2 20 ohms	3.2 20 ohms	3.2 20 ohms	8 200 ohms	3.2 20 ohms	3.2 20 ohms	3.2 20 ohms
Microphone Frequency Response					50 8000 Hz	50 8000 Hz	50 8000 Hz	50 8000 Hz	50 1200 Hz	100 3000 Hz	100 3000 Hz	100 3000 Hz
Microphone Impedance				1	High	High	High	High	Low	Low	Low	Low
Microphone Sensitivity Below 1 volt/microbau					51 dB ±5 dB	51 dB ±5 d8	51 dB ±5 dB	51 dB ±5 dB	Taxa a	1		wome
					20	869 75	20.309		010 DE	624 50	61F F0	60.00

00

25.

ed

18

18



Headphone Jack Box

3



Case 3 (H) + 4% (W) + 5% (O) Shoping Weight 5 lbs ъe



Case 3'(H) + 4' (W) + 5 - 101 Shipping Weight 3 lbs

COMPLETE 25G TOWER PACKAGES

50' Guyed Tower: Includes top section, 4 regular sections, base plate, rotor plate, 50' guy wire, 2 guy assemblies with torque bars, 3 concrete guy anchors and other miscellaneous hardware.

> **REGULAR PRICE \$698.00** SALE PRICE 499.00 SAVE \$199.00

50' Bracketed Tower: Includes top section, 4 regular sections, base plate, rotor plate and universal house bracket.

> **REGULAR PRICE \$430.00** SALE PRICE 299.00 SAVE \$131.00

tts, 02155 == TEL. 1-617-391-3200

Drake L-7

2kW Linear Amplifier

primary line voltage.

10m-160m coverage. 2kW PEP, 1kW CW, RTTY, SSTV operation - all modes, full

rated input, continuous duty cycle. Accurate

built-in rf wattmeter, with forward/reverse

readings, is switch selected. By-pass switch-

ing for straight through, low power opera-

tion without having to turn off amplifier.

Bandpass tuned input circuitry for low distortion and 50 Ohm input impedance. Operates from 120/240 Vac, 50/60 Hz



Drake "Dry" Dummy Loads-no oil required



Model 1951 Drake DL-1000

MODEL

- Seat for deak or brench cost.
 Sign 14' x 3.6'' (30.6 x 9.1 cmil Wt. 2 lbs 1910 g)

\$26.95

 Builton PL-200 issue tomostos far direct convector to real of transmiser or transmister - no partper con-VERM or T.T.T. man, IP-30 MHz T.S. man. 20-100

· Meal as bandh twill device for amateur or torms M and whit gear
 Small size fits conversently in any field service tool box: 6.7" x 2.68" (17.0 x 5.3 cm), WL 13.02 (330 pl.

DRAKE PRICE LIST

NUMBER	MODEL	DESCRIPTION	PRICE
COMMUNI	CATIONS RE	CEIVERS AND ACCESSORIES	
1242	DSR-2	VLF-HF Digital Synthesized SSB, AM, CW,	
		RTTY, ISB Laboratory Communications	\$3400.00
1240	87-/D8-7	0-30 MHz General Coverage Digital	33400.00
1240	117-7611-7	Synthesized Receiver	1449.00
1548	R-7/TR-7	Cable Interface Kit	24.50
1532	NB-7A	Noise Blanker for R-7	90.00
7021	SL-300	300 Hz CW Filter for 7-line	55.00
7022	SL-500	500 Hz CW Filter for 7-line	55.00
7023	SL-1800	1800 Hz AM Filter for R-7	55.00
7020	SL_6000	6000 Hz AM Filter for 7-line	55.00
1531	MS-7	Speaker for 7-line	39.00
1217	4-NB	Noise Blanker for R-4C	74.00
7011	FL250	250 Hz CW Filter for R-4C	55.00
7013	FL-500	500 Hz CW Filter for R-4C	55.00
7015	FL-1500	1500 Hz RTTY Filter for R-4C	55.00
7017	FL-4000	4000 Hz AM Filter for R-4C	55.00
7019	FL-6000	6000 Hz AM Filter for R-4C	55.00
VHF-FM T	RANSCEIVE	RS AND ACCESSORIES	
1330	UMK-3	Remote Trunk Kit for UV-3	69.95
1339		Extra Control Head for UV-3	90.00
1525	1525EM	Encoder Microphone for UV-3	49.95
AMPLIFIE	HS	160 15m Amelifier Deves County	1000.00
1528	L-/	160-15m Amplifier, Power Supply	1090.00
ANTENNA	TUNERS AN	D ACCESSORIES	1030.00
1538	MN-7	250W 160-10m Tuner	175.00
1539	MN-2700	2KW, 160-10m Tuner	299.00
1510	B-1000	4:1 Balun for MN-7/MN-2700	26.95
1533	CS-7	Remote Controlled Antenna Switch	169.00
1514	WH-7	1.8-54 MHz 20/200/2000 Wattmeter	99.00
1550	DL-300	300W Dummy Load	26.95
1551	DL-1000	1000W Dummy Load	53.00
1529	FA-/	Fan for DL-1000/TR-7/PS-7	29.00
1336	TR-7/DR-7	Digital HF transceiver 160-10m	
		(receives 1.5-30MHz)	\$1549.00
1537	NB-7	Noise Blanker for TR-7	90.00
7021	SL-300	300 Hz CW Filter for 7-line	55.00
7022	SL-500	500 Hz CW Filter for 7-line	55.00
7023	SL-1800	1800 Hz RTTY Filter for 7-line	55.00
7024	SL-6000	6000 Hz AM Filter for 7-line	55.00
1536	AUX-7	Auxiliary Hange Program Board for TH-7	45.00
1546	PPM 7	(for out of band coverage) Ranges Receive Medules	45.00
1547	RTM-7	Range Transcolue Modules	8.00
1529	FA-7	Fan for TR-7/PS-7/D1-1000	20.00
1338	RV-7	Remote VFO for TR-7	195.00
1531	MS-7	Speaker for 7-line	39.00
1335	MMK-7	Mobile Mount for TR-7	49.95
7073	7073	Dynamic Mobile mic. w/Plug TR-7	24.50
7077	7077	Dynamic Desk mic. w/Plug TR-7	49.00
7037	7037	TR-7 Service Kit	50.00
POWER SU	PPLIES AND	ACCESSORIES	
1501	AC-4	Power Supply for 4-line, 110/220V	\$ 150.00
1505	DC-4	12 VDC Power Supply for 4-line	195.00
1504	PS-3	Power Supply for UV-3, 110/220V	89.95
1502	PS-7	Power Supply for TR-7, 110/220V	299.00
1529	FA-7	Fan for PS-7/TR-7/DL-1000	29.00
LOW PASS	AND HIGH P	ASS IVI FILTERS	
1608	TV-22001 0	1000W Low Pass Filter	14.60
1603	TV-300HP	High Pass Filter for 300 Ohm Twin Load	26.60
1610	TV-75HP	High Pass Filter for 75 Ohm	13.25
			13.20
ACCESSOR	Y CRYSTALS		
		Crystals for 2C/H4B/H4C/SW4A/	0.50
		Crystals for fixed frequency operation	9.00
		of tunable units/2NT	10.50
		Crystals for TR22/TR22C	9.50
		Crystals for TR72/TR33C	9.50

RICE **TR7/DR7 TRANSCEIVER** 00.00 49.00 24.50 90.00 55.00 55.00 55.00

In the past few years, several amateur transceivers have appeared on the market boasting features and techniques considered to be "state-ofthe-art** in regards to communications technology, More often than not, these features and techniques have been incorporated without the initial expense of the development time necessary to assure that the resulting equipment represented an advancement in communications technology with respect to both performance and operator convenience,

The Drake TR7 Transceiver represents a unique blend of proven state-of-the-art techniques cul nating in the first truly state-of-the-art transceiver presently available.



Drake UV-3 **UHF-VHF FM Transceiver**

- Fully synthesized on each band, 5 kHz steps, digital readout.
- FM coverage on complete 144, 220 and 440 Amateur bands, depending on model purchased. Completely band-switched from front panel.
- Four extra diode programmable fixed channels, with offsets, available for each band, in addition to the synthesizer.
- Diode programmable non-standard offsets available for each band.
- Separate SO-239 Antenna Connector for each band.
- Scan a programmed fixed channel from any synthesizer frequency. Scan any synthesizer frequency from a programmed fixed channel. Scan a specific programmed fixed channel from another programmed fixed channel.



A product of the Drake "anything worth doing is worth doing right" philosophy, the TR7's many new techniques and operational features complement each other producing performance and convenience which will remain unexcelled for many years to come.

UV-3 OPTIONAL ACCESSORIES:

- Removable control head will operate. radio in trunk compartment from driver's. seat.
- PS-3 companion ac power supply.
- Drake 1525EM Encoding Mike.

High Pass Filters for TV Sets

provide more than 40 dB attenuation at 52 MHz and lower.



DRAKE TV-300-HP Model No. 1603 For 300 Ohm twin lead. New terminals for easy installation.



DRAKE TV-75-HP Model No. 1610 For 75 Ohm tv coaxial cable; tv type "F" connectors installed.

Low Pass Filters for Transmitters

have four pi sections for sharp cut off above the hf amateur bands and to attenuate transmitter harmonics falling in any ty channel and FM band, 52 Ohm, SO-239 connectors built in.

DRAKE TV-3300-LP Model No. 1608

1000W max, below 30 MHz, Attenuation better than 80 dB above 41 MHz. Helps tv i-f interference, as well as harmonic interference.

DRAKE TV-42-LP Model No. 1605 A four section filter designed with 43.2 MHz cut-off and extremely high attenuation in all tv channels for transmitters operating at 30 MHz and lower. Rated 100W input.

P.O. Box 27, Medford, Massachusetts, 02155 == TEL. 1-617-391-3200



handles full legal power and then some, and works with coax, single wire and balanced lines. And it lets you tune up without going on the air.

All tuners lose some rf power, mostly in the inductance coil and the balun core. To avoid this we switched from No. 12 wire for the main inductor to 14" copper tubing. It can carry ten times the rf current. And we've moved the balun from the output, where it almost never sees its design impedance, to the input where it always does. Thus more power to your antenna.

The biggest problem with tuners is getting them tuned up. With three knobs to tune on your tranceiver and three on the tuner and ten seconds to do it (see the warning in your transceiver manual) that's 1% seconds per knob. We have a better way; a built-in 50 Ohm noise bridge that lets you set the tuner controls without transmitting. And a switch that lets you tune your transmitter into a dummy load. So you can do the



... the new S-5

- * The only synthesized hand-held offering 5 watts output. (Switchable for 1 or 5 watt operation)
- * The same dependability as the time proven S-1. Circuitry that has been proven in more than a million hours of operation.
- Heavy duty battery pack.
- * Telescoping whip antenna.
- Ni-cad battery pack, charger.
- External microphone capability.

the Tempo S-2

\$

\$

\$

Tempo is first again. This time with a superior quality synthesized 220 MHz handheld transceiver. With an S-2 in your car or pocket you can use 220 MHz repeaters throughout the U.S. It offers all the advanced engineering, premium quality compo-



PRICE LIST

Tempo S-5	\$299.00
Tempo S-5 with touch tone pad	339.00
12 Button touch tone pad	
(not installed)	39.00
16 Button touch tone pad	
(not installed)	48.00
Tone burst generator	29.95
CTCSS sub-audible tone control	29.95
Rubber flex antenna	8.00
Leather holster	16.00
Cigarette lighter plug mobile	
charging unit	6.00
Matching 30 watt output 13.8 VDC	
power amplifier (S30)	89.00
Matching 80 watt output	
power amplifier (S80)	149.00
Tempo S-2	349.00
Tempo S-2 with touch tone pad	399.00
Tempo S-1	259.00
Tempo S-1 with touch tone pad	289.00

돠

3

2

If you're not on 220 this is the perfect way to get started. With the addition of the S-25 (25W output) or S-75 (75W output) Tempo solid state amplifier it bcomes a powerful mobile or base station. If you have a 220 MHz rig, the S-2 will add tremendous versatility. Its low price includes an external microphone capability, heavy duty ni-cad battery pack, charger, and telescoping whip antenna.

Tempo S-1

2

- The first and most thoroughly field tested hand-held synthesized radio available. 800 channels in the palm of your hand.
- · Simple to operate. (You don't need a degree in computer programming).



TUFTS Electronic Department Store TUFTS Xcelite XST-5 — Super-Tru Tip (phillips type) Screwdriver Set Tools, Parts, Needle-Nose Pliers Accessories \$8.37 Contains 5 pieces - all Phillips *56CG **Diagonal Pliers** \$13.97 6" size Long slim NANTTALECT SHARE DEPTIMI entry inacciesible 10 regular long nose plan 1540G \$6.60 Midget 4" size for close \$8.27 quarter work. SDS-44 — Square Blade Screwdriver Set *57CG *55CG \$14.76 Contains 5 Square Blade Screwdrivers for stol-ted screws. Catalog Not 5:141, 5:3164, 5:144 STUT BUT with time 5" Plier for most cutting sentanted sews and cost \$7.13 S-5166 S-388 needs spring for tim gripping. and looping of wire Xcelife a exclusive thin-pattern design permits Adjustable Long-Nose Pliers access where regular adjustables will not fit. *64CG Augged construction, chrome-plated, polished heads, with quick one-hand adjustment and Wrenches 4º long fortast Cushion-GHp (CG) clean easy tip \$6.85 "44CG - 4" length No" opening \$6.38 cutting of time \$8.87 46CG - 6" length 1's" opening worms (r) closer 48CG - 8" length " a opening \$6.45 quarters *41CG \$7.28 Midget 4" pliers. serrated jaws without side cutters. **Wire Strippers** *66CG & Cutters 1-\$7.92 e all purpose diagonal plent. \$2.63 *100-X \$7.48 With Cushion Grip Handles '51CG Has adjustable screw stop for different wire sizes and cushion grips. Cuts and ships both 6" long-riose phers with soud and stranded wire cleanly neatly Hard-SHOP CARTER enert with ground blades *101-S \$3.32 \$6.37 Specifications same as 100, except with \$7.33 *67CG *52CG spring-equipped self-opening handles 7" diagonal pliers for 6" long nose pliers neavy duty cutting without sude outters ·103-S \$4.12 Has unique cam stop adjustment for different wire sizes. Cam adjustment stays put, won't move, even with screw loose. Fine for industrial **Quality Coaxial Cable** 104CG Wire Stripper and Cutter

for All Applications

• LOW LOSS CABLE • NON TARNISHING CONNECTORS FACTORY ASSEMBLED, TESTED FOR 100% RELIABILITY

RG58/UType

NUMBER	DESCRIPTION	APPLICATIONS			
\$3.20	\$3.20 18 * 18" length with UHF CB plugs on both ends Used as patch cords for mobile & base station				
581-583 * \$3.70	3' length with UHF CB.plugs on both ends	SWR & power meters, an- tenna switches, and SWR matchers	RG 58/U Type		
581-585i * \$4.10	5' length with UHF CB plug & spade lugs	Used to connect mobile	RG8/U		
581-5812L* \$4.10	12' length with UHF CB plug & spade lugs	CB sets to trunk mirror gutter or bumper mount antennas using spade lug terminations to the an-	PART	DESC	
581-5820L* \$4,99	20' length with UHF CB plug & spade lugs.	tenna	581-83 *	3' len UHF 1	
581-5812 * \$4,99	12' length with UHF CB plugs on both ends	Used to connect mobile CB sets to trunk mirror	\$4.10	on bo	
\$5.49 *	20' length with UHF CB plugs on both ends	antennas requiring a UHF CB plug termination to the antenna	581-820 \$8.50	20' ler UHF (on bo	
\$81-5850-420 \$7.25	50' length with UHF CB plugs on both ends		\$81-850-420 \$14.99	50' let UHF (on bo	
\$9,29	75' length with UHF CB plugs on both ends	Used where smaller diameter cable is requir-, ed and signal loss is not critical	581-875-420 \$22.50	75' ler UHF (on bo	
\$10.99	100' length with UHF CB plugs on both ends		\$26.50	100° H UHF (on bo	



B

RG 8/U Low Loss Type

Low Loss Type

				No. 652	5 feet	\$ 7.05	
ION	APPLICATIONS	-		No. 653	10 feet	\$ 8.34	
with plugs nds	Used as patch cords for mobile and base station SWR and power meters antenna switches & SWR matchers	(n -	5-	>		
	10. 300 T 201 1030	50 ohm BN	IC Plug to	UHF Plug			
with plugs nds	or base stations with an- tennas requiring a UHF CB plug termination at the antenna	No. 657 No. 658 No. 656	1 foot 3 feet 5 feet	\$ 7.20 \$ 7.72 \$ 8.24			
with plugs nds	Used to connect base			()	
with lugs nds	antennas Where loss is critical these cables will out perform RG 58/U			50 ohm B	NC Plug to	BNC Plug	1
with.	cables of the same			No. 668	3 feet	\$ 8.91	
nds				No. 662 No. 666	5 feet 10 feet	\$ 9,43 \$10,73	
	1				10-030		

\$10.08

Features sciesor action-up front wine culting and wire stripping, bolt cutters, cushion grips, plier nose, hardened pixot joint bushing and crimp stations.

Cutter, stripper and crimpler for all types and

LAB QUALITY CABLES

BNC Test Voltage

1500 vac; Frequency: 0-4 GHZ; Impedance: 50 Ohms nominal; Cable Retention Force: 60 lbs. minimum (RG-58C/U)

UHF Test Voltage

1500 vac; Frequency: 0-500 MHz; Impedance: Non Constant; Cable Retention Force: 60 lbs. minimum (RG-58C/U)



50 ohm UHF Plug to UHF Plug

No. 651	3 feet	\$ 6.52
No. 652	5 feet	\$ 7.05
No. 653	10 feet	\$ 8.34



Panasonic



\$179.00 Panasonic RF-2200 International Band

Eight-band worldwide shortwave radio. AC or battery power. Includes AM, FM and six shortwave bands, Combination 2-stage selectivity and AFC switch. RF gain control, Separate bass, treble, and volume controls, FM/SW telescoping antennas. Four "D" batteries, AC power cord, and earphone included.



\$239.00 Command Series RF-2600

Six-band portable shortwave radio with all-band, five-digit fluorescent frequency display. SW frequencies from 3.9-28 MHz, FM/AM radio. Battery/signal strength meter. AFC on FM. RF gain control. 4" dynamic speaker. Comes with AC power cord, shoulder belt and earphone. Operates on 6 "D" batteries (not included).



\$249.00

Command Series RF-2900

Portable 5-band shortwave radio. Five-digit fluorescent display. SW from 3.2 to 30 MHz, RF gain control. BFO pitch control. Comes with AC power cord, shoulder belt, dial hood and earphone. Operates on 6 "D" batteries (not included)



\$399.00

Command Series RF-4900

Ten-band communications receiver with 5-digit, all-band fluorescent display. SW from 1.6 to 30 MHz. FM and AM frequencies. FET RF amplifier. BFO pitch control. RF gain control. Comes with earphone, AC power cord and headphone converter. Operates on 8 "D" batteries (not included).



Drake R-7 / DR-7

Synthesized, General Coverage Receiver

- Fully synthesized with a permeability tuned oscillator (PTO) for smooth, continuous tuning.
- Covers complete range 0-30 MHz. Both digital and analog readout.
- Special low distortion "synchro-phase" AM detector provides superior inter-



See back cover for specials!

panel. Provides simultaneous dual receive with the TR-7, making possible the reception of two different frequencies

Built-in power supply operates from

100, 120, 200, 140 Vac, 50/60 Hz, or

ent Store



NEW! INCLUDES 24-hour UTC Clock 110 and 300 baud ASCII, & tuning eye!

Field Day®

If someone tells you they offer the same features we do, check them out with the list below.

- Morse copying ability
- 3 to 80 WPM Morse range
- Computer programs for improving sloppy Morse
- Radioteletype copying ability - 60, 67.75 and 100 WPM Baudot
- ASCII radioteletype ability - 110 and 300 WPM baud
- Copies any shift of RTTY
- 24-hour UTC clock available in any mode
- Entire unit contained in one package
- Automatic code-speed tracking
- Full 10-character, large-size display

Displays code speed

\$399.00

- Tuning eye for faster tuning
- Full year limited warranty
- Internal speaker
- Requires no TV set for use
- Advanced demodulator circuits
- Internal 200 Hz bandwidth filter
- All leters, numbers and punctuation plus special Morse characters and 5 special RTTY characters

- national shortwave broadcast reception.
- Tunable IF notch filter effectively reduces heterodyne interference from nearby stations.
- Multi-function antenna selector/50 Ohm splitter is switch-selected from the front

YAESU



- \$599.00 FRG-7000 **Digital Display Communications Receiver** with CPU Digital Clock and Timer
- 0.25 Thru 29.9 MHz Coverage with 1 kHz Readout

Computer technology and convenience features are brought together in the FRG-7000, a digital-display general coverage receiver for the discriminating SWL. The digital clock and timer, controlled by a CPU (Central Processing Unit) chip, will read out both local and GMT time, and will control peripheral station equipment such as a tape recorder.



General Coverage Receiver

at the same time.

nominal 13,8 Vdc.

 0.5-29.9 MHz Coverage with 10 kHz. Readout

The FRG-7 is a precision-built all-purpose communications receiver, featuring all solid state construction for long life and high performance. Utilizing the Wadley Loop drift cancellation system, in conjunction with a triple conversion superheterodyne circuit, the FRG-7 boasts high sensitivity along with excellent stability



\$499.00

Kenwood R-1000

The R-1000 is a highly advanced communications receiver. Up-conversion, PLL circuitry and other new technology provide optimum sensitivity, selectivity, and stability from 200 kHz to 30 MHz. Featuring easy-to-operate single-knob tuning and digital frequency display, it's perfect for listening to shortwave, medium-wave, and long-wave bands. Even SSB signals are received perfectly, Included is a quartz digital clock and timer.

R-1000 FEATURES:

NWOOD

pacesetter in amateur radio

- Continuous frequency coverage from 200 kHz to 30 MHz.
- 30 bands, each 1 MHz wide.
- Five-digit frequency display and illuminated analog dial.
- Quartz digital clock and ON/OFF timer.
- Multi-modes AM (wide and narrow). SSB (USB and LSB), and CW.
- Three IF filters 2.7 kHz for SSB and CW, 6.0 kHz for AM narrow, and 12 kHz for AM wide.
- Effective noise blanker, built-in speaker, three antenna terminals, rf step attenuator, tone control, recording terminal.
- Remote terminal, for access to timer relay ON/OFF circuit and muting circuit.
- SSB sensitivity of 0.5 µV from 2 to 30 MHz.
- More than 60 dB IF image ratio.
- More than 70 dB IF rejection.





Aircraft, Marine, Public Service. The 220 adds features and advanced sophistication.

- Aircraft and Marine press button to search entire Aircraft Band, another for Marine
- 7 Bands Low, High, UHF, UHF-T, 2m amateur and 75 CM Ham - plus the Aircraft Band
- 20 Channels scan up to 20 frequencies or either of two banks of 10 channels each
- Automatic Search Selective Scan Delay - Automatic Lock-Out - Patented Track Tuning - Manual Scan Control - Single Antenna
- Priority automatically samples designated channel every two seconds
- AC/DC operation



BEARCAT 300 Service Search

Over 2100 pre-programmed frequencies.

- 11 Service Search categories arrange stored frequencies into "interest" groups - Police, Fire, Marine, HAM, Emergency, Telephone, Government, Forestry, Industrial, Transportation and Aircraft.
- 50 Channels/5 bands
- 7 Bands (Low & High VHF, UHF, and UHF-T, AM Aircraft, 2m & 75 CM Amateur)
- Non-volatile memory, AC/DC
- Automatic Search with Hold & Resume functions
- Patented Selective Scan Delay
- Vacuum Fluorescent Decimal-Display with Dimmer Control
- Speed Control

Only \$179.00

- Quartz Clock
- Patented Track Tuning
- Direct Channel Access
- Automatic Squelch



\$199.95



capabilities than other Hand-Helds. 4 Bands (Low, High, UHF and UHF-T) 6 Channels – more monitoring capacity "Rubber Ducky" Antenna

Belt Clip frees hands while monitoring

More bands, more channels - more scanning

- 8 channels per second scan speed
- Automatic or manual scanning
- Individual channel lock-outs

BEARCAT 210

- Portable weighs only 12 ounces
- Battery operated (6 Vdc)

The one that pioneered synthesized scanning - and unlocks new channels of communication.

- No crystals to buy full 6-band coverage.
- Keyboard programming makes frequency selection as easy as punching a pushbutton telephone.
- Decimal display and exclusive rolling zeros to show what's being programmed and monitored.
- Automatic search for finding new frequencies.



CB Antennas

AV-101 ASTRO PLANE" - Patented performance. Best value available today in an omni directional base antenna. \$47.95

ectroni

Cobra 29GTL Recognized Industry Standard Cobra's most popular CB mobile-the "Truckers' choice" • Delta tune • "DynaMike" • Antenna warning indicator • Illuminated S/RF/SWR meter . Switchable automatic

PUNCHES THROUGH LOUD and CLEAR

noise limiting and noise blanking

obra

avanti antennas

AV-122



distance with 12 full watts of power, plus guleter communications and 120 channels (80 on side Only



Cobra 142GTL CB Base Station The COBRA 142GTL SSB/AM Base Station is for CB-ets who want extra distance, full 12 watts of power, quieter communications due to elimination of AM "clutter," and 120 channels - 80 of them on sideband



AV-122 PDL II" - Patented design dual polarity antenna with orbital gamma match. Light weight and long range communication in a beam antenna. Five elements on each polarity. \$199.95

AV-140 MOONRAKER* - America's most popular and most imitated CB antenna design in a dual polarity beam. Includes cast aluminum hubs, stainless steel tip wires and many other Avanti quality features. \$515.95

AV-146 MOONRAKER[®] - King of CB antennas. All the guality features of Avanti Moonraker 4 plus the exclusive 4-way boom support that protects against structural failures common to com-Perter's super big beam antennas. \$99.95

AV-150 ASTRO BEAM" - Big power in a small package. Unprecedented 40 dB front-to-back ratio

AV-160 RAMROD" - The versatile all purpose antenna . CB . low or high band Business radio . short wave listening . monitor . TV-FM . civil defense • amateur • aircraft • marine • experimenting . a no nonsense full 1/2 wave antenna that is fully adjustable from 25 to 175 MHz (adjustment chart provided). \$29.95

AV-170 SIGMA II" - Second generation 5/8 wave with incredibly low S.W.R., 5.14 dBl gain. New static arrestor system. Easy installation. New H.D. mounting tube. Aircraft quality aluminum. New low price. \$89.95

AV-190 SATURN" - New scientific breakthrough. Now vertical and horizontal polarity in an omni directional antenna. Strong, long distance power in a unique dual polarity design. Unsurpassed omni power gain and SWR characteristics. Static arrestor system for clearest possible communications in all weather conditions. Easy assembly aero space light, high strength construction tested to withstand years of wind and weather. Switchbox included. \$199.95

Tri-Band Monitor Antenna

AV-801 ASTRO SCAN" - A patented Tri-band base monitor design with no compromises. Unmatched gain over the whole tri-band range from 25 MHz to 512 MHz, including the new "T" band. Aerospace light construction of aircraft quality aluminum and stainless steel is well balanced on the mast to withstand years of severe wind and weather.

\$34.95



OMNI-Series C.

OMNI moves boldly forward to meet the new decade. With new features, new conveniences, new techniques, and new band coverage. Full amatuer band coverage from 160 through 10 meters. With its new hf capability, OMNI-C covers all six of the present hf bands and all three of the new hf bands. Crystals are supplied for seven bands (crystals for 18 and 24.5 MHz bands will be available when the bands are ready). New built-in noise blanker is standard equipment in the OMNI-C. A new design with a 2-pole monolithic crystal filter to handle the big signals with ease, to make impossible locations usable. New "Hang" AGC for smoother operation, less abrupt action.



Model 255 - Deluxe Power Supply/ Speaker Combination,

Includes the electronics of Model 280 power supply plus a built-in 3" x 5" front facing speaker.





DELTA - Transceiver

DELTA is the name of a great new TEN-TEC transceiver. All 9 HF bands. First new rig since WARC, 160m through 10, including the new 10, 18 and 24.5 MHz bands! With everything incorporated except the plug-in crystals for 18 and 24.5 MHz segments (available when bands open to amateurs). No receiver front end or final amplifier adjustments. From the pioneer in broadband design. 200 Watts input on all bands including 10m (with 50 ohm load). High SWR does not automatically limit output to a few watts. With a proven, conservatively rated final amplifier whose solid-state output devices are fully warranted the first year and pro-rata warranted for an additional five years. Has all the options you could want. Model 289 Noise Blanker, Model 282 200 Hz CW Filter, Model 285 500 Hz CW Filter, Model 283 Remove VFO. Model 287 Mobile Mount, Model 280 18A Power Supply with over-current and overvoltage protection. Other matching accessories include Model 645 Dual Paddle Keyer, Model 670 Single Paddle Keyer, Model 247 Antenna Tuner, Model 234/214 Speech Processor and Mircophone, Models 215P and 215PC Ceramic Microphones, Model 252MO Power Supply.



MODEL 280 - Dual Primary Power Supply Ideal for powering the DELTA or OMNI transceivers on either 115 or 230 VAC, 50-60 Hz. Easy to chagne for either primary voltage. Regulated output, over-voltage and over-current protected, and can be switched from transceiver or power supply Styled to match DELTA and OMNI colors.



HERCULES 444 All Solid-State KW Linear Amplifier

No tubes, no tuning, full coverage: 160-15m, bands switched from OMNI panel or linear, instant break-in. 1000 Watts input, all bands, 600 Watts output, typical. Forced air cooling, automatic line voltage correction, automatic exciter by-pass, blackout meter panel, 6 status monitors with LEDs. Two meters - collecter current and voltage - forward and reverse power. Negative ALC voltage, adjustable. Built-in control power supply. Tape wound transformer and choke in, separate power supply, 117/ 230 VAC. Styles to match OMNI.

MODEL 247 - Antenna Tuner.

Matches 50 ohm unbalanced output of OMNI to variety of balanced or unbalanced antenna impedances, Universal Transmatch circuit. 46-tap inductor allows vernier adjustment, 200 watts intermittant, 100 watts continuous.

MODEL 217 - 500 Hz 8-Pole Crystal Ladder CW Filter MODEL 218 - 1.8 kHz 8-Pole Crystal Ladder SSB Filter. MODEL 219 - 250 Hz 6-Pole Crystal Ladder CW Filter.

MODELS 215P and 215PC - Microphones Ceramic types for hand held or desk top operation. Include cable, 3-circuit plug, PTT



Argonaut 515 - QRP Transceiver

Totally solid state, full band coverage: 3.5, 7, 14, 21, and 28 MHz (optional crystals) for 29-30 MHz). 10m band now in four 500 kHz segments for greater bandspread. Improved receiver sensitivity: 0.35uV for 10 dB S+N/N, max. Four-pole 9 MHz crystal filter, 2.4 kHz Bandwidth, 1.7 shape factor. New heterodyne VFO with new permeability tuned oscillator for new frequency calibration accuracy. Direct frequency readout with new dial pointer zero-set. WWV receive at 10 and 15 MHz. Offset receiver tuning with new LED indicator. Receiver resonate control. New design no-tune broadband final amplifier. New LED rf output indicator flashes on 2 Watt voice peaks. PTT.



MODEL 645 Dual Paddle Electronic Keyer

The 645 keyer uses transistor switching and is powered by the transceiver. Adjustable magnetic paddle return. Paddle force 5-50 gms. Speed 6-50 wpm. Weighting ratio 50-150% of classical dit length. Self completing characters. Dit and dah memories with defeat switches. Torque drive paddles with 4 ball bearing pivots. Powered through the OMNI system.



MODELS 214/234 - Speech Processor and Microphone

Extends operating range of ssb transmitters under adverse and low propagation conditions. Converts audio signal into ssb signal, clips and processes it through 4-pole monolithic filter for greater average envelope power and converts signal back into audio. Adjustable levels of processing and output plus disable switch and passband adjustment. Powered through the OMNI system or by calculator type plug-in AC adapter which supplies 12 VDC @ 75 mA. Model 214 Electret Microphone is designed specifically to be used with Model 234 Processor.

ment Store



570

Century 21 (570) **Novice Exclusive**

Purchase your Century 21 570 from us and have up to one year to apply the full purchase price towards a Ten-Tec model of your choice when you upgrade your station.



MODEL 243 – Remote VFO

A duplicate of the OMNI VFO, Model 243 VFO, is housed in a matching enclosure and provides 6 modes of dual frequency operation. LEDs indicate selection of any of six modes of operation. OMNI transmit and receive, REMOTE transmit and receive, OMNI transmit-REMOTE receive, RE-MOTE transmit-OMNI receive, OMNI transmit-both receive, or REMOTE transmitboth receive. Full break-in is retained in all modes. Frequency range and accuracy is the same as OMNI.

In addition to the remote VFO capability, Model 243 also has a 4-position crystal oscillator for fixed frequency operation. Out-of-band crystal frequnecies (with some limitations) may be used as well as any nband amateur frequencies.

Model 243 comes with connecting cable, less crystals. Power is obtained from the OMNI system, Semiconductors: 9 transistors, 5 diodes, 6 LEDs. SIZE: HWD 5% x 8% x 8. Wt.: 3 lbs.



MODEL 210 - Power Supply

Delivers up to 15 watts, sufficient for the 515. 117 VAC, 50-60 Hz input, 13 VDC, ±0.5 V, 1.2 A. output. Solid-state. Finish matches 515.



MODEL 206A - Pulsed Crystal Calibrator

Companion to the 515, but useful with any receiving system. 25 and 100 kHz fundamental with harmonics into the VHF region. Pulsed output for easy identification. Powered by the 515 or any 9-12 VDC source. Finish matches the 515.



MODEL 208A - CW Filter/Variable Notch Filter.

CW filter has 3-position bandwidth switch, 450, 300, or 150 Hz, centered at 750 Hz; "off" position removes filter from circuit. Variable notch filter is effective over range of 200 Hz to 3.5 kHz with a depth down to 50 dB or more. Together these filters offer superb defense against unwanted signals, allow operation under most adverse conditions.



MODEL 670 - Single Paddle Electronic Keyer

Uses transistor swtiching and is powered through the OMNI system. Speed 6-50 wpm, Self-completing characters, Preset weighting for optimum articulation in the most used speed range (dit length increased approx. 10% at 20 wpm).

switch, and separate desk stand. Offer optimum articulation, free of power peaks, impervious to temperature and humidity changes. High impedance; 200-4000 Hz response; -50 dB level; die cast zinc and Cycolac; 81/4"h; 4' cable, single conductor shielded, two conductors unshielded. 3-circuit phone plug included. 215P has 4' regular cable; 215PC has 4' coiled cable.

DESCRIPTION PRICE MODEL ACCESSORIES 34.50 206A Crystal Calibrator Notch/CW Filter for Model 515 208A 39.00 212 Crystal, for Model 515, 29.0-29.5 MHz 5.00 213 Crystal, for Model 515, 29.5-30.0 MHz 5.00 214 Electret Microphone for Model 234 39.00 215P Microphone, Ceramic with plug 29.50 215PC Microphone, Ceramic with plug and coil cord 34.50 217 500 Hz 8 Pole Ladder Filter, for Models 545/546 55.00 218 1.8 kHz 8 Pole Ladder Filter, for Models 545/546 55.00 219 250 Hz 6 Pole Ladder Filter, for Models 545/546 50.00 234 Speech Processor 124.00 243 Remote VFO, for Models 545/546 139.00 247 Antenna Tuner 69.00 248 Noise Blanker, for Models 545/546 49.00 273 Crystal, for Model 570, 28.5-29.0 5.00 276 Crystal Calibrator, for Model 570 29.00 277 Antenna Tuner/SWR Bridge, for Model 579 85.00 282 250 Hz 6 Pole Ladder Filter, for Model 580 50.00 283 Remote VFO, for Model 580 179,00 285 500 Hz 6 Pole Ladder Filter, for Model 580 45.00 287 Mobile Mount, for Model 580 TBA 289 Noise Blanker, for Model 580 \$ 39.00 POWER SUPPLIES 117 VAC, 13 VDC, 1A \$ 34.00 210 210/E Same as Model 210, but 115/230 VAC 39.00 255 Deluxe, 117 VAC, 13.5 VDC, 18 A with 3" x 5" speaker 169.00 280 117/230 VAC, 13.5 VDC, 18 A 139.00 LINEAR AMPLIFIERS 444 Hercules, 1 kW with 115/230 VAC Power Supply \$1575.00 TRANSCEIVERS 515 Argonaut, 5W, SSB/CW, 3.5-30MHz \$ 429.00 545 OMNI-A, Analog, Series B, SSB/CW, 1.8-30 MHz 949.00 OMNI-D, Digital, Series C, SSB/CW, 1.8-30 MHz 546 1189.00 570 Century/21, 70 W. CW, 3.5-29 MHz 349.00 580 DELTA, 200 W. SSB/CW, 1.8-30 MHz 849.00 KEYERS 645 Ultramatic, Dual Paddle 85.00 s 670 Single Paddle Keyer 34,50

FINCO STINGER VHF/UHF Antennas



10 meter

STINGER A 10-4 DESCRIPTION

The model Stinger A 10-4 is a wide spaced, full size, high gain four element 10-meter monobander designed for optimum DX performance. Utilizing the ex-clusive Stinger Series square boom construction, the A 10-4 is light enough to be easily stacked for an additional 3 dB gain yet strong enough to withstand the most adverse weather conditions. The highly efficient gamma match sys-tem easily withstands 2,000 worts P.E.P. of power and maintains a relatively low V.E.W.B. arous the entire 10 meter amateur band. low V.E.W.R. across the entire 10-

SPECIFI

IS MOGER

STINGER A 65 DESCRIPTION

ELECTRICAL-Forward Gain Frish to Back Platio V.S.W.R. (at resonance) Half Power Beam Width 28 to 30 I Matching System: Adjustable Ga

-united	Contraction Consider	
CATH	ONS - A 10-4	
	MECHANICAL	
0:HE	Boom Length	1. a. a. a.
5d0	Longest Element	
3.3	Turning Fladius	See. 1
SIS C	Maximum Surface Area	10.94
414	Winit Load at 80 MPH	100
11114	AAAAAAAAAAAAAAAAAAAAAAAAAAAAAAAAAAAAAA	10.04

7.4 11 ELECTHICAL-Forward Galin Front to-Back Hatin 18 ibs V.S.W.R. Lat resona Halt Power Beam W Barschauldth

40.2 Hts. 11.5 Hts.

当其作

17.0 Htt

2 meter

STINGER A 3-10 DESCRIPTION The model Stinger A 2-10 is a high performance wide spaced ten element 2 meter yapi designed for the serious VHF operator. Utilizing the Stinger con-struction features, the A 2-10 is almost indestructable no metter what weather

conditions are encountered. Complete coverage of the 2-metter what weather CSW.R is assured through the use of new loss from density to the 2-metter band and low S.W.R is assured through the use of new loss trace spaced alweights thus also achieving maximum forward gain. Power rating - 2,000 wetts P.E.P. The A 2-10 can be mounted for vertical polarization, there by making the an-tering pulse weful in repeater accessing, or mounted for horizontal polariza-tion for station to station VHF DX work. Additional bays of the A 2-10 can be easily starked for even orester accessing from to hark ratio. be easily stacked for even greater gain and front to back ratio.

SPECIFICATIONS - A 2-10

	MECHANICAL-	
13.6dB	Boom Length	
dth 40"	Turning Radius Maximum Surface Area	3
144 to 148 3/Hz 50 Ohm	Wind Load at 80 MPH	6
division of the Constantion		

STINGER A 2.6 DESCRIPTION

The model Stroger A 2.5 is a fire element high gain antenna similar to the A 2.10 but having physically less of a profile. The A 2.5 finds excellent applications at a pertable enterna as it disasteribles into a very compact package. Like the A 2.10, the accents are be mounted for entrical or herizontal pelascation for repeates or general onverses work. Constructed of the Sciegar beavy duty materials, the A 2.5 is ideal for locations encountering adverse weather conditions. Power rating 2,000 wetts $P \in P$.





Matching Dy stern



dual polarization 2-meter antenna tional or where switching from horizontal to he A 2+2 can even be phased to operate on ical polarization at the same time. This is not only for ground carrier

nt spacing great the A 2+2 superior gain, however, since is the stament beam in one given plane, the half power beam width does of make satellite tracking difficult because of sharp directivity. The dual amma match assemblies provide for a very low V.S.W.R. and will withstand 000 wetts P.E.P

The Stinger construction features make the A 2+2 extremely heavy duty. Proexposes are made for reporting the extense at the end of the boom-muth control - or at the middle of the boom for normal applications. - For azi

58"

62%

SPECIFICATIONS - A 2+2 MECHANICAL-

Biocere & avoid h.

Invigent Element

Maximum Surface Area

Wind Load at 80 MPH

Furning Badius-

ELECTRICAL -9.548 10.548 2246 Forward Gain Circular Gam Front to Back Platio Half Power Beam Width Horizontal Polarization E Plane 52 H Plane Vertical Polarization -E Plane 58 H Plane -Circular Polarization H Flane 62" 144 to 148 MHz E Plane Bandwidth spedance 5D Chimi Matching System Adjustable Gamma

1914 meter

Weight



Hitachi Alliance

On this page Tufts brings you . . .

Finco Stinger

Ham-Key

10月

311 441 H. 210.2 Mrs. 9.8 Mrs.

6.5.11 41 in. 47 in. 73 so. 11 13.3 lbs.

41 11.

55 ft. 3.4 tt.

11 IDs.

1.51 sq 11. 13.4 lbs





100

\$32.95



P

ELECTRICAL-Forward Gain Front to Back Ratio \$46.50 mpedance finds excellent application high termile strangeh plus ELECTRICAL

VSWA

Half Powe

Handwicht

Impedation Matching liver

a mamory





Bandwillth

mpedance

MECHANICAL-Boom Length 13.11 Longest Element 10.11 Turhing Radius 8.3.11 Maximum Surface Area 3.23 vs. 11

25dlt 1.1.1 12⁰ V.S.W.R. fat resonancel 1.1.1 Half Power Beam Width 52° Bandwidth 50 to 54 MHz 50 ahmi Matching System Autjustable Gamma

STINGER A 6-3 DESCRIPTION

Weight

Wind Load at 80 MPH

ECHANICAL

Winet Load at BO MPH

The model Stinger A 5.3 is a 3 element high gain 6 met A 5.5 but expressly designed for the casual 6 meter enth for portable use as it de package. Due to the units light weight and minim sheat for double stacked and quast stacked arrays The A 8-3 is called at 2,000 watts P.E.P.

6 and 2 meter

STINGER A 62 DESCRIPTION The model Stinger A 52 is a truly remarkable combination 6 and 2-meter beam designed for optimum performance on both bands yet only requiring ONE transmission line. This is accompliabled through the use of exchance phase.



This electrically small 80/75, 40 & 20 meter antenna operates at any length from 24 to 70 ft. no extra balun or transmatch needed portable - erects & stores in minutes • small enough to fit in attic or apt. . full legal power low SWR over complete 80/75, 40 & 20 meter bands • much lower atmospheric noise pick-up than a vertical & needs no radials kit incl. a pr. of specially-made 4" dia. by 4" long coils, containing 335 ft. of radiating conductor, balun, 50 ft, RG58/U coax, PL259 connector, nylon rope & manual.



- \$219.95 Frequency - Agile Audio Filter The Datong Frequency-Agile Audio Filter is intended primarily for post-detector signal filtering in RF and LF communications receivers for SSB and CW. It offers an unusually versatile combination of benefits to the user including: For the SSB operator: Fast automatic suppression of interfering heterodyne whistles in the range 280-3000 Hz by a unique search-lock-andtrack notch filter. The tracking notch can be left in circuit with no audible effect until a whistle appears in which case the whistle will 'disappear' within typically one second.
- A continuously adjustable audio 'window' or a variable-width notch to improve reception in the presense of other off-tune SSB, RTTY or SSTV signals.

For the CW operator:

- Continuously variable center-frequency (280-3000 Hz) and bandwidth (25-1000 Hz) for perfect matching of receiver passband to changing band conditions, sending speeds, and personal preference.
- Flat-topped, steep-skirted response shape for optimum ease of tuning combined with excellent noise rejection.
- Linear tuning law with bandwidth inde-. pendent of frequency and gain independent of bandwidth for natural 'feel'

MODEL

30PB

50PB

53PB

137PB

144PB

PM-1

OSA 5

QSA 6

220PB

432PA

432PC

432PE

PB

TUFTS Electronic Department Store, TUFTS

LABORATORIES

CLASSIC 2 METER PREAMP This widely used 2 meter preamp is probably the most sensitive available today. One model provides a uniformly low noise figure across the full band. Equally applicable for DX, AM, SSB_FM and OSCAR_18 dB gain, 2 dB noise figure, 12 vdc power (SmA) BNC connectors. Aluminum box is 11x21x21; 144-148MHz Model 144PB PRICE DESCRIPTION PREAMPS \$ 21.95 28-30 MHz (BNC) 21.95 50-52 MHz (BNC) 21.95 52-54 MHz (BNC) 21.95 135-139 MHz (BNC) 21.95 144-148 MHz (BNC) 16.95 2m Preamp Module (Solder Terminals) 41.95 144-148 MHz for Transceivers (S0-239) 43.95 50-52 MHz (S0-239) 21.95 220-225 MHz (BNC) 33.00 420-450 MHz (BNC) 3.5 dB maximum NF 54.95 420-450 MHz (BNC) 2.0 dB maximum NF 90.00 1.0 dB typical NF Any single frequency between 30 and 50, or 148-174 MHz (BNC) 27.00 CONVERTERS 144-146 MHz IN, 28-30 MHz OUT (BNC) \$ 79.95

144CF 12.00 2nd crystal for 144CF (146-148 IN, 28-30 OUT) 79.95 432CF 432-434 MHz IN, 28-30 MHz OUT (BNC) 2nd crystal for 432CF (434-436 IN, 28-30 OUT) 10.00 (Also available with 434-436 MHz IN and 28-30 MHz OUT, (Oscar 8, 79.95 Mode J) OSCILLATORS 01-A Precision, Specify 4 or 10 MHz \$ 79.95 D1-A 10 to 1 Digital Divider 11.95 D8-A Eight, 10 to 1 Dividers 27.95 USEFUL ACCESSORIES 17013 BNC to BNC, 36" RG-58C/U Cable \$ 6.00 BNC to UHF, 36" RG-58C/U Cable 6.00 17010 17014 BNC to RCA Phono, 36" RG-58C/U Cable 6.00 03005 Adaptor, BNC Plug to UHF Jack 4.00 03006 BNC Connector, UG-88/U for RG-58 size cable 1.25 MISCELLANEOUS ISOLINE \$ 14.95

Antenna Isolator, 144-174 MHz (S0-239) Cavity Filter, .5 dB loss



The QSA 5 preamp is a high performance, low noise preamp for improving the receiving sensitivity of 2 Meter transceivers. This preamp leatures easy installation with no modification to the transceiver required. This preamp can be used with virtually all 2 meter transceivers and on all modes - FM. SSB. CW or AM. Relays in the QSA 5 automatically bypass the preamp when transmit power is sensed. A LED indicator shows the status of the QSA 5. A front panel switch allows the preamp to be bypassed while receiving. The low noise figure of the QSA 5 pro-vides for exceptional sensitivity. The gain has been set to optimize the performance with 2 meter trans-CRIVERS.



PREAMP MODULE

This low noise preamp is designed to be easily incorporated into new or existing 2 meter equipment Solder pris are provided for mounting to a PC board or for connection to wire or coax. Uses low noise JANEL MOSFET circuitiv Each unit is fully tested for gain and noise figure. Quantity prices are available for OEM's.



UHF PREAMPS Model 432PA 420-450MHz

Low Cost All Around Favorite

This two stage amplifier provides high sensitivity across the full 420 to 450 MHz band. A low 3.5 dB noise figure makes this preamp ideal for most amateur applications. Can be used for all modes. 17dB. gain, 12vdc power (10mA), BNC connectors (50 ohms), aluminum box 11+4x2 ...

Model 432PC 420-450MHz **Extremely Sensitive**

This preamp provides a low noise figure required for demanding applications. A premium state-of-the-art transistor is used to provide extremely high sensitivity Two stages, 20 dB gain, 2 dB maximum noise

6 METER PREAMP Ideal for DX

This low noise preamp significantly improves the sensitivity of most 6 meter receivers. Available m two frequency versions to cover DX and FM porfrom of the band, 18 dB gain, 2 dB noise figure, 2 vitt power: BNC connector



For 6 Meter Transceivers

All of the features of our popular QSA-5 but for 6 meters Fully compatible with transceivers (unning 30 watts or less. All mode use. Nome Figure 2d8. Gain, 15dB, VSWP (transmit) 1 2. Available for 50-52 or 52-54MHz (specify when ordering) UHF conrunctors Model QSA-6.



Ideal for pulling weak satellite signals out of the noise. This preamp hills been responsible for producing many impossible OSCAR OSCI's 18 dB gain. 2 dB noise figure, 12vdc power (5mA), BNC connectors. Aluminum box is 12x21x21, Model 30 PB 28-30MHz

220 MHz

A Low Noise Preamp

114 Meters-Covers full 220-225 MHz range with 15 dB gain, 3 dB norse figure, 12 volt power and BNG connectors. Model 220PB.



Our Finest UHF Preamp-1.0 dB NF

This outstanding 432 MHz preamp provides the lowest practical noise figure. The finest transistors available loday are combined with the ultimate in construction and alignment Single stage Gain 15dB (mim) Noise Figure 1.2dB (max including measurement uncertainty: 0.8 to 1.0dB typical Bandwidth 100 MHz. 12 volts at about 7 mA. Type N connectors. Size 1, aix1, inches, Cantai Frequency 400 to 51



\$65.95

JANEL

trees

Interference Filters from J. W. Miller



Coaxial Switches 2 Position/Model CS-201 4 Position/Model CS-401

SWR & Power Meters Models CN-720, CN-620 and CN-630

Professionally engineered cavity construction. Power Rating: 2.5kW PEP, 1kW CW Impedance: 50 Ohms Connectors: SO-239 Insertion Loss: Less than 2 dB VSWR: 1:1.2 Maximum Frequency: 500 MHz Isolation: Better than 50 dB at 300 MHz; better than 45 dB at 450 MHz; adjacent terminal.





CN-720 \$166.95



105.00

115.00

RF Speech Processor Models RF-400

DAIWA

Increases talk power with splatter free operation. RF clipping assures low distortion. Simply install between microphone and transmitter. Talk Power: Better than 6 dB.

Frequency Response: 300-3000 Hz at 12 dB down.

Distortion: Less than 3% at 1 kHz, 20 dB clipping.

CN-720 and CN-620 Frequency Range: 1.8-150 MHz SWR Detection Sensitivity: 5W min. Power: 3 Ranges (Forward, 20/200/100W) (Reflected, 4/40/200W)



CN-620



Low Pass Filters

Eliminate or greatly reduce interference to TV receivers by radio amateur staions when installed in antenna lines of those transmittars. Input and output impedance 50 ohme. Tenertion loss 3 dB max_VWSR 1.2-1 Attenuation greater than 75 dB above 41 MHz C-511-T: 25 W AM 50 W PEP SS8. \$19.50 C-514-T: 1000 W AM 2000 W PEP SSB \$26.80

High Pass Filters

When installed in the antenna, eliminate or greatly reduce front and overload interference. to TV or FM receivers caused by amateur \$10.18 radio transmitters and other high frequency. radio services. Filter attenuates signals below. \$10,18 40 MHz by a power factor greater than 1,000,000:1. Impedance C 513 T 1: 75/300 ohm C-513-T2: 75/75 ohm; C-513-T3: 300/300 ohm

Audio Interference Filters

Eliminate interference caused in your audio equipment by cadio anateur transmitters and other ratio services. C.505-R installs in the input lines of autio equipment. Conjists of 1 pair, C'506-R installs in speaker lines. Unit will take care of stored speaker system.

\$5.07 \$6.67

AC Power Line Filters

Diminate or reduce interference to radio	
revent radio signals from entiring power	
5608 L. 3-section LC filter, 3 A max.	\$ 8.33
C 509 L Strection LC filter (for more severe nterferation), 5.4 mas	\$18.35

CN-630 Frequency Range: 140-450 MHz Power: 2 Ranges (Forward 20/200W) (Reflected 4/40W)





\$99 VHF model 4362 (140-180 MHz) HF model 4360 (18- 30 MHz)

> The 4360, 4362 HAM-MATE Directional Wattmeters are insertion type instruments for measuring forward or reflected power in S0-ohm coaxial transmission lines. They are direct descendants of the model 43 THRULINE® Wattmeter - the professional standard of the industry-and will accurately measure RF power flow under any load condition. Each wattmeter is made up of a precisely machined section of 50-ohm line, a rotatable sensing element and meter calibrated in watts, all mounted in a high-impact plastic housing. It is this type of solid construction and the directional THRULINE coopling circuit, without toroids, that account for the superiority of the HAM MATE Wattmeters.

the indianon cable		1	Frequency Bands (MHz)			
the indispensable	Range	2- 30	23- 60	100- 250	200- 500	400
THRULINE WATTMETER	5 watts 10 watts 25 watts 50 watts 100 watts 250 watts 500 watts 2500 watts 500 watts 500 watts		54 104 254 504 504 504 504	90 X X X X X X X X X X X X X X X X X X X	50 100 250 1000 2500 1000 10000	51 105 251 505 1006 505 505 1006
ODEL 43 Elements (Table 1) 2-30 N Elements (Table 1) 25-100 Carrying case for Model 43 &	1Hz 00 MHz 6 elemen	ts	\$135 50 42 28	00, 00, 00,		

READ RF WATTS DIRECTLY! (Specify Type N or SO239 connectors) 0.45 - 2300 MHz, 1-10,000 Watts ±5%, low insertion VSWR 1.05, Unequalled economy and flexibility. Buy only the element(s) covering your present frequency and power needs, add extra ranges later if your requirements expand.



Carrying case for 12 elements

SERIES 31 - BNC CONNECTORS Amphenol's BNC connectors are small, lightweight, weatherproof connectors with bayonet action for quick disconnect applifications.

Shells, coupling rings and male contacts are accurately machined from brass. Springs are made of beryllium copper. All parts in turn are ASTRO plated^(E) to give you connectors that can take constant handling, high temperatures and resist abrasion.

83-877-385

575-102-385

UG-273

83-5SP-385

575-105-385

UG-88

UG-914

UG-290

CT 3

UG-306

R

FUE

UG-274

SO239



17.00



Single and dual trace, 15 and 30 MHz, All four high sensitivity Hitachi oscilloscopes are built to demanding Hitachi quality standards and are backed by a 2-year warranty. They're able to measure signals as low as 1mV/division (with X5 vertical magnifier), It's a specification you won't find on any other 15 or 30 MHz scope. Plus: Z-axis area. Mast support bracket design permits modulation, trace rotation, front panel X-Y operation for all four scope models, and X10 sweep magnification, And, both 30 MHz oscilloscopes offer internal signal delay lines. For ease of operation, functionally-related controls are grouped into three blocks on the color coded front panel.

 V-302 30 MHz Dual Trace \$850.50 V-301 30 MHz Single Trace \$670.50 V-152 15 MHz Dual Trace \$625.25 V-151 15 MHz Single Trace \$490.50

New Thickwall Casting

New Metal Pinion Gear

New Super Wedge Brake

New L.E.D. Control Box

Designed for the newest of the

king-size communications anten-

nas, the TAIL TWISTER IM is the

ultimate in antenna rotational

devices. The TAIL TWISTER IM

starts with a deluxe control box

featuring snap action controls for

brake and directional controls;

L.E.D. indicators signal rotation

and brake operation, while the

illuminated meter provides direc-

tion readout. This new control

box couples to the newest bell

rotor. Using the time tested bell

rotor principle, the TAIL TWIST-

ERTM is a brand new design with

thickwall castings and six bolt

assembly. A brand new motor

with prebrake action brings the

antenna system to an easy stop,

while the massive square front

brake wedge locks the assembly in

place. A new stainless steel spur

gear system provides final drive

Safe 26 Volt Operation

New Steel Ring Gear

New Motor Prebrake



For antennas up to 10.7 sq. ft. of wind load easy centering and offers a positive drive no-slip option. Automatic brake action cushions stops to reduce inertia stresses. Unique control unit features DUAL-SPEED rotation with one five-position switch. SPECIFICATIONS: Max, wind load bending moment - 10,000 in.-lbs. (side-thrust overturning); Starting torque - 400 in.-lbs.; Hardened steel drive gears; Bearings -100-3/8" diameter (hardened); Meter -D'Arsonval, taut band (back-lighted). There's much, much more.

BNC BULKHEAD RECEP-TACLE 31-221-385 UG-1094 Mates with any BNC plug Receptacle can be mounted into panels up to 104" thick. UG-1094

\$1.25 BNC (M) TO UHF (F) ADAPin a did TER 309-2900-385 UG 255 Adapts any BNC jack to any UG-255

UHF plug. \$3.63 DOUBLE MATE ADAPTER 83-877-385 Both coupling rings are free turning. Connects 2 female components. \$2.72

JACK ADPATER \$1.95 575-102-385 Adapts 83-1SP-385 to Motorola type auto antenna jack or pin jack. PANEL RECEPTACLE 83-1R-385 SO239 Mounts with 4 fasteners in 21/32" diameter hole. \$1.17 PANEL RECEPTACLE

BNC(F) TO UHF (M) ADAF-TER 31-028-385 UG-273 Adapts any BNC plug to any UHF jack. \$2.39 PUSH-ON

83-5SP-385 Features an unthreaded, springy shell to push and fit on female connectors. \$2.27

LIGHTNING ARRESTOR 575-105-385 Eliminates static build-up from antenna. Pro tects your valuable equipment against lightning damage \$4.80

BNC PLUG 31-002-385 UG-88 Commonly used for communications antenna lead cables. For RG 55/U & RG 58/U cables. \$1.59 BNC STRAIGHT ADAPTER 31-219-385 UG-914 1 9/32" long, allows length of cables to

be joined. Mates with BNC plugs. \$2.12 BNC PANEL RECEPTACLE 31-003-385 UG-296 Mounts with 4 fasteners in 29/64" diamieter hole. \$1.74

83-878-385 SO239SH Mounts in single 21/32" diameter hole. Knurled lock nuts prevent turning. \$1.59 SO2395H BNC ANGLE ADAPTER 31-009-385 UG-306 Adapts any BNC plug for right angle use. \$4.23 BNC TEE ADAPTER 31-008-385 UG-274 Adapts 2 BNC plugs to 31-003-385 or other female BNC type receptable. \$4.56



First is the Fox XK. It reads all bands and tucks away on the visor.



Our remote (RW) unit is "out-ofsight" when installed. Out-of-sight in performance, too.



And now there's Superfox!

The first remote, superheterodyne radar warning system. Superlox has 10 times the sensitivity capability of any conventional radar detector. It is ideal for custom installations.

PRICE LIST Order Description No. Price Fox XK 60 All band detector w/self contained aural/visual alarm \$109.00 Fox XK (RW) 60-2 All band detector w/remote control, waterproof \$139.00 Super Fox 60-3 Super-Heterodyne remote \$279.95 radar warning system



Two NEW Rotors

into a new steel ring gear for total reliability. Triple race, 138 ball bearing assembly carries dead weight and maintains horizontal stability.

An optional heavy duty lower mast adaptor is available for lighter loads with mast mounting. Price: \$249.00

The HAM IV sets new levels of performance. Snap action switched wedge brake and rotational controls brings pinpoint accuracy to large directional arrays popular in communications. A new motor provides pre-brake action to assist in slowing down rotational mass, and the new thicker wedge brake offers far stronger lock-in phase action. To take full advantage of this new design, the HAM III is designed for in-tower mounting. A new optional heavy duty lower mast adaptor is available when the HAM III is to be mast mounted with smaller arrays. A stainless steel spur gear system multiplies the torque into the dual race 98 ball bearing support assembly assuring years of trouble free performance. Price: \$169.00





299.95

199.95

199.95

169,95

169.95

149,95

129.95

79.95

69.95

69.95

69.95

3.00

MFJ-40T ORP Transmitter MISCELLANEOUS MFJ-202 RF Noise Bridge. MFJ-1030BX Receiver Preselector.	MFJ-900 MFJ-16010 59.95 49.95	balance lines, 200W output. Econo Tuner. Matches coax and random wires. 200W Random Wire Tuner. For random and long wires, 200W	49.9 39.9 29.9
MFJ-200BX Frequency Standard, MFJ-40T QRP Transmitter, MFJ-40V Companion QRP VFO for 40T CPO-555 Code Practice Oscillator TK-555 Optional Telegraph Key.	29.95 29.95 29.95 17.95 1.95 24-H(SOLI	OUR DIGITAL CLOCK D-STATE	
s 49 95	\$ 5995	E 3:59 \$299	5
LSP-5208X LSP-5208X II		EW,E	
MFJ-525 RF Speech Processor. Plugs between.microp rig. Powerful natural sounding speech. Vu n	hone and 24 HOUR I	DIGITAL CLOCK	
for adjustment of processing, 4 pin mic jack more average SSB power, use with any rig a mic, push button on-off/bypass. LSP-520BX II Logarithmic Speech Processor. Deluxe mode	, 6 dB nd any 119.95	display (like TS-820S), ID time, lock function (prevents accidental missetting of time).	29.9
for adjustment of processing, 4 pin mic jack more average SSB power, use with any rig a mic, push button on-off/bypass. LSP-520BX II Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor.	, 6 dB nd any 119.95 el. 59.95 49.95	These MFJ active filters are the most copied in Industry. CHI 24 HOUR DIVISION CONTRACT OF THE STATE OF THE	29.9
for adjustment of processing, 4 pin mic jack more average SSB power, use with any rig a mic, push button on-off/bypass. LSP-520BX II Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor.	6 dB nd any 119.95 el. 59.95 49.95 49.95 49.95 SSB/CW FI MFJ-752 SSB/CW FI	24 Hour digital clock, totally solid state, 50 blue display (like TS-820S), 1D time, lock function (prevents accidental missetting of time). These MFJ active filters are the most copied in Industry. Set of an effective filter are the most copied in Industry. Set of an effective filter are the most copied in Industry. Set of an effective filter are the filter are	29.9
for adjustment of processing, 4 pin mic jack more average SSB power, use with any rig a mic, push button on-off/bypass. LSP-520BX II Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor. 5549 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540 540540	 6 dB nd any 119.95 al. 59.95 49.95 Dot memory • lambic opera- roal squeeze key • 8 to 50 ie and speaker • Speed vol- it controls • Unita reliable solid 300 volts max • 4 position E OFF ON SIDETONE OFF ht cells • 2.3 16 • 3.114 • 4 MFJ-751 MFJ-721 	Are notice digital clock, totally solid state, 5 bits display (like TS-820S), 1D time, lock function (prevents accidental missetting of time).	29.9 79.9 59.9
for adjustment of processing, 4 pin mic jack more average SSB power, use with any rig a mic, push button on-off/bypass. LSP-520BX II Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor. 5549 5549 564 6 6 6 6 6 6 6 6 6 6	• Dot memory • lambsc operations • Dot memory • lambsc operations rical squeeze key • 8 to 50 e and speaker • Speed vol- it controls • Unita reliable solid 300 volts max • 4 position E OFF ON SIDETONE OFF In cells • 2:3:16 • 3:1:14 • 4 MFJ-751 MFJ-721	Ar hour digital clock, totally solid state, 5 bibe display (like TS-820S), 1D time, lock function (prevents accidental missetting of time). These MFJ active filters are the most copied in Industry. State of the state of the state of the state of the state state of the state o	29.9 79.9 59.9
for adjustment of processing, 4 pin mic jack more average SSB power, use with any rig a mic, push button on-off/bypass. LSP-520BX II Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor. Deluxe Mod Logarithmic Speech Processor.	 6 dB nd any 119.95 el. 59.95 49.95 Dot memory • lambic opera- mai squeeze key • 8 to 50 e and speaker • Speed vol- t controls • Ultra reliable solid 360 volts max • 4 position E OFF ON SIDETONE OFF m cells • 2:3 16 • 3:1:4 • 4 MFJ-751 MFJ-721 MFJ-720 	All hour digital clock, forally solid state, 5 bibe display (like TS-820S), 1D time, lock function (prevents accidental missetting of time).	29.9 79.9 59.9 59.9
tor adjustment of processing, 4 pin mic jack more average SSB power, use with any rig a mic, push button on-off/bypass. LSP-520BX II Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor. Deluxe Mod Logarithmic Speech Processor.	6 dB md any 119.95 el. 59.95 el. 59.95 el. 59.95 el. 59.95 49.95 SSB/CW FI MFJ-752 MFJ-751 MFJ-721 MFJ-720 69.95 S9.95 CWF-2BX	Ar hour digital clock, forally solid state, 5 bibe display (like TS-820S), 1D time, lock function (prevents accidental missetting of time).	29.9 79.9 59.9 59.9 59.9
for adjustment of processing, 4 pin mic jack more average SSB power, use with any rig a mic, push button on-off/bypass. LSP-520BX II Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor. Deluxe Market Speech Processor.	 6 dB nd any 119.95 el. 59.95 49.95 Dot memory • lambsc opera- nal squeeze key • 8 to 50 e and speaker • Speed vol- t controls • Unita reliable solid 360 volts max • 4 position E OFF ON SIDETONE OFF ht cells • 2/3/16 • 3/1/4 × 4 MFJ-751 MFJ-721 MFJ-720 69.95 59.95 44.95 CWF-2BX SBF-2BX 	A nour digital clock, forally solid state, 5 bibe display (like TS-820S), 1D time, lock function (prevents accidental missetting of time).	29.9 79.9 59.9 59.9 44.9 29.9 29.9
for adjustment of processing, 4 pin mic jack more average SSB power, use with any rig a mic, push button on-off/bypass. LSP-520BX II Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor. Composed for the second speech Processor. CMOS-8043 Electronic Keyer State of the art design uses CURTIS-8043 Keyer-on-a-chip ELECTRONIC KEYERS MFJ-404 Deluxe Keyer. Dot and dash memory. MFJ-404 Econo Keyer. Built in paddle, plus extras. MFJ-405 Econo Keyer. Built in paddle, plus extras. MFJ-406 Econo Keyer. Built in paddle, plus extras. MFJ-408 New Deluxe Electronic II, speed readout met Memory random code senerator backgread	 6 dB nd any 119.95 59.95 49.95 59.95 49.95 59.95 49.95 SSB/CW FI MFJ-752 MFJ-751 MFJ-751 MFJ-751 MFJ-721 MFJ-721 MFJ-721 MFJ-721 MFJ-720 69.95 59.95 44.95 49.95 CWF-2BX SBF-2BX AC Adapter CWF-2PC 	Ar hour digital clock, totally solid state, 5 blue display (like TS-820S), 1D time, lock function (prevents accidental missetting of time). These MFJ active filters are the most copied in Industry. Sector WJ takes of white Page 5 act Page 5 a	29.9 79.9 59.9 59.9 59.9 44.9 29.9 29.9 29.9 29.9
tor adjustment of processing, 4 pin mic jack more average SSB power, use with any rig a mic, push button on-off/bypass. LSP-520BX II Logarithmic Speech Processor. Deluxe mod Logarithmic Speech Processor.	 6 dB nd any 119.95 el. 59.95 49.95 Dot memory • lambac opera- mal squeeze key • 8 to 50 e and speaker • Speed vol- t controls • Ubtra rehable solid 300 volts max • 4 position E OFF ON SIDETONE OFF th cells • 2 3 16 • 3 114 • 4 MFJ-751 MFJ-751 MFJ-751 MFJ-720 69.95 59.95 44.95 44.95 49.95 CWF-2BX SBF-2BX AC Adapter CWF-2PC SBF-2PC 	Ar hour digital clock, totally solid state, 5 bibe display (like TS-820S), 1D time, lock function (prevents accidental missetting of time). These MFJ active filters are the most copied in Industry.	29.1 79.9 59.9 59.9 44.9 29.9 29.9 7.9 19.9

MFJ-943

Versa Tuner II. Less SWR/wattmeter, antenna switch





ORDER BLANK



Prices FOB Medford, Mass. Mass. residents add 5% sales tax.

Electronic Department Store

OPEN DAILY 9-9

206 Mystic Ave., Medford, Mass., 02155, Tel. 1-617-391-3200

Minimum \$3.50 for shipping and handling on all orders.

SATURDAY 9-6

CAT. NO.	PAGE NO.	DESCRIPTION	QUANTI	TY D	UNIT PRICE	PRICE
		gine his 1Diar		1	nes.	
dana ji				140		
Name .		Call		5% (Ma	Sales Tax ss. Residents)	
City _	•	State Zip		Ship	ping	\$3.50

PUPPS Electronic De

Check Enclosed Visa	Master Charge	and Handling	Min.
PRICES SUBJECT	TO CHANGE WITHOUT NOTICE	Amount	
Card no	Card exp. date	Enclosed	
Signature		-	

SPECIAL PRICING NOTICE

Many of the major items, such as transceivers, are available at special discount prices. A complete list of these special discount prices may be obtained by writing or calling our mail order department. If your order contains one of the items on the current discount list our sales staff will make sure that you receive the lower prices.



Peter A. Stark K2OAW PO Box 209 Mt. Kisco NY 10549

Build a Talking Digital IDer - K2OAW redesigns his IDer at last

hen my CW identifier and repeater control circuit article appeared in the February and March, 1973, issues of 73 Magazine, I thought that those circuits were about as modern and simple as they could get. Over the years, I've heard of printed circuit boards and kits being sold at hamfests, and several ham repeater manufacturers have

used the CW identifier circuit in their systems. The identifier also has been used in RTTY stations to provide Morse code identification.

But times do change; sev-

time for a new identifier design.

Here is an identifier circuit which should renew interest in identifiers for a while. It uses six ICs, the same as the 1973 version, but this identifier talks.

little muffled, perhaps (after all, what can you expect from six commonly-available ICs?), but clear enough to understand.

I'm having some fun with mine right now. It's sitting

eral articles have appeared in 73 Magazine giving circuits which modified or expanded the original design. I finally decided that it was

Yes, you read it right. It doesn't whistle or hum your call-it says it right out loud, in plain English, for the whole world to hear. A



Although it makes a great conversation piece, that is not its main purpose. I started designing this identifier while driving on a long vacation trip last summer. Every half hour or so, 1 would remember to key up my 2-meter rig on .52, hoping that somebody would come back. In the meantime, a hundred hams could have passed me by going in the opposite direction. But unless I picked up the mike and gave my call every minute or two, the chances of either one of us knowing about the other were slim. Wouldn't it be nice (I thought) to have an automatic IDer which would key up the rig every minute or so and announce itself? If there were anybody around, they surely would









FAST SCAN AMATEUR TELEVISION PRODUCTS FOR THE 420-450 MHZ BAND

P. O. Box 7127

817/848-4435

Waco, Texas 76710

V 79

*ATV REPEATER Model 1570B - a complete system with filters ready to connect to antennas	*ATV R vertice	EPEATER ANTENNA – a dual antenna system, omnidirectional, al polarization
*ATV TRANSCEIVERS Model TXR 15A – 15 watt peak output, audio s Model TXR 15T – 15 watt peak output, audio s	ubcarri subcarr	er, 2 frequency crystal controlled receiving converter ier, tuneable receiving converter
*ATV TRANSMITTER Model TX 15A - 15 watt peak output, audio sub	ocarrier	*IN-LINE DETECTOR Model XD 25C - monitor your actual transmitted picture
*ATV RECEIVING CONVERTERS Model TR 70A - tuneable 420 - 450 MHz Model XR 70A - crystal controlled, single free Model XR 70B - crystal controlled, dual frequ	quency	*AUDIO-VIDEO DEMODULATOR Model TD 100A- connect a converter, speaker, and video monitor and you have a commercial quality receiving system
TELEVISION HANDBOOK FOR THE AMATEUR		*ANTENNAS – 48 and 88 element models
EVERY APTRON ATV PRODUCT IS COMPLETE, FACTORY A PROVIDES COMMERCIA SOLD WITH A 30 DAY S AND A ONE YEAR WAI	SSEMBI L QUA SATISFA	LED AND TESTED LITY COLOR PERFORMANCE CTION OR MONEY BACK GUARANTEE-
FOR INFORMATION CALL 812-336-4 APTRON L	.775 .A	5, OR WRITE TO- BS 18 PO BOX 323 BLOOMINGTON INDIANA,47402

hear me. And voilà-necessity was the mother of invention.

The identifier uses an EPROM (Erasable Programmable Read Only Memory) to store the voice data to be spoken. The secret, of course, is in knowing how to program this EPROM. I do the programming on my SWTP 6800 computer system, but it could be done on another computer just as well. This article includes the programs and a PC board layout to make your job easier. (Etched and drilled PC boards as well as preprogrammed EPROMs are available from Star-Kits, PO Box 209, Mt. Kisco NY 10549.)

How It Works

There are many ways either to store a real sound recording in a digital memory or to synthesize a fake voice. Quite a few voice synthesizers are available today, ranging from the Texas Instruments Speak and SpellTM to the Computalker synthesizer available for S-100 computers and the Radio Shack synthesizer for the TRS-80. Unfortunately, most of these are fairly complex, require some custom-integrated (and often secret) circuits, and are difficult to program. Simply storing a digital image of a real voice and playing it back from memory turns out to be much easier and cheaper. That is how this identifier works. Its EPROM contains a digitized "recording" of a voice (which had been digitized previously on a computer), and a fairly simple circuit then scans the memory and "plays" it back. The only problem is to store the voice recording in such a way that it doesn't exceed the capacity of the EPROM. If memory capacity were not a problem, then the voice pattern could be

stored with voice fidelity better than any commercial hi-fi recording. In fact, digital stereo recording is the latest technique on the hi-fi scene because it can provide frequency response and distortion figures beyond anyone's wildest dreams of just a few years ago. But there is a price to be paid-very large amounts of digital data are involved. Digital recording often is done with videotape recorders which can record and play back millions of bits per second. Squeezing two seconds worth of voice into an **EPROM** which contains just 16,384 bits obviously requires some compromises, and it results in audio quality which is far from hi-fi. But it works.

To see how voice can be digitized, look at Fig. 1(a). Here we see a typical sound waveform such as might be picked up by a microphone. In order to digitize that waveform, we sample it at fixed, periodic intervals, and digitize the voltage that that waveform has at those instants of time. For instance, suppose we measure the waveform voltage at the points marked with a dot, convert the value of that voltage to a binary number, and store it. If that is later "played" back, we get the waveform shown in Fig. 1(b). The result is a square waveform which changes to a new value at each of the sampling points. Although the square wave doesn't look anything like the original audio signal, if it is fed through a low-pass filter the sharp corners will be chopped off and the signal will look a bit better. If, on the other hand, we were to sample the audio signal more often-not only at the dots but also at the intermediate points marked with an X-and digitize that, the resulting wave-



Fig. 1. Digitizing audio at various sampling rates.

form, shown in Fig. 1(c), would be a better approximation.

Fig. 1(d) shows that when we digitize very often, we get the best waveform yet. Although this waveform does have some sharp corners, they occur at a very high frequency and would be removed very easily with a filter. squiggles that have a highfrequency component. To get those, we need a high sampling rate.

Fig. 2 shows a block diagram of the circuitry which would be needed to do the digitizing. Starting with the audio signal, the signal is amplified and sent through a low-pass filter. The purpose of the filter is to remove those frequencies which are too high to be digitized (that is, more than half the frequency of sampling). These components have to be removed to avoid further distortion during the digitizing.

How often must we digitize to get an acceptable digitized waveform? There is a rule called the "sampling theorem" which says that the sampling rate must be at least twice the frequency of the highest frequency component in the audio signal. In other words, a hi-fi signal with a frequency response to 20,000 Hz would have to be sampled at least 40,000 times per second. A communications-quality voice signal with a response to 4000 Hz would require sampling at least 8000 times per second.

We can get an idea of this from Fig. 1(b). Sampling at the black dots is enough to get a waveform which follows the large swings of the audio waveform which have a low frequency but cannot capture the small

The filtered signal is now sent to a sample-and-hold circuit. This circuit takes a sample of the waveform and holds it in a capacitor while the analog-to-digital (A/D) converter converts the resulting voltage to a binary number. This is necessary because most A/D converters require a steady input voltage while they are converting; if the voltage is changing, then they will probably convert the voltage to the wrong value. Both the sample-and-hold circuit as well as the A/D converter are driven by a

CONTESTING?



THE NEW LOW COST AEA CONTEST KEYER MODEL CK-1 WILL MAKE YOU MORE COMPETITIVE THAN EVER! S129.95 SUGGESTED AMATEUR NET

- Automatic Serial Number Generator From 01 to 9999.
- 500 Character Soft Partitioned [™] Memory That Can Be Divided Into as Many as 10 Messages.
- Exclusive AEA Memory Editing Capability.
- Two Presettable Speeds With Fast Recall Plus Stepped Variable Speed Selection.
- Iambic Operation From 1 to 99 wpm and Complete Weighting Control.
- Extreme R.F. Immunity, Will Key Any Modern Transceiver, Operates from 12 ± 3 Volts D.C.

SEE YOUR FAVORITE DEALER OR CONTACT

Advanced Electronic Applications, Inc., P.O. Box 2160, Lynnwood, WA 98036. Call 206/775-7373



The 48 Hour Miracle.

From our hands to yours in record time. Like two days or less. But there's more to the miracle than Emergency Service and Guaranteed Shipment.

Sentry produces the highest quality crystal made. Anywhere. Each crystal is a work of art, made from the finest raw materials, utilizing state-of-the-art technology.

Put a miracle in your hands. Just call Sentry's toll free number, 1-800-654-8850.



Crystal Park, Chickasha, Oklahoma 73018

SENTRY

- 333

FALL TUNE UP TIME

Check-Tune your rig for maximum power with a B & W Dummyload-Wattmeter



Model 334A

Freq. Range: DC-300 MHz VSWR: Less than 1.3:1 Power Range: Up to 1000 watts

Model 374

Freq. Range: DC-300 MHz VSWR: Less than 1.3:1 Power Range: Up to 1500 watts



Model 333 Medium Power Model

Freq. Range: DC-300 MHz VSWR: Less than 1.3:1 Power Range: Up to 250 watts



Barker & Williamson, Inc. 10 Canal Street, Bristol, Pa. 19007



Fig. 2. Circuitry needed to digitize audio.

clock oscillator which sets the rate at which the input signal is sampled.

The output of the A/D converter is now a binary number which can be stored in memory or recorded on tape. When the digitized data is played back, as shown in Fig. 2(b), the binary data is converted back to an analog signal with a digital-to-analog (D/A) converter, passed through a low-pass filter to remove the sharp corners from the wave, amplified, and fed to a speaker. consisting of just one bit. That one bit is not enough to indicate the precise voltage of the input. With one bit, we can tell only whether the input was positive or negative. This obviously will lead to a very distorted wave, since we cannot hope to keep all the little squiggles in the audio signal.

On the other hand, a ten-

tion and to give a little "headroom" so that an occasional burst of extra volume can get through, you are close to 14 bits per sample.

The digital systems being proposed in the hi-fi industry use between 14 and 18 bits per sample; 14 bits are used in consumer products and up to 18 bits are used in the studio-quality recorders which produce the master tapes.

How many bits per second (bps) does this add up to? For pure hi-fi, we need at least 40,000 samples per second, each with at least 14 bits, for a minimum of 560,000 bps (and up to 2 MHz in studio-quality systems). At a rate of 560,000 bps, a 16,384-bit EPROM would provide hi-fi for about 0.03 second. Not enough for a grunt, let alone a ham call.

So we must limit the number of bits per second. This is done by drastically reducing the sampling rate and also reducing the number of bits from the A/D converter. sult quite understandable.

The Talking Identifier

Let's leave for a moment the question of how you "record" the voice and store it in the ROM, and look at the circuit of the talking IDer itself, Fig. 3.

The voice pattern is stored in a 2716 EPROM. This is a memory IC currently selling for about \$10-\$15. It is organized as 2K × 8, meaning that it has 2K storage locations (which is 2048), each holding an 8-bit number.

Now that we know how often a sample should be taken of the input wave, we have another question: How accurately must it be digitized in the A/D converter? This is related to the number of bits produced by the converter for each sample.

A binary number consisting of just one bit can take on only one of two values either 0 or 1. A binary number consisting of two bits can have values of 00, 01, 10, or 11, a total of four different values. In general, a number which consists of n bits can take on 2ⁿ different values. For instance, ten bits allow 1024 different numbers.

Suppose the converter produces a binary number

bit number can represent 1024 different numbers. Thus, we could measure and encode 512 different positive voltage levels and 512 different negative voltage levels. Thus, the more precise we want our measurements of the sample voltages to be, the more bits we need for each measurement.

In a hi-fi system, we often try to get a signal-to-noise ratio (S/N) of 60 dB or more. 60 dB is a voltage ratio of 1000 to 1, so that we must be able to reproduce two signals even if one is 1000 times larger than the other. This requires being able to measure at least 1000 different positive voltage levels and 1000 different negative voltage levels, for a total of 2000 different voltage levels. Since $2^{11} =$ 2048, we need at least 11 bits for this. By the time you add a few more bits to allow these signals to be reproduced with low distor-

To squeeze a two-second call into this ROM, we can store 8192 bps. At a sampling rate of 8000 Hz or so (to cover the communications audio range to 4000 Hz), that gives us about one bit per sample. This means that we don't need a complex sample-and-hold circuit, an A/D converter, or even a D/A converter. All we need is some circuit which can tell whether the input audio is positive or negative at the sampling intervals, and which produces a one-bit output -1 if positive, 0 if negative. That turns out to be very simple to do.

The disadvantage is that our voice recording will be very distorted. But by heavily filtering the output with a low-pass filter, we can remove some of that distortion and make the reof the EPROM.

The eight bits in the location come out in parallel, meaning all at the same time. But we want the bits one at a time, roughly 1/8000 of a second apart, since each bit represents one sample of the recorded voice pattern. (Over a space of two seconds there is a total of 16,384 samples or bits, which are stored in consecutive locations on the EPROM. The first eight bits are in memory location 00000000000, the next eight bits are in location 0000000001, and so on, up to the last eight bits, which are in location 111111111111.)

The job of splitting up the eight bits in one location into individual bits is handled by the 74LS151 multiplexer. This IC behaves like an SP8T switch which is continuously rotating, scanning the eight bits coming in from the EPROM



Fig. 3. Talking identifier diagram.

much like the distributor in a V8 car engine. It changes the parallel data coming into the multiplexer into serial data. The result, on pin 5 of the multiplexer, is a square wave which carries the frequency components of the voice but, of course, doesn't have any amplitude information because amplitude was never digitized. This signal is fed into an active low-pass filter which uses an LM3900 Norton op amp, and which cuts off at just under 4000 Hz. This provides the audio output.

about 8 kHz. The output of this oscillator is sent to pin 10 of a 4020 CMOS counter. nal which goes to the 4020 goes also to the B input, pin 1, of the 74LS93. Three of the flip-flops in this IC (called B, C, and D) count in parallel with the first three flip-flops of the 4020, and give us the missing signals.

imum count and reset themselves back to zero. At the instant that this happens, the Q14 output of the 4020 switches from a high level (near 5 volts) to a low level (near 0 volts). This signal goes to an unused section of the 74LS93 and turns on a fourth flip-flop in that counter; as a result, its QA output goes high. This signal is inverted into a low by another section of the 74LS132 and is fed back to stop the clock oscillator. As soon as the 2-second voice ID is done, therefore, the clock stops, all the counters (except the A flip-flop in the 74LS93) freeze at zero, and the IDer stops.

AUDIO OUT

The IDer is restarted by resetting all counters to zero with a positive pulse coming out of pin 3 of still another section of the Schmitt trigger NAND. This start signal could be generated externally, but for use with a 2-meter FM rig on 146.52 we have a 555 timer which automatically generates a very short reset pulse every 30 seconds or so. This pulse resets the A flip-flop in the 74LS93, which releases the clock and starts the ID process all over again. Connected to the clock control line is an NPN transistor. When the clock is running (that is, when the IDer is identifying), that transistor is turned on; when the IDer is off, so is the transistor. By connecting the collector to the push-to-talk (PTT) line of the rig, the IDer automatically keys the transmitter while it is identifying. This circuit is suitable only for

The rest of the circuit simply provides different addresses to the EPROM to scan through its memory and also drives the multiplexer.

This part of the circuit starts with one section of a 74LS132 quad, two-input NAND, Schmitt-trigger IC which, along with a 220-Ohm resistor and 0.4-uF capacitor, forms an oscillator which oscillates at

The 4020 is a 14-stage ripple counter which contains fourteen flip-flops. Since $2^{14} = 16,384$, this counter can count off 16,384 clock pulses. Since the clock frequency is about 8 kHz, if we start this counter at a count of 0, it will take approximately two seconds to count up to its maximum count. As it does so, it's counting off the 16,384 data bits which are being converted into an audio signal.

We really need 14 outputs from that counter to drive the EPROM address lines and the multiplexer. Unfortunately, to save on pins the 4020 provides only the 11 outputs from the 4th flip-flop (Q4) through the 14th flip-flop (Q14); the outputs of the first three flipflops are not accessible. So, we have a second counter, which is a 74LS93 binary counter. The oscillator sigThese three signals, on pins 11, 8, and 9 of the 74LS93, change very rapidly and continuously drive the multiplexer which, therefore, scans the output of the EPROM at a high speed (one bit every 1/8000 second).

The eleven bits from the 4020 have a lower frequency and, therefore, drive the address lines of the EPROM at a slower rate (one address every 1/1000 second). Thus, the EPROM feeds out a new group of eight bits every 1/1000 second. Since there are 2K such groups, this again takes about two seconds.

When the two seconds are up, the 4020 and 74LS93 counters reach their max-



Fig. 4. PC board, copper side.



driving the PTT line in small, transistorized transceivers. Those rigs which require large currents to drive a PTT relay may require an additional buffer transistor.

Although there are no potentiometers in the circuit, there are several components which may require adjustment. The 100k resistor in the active filter is chosen to provide a fairly small output audio level; if more audio signal is needed, it can be reduced to as low as 5k. Incidentally, do not use disc capacitors in the active filter circuit. Use good quality polystyrene or dipped mica caps. The oscillation frequency of both the 74LS132 oscillator and the 555 timer depends on the tolerance of the resistors and capacitors used. Since capacitors, especially, tend to have very wide variations, some trimming may be needed to get the right results. To vary the spacing between IDs, you may want to increase or decrease the capacitor value in the 555 timer circuit. If the 74LS132 oscillator runs too fast or too slow, the voice pattern in the EPROM will be scanned too fast or too slowly, with the same result as when a record is played too fast or too

slow. You may like the Donald Duck quality this gives, but for best results you should trim the RC values in this oscillator for the most natural speech sound.

The circuit layout is not critical, and almost any construction method will work, including wire-wrap and temporary prototype socket hookup. If desired, you can use the printed circuit board shown in Fig. 4. Fig. 5 shows the parts layout for the PC board.

The identifier needs approximately 100 mA of +5 volt power. This is provided easily by a three-terminal regulator. If you use the IDer in your mobile, simply include the regulator circuit of Fig. 6. Assuming a load current of 100 mA and a worst-case auto battery voltage of 16 volts, the regulator must drop 11 volts for a power dissipation of 1.1 Watts. With a good heat sink, all this can be dropped in the three-terminal regulator itself; by adding a 39-Ohm, 2-Watt resistor as shown in the circuit, however, we drop 3.9 volts across the resistor. This removes almost .4 Watts of heat from the regulator and dissipates it in the resistor instead. For applications that require even lower power (such as for battery-powered applications), total circuit power can be reduced even more by lifting the chip enable pin (pin 18) of the 2716 from ground and connecting it instead to pin 12 of the 74LS93. This disables the 2716 when the circuit is not identifying. The circuit still draws around 100 mA when identification is in progress, but cuts it down to less than half during other times.

"Recording" the EPROM

To digitize the audio signal, we need a filter to remove high-frequency components above 4000 Hz and a comparator circuit to





BETTER QUALITY TOUCH-TONE® DECODING

With this Touch-Tone® Decoder in your radio network, you can turn on transmitters, control attennae direction, and signal over public and private telephone networks.

The Teltone M-917 accepts pushbutton DTMF signals from a radio, telephone, or prerecorded tape.

Pin selectable, logic level, binary output can drive a Schottkey TTL gate, a low power transistor, a CMOS or MOS device.

It's compact, complete, field tested, and proven.







BECKMAN 3½-DIGIT MULTIMETER MODEL TECH 310

COMPLETE MULTIMETER CAPABILITY: DC VOLTS: 100 uV TO 1500 V AC VOLTS: 100 uV TO 1000 V rms RESISTANCE: 0.1 OHMS TO 20 MEGOHMS DC CURRENT: 100 nA TO 10 A AC CURRENT: 100 nA TO 10 A DIODE/SEMICONDUCTOR TEST FUNCTION. CONTINUITY FUNCTION - INSTA-OHMS [TM]. COMPLETE OVERVOLTAGE PROTECTION. LOW-POWER OHMS IN ALL RESISTANCE RANGES.

FULLY EQUIPPED WITH THE FOLLOWING: 9-VOLT BATTERY, A SPARE FUSE, SAFETY-DESIGNED TEST LEAD SET, OPERATOR'S MANUAL AND BECKMAN'S FULL ONE-YEAR WARRANTY.

OPTIONAL ACCESSORIES AND PRICES:

TECH 310 DIGITAL MULTIMETER \$140.00
DC-202 DELUXE CASE
VC-201 VINYL CASE
DL-241 DELUXE TEST LEAD KIT 10.00
TL-242 TEST LEAD SET [AS SUPPLIED]6.00
RF-221 RF PROBE

LaRUE ELECTRONICS 1112 GRANDVIEW STREET SCRANTON, PENNSYLVANIA 18509 PHONE [717]343-2124 sense the polarity of the input audio. This circuit uses another LM3900 quad Norton op amp and is shown in Fig. 7.

One op-amp in the LM3900 is used as an active low-pass filter with a cutoff frequency of just under 4000 Hz. This amplifier/filter has a small amount of gain but not enough to accept the weak signal from a microphone. It is designed for use with an external mike preamp or with the higher-level output of a tape recorder. I generally record the desired message on tape first and then feed the speaker output of the recorder to the audio input of this circuit.

A battery-operated recorder is best in this case, since with a high gain it is possible for hum to be digitized between words. Hum gets swamped out during speech, but when there is silence, the circuit works much like a volume compressor by boosting lowlevel sounds. Thus, a good S/N ratio is essential. The 10k volume control on the input helps to cut down excessive signal; its correct adjustment is important. The output of the filter is sent to another op-amp section of the LM3900, which is used as a slicer or comparator. The signal coming from the filter is sent to one input of this op amp while a reference current from the 10k zero-set pot is fed to the other. As the filtered audio output goes above or below the reference signal, the digital output from pin 9 switches between 0 and +5volts. The 10k zero-set pot should be adjusted so that with the audio input shorted to ground, the output is just on the verge of switching between 0 and +5 volts. With proper adjustment, positive audio peaks will clip the digital output one way while negative peaks flip it the other way.

For testing purposes, an audio amplifier/speaker combination can be connected to the digital output to monitor the signal after it has been digitized; I use an inexpensive Radio Shack signal tracer for this purpose. The digitized signal is supposed to be filtered before being heard, so this signal will sound excessively harsh, but it is good enough to give you an idea of whether the circuit is working.

Once we have the one-bit digital output, we must sample it at intervals of about 1/8000 second, convert the samples into 8-bit bytes, and store them. Before burning them into the EPROM, however, it is very convenient to be able to "play" them back to make sure that the volume controls have been set right and that we have the right voice segment. It also would be very convenient if in some way we could edit the digital code to eliminate any noise just before and after the call. In other words, it would be very convenient if we could store the message in RAM and read or modify it before it is permanently stored in EPROM. Building a special piece of hardware for just this purpose is difficult and expensive. Fortunately, most home or personal computers have an input and output port which could be used to input or output this one-bit digital signal and also have RAM which could be used to store the code temporarily. This makes the job almost trivial. To do this, you need a program which will input data, group bits together in sets of 8, and store them. In most cases, this program has to be written in machine or assembly language since most BASIC systems are not fast enough to take 8000 samples per second and process them.







Fig. 7. Audio-to-digital conversion circuit.

Obviously, the program will depend on the particular computer used, but as a starter, I'm including here three programs written for an SWTP 6800 system which are very useful.

Parallel input/output on 6800 systems is usually handled by an IC called a PIA or Peripheral Interface Adapter. Although this IC has twenty input/output pins, only two are used in this application—bit 0 of port A gets the input from the circuit of Fig. 7, while bit 1 of the same port feeds an audio amplifier/speaker combination which is used to listen to the recorded sound.

Program 1 is an echo program which is used only for testing. It inputs via bit 0, outputs the bit right back to bit 1 of the input/output port, and then waits for a short while to simulate the delay between samples. When everything is running correctly, the audio coming out of the computer will sound very similar to the audio you could hear directly at the output of the circuit of Fig. 7. (It, too, will sound harsh because of the lack of filtering.) The program starts by initializing the PIA to set up the correct bits for input and output. The main part of the program (starting at

* THIS PROGRAM INPUTS DATA FROM PORT A BIT 0 * * OF A PIA IN PORT 7, AND ECHOES IT TO BIT 1 * ************* PIADAT EQU \$8010 PORT A DATA/DIRECTION REG (801C) PIADAT+1 PORT A CONTROL REGISTER (801D) PIACTL EQU \$0100 ORG (0100) 0100 7F 801D START CLR PIACTL RESET PIA SET BIT 0=INPUT, BIT 1=OUTPUT 0103 86 02 LDA A #\$2 0105 B7 801C STA A PIADAT RESET BACK TO DATA 0108 86 04 LDA A #\$4 STA A PIACTL 010A B7 801D LOAD DATA FROM PORT A BIT O 0100 86 801C LOOP LDA A PIADAT SHIFT LEFT INTO BIT 1 ASL A 0110 48 STA A PIADAT OUTPUT TO PORT A BIT 1 0111 B7 801C 0114 8D 02 BSR WAIT LOOP GO BACK AND REPEAT 0116 20 F5 BRA * FOLLOWING WAIT ROUTINE INTRODUCES A DELAY # WHICH PERMITS SAMPLING RATE TO BE CHANGED INITIALIZE INDEX REGISTER 0118 CE 0010 WAIT LDX #\$0010 DECREMENT INDEX WAIT1 DEX 011B 09 REPEAT IF NOT YET ZERO WAIT1 BNE 011C 26 FD OTHERWISE RETURN RTS 011E 39

Program 1. Echo test.





Reader Service—see page 226

73 Magazine • December, 1980 171

			******	****	1903	********	******
			*				*
			* THIS	PROC	RA	M INPUTS	DATA FROM PORT A BIT O *
			* 0F A	PIA	I	PORT 7,	PACKS 8 BITS PER BYTE, *
			* AND	STORE	S	THE DATA	IN MEMORY LOCATIONS 1000 *
			* TO 7	FFF.			*
			*				*
			******	****		*******	*******************
(8	3016	.)	PIADAT	EQU		\$8010	PORT A DATA/DIRECTION REG
(8	3011	00	PIACTL	EQU		PIADAT+1	PORT A CONTROL REGISTER
(()10())		ORG		\$0100	
0100	7F	801D	START	CLR		PIACTL	RESET PIA
0103	86	02		LDA	A	#\$2	SET BIT 0=INPUT, BIT 1=OUTPUT
0105	87	8010		STA	A	PIADAT	
0108	86	04		LDA	A	#\$4	RESET BACK TO DATA
010A	87	BOID		STA	A	PIACTL	
010D	CE	1000		LDX		#\$1000	POINT TO MEMORY BUFFER ADDRESS
0110	60	08	LOOP1	LDA	B	#\$08	
0112	F7	0132		STA	B	BITCTR	COUNT 8 BITS PER BYTE
0115	4F			CLR	A		ERASE A ACCUMULATOR
0116	F6	801C	LOOP2	LDA	B	PIADAT	READ DATA INTO B ACCUMULATOR
0119	C4	01		AND	B	#\$01	HASK OFF EVERYTHING EXCEPT BIT O
011B	48			ASL	Α		SHIFT A ACCUM LEFT
0110	1 B			ABA			ADD NEW BIT FROM B TO A
011D	C6	1.0		LDA	B	#\$10	SET UP COUNTER FOR SAMPLING DELA
011F	5A		TIAK	DEC	B		DECREMENT B
0120	26	FD		BNE		WAIT	REPEAT IF NOT YET ZERO
0122	7A	0132		DEC		BITCTR	DO FOR 8 BITS
0125	26	EF		BNE		LOOP2	GET NEXT BIT
0127	A7	00		STA	A	0.X	STORE BYTE WHEN COMPLETED
0129	08			INX			INCREMENT INDEX REGISTER POINTER
012A	80	7FFF		CPX		#\$7FFF	CHECK FOR END OF MEMORY
0120	26	E1		BNE		LOOPI	REPEAT IF OK
012F	7E	EODO		JMP		\$EODO	RETURN TO MONITOR WHEN DONE

0132

(801C)

(801B)

FITCTR RMB

BIT COUNTER TO COUNT 8 BITS

Program 2. Input.

*********************************	***	**
*		*
* THIS PROGRAM GETS DATA FROM MEMORY		*
* LOCATIONS 1000-7FFF, UNPACKS IT INTO		*
* INDIVIDUAL BITS, AND OUTPUTS TO PORT	A	*
* BIT 1 OF A PIA IN PORT 7.		*
******	**:	**
PIADAT EQU \$801C PORT A DATA/DIR	RE	EGISTER
PIACTL EQU PIADAT+1 PORT A CONTROL F	REC	GISTER

WAIT1 loop. With the WAIT1 loop initialized (with the LDX instruction) to run 16 times (0010 hexadecimal), the total time between samples is 31 + (16)× (8) = 159 clock cycles.

In a typical SWTP computer running with a 900-kHz clock, each clock cycle takes 1.11 microseconds, so that the total delay between samples is 177 microseconds; this translates into a sampling rate of about 5600 samples per second, which is about the minimum that can be used for acceptable results. For 8000 samples per second, the LDX instruction should be changed to run the WAIT1 loop 10 times.

Once the echo test program reveals that the A/D conversion and the computer input/output circuitry is working correctly, Program 2 can be used to input data into the computer's memory, while Program 3 is used to output it back to the speaker. Both of these programs have a WAIT loop which provides some control over the delay between samples. There is some leeway here in adjusting this delay. If the number of samples taken per second is changed above or below 8000 (to increase playing time, for instance), the clock oscillator frequency in the identifier circuit of Fig. 3 also has to be changed to a similar value or the final output will have a pitch which is too high (like Donald Duck) or too low. Both programs are located in low memory, with the input program starting at location 0100 (hex) and the output program at 0180. They do not overlap and, therefore, can be in memory at the same time. Thus, we can input audio, store it in memory, and then output it right back.

through 7FFF to store the resultant digital data. This is a total of 28K of memory; at the rate of 1K per second, this can store a total of 28 seconds of sound. When Program 2 is finished, it returns to the monitor. Rather than calculate the sampling rate by computing the number of cycles per loop, etc., an easier way to adjust the WAIT loop is to note how long the overall program runs. If it runs exactly 1 second per K of memory used, then it is running at 8192 samples per second.

By changing the starting address (1000 hex) or the ending address (7FFF) in Program 3, we can "play" back just selected portions of the input. In this way, we can pick one of several versions of the same call, choosing the one that sounds best. This allows us to edit the data before it is stored into EPROM. Once you find the portion which sounds best, burn that portion into the EPROM and keep the rest of the EPROM data empty (an erased 2716 EPROM has a hex FF in every location). This will assure that no noise or sounds are in the EPROM other than the actual call.

(0180)	ORG	\$0180	
0180 7F 801D ST	ART CLR	PIACTL	RESET PIA
0183 86 02	LDA A	#\$2	SET BIT 0=INPUT. BIT 1=OUTPUT
0185 B7 801C	STA A	PIADAT	and the second second second
0188 86 04	LBA A	#\$4	RESET BACK TO DATA
018A B7 801D	STA A	PIACTL	
018B CE 1000	LDX	#\$1000	POINT TO MEMORY BUFFER ADDRESS
0190 C6 08 LD	OP1 LBA B	#\$08	
0192 F7 0184	STA B	BITCTR	COUNT 8 BITS PER BYTE
0195 86 00	LDA A	0.X	GET NEXT BYTE FROM MEMORY
0197 16 LO	OP2 TAB	. i.e.	TRANSFER IT TO B REGISTER
0198 48	ASL A		SHIFT A ACCUM LEFT 1 BIT
0199 59	ROL B		ROTATE & LEFT 3 BITS TO MOVE THE CURRE
019A 59	ROL B		BIT FROM BIT 7 (LEFT-MOST) INTO
0198 59	ROL B		BIT 1 (SECOND FROM RIGHT)
0196 64 02	AND B	#\$02	MASK OFF EVERYTHING EXCEPT BIT 1
019E F7 801C	STA B	PIADAT	OUTPUT TO PIA
0141 66 08	LDA B	#\$08	SET UP COUNTER FOR SAMPLING DELAY
01A3 5A WA	IT DEC B		DECREMENT B
0144 26 FD	BNE	UATT	REPEAT IF NOT YET 7FRO
0146 ZA 0184	DEC	BITCTR	DO FOR 8 BITS
0149 26 EC	BNE	LOOP2	IF BIT COUNTER NOT ZERO
01AB 08	INX		INCREMENT INDEX WHEN BYTE IS DONE
01AC BC 7FFF	CPX	#\$7FFF	CHECK FOR END OF MEMORY
01AF 26 DF	BNE	LOOPI	REPEAT IF OK
01B1 7E E0D0	JMP	\$EOD0	RETURN TO MONITOR WHEN DONE
			PTT COUNTED TO COUNT O FITTO
0184 BI	ILIK KMB		BIT LUUNTER TU LUUNT 8 BITS

Program 3. Output.

the statement labeled LOOP) loads a bit from the PIA, shifts it left from bit 0 into bit 1, and outputs it. Then it branches to a WAIT subroutine for a short delay, after which it branches back to LOOP.

For experimental purposes, it's important to be able to calculate how many samples are taken per second. This is done by computing how many computer clock cycles are required for each instruction in the loop. In Program 1, the main loop takes 31 clock cycles plus 8 cycles for each repetition of the

The programs are written for a 32K computer and use locations 1000 (hex)

Conclusions

While this talking identifier won't win any awards for hi-fi quality, it is perfectly understandable and fulfills its purpose well. It also gives you a chance to experiment with speech reproduction via digital means. In addition, it's a lot more satisfying to build such a device from commonly-available ICs than to go out and buy an expensive synthesizer chip or system. Why don't you try it?

So, if you ever hear something grumble "K2OAW" on 146.52 as I speed by your house on the nearby Interstate, maybe you'll be able to turn on your own IDer and have it come back to me.







MICROWAVE ANTENNAS&KITS	SLOTTED ARRAY
MICROWAVE TRANSISTORS	ANTENNA → 378 • 2100 + /- 100 MHz • 16 dBi gain
MICROWAVE DIODES	H or V polarization Type N connector Low wind loading
PARABOLIC REFLECTORS	 Alodined 24"×5"×1" Mast mount

0.1	0000	
S-1	\$232.8	s0 2 Meter
S-1T	\$260.9	10 With Ione Pa
S-2	\$315.0	0 220 MHz
S-2T	\$359.0	00 With Tone Pa
S-5	\$264.5	50 2 Meter 5 Wa
S-5A	\$299.9	15 With Tone Pa
AZDEN PCS-20	000	
2 Meter	\$259.95 MAR	S CAPABILITY WITH MOL
AZDEN PCS	2800	
10 Meter		\$259.5
SWAN ASTR	to 1028X	
160/10 M	leters	\$995.
Astro 150)	\$785.
100 MX		\$589.
TEN-TEC OMNI	C NEWI	\$998.
TEN-TEC OMNI	D	\$795.0
Six other	s lower price	d Limited Quantities.

adia fim

-house

ALUMINUM LEED-UUUNO

Your source of supplies for the fastest growing field of communications. Here is a low cost entry into the fascinating area of microwave technology. We offer a complete line of antennas, receivers, pre-amps, power supplies, etc Call or write for details.



DATA SERVICE COMPANY V 346 3110 Evelyn Street Roseville, MN 55113 612-636-9469

Satellite TV FOR THE HOME

Sick of Network TV?

Our receiver lets you get over 75 channels of television directly from earthorbiting cable TV satellites!: HBO, Showtime, super stations, sports and movies from around the world.



We don't just sell information! We Manufacture Hardware!

Our 94-page catalog and information book tell the whole story! Inexpensive dishes, high profeeds, computer aiming software! Specs, kits and more! Send \$7.95 today!

24-hour C.O.D Hotline (305) 339-7600



SPACECOAST RESEARCH Dept. S, P.O. Box 442, Altamonte Springs, FL 32701



- Commercial grade
- Mast mount

Postpaid.....\$35

Optional small corner reflector narrows beam width to 14×14 degrees; increases gain 4 dBi. FREE PLAN.

1508 Ports O'Call Plano, Texas 75075



. Covers 100 to 179.999 MHz in 1 kHz steps with thumb-wheel dial . Accuracy .00001% at all frequencies . Internal frequency modulation from 0 to over 100 kHz at a 1 kHz rate . Spurs and noise at least 60dB below carrier . RF output adjustable from 50 to 500mv across 50 ohms . Operates on 12vdc @ 1/2 amp . Price \$299.95 plus shipping.

In stock for immediate shipping. Overnight delivery available at extra cost. Phone: (212) 468-2720. / 311

VANGUARD LABS 196-23 Jamacia Ave. Hollis, NY 11423

GBTO IMMETER **10 METER CONVERSION KITS** FOR CB RADIOS AM-FM & SSB

- Kits for over 300 Models of CB Radios
- Low Cost from \$10.00 Easy to Install with All Instructions Tune-Up Procedure Alignment
- KITS FOR MOST POPULAR UNITS Over 5,000 Satisfied Customers
- Write or Call Today for Our Free 1980 Catalogue

AMERICAN CRYSTAL SUPPLY COMPANY PO Box 638 W Yarmouth, MA 02673 (617) 771-4634 17

Dear Subscriber:

73 Magazine does not keep the subscription records on the premises, therefore, calling the Peterborough offices doesn't solve your subscription problem.

To quickly solve your problem please send your most recent address label and a description of the problem to:

> 73 Magazine Subscription Department PO Box 931 Farmingdale, NY 11737

Please allow the subscription department at least two weeks for an answer or a solution to your problem.

Thank you and enjoy your subscription.

Sincerely,

Debra L. Boudrieau Circulation Manager



Selling 73 Magazine, the ham radio magazine



Let us know 8 weeks in advance so that you won't miss a single issue of 73 Magazine.

Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us to serve you promptly. Write to:

73 Magazine Subscription Dept. P.O. Box 931, Farmingdale NY 11737

Address change only
 Extend subscription
 Enter new subscription

□1 year \$25.00 □Payment enclosed □Bill me later

If you have no label handy, print OLD address here.

Name		Call	
Address	Cher State Only 1910		1
City	State	Zip	
	print NEW addre	is here:	
Name	EDITAR CRYSTAL STR	Call	
Address	1.50.02	280	10
City	State	Zip	

that offers quality and quantity, brings the ham into your store. Once through the door you can sell him anything.

Our dealers are telling us that "73" outsells them all...so call today and join the dealers who make money with 73 Magazine.

For information on selling 73 Magazine call 603-924-7296 and speak with Ginnie Boudrieau, our Bulk Sales Manager. Or write to her at:



CORRECTIONS

May, 1980

"A 'Short-Yard' Antenna for 40/75-fits where others won't"

The spacing between the length of vertical copper or aluminum wire shown in Fig. 1, page 78, should be 8 inches, not 8 feet!

June, 1980

"Down with Interpolation-a digital display for the Triton and others"

On page 36, Fig. 1, the pin 6 of the 74196 shown going to +5 V should be pin number 10. On page 39, column 2, line 2, pins to check on the 7490 should be 8, 9, and 11.

If the readout displays changing random figures, the crystal is probably not oscillating. When ordering crystals, it is always a good idea to send along a schematic of the circuit, with values indicated, in which the crystal will be used.

As stated in the caption for Fig. 3, page 38, there are frequencies other than 409.6 kHz which can be used. If your readout works on all bands except 28 MHz, it is probably the 74C925 which is at fault. This chip is specified for a minimum response of 2 MHz-typically 4 MHz. Since the mixer frequency for the 10-meter band is 2.1 MHz, your 74C925 may have a response of less than this.

what is shown. We apologize for the error in the author's call. It should be WB9SFC.

"The Sweet Sounding Probe"

The reference designators for the ICs shown in Fig. 1, page 84, were omitted. The 555 is U1; 741 is U2; and 78L12 is U3.

August, 1980

"On Ten FM-home of the free, land of the brave"

I'd like to add a few words of clarification to my article. The best source I've found for the CB circuit boards is Surplus Electronics (Miami, Florida) who advertise in 73. Specify the PTBMO36AOX CB circuit board with 40-channel switch. These boards contain the easy-towork-with PLL02A frequency synthesizer PLL chip, rather than some odd-ball chip for which there is no readily available data, and are of better quality than other boards I've seen. Sam's CB series of Photofacts, Nos. CB-129 (Midland 13-888B) and CB-131 (Hy-Gain IX), are the best sources of schematics and technical information for these boards.

October, 1980 "NASA Satellites You Can Use-with permission, of course"

In the math box on page 52, the calculations for Washington DC should have indicated that X, the difference between satellite longitude and site longitude, was obtained using Washington DC's west longitude of 77.2 degrees.

> Joseph D. Novak K4OVK Vienna VA

Map of States Worked

A calming note to our readers in British Columbia and Michigan: No, Vancouver Island has not been traded for the Upper Peninsula.

November, 1980

"Direct Conversion Lives-excitingly simple receiver project"

There are three corrections to this article-the easy ones first:

On page 66, Fig. 3, pin 6 on the LM380 is shown in two places. The pin 6 shown as being grounded should be pin 4.

On page 68, column 3, 8 lines

The capacitors of this doubletuned circuit are two gang-tuned 350-pF variable capacitors (700 pF total) and the inductances are so chosen such that the 3.5-MHz resonance occurs with the plates nearly fully closed. Resonance at 7.0 MHz then occurs with the plates nearly fully open.

Audio Amplification

After some trials with other circuits, I agree with PA0SE that an FET audio amplifier is about the best device for a first audio stage after the mixer. The audio transformer, T2, is a 1k:10k, which is far from ideal, but it was the only one available locally. Far better would be one with a 50 Q: 10k impedance ratio, as the output impedance of the MD108 is 50 Q. The final audio amplifier, the LM380, provides plenty of audio and is better than the LM386 which I used at first.

"Tune In the Wind-a do-it-yourself hot-wire anemometer"

On page 81, column 4, line 3 would make more sense if "about" were to be replaced with "above."

Brooks Carter W4FQ Irmo SC

July, 1980

"ADDSCAN-now you can be two places at once"

In Fig. 2, page 52, the polarity of C1 should be reversed from

John F. Sehring WB2EQG **Oradell NJ**

September, 1980 "The Penultimate CPO-a nondiscrete LSI device"

Pin numbers for IC2b were inadvertently left out in Fig. 2, page 62. The missing numbers are shown in the accompanying diagram.



Revised Fig. 2, "The Penultimate CPO."

from the bottom, mH should be uH.

Now for the big one! Also on page 68, insert the following just before Audio Filters in column 1.

The VFO and Buffer

I used separate vfos for 80m and 40m and after trying several circuits, I chose the series-tuned Clapp oscillator because of its good stability. The output part of the vfos and the buffer are exactly like that used by PA0SE. His was a good design and I find no need to change it. It has one weakness, though: Because it is a broadband buffer, the second harmonics of the vfos also appear at the mixer. This is especially true of the 80m vfo where the second harmonic of, for example, 3.6 MHz mixes with a very strong commercial station on 7.2 MHz. I tried a 40m seriestuned trap from the drain of the FET in the 80m vfo, but it cured the problem only partially. (This also was the case without rf amplification at the front end.) I solved this problem by changing the single-tuned input circuit as used by PA0SE to a doubletuned one as shown in Fig. 3.

"The Odd Couple-CASEY/1 tackles OSCAR's telemetry"

In column 4, page 110, the last two lines of the article refer to the article listed in reference 2. The reference number was omitted from the last line. Also, please note my new address.

> **Rich Casey WA9LRI** 1818 Hemlock Garland TX 75041

"Be Prepared!-30 meters for the FT-101B"

Please note a change in my address.

Mark H. Monson EL5G/KB8NO Box 1046 Monrovia, Liberia

"New Weather Eye in the Skya primer on NOAA's TIROS"

In Table 1(b) on page 177, subpoint latitude for 76 minutes after crossing should be -81.1, not -91.1.

On page 181, column 1, the first sentence of step 3(A) should read, "Break the connection between the vertical size pot and the input line of the vertical deflection amplifier."

73 Magazine · December, 1980 175

Children of Mary	OPOT PROPERTY
1980 INDEX	

AMPLIFIERS

They Don't Make 'Em Like They Used To	108	Jan
Shoes and Socks for the IC-502N4QH	66	Apr
A Final SolutionW4ANL	125	Jul
The Two-Meter MonkeyKL7GLK	84	Sep
A Conversion with GustoWB2WIK	130	Sep

ANTENNAS

The Procrastinator's Special:

W6TKA/0	106	Jan
W6TYH	36	May
W8HXR	44	May
WB5SFB	48	May
WA4JQS	50	May
rW9YFG	52	May
W9NMX	58	May
W2JTP	60	May
W8HXR	61	May
W4UCH	62	May
W9CRC	78	May
Staff	80	May
WB2MYT	83	May
WA4LLE	84	May
K4TWJ	104	May
KA8CGE	122	May
W6WDF	131	May
K1QPS	132	May
K4IQJ	134	May
WA4JQS	136	May
WA5TDT	138	May
WB6MMV/7	146	May
SVØWX	148	May
WA8WTE	70	Jul
AB5S	134	Jul
WA4PYQ	68	Sep
WB3ICL	116	Sep
W9HBF	88	Oct
W9HBF	179	Oct
N6RY	72	Dec
W8HXR	110	Dec
	W6TKA/0 W6TYH W8HXR W85SFB W9YFG W9YFG W9YFG W9YFG W9YFG W9YFG W8HXR W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W9CRC Staff W82MYT Staff W84LLE Staff W8WTE SV0WX WA4JQS WA4JQS WA5TDT WB6MMV/7 SV0WX W86MMV/7 SV0WX W85TDT WB6MMV/7 SV0WX W86MMV/7 SV0WX W86MMV/7 N6RY	W6TKA/0 106 W6TYH 36 W8HXR 44 W85SFB 48 W95SFB 48 W95SFB 48 W9YFG 52 W9NMX 58 W9YFG 52 W9NMX 58 W2JTP 60 W8HXR 61 W8HXR 61 W9CRC 78 Staff 80 W9CRC 78 Staff 80 W82MYT 83 W9CRC 78 Staff 80 W8WTE 70 K4IQJ 134 WA4JQS 136 WA4JQS 136 WA5TDT 138 WB6MMV/7 146 WA5TDT 138 WB6MMV/7 146 WA4JQS 134 WA4JQS 134 WA4JQ

Goin' Mobile-equipment for		
air-conditioned gypsiesKL7IPE/DA1SM, DF7NM	76	Sep
CB to 10-part XXIX:		
put that Hy-Gain CB board to useW1BG	102	Sep

CONSTRUCTION

Go-CartW4MEA	134	Feb
The PL-259 ConnectionAC5P	73	Apr
The IC OutenerWA4WDL, WB4LJM	150	May
Constructing QRP Dummy LoadsW10LP	64	Jun
PC Artwork Made EasyW3HIK	80	Jun
Rubber Thumbs and Pilot LampsK3MPJ	114	Jun
A Proper Pedestal for PCBsStaff	120	Jun
Silence is GoldenPowell	91	Jul
Meet the Little GiantK4JHN	46	Aug
Load a Lawn ChairWB5PPV	60	Sep
PC Boards—A Photographic MethodWB5HGR	104	Oct
Cheap Connectors for Half-Inch HardlineWD4LWC	100	Dec

CONTROL

Personalize Your Repeater with a Voice IDK9EID	92	Jan
Personality Plus for your Repeater	136	Jan
Trouble-Free ID TimerWA8HEB	76	Feb
Good-Bye to Autopatch HasslesWB2LEI/4	30	Mai
Repeater Time-Out WarningKA6A	120	Jul
Get Out and VoteWA9FDP/WR9ACD	64	Sep

CORRECTIONS AND FURTHER INFO

"The MICROSIZER: Computerized Frequency		
Control'' (October, 1979)	146	Jan
"Yes, You Can Build This Synthesizer" (October, 1979)	146	Jan
"Son of Keycoder" (November, 1979) "What Do You Do When Your Rotator Dies?"	154	Feb
(November, 1979)	147	Mar
"The Dollar-Saver DVM" (January, 1980)	147	Mar
"Build this \$50 Mini-Counter" (December, 1979)	147	Mar
"The Dollar-Saver DVM" (January, 1980)	132	Apr
"An LED Display for the HW 2036" (October 1070)	122	Apr

CB CONVERSIONS

CB-to-10 FM—best conversion yet?		
	117	Jan
CB-to-10 FM Continued—		
another way to join the fun on 29.6WB2EQG	42	Feb
CB to 10-part XXII:		
more talk power for the TRC-11N4APN	38	Ma
CB to 10-part XXIII: the Sears Roadtalker 40W6SZS	58	Ma
CB to 10-part XXIV: Penney's SSB rigWA4UUV	100	Apr
CB to 10-part XXV:		
using those surplus 40-channel boardsAF8B	58	Jur
CB to 6-		
convert a 49-MHz HT into somethingW9CGI	148	Jur
CB to 10-part XXVI: the Cobra 132WA1UQC	72	Jul
CB to 10-part XXVII: new life for SSB CB rigsN6SD	108	Jul
CB to 10-part XXVIII:		
double your channels in SSB conversionsWB2EQG	122	Jul
On Ten FM—		
home of the free, land of the braveWB2EQG	52	Aug

"An LED Display for the HW-2036" (October, 1979)	132	Apr
"You Can Watch Those Secret TV Channels"		
(August, 1979)	132	Apr
"Neat Readout for the 2036" (March, 1980)	159	May
"Lab-Quality Hi I Supply" (March, 1980)	195	May
"A Micro-Controlled Ham Station" (April, 1980)	180	Jun
"The Paper, the Station, and the Man" (February, 1980)	180	Jun
"Antenna Engineer" (May, 1980)	160	Jul
"Fun with Foozle" (June, 1980)	160	Jul
"Prefix Challenge" (June, 1980)	160	Jul
"Cheapy Scanner for the Memorizer" (April, 1980)	166	Aug
"Down with Interpolation" (June, 1980)	166	Aug
"Electronic Dice—A Family Pleaser" (June, 1980)	166	Aug
"The Stolen Rig Retriever" (June, 1980)	166	Aug
"A 'Short-Yard' Antenna for 40/75" (May, 1980)	175	Dec
"Down with Interpolation" (June, 1980)	175	Dec
"ADDSCAN" (July, 1980)	175	Dec
"The Sweet Sounding Probe" (July, 1980)	175	Dec
"On Ten FM" (August, 1980)	175	Dec
"The Penultimate CPO" (September, 1980)	175	Dec
"NASA Satellites You Can Use" (October, 1980)	175	Dec
"Map of States Worked" (October, 1980)	175	Dec
"Direct Conversion Lives" (November, 1980)	175	Dec
"Tune In the Wind" (November, 1980)	175	Dec
"The Odd Couple" (November, 1980)	175	Dec
"Be Prepared!" (November, 1980)	175	Dec
"New Weather Eye in the Sky" (November, 1980)	175	Dec

CW

Sound-Sensitive CW Sender	W2GZ	106	Apr
QRQ, QRS-By the Numbers!	W7BBX	50	Jun
Check Chirp with a Choke	.WA2MEL/6	111	Jun
Build the ZL Paddle	ZL2GA	118	Jul
The Confidence Builder	WB4TYL	134	Sep
Double-Duty CW Keyboard	K1GN	126	Dec

EQUIPMENT MODIFICATIONS

A Brasspounder Improves Heath's HR-	1680KA5N	76	Jan
The Nearly Perfect WE-800	K10TW	96	Jan
Catch You on the Flip-Flop	K7ACN	132	Jan
Add 'Em Up: An IC-22S Programmer	AA4RM	103	Feb
Gone But Not Forgotten	AD5X	48	Mar
Neat Readout for the 2036	K3GRX	62	Mar
Modernize That Boat Anchor!	AD5X	66	Mar
Cheapy Scanner for the Memorizer	WA2ORU	38	Apr
Hi-Fi CW for the TS-820	КЗНВР	70	Apr
SWLing? Try This Souped-Up SSR-1	G3WDI	92	Apr
Off the MARS with the S1	K5EDS	96	Apr
Down with Interpolation	W4FQ	36	Jun
The Phoenix Fix	WA3AJR	48	Jun
Adding a Scanner to Your 2m Rig	WA8HEB	54	Jun
The IC-211 Cookbook	K3VGX	68	Jun
Priority Frequency Power-Up			
for the FT-227R	WA1AUM	90	Jun
10 Meters for the SB-221	WA2KSM	134	Jun
Outboard Power for the 820	KL7GRF/6	146	Jun
Digital Boat Anchor	WB1ASL	152	Jun
Top-Banding the DX-60B-part I	WB1ASL	44	Jul
FT-227 Update	WA1GPO	74	Jul
Triton IV Quick Trick	AG4R	126	Jul
Who Needs SSB?	K8JS	130	Jul
How to Make a Good Scanner Better	WA4PYQ	68	Oct
Gilding the Lily	WB4HLZ	188	Oct
Mike Mods for the KDK-2016A	WB9WNU	190	Oct
Getting the SB-220 to Idle	W9RY	197	Oct
Be Prepared!	KB8NO	156	Nov
Top-Banding the DX-60B-part II	WB1ASL	64	Dec
Clean Sweep for the FT-221	WBØLLP	82	Dec
Scanner Magic for Heath's 2036	WA4BZP	88	Dec
Single-Tone Paging for Wilson HTs	W4BF	112	Dec

GADGETS

A Better Car	Regulator	Gelsinger	58	Apr
--------------	-----------	-----------	----	-----

How to Write a RTTY ProgramWA4FMZ	46	Jan
The Perfect Morse MachineWA5VQK	53	Jan
Microcomputers and Your Satellite		
Station-part IWB8DQT	63	Jan
Microcomputers and Your Satellite		
Station-part IIWB8DQT	86	Feb
Design Practical PLL and Timer CircuitsN2RG	92	Feb
DUPECALLfor Your Next ContestK4TSY	96	Feb
COMPULOG: A Multi-Purpose		
Record KeeperWA1ZSE	74	Mar
Computer System I/O InterfaceVE3CAF	78	Mar
Number Fun on your MicroW3KBM	80	Mar
Baudot Message FormatterW6RLL	82	Mar
A Micro-Controlled Ham StationW4UCH/2	76	Apr
CW and the TRS-80WB7TUG	80	Apr
Breakthrough! A Computerized		
Antenna Rotator!	86	May
Antenna Engineer	96	May
SWTP/H14 Get-TogetherWA8GRG	100	May
Computerize Your Contest PaperworkWA8WIA	94	Jun
Emulate an ElephantVE6BB	98	Jun
Prefix Challenge	104	Jun
Welcome to the '80sK3PUR	92	Jul
A Soft Approach to LoggingMinor	100	Aug
RTTY with the H8W5IFQ	106	Aug
A Programmer's Potpourri	90	Sep
Late Check-Ins Come Now	120	Oct
A Computer-Controlled		
Talking Repeater-part IWA6AXX	124	Oct
Murphy's Own OSCAR Tracker K8BG	132	Oct
The Odd Couple WA9I RI	110	Nov
PL Tones from a KIM-1 WD8CHH	112	Nov
Super Duper for Field Day. WB5KV7	114	Nov
A/D Converters Explained! WB4UHY	122	Nov
A Computer-Controlled Talking		
Repeater-part II. WA6AXX	132	Nov
	1 to the	1101

1/0

Field-Strength FeverW6DOB	98	Apr
The Stolen Rig RetrieverWB6KBM	60	Jur
Electronic Dice-a Family PleaserW7BBX	82	Jur
Fun with FoozleW7BBX	84	Jur
Listen in Secrecy		
with a Giant Inductive LoopZL2AMJ	124	Jur
Transform Noisy Fluorescents	64	Jul
The Penultimate CPON6HI	62	Sep
The Two-Hour Audio AmpK7HKL	118	Sep
The Little ThinkerWB4RXB	126	Sep
UndertonesW4FEC	56	Oct
Field Strength for FreeStaff	82	Oct
Stay Cool with TMWB2EQG	144	Oct
Tune In the WindVE7DKR	80	No
An Amp for QRPp AddictsWA0RBR	68	Dec
Build a Talking Digital IDerK20AW	162	Dec

HISTORY

The Paper, the Station, and the ManW3CFC	54	Feb
Albert and his Momentous TheoriesLutus	116	Feb
The History of Ham Radio-part XIW9CI	54	Mar
Early Radio Detectors-A Backward GlanceW5JJ	66	Jul
"That's the Way It Was "	78	Jul
Notes from Big Sky CountryK6CK	36	Aug
Those Fabulous FiftiesW1FK	64	Aug
Over ThereW9IWI	86	Aug
One Man's Magazine: Twenty Years of 73N1AUI	146	Oct
Who Really Invented Radio?WB2NEL	36	Dec

HUMOR

Future Rig and RigamaroleW6HDM	44	Mar
Let's QSY to .52WB2RVA	44	Jun
A Transistor for True BelieversWB7CMZ	142	Oct
How To Be An AmateurW2ZGU	156	Oct
Some Guys Make ItK2ORS	168	Oct

Sixteen Channels of Digital DelightWB4UHY	132	Dec
A Computer-Controlled Talking Repeater-		
part IIIWA6AXX	138	Dec
Make a Microcomputerist SmileAL7G	148	Dec

MISCELLANEOUS

DX with a Difference: the Utility StationsWA3EOP	40	Jan
Home-Brew Holders for Icom PortablesKH6IAA	131	Jan
Sunspot Predictions for 1980WA3NKP	47	Feb
Excavation Litigation	72	Feb
On the Trail of the HamburglarWØEX	116	Mar
SunspotsWhat Do They Mean?G3WDI	32	Apr
More on Jammer NabbingWB0CMC	36	Apr
Hams on the Trail of UFOsK8NQN	68	Apr
The Demise of Component StoresVE3FLE	88	Jun
Another Place, Another TimeAnon.	136	Jun
The Rites of SpringN1AUI, WB8BTH, KA1HY	30	Jul
All About Coordinated Universal TimeWA7NEV	80	Jul
Ham Economics: Selling Used GearK5CA	124	Jul
Like to See My Etchings?W6OJJ	132	Jul
In Profile: Dick Bash KL7IHPN1AUI	40	Sep
Escape from Mt. St. Helens!W7WFO	34	Oct
Sheila Ran!WB0IFF	38	Oct
The First Man in Space Was a Ham	42	Oct
Win Friends for Your ClubWA5TUM	76	Oct
Welcome Back, Barry!	52	Nov
Return to Shangri-laW1QMS	58	Nov
An Even Better IC TimerWA0PBQ	46	Dec

MOBILE/PORTABLE

The Soft Mount	.W2QFC	32	Aug
Power x 2 Plus!	WA5TDT	122	Sep

NEW PRODUCT ARTICLES

The Europa-B	Two Meter	TransverterG3ZCZ	110	Jan
--------------	-----------	------------------	-----	-----

73 Magazine • December, 1980 177

Going 2m All-Mode with Yaesu's FT-225RDW6OJF Tempo S1 2-Meter PortableWB9HRV	72 118	Ap Ju
Tempo S1 2-Meter PortableWB9HRV	118	Ju
Those Hamtronics Kits		
How Can You Use Them?WA4PYQ	130	Ju
The Don Nobles DescramblersWA4PYQ	148	Ju
Inside Radio Shack's Digital ReceiverW4PGI	80	Se
Automated Operating Comes of AgeK3CMY	170	No

Azden PCS-2000 Transceiver	26	Jan	Hamtronics Converters and Amps	31	Aug
DSI 5600A Frequency Counter	26	Jan	Collins/Rockwell KWM-380 TransceiverK4TWJ	31	Aug
AEA Morsematic Keyer	26	Jan	Kenwood R-1000 General Coverage Receiver		
EP-8 Pocket Shortwave Receiver	147	Jan	WA4PYQ	162	Auc
OK Machine and Tool Mini-Shears	147	Jan	Peripheral People Software	162	Auc
Curtis IM-480 Kever	147	Jan	KLM 40-10V Multiband Vertical.	163	Auc
Ten-Tec Model 299 Talking Counter	148	Jan	RSGB World Prefix Map	163	Auc
Ontoelectronics Frequency Counters	148	lan	Swan Astro 102BX Transceiver N8BK	32	Sen
Discoil HE Mobile Antenna	24	Eob	Con-puter 1 Memory Kever	34	Sen
Info Tech M 200E Tri Mode Convertor WAARYO	24	Ech	loom IC 2AT Synthesized Handia Talkia KATWI	24	Son
Vacu ET 207P HT (2m)	145	Feb	Coundrower CD100 Creech Processor NODK	34	Sep
Del 50 Ha 500 MHa Dookot Exeguerou Countere	140	Feb	Soundpower SP100 Speech ProcessorNork	30	Sep
DSI 50-HZ-500 MHZ POCKET Frequency Counters	14/	Feb	Microcraft RTTY Reader.	37	Sep
Heath 1680/1681 CW Receiver/Transmitter	148	Feb	Instant Software "QSL Manager" SoftwareN8RK	38	Sep
Fox-Tango Crystal Filters	148	Feb	Circuit Specialists Repeater "Tail Chopper"	38	Sep
Fotografix Magnetic Signs	148	Feb	Grove Enterprises Sounds of Shortwave		
Hamtronics Catalog	149	Feb	CassetteN8RK	38	Sep
OK Machine and Tool BW-2630 Wrapping Tool	149	Feb	Hy-Gain HG-70HD Tower and Accessories	39	Sep
Bullet Zulu Clock Kit	149	Feb	Archer Engineer's Notebook	160	Sep
Selectone Multi-Frequency Encoder	149	Feb	P. C. Electronics TVC-4 ATV Downconverter	30	Oct
Radio Shack Wireless Remote Control	26	Mar	Heathkit HDP-1473 Allband Vertical	30	Oct
Heath 2-kW Antenna Tuner	26	Mar	Azden PCS-2800 10-Meter FM TransceiverW1GV	30	Oct
Clutterfree Modular ConsolesWA4PYQ	26	Mar	Hickok LX 304 Digital VOM	32	Oct
Macrotronics M650 RTTY Interface UnitW8FX	27	Mar	Radio Shack Safe House Alarm SystemN8RK	32	Oct
MFJ Phone Patches. WA4PYO	145	Mar	Ten-Tec Omni-C Transceiver	242	Oct
AEA KM-1 Kever	145	Mar	Spectrum Communications SCB4000	And The	001
Kantronics Field Day Morse/RTTY Reader	146	Mar	LIHE Beneater	242	Oct
OK Machine and Tool Prototype Boards	146	Mar	ME I Model 959 Receiver Antenna	242	001
Skytec CW Speaker KATW I	147	Mar	Tuner/Preamplifier WAAPVO	243	Oct
KI M KT-34XA Triband Vagi	28	Apr	Hamtronics CA Series Receiving Converters	240	Oct
Prot Mose VHE Transmitter WAADVO	20	Apr	Drake B7 Conoral Coverage Communications	240	UCI
OK Machine and Tool Just Wrap Kit	20	Apr	Drake n/ General Coverage Communications		hler
DopTrop CLA 1000 Lippor Amplifier	20	Apr	Receiver	32	NOV
Veeth Demete Ceev Culter	28	Apr	Radio Shack DX-302 General Coverage		
Reath Remote Coax Switch	29	Apr	ReceiverWA4PYQ	32	No
Bird Digital Hr wattmeters	29	Apr	Mirage Model B23 2-meter Amp	36	No
Bullet SE-01 Sound Effects GeneratorN4XX	162	Apr	Jameco JE610 ASCII-Encoded Keyboard Kit	36	No
MS COMM BIA-1 RITY Control Center	26	May	Grove Enterprises VHF/UHF Scanner Beam	36	No
Azden PCS-2000 2m FM TransceiverWA00KV	190	May	Heathkit Frequency Counter Line	37	No
Pace Communicator MX HTKA5ECP	190	May	International Crystal TV-4300 Satellite Receiver	38	No
Kenwood TR-2400 HTN6HI	191	May	COMMSOFT RTTY89 Software	38	No
Spectrum TTC100 Decoder/Control	192	May	Teltone DTMF Decoder	38	No
Telex HDR300 Rotator	192	May	Kantronics Field Day 2 RTTY ReaderWA4PYQ	38	No
Hustler G7-220 220-MHz Base Antenna	192	May	R. H. Johns Current Shunts for DMMs	40	No
Heath SA-7010 Triband Yagi	193	May	Palomar Engineers Antenna TunersN8RK	40	No
Communications Specialists TE-12P Encoder	193	May	ETCO Catalog	41	No
Regency K500 Programmable ScannerWA4PYQ	193	May	Radio Shack Space-Saver DeskKBØNV/1	41	No
Microcraft Morse-A-Word Code Reader	194	May	MFJ Model 1020 Active AntennaWA4PYQ	196	No
AEA Morsematic KeyerWB8BTH	22	Jun	Shure Model 444D Microphone	197	No
Global Specialties Wire Kit	23	Jun	Micro-80 Amateur Radio Theory		
Amerex Unibox Packaging Components	23	Jun	Review SoftwareKA0BYS	197	No
Grove Enterprises Frequency Directory	23	Jun	AEA Model CK-1 Electronic Kever	32	Dec
Ten-Tec Argonaut 515.	166	Jun	Jameco Desk-Top Enclosures	32	De
Icom IC-2A HT. WB6TOV/1	166	Jun	Heath IC Timers Self-Instruction Program	186	De
Technical Clinic Ham Scan-2 WD8.II W	166	Jun	Hamtronics VHE EM Exciter Kit	186	De
THS Electronics PA 1-10 2m Amn	168	Jun	Centurion Antennas	186	De
Larsen Kulduckie Antennas	168	Jun	Gilfer NRD 515 Allband Pageiver	100	Del
Xitex LIDT-170 TU	160	lun	Sony ICE 2001 Conoral Coverage Desciver MIA (DVO	100	De
Robot Model 650 Scan Converter	109	Jul	BRW T2ED Eelded Dinele	187	De
Micro Control Specialtics Mark 200 Demoster	20	Jul	Karatron SC 76 Sacaning Madula	188	De
Top Top Heroulog Linears Ame	20	Jui	Kaletron SC-76 Scanning Module	188	De
P & W PC 1 Palue	26	Jui			
Trac Model TE 200 Kaves	28	Jul	OPERATING	New Con	1
Trac Model TE-292 Keyer.	28	Jul	QRP from Canton IslandKH6GB	63	Fel
Kantronics Signal Enforcer Audio Filter	28	Jul	Hurricane!	68	Ma

6m Fun with the FT-625RDW60JF	114	Feb	KLM SSV 80-40-15 Triband Vertical	156	Jul
Going 2m All-Mode with Yaesu's FT-225RDW6OJF	72	Apr	Hustler 5-BTV Vertical Antenna	156	Jul
Tempo S1 2-Meter PortableWB9HRV	118	Jun	Bearcat Four-Six ThinScan Scanner	157	Jul
Those Hamtronics Kits			Hy-Gain Catalog	157	Jul
How Can You Use Them?WA4PYQ	130	Jun	Hustler MKR-22m Fixed Station Mounting Kit	157	Jul
The Don Nobles Descramblers WA4PYO	148	Jul	Heathkit SA-2040 Antenna Tuner K4KYO	30	Aug
Inside Radio Shack's Digital Receiver W4PGI	80	Sen	Spectrum Communications ID 1000 CW	00	riug
Automated Operating Comes of Age K3CMV	170	Nov	Station Identifier	30	Aug
Automated Operating Comes of Age	170	INOV	Top Top Dolto Transpoivor	20	Aug
NEW PRODUCT SECTION				21	Aug
NEW PRODUCT SECTION			AEA KI-I Keyer TrainerWB8BTH	31	Aug
Azden PCS-2000 Transceiver	26	Jan	Hamtronics Converters and Amps	31	Aug
DSI 5600A Frequency Counter	26	Jan	Collins/Rockwell KWM-380 TransceiverK4TWJ	31	Aug
AEA Morsematic Keyer	26	Jan	Kenwood R-1000 General Coverage Receiver		
EP-8 Pocket Shortwave Receiver	147	Jan	WA4PYQ	162	Aug
OK Machine and Tool Mini-Shears	147	Jan	Peripheral People Software	162	Aug
Curtis IM-480 Kever	147	Jan	KLM 40-10V Multiband Vertical	163	Aug
Ten-Tec Model 299 Talking Counter	148	Jan	RSGB World Prefix Map	163	Aug
Ontoelectronics Frequency Counters	1/9	lan	Swan Astro 102BX Transceiver N8BK	32	Sen
Discoil HE Mobile Antenna	140	Eab	Con puter 1 Memory Keyer	24	Sop
Info Tools M 200E Tri Mode Converter	04	Feb	Loom IC OAT Curthenized Llondie Tellie	04	Sep
More Tech M-200E The Mode Converter	34	Feb	Icom IC-2AT Synthesized Handle-Talkle	34	Sep
Yaesu F1-20/H H1 (2m)K41WJ	145	Feb	Soundpower SP100 Speech ProcessorN8RK	36	Sep
DSI 50-Hz-500 MHz Pocket Frequency Counters	147	Feb	Microcraft RTTY Reader	37	Sep
Heath 1680/1681 CW Receiver/Transmitter	148	Feb	Instant Software "QSL Manager" SoftwareN8RK	38	Sep
Fox-Tango Crystal Filters	148	Feb	Circuit Specialists Repeater "Tail Chopper"	38	Sep
Fotografix Magnetic Signs	148	Feb	Grove Enterprises Sounds of Shortwave		e siĝ
Hamtronics Catalog	149	Feb	Cassette N8BK	38	Sen
OK Machine and Tool BW-2630 Wrapping Tool	149	Feb	Hv-Gain HG-70HD Tower and Accessories	39	Sen
Bullet Zulu Clock Kit	140	Ech	Archer Engineer's Notebook	160	Son
Selectore Multi Erequerey Erecder	149	Feb	P C Electropico TVC (ATV Downcoopertor	100	Oct
Selectone Multi-Frequency Encoder	149	Feb	P. C. Electronics TVC-4 ATV Downconverter	30	OCI
Radio Shack Wireless Remote Control	26	Mar	Heathkit HDP-1473 Allband Vertical	30	Oct
Heath 2-kW Antenna Tuner	26	Mar	Azden PCS-2800 10-Meter FM TransceiverW1GV	30	Oct
Clutterfree Modular ConsolesWA4PYQ	26	Mar	Hickok LX 304 Digital VOM	32	Oct
Macrotronics M650 RTTY Interface UnitW8FX	27	Mar	Radio Shack Safe House Alarm SystemN8RK	32	Oct
MFJ Phone PatchesWA4PYQ	145	Mar	Ten-Tec Omni-C Transceiver	242	Oct
AEA KM-1 Kever	145	Mar	Spectrum Communications SCB4000		
Kantronics Field Day Morse/RTTY Reader	146	Mar	LIHE Repeater	242	Oct
OK Machine and Tool Prototype Reards	146	Mor	MEL Model 050 Receiver Antenne	242	001
Claster CIV Caseline	140	war	Turse/Decemer Antenna	0.40	~ .
Skytec Gw Speaker	147	Mar	Tuner/PreamplifierWA4PYQ	243	Oct
KLM K1-34XA Triband Yagi	28	Apr	Hamtronics CA Series Receiving Converters	243	Oct
Prat Moss VHF TransmitterWA4PYQ	28	Apr	Drake R7 General Coverage Communications		
OK Machine and Tool Just Wrap Kit	28	Apr	ReceiverWA4PYQ	32	Nov
DenTron GLA-1000 Linear Amplifier	28	Apr	Radio Shack DX-302 General Coverage		
Heath Remote Coax Switch	29	Apr	ReceiverWA4PYQ	32	Nov
Bird Digital Rf Wattmeters	29	Apr	Mirage Model B232-meter Amp	36	Nov
Bullet SE-01 Sound Effects Generator N4XX	162	Apr	Jameco JE610 ASCIL-Encoded Keyboard Kit	36	Nov
MS COMM BTA-1 BTTY Control Conter	26	May	Grove Enterprises VHE/UHE Seeppor Beam	20	Nov
Arden BCS 2000 2m EM Transportuer	100	iviay	Heathkit Engruenes Countral Line	30	NOV
Azden PG5-2000 2m FWI TransceiverVVA00KV	190	May	Heathkit Frequency Counter Line	37	Nov
Pace Communicator MX H1KA5ECP	190	May	International Crystal TV-4300 Satellite Receiver	38	Nov
Kenwood TR-2400 HTN6HI	191	May	COMMSOFT RTTY89 Software	38	Nov
Spectrum TTC100 Decoder/Control	192	May	Teltone DTMF Decoder	38	Nov
Telex HDR300 Rotator	192	May	Kantronics Field Day 2 RTTY ReaderWA4PYQ	38	Nov
Hustler G7-220 220-MHz Base Antenna	192	May	R. H. Johns Current Shunts for DMMs.	40	Nov
Heath SA-7010 Triband Yagi	193	May	Palomar Engineers Antenna Tuners N8RK	40	Nov
Communications Specialists TE-12P Encoder	193	May	FTCO Catalog	41	Nov
Begency K500 Programmable Scapper WAAPYO	102	May	Padio Shack Space Saver Deck KDANIV/1	41	Nov
Microcraft Moreo A Word Code Booder	195	iviay	Hadio Shack Space-Saver Desk	41	NOV
Microcraft Worse-A-word Code Reader	194	May	MFJ Model 1020 Active AntennaWA4PYQ	196	Nov
AEA Morsematic KeyerWB8BTH	22	Jun	Shure Model 444D Microphone	197	Nov
Global Specialties Wire Kit	23	Jun	Micro-80 Amateur Radio Theory		
Amerex Unibox Packaging Components	23	Jun	Review SoftwareKA0BYS	197	Nov
Grove Enterprises Frequency Directory	23	Jun	AEA Model CK-1 Electronic Keyer	32	Dec
Ten-Tec Argonaut 515	166	Jun	Jameco Desk-Top Enclosures	32	Dec
Icom IC-2A HT. WB6TOV/1	166	Jun	Heath IC Timers Self-Instruction Program	186	Dec
Technical Clinic Ham Scan-2	166	Jun	Hamtronics VHE EM Excitor Kit	196	Dec
THS Electronics PA 1 10 2m Amo	100	Jun	Conturion Antonnos	100	Dec
Loroon Kulduskis Asterios	108	Jun	Out NED FIE AN	186	Dec
Larsen Kulduckie Antennas	168	Jun	Gilfer NRD-515 Allband Receiver	186	Dec
Altex UD1-170 TU	169	Jun	Sony ICF-2001 General-Coverage ReceiverWA4PYQ	187	Dec
Robot Model 650 Scan Converter	26	Jul	B&W T2FD Folded DipoleWA4PYQ	188	Dec
Micro Control Specialties Mark 3CR Repeater	26	Jul	Karetron SC-76 Scanning Module	188	Dec
Ten-Tec Hercules Linear Amp	26	Jul		211 2-2	
B & W BC-1 Balun	28	Jul	OPERATING		
Trac Model TE-292 Kever	28	Jul	ORP from Canton Island	60	Eab
Kantropics Signal Enforcer Audio Eilter	20	lul	Hurrissenel	03	reb
Rantionico olgital Entorcer Audio Filler	20	Jul	numeane:	68	May

The Pope Comes to the Cornfields WDØAKB, AK	DQ 108	May
Take a HikeK4	FD 74	Jun
The Rains of MorviVU2	ST 60	Aug
Trash All Your WorriesWA5TU	JM 70	Aug
Busman's Holiday	RS 96	Aug
"No Problem No Problem"	/M 122	Aug
Hams vs. Hurricane AllenN8F	RK 70	Nov
The Radio Spectrum at a GlanceWA4PY	(Q 142	Nov
A New Frontier	VJ 84	Dec

POWER SUPPLIES

n

g p

D

A Better Overvoltage Protection Circuit	W7RXV	140	Ja
Lab-Quality Hi I Supply-part I	McClellan	88	Ma
Lab-Quality Hil Supply-part II	McClellan	54	Ap
Flat Cells are No Fun!	WA3ENK	56	Ju
When Plus Goes Minus	Minchow	58	Ju
Depolarize that Power Supply!	AA6C	60	Ju
A Different Kind of Charger	WB6MXD	115	Au
Bridge Over Troubled Audio	K4IPV	56	Se
The Battery Minder	K4GOK	112	Se

RECEIVERS

Reawaken that Sleeping RxSara	112	Jun
Forward into the Past!W5JJ	48	Jul
Old Receivers Never DieW4ANL	111	Sep
In Search of the Elusive SESWA3UER	42	Dec

RTTY

Baudot-ASCII Converter Follow-UpVE4YD, VE4CM	34	Ma
Moving Display ASCII ReadoutW8VL	46	Ap
A Solid-State RTTY KeyboardK2BLA	88	Ap
A Tightwad's FSK DemodulatorWA5WPQ	108	Ap
Hooray! An AFSK Auto IDer!K3IJ	42	Jur
RYRYRYRYMinchow	70	Se
RTTY QSK CT1EM/PY1AQL	88	Se

SATELLITE-OTHER THAN OSCAR

NASA Satellites You C	an Use	K4OVK	50	Oc
-----------------------	--------	-------	----	----

Don't Be a dB Dummy!	McMahan	82	Jul
The NMX Relay Deceiver	W9NMX	128	Jul
That Mysterious Mode: 10 FM	WB2EQG	44	Sep
Free CMOS Timers	WD5DDR	113	Oct
Clock Blocks	K4IPV	192	Oct
Egad! An Easy-to-Build Synthesizer!	N4CEY	210	Oct
Direct Conversion Lives!	ZS6UP	64	Nov
HV Power Rectifiers	WB2UIK	92	Dec
Teletext and Viewdata:			
Are You Ready for the Information Boom	?WB9KPT	120	Dec

TEST GEAR

Frequency Counter Survival CourseMcClellan	36	Jan
The Dollar-Saver DVMMcClellan	83	Jan
The Oscilloscope Survival CourseMcClellan	106	Feb
Test Gear Bargain from HeathStaff	62	Apr
Semiconductor Test GadgetTruesdale	64	Apr
Build an Audio VOMAC5P	104	Apr
Measure Frequency on your DVMW3HB	115	Apr
Five Test Equipment Bargains from HeathW2QFC	46	Jun
Digital Transistor CheckerW4QBU/PY2ZBG	56	Jun
The Sweet Sounding ProbeW7BBX	84	Jul
The Multi-Media Bench TesterWD4KFF	106	Jul
Counting with ClassWB4EKB	134	Oct
Build a Better Battery TesterStaff	196	Oct
VSWRAutomatically!WB0GWP	42	Nov
Breadboard Signal Generator	100	Nov
A 600-MHz Universal CounterW4VGZ	58	Dec

TRANSMITTING

So You Want	to Build a Beacon?	K9EID	78	Feb

VHF AND HIGHER

ADDSCANWB9FSC	52	Jul
Two Dollars a Tone	74	Aug
The World Above 430-part IW9CGI	80	Aug
The World Above 430-part IIW9CGI	52	Sep

Direct Printing FAX-part IWB8DQT	90	Nov
New Weather Eye in the SkyWB8DQT	176	Nov
Direct Printing FAX-part IIWB8DQT	52	Dec
The Microwave MidgetW3KH	106	Dec

SURPLUS

Surplus Treasures	.K1	V	IC/2	122	J	un
-------------------	-----	---	------	-----	---	----

TECHNICAL AND THEORY

NBVM: Dawn of an Era or Promotional Hype?N8RK	30	Jar
How to Make Your Own Crystal FiltersStaff	98	Jar
Zero In on Zero BeatW2OLU	112	Jar
An End to Dials and Meters?Staff	50	Fet
In Search of Power Line InterferenceW4PZV	66	Feb
Hard Copy from your Xitex TerminalW5SBL	70	Fet
Noise Rejector IIWB6ZYK	74	Fet
Working with FETsWA2SUT/NNNØZVB	82	Fet
The L With ItK4KI	40	Ma
Ham Shack NumerologyW6HDM	70	Ma
A Do-It-Yourself Speech Compandor	96	Ma
Morse Converter for		
Frequency DisplaysWA6AXE/KH6	107	Ma
Back to SchoolW6HDM	40	Apr
Home-Brew Rf Impedance BridgeWB6BIH	30	Ma
VHF Signal DiffractionW5GFE	56	Ma
The Capacitive Coaxial		
Ground WireDA1TM/WD9HBB	82	Ma
Confused About Phased Arrays?W5JJ	118	Ma
One Step at a Time:		
Designing Your Own Ham Gear-part IW4RNL	28	Jur
Tuning Antenna-Mounted PreampsStaff	78	Jur
Who Needs a \$40 Soldering Iron?Staff	144	Jur
One Step at a Time:		
Designing Your Own Ham Gear-part IIW4RNL	36	Jul

HAM HELP

Help!!! I am having difficulty in locating a schematic or operating manual for the following piece of equipment. It looks like a modem but I want to be sure. It has a transmit and receive section. The model number on the receive section is 1CRCU-RS-1. The model number on the transmit section is 1CTCU-RS-1. It carries the Burroughs Trademark on the case but it was manufactured by Stelma, Inc. Burroughs and Stelma, Inc., have not been able to help. Any information would be greatly appreciated.

Terry Hazelett 2107 Capitol Dr. Parkersburg WV 26101

I need a schematic and/or instruction manual for a Collins 310B-1 exciter. I will buy a copy or reproduce one and return it. I also need an ac power supply

for a KWM-2A.

Herman F. Shnur K4CTG 115 Intercept Ave. North Charleston SC 29405

I would like to correspond with people who have working models of computer-controlled or radio-controlled humanoid robots. Thank you.

> Matt Beha N8BPI 3752 Lane Court St. Joseph MI 49085

Our school amateur radio club is in need of the schematic and/or instructions for a Hammarlund four-20 transmitter. Payment for copies will be mailed or we will copy and send back if preferred.

> Barringer High School c/o F. Rice N2BVZ 90 Parker Street Newark NJ 07105

73 Magazine • December, 1980 179



from page 26

- Slow-scan television is permitted only on upper-sideband.
- Hertz rotation is an important factor in moonbounce communication.
- Amplitude-shift radioteletype is also called "make-and-break" keying.
- Color amateur television is permitted only above 1296 MHz.

ELEMENT 4-SCRAMBLED WORDS

Unscramble these words dealing with specialized mode activities.

rswohe	hpcun	craos	cibsa
trenrip	ivode	anocbe	puknil
lebl	olop	ormci	xfa
iliadgt	lupes	cnsy	eramac
rtc	nisp	retmoe	nigp

ELEMENT 5—HAMAZE

Here's a new type of maze specifically geared to hams. The object is to start at the circle and trace your way to the square by filling in the answers to the clues given below. To help you on the way, we've already given you the first and last clue answers. All words read either vertically downward or from left to right. Each new word is on a *perpendicular* angle to the previous word. Words join on a common letter. Good luck.

- 1) Mark and space (given)
- Without pattern or a mem-

- 11) You type on one
- 12) CRT, digital, etc.
- 13) TV scale
- 14) Satellite protection band
- 15) WAS, DXCC, etc.
- People who sank Phase III (abbr.)
- 17) Greek: at a distance
- 18) RTTY error
- 19) Highest point or radio company
- 20) OSCAR rotator: ____-el
- 21) Skyhook: an____ (given)

THE ANSWERS

Element 1: See illustration.

Element 2: 1-I, 2-D, 3-E, 4-K, 5-C, 6-H, 7-G, 8-A, 9-J, 10-F.

Element 3:

 True – Yes, but now there are many other funny noises to be heard on this band.

2) True – With Charles Krum he formed the Morkrum Company which was eventually bought out by AT&T. He got to keep the salt business, however.

 False – No, F1 is. The only FCC designation AF2M has is his Extra ticket.

4) True - Like clockwork.

5) False - Only RTTY.

6) True - Many times.

7) True - With a little on 50 MHz and some activity above 432.

8) True - WB2IBE to K7OFT, November 20, 1979, on 50 MHz.

 True – Still not quite television in the conventional sense, but an improvement beyond slow scan.

10) True - Write to Washington stating your reason.

11) False - Most awards require a real signature on them for credit.

12) False - That's really wideband! Kill the "k."

13) False - No, it stands for Narrow Band Voice Modulation. The meter, however, would probably be more useful.

14) False - Eighty and up.

15) False - All CW bands but Novice and 160.

- RTTY automatic monitoring
- Phase III computer channel (abbr.)
- 4) Take antenna for a turn
- 5) Meteor and rain

- ory
- Between short and long waves
- Frequency above 1 GHz
- 9) Moonbouncer's reply
- 10) Thousand prefix



16) False - Means "Earth-Moon-Earth."

17) False - Only by convention on 20 and up.

18) False - The polarization change of a signal passing through the Earth's ionosphere is known as *Faraday* rotation.

19) True – Old practice that was eliminated when FCC approved frequency-shift keying.

20) False – Color television, fast scan or slow scan, is allowed on any appropriate amateur TV frequency.

Element 4:

(Reading from left to right) shower, punch, oscar, basic; printer, video, beacon, uplink; bell, loop, micro, fax; digital, pulse, sync, camera; crt, spin, meteor, ping.

Element 5: See illustration.

SCORING

Element 1:

See illustration. Twenty points for the complete puzzle, or 1/2 point for each question you got.

Element 2:

Two points for each mode you matched to its equipment.

Element 3:

One point for each correct answer.

Element 4:

One point for each word successfully unscrambled.

Element 5:

Twenty points for complete puzzle, or one point for each word.
Total up your points and see the level of your technical expertise:

0-20 points - Lid 21-40 points - Physically-fit Conditional

- 41-60 points KA
- 61-80 points A pro

81 and up - A Technician in the full sense of the term

A	М		т	E	L	E	т	Y	Р	E
Р	S		D		0	x			R	G
E		D		Н		Р		R	А	G
x	Ρ	E	R	1	М	Е	N	Т		
	Е		С		A	R		Т	т	Y
	R		А	Ρ	R	Т		Y		L
N	F	0			к	S	R		R	S
Line I			А	G	E		С	Р	Y	
0	Ν	1	т	0	R		V		S	Т
М	E		V	Т		А	R	S		А
	W	R			U				Α	P
V		F	A	С	S	1	М	1	L	E
	A P E X N O M	A M P S E I X P X P X P I I N F O N M E I I I	AMPSEDXPERIRINFONIMEMEVF	AMTPSDEDDXPERXPECRGANFOANFOAONITMEIVVFA	AMTEPSDDEDHXPRIKERIRIAPNFOINITOMEIIMEVTVFAC	A M T E L P S D D O E D H M X P E R I M X P E R I M N F O I A A N F O I I K N F O I I K N F O I I K N F O I I I N F O I I I N F A G I I N I I T O R M I I I I I I N I I I I I I I I I I I I I I I I I I I	AMTELEPSDDOXEDFHPPXPERIMEXPERIMEKECIARRIAPRTANFOIIKSONITORIMEIVTIAMEIVTIAVFACSI	AMTELETPSDDOXFEDHMPFXPERIMENKPERIMENKFCJARFNFOIIARNFOIISRNFOIISRNFOIISINFAGEIVMEIVTIANFACSIM	AMTELETYPSDDOXFFEDHFPRRXPERIMENTKPERIMENTRECIARTTRIAPRTYYNFOIIARYNFOIIASRYNFOIIORIYNFACSIMIMFACSIMI	AMTELETYPPSDDOXTREDDHVPRAXPERIMENTXPERIMENTXPERIMENTXPERIMENTAPRTIYYYNFOIIKSRINFOIFASIYYONITORIYSMEIVTIARSMEIVTIARSVFACSIMII



Next month: Ham History



"those secret TV channels." If you have a fistful of money or a lot of technical expertise, you 15-kHz pulse train and have special subcarrier audio. Block diagrams, oscillographs, and spectrum analyzer photographs supplement the descriptive text.

AND SUPPLIES

It's been estimated that there are at least 8,000 collectors and enthusiasts of antique radio equipment in the United States. As is the case with all manner of antiquities, there's a great demand for literature on these old sets and the equipment that was used three generations back, when radio began to make itself known to the public.

Radio Equipment and Supplies is a 160-page catalog originally issued in 1922 by the Robertson-Cataract Company of Buffalo, New York, a major distributor in the field. It's full of pictures of receivers, transmitters, tubes, vario-couplers, tuning inductances, headphones, and all the apparatus that radio people of that day had to grapple with in order to "bring in the stations" or to "get on the air."

To serve the interests of the antique radio buffs of today, The Vestal Press has made a top-

quality reprint of this 81/2" × 11" book. With its contents including 30 pages of receivers, 74 pages of accessories for receivers, 30 pages on transmitting equipment, and 20 pages of basic "Radio Information and Data," there's something for every one of the present-day enthusiasts. It contains literally hundreds of photographs and drawings, and the 1922 prices would make anyone weep! It's certainly interesting, in the light of today's highly sophisticated electronics, to view the astounding changes that have occurred in the past 60 years.

Copies are available directly from The Vestal Press Ltd., Box 97, Vestal NY 13850, or through any bookstore, for \$12.50 + 75¢ shipping (NY residents add sales tax).

CODING AND DECODING TELEVISION SIGNALS Science Workshop

Everyone is talking about

might build an earth satellite terminal. For a bit less cash an MDS microwave receiver capable of catching local pay TV signals can be had. A third source of limited access viewing is signals transmitted on conventional UHF TV channels but scrambled at least part of the time. As nonpaying "customers" become prevalent, more and more of these common carrier video signals will be encoded and, of course, more than a few hams will be busy trying to unscramble them. Now, much of the current scrambling technology is discussed in Science Workshop's book, Coding and Decoding Television Signals.

A video freak is likely to exclaim, "So that's how they do it!" after reading *Coding and Decoding* for the first time. Material for this book was gathered from a variety of public and private sources. Included in the contents is a word-for-word reproduction of a NASA report on the scrambling technique used for the Application Technology Satellite video signals. Later sections explain how some UHF signals are encoded with a The editor of Coding and Decoding Television Signals states, "This is not a 'how-to' book. It does not contain any construction projects." However, an amateur knowledgeable about video and experienced in building rf circuits should be able to successfully reproduce the designs shown. You'll have to make your own parts lists and circuit board templates, though.

For some reason, beating the system at its own game has always been an attraction for electronics experimenters. As the issue of the freedom of the airways is discussed in high places, hundreds or even thousands of tinkerers will be using information from books like Coding and Decoding Television Signals to build their own units. Costing \$9.95 (\$1.00 postage), this 43-page softcover pay-TV primer for experimenters is available from Science Workshop, Box 393, Bethpage NY 11714.

Tim Daniel N8RK 73 Magazine Staff

73 Magazine • December, 1980 181



from page 14

point of view on the subject, but there should be no doubt just what its point of view is.

FOR SALE: QSLS

As long as we are rampaging, might as well take up one additional subject recently beaten nearly to death in the amateur press. Maybe we can breathe a little life into it. Some have complained about the practice of requiring payment of a dollar for a QSL for an expedition contact. Actually, this is not new. W9WNV (and others) were doing it fifteen or more years ago, only then you paid for the contact before the expedition was undertaken. Those who anted up found that the DXpeditioner was able to hear them without difficulty; those who held out were just not heard or worked.

Grousing when required to supply a buck for a QSL shows little appreciation for the sacrifices made by expeditioners. When they moan in print about it, that constitutes almost a personal affront to the DXer who has made it possible for many to work a new country. As plane tickets are not free, we see little wrong with QSLing *only* to those who help with the expenses. Most expeditioners are not independently wealthy and are only practicing economic horse sense. If they recoup some of the expenses from one trip, they are more likely to make another.

ISTANBUL REPORT

The accompanying letter from an amateur in Turkey is printed in full, except that all references to callsigns and names have been deleted. Anyone wishing to act as QSL manager for the writer of the letter can make arrangements by writing to me at the address given at the beginning of this column.

"Istanbul, Aug. 26, 1980

Dear OMs: I am a subscriber to 73, and I am very glad to see a DX column in your excellent magazine. The purpose of my letter is to provide you with some material and information for the section, and possibly seek your help on a subject.

Here in Turkey, for a long time there has been on-and-off operating by courageous local and by temporarily resident foreigners (mainly from the US). I am sure some of your fellow hams and subscribers do not know that ham radio in Turkey is still illegal due to a law dated 1937! I say TA is activated by courageous people because possession and operation of transmitters has severe penalties, including imprisonment of up to five

years!

"Terrorism all over the world is well known, and we too have a fair share of it in TA Land. I am sure there would be far less of it if we had worthwhile hobbies like amateur radio to keep the young people occupied. We have martial law in certain parts of the country (including Istanbul), during which the penalty for the above mentioned offense is ten years in jail! Big risks are taken in operating, but you know ham radio is a bug and...

"Therefore, operation from TA is sporadic; at present we must be at an all-time low. I have been QRT since March, 1980, and will be so for another few months.

"We have an amateur radio club, TRAC, which is listed in the *Callbook* for incoming QSLs. That is the only service provided by TRAC except for a magazine which gets published now and then. Since there is no outgoing QSL service, I suspect the QSL record of TA stations is not very good, as everyone is on his own for sending cards. Having a 100% QSLing record is very important to me.

"One question which is often asked is how and by whom we get our calls assigned. The answer is that we do not get them assigned, we just pick them ourselves. The country was divided into call areas by the club when it was founded in the 1960s. Most of us pick our initials and we all know each other so duplicates are prevented. We watch out for newcomers, too. cerned, it simply is not available. Transmitters and transceivers are illegal, and even receivers are almost nonexistent. I personally would be willing to pay twice the list price for a good receiver. We make do with whatever we can find in surplus, and that, too, is something which may come once in a lifetime. Surplus and simple homemade rigs are what you hear from Turkey. If our signals are drifting and we cannot hear you S9, I think we can be excused if people know the conditions we work in.

"Attempts have been made to change the 1937 law but have failed for various reasons, mainly because the people concerned did not know what amateur radio was about. Lately, the final word has been that to ensure the national security, monitoring stations tied to a computer center where 'exact location of any transmission can be found' is the only way for amateur radio to be legal in Turkey. Estimated cost of this is twenty million dollars!

"I hope 73 can find a manager for my QSLs when I return to the air. I am sure you have a heavy workload, so if you cannot spare the time I shall understand.

This is a somewhat abbreviat-

ed column due to things backing

up at the editor's shop. The col-

umn will be back to its usual size

in January. Your input of letters

and pictures is appreciated.

73,

TA2--."

"As far as equipment is con-

28570, 3725, 7125, 21125, 28125.

SCORING:

Add the number of Zero District ARRL sections worked plus the number of Zero District counties, then multiply by the number of contacts. Zeros score by adding ARRL sections, Zero District counties, and DXCC countries worked, and then multiplying by total contacts.

ENTRIES & AWARDS:

Awards will be issued to the high scorer in each ARRL section and DXCC country. Also to top Novice/Technician and top in special mobile class. Mail logs by February 15th to: W0SI, 3518 W. Columbia, Davenport IA 52804. Include an SASE for log forms or results. 2nd ANNUAL INTERNATIONAL 160-METER PHONE CONTEST Sponsored by 73 Magazine Starts: 0000 GMT January 17 Ends: 2400 GMT January 18

This is the second annual 160-meter contest sponsored by our magazine. The object is to work as many stations as possible on 160-meter phone in a maximum of 30 hours allowable contest time. Multi-operator stations may operate the entire 48-hour contest period. Entry categories include single- and multi-operator, both with single transmitter on phone only.

EXCHANGE:

Stations within the Continental USA and Canada transmit RS report and state or province. All others transmit RS report and

from page 16

couver, BC Canada V6J 1E3, postmarked before January 15th. Results will be published in *TCA*, the Canadian amateur magazine. Non-subscribers may include an SASE for a copy of the results.

ZERO DISTRICT QSO PARTY Starts: 2000 GMT January 3 Ends: 0200 GMT January 5

Organized by the Mississippi Valley Radio Club. Stations outside of Zero District will work Zero stations only; Zeros may work any station. The same station may be worked once on each band and each mode. However, stations in the special mobile class may be worked each time they change counties.

EXCHANGE:

CONTESTS

RS(T) and ARRL section. Zero District stations also must send county.

FREQUENCIES:

3560, 7060, 14060, 21060, 28060, 3900, 7270, 14300, 21370,

DX country. SCORING:

All valid two-way contacts score 5 points per QSO. A station may be worked only once for contest credit! Multipliers are as follows: 1 multiplier point for each of the Continental US states (48 max.); 1 multiplier point for each of the Canadian provinces (13 max.); 3 multiplier points for each DX country outside the Continental US and Canada.

The final score is the total QSO points times the total multiplier points.

DX WINDOW:

Stations are expected to observe the DX window from 1.825 to 1.830 MHz as mutually agreed by Top Band operators. Stations in the US and Canada are asked not to transmit in this 5-kHz segment of the band.

AWARDS:

Contest awards will be issued in each award category in each of the Continental US states, each Canadian province, and

each DX country. DISQUALIFICATIONS:

Disqualifications may result if contestant omits any required entry forms, operates in excess of legal power authorized for his given area, manipulates operating times to achieve a score advantage, or fails to omit duplicate contacts which reduce the overall score more than 2%. ENTRIES:

Each entry must include log sheet, dupe sheet for 100 or more contacts, a contest summary sheet, and a multiplier checklist. All entries must be postmarked no later than February 21st. To request contest forms or submit your entry, write: Dan Murphy WA2GZB, PO Box 195, Andover NJ 07821 USA. Please include an SASE!

SPECIAL CHRISTMAS **EXPEDITIONS**

With the Christmas holidays fast upon us, there are two special operations planned for the holidays. The Delaware-Lehigh Amateur Radio Club (W3OK) will

have a special events station on the air as part of Bethlehem PA's Christmas City Celebration. The station will be on the air from 2300 to 0300 GMT starting December 15th and will continue to operate through January 1st. The operating hours will increase during the period whenever possible. Operation will be on the Novice CW and General phone bands. Suggested frequencies are: 15 kHz down from the top of the Novice band, and 15 kHz up from the bottom of the General phone band. Special QSO certificates will be sent from the Christmas City Station. QSLs or requests should be mailed with a business-size SASE to: W3OK, DLARC, 1719 Callone Avenue, Bethlehem PA 18017. SWL requests will also be honored.

The Indian River Amateur Radio Club of Cocoa FL will be operating from Christmas FL from December 20 through 27. Operating times will generally be from 1400 to 2000 GMT daily. The town of Christmas, located

on the east coast of Florida, welcomes many visitors each year from around the USA. Christmas is celebrated each and every day of the year. There are fully lighted Christmas trees, wreaths, and decorations along with Santa and his helpers. The Indian River Amateur Radio Club, as a celebration of its 26th year of organization, will use the club callsign W4NLX/4. A special handsome certificate will be awarded to all worked stations. This certificate depicts some of the aspects of Christmas in Florida. Arrangements have been made to have a special cancellation at the US Post Office for this award. Please send a large SASE for the certificate. Operating frequencies on SSB will be 7280, 14280, 21380, and 28680. On CW, the club will operate 60 kHz up from the bottom edge of the 40-, 20-, 15-, and 10-meter bands. The 146.34/.94 repeater will also be operational for local contacts. QSL to Indian River Amateur Radio Club, W4NLX, PO Box 105, Christmas



Freshwater, Isle of Wight, England, United Kingdom.

ber 1, 1960, and after to be valid. There are no band or mode restrictions, but recognition will

FL 32709.

from page 20

bands the same day (6 \times 3 = 18) or work him on twenty meters three individual days (6 × 3 = 18), you will have qualified very easily for the Gold Sardinian Award. Sounds easy, doesn't it?

To be valid, all signal reports must be a minimum of 338 for CW and 43 for phone.

To apply, have your claimed contacts verified by at least two amateurs or a local radio club official. Enclose your application with an award fee of 15 IRCs or \$4.00 US to: URS Club, via Sardegna 16, 07100 Sassari, Sardinia.

While in Europe, let's visit the United Kingdom, where last time I failed to include two very interesting awards.

HAMPSHIRE COUNTY AWARD

The Hampshire County Award is made available to amateurs worldwide who have established two-way contact with

amateur operators of Hampshire County in England. The award is issued on a point basis in which all contacts count 1 point, with the exception that contacts with G3BZU, GB3RN, or any other special-event station count 2 points.

There are three award classes: Class I-UK/50 points; EU/20 points; DX/15 points. Class II-UK/30 points; EU/15 points; DX/10 points. Class III-UK/20 points; EU/10 points; DX/5 points.

To be valid, all contacts must be made after October 1, 1960. There is no mode or band restriction, but special band or mode recognition will be made if requested at the time of application.

To apply, have your list of claimed contacts verified by at least two amateurs or a local radio club official. Forward this application and an award fee of 50 pence or 6 IRCs to: F. D. Cawley G2GM, Award Manager, Bay Sound, Freshwater Bay,

THE MERCURY AWARD

While in England, it is my honor to feature to our readers the very respectable Mercury Award, sponsored by the Royal Naval Amateur Radio Society. This award was initiated to encourage contact with the many members of the Royal Naval Society. The award is issued to any amateur who can meet the requirements of the program which are tabulated on a point basis. Contacts with RNARS members on the HF bands earn 1 point each, while two-way contacts established 30 MHz and above constitute 2 points apiece. In addition, any specialevent station, such as GB3RN or G3BZU, counts double the normal point value.

To attain the award, stations within the United Kingdom must accumulate a total of 20 points, other European stations must total a minimum of 10 points, and stations outside Europe must gather a total of at least 5 points. Once an applicant earns 10 points (for US) or 20 points (for Europeans), stickers will be issued for each multiple of 10 points earned thereafter.

Contact must be made Octo-

be given if special band or mode accomplishments are attained.

The Mercury Award also is made available to shortwave listeners who must meet the same criteria on a "heard-only" basis.

Do not send QSLs! Have your list of claimed contacts verified by at least two fellow amateurs or a radio club official. Enclose this application along with the award fee of 6 IRCs to: Awards Manager G3HZL, 153 Worple Road, Isleworth, Middlesex TW7 7HT, England, United Kingdom.

To be successful in confirming contacts with members of the Royal Naval Amateur Radio Society, it is advisable that you obtain a list of their members before attempting the challenge of this award. It is unfortunate that the list is so lengthy, as space does not permit the list to be printed at this time. As an alternative, however, the Mercury Award is featured in the DX Awards Guide published by Chuck Ellis W0YBV. The entire list of RNARS members is contained within this publication. This DXer's award guide, featured in last month's column in detail, is available for a very modest price of \$14.95 (plus 1-lb. postage for DX shipment) by enclosing payment to Chuck Ellis, PO Box 1136 Welch Station, Ames IA 50010. Be sure, if that is the reference you plan to use, that you tell Chuck you read about it here in the 73 Magazine Awards column.

If you are like many of us on the west coast and are looking for a real toughie, try your hand at working toward the Worked All Gozo Award.

WORKED ALL GOZO AWARD

The WAG Award, as it is called, is open to amateurs and SWL stations and has no band or mode restrictions. To be valid, all contacts for this award must be made on or after August 1, 1972.

To qualify, European stations

must confirm 8 individual stations from Gozo Island (9H4). Now, if you are considered a DX station like we are in the USA, you only have to work 5 different Gozo Island stations. And, of course, if you are like me, you'll be happy to settle for just an SWL Heard Only Award which also is available under the same requirements.

Do not send QSL cards, please! Have your list of claimed Gozo Island contacts verified by at least two amateurs or a radio club official. Forward this verified application and an award fee of \$3.00 or 12 IRCs to: Joe Cauchi 9H4L, 20 P. P. Hili Street, Victoria, Gozo Island, Malta. All award fees are contributed to aid the blind and handicapped operators; we all should apply for this award if for no other reason than to aid this cause.

OUR AWARDS PROGRAM

By the time this magazine reaches your hands, the hundreds of certificates already earned via the 73 Awards Program will be on their way to amateurs around the world. Now, if you are one of the many who qualified for an award months and months ago, you're no doubt saying, "It's about time!" Right you are.

What caused the incredible delays? First of all, some of us underestimated the work involved in getting the certificates designed and produced. But more than that, we too often allowed the Awards Program to take a back seat to other projects which, at the time, seemed more important. Few of us at 73 wear only one hat, and it was all too easy to stop working on the awards when article titles needed to be written or when manuscripts needed to be read. After all, we had magazine deadlines to meet each and every month, and it always seemed that the awards could wait... and wait... and wait. In short, we blew it.

In retrospect, it's easy to see what we should have done. For starters, we should have had the awards printed and on the shelf before the Awards Program was even announced. Then, we should have assigned one person to stay on top of gram is finally up to speed. The debacle of the past 14 months is over, and the awards are going out.

Before proceeding any further, a note of commendation is in order. The man who writes this column each month and serves as manager of our Awards Program is Bill Gosney WB7BFK. Bill has been with the program from the beginning, and he has done an outstanding job under very difficult circumstances. He's done everything we have asked of him and more. If you've been waiting for an award, the delay was at our end, not his. Thank you, Bill.

To those of you who have earned awards through our program goes a special note of thanks for getting involved in our new and untried venture. Now that we're back on track, we hope you enjoy your awards and that you'll apply for others in the future. If you have never applied for a 73 award, please do so; the system is working, and it's our goal to handle all future applications quickly and efficiently.

As we move into the third decade of 73 Magazine, we're looking forward, not back. There are exciting times ahead for amateur radio, and we want the 73 Awards Program to be a part of it.

the program and keep it moving. The good news is that we have, at last, recognized these failings, and the Awards Pro-

Jeff DeTray WB8BTH Assistant Publisher/Editor

73 AWARD WINNERS

NORTH A	MERICAN	67 WB7PKD	88 AITY	23 WBOLXM	59 DA1MV	95 WB7RUV	97 WD4LYA
CONTINEN	TAWARD	68 S8AAT	89 WB5SND	24 WB3ICM	60 HK4DUM	96 S8AAP	
00111111		69 HK4DUM	90 NØAMI	25 KA9ACM	61 WD9IIC		
1 WA2GUM	34 N6PV	70 WDØAVG	91 WD8QEO	26 WB7TXY	62 WOYBV	OF AWARD OF	
2 WB8VPA	35 F2YS/W2	71 WD9IIC	92 VE3JGT	27 WB3CIW	63 WB3JUK	Q-5 AWARD OF	EXCELLENCE
3 K4HRG	36 W8CHV	72 WIAGA	93 KA5CTZ	28 K9PSN	64 W1AGA	1 WB8ZJL	17 KA4KJI
4 KE4E	37 AJ8L	73 WB3JUK	94 WD8DEL	29 F2YS/W2	65 PY8ZLC	2 WD8ONV	18 N3ADF
5 N6TK	38 WA2YEX	74 WA2RVF	95 WB6CDM	30 K8ZIP	66 KA2K	3 KA8HNR	19 K6TMB
6 AA6TK	39 SM5AKT	75 KA2K	96 KB8LT	31 WA2SRM	67 WA2RVF	4 K8IU	20 WOCJG
7 WA1SMI	40 AC30	76 PY8ZLC	97 NØGP	32 AJ8L	68 K4LQ	5 WB7QEP	21 KA8IGM
8 WA9BBX	41 WA2SRM	77 K4LQ	98 A16I	33 WA2YEX	69 DA1UO	6 KA0FPG	22 WD8NHN
9 K8ZIP	42 K9TI	78 DA1UO	99 N4AKO	34 AC3Q	70 N8AC	7 WL7ADX	23 WB3GSO
10 WBØYMR	43 WD0EPE	79 IC80GS	100 KB8DB	35 SM5AKT	71 IC80GS	8 WD5EHI	24 KAOHTU
11 WB6VVI/9	44 K4JYD	80 DA1QR	101 N8BJQ	36 WDØEPE	72 DA1QR	9 KA3DBN	25 KA8GXN
12 WB3BAP	45 N8AC	81 WD4IIU	102 K5BLV	37 JH1VRQ	73 AG5X	10 KA3COP	26 KA9CDR
13 WD8MGQ	46 JH1VRQ	82 AG5X	103 DF9ZP	38 WB3BVL	74 K9BIL	11 KA3CGM	27 KA1ESG
14 WB7BFK	47 WB3BVL	83 K9BIL	104 KB5OU	39 WD4DVZ	75 N4BQD	12 WD2AKK	28 WD8QHN
15 WB1DQC	48 WD4DVZ	84 N4BOD	105 K8GAK	40 W5TJQ	76 WA2LYF	13 WD8IDD	29 WD4BLU
16 K4BQZ	49 WØYBV	85 WA2LYF	106 N1BCV	41 WD8DZO	77 WD9HWY	14 SM2COR	30 KA3ENQ
17 KOJSY	50 WB2FFY	86 WD9HWY	107 S8AAP	42 WB4SXX	78 WB5SND	15 KØTBB	31 KA4JQS
18 KA5CQJ	51 W5TJQ	87 N4BQD	108 WB7RUV	43 WD4KRK	79 K800E	16 WD5ICQ/1	
19 K1TH	52 WD8DZO			44 K9MD	80 NØAMI		
20 W7ULC	53 KB4JA	COUTU	MEDIOAN	45 KB4JA	81 WD8QEO	CDEC	VTIALTY
21 WB3ICM	54 WB4SXX	SOUTHA	AMERICAN	46 N7BZ	82 VE3JGT	SPEC	ALIT
22 K8WD	55 DJ2UU	CONTINE	NT AWARD	47 DJ2UU	83 KA5CTZ	COMMUNICA	TIONS AWARD
23 W9NAX	56 WD4KRK	1 WB8VPA	12 WB7BFK	48 W8CHV	84 WD8DEL	CLAS	SS A-1
24 VE1BVD	57 KA2EAO	2 KE4E	13 WB1DQC	49 K9TI	85 WB6CDM	1 W20DA (BTTY)	5 WD9GRI (RTTY)
25 WD9HRH	58 K9MD	3 N6TK	14 KØJSY	50 W20DA	86 KB8LT	2 WBOOCD (SSTV	6 WBSCOM (BTTY)
26 WD8MOV	59 N7BZ	4 AA6TK	15 KA5CQJ	51 WB2MVC	87 NØGP	3 WB7BEK (BTTY	7 N3AKO (BTTY)
27 K9PSN	60 W20DA	5 WA1SMI	16 K1TH	52 KA2EAO	88 N4AKO	4 WBOOCD (BTTY) / ///////////////////////////////////
28 AD15	61 WB2MVC	6 VE1BVD	17 W7ULC	53 K4BYK	89 KB8DB	a moraco (mini	CO CONTRACTOR DA
29 DA1MV	62 K4BYK	7 WD6EEQ	18 K8WD	54 KB8JF	90 N8BJQ	DISTRICT	NDUDANCE
30 WBOLXM	63 KB8JF	8 WBOYMR	19 K4HRG	55 KB2BE	91 K5BLV	DISTRICT	NDUMANCE
31 KA9ACM	64 WA2PIP	9 WB6VVI/9	20 WD9HRH	56 WA2PIP	92 DF9ZP	AW	ARD
32 WB7TXY	65 KB2DE	10 WB2BAP	21 WD8MOV	57 WB7PKD	93 KB5OU	1 AJ8L	3 WB6CDM/7
33 WB3CIW	66 N9ADL	11 WD8MGQ	22 AD1S	58 SBAAT	94 N1BCV	2 WL7ACY	

184 73 Magazine • December, 1980

FUROPEAN	CONTINENT	47 HK4DUM	63 N4BQD	55 WB2JUK	68 VE3JGT	DX CAPITALS O	F THE WORLD
LUNOT LAW	APD	48 K9TI	64 WD9HWY	56 K9TI	69 KA5CTZ	1 WB1DOC	6 KB8JF
AVV	AND	49 WA2SRM	65 WB7PKD	57 KA2K	70 WD8DEL	2 WB7BEK	7 WD4DVZ
1 WB8VPA	63 W2ODA	50 WD9IIC	66 NØAMI	58 K4LQ	71 WB6CDM	3 KITH	8 WIAGA
2 K4HRG	64 WB2MVC	51 W1AGA	67 WD8QEO	59 IC8OGS	72 KB8LT	A WDAKRK	9 NOGP
3 KE4E	65 K4BYK	52 WB3JUK	68 VE3JGT	60 DA1QR	73 NØGP	5 D 121111	o nodi
4 N6TK	66 KB8JF	53 WA2RVF	69 WD8DEL	61 SBAAT	74 KB8DB	5 05200	
5 WA1SMI	67 WA2PIP	54 KA2K	70 WB6CDM	62 AG5X	75 N8BJQ	72 DY COUNTRY	CI UR AWARD
6 WB3ICM	68 KB2DE	55 K4LQ	71 KB8LT	63 K9BIL	76 N7AHQ	13 DA COUNTRI	CLUD AWAND
7 VE1BVD	69 WB7PKD	56 DA1UO	72 NØGP	64 WD9HWY	77 K5BLV	2X 3	SB
8 WA9BBX	70 N8AC	57 IC80GS	73 KB8DB	65 N4BQD	78 DJ2UU	1 WB8VPA	26 W5ZKJ
9 WBØYMR	71 S8AAT	58 DA1QR	74 N8BJQ	66 NØAMI	79 WB7RUV	2 WB3ICM	27 WB7TXY
10 WB6VVI/9	72 WD4IIU	59 WDØAVG	75 K5BLV	67 WD8QEO	80 S8AAP	3 WB1DQC	28 F2YS/W2
11 WOHMA	73 WD4IIU	60 AG5X	76 DF9ZP			4 N6TK	29 WA2GUM
12 WB3BAP	74 KA1CBD	61 KB4JA	77 S8AAP	WORK THE WO	DID AWARD	5 WA1SMI	30 KB4NJ
13 WD8MGQ	75 WDQAVG	62 K9BIL	78 WB7RUV	WORK THE WO	ALD AWAND	6 WB6VVI/9	31 KB4JA
14 WB7BFK	76 WD9IIC			1 WB8VPA	37 K4BYK	7 WD8MGQ	32 DJ2UU
15 WB1DQC	77 W1AGA	AEDICAN CONT	INENT AWARD	2 KE4E	38 KB8JF	8 WB7BFK	33 K9MD
16 WA2GUM	78 WB3JUK	AFRICAN CONT	INENTAWARD	3 WB6VVI/9	39 KB2DE	9 WB9JBH	34 K4BYK
17 N9ND	79 WA2RVF	1 WB8VPA	43 DJ2UU	4 WD8MGQ	40 WA1SMI	10 KOJSY	35 KB8JF
18 K4BQZ	80 KA2K	2 K4HRG	44 WD4KRK	5 WB7BFK	41 DA1MV	11 K8WD	36 HK4DUM
19 KØJSY	81 PY8ZLC	3 KE4E	45 K9MD	6 WB1DQC	42 HK4DUM	12 WA2JCX	37 S8AAT
20 N6PV	82 K4LQ	4 WA1SMI	46 N7BZ	7 KOJSY	43 WD9IIC	13 K1TH	38 IC80GS
21 KA5CQJ	83 DA1UO	5 WB3ICM	47 W20DA	8 W7ULC	44 WIAGA	14 K9PSN	39 K9TI
22 W8CHV	84 IC80GS	6 WB6VVI/9	48 K4BYK	9 K8WD	45 WB3JUK	15 W5TJQ	40 SV1IW
23 K1TH	85 DA1QR	7 WB3BAP	49 KB8JF	10 K4HRG	46 KA2K	16 WD8MOV	41 WB3JUK
24 W7ULC	86 AG5X	8 WD8MGQ	50 KB2DE	11 WD9HRH	47 K911	17 DA1MV	42 WA2RVF
25 N9ADL	87 K9BIL	9 WB7BFK	51 N9ADL	12 WD8MOV	48 K4LQ	18 WD4DVZ	43 KA2K
26 K8WD	88 N4BQD	10 WB1DQC	52 S8AAT	13 AD1S	49 N8AC	19 WB3CIW	44 9G1LL
27 WØYBV	89 WA2LYF	11 KØJSY	53 K9TI	14 WBØLXM	50 IC80GS	20 KB9IS	45 DA1QR
28 W9NAX	90 WD9HWY	12 KA5CQJ	54 HK4DUM	15 WB3ICM	51 DA1QR	21 KL7EO	46 DA5CTZ
29 WA2SRM	91 WB6CDM	13 K1TH	55 WD9IIC	16 WB7TXY	52 AG5X	22 EA6ET	47 VE3JGT
30 WD9HRH	92 WD8DEL	14 W7ULC	56 W1AGA	17 WB3CIW	53 S8AAT	23 WA2YEX	48 WB6CDM
31 WD8MOV	93 KA5CTZ	15 K8WD	57 WB3JUK	18 K1TH/9	54 KB4JA	24 N4AOJ	49 N4AKO
32 K9PSN	94 VE3JGT	16 WD9HRH	58 WA2RVF	19 F2YS/W2	55 K9BIL	25 WA2SRM	50 DF9ZP
33 AD1S	95 WD8QEO	17 WD8MOV	59 PY8ZLC	20 K8ZIP	56 WD9HWY		
34 DA1MV	96 NOAMI	18 AD1S	60 K4LQ	21 AJ8L	57 WB7PKD	73 DX COUNTRY	CLUB AWARD
35 KA3DBN	97 W8EVH	19 DA1MV	61 DA1UO	22 WBØYMR	58 WB6CDM		HODE
36 WB0I XM	98 WD0EPV	20 WBØLXM	62 IC80GS	23 AC3Q	59 WD8DEL	MIXED	MODE
37 WB7TXY	99 AI1Y	21 WB7TXY	63 DA1QR	24 SM5AKT	60 VE3JGT	1 WØANZ	12 JH1VRQ
38 WB3CIW	100 WB5SND	22 WB3CIW	64 AG5X	25 WDØEPE	61 WD8QEO	2 K4HRG	13 WB4SXX
30 F2VS/W2	101 KAAKST	23 K9PSN	65 K9BIL	26 JH1VRQ	62 NØAMI	3 WD8DNG	14 N7BZ
40 K871P	102 KB70	24 F2YS/W2	66 N4BQD	27 K9PSN	63 N4BQD	4 K8ZIP	15 W8CHV
40 ROLIF	102 ND/Q	25 K87IP	67 WD9HWY	28 WD4DVZ	64 KB8LT	5 AA8Z	16 WDØEPE
41 DROWS	TOA KPRIT	28 WA2YEX	68 WB7PKD	29 W5T.IO	65 NØGP	6 KA5CQJ	17 WA1GTO
42 WALTEA	TOF NOCO	27 4 181	69 WB6CDM	30 WD8DZO	66 KB8DB	7 K1VKO	18 WD9IIC
43 AJOL	105 NUGP	20 WRAVMR	70 WD8DEL	21 WRASYY	67 N8BJQ	8 WD8DZO	19 PY8ZLC
44 ACSQ	100 KB900	20 4020	71 KA5CTZ	22 WDAKPK	68 K5BLV	9 AC3Q	20 K4LQ
45 SM5AKT	107 AIDI	29 4030	72 VE3 IGT	32 WD4RAR	69 DJ2UU	10 WBØYMR	21 W2XQ
46 WDWEPE	108 N4AKO	30 WAZORMI	72 VE0001	24 N787	70 WB7RUV	11 K4JYD	
47 W4JYD	109 NJAKO	21 SMOANT	74 NRAMI	25 WR2RAD	71 SBAAP		
48 JHIVRQ	110 KB8DB	32 WOURV	74 NUMANI	35 WESDAF			
49 WB3BVL	111 N8BJQ	33 WUWEPE	75 NOCH	30 WOCHV		73 DX COUNTRY	Y CLUB AWARD
50 K911	112 K5BLV	SA NAATU	77 N44KO	WORKED ALL I	ISA AWARD	2X	CW
51 WD4DVZ	113 DF9ZP	35 NOAC	70 KRODR	WORKED ALL		1 4487	5 WR7PKD
52 WB2FFY	114 KB500	30 JHIVHU 27 WD4DV7	70 N8R 10	MIXEDE	SAND	2 W7111 C	6 WAYRY
53 W5TJQ	115 K8GAK	37 WD4DVZ	PO KERLV	1 KA1CBD	16 K6ARE	3 SM5AKT	7 WR2EEV
54 WD8DZO	116 K8GAK	30 WETIO	OU NODLY	2 WD8QMS	17 N8BKB	4 WDRMAS	8 WB3RVI
55 KB4JA	117 N7AHQ	39 W51JQ	01 DF92P	3 WD4RAF	18 WL7AHL	4 WDOMAS	0 WDDDVL
56 WB4SXX	118 KA4ITQ	40 WD8D20	02 SOAAP	4 KA3CBC	19 WN5MBS		
57 DJ2UU	119 WOOLL	41 KB4JA	03 WB/RUV	5 KA9DLI	20 KA4GML	WORKED AL	USA AWARD
58 WD4KRK	120 N1BCV	42 WB4SXX		6 KA4HEP	21 WB7RBH	WORKED AL	LUSAANAND
59 K9MD	121 WB7RUV			7 KL7EO	22 WD8LCE	6 ME	TERS
60 N7BZ	122 WD4LYA	OCEANIC CONT	INENT AWARD	8 KA4DNW	23 WB3BVL	UWE	
61 JA1VDJ	123 DA2AL	1 WBRVPA	28 K87IP	9 N4ACS	24 WD6EQP	1 WB0ZKG	2 K6PHE
62 K1KOB	124 S8AAP	2 KAHRG	29 A.I8I	10 N7AGD	25 KB4NJ		
		3 KEAE	30 4030	11 KA3DBN	26 WARCED	10 ME	TERS
ASIAN CONTI	NENT AWARD	4 NETK	31 SMSAKT	12 KB5NE	27 WD9GFL	1 KLZIEN	A IHADSO
1 WPOVDA	24 4 101	5 AASTK	32 WDAEDE	13 K2EQU	28 KA3CGM	2 W57K1	5 VK7NPT
1 WDOVPA	24 AJOL	6 WROLCH	33 KAIVD	14 KA6FYQ	29 KB7EY	2 VE18VD	5 WITHDI
2 141110	20 AUGU	7 WDEEEO	24 NRAC	15 K4JYD	30 AF8D	3 VEIDVD	
3 KE4E	20 SMOANT	P WDOLEG	25 IHIVDO	and the second s			
4 WOOLCM	20 INTUDO	e woewco	36 WD40V7	CENTURY CITI	ES AWARD	15 ME	TERS
2 MBCAANA	20 JHIVHU	40 WP7PEK	30 WD4DVL	CENTONI CIT	LOANAND	1 WD5DRB	3 KA6ACO
6 WD8MGQ	29 KBPSN	10 WOIDPA	37 W5130	1 K2MF	10 N8BKB	2 WARCEL	4 WB6CDM
7 WB/BFK	30 WD9DV2	12 KALEY	30 WD6020	2 WA2SRM	11 KB8JF		
8 WBIDQC	31 WSIJQ	12 10051	AD HUD LOVY	3 WD4RAF	12 WD0EPE		TEDO
a Majst	32 W08020	13 NOPV	40 WD45AA	4 KAQAZQ	13 WIAGA	20 ME	TENS
10 W/ULC	33 WB4SXX	14 KASCUJ	41 WUARAK	5 K1TH	14 KA2CLQ	1 WA9BBX	4 KB8JF
11 K8WD	34 DJ200	15 WOCHV	42 N3MD	6 K4JYD	15 KA8FOQ	2 WA9WGJ	5 WDØEPE
12 WD9HRH	35 WD4KRK	IS KITH	43 N/BZ	7 WA9WGJ	16 KA4BNQ	3 K1TH	
13 WD8MOV	36 K9MD	17 WIULC	44 JATVDJ	8 KA4HEP	17 WB6CDM		
14 AD1S	37 N7BZ	18 K8WD	45 WB3BAP	9 JH8DSC	18 AK2H	40 ME	TERS
15 DA1MV	38 JA1VDJ	19 WD9HRH	46 K4BYK			40 111	
16 WBQLXM	39 WB3BAP	20 WD8MOV	47 KB8JF	10 METER DX DE	CADE AWARD	1 WA2SRM	3 WD4DBJ
17 WB7TXY	40 W8CHV	21 AD1S	48 KB2DE	1 WB4WRE/M	4 WDØAVG	2 N8AZD	4 WDØBOS
18 WB3CIW	41 K4BYK	22 WBOLXM	49 WA1SMI	2 AC30	5 DA2AL		
19 K1TH	42 KB8JF	23 WBOYMR	50 WB7PKD	3 W5TJQ		75/80 M	ETERS
20 F2YS/W2	43 KB2DE	24 WB7TXY	51 DA1MV			10100 1	
21 K8ZIP	44 WA1SMI	25 WB3CIW	52 HK4DUM	TEN METER "10	40" AWARD	1 KAØAZQ	4 KS4B
22 WB0YMR	45 SBAAT	26 K9PSN	53 WD9IIC	I LITTLE IV	N ANAND	2 WDBBOS	5 WB9UKS

73 Magazine • December, 1980 185



from page 32

sizes: Model DTE-8 (8" wide), Model DTE-11 (10.65" wide), and Model DTE-14 (14" wide). The overall height of the series is 3.15 inches and the depth is 8.25 inches.

For further information, contact Jameco Electronics, 1355 Shoreway Road, Belmont CA 94002; (415)-592-8097. Reader Service number 479.

HEATH CONTINUING EDUCATION INTRODUCES NEW IC TIMERS SELF-INSTRUCTION PROGRAM

Heath Continuing Education has announced a new self-instruction program which covers integrated circuit timers. The new program, Model EE-103, includes an introduction to the common types of IC timers, how each works, what they do, and where they are used.

Among the types of IC timers covered are the popular 555 and 556 series general-purpose timers, the 322 and 3905 widerange, precision, monostable timers, and programmable timer/counters—including the 2240 binary programmable timer/ counter, the 2250 BCD programmable timer/counter, and the 8260 seconds/minutes/ hours BCD programmable timer/ counter. periments, completely covers how each timer works and how each is used—in logic functions, output drive circuits, timedelay relay circuits, wide-range pulse generators, phase-locked loops, universal appliance timers, and as precise clock sources.

All of the electronic components required to perform the experiments are included with the program. The Heathkit ET-3300 laboratory breadboard is a recommended option.

The EE-103 IC timers course is one of four Electronic Technology Series self-instructional programs. They are designed to provide detailed knowledge for engineers, technicians, and other technical people. Other programs in the series include Operational Amplifiers (EE-101), Active Filters (EE-102), and Phase-Locked Loops (EE-104).

For further information, contact Heath Company, Dept. 350-230, Benton Harbor MI 49022. Reader Service number 481. adjacent commercial bands. It is ideal for control links, repeater service, telemetry, and other applications for which a small unit is required. A multichannel adapter is also available to extend operation up to 5 channels.

Features include low-impedance dynamic mike and high level audio inputs; crisp, clear modulation; low spurious output; pre-wound coils; adjustable output level; and built-in test points for easy alignment. A commercial grade frequency stability option is available.

For further information, contact Hamtronics, Inc., 65F Moul Rd., Hilton NY 14468; (716)-392-9430. Reader Service number 476.

CENTURION ANTENNAS

Centurion International has introduced a new line of heavyduty telescoping replacement antennas. These antennas are full-length 1/4-wave radiators providing increased efficiency for radios that are not normally available with a telescopingtype antenna.

Three models are offered, each fitted with one of the five connector configurations: a straight telescoping antenna, a flex-spring model, and rightangle mounting model. The right-angle model is suitable for radios with front- or rear-mounted connectors or test equipment applications.



Centurion's telescoping antennas.

nectors: BNC, TNC, PL-259, F, and 5/16-32 threaded stud.

For further information, contact Centurion International, PO Box 82846, Lincoln NE 68501; (402)-467-4491. Reader Service number 477.

GILFER'S ALLBAND RECEIVER WITH 24-CHANNEL MEMORY OPTION

Gilfer Associates has just introduced in the USA the Japan Radio Company's NRD-515 communications receiver. The NRD-515 continuously tunes from 100 kHz to 30 MHz using a 100-Hz "step" photo-type encoder. Received frequencies are read to 100 Hz and the PLL-synthesized circuit can be locked to any frequency with assurance that the drift will be less than 50 Hz/hour. The rf/i-f circuit is a double conversion upverter (70.455-MHz first i-f).

The program's self-teaching text, with the assistance of review quiz questions and lab ex-

NEW HAMTRONICS® VHF FM EXCITER KIT

Hamtronics has announced a new single channel VHF FM exciter called the model T51. Patterned after the popular T50 exciter, the new unit is rated at 2 Watts continuous output and is contained on a 3- \times 5-inch PC board. It is available for the 28-, 50-, 144-, and 220-MHz bands and may be modified for use on

Exectronic factorizations

Heath's IC Timer self-instruction program.

The flex-spring model has a shock absorbing spring fitted to its base to provide the popular flexible feature. The spring is protected with a tight-fitting neoprene sleeve. The sleeve retains its flexibility from -55° C to 100° C.

All models are available with a choice of five different con-

The "kHz" tuning knob moves



Hamtronics' T51 VHF FM exciter board.

186 73 Magazine • December, 1980

10 kHz per revolution and a momentary "UP/DOWN" switch permits rapid frequency changes at 200 kHz/sec. There are no mechanical tuning stops and the all-electrical bandswitching circuit automatically tracks from MHz to MHz. Also featured in the NRD-515 are passband tuning, AM broadcast preselection, noise blanker, 10- and 20-dB switchable attenuator, variable bfo, LSB/USB/ RTTY offsets, and RIT. Four switchable selectivity options are available (two supplied).

The optional 24-channel memory unit eliminates manually re-tuning your favorite frequencies—just turn the channel selector switch and the receiver is automatically and completely re-tuned. The memory is nonvolatile and the input/output data base is a 22-bit BCD code. Other optional extras include a matching loudspeaker and CW filters of 600- and 300-Hz selectivity.

For further information, contact Gilfer Shortwave, Box 239, Park Ridge NJ 07656. Reader Service number 478.

SONY ICF-2001 PROGRAMMABLE GENERAL-COVERAGE RECEIVER

MHz AM/SSB/CW, and 76-108 MHz FM. Frequency entries are made via a standard keyboard, registered to the nearest kilohertz (nearest 100 kHz on FM). Fine tuning of CW/SSB in the 150 kHz-30 MHz range is provided by an accurately-calibrated thumbwheel.

Frequency readout accuracy is excellent, fully reliable to a few hundred Hertz. Frequency stability is outstanding; CW and SSB signals are readily copyable from power-on until you get tired of listening! A series of slaps at the cabinet caused no shift in frequency.

A built-in four-foot telescoping whip antenna is adequate for casual worldwide reception. Relative signal strength is indicated by a light bar graph composed of 5 LEDs. Signals may be peaked by the use of an antenna-resonating thumbwheel.

A series of six push-button memory channels may be used to store and recall any six frequencies between 150 kHz-30 MHz, or 76-108 MHz, depending upon which band is switched in. The low-frequency FM band allows monitoring of channels 5 and 6 of TV audio as well. And for the paranoids among us, the common bugging frequencies between 86 and 92 MHz may be searched! For the hunt-and-peck frequency hopper, the microprocessor is a dream come true. Merely load suspected channels into the six memory positions and punch up any one of them at any time. The non-volatile memory retains the frequency entries even with power disconnected. The ICF-2001 also features a scanning function. Any limits within the passband being received may be programmed, and the receiver may be automatically or manually scanned. A slide switch may be activated

for automatic stop when a signal is discovered.

Tuning is also accomplished by the push-button scanning method; any frequency displayed serves as a starting point from which up or down search begins.

Tuning or scanning speeds may be increased by another key, raising the rate from 1 kHz per increment to 10 kHz (approximately 4 or 40 kHz per second). On FM, the rate is either 400 kHz or 800 kHz per second, corresponding to 4 or 8 FM channels.

Power for the little Sony may be chosen from 3 internal D cells, 4.5 V dc (accessible from an automotive cigarette lighter using a Sony power plug accessory), or 120 V ac (power supply included). If you are tempted to use the receiver on batteries, use alkaline cells...current drain is a bone-crushing 400 milliamps! Yes, microprocessors still use a great deal of power!

But How About Specs?

The promotional and owner's literature give us little meaningful insight into the electrical specifications for the ICF-2001. A call to the factory was of little help, as even the product manager did not know. However, private measurements give us a little more information. Image rejection averages - 35 dB throughout the shortwave spectrum. The 6 dB/60 dB selectivity points are at 6 kHz and 17.5 kHz, making the 2001 a little broad for serious communications work. But it's about what could be expected from the custom 2-pole ceramic filter. As far as intermodulation and

spurious signals go, we found them no problem. In fact, we couldn't find them! Sure, they're there, but with an antenna connected and strong or weak signals being received, intermod and spurs were virtually absent.

A second i-f of 10.7 MHz (first and only i-f on FM) is used on both frequency ranges, with a first conversion i-f of 66.35 MHz on 150 kHz-30 MHz. Up-conversion is a standard technique in frequency synthesis to avoid inband i-f images.

The 2001 sports 9 ICs, 11 FETs, 42 bipolar transistors, 24 diodes, 5 LEDs, and 1 largescale IC microprocessor chip.

Swell, But Does It Work?

You bet! The ICF-2001 is an extraordinary performer for a portable. Our first experience with the little unit was with the self-contained whip antenna extended. Punching up 6 known SAC SSB channels into the memory banks, airborne and ground stations worldwide were received, solid copy. Step-tuning through the ham bands, single-sideband and CW stations were easily copied with excellent quality. No frequency drift was detectable over several minutes of portable handling, carrying the unit from room to room. Attaching the 135-foot windom antenna, we fully expected that the receiver would come apart at the seams from signal overload. Surprisingly, although signals were much louder, the receiver behaved very respectively. Some signal bleedthrough was detectable at night, but it was easily removed with the attenuator switch.

In most cases a portable radio would be only casually interesting. But most cases aren't like the new ICF-2001 from Sony.

It is evident that frequency synthesis and scanning techniques are gradually winding their ways into the manufacture of reliable, inexpensive, consumer-oriented radio equipment. The little Sony package is an excellent example.

Approximately the physical dimensions of a cassette recorder (12" \times 7" \times 2"), the ICF-2001 features a liquid crystal display frequency readout. Coverage is 150 kHz through 30



Gilfer's NRD-515 communications receiver.



Sony's ICF-2001 general-coverage receiver.

We haven't even discussed some of the other features... sleep switch, accessory jacks, LCD function displays.

In Conclusion

The new Sony ICF-2001 is meticulously designed, extremely functional, compact and flexible, and an outstanding performer. While it was never intended to compete with a Collins receiver, it makes one potent backup receiver and a fine vacation portable!

The Sony ICF-2001 lists for \$329. For further information, contact Sony Corporation, 4747 Van Damm St., Long Island City NY 11101. Reader Service number 484.

Robert Grove WA4PYQ Brasstown NC

B&W BROADBAND FOLDED DIPOLE ANTENNA

It would seem that after a century of experimentation with radiating wires, every possible configuration of single-wire antennas would have been explored and exploited. But new antennas keep popping up, proving that experimentation still is wide open in this aspect of communications.

terminated rhombic and a sloping folded dipole.

It seems that B&W is impressed enough with the commercial feasibility of such a contrivance to produce a similar antenna for both its military and its consumer market. The model 370-15 broadband folded dipole is the result.

The antenna comes fully assembled, wrapped around two cardboard tubes for shipping. It is designed for continuous frequency coverage, 3.5-30 MHz. The antenna dipole is constructed of #14 stranded 40% copperweld wire, the upper and lower dipole sections held apart by six spacers of rigid PVC pipe.

The antenna system is rated at 2.5 kW (5 kW PEP), enough to take the full power of any amateur-rated linear amplifier. Allweather construction ensures years of maintenance-free operation.

The antenna is coupled to a balun transformer and fed by approximately fifty feet of permanently-attached RG-8/U coaxial cable. A special impedance terminating network maintains the constant characteristics of the antenna throughout its usable frequency range.

but it is ninety feet long, consisting of two wires, fifty feet of cable, and other accessory accoutrements along the way! Merely keeping the copperweld wire from kinking is important and requires attention while unrolling the dipole.

B&W recommends using the allband dipole in one of three configurations: a sloper, a flattop, or an inverted V. Among the three, the sloper is the best allaround antenna. It requires only one high and one low support and it is essentially omnidirectional. The manufacturer recommends an upper height of 24 to 40 feet, allowing six feet of clearance for the lower support.

Our Experience

The ninety-foot dipole posed no particular problem in installation even when erected by one individual. By anchoring the center of the antenna, the remaining lengths are easily unfurled, ready for elevation.

Although fifty feet of coax may seem like a lot, keep in mind that a ninety-foot antenna is an imposing length to permit the coax to come close to the shack. Add to that the fact that the antenna must be removed from metallic influences (siding, electrical and power line wiring, metal roofing, air-conditioning ductwork, automobiles, etc.), and you may very well need an additional length of feedline; I did.

mounted as free from reactive materials as possible.

In the case of less-than-ideal environments, the use of an external matchbox is recommended. While the matchbox will not help the reflective and absorptive tribulations of nearby metal, it will keep the vswr at a respectable level.

Wind and ice characteristics of the antenna should prove adequate for most localities. With end supports only, 100mph winds may be tolerated-150 mph with an additional center support pole. Ice accumulation of 40-50 pounds (80 pounds with center pole) is also endurable by the system.

While the antenna is designed to operate through 30 MHz, chances are that the ferrite materials in the balun would behave at frequencies somewhat higher. It would be interesting to find out how the antenna would perform on six meters. With ninety feet of dipole length, there are bound to be some directional lobes, as there are on ten meters.

The cost of the B&W antenna is substantial, but for allband performance with no external feedline tuning necessary, it is worth considering, especially with the advent of the new amateur band plan obsoleting many present-day antenna systems. B&W's 370-15 allband folded dipole lists for \$149.50. For further information, contact Barker & Williamson, Inc., 10 Canal St., Bristol PA 19007. Reader Service number 483.

During the 1950s, a series of articles by G.L. Countryman W3HH discussed the possibilities of the "tilted terminated folded dipole." The T2FD, as it was popularly called, was a cross between a resistively-

Installation

All large dipole antennas are somewhat unwieldy to install. The 370-15 is no exception. It is recommended, although not mandatory, that two people cooperate in erecting the antenna. It is not particularly heavy,



Fig. 1. Typical installations for B&W's 370-15 allband folded dipole.

Additional feedline at frequencies below 30 MHz is no liability. Even the smaller RG-58/U would be perfectly satisfactory for another fifty feet or more if power levels on the order of 200-300 Watts are all that will be used. Line loss is insignificant.

After erecting the folded dipole as a sloper, we loaded it with a Drake TR-7 for our field trials. Sure enough, the vswr curve on all bands was very close to that shown on a graph which accompanies the instructions. Curiously, there is a vswr hump on 40 meters, rising to nearly 3:1 at our location.

With one end of the dipole tied to a 35-foot tree, we moved the lower end around the yard, testing its response on all bands. Proximate metallic masses (a power line, a utility shed, the car) showed their deleterious effects on the antenna. Clearly, the antenna must be

Robert Grove WA4PYQ **Brasstown NC**

SC-76 SCANNING MODULE

The SC-76 is a low-cost scanning module for the Kenwood 7600 and 7625. It installs in a matter of minutes, requires no soldering, and comes complete with detailed instructions. Once installed, it is placed in operation by turning the radio's mode switch to position "M". It then causes the radio to scan between the frequency in memory and the frequency on the dials. Either frequency becoming active will stop the scan. Normal operation is resumed by placing the mode switch to the simplex or offset positions.

For further information, contact Karetron Engineering Co., PO Box 241, Middletown OH 45042. Reader Service number 482.

W2NSD/1 NEVER SAY DIE editorial by Wayne Green

from page 8

read guess-what magazine and talk mostly to other old-timers...all who have 20-year-old ham gear, factory made...all you have to do is take one look at the number of pages of ads in 73 for parts. Look here, if hams weren't building equipment, those firms wouldn't spend all that money to advertise parts.

One of the hottest microwave receivers on the market today was first designed by hams. It did so well they went into business making 'em...and these are the Cincinnati Microwave "Escort" radar detectors. The hams are a bunch of chaps who split from Drake and went into the detector business...and are cleaning up. Do you think they would be doing that if they hadn't been hams and learned about that through hamming? were to become the patented reserve of another country. Perhaps as a first step in regaining world leadership in this area, we should look to Shakespeare's Henry VI: 'First we kill all the lawyers...'"

I see the fault lying not in the restrictions on the commercial field, but rather as a failure of amateur radio to provide the needed pioneering and inventing which is our responsibility ... and to hell with the FCC lawyers. I don't think it is necessary to kill them, just find honest work for them... fixing roads or something.

IT'S LOBBY TIME

A bill (HR-7747) has been entered into the legislative logjams which could cause amateur radio one hell of a headache if we don't muster our forces to beat it to death in committee.

radio is constantly being threatened by firms which want to use our frequencies for making money and are fearful that even a tiny body of people will tune in without paying in full. Rather than using sophisticated protective measures such as coding of the signals, they have tried to use their lawyers and their lobbying money to get around the FCC through Congress. Congress reacts positively to money, as we know, so it is a logical approach. Congress reacts even more positively to an outcry by the people they need even more than the lobbyistsvoters-and in this case this means you, your family, and your friends.

One ham should, with some motivation, be able to make one hell of a stink about something which is not only bad for the country, but in particular has very ominous portents for amateur radio. You know as well as I that once we let them start setting up laws prohibiting the use of the radio spectrum, it will be no time until we are not allowed to have all-band receivers or to even build experimental circuits.

WHAT WAS PURAC?

number of firms which had figured out how to get the contracts and how to fulfill them, all with a minimum of actual work and value of the end reports. Having participated in one aspect of this and having gotten a good look at how the whole system worked, I'd say it was a good move to put a stop to that boondoggle.

REPEATERS CAN SAVE LIVES

Perhaps you've read about the emergency locator transmitters (ELT) which planes have aboard. They are small VHF transmitters which are triggered in a crash to help locate the downed plane. Obviously, the sooner a downed plane can be found, the more chance there is that survivors can be saved, so every minute helps.

VHF being what it is, and planes which have crashed being on the ground in most cases, it figures that the higher you are when listening for these little low-powered ELT rigs, the better chance you will have of hearing them. So what is up in the air as high as we can put it? Repeater stations, of course.

It makes a lot of sense to me for every repeater site to have a receiver tuned to the ELT fre-

KILL THE LAWYERS?

One of our readers (W2JTP) sent along a copy of *Industrial Communications*, a most interesting newsletter which covers the mobile radio field, among others. There was an article on the state of the art in spread spectrum (SS) communications such as was pioneered by John Costas in 1959, when I published an article by him on the subject in CQ. Much of the experimentation with these techniques is presently taking place in Japan.

Let me quote Industrial Communications on the subject of why the U.S. commercial sector has not pursued this: "It appears that the principle 'wet blanket' in this regard is the regulatory atmosphere that pervades the nation's capital. The present adversary structure and rigid rulemaking are so inconducive to innovative technologies that the prudent industrialist is obliged to shift his ground in miniscule steps or not at all.

Already this native American technology is being investigated more seriously in Japan than in the U.S. It would be sad indeed if a burgeoning new field

This is a matter which should involve every amateur...individually and via action through ham clubs. If any ham club does not take action on this, they need restructuring quickly.

The bill is designed to protect the interests of the pay-TV people, who seem to be utterly paranoiac about a handful of experimenters managing to see their shows without helping to pay for the corporate jets.

Historically, the FCC has had a strict policy of protecting the availability of all radio frequencies against corporate privilege. Despite local regulations in some cities against listening to some frequencies, the FCC has stuck by their manifesto that the airwaves are the property of the people of our country, not those wishing to use them for making money or governing us. Thus it is and has been legal to tune any receiver to anything you wish.

In order to give some degree of protection to the users of radio channels, there is a rule which prohibits a listener from using information heard over the air for commercial gain or other such financial benefit.

This freedom to listen to the

This was an advisory committee set up to work with the FCC and help them to cope with the growing CB problems of the mid-70s. It was made up of volunteers who worked at no cost to the FCC to solve the CB problems. The committee was broken into eleven subcommittees, each reporting on one aspect of the interlocking problems. The committee included quite a few hams and brought forth a report which was published in three volumes...a most authoritative report. Unfortunately, due to a shortage of funds, only ten copies of the report were ever printed. The part on RFI solving is considered by many in the FCC as definitive. The PURAC committee functioned from 1976 to 1978 and was decommissioned by the FCC when the new administration came in and decided that there should be no further advisory committees.

In fairness, I gather that this demolishment of PURAC was a case of overkill, resulting from a desire to end the FCC practice of giving out contracts for reports...and paying dearly for them. This was a juicy little business in the 70s and attracted a quency so that any transmissions on this channel can be picked up as soon as they start. You still want to be able to use the repeater, so the ELT would not want to take complete control, but you might want to have the repeater stay on the air once an ELT signal was coming in, perhaps with a low-level tone modulation so you can talk over it for search coordination.

Advanced tinkerers might set up an omnidirectional antenna for normal ELT listening, with a remote switching system to change to a directional antenna which can be rotated via the repeater...and the peak signal direction (or null) indicated in some way. I'll bet we can drum up some interesting articles on how to do that! We need 'em anyway for eventual remote controlling of low-band beams via repeaters.

Every service we can supply with our repeaters is another merit badge for amateur radio. All of us should be thinking in terms of putting our expertise and equipment to the public good as often as possible... and then making darned sure the public knows about it. That's not being glory hungry or cynical about it, just being practical. If you want to attract more kids into hamming, you've got to be visible and make it seem like fun ...which should not be much of a challenge.

All is not perfect with ELT transmitters either. Sometimes one will go off unintentionally due to being set wrong, bumped, or even jarred in a bad landing. If we have more people listening to the channel, we will put pressure on pilots and technicians to be sure that errant transmissions on the ELT channel are cut to a minimum and not just shrugged off.

You may be sure that I'd like to hear about any repeaters set up to help with the ELT situation...and so would the other readers.

RADAR JAMMING

During the time when Chuck Martin WA1KPS and I were making our tests of the 10-GHz ham gear...and running up our record of making contacts from here in New Hampshire to seven other nearby states...we did not entirely ignore the possibilities of using these little rigs to interfere with police radar.

The area out in front of our Elm Street building (with the 73 Magazine ham shack) is a favorite haunt for both the local and state police. It is at the top of a hill rising from the center of town and just over the lip of the hill. The result is that cars come roaring up the wide highway and tend to ignore the 35-mile-perhour speed limit . . . after all, it is a restricted entry road, so why drive that slowly? As they come over the top of the hill, there are the police, handing out speeding tickets. On several occasions, I tried zapping these money makers with our 10-GHz ham rigs, but they never fazed them. After thinking about it, I realized that at 10 GHz the likelihood of being close enough in frequency to really interfere was remote. You have to get down to about 3 kHz and you just aren't going to be able to do that. Upon reflection, I can see that those firms making radar-jamming rigs are just selling smoke. Sure, if you tuned one of them up exactly on the channel of a radar unit, you could get it to work. But as soon as another radar came along, you'd get into trouble if you expected to cause false readings on it.

Despite the come-on mph calibration of the bogus radar jammers, I suspect that the main value of these is for 10-GHz ham experimenting. I'm sure that many 73 readers would like to see more articles on 10-GHz equipment and tests, whether the stuff will jam radar or not.

THOSE SILLY EQUATIONS

One of the more serious wastes of my time in college was the time I spent learning enough to pass the courses on calculus. I've had a fundamental rule with 73 down through the years: Edit out the math equations unless they are absolutely necessary. They rarely are, so you've seen precious few equations in 73 during its twenty years of publication.

To give you an idea of how little calculus is really needed and what a waste of time it is in school, harken to my personal experience with it. I started in college in 1940 and went for two years, thus taking two damned years of calculus. Then, urged on by the government to cut out all this college nonsense and to get out there and fight, I joined the Navy (one lousy day before the Army was going to draft me ... close call!). After a year of schooling in the Navy, I was shipped out to the fleet and spent the rest of the war...or most of it...on a submarine, making five war patrols on the USS Drum (SS228). Managing to survive that, despite stubborn efforts by both the Japanese and our own Air Force to put me into the Silent Key columns, I eventually got discharged and went back to college. Having finished all but one of the calculus courses during the first two years, all I had to do was breeze through that one remaining course. Easier said than done. I found myself with virtually a zero recollection of two years of calculus. It had never come up during the intensive Navy electronics school courses, so I'd managed to completely forget everything. This put quite a strain on my first term back at school because I had to first go back over four terms of calculus so I could hack the fifth term. Boy, did I hate that!

to sing most of several Gilbert and Sullivan operettas, but I just had no recall on calculus.

In the over 30 years since college, I have had no occasion to use any calculus, despite a wide variety of work...and the editing of several thousand manuscripts. I remember enough of it now so I am not intimidated by the use of calculus and I know that I can just edit most of it out of articles without hurting them at all.

This came to a head recently when a reader sent in a copy of a letter he'd written to *Ham Radio* magazine complaining about their excessive use of math in a W2PV article series. The writer, who is quite familiar with the math involved, took the editor to task for letting the author snow the readers with the totally unnecessary math.

One of the reasons that the scientific calculators did not achieve more popularity was that there were no instruction books available for them to explain how to make use of the scientific calculations which they made possible. Few businessmen have the vaguest notion of what chi-squared represents... and none of the calculator instructions helped them. Most of these same people would have loved to have been able to use the calculator to find out statistical data, if there had been any simple instructions on the application. The lack of such instructions has cost the calculator people dearly. I'll bet they could have made millions more in sales if such a book had been available. The technical articles in 73 are the equal of any in ham magazines, but we do try to make them easier to understand by filtering out the math which some authors want to put in . . . mostly for ego purposes. We want to make it easy and fun to learn, not scare the hell out of you.

A recent report by Stanford University indicates that there are some new techniques which hams should be checking out ... techniques which could provide us with three times as many two-meter channels as we already have. This would enable us to have three times as many unused repeaters as at present...and three times the number of happy repeater owners kerchunking away every now and then. And think of the joy in Japan when a whole new set of ham gear is needed!

The new technique, called Amplitude Compandored Sideband Radio (ACSB), has some similarities to the recently discredited Narrow Band Voice Modulation (NBVM) craze which the ARRL went through and then dropped. With this system, it is possible to have voice channels every 5 kHz on the VHF bands without interference. It also has a nice benefit in that it provides about a 10-dB improvement in reception over FM, which takes about 25 kHz or so...despite our attempts to contain it within 15 kHz.

The ACSB signal is a sideband type, but with some differences. It has a voice processor which boosts the low and high frequencies to bring up the average power of the voice ... plus it has a pilot tone about 7 dB weaker than the peak voice which keeps the receiver on tune (AFC) and provides decoding of the compandoring, a standard signal for automatic gain control (AGC) to smooth out fading and the picket fence syndrome. The pilot also has a subaudible FM tone for selective calling. In some ways this system is quite similar to my proposed automatic identification system described recently. Of course we would have to change over to sideband from FM, which would mean all new rigs. That should bring about \$500,000,000 in joy to the manufacturers. It is not difficult to change present SSB rigs for the new system, but FM gear has receivers which are far too wide for the 5-kHz channels. Needless to say, I would like to see some experimentation with this system by amateurs and some articles on it. The circuits necessary to do the pilot, the FM subcarrier, the AFC, the AGC, the compandoring, and all else involved are being integrated into an LSI chip, so our

Funny thing... I have a remarkable memory for songs, poetry, and operettas, being able

CROWD PLEASER

For a while it was beginning to look as if every newcomer to two-meter FM would eventually have his own repeater and sit there listening to it kerchunking every now and then with satisfaction. When the number of channels ran out in some areas, there were bitter fights...oddly enough, usually over the most active channels rather than those merely sitting there unused. work may not be difficult.

The 5-kHz channel spacing would mean that we could fit 80 channels between 146.00 and 146.40, where we now have 26, none of which can do well if anywhere near an adjacent channel repeater. This would give us 160 channels in the 146- and 147-MHz repeater segments of the band. With more channels, we would not need as many simplex channels and could take at least half of them for one-MHz split repeaters, giving us 200 channels in the 146-148 segment alone. That might even take care of Los Angeles for a year or two.

The pilot carrier system would fit right in with my proposed identification scheme, making it simple to locate any individual station desired. Each station would continuously send out identification, allowing you to see instantly the call of anyone using the repeater. Good-bye kerchunking and bad language.

The doubling of the range of reception for repeaters and the elimination of most of the fading problems by the system would greatly improve our repeater coverage and value. This would also help with hand transceivers, which could be made smaller due to the lower power which could be effective. Ten dB is equivalent to ten times the power, so a one-watt HT would be about the same as a 10-Watt mobile rig in effectiveness... unless we throw the power away with a rubber duckie.

the future than it is now...and that includes computers, obviously.

We're heading into a world full of micro communications devices which will put us in touch with each other at will and be able to gather information on a magnitude not even realized today. The bottom line in all of this is electronics...and how better to learn and be ahead of the pack than to get sucked into amateur radio? It happened to me and it happened to you.

Surveys show us that currently almost 90% of the teenagers who get hooked on amateur radio are going into electronics in some form. We also know that about 50% of the newly licensed amateurs are either 14 or 15 years old, so it is obvious that the growth of amateur radio is tied closely to the growth in the number of electronics oriented people...who are or will become technicians and engineers.

The Japanese took clever advantage of us when they instituted a code-free ham ticket and thus laid the groundwork for the incredible amateur population they have today. Next they got their amateurs to talk up amateur radio in the high schools and get ham clubs going. The result is that today amateur radio in Japan is known to everyone in the country and they have nearly one million hams, virtually all active. That's almost six times our active hams, and we have twice their population. Is it any wonder Japan is ahead of us in technology? As I see it, the future of amateur radio as well as the future of our country depends on how much enthusiasm our ham clubs and repeater groups can put into developing interest in amateur radio in the high schools. We need to expose these kids to hamming and get them involved with ham clubs. One approach to this is for your club to set up a demonstration ham station in the local high school and pass out literature about hamming which will explain the fun involved, the practical long-range advantages, and give details on how to get started. If you keep after 'em, you'll have plenty of kids in your classes at the club...and we'll start seeing some significant growth in amateur radio again.

club who has some experience in public speaking, you might get them to go around to the local schools and explain the advantages and fun of amateur radio. From a practical standpoint, the kids could hardly ask for a better hobby since hamming will aim them at the pot of gold ahead in electronics.

When it comes to being a success in life, it is a lot easier to make it in a field which is growing than in one where the field is dying...such as education. I give a lot of talks to groups on the fundamentals of success and I usually start out by explaining that there are several time-proven ways of investing your life so that you will never be a commercial success...never be able to make much money. One is to go into teaching. Now this may be very rewarding in spirit, but it sure results in very few yachts and planes...or security. Then there is working for the government, which does have security, but at one hell of a price in salary and opportunity. Another big loser is working for a large corporation. Again there is a tight lid on salaries, though a mere handful do manage to work up into the 90% income tax bracket. It's a tough way to go...and you can get canned at any time. So if the direction that our colleges and all the media push on us aims us at losing, how can we aim kids at careers which will give them the probability for making real money? The secret to being successful is to plan for it and work at things which will have a good chance of resulting in getting rich. Certainly, considering the growth which has come about in electronics (and computers), this is a lot better field to go into than English, art, or law. Just what we really need is more lawyers. Hamming is particularly good because it gets kids into the habit of thinking about their life's work more than the usual eight hours a day. Hams never really stop thinking about their interest. Hundreds of hams get ideas for new products and start up small firms to make them... and a few of these pan out well and we have big firms such as Drake resulting...Electro-Voice, etc. Others go for a while and then fade away, but the experience gained by the entrepreneur is invaluable and will surface later. When I meet the

heads of medium-sized firms in electronics, it is rare that I don't find a ham heading things up.

So get out there and spread the contagion...let's get the ham virus going in high schools. You'll enjoy seeing your handiwork...the kids will certainly benefit...amateur radio will grow and perhaps we can even get the leadership in electronic technology back from Japan.

THE CODE-FREE HASSLE

Some years ago, in response to the pressures from the CB industry, I could see a concerted move afoot to grab the ham 220-MHz band. I thought we might be able to fight this off with some stratagems, but I wanted to make sure that we were as well covered as possible so I came up with a no-code ham ticket proposal for the 220-MHz band.

My strategy was to give the CB manufacturers an out which would sell equipment for them ... possibly as well as making 220 into a CB band, but which would still leave it a ham band and thus not force hams out of it. The growth of hamming, which this would bring about, was needed...and still is. By starting people in as hams instead of CBers, I felt that we could exert ham influence on them to upgrade much more than we could if they were just CBers. The license that I proposed was not a sign-it-and-own-it CB ticket, but one which would be granted by ham clubs only after people interested graduated from ham training classes and passed exams in very simple theory, operating techniques, and rules. I felt this would, at the same time, put the new licensees in touch with clubs where they could continue on to higher classes of license and experience the ham spirit. The proposal I made also specified that the no-code license part of the band would be bordered by parts of the band open only to higher classes of license such as Technicians. I had in mind the use primarily by repeaters which would have to be operated by higher class licensees and would thus give the newcomers a good introduction to amateur radio and make sure that they did not think of it as CB. That, plus the ham club license classes, I felt, would get these new people aimed in a

Let's see what we can do to pioneer this idea.

INFECTING THE ACNE SET

Now that it is no longer unpopular to be successful, it may be possible to carry the message about amateur radio into the high schools and turn on the students to hamming instead of pot or the development of a lifelong dependency on tobacco or booze.

The fact is that we have one hell of a message for the kids, for not only is hamming fun, but it also is one of the best keys one can find these days to getting an edge on the future. Is there any question in your mind that the electronics field is not going to keep right on growing at a healthy rate for the next 50 years? Every sign is that electronics is going to be more mixed into everything we do in

If you have someone in your

good direction.

If the band were set up with repeater inputs from, say, 220.5 to 222.0, and outputs from 223.0 to 224.5, this would provide a half meg on each end of the band for higher class operators (and repeaters) plus a full meg in the middle for higher class...or perhaps split with half of it for the new class simplex and half for higher class.

With 220 still not very much used in most areas of the country, this concept could still fly.

The plan did cause some weakening of the CB industry ranks and it helped us in that respect. I also got after my friends in Mexico and Canada to put on their pressures to stop the CB takeover of 220 and that had even more of an impact.

When I first proposed the nocode license, the ARRL was opposed to it. Then, as pressures from the industry mounted, they flopped over and were in favor of it. Now I understand that they are opposed again.

Seeing what a no-code ticket has done for Japan, with many benefits and no detectable drawbacks, I'm still very much in favor of the idea. I was more enthusiastic before Dick Bash started publishing his detailed cheat sheets on the FCC licenses, which essentially cancelled their effectiveness. Right now the only thing between anyone wanting a ticket and having it is the code or being too cheap to buy the Bash cheatos. Until we are able to resolve that mess, I'm not inclined to push for going to a purely written nocode ham test.

If we could set it up as I had proposed with ham clubs issuing the licenses to those people who had taken and passed their courses on being a ham, I would again favor a no-code situation. There are some problems to be resolved before clubs would be able to have the right to issue tickets. I would like to see amateur radio get more autonomous, having much more of a say in our regulations and the granting of licenses. We might be able to work out a system where we could get needed rule changes made in less than ten years, thus allowing amateur radio to keep up with technological developments instead of having to stay at least ten to twenty years behind.

If you have any well-thoughtout ideas on a no-code license situation, please write in. None of us needs any emotional outburst or other red-neck responses...just good ideas.



from page 12

Frankly, I have a feeling that this is where the problem in relation to this dismissal order comes from.

While I cannot speak for the Commission, I can surmise what transpired. Mr. Talley submitted his petitions under the assumption that the Commission understood amateur radio's internal interpretation regarding repeater categorization. He even told me that his opposition was toward repeaters that required one to become a member of some club or organization in order to use the repeating facilities. Again remember, we in amateur radio consider closed and private repeaters as those which restrict system access to club members. But the FCC did not read it that way. To the Commission, an open repeater is apparently one that offers no control over system operation, either technically or operationally. At least that's what seems to come to light when you read the dismissal order.

parently looked upon Mr. Talley's request as one of removing all controls and guidance from repeater operation and reacted along those lines. Unfortunately, they may well have set an unwelcome precedent and started us on the road toward reregulation rather than continuing with deregulation. repeater categorization. In my opinion, the defeat of RM-2844 was justified, but not for the reasons noted in the dismissal order. Had it been stated that the reasons I have outlined were the basis of their decision to deny, then I could agree with it. Maybe it's time that we in amateur radio begin to educate those who regulate our service, get them to understand our terminology and definitions in regard to our day-to-day operations. If this can be achieved,

SHOULD THERE BE PRIVATE REPEATERS DEPARTMENT

In any discussion, we must first set some ground rules for understanding. In this case, I feel it is best that we begin by reviewing the definitions of the three categories of repeater operation as accepted within the amateur community. Over the years, the following definitions have developed:

Open Repeater: An amateur relay device placed into operation by an individual or group to

Therefore, if my guess is right, a system that has some form of control is looked upon as a closed or private repeater. It seems to have become a problem of semantics. They have never bothered to reseach what we in the amateur community accept on a day-to-day operational level. The Commission ap-

Even more unfortunate is that in using the rationale they have, the Commission has overlooked the true intent and purpose of Mr. Talley's filings. In my view, Mr. Talley was actually raising a Constitutional issue. His contention is that amateur repeaters should be by law available to any qualified licensed amateur. I oppose this because it is my sincere belief that to force anyone operating a repeater to make it available to anyone is akin to forcing him to provide a service for another person that he may not wish to provide for that person. If you are going to open all repeaters to all qualified amateurs, then, by the same token, you also must make all individual amateur stations available to all qualified amateurs, regardless of where such stations are located.

The concept of forcing one amateur to provide a service for another is what I object to, and this has nothing to do with either amateur radio's or the Commission's interpretation of then we can really get on with things.

There is nothing wrong with the system by which regulations governing our hobby are generated. For the most part, it is people like you and I who generate them, for better or worse. We are very lucky: In most other places, rules are simply by government decree. There is nothing that the amateur can do but abide by them without recourse.

Here, in America, we can help generate and guide the destiny of amateur radio through the public rulemaking procedure. This is a liberty we must cherish and utilize for the good of our hobby. But we also must find a way to overcome the semantics problem so that when we talk about open repeaters, the FCC understands our meaning and we theirs. When we speak of modes, power levels, or anything else, each must know the meaning of the other's words. This will go a long way in developing more positive lines of interaction between those of us who comprise the amateur community and the agency that regulates our operations.

serve the needs of all licensed and qualified amateurs in a given area. In most cases, no form of tone access is necessary to access such a system.

Closed Repeater: An amateur relay device which requires that one become a member of the sponsoring organization to gain use of the relay system facilities. However, membership in such organizations is open to any interested amateur licensee.

Private Repeater: An amateur relay device which, like the closed repeater, requires membership in the sponsoring organization. However, the availability of such membership is at the discretion of the system licensee. Both closed and private repeaters are usually tone accessed, and such access tones are considered to be proprietary information.

If we accept these as our definitions of operational categorization, then a question arises. Should the latter two be permitted to exist in today's amateur society? It probably depends upon where you reside, conditions of crowding on various bands, and, most importantly, your own personal taste. I cannot comment on the last, but in regard to the others, I have a number of words, some of which will not make the owners of closed and private repeaters too happy. What I have to say differs from earlier commentary that has appeared over the years in this column, but this is because of the ever-changing face of the amateur service itself.

If you live out in the boondocks where nobody cares, you can basically do your own thing and nobody will say boo. If there are only three or four repeaters in your area and a clear band, then I do not think anyone will really care what category of operation you choose. However, in crowded urban areas where one finds a repeater or two every 15 kHz between 146 and 148 MHz and the same condition every 20 kHz from 144.5 through 145.5 MHz, then the two-meter band is no place to start or continue a closed or private device. Two meters has become "the people's band" and, for the most part, "the people" want and demand access to the entire spectrum. While densely populated metro areas might have been able to tolerate a number of private repeaters on two meters only a few short years ago, with today's spectrum crunch it may be time for those wishing this category of operation to look toward greener, less occupied spectrum.

the past several years, I have been invited onto a number of private two-meter systems here in the Los Angeles area, but each time have declined such an invitation. Yes, there is a place in our society for those who want their privacy and there is nothing wrong with their wanting it. But the urban private repeater of today, operating within the crowded confines of the two-meter band, is somewhat akin to a case of the flu. Neither is very welcome anymore. As time progresses and the spectrum crunch tightens, they will probably become a definite liability within our amateur community.

On the other hand, there are bands with practically no utilization. This holds true even for areas where the two-meter band is saturated with 24-hour-a-day activity. Such spectrum would welcome any activity, private or otherwise. This is where such systems belong, out of the mainstream of today's amateur activity. Further, those wishing the luxury of operation on such a system should be prepared to spend the extra bucks for the necessary equipment, be it on 6 meters, 220 MHz, or 450 MHz. If you want the luxury, then be prepared to pay the price tag that comes with it. After all, the vast majority of those using the twometer band are not that interested in getting on a private or closed system. For most, amateur radio is a recreation and not an avocation. I can see no reason to displace the masses in deference to the few. I do not

condemn private or closed operations. They have their place within the structure of amateur radio society and as such serve a definite purpose. Many of the earliest systems had restricted access, and from them has come much of the open operation of today. However, in areas where the two-meter band is overflowing with activity, where the coordinator or coordination council has a waiting list a yard long for new open repeaters, the closed and private category system should take a back seat to the will of the majority.

SIX-METER BAND PLANNING, CONTINUED

The band plan outlined in the September issue on page 163 has begun to get some response. What I find very scary is that thus far I have not received any negative commentary. Some suggested changes, yes, but nothing that says "NO" emphatically. One important addition that I want to note concerns the existence of another Pacific DX corridor. It was not brought to my attention prior to the formulation of the band plan and therefore was not included. would fall under a voluntary program and not be part of the amateur rules and regulations. It would be exactly the same as the Pacific DX corridor that exists from 52.0 through 52.1 MHz. I might suggest that you pencil this into the band plan for future reference.

For the moment, that's about it in regard to six meters. More on the subject will be included in future columns and as comments come in.

FINAL UPDATE ON STORY ONE

We opened this month's column by reporting on the dismissal order to RM-2844, an order that on the surface seems to eliminate open repeater operation. We also included a scenario on what we hypothesized as being the sequence of events leading up to it. Well, information we have gathered seems to point to this being similar to what really happened.

It appears as though the order was given to a member of staff to prepare the document. The person was not all that familiar with Part 97 as it governs repeater operation and wrote the document based upon his own understanding. After its release, a number of inquiries were made to its validity and it was brought to the attention of a senior member of the staff who agreed that its wordage was somewhat contradictory to the rules as written. A clarification has been promised. It should be forthcoming and we may have it for next month's column. I hope that it will clear the air.

I have no qualms with closed and private repeaters. In fact, I freely admit to being a member of two such entities, but neither of these are on two meters. Over A second Pacific DX corridor does exist from 51.0 through 51.1 MHz. It has been around for some time but never has been given very much publicity. So, if we were to obtain deregulation down to 51 MHz for FM relay operations, in some areas it might be wise to keep FM away from this small slot to protect weaksignal operations. Again, this



from page 24

what about the other 99% of the time? Unfortunately, although they expect us to operate in the public interest, we really can't expect them to do likewise.

If the FCC doesn't resume testing in Germany, there is only one option left. That is to reinstate the Conditional class license which we had many moons ago. If this can't be done, then they should put the testing program in the hands of the Extras. The FCC would undoubtedly balk at a suggestion such as this because of past problems concerning "mail-order" Technicians. But I am sure that the Extra class hams can run an honest and sound testing system not only for amateurs, but also for the commercial applicants. I have already earned my Extra class ticket, but I am speaking for the hundreds of hams and those desiring their phone Iicenses. In closing, all I can add is that "the FCC giveth, the FCC taketh away."

Harry A. Schools KA3B/DA2AL APO NY

Thanks for the letter, Harry; you are expressing what I heard everywhere I went in Europe a few months ago. Perhaps someone should petition the FCC to solve the problem with an overseas Conditional license arrangement? The major problem, both with lack of growth of the hobby and with the FCC problems, stems from our lack of a lobby to push for amateur radio in Washington...and in particular with the FCC. It is completely unfair to blame the FCC for acting like any other government bureau and reacting to lobbying pressures which are on them from all sides...except amateur.— Wayne.

IT'S A MESS

Every time I read an article or letters from readers regarding FCC decisions, which are usually negative, causing more government control of amateur radio and more restrictions, I wonder if the founders of the Federal Communications Commission were of this mind?

Amateur radio has been the victim of the Commission's inability to cope with their bum decisions on CBers. But the worst of all is the alphabet soup call letters of all descriptions. As I see it, it is further degradation of amateur radio. We used to be able to tell where a particular callsign would originate from, but not now; it's a mess! Possibly, they want to fracture this sacred organization, i.e., to make it like CB. I surely hope not.

I have been a licensed ham since 1939 and I still enjoy ham radio. This brings to mind a recent overseas contact on 20 CW with a ham in northern Norway. My comment that I had been an amateur since 1939 brought this response: "I, too, am an old-timer, receiving my first ticket in '38, and I dearly love my hobby."

Henry S. Mitchell Seattle WA

Henry, a lot of us grumble about the FCC, and certainly some of the rules they put through are for political reasons and not in the best interests of the hobby ... but then we have virtually no lobby there to deal with the FCC and guide them in a positive way, so we can expect no more than we get. When you are dealing with government, you have to do things the government way, and this means lobbying for your hobby. It is useless to get mad at the FCC for acting perfectly normal and hold blameless the real villains... the people we are paying to represent us.-Wayne.

mum, or at $\lambda/2$ intervals from the feedpoint. I have found that a choke coil like yours placed at the feedpoint of a dipole is *much* more effective at eliminating rf on the feedline than a conventional balun. I no longer use a balun, just a choke.

"Field strength measurements have shown that the radiation pattern of a dipole antenna is drastically altered when there is rf on the feedline, but the addition of a choke at the feedpoint corrects this problem.

"I first found that I had rf on the feedline when I noticed that the swr was different at different points along the feedline. With the choke installed, this problem goes away.

"P.S. If you resonate the choke with a variable capacitor the results are even better!"

Thanks for the interesting feedback, Al. Resonating with a capacitor had not occurred to me, but for single-band operation, an improvement could certainly be obtained by this expedient. For allband operation, it would be best to stick with the choke method. Another application for choke isolation of undesired antenna currents comes to mind. This is the suppression of rf energy from the shack when necessary to eliminate rf burns resulting from contact with "hot" equipment.

there is a good chance he is where he says he is. But remember one thing, Hugh: If I haven't worked a particular country, that's DX for me and the chap visiting is on a valid DXpedition. The bottom line is fun... the fun of working DX for us and the fun of being DX for you—Wayne.

OPERATOR'S LICENSE

With regard to the new flap over the tactics of Mr. Bash and his "educational services," I would like to add some additional comment.

Personally, I never could understand why someone had to have an understanding of the workings of electronics to become a ham. Frankly, it stems from the old days when you had to put things together (homebrew) to even get on the air. Today we are flooded with state-ofthe-art rigs. Who needs home brew unless you are personally interested in doing that; why do I have to know the stuff?

Before someone jumps on me, I'd better mention that I have a background in electronics and work for an electronics firm here and was originally licensed in 1957. all this theory is for the people that really like it. Heck, you can get a pilot's license without knowing how to fix the plane. Too many old folks reluctant to make change stagnate anything they are involved in. Let's wake up and revitalize ham radio. Now is the time.

Alan Davis KB7HM Salt Lake City

Let's hear it for the code-free, theory-free license.—Wayne.

KEEP IT SHORT

I am pleased that you have seen fit to promote 10-meter FM in 73.

As one who has been on 29.6 for many years (at the bottom of the sunspot cycle), I am disturbed at the new arrivals on 29.6 complaining about people who aren't QRP or running a converted CB. (Everyone else is using excessive power.) I welcome these newcomers and hope they will contribute to the band. The fact that most have converted a CB or old mobile rig places them among the few hams who are not merely appliance operators.

QRP contacts are an everyday thing on 29.6, but they are usually brief. I would hope that for the first few exchanges, the QRP operator would keep it short-QTH, handle, rig, signal report. As exchanges prove the band is holding up, then rag chew. Over 50% of my contacts were fading into the noise before I could get basic information, so I have stopped calling the marginal ones. The newcomers are probably not aware that 1 kW and a 5-el beam on 29.6 will provide a fade margin for long, frequent contacts while they are fading into the noise. Hopefully, everyone will be able to coexist on this small piece of 10 meters. QRP signals are great for studying propagation, and we all have lots to learn. My hope is that some of these QRPers will see the value of power and gain before we hit a low in the sunspot cycle. There is a whole world of 600-1200-mile sporadic-E activity while 20/15 meters are closed, but a QRP will be unable to take advantage of it.

ANTENNA CHOKES

I've received an interesting letter from AI Stahler AD6G commenting on my article, "Check Chirp with a Choke," which appeared in the June issue. Al comments as follows: "I've used a similar device in all of my antennas-but for a slightly different reason. The idea is to remove rf from the feedlines. King, in his book Transmission Lines, Antennas and Wave Guides (Dover, 1965), page 151, states that common mode currents, i.e., antenna currents on the outside of a coax or antenna currents on both conductors of a parallel feedline, can be de-tuned or eliminated by placing a high impedance to these currents at a point on the line where the current would be maximum.

"For a dipole antenna, the optimum location for the high impedance would be at the feedpoint where the current is maxiStanford J. Solms WA2MEL Sunnyvale CA

FUN-PEDITIONS

Caribbean vacation spots are certainly *not* DXpeditions—they are DX operations or are sometimes called fun-peditions. Let's start putting DXpeditions vs. DX operations in true perspective. True DXpeditions include, but are not limited to, for example, Malpelo, Bouvet, Okino Torishima, Spratly, et al. My *new* show is *all* of these plus many others. Hope you can catch my show on the circuit. It's a great show.

Hugh G. Vandegrift WA4WME Killeen TX

We'll be looking for you, Hugh, and be sure to take a lot of good color pictures for the write-ups on your trip. One of the problems with some of the earlier DXpeditions to many of the places you mentioned was that they were fakes. At least when someone says he is on a fairly rare island in the Caribbean, The second state in the second state

Most everyone today is an appliance operator anyway. What we need is a test that makes all potential operators have a thorough knowledge of the rules of the road, proper operating procedures, proper use of radios and tuning up, and etiquette on the air. As far as I am concerned, it is no different than a license to own or operate a car, truck, gun, fishing rod, camper, or whatever. Look at all of the people out there that took a driver's test many years ago in a car and go out and buy a big camper, get behind the wheel, and create a menace on the highways. (This is not to say that many people don't drive campers well.) I fail to see a big difference. Who really cares what a MOSFET does, or a diode, or a spark plug, as long as the rig/car works. Some folks would not know a spark plug from a rotor.

I endorse and support Mr. Bash, will use his services, provide feedback, and do whatever else I can. To those that scorn him, I detect a note of jealousy (these services were not available to them) and a desire to maintain some elitist group. We should keep the code as it is, but

Les Whittaker Jr. WB0PXA Miami FL



№64 2822 North 32nd Street, #1 • Phoenix, Arizona 85008 • Phone 602-956-9423

2N2857JAN	\$ 2.50	2N6097 \$28.00	ORDERING INSTRUCTIONS
2N2949	3.60	2N6166 38.00 0	heck, money order, or credit cards
2N2947	15.00	2N6368 22.99 weld	come. (Mastercharge and VISA only)
2N2950	4.60	2N6439 40.00 No p	personal checks or certified personal
2N3375	8.00	A210/MRF517 2.00 chec	cks for foreign countrys accepted.
2N3553	1.57	BLY38 5.00 Mone	ey order or cashiers check in U.S.
2N3818	5.00	40280/2N4427 1.10 fund	is only. Letters of credit are not
2N3866	1.00	40281/2N3920 7.00 acce	eptable.
2N3866JAN	2.50	40282/2N3927 10.48 M	Ainimum shipping by UPS is \$2.35 with
2N3866JANTX	4.00	insu	rance. Please allow extra shipping
2N3925	10.00	NE555V TIMERS char	ges for heavy or long items.
2N3948	2.00	<u>39¢ each or 10/\$3.00</u> A	11 parts returned due to customer error
2N3950	25.00	will	be subject to a 15% restock charge.
2N3959	3.00	NEW DUAL COLON LED	f we are out of an item ordered, we
2N3960JANTX	10.00	69¢ each or will	try to replace it with an equal or
2N4072	1.60	10/\$5.00 bett	er part unless you specify not to,
2N4427	1.10	or w	we will back order the item, or
2N4429	7.00	HEP170 1000 PIV refu	ind your money.
2N4877	1.00	2.5 Amps 25¢ each or P	PRICES ARE SUBJECT TO CHANGE WITHOUT
2N4959	2.00	100/\$15.00 NOTI	CE. Prices superseade all previously
2N4976	15.00	publ	ished. Some items offered are
2N5070	8.00	HIGH VOLTAGE CAPS Timi	ted to small quantities and are
2N5071	15.00	420 MFD @ 400 VDC OR subj	ect to prior sale.
2N5108	4.00	600 MFD @ 400 VDC W	e now have a toll free number but
2N5109	1.50	\$6.99 each we a	isk that it be used for CHARGE ORDERS
2N5179	1.00	ONLY	. If you have any questions please
2N5583	4.00	NEW ROTRON BISCUIT FANS use	our other number. We are open from
2N5589	6.00	Model BIZAT TIS VAC 8:00	a.m 5:00 p.m. Monday thru Saturday.
2N5590	8.00	\$12.99 each 0	ur toll free number for orders only
2N5591	11.00	15 0	00-528-3611.
2N5035	5.44	TUKIN TA/OU FANS NEW	
2N5030	11.00	Model A30340 JUMB	O LED'S MEDIUM LED'S
2N503/	20.00	230 VAL @ ./o Amps R	lea 0/\$1.00 Ked 0/\$1.00
2N5041	5.00	WITT also work on 115 VAC C	allow 6/61.00 Green 0/\$1.00
215043	14.00	<u>329.99 each</u>	errow 0/\$1.00
215045	8.00		mbor 6/\$1.00
215042	20.00	UTO OF O LE KY C2 00 020	hiber 0/31.00
215049	20.00	4/0 p1 @ 15 KV 5.99 eac	NEW C E OPTO COUPLERS 4N26
2115942	14.00	680 of 6 KV 3.99 eac	h 694 each or 10/\$5.00
2115940	50.00	800 pf @ 15 KV 3 99 eac	h
2115002	7.00	1000 pf @ 19 KV 5.00 eac	MICRO-MINI WATCH CRYSTALS
2N6081	10.00	2700 pf @ 40 KV 5.99 eac	h 32 768 Hz \$3.00 each
2N6082	11 00	2/00 pi (10 kt).)) cao	<u></u>
2N6083	13 00	NEW & LISED BCD SWITCHES	NEW 2 inch ROUND SPEAKERS
2N6084	14.00	3 switch with end plates	100 0hm coil 99¢ each
2N6095	11.00	New \$8,99	
2N6096	20.00	Used \$6.95	PLASTIC TO-3 SOCKETS 4/\$1.00
		NO ORDERS UNDER \$10	
and the second s			

2N285/JAN	\$ 2.50	20009/ \$25.00	ORDERING INSTRUCTIONS
2N2949	3.60	2N6166 38.00	Check, money order, or credit cards
2N2947	15.00	2N6368 22.99	welcome. (Mastercharge and VISA only)
2N2950	4.60	2N6439 40.00	No personal checks or certified personal
2N3375	8.00	A210/MRF517 2.00	checks for foreign countrys accepted.
2N3553	1.57	BLY38 5.00	Money order or cashiers check in U.S.
2N3818	5.00	40280/2N4427 1.10	funds only. Letters of credit are not
2N3866	1.00	40281/2N3920 7.00	acceptable.
2N3866.JAN	2.50	40282/2N3927 10.48	Minimum shipping by UPS is \$2.35 with
2N3866.IANTX	4.00		insurance Please allow extra shinning
2N3925	10.00	NE555V TIMERS	charges for heavy or long items
2N3948	2.00	39¢ each or 10/\$3.00	All parts returned due to customer error
2N3950	25.00	220 0001 01 10142.00	will be subject to a 15% restock charge
2N3959	3 00	NEW DUAL COLON LED	If we are out of an item ordered we
2N3960 IANTY	10.00	694 each or	will try to replace it with an equal or
211390034114	1 60	10/\$5.00	better part uplace you spacify not to
2140/2	1.10	10/32.00	or we will back order the item or
211442/	7.00	HEP170 1000 PIV	of we will back order the item, or
214429	1.00	2 E Amps 2Et arch or	DDICES ADE SUDJECT TO SUANCE VITUOUT
2140//	1.00	2.5 Amps 25¢ each or	PRICES ARE SUBJECT TO CHANGE WITHOUT
2N4959	2.00	100/\$15.00	NUTICE. Prices superseade all previously
2N49/6	15.00		published. Some items offered are
2N50/0	8.00	HIGH VOLTAGE LAPS	limited to small quantities and are
2N5071	15.00	420 MFD @ 400 VDC OR	subject to prior sale.
2N5108	4.00	600 MFD @ 400 VDC	We now have a toll free number but
2N5109	1.50	<u>\$6.99 each</u>	we ask that it be used for CHARGE ORDERS
2N5179	1.00		ONLY. If you have any questions please
2N5583	4.00	NEW ROTRON BISCUIT FANS	use our other number. We are open from
2N5589	6.00	Model BT2A1 115 VAC	8:00 a.m 5:00 p.m. Monday thru Saturday.
2N5590	8.00	\$12.99 each	Our toll free number for orders only
2N5591	11.00		is 800-528-3611.
2N5635	5.44	TORIN TA700 FANS NEW	
2N5636	11.60	Model A30340	JUMBO LED'S MEDIUM LED'S
2N5637	20.00	230 VAC @ .78 Amps	Red 8/\$1.00 Red 6/\$1.00
2N5641	5.00	Will also work on 115 VAC	Clear 6/\$1.00 Green 6/\$1.00
2N5643	14.00	\$29.99 each	Yellow 6/\$1.00
2N5645	10.00		Green 6/\$1.00
2N5842	8.00	DOOR KNOB CAPS	Amber 6/\$1.00
2N5849	20.00	470 pf@ 15 KV \$3.99	each
2N5942	40.00	Dual 500 pf @ 15 KV 5.99	each NEW G.E. OPTO COUPLERS 4N26
2N5946	14.00	680 pf @ 6 KV 3.99	each 69¢ each or 10/\$5.00
2N5862	50.00	800 pf @ 15 KV 3.99	each
2N6080	7.00	1000 pf @ 20 KV 5.00	each MICRO-MINI WATCH CRYSTALS
2N6081	10.00	2700 pf @ 40 KV 5.99	each 32.768 Hz \$3.00 each
2N6082	11.00		
2N6083	13.00	NEW & USED BCD SWITCHES	NEW 2 inch ROUND SPEAKERS
2N6084	14.00	3 switch with end plates	100 Ohm coil 99¢ each
2N6095	11.00	New \$8.99	
2N6096	20.00	Used \$6.95	PLASTIC TO-3 SOCKETS 4/\$1.00
		NO ORDERS UNDER \$	10
			TRAFT OF THE REPORT

Save on Scanners! NEW Rebates!

Communications Electronics," the world's largest distributor of radio scanners, celebrates Christmas early with big savings on *Bearcat* synthesized scanners. Electra Company, the manufacturers of *Bearcat* brand scanners is offering consumer rebates on their fantastic line of crystalless scanners purchased between September 15 and November 15, 1980.

We give you excellent service because CE distributes more scanners worldwide than anyone else. Our warehouse facilities are equipped to process thousands of scanner orders every week. We also export scanners to over 300 countries and military installations. Most items are in stock for quick shipment. Do your Christmas scanner shopping early and order today from CE!

Bearcat[®] 300

The Ultimate Synthesized Scanner! List price \$519.95/CE price \$329.00/\$20.00 rebate Your final cost is a low \$309.00

4-Band, 50 Channel
Service Search
Nocrystal scanner
AM Aircraft and Public Service bands.
Priority Channel
AC/DC

Bands: 32-50, 118-136 AM, 144-174, 421-512 MHz. The new Bearcat 300 is the most advanced automatic scanning radio that has ever been offered to the public. The Bearcat 300 uses a bright green fluorescent digital display, so it's ideal for mobile applications. The Bearcat 300 now has these added features: Service Search, Display Intensity Control, Hold Search and Resume Search keys, Separate Band keys to permit lock-in/lock-out of any band for more efficient service search.

FREE Bearcat® Rebate Offer

Get a coupon good for a \$20 rebate when you purchase a Bearcat 300, 250, 220 or 210XL, \$10 rebate on models 211, 210 and 160. To get your rebate, mail this coupon with your original dated sales receipt and the Bearcat model number from the carton to Electra. You'll receive your rebate in four to six weeks. Offer valid only on purchases made betwen September 15, 1980 and November 15, 1980. All requests must be postmarked by November 29, 1980. Limit of one rebate per household. Coupon must accompany all rebate requests and may not be reproduced. Offer good only in the U.S.A. Void where taxed or prohibited by law. Resellers, companies, clubs and organizations-both profit and nonprofit-are not eligible for rebates. Employees of Electra Company, their advertising agencies, distributors and retailers of Bearcat Scanners are also not eligible for rebates. Please be sure to send in the correct amount for your scanner. Pay the listed CE price in this ad. Do not deduct the rebate amount since your rebate will be sent directly to you from Electra. Orders received with insufficient payments will not be processed and will be returned.

NEW! Bearcat® 160

List price \$279.95/CE price \$189.00/\$10.00 rebate Your final cost is a low \$179.00

16 Channels • 3 Bands • AC only • Priority Dual Scan Speeds • Direct Channel Access Frequency range: 32-50, 144-174, 440-512 MHz. The Bearcat 160 presents a new dimension in scanning form and function. The keyboard is smooth. No buttons to punch. No knobs to turn. Instead, finger-tip pads provide control of all scanning operations, including On/Off, Volume and Squelch. Green easy to read fluorescent display.

NEW! Bearcat® 5/800 MHz The world's first 800 MHz. scanner!

This is a new model. Shipments will begin in December, 1980. List price \$179.95/CE price \$129.00

8 Crystal Channels • 4 Bands • AC only Frequency range: 33-50, 144-174, 440-512, 806-870 MHz. The Bearcat 5/800 MHz is the only scanner on the market today that offers coverage of the 800 MHz. public service band and the other public service bands. Individual channel lockout. Scan Delay. Manual Scan.

Bearcat[®] 5

List price \$129.95/CE price \$89.00 8 Crystal Channels • 3 Bands • AC only

Frequency range: 33-50, 146-174, 450-508 MHz. The Bearcat 5 is a value-packed crystal scanner built for the scanning professional — at a price the first-time buyer can afford. Individual lockout switches.

Bearcat[®] Four-Six ThinScan[™] List price \$179.95/CE price \$114.00

Frequency range: 33-47, 152-164, 450-508 MHz. The incredible, new Bearcat Four-Six Thin Scan[®] is like

NEW!Regency® M400

List price \$379.95/CE price \$259.00 30 Channel • Synthesized • Service Search Digital clock • Digital timer • M100 styling Search/Store • Priority Channel • AC/DC Frequency range: 30-50, 144-174, 440-512 MHz. The new Regency M400 is a compact programmable FM monitor receiver for use at home or on the road.

(DTHE	RRI	EGE	NCY	SCAN	INERS	
ouch	K100				and the second	\$1	99.00
ouch	M100					\$1	99.00

NEW! Telephone Products

Electra's cordless Freedom Phone does everything an ordinary phone does and more. Because it is cordless, you can take it anywhere, inside or outside—on the patio, by the pool, in the garage, in the workshop...even next door at the neighbor's.

Model FF-500 has pushbutton dialing. Rechargeable ni-cad batteries included. Battery low light. Secure feature. Telescopic antenna. Your cost is \$179.00. Model FF-1500 has the same features as the FF-500 but also includes a charger/cradle that allows the phone's handset to be recharged away from the base station. Your cost for this cordless phone is \$199.00. The model FF-3000 has all the standard features (except charger/cradle) plus interchangeable telescopic and rubber ducky antenna. Redial feature. Belt clip. Carrying case. Greater range. Your cost is \$229.00.

World Scanner Association"

The WORLD SCANNER ASSOCIATION is sponsored as a public service by **Communications Electronics**." When you join, you'll receive a one-year membership and our quarterly newsletter with scanner news and features. You'll also get a wallet I.D. card, an Official WSA Membership Certificate, and more. FREE classified ads for members so you can contact other scanner owners when you want to sell or buy a scanner. FREE membership in the WSA Buyer's Co-op. Your Co-op membership will allow you to get special discounts on scanners and scanner related products. Since the WSA Buyer's Co-op gives you group purchasing power, you can easily pay for your membership dues the first time you make a Co-op purchase. To join, send \$12.00 (\$20.00 outside U.S.A.) for your membership materials.

BUY WITH CONFIDENCE

To get the fastest delivery from CE of any scanner, send or phone your order directly to our Scanner Distribution Center." Be sure to calculate your price using the CE prices in this ad. Michigan residents please add 4% sales tax. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 30 billing. All sales are subject to availability. All sales on accessories are final. Prices, terms and specifications are subject to change without notice. Out of stock items will be placed on backorder automatically unless CE is instructed differently. Most products that we sell have a manufacturer's warranty. Free copies of warranties on these products are available prior to purchase by writing to CE. International orders are invited with a \$20.00 surcharge for special handling in addition to shipping charges. All shipments are F.O.B. Ann Arbor, Michigan. No COD's please. Non-certified and foreign checks require five weeks bank clearance. Mail orders to: Communications Electronics, Box 1002, Ann Arbor, Michigan 48106 U.S.A. Add \$6.00 per scanner or phone product for U.P.S. ground shipping, or \$12.00 for faster U.P.S. air shipping to some locations. If you have a Master Charge or Visa card, you may call anytime and place a credit card order. Order toll free in the U.S.A. 800-521-4414. If you are outside the U.S. or in Michigan, dial 313-994-4444. Dealer inquiries invited. All order lines at Communications Electronics" are staffed 24 hours.

Bearcat[®] 250

List price \$419.95/CE price \$259.00/\$20.00 rebate Your final cost is a low \$239.00 50 Channels • Crystalless • Searches Stores • Recalls • Digital clock • AC/DC Priority Channel • 3-Band • Count Feature. Frequency range 32-50, 146-174, 420-512 MHz. The Bearcat 250 performs any scanning function you could possibly want. With push button ease you can program up to 50 channels for automatic monitoring. Overseas customers should order the Bearcat 250FB at \$349.00 each. This model is like a Bearcat 250, but

designed for international operation with 220 V AC/12 V DC power supply and 66-88 MHz low band coverage instead of 32-50 MHz.

Bearcat[®] 220 List price \$419.95/CE price \$259.00/\$20.00 rebate

Your final cost is a low \$239.00

Aircraft and public service monitor. Frequency range 32-50, 118-136 AM, 144-174, 420-512 MHz. The Bearcat 220 is one scanner which can monitor all public service bands plus the exciting AM aircraft band channels. Up to twenty frequencies may be scanned at the same time. Overseas customers should order the Bearcat 220FB at \$349.00 each. This model is like a Bearcat 220, but designed for international operation with 220 V AC/12 V DC power supply and 66-88 MHz low band coverage instead of 32-50 MHz.

NEW! Bearcat® 210XL List price \$319.95/CE price \$209.00/\$20.00 rebate

Your final cost is a low \$189.00

18 Channels • 3 Bands • Crystalless • AC/DC Frequency range: 32-50, 144-174, 421-512 MHz. The Bearcat 210XL scanning radio is the second generation scanner that replaces the popular Bearcat 210 and 211. It has almost twice the scanning capacity of the Bearcat 210 with 18 channels plus dual scanning speeds and a bright green fluorescent display.



NEW! 50-Channel Bearcat 300

having an information center in your pocket. This three band, 6 channel crystal controlled scanner has patented Track Tuning on UHF. Scan Delay and Channel Lockout. Measures 2³/₄ x 6¹/₄ x 1." Includes rubber ducky antenna. Order crystals for each channel. Made in Japan.

NEW! Fanon Slimline 6-HLU List price \$169.95/CE price \$109.00 Low cost 6-channel, 3-band scanner!

The new Fanon Slimline 6-HLU gives you six channels of crystal controlled excitement. Unique Automatic Peak Tuning Circuit adjusts the receiver front end for maximum sensitivity across the entire UHF band. Individual channel lockout switches. Frequency range 30-50, 146-175 and 450-512 MHz. Size 2¾ x6¼ x 1." Includes rubber ducky antenna. Order crystal certificates for each channel. Made in Japan.

NEW! Fanon Slimline 6-HL

List price \$149.95/CE price \$99.00

6-Channel performance at 4-channel cost! Frequency range: 30-50, 146-175 MHz.

If you don't need the UHF band, get this model and save money. Same high performance and features as the model HLU without the UHF band. Order crystal certificates for each channel. Made in Japan.

FANON SCANNER ACCESSORIES CHB-6 AC Adapter/Battery Charger \$15.00 CAT-6 Carrying case for Fanon w/Belt Clip \$15.00

AUC-3 Auto lighter adaptor/Battery Charger \$15.00

OTHER SCANNER ACCESSORIES

SP50 AC Adapter\$8.00SP51 Battery Charger\$8.00SP58 Carrying Case for Bearcat 4-6 ThinScan*\$12.00FB-E Frequency Directory for Eastern U.S.A\$12.00FB-W Frequency Directory for Western U.S.A\$12.00FFD Federal Frequency Directory for U.S.A\$12.00B-4 1.2 V AAA Ni-Cad's for ThinScan* and Fanon\$9.00A-135cc Crystal certificate\$3.00Add \$3.00 shipping for all accessories ordered at the same time.

INCREASED PERFORMANCE ANTENNAS

If you want the utmost in performance from your scanner, it is essential that you use an external antenna. We have six base and mobile antennas specifically designed for receiving all bands. Order #A60 is a magnet mount mobile antenna. Order #A61 is a gutter clip mobile antenna. Order #A62 is a trunk-lip mobile antenna. Order #A63 is a ¾ inch hole mount. Order #A64 is a ¾ inch snap-in mount, and #A70 is an all band base station antenna. All antennas are \$30.00 and \$3.00 for UPS shipping in the continental United States.

TEST ANY SCANNER

Test any scanner purchased from **Communications Electronics**" for 31 days before you decide to keep it. If for any reason you are not completely satisfied, return it in original condition with all parts in 31 days, for a prompt refund (less shipping/handling charges and rebate credits). WSA," Scanner Distribution Center" and CE logos are trademarks of Communications Electronics."

†Bearcat and Freedom Phone are federally registered trademarks of Electra Company, a Division of Masco Corporation of Indiana.

‡ Regency is a federally registered trademark of Regency Electronics Inc.

Copyright [°]1980 Communications Electronics[™]



× 377

COMMUNICATIONS ELECTRONICS"

854 Phoenix D Box 1002 Ann Arbor, Michigan 48106 U.S.A. Call TOLL-FREE (800) 521-4414 or outside U.S.A. (313) 994-4444

We're first with the best."



7400111 19 7402N 20 7402N 20 7404N 25 7409N 23 7410N 20 7414N 70 7414N 70 7420N 29 7430N 29	LM323K-5 3 50 LM320K-12 1 50 LM320K-15 1 50 LM320T-5 1 35 LM320T-8 1 35 LM320T-12 1 35 LM320T-12 1 35 LM320T-15 1 35 LM324N 1 40 LM339N 1 00 LM340K-5 1 35	CD4026 2 50 CD4027 68 CD4028 85 CD4029 1 35 CD4030 45 CD4035 1 35 CD404040 1 35 CD404040 1 35 CD40403 85 CD40444 85	4) 10 200ms 7.95 B/4116 200ms 49.00 2513B 6.30 MM5262 40 MM5280 3.00 MM5320 8.95 MM5330 5.94 PD4110-3 4.00 P04110-4 5.00 P5101L 8.95	30 pin edge 2 50 44 pin edge 2 75 100 pin edge 4 50 100 pin edge 90 100 pin edge 2 30 100 pin edge 14 24 35	Se key ASCII keyboard kit 567.50 Fully assembled 77.50 S3 key ASCII keyboard kit 60.00 Fully assembled 70.00 Fully assembled 70.00 Enclosure Plastic 14.95 Metal Enclosure 29.95 LEDS Red T018 15
7442N 58 7445N 74 7445N 74 7445N 74 745N 20 7474N 35 7475N 49 748N 88	LM340K-8 1.35 LM340K-12 1.35 LM340K-12 1.35 LM340K-24 1.35 LM340K-24 1.35 LM340T-5 1.25 LM340T-8 1.25 LM340T-12 1.25 LM340T-12 1.25	CD4046 1.67 CD4049 45 CD4050 49 CD4051 1.13 CD4060 1.42 CD4066 71 CD4068 40 CD4068 40	42004 9 95 82525 2 90 91L02A 1 50 HD0165-5 6 95 MM57100 4 50 GIAY38500-1 9 95 MCM66751A 9 95 9959 2 50	16 16 28 42 16 16 28 42 18 27 36 58 20 29 40 57 2 lovel 14 pm ww 20 WIRE WRAP LEVEL 3 PIN PIN	Green, Yellow T018 20 Jumbo Red 20 Green, Orange Yellow Jumbo 25 Clipite LED Mounting Clips 8(\$1.25 (specify reil, amber, green, yellow, clear) CONTINENTAL SPECIALTIES in stock
7488N 1.85 7488N 1.85 7490N 43 7492N 43 7492N 43 7493N 43 7495N 66	LM3407-13 1.25 LM340T-18 1.25 LM340T-24 1.25 LM350 7.50 LM377 3.50	CD4003 40 CD4070 50 CD4071 45 CD4072 45 CD4072 45 CD4073 45 CD4075 45	4100 10.00 416 16.00 CLOCKS	14 32 24 80 16 33 28 1.00 18 57 40 1.23 CRYSTALS 1 MH2 4 50	MAX-100 8 digit Freq. Ctr. \$128,95 OK WIRE WRAP TOOLS is stock Portable Multimeter \$18.00
74100N 120 74107N 35 74107N 35 74121N 34 74123N 59 74125N 45 74145N 77 74160N 120 74151N 69 74154N 200 74157N 69 74161N 87 74162N 125 74163N 87 74163N 87 74174N 96 74190N 157 74190N 157 74190N 85 74221N 275	LM380N 1 00 LM380N 1 00 LM381 1 50 LM382 1 60 LM703H 65 LM703H 85 LM723H/N 80 LM723H/N 86 LM741CH 35 LM741CH 35 LM741CH 35 LM747H/N 75 LM748N 35 LM748N 35 LM1303 1 27 LM1307 2 00 LM1307 2 00 LM1307 2 00 LM1310 2 75 LM1458 47 LM1812 7 50 LM1889 3 00	CD4076 165 CD4078 40 CD4081 35 CD4082 35 CD4082 35 CD4116 47 CD4507 100 CD4507 100 CD4507 100 CD4508 4 25 CD4510 102 CD4515 2 52 CD4515 2 52 CD4516 110 CD4518 102 CD4518 102 CD4518 102 CD4527 151 CD4528 79 CD4553 350 CD4566 2 25 CD4583 2 35	mmislall 3.30 MM5312 3.90 MM5312 3.90 MM5312 3.90 MM5312 3.90 MM5312 3.90 MM5369 2.10 MM5369 2.10 MM5369 2.10 MM5369 2.10 MM5375A0 95 CT7015 6.95 MM5375AG/N 90 MM5375AG/N 4.90 7205 16.50 7207 7.50 7208 15.95 7209 4.95 DS0026CN 3.75 DS0056CN 3.75 MM53104 2.50 MICROPROCESSOR 6502 6502 10.95	2 MHz 4 50 4 MHz 4 25 5 MHz 4 25 10 MHz 4 25 10 MHz 4 25 10 MHz 3 90 20 MHz 3 90 32 MHz 3 90 32 MHz 3 90 32768 Hz 4 00 1 8432 MHz 4 50 2 0100 MHz 1 95 2 0100 MHz 1 95 2 0100 MHz 4 50 2 4576 MHz 4 50 3 2768 MHz 4 50 5 0686 MHz 4 50 5 185 MHz 4 50 5 7143 MHz 4 50 5 7185 MHz 4 50 5 7143 1818 MHz 4 25	SPECIAL PRODUCTS MM5865 Stopwatch Timer with 10 pg, spec 9,00 PC board 7,50 Switches Mom Pushbatton 27 3 pos slide 25 Encoder HD0165-5 6,95 Paratronics 100A Logic Analyzer \$425.00 Model 10 Trigger Expander Kit \$229.00 Model 150 Bus Grabber Kit \$369.00 Clock Calendar Kit \$23.95 2,5 Mitz Frequency Counter Kit \$37.50 30 MHz Frequency
74296N 1 65 74365N 89 74366N 89 74367N 89 74367N 89 741,500 TTL 741,500N 35 741,500N 35	LM2111 1.75 LM2902 2.25 LM3900N 60 LM3905 1.75 LM3909N 95 MC1458V 50 NE550N 1.00 NE555V 39	CD4585 1 10 CD40192 3 80 74C00 35 74C04 40 74C10 35 74C14 1 95 74C20 35 74C20 35	6504 9.95 6522 9.95 6800 6.95 6802 11.95 6820 4.95 6850 5.95 8080A 5.95 8085 12.95	18 432 MHz 4.50 22 1184 MHz 4.50 KEYBOARD ENCODERS AY5-2376 \$12 50 AY5-3600 17 95 AY5-9100 10 50 AY5-9200 16 50	Counter Kit \$47.75 TRANSFORMERS 3 25 6V 300 ma 3 25 12 Volt 300 ma transformer 1 25 12 6V CT 600 ma 3 75 12V 250 ma wall plog 2 95 12V CT 250 ma wall plog 5 50
74LS04N 55 74LS05N 40 74LS05N 40 74LS10N 45 74LS10N 45 74LS13N 55 74LS14N 125 74LS14N 125 74LS20N 45	NE556A B5 NE565A 1 00 NE566V 1 50 NE567V 1 00 NE5708 4.75 78105 60 78405 85	74C48 2.25 74C74 85 74C76 1.75 74C90 1.75 74C93 1.75 74C154 3.00 74C155 2.00 74C154 3.00	8086 75.00 Z80 9.95 Z80A 11.95 8212 2.90 8214 3.95 8216 2.90 8224 3.45 8298 4.95	740922 3.50 740923 5.50 HD0165-5 6.95 AY5-9400 10.50 D Connectors RS232 DB25P DB25S 5.20	24V CT 400 ma 3.95 10V 1.2 amp wall plug 4.85 12V 6 amp 12.95 12V 500 ma wall plug 4.75 12V 1 amp wall plug 6.50 10/15 VAC 6/16 VA wall plug 9.75
14LS22N 45 74LS28N 45 74LS30N 45 74LS33N 75 74LS38N 75 74LS38N 75 74LS38N 75 74LS38N 75 74LS38N 125 74LS78N 1.00 74LS790N 1.00	75108 1.75 75491CN 50 75492CN 55 75494CN 89	740113 1.33 740192 2.25 740221 2.50 740905 6.00 740905 75 740914 1.95 740922 6.00 740923 6.00	8251 6.95 8253 15.00 8255 5.75 8257 10.95 8259 14.95 1802CP plas 13.95 1802DP plas 17.95	Cover 1.67 DE9S 1.95 DA15P 2.10 DA15S 3.10 Complete Set 9.50 Hickok 3½ Digit LED mul-	DISPLAY LEDS MAN1 CA 270 2.90 MAN3 CC 125 39 MAN72/74 CA/CA 300 1.00 DL704 CC 300 1.25 DL707/DL707/R CA 300 1.00 DL727/728 CA/CC 500 1.90
74LS93N 1.00 74LS95N 1.10 74LS107N 65 74LS112N 65 74LS112N 65 74LS132N 85 74LS132N 89 74LS136N 65	80388 4.50 8700CJ 13.95 8701CN 22.00 8750CJ 13.95 LD130 9.85 9400CJV/F 7.40 CL17103 9.50	74C925 750 74C926 695 74C927 695 INTERFACE 8095 65 8096 65	1861P 11.50 CDP1802C0 28.95 CDP1802D 35.00 CDP1861 15.95 UART/FIFO AY5.1013 5.50	timeter 74.95 Stopwatch Kit 26.95 Auto Clock Kit 17.95 Digital Clock Kit 14.95 8K/16K Eprom Kit (less PROMS) \$89.00	DL747/750 CA/CC 600 1 95 DL750 CC 600 1 95 FN0359 CC 357 70 FN0500/507 CC/CA 500 1 35 FN0500/507 CC/CA 500 90 90 FN0500/510 CC/CA 500 90 90 FN0800/B07 CC/CA 800 2 29 3 digit Bubble 60 60
74LS151N 1 10 74LS155N 1 10 74LS157N 1 10 74LS162N 1.65 74LS163N 1.65 74LS163N 2.60	ICL7107 14.25 CMOS CD4000 25 CD4001 35 CD4001 35	8097 .65 8098 .65 8109 1.25 8110 4.50 8113 3.00 8120 5.50	A75-1014 7.50 3341 6.95 PROM 1702A 4.95 2513B unner case 8.7	Motherboard \$39.00 Extender Board \$15.00 RESISTORS % watt 5% 10 per type .03 525 per type .025	4 digit Bubble 80 DG5 Fluorescent 1 75 DG10 Fluorescent 1 75 10 digit display 1 25 7520 Clairex photocells 39 Til 311 Hex 9 50
74LS190N 1.25 74LS221N 2.50 74LS258N 1.65 74LS367N 1.65	CD4006 1 10 CD4007 35 CD4008 28 CD4009 45 CD4010 45 CD4011 45	8723 3.10 8724 3.50 8725 3.20 8726 1.69 8728 2.75 8797 1.65	2708 7.75 271671 18.00 2716 Intel 23.00 8/2716 Intel 160.00 2732 65.00 2758 25.50	100 per type 015 1000 per type 012 350 piece pack 5 per type 6 75 1s watt 5% per type 05	MAN3640 CC 30 1 10 MAN4610 CA 40 1 20 MAN4640 CC 40 1 20 MAN4640 CC 40 1 20 MAN4740 CC 40 1 20 MAN4740 CC 40 1 20 MAN4740 CC 40 1 20
CA3045 90 CA3046 1 10 CA3081 1 80 CA3082 1 90 CA3082 1 90	CD4012 28 CD4012 28 CD4013 47 CD4014 1 25 CD4015 100	MOS/MEMORY RAM	8741A 60.00 8748 65.00 8748-8 60.00 8755A 55.00	Televideo Terminal Model 912 \$845.00 Model 920 \$945.00	MAN6710 CA 60 1 35 MAN6740 CC 60 1 35 MA1002A 8.95
LM3089 2 95 LM301AN/AH 35 LM305H 87 LM305H 87 LM305N 150 LM308N 1 50	CD4016 55 CD4017 1.05 CD4018 94 CD4018 45 CD4020 1.02 CD4021 1.35	2102-1 .95 2102-1 .95 2102AL-4 1.34 2102AN-2L 1.60 2104A-4 4.95 2107B-4 3.75	N825123 6.50 N825126 3.75 N825129 8.50 N825131 8.50 N825136 8.75	They Basic Experimentors Kit \$10.00 BSR Controller \$39.95	MA1002E 8.95 MA1012A 8.95 102P3 transformer 2.25 MA1012A Transformer 2.25
LM311H/N 90 LM317UK 3.75 LM318 1.35 LM320K-5 1.50	CD4022 1 10 CD4023 28 CD4024 75 CD4025 28	2111-1 3.75 2112-2 3.95 2114L 300ms 6.75 2114L 450ms 5.95	N825137 8.75 DM8577 2.90 8223 2.90	Connect your computer to the BSF System Computer controlled of rotter for your BSR. Software for	Home Control rasonic Mans • 1802 user

IRS		KEYBOAROS
inia .	10.66	SE kou ASCII keyboard kit SE7.40
90	2 75	Fully sceembled 77.50
ge no	1.80	52 key ACC11 keyboard bit EO 08
ge www	5.25	Fully secondial 70.00
	0.20	Federation Disette 14.05
CKETS		Enclosure Plastic 14.95
Low P	rofile	Metal Enclosure 29.95
PIN	1HP	1 FDR
22	30	LEUS
24	35	Heg 1018 .15
28	62	Green, Yenow toth .20
40	50	Jumbo Red 20
20	67	Green, Orange, Yellow Jumbo 25
10 Tan	1991	Cliplite LED Mounting Clips 8/\$1.25
0.444 51	1. m	(specify red, amber, green, yellow, clear)
AP LEVI	EL 3	
PIN		CONTINENTAL SPECIALTIES in stock
34	88	Complete line of breadboard test equip
28	1.00	MAX-100 8 digit Freg. Ctr. \$128.95
40	1 99	
78	1.64	OK WIRE WRAP TOOLS in stock
		Portable Multimeter \$18.00
	4.86	
	4.50	Lomplete line of AP Products in stock.
	1 25	
	1 02	SPECIAL PRODUCTS
	4.20	MM5865 Stopwatch Timer
	7 20	with 10 pg, spec 9.00
	3.90	PC board 7 50
	3.30	Switches Morn. Pushbetton 27
	3.90	3 pos slide 25
	4.00	Encoder HD0165-5 6.95
<u>и</u> : :	4.50	Paratronics 100A Logic
1	1.20	Analyzer \$425.00
2.	1.95	Model 10 Trigger
VH2	4.50	Expander Kit \$229.00
123 C	4.50	Model 150 Bus
\$2.5 · · · ·	4.50	Grahher Kit \$369.00
10	4.50	
	4.50	Clock Calendar Kit \$23.95
2	4.50	2.5 MHz Frequency
7	4.50	Counter Kit \$37.50
M Hz	4.25	30 MHz Frequency
126 I	4.50	Counter Kit \$47.75
HZ I	4.50	
		TRANSFORMERS
ENCOL	JENS .	6V 300 ma 3 25
	812.50	12 Volt 300 ma transformer 1.25
	17.95	12 6V CT 600 ma 3 75
	10.50	12V 260 ma wall plan 2 95
	16.50	12V CT 250 ma wall now 3 50
	5.50	24V CT 400 ma 3 95
	5.50	10V 1.2 year wall plan 4.95
	6.95	124 6 amn 12 06
	10.50	124 0 Bing
	1990 B	124 July hid wer prog 7.73
ars RS2	32	12 Y T drip wait prog. 0.00
	3.62	TO 10 AND AND AN MULTING A 10
	5.20	
	1.67	DISDLAY LEDS
	1.95	STANS CA OTE O OF
	2,10	MANO 00 100 00
	3.10	MANJ 66.123 39
Set.	9.50	MAN/2/14 GALLA 300 1.00
	- and a state of the	DL704 66 380 1 29
Digit LE	D mul-	DETUTION CA 300 1 00
	74.95	UL/2///28 CA/CC 500 1.90
KH.	26.05	UC/4/7/50 CA/CC 600 1.95
WIR	17.08	UL750 CC 600 1.95
and all a	14.00	IND359 CC .357 70
CS ALL	14,95	FN0500/507 CG/CA 500 1 35
1999		FN0503/510 CC/CA 500 90
OM KIT	and the second	FND800/807 CC/CA 800 2.20
OMS)	\$69.00	3 digit Bubble 60
14	239.00	4 digit Bubble
David	\$15.00	DG8 Fluorescent 1 75
-	14053	DG10 Fluorescent 1.75
HS II W	all of a	10 digit display 1.25
ype 03	10	7520 Clairex photocells 39



RCA Cosmac 1802 Super Elf Computer \$106.95

Compare features before you decide to buy any other computer. There is no other computer on the market today that has all the desirable benefits of the Super Elf for so little money. The Super Elf is a small single board computer that does many big things. It is an excellent computer for training and for learning programming with its machine language and yet it is easily expanded with additional memory, Full Basic, ASCII Keyboards, video character generation, etc.

Before you buy another small computer, see if it includes the following features: ROM monitor; State and Mode displays; Single step; Optional address displays; Power Supply; Audio Amplifier and Speaker, Fully socketed for all IC's; Real cost of in warranty repairs; Full documentation.

The Super Elf includes a ROM monitor for program loading, editing and execution with SINGLE STEP for program debugging which is not included in others at the same price. With SINGLE STEP you can see the microprocessor chip operating with the unique Quest address and data bus displays before, during and after executing instructions. Also, CPU mode and instruction cycle are decoded and displayed on 8 LED indicators.

An RCA 1861 video graphics chip allows you to connect to your own TV with an inexpensive video modulator to do graphics and games. There is a speaker system included for writing your own music or using many music programs already written. The speaker amplifier may also be used to drive relays for control purposes.

A 24 key HEX keyboard includes 16 HEX keys

Super Expansion Board with Cassette Interface \$89.95

plus load, reset, run, wait, input, memory protect, monitor select and single step. Large, on board displays provide output and optional high and low address. There is a 44 pin standard connector slot for PC cards and a 50 pin connector slot for the Quest Super Expansion Board. Power supply and sockets for all IC's are included in the price plus a detailed 127 pg. instruction manual which now includes over 40 pgs. of software info. including a series of lessons to help get you started and a music program and graphics target game. Many schools and universities are using the Super Elf as a course of study. OEM's use it for training and R&D.

Remember, other computers only offer Super Elf features at additional cost or not at all. Compare before you buy. Super Elf Kit \$106.95, High address option \$8.95, Low address option \$9.95. Custom Cabinet with drilled and labelled plexiglass front panel \$24.95. All metal Expansion Cabinet, painted and silk screened, with room for 5 S-100 boards and power supply \$57.00. NiCad Battery Memory Saver Kit \$6.95. All kits and options also completely assembled and tested

Questidata, a software publication for 1802 computer users is available by subscription for \$12.00 per 12 issues. Single issues \$1.50. Issues 1-12 bound \$16,50.

Tiny Basic Cassette \$10.00, on ROM \$38.00, original Elf kit board \$14.95. 1802 software; Moews Video Graphics \$3.50. Games and Music \$3.00, Chip 8 Interpreter \$5.50.

PROM Eraser

assembled. 25 PROM capacity \$37.50 (with timer \$69.50). 6 PROM capacity OSHA/ UL version \$69.50 (with timer \$94.50).

Z80 Microcomputer

16 bit I/O, 2 MHz clock, 2K RAM, ROM Breadboard space. Excellent for control. Bare Board \$28.50. Full Kit \$99.00. Monitor \$20.00. Power Supply Kit \$35.00. Tiny Basic \$30.00

S-100 Computer Boards

8K Static Godbout Econo IIA Kit	145.00
16K Static Godbout Econo XIV Kit	285.00
24K Static Godbout Econo VIIA-24 Kir	t 435.00
32K Static Godbout Econo X-32 Kit	575.00
16K Dynamic RAM KIt	199.00
32K Dynamic RAM Kit	310.00
64K Dynamic RAM Kit	470.00
Video Interface Kit	\$135.00

80 IC Update Master Manual \$55.00

Comp. IC data selector, 2700 pg. master reference guide. Over 51,000 cross references. Free update service through 1980. Domestic postage \$3.50.

Modem Kit \$60.00

State of the art, orig., answer. No tuning necessary. 103 compatible 300 baud. Inexpensive acoustic coupler plans included.

LRC 7000 + Printer \$389.00

40/20 column dot matrix impact, std. paper. Interface all personal computers.

64/40/32/20 version \$405.00. Optional cables available.

LRC 7000 printer interface cable for Super Elf \$26.00 with software

NiCad Battery Fixer/Charger Kit

Opens shorted cells that won't hold a charge and then charges them up, all in one kit w/full parts and instructions. \$7.25

Rockwell AIM 65 Computer

6502 based single board with full ASCII keyboard and 20 column thermal printer. 20 char. alphanumeric display, ROM monitor, fully expandable. \$375.00. 4K version \$450.00. 4K Assembler \$85.00, 8K Basic Interpreter \$100.00.

Special small power supply for AIM65 assem. in frame \$54.00. Complete AIM65 in thin briefcase with power supply \$499.00. Molded plastic enclosure to fit both AIM65 and power supply \$47.50. Special Package Price: 4K AIM, 8K Basic. power supply, cabinet \$599.00

AIM65/KIM/VIM/Super Elf 44 pin expansion board; 3 female and 1 male bus. Board plus 3 connectors \$22.95.

60 Hz Crystal Time Base Kit \$4.40 Converts digital clocks from AC line frequency

to crystal time base. Outstanding accuracy.

Video Modulator Kit \$8.95 Convert TV set into a high guality monitor w/o affecting usage. Comp. kit w/full instruc.

Multi-volt Computer Power Supply 8v 5 amp, ±18v .5 amp, 5v 1.5 amp, -5v .5 amp, 12v .5 amp, -12v option. ±5v, ±12v are regulated. Basic Kit \$29.95. Kit with chassis and all hardware \$43.95. Add \$4.00 shipping. Kit

of hardware \$14.00. Woodgrain case \$10.00. \$1.50 shipping.

This is truly an astounding value! This board has been designed to allow you to decide how you want it optioned. The Super Expansion Board comes with 4K of low power RAM fully addressable anywhere in 64K with built-in memory protect and a cassette interface. Provisions have been made for all other options on the same board and it fits neatly into the hardwood cabinet alongside the Super Elf. The board includes slots for up to 6K of EPROM (2708, 2758, 2716 or TI 2716) and is fully socketed. EPROM can be used for the monitor and Tiny Basic or other purposes.

A IK Super ROM Monitor \$19.95 is available as an on board option in 2708 EPROM which has been preprogrammed with a program loader/ editor and error checking multi file cassette read/write software, (relocatable cassette file) another exclusive from Quest. It includes register save and readout, block move capability and video graphics driver with blinking cursor. Break

Announcing Quest Super Basic— SECOND GENERATION

A new enhanced version of Super Basic now available. Quest was the first company worldwide to ship a full size Basic for 1802 Systems. A complete function Super Basic by Ron Cenker including floating point capability with scientific notation (number range ± .17E3), 32 b1t integer ±2 billion; multi dim arrays, string arrays; string manipulation; cassette I/O; save and load, basic, data and machine language programs; and over 75 statements, functions and operations

points can be used with the register save feature to isolate program bugs quickly, then follow with single step. If you have the Super Expansion Board and Super Monitor the monitor is up and running at the push of a button.

Other on board options include Parallel Input and Output Ports with full handshake. They allow easy connection of an ASCII keyboard to the input port. RS 232 and 20 ma Current Loop for teletype or other device are on board and if you need more memory there are two S-100 slots for static RAM or video boards. Also a 1K Super Monitor version 2 with video driver for full capability display with Tiny Basic and a video interface board. Parallel I/O Ports \$9.85, RS 232 \$4.50, TTY 20 ma I/F \$1.95, S-100 \$4.50. A 50 pin connector set with ribbon cable is available at \$15.25 for easy connection between the Super Elf and the Super Expansion Board.

Power Supply Kit for the complete system (see Multi-volt Power Supply).

Enhancements include increased speed, builtin provisions for Stringy Floppy, Floppy Disc, Printer Driver, 1/0, user definable command library and statement renumbering.

Easily adaptable to most 1802 systems. Requires 16K RAM minimum for Basic and user programs. Source listing for both Serial and Parallel I/O included.

Super Basic on Cassette \$40.00.

Gremlin Color Video Kit \$69.95 32 x 16 alpha/numerics and graphics; up to 8 colors with 6847 chip; 1K RAM at E000. Plugs into Super Elf 44 pin bus. No high res. graphics. On board RF Modulator Kit \$4.95	Elf II Adapter Kit \$24.95 Plugs into Elf II providing Super Elf 44 and 50 pin plus S-100 bus expansion. (With Super Ex- pansion). High and low address displays, state and mode LED's optional \$18.00.
1802 16K Dynamic RAM Kit \$149.00Expandable to 32K. Hidden refresh w/clocks up to 4MHz w/no wait states. Addl. 16K RAM \$63.00Super Elf 44 pin expansion board; 3 female and 1male bus. Board plus 3 connectors \$22.95Tiny Basic Extended on Cassette\$15.00(added commands include Stringy, Array, Cassette I/O etc.)S-100 4-Slot Expansion\$ 9.95Super Monitor VI.I Source Listing\$15.00	Super Color S-100 Video Kit \$129.95Expandable to 256 x 192 high resolution color graphics. 6847 with all display modes computer controlled. Memory mapped. 1K RAM expanda- ble to 6K. S-100 bus 1802, 8080, 8085, Z80 etc.Editor Assembler\$25.00(Requires minimum of 4K for E/A plus user source)1802 Tiny Basic Source listing\$19.00Super Monitor V2.0/2.1 Source Listing \$20.00

TERMS: \$5.00 min. order U.S. Funds. Calif residents add 6% tax. \$10.00 min. order BankAmericard and Master Charge and COD. \$1.00 insurance optional. Shipping charges will be added on charge cards.

FREE: Send for your copy of our NEW 1980 QUEST CATALOG. Include 48¢ stamp.

Electronics 6

Toll Free Number 800-528-0180 (For orders only)

1900 MHz to 2500 MHz DOWN CONVERTER

This receiver is tunable a range of 1900 to 2500 mc and is intended for amateur radio use. The local oscillator is voltage controlled (i.e) making the i-f range approximately 54. to 88 mc (Channels 2 to 7)

	\$10.00
PC BOARD WITH DATA	
PC BOARD WITH CHIP CAPACITORS 13	\$44.99
PC BOARD WITH ALL PARTS FOR ASSEMBLY	\$69.99
PC BOARD WITH ALL PARTS FOR ASSEMBLY PLUS 2N6603	\$89.00
PC BOARD ASSEMBLED AND TESTED	\$99.99
PC BOARD WITH ALL PARTS FOR ASSEMBLY POWER SUPPLY AND ANTENNA	\$159.99
POWED SUDDI VASSEMBI ED AND TESTED	\$49.99
VACIANTENNIA ALLONIC APPROX 20 TO 22 dB CAIN	\$49.99
VACIANTENNA 4 WITH TYPE (N. PNC. CMA Connector)	\$64.99
YAGIANTENNA 4 WITH TTPE (N, BNC, SMA Connector)	\$59.99
2 FOOT DISH WITH FEED AND MOUNT	
2300 MHz DOWN CONVERTER	000000
Includes converter mounted in antenna, power supply, Plus 90 DAY WARRANTY	
OPTION #1 MRF902 in front end. (7 dB noise figure)	\$299.99
OPTION #2 2N6603 in front end. (5 dB noise figure).	\$359.99
2300 MHZ DOWN CONVERTER ONLY	
10 dB Noise Figure 23 dB gain in hox with N conn Input F conn Output	\$149.99
7 dB Noise Figure 23 dB gain in box with N conn. Input E conn. Output	\$169.99
F dB Noise Figure 22 dB agin in box with CMA cons. Input E cons. Output	\$189.99
5 dB Noise Figure 25 dB gain in box with SMA contributer contributer of the second sec	\$15.00
DATA IS INCLUDED WITH KITS OF MAT BE PURCHASED SEPARATELT	NAME OF A DAY OF A DAY OF A

Shipping and Handling Cost:

Receiver Kits and \$1.50. Power Supply add \$2.00. Antenna add \$5.00. Option 1/2 add \$3.00. For complete system add \$7.50.

HOWARD/COLEMAN TVRO CIRCUIT BOARDS DUAL CONVERSION BOARD This board provides conversion from the 3.7-4.2 band first to 900 MHz where gain and bandpass filtering are provided and, second, to 70 MHz. The board contains both local oscillators, one fixed and the other variable, and the second mixer. Construction is greatly simplified by the use of Hybrid IC amplifiers for the gain stages. Bare boards cost \$25 and it is estimated that parts for construction will cost \$270. (Note: The two Avantek VTO's account for \$225 of this cost.) 47 pF CHIP CAPACITORS For use with dual conversion board. Consists of 6-47 pF. 70 MHz IE BOARD
This circuit provides about 43 dB gain with 50 ohm input and output impedance. It is designed to drive the HOWARD/COLEMAN TVRO Demodulator. The on-board band pass filter can be tuned for bandwidths between 20 and 35 MHz with a passband ripple of less than ½ dB. Hybrid ICs are used for the gain stages. Bare boards cost \$25. It is estimated that parts for construction will cost less than \$40. 01 pF CHIP CAPACITORS \$7.00 For use with 70 MHz IF Board. Consists of 7-01 pF. DEMODULATOR BOARD \$40.00 This circuit takes the 70 MHz center frequency satellite TV signals in the 10 to 200 millivolt range, detects them using a phase locked loop, deemphasizes and filters the result and amplifies the result to produce standard NTSC video. Other outputs include the audio subcarrier, a DC voltage proportional to the strength of the 70 MHz signal, and AFC voltage centered at about 2 volts DC. The bare board cost \$40 and total parts cost less than \$30. SINGLE AUDIO
This circuit recovers the audio signals from the 6.8 MHz frequency. The Miller 9051 coils are tuned to pass the 6.8 MHz subcarrier and the Miller 9052 coil tunes for recovery of the audio. DUAL AUDIO Duplicate of the single audio but also covers the 6.2 range. S15.00 This circuit controls the VTO's, AFC and the S Meter.

TERMS:

WE REGRET WE NO LONGER ACCEPT BANK CARDS.

PLEASE SEND POSTAL MONEY ORDER, CERTIFIED CHECK, CASHIER'S CHECK OR MONEY ORDER. PRICES SUBJECT TO CHANGE WITHOUT NOTICE. WE CHARGE 15% FOR RESTOCKING ON ANY ORDER.

ALL CHECKS AND MONEY ORDERS IN US FUNDS ONLY

ALL ORDERS SENT FIRST CLASS OR UPS.

ALL PARTS PRIME AND GUARANTEED.

WE WILL ACCEPT COD ORDERS FOR \$25.00 OR OVER, ADD \$2.50 FOR COD CHARGE.

PLEASE INCLUDE \$2.50 MINIMUM FOR SHIPPING OR CALL FOR CHARGES.

WE ALSO ARE LOOKING FOR NEW AND USED TUBES. TEST EQUIPMENT, COMPONENETS ETC.

WE ALSO SWAP OR TRADE.

FOR CATALOG SEE JANUARY, 1980, 73 Magazine, 10 Pages.

(602) 242-8916 2111 W. Camelback Phoenix, Arizona 85015

MHZ electronics

FAIRCHI	LD VHF AND UHF PRESCALER CHIPS		RF TRANSIST	ORS				
95H90DC	350 MHz Prescaler Divide by 10/11	\$9.50	TYPE	PRICE	TYPE	PRICE	TYPE	PRIC
95H91DC	350 MHz Prescaler Divide by 5/6	9.50	2N1561	\$15.00	2N5590	\$8.15	MM1550	\$10.0
11C90DC	650 MHz Prescaler Divide by 10/11	16.50	2N1562	15.00	2N5591	11.85	MM1552	50.0
11C91DC	650 MHz Prescaler Divide by 5/6	16.50	2N1692	15.00	2N5637	22.15	MM1553	56.5
11C83DC	1 GHz Divide by 248/256 Prescaler	29.90	2N1693	15.00	2N5641	6.00	MM1601	5.5
11C70DC	600 MHz Flip/Flop with reset	12.30	2N2632	45.00	2N5642	10.05	MM1602/2N5842	7.5
11C58DC	ECL VCM	4.53	2N2857JAN	2.52	2N5643	15.82	MM1607	8.6
11C44DC/N	AC4044 Phase Frequency Detector	3.82	2N2876	12.35	2N6545	12.38	MM1661	15.0
11C24DC/N	AC4024 Dual TTL VCM	3.82	2N2880	25.00	2N5764	27.00	MM1669	17.5
11C06DC	UHF Prescaler 750 MHz D Type Flip/Flop	12.30	2N2927	7.00	2N5842	8.78	MM1943	3.0
11C05DC	1 GHz Counter Divide by 4	50.00	2N2947	18.35	2N5849	21.29	MM2605	3.0
11C01FC	High Speed Dual 5-4 input NO/NOR Gate	15.40	2N2948	15.50	2N5862	51.91	MM2608	5.0
			2N2949	3.90	2N5913	3.25	MM8006	2.2
			2N2950	5.00	2N5922	10.00	MMCM918	20.0
			2N3287	4.30	2N5942	46.00	MMT72	1.1
			2N3294	1,15	2N5944	8.92	MM1/4	1.1
			2N3301	1.04	2N5945	12.38	MM12857	2.6
TRW BRC	ADBAND AMPLIFIER MODEL CA615B		2N3302	1.05	2N5946	14.69	MRF245	33.3
Frequency	response 40 MHz to 300 MHz		2N3304	1.48	2N6080	1.74	MRF247	33.3
Gain: 3	300 MHz 16 dB Min., 17.5 dB Max.		2N3307	12.60	2100081	10.05	MRF304	43.4
1	50 MHz 0 to - 1 dB from 300 MHz		2113309	0.20	2110002	12.02	MPE420	20.0
Voltage: 2	24 volts dc at 220 ma max.	\$19.99	2113373	1.52	2110003	14.66	MPE450A	11.6
CARRIDE	- CIRCUIT BOARD DRILL BITS FOR PC BOARD	S	21133333	7.00	2110004	7 15	MPEASA	11.8
Cine 25 10	17 40 51 52	60.15	2113733	6.00	2N6095	11.77	MRE459	21.0
Size: 35, 42,	47,49,01,02 65 56 57 59 50 51 50 54 55	\$2.15	2N3866	1.00	2N6096	20.77	WITH 400	20.0
Size: 53, 54,	, 55, 56, 57, 56, 59, 61, 65, 64, 65	1.00	2N3866 IAN	2.80	2N6097	29.54		
Size: 1 25 m	m 145 mm	2.00	2N3866 14NTX	4 49	2N6136	20.15	MRE502	10
Size: 3.20 m	ini, 1.45 mm	2.00	2N3924	3.34	2N6166	38 60	MRE504	6.9
5128. 5.2011		5.50	2N3927	12 10	LITOTOO	00.00	MRE509	49
CRYSTAL	FILTERS: TYCO 001-19880 same as 2194F		2N3950	26.86			MBF511	8.1
10.7 MHz N	arrow Band Crystal Filter		2N4072	1.80	2N6439	45.77	MRF901	3.0
3 dB bandw	idth 15 kHz min. 20 dB bandwidth 60 kHz min. 40 dB ban	dwidth 150	2N4135	2.00	2N6459/PT9795	18.00	MRF5177	21.6
kHz min.			2N4261	14.60	2N6603	12.00	MRF8004	1.6
Ultimate 50	dB: Insertion loss 1.0 dB max. Ripple 1.0 dB max. Ct. 0+/	- 5 pf 3600	2N4427	1.20	2N6604	12.00	PT4186B	3.0
ohms.		\$5.95	2N4957	3.62	A50-12	25.00	PT4571A	1.5
MURATA	CERAMIC EIL TERS		2N4958	2.92	BFR90	5.00	PT4612	5.0
Modeler		\$2.00	2N4959	2.23	BLY568C	25.00	PT4628	5.0
Models: 5		33.00	2N4976	19.00	BLY568CF	25.00	PT4640	5.0
0	EM 455E 455 LH2	7.05	2N5090	12.31	CD3495	15.00	PT8659	10.7
9	EE.10 7 10 7 MHz	5.95	2N5108	4.03	HEP76/S3014	4.95	PT9784	24.3
		0.00	2N5109	1.66	HEPS3002	11.30	PT9790	41.70
			2N5160	3.49	HEPS3003	29.88	SD1043	5.00
TEST EQU	JIPMENT - HEWLETT PACKARD - TEKTRONIX	- ETC.	2N5179	1.05	HEPS3005	9.95	SD1116	3.00
Hewlett Par	skard.	1-2-6-12	2N5184	2.00	HEPS3006	19.90	SD1118	5.00
riumion rat			2N5216	47.50	HEPS3007	24.95	SD1119	3.00
491C TWT	Amplifier 2 to 4 Gc 1 watt 30 dB gain	\$1150.00	2N5583	4.55	HEPS3010	11.34		
608C 10 mg	c to 480 mc .1 uV to.5V into 50 ohms Signal Generator	500.00	2N5589	6.82	HEPS5026	2.56		
608D 10 to	420 mc .1 uV to.5V into 50 ohms Signal Generator	500.00			HP35831E/	60.00	THWMHA2023-1.	5 42.50
612A 450 to	o 1230 mc .1 uv to .5v into 50 onms Signal Generator	750.00			MA1600	32.20	40201	10.90
614A 900 to	0 2100 mc. Signal Generator	500.00			MINI DOO	32.20	40202	11.90
616A 1.6 10	4.2 Go Signal Generator	400.00					40290	2.40
6106 1.0 IC	7.2 Go Signal Concrator	400.00						
610A 3.0 10	7.2 Go Signal Generator	400.00			CHIP CAPACITO	RS		
620A 7 to 1	1 Co Signal Constator	500.00			UNIF CAFACITO	07-4	000-1 1	000-4
620A / 10	The Signal Generator	900.00			1pr	2701	220p1 1	200pt
6256 MICIC	to 15 Go Signal Generator	2500.00	We can su	pply any	1.501	33p1	240p1 1	900pt
605A 12 4	n 18 Go Sween Generator	900.00	value chip	capac-	2.2pt	39pt	20001 1	20001
000A 12.4 1	to to do oweep delicitator	500.00	itors you r	may need.	2.7pt	47pt	330pt 2	700of
Alltech:			0010	EC	3.3pt	68of	360pt 2	300pt
473	225 to 400 mc AM/FM Signal Generator	750.00	PHIC	1.10	0.901 4.7of	8201	390pf 3	900of
Singer			1 to 10	1.49	4.7p1	10001	430pt 4	700pt
MF5/VB-4	Universal Spectrum Analyzer with 1 kHz to 27.5 mc Plug I	n 1200.00	11 - 50	1.29	5.0p1 6.8pf	110of	470nf 5	600pf
Keltek			51 - 100	.09	8.2pf	120pf	510of 6	800pf
VR620 100	TWT Amplifier 8 to 12 4 Go 100 watte 40 dB coin	0200.00	101 - 1,000	.09	0.2p1	130pf	560pf 8	200pf
1000-100	TWT Ampiniero to 12.4 GC 100 watts 40 GB gain	3200.00	1,001 up	.49	1201	150pf	620pf 0	010mf
rolarad:	1024				15pf	160pt	680pt ()12mf
2030/2436/1	Calibrated Display with an CCD Applying Madula and a 10	Ito			18pf	180pf	820pf .0)15mf
	40 mc Single Tone Synthesizer	1500.00			22pf	200pf	1000pf .0)18mf

Toll Free Number 800-528-0180 (For orders only)

HAMLIN SOLID STATE RELAYS: 120vac at 40 Amps. Input Voltage 3 to 32vdc. 240 vac at 40 Amps. Input Voltage 3 to 32 vdc.	YOUR CHOICE \$4.99	ATLAS CRYSTAL FILTERS FOR AT 5.52-2.7/8 5.595-2.7/8/U 5.595-2.7USB 5.595-2.7USB 5.645-2.7/8 9.OUSB/CW	LAS HAM GEAR YOUR CHOICE \$24.95



MOTOROLA Semiconductor

MRF454

\$21.83

NPN SILICON RF POWER TRANSISTORS

. . . designed for power amplifier applications in industrial, commercial and amateur radio equipment to 30 MHz.

Specified 12.5 Volt, 30 MHz Characteristics Output Power = 80 Watts Minimum Gain = 12 dB Efficiency = 50%

Toll Free Number 800-528-0180 (For orders only)

The RF Line

MRF458 \$20.68

NPN SILICON RF POWER TRANSISTOR

designed for power amplifier applications in industrial, commerical and amateur radio equipment to 30 MHz

Specified 12.5 Volt, 30 MHz Characteristics

Output Power = 80 Watts Minimum Gain = 12 dB Efficiency = 50%

Capable of Withstanding 30:1 Load VSWR @ Rated Pout and VCC.

MRF472

\$2.50

NPN SILICON RF POWER TRANSISTOR

designed primarily for use in large-signal output amplifier stages. Intended for use in Citizen-Band communications equipment operating at 27 MHz. High breakdown voltages allow a high percentage of up-modulation in AM circuits.

 Specified 12.5 V, 27 MHz Characteristics – Power Output = 4.0 Watts Power Gain = 10 dB Minimum Efficiency = 65% Typical



MRF475

NPN SILICON RF POWER TRANSISTOR

..... designed primarily for use in single sideband linear amplifier output applications in citizens band and other communications equipment operating to 30 MHz.

\$46.45 440 to 470MC

UHF POWER AMPLIFIER MODULE

designed for 12.5 volt UHF power amplifier applications in

\$5.00

- Characterized for Single Sideband and Large-Signal Amplifier Applications Utilizing Low-Level Modulation.
- Specified 13.6 V, 30 MHz Characteristics Output Power = 12 W (PEP) Minimum Efficiency = 40% (SSB) Output Power = 4.0 W (CW) Minimum Efficiency = 50% (CW) Minimum Power Gain = 10 dB (PEP & CW)

Common Collector Characterization

Tektronix Test Equipment

8	Wideband High Gain Plug In	5 61 00
CA	Dual Trace Plug In	120.00
5	Fast Rise DC Plug In	53.00
	Sampling Flug in Transition Direction Plan in	116.00
0	With Lain Differential Connergion Plus In	283 (1)
10.2	Test Load Plus In for SHI/540/550 Main Frames	50.00
147	Wideband Dual Trace Plug In	216.00
151	Sampling Unit with 350PS Rivetime DC to 1007	730.00
2461	AC Differential Plug In	133.00
253	Dual Trace Sampling DC to 1042 Plug In .	250.00
3576.	Dual Trace Sampling DC to R750012 Plug IN	250.00
3177A	Sampling Sweep Plug In	250,00
31.10	Spectrum Analyzer 1 to 36MHZ Plug 18	1000.00
50	Applifier Plug In	50.00
51	Sweep Plug In	50.00
9.3B	Wideband High Gain Plug In	25,00
53/548	Wideband High Gain Plug In	45,00
51/546	Dual trace Plug in	112.50
53/540	High Lain U. Differential Flug In	58.00
53/540	Fast Dive Wish Cale Dive to	68,00
84	Tast Plug to For 580/581 Main Frames	75.00
107	Sourre Wave Cenerator _ 4 to 1967	48.00
RM122	Preamplifier 2Hz to 40KHZ	63.00
123	AE Coupled Preamolifier	25.00
	He soupted is completines	
131	Current Probe Amplifier	50,00
184	Time Mark Generator	363.00
R240	Program Control Unit	150,00
280	Trigger Countdown Unit	84:00
455	Portable Dual Trace 50MHZ Scope	2000.00
400	Portable Dual Trace 100MH/ Scope	2500.00
0.16.0	DE to LEMAT Scope Back Mount	250.00
543	DE LO IDENE DEODE NACK POUNE	263.00
567	DE to 10MH7 Scope Back Mount	160.00
5614	DC to 10MH7 Scope Back Mount	200.00
		C ONAL DIA

industrial and commercial FM equipment operating from 400 to 512 MHz.

- Specified 12.5 Volt, UHF Characteristics Output Power = 13 Watts Minimum Gain = 19:4 dB Harmonics = 40 dB
- 50 Ω Input/Output Impedance

MHW 710 - 2

- Guaranteed Stability and Ruggedness
- Gain Control Pin for Manual or Automatic Output Level Control
- Thin Film Hybrid Construction Gives Consistent Performance. and Reliability

Scopes with Plug-in's

6614	DC to 109912 Scope with a 3576 Dual Trace HE to 8759912 Sampling Plug In and a 31774 Sweep Plug In. Rack Hount	A00.05
565	DC to 10962 Dash Beam Scope with a 2863 Diff and a 2863 Diff. Plug In's	908,00
993	DE to 50MHZ Scope with a 52 Dual Trace High Game Flug In	650.00

Tubes

226 - 5007 - 10007 828/866A (x2500A3 - 65A - 125A - 250A - 250A - 400A - 1000A - 500A (x250B (x250F/G (x250K	\$ 5.00 102.00 268.00 5.00 150.00 45.00 58.50 68.50 71.00 184.00 145.00 65.00 55.00 113.00	4C.8350FJ 4C.8350FJ 4C.815000A 4C.815000A 4E27 4.8150A 4.8150A 4.8150D 4.8150D 4.8150G 5.726/T160L 6LF6 6L06 811A 813 5394/A	\$116.00 300.00 350.00 750.00 41.00 52.00 74.00 39.00 5.00 12.95 29.00 42.00	6.146W 6.159 6.159 6.360 6.907 6.939 7.360 7.964 8072 8106 8156 8226 8295/PL172	12.00 10.60 75.00 18.50 6.95 40.00 14.75 12.00 10.40 49.00 2.00 7.85 127.70 328.00
ICX2508 ICX250F/G ICX250K ICX250R ICX250R ICX300A ICX350A	65,00 55,00 113,00 92,00 147,00 107,00	811A 813 5894/A 6146 6146A 6146B/8298A	12,95 29,00 42,00 5,00 6,00 7,00	8166 8226 8295/PL172 P458 8560A/AS 8908 8950	7.85 127.70 328.00 25.75 50.00 9.00

MICROWAVE COMPONENTS

COMPUTER I.C. SPECIALS

DOIOF

^			n
Ar	71	χ,	ч

ARRA			MEMORY	DESCRIPTION	PRICE
2416 3614-60 KU520A 4684-20C 6684-20F	Variable Attenuator Variable Attenuator 0 to 60dB Variable Attenuator 18 to 26.5 GHz Variable Attenuator 0 to 180dB Variable Attenuator 0 to 180dB	\$ 50.00 75.00 100.00 100.00 100.00	2708 2716/2516 2114/9114 2114L2 2114L3	1K x 8 EPROM 2K x 8 EPROM 5Volt Single Supply 1K x 4 Static RAM 450ns 1K x 4 Static RAM 250ns 1K x 4 Static RAM 350ns	\$ 7.99 20.00 6.99 8.99 7.99
General	Microwave		4027 4060/2107	4K x 1 Dynamic RAM 4K x 1 Dynamic RAM	3.99 3.99
Directional Co	oupler 2 to 4GHz 20dB Type N	75.00	4050/9050 2111A-2/8111	4K x 1 Dynamic RAM 256 x 4 Static RAM	3.99 3.99
Hewlett	Packard		2112A-2 2115AL-2	256 x 4 Static RAM 1K x 1 Static RAM 55ns	3.99 4.99
H487B H487B 477B X487A X487B	100 ohms Neg Thermistor Mount (NEW) 100 ohms Neg Thermistor Mount (USED) 200 ohms Neg Thermistor Mount (USED) 100 ohms Neg Thermistor Mount (USED) 100 ohms Neg Thermistor Mount (USED)	150.00 100.00 100.00 100.00 125.00	6104-374104 7141-2 MCM6641L20 9131	4K x 1 Static RAM 320ns 4K x 1 Static RAM 200ns 4K x 2 Static RAM 200ns 1K x 1 Static RAM 300ns	14.99 14.99 14.99 10.99
J468A	100 ohms Neg Thermistor Mount (USED)	150.00	C.P.U.'s EC	<u>DT.</u>	
478A	200 ohms Neg Thermistor Mount (USED)	150.00	MC6800L	Microprocessor	13.80
J 382 X 382A	5.85 to 8.2 GHz Variable Attenuator 0 to 50dB 8.2 to 12.4 GHz Variable Attenuator 0 to 50dB	250.00 250.00	MCM68A10P MCM68B10P MC6820P MC6820L	128 x 8 Static RAM 450ns 128 x 8 Static RAM 360ns 128 x 8 Static RAM 250ns PIA PIA	3.99 4.99 5.99 8.99 9.99
394A NK292A	1 to 2 GHz Variable Attenuator 6 to 120dB Waveguide Adapter	250.00 65.00	MC6821P MC68B21P	PIA PIA	8.99 9.99
K422A	18 to 26.5 GHz Crystal Detector	250.00	MC6840P MC6845P	PTM CRT Controller	14.99 8.99 29.50
04304	panupass rifter o to 12.4 GHZ	75.00	MC6845L MC6850L	CRT Controller ACIA	33.00
8439A 8471A	2 GHz Notch Filter RF Detector	75.00 50.00	MC6852P	SSDA	5.99
H532A G532A	7.05 to 10 GHz Frequency Meter 3.95 to 5.85 GHz Frequency Meter	300.00	MC6854P MC6860CJCS	ADLC 0-600 BPS Modem	22.00 29.00
J532A	5.85 to 8.2 GHz Frequency Meter	300.00	MC6862L MK3850N-3	2400 BPS Modem F8 Microprocessor	14.99 9.99
809A	Carriage with a 444A Slotted Line Untuned Detector Probe and 809B Coaxial Slotted Section 2.6 to 18 GHz	175.00	MK3852P MK3852N MK3854N 8008-1 8080A Z80CPU 6520	F8 Memory Interface F8 Memory Interface F8 Direct Memory Access Microprocessor Microprocessor Microprocessor	16.99 9.99 9.99 4.99 8.99 14.99
Merrimac			6530 2650	Support For 6500 series Microprocessor	15.99
AU-25A/	801115 Variable Attenuator	100.00	TMS1000NL TMS4024NC	Four Bit Microprocessor 9 x 64 Digital Storage Buffer (FIFO)	9.99
AU-26A/	801162 Variable Attenuator	100.00	TMS6011NC MC14411	UART Bit Rate Generator	9.99 11.99
			AY5-4007D AY5-9200 AX5-9100	Four Digit Counter/Display Drivers Repertory Dialler	8.99 9.99
Microlab/	FXR		AY5-2376 AY2-8500	Reyboard Encoder TV Game Chip	7.99 19.99 5.99
X638S	Horn 8.2 - 12.4 GHz	60.00	TR1402A PR1472B	UART	9.99 9.99
601-818 Y610D	X to N Adapter 8.2 - 12.4 GHz Coupler	35.00 75,00	PT1482B 8257 8251	DMA Controller	9.99 9.99
			8228 8212	System Controller & Bus Driver	9.99 5.00
Narda			MC14410CP MC14412	2 of 8 Tone Encoder Low Speed Modem	9,99 14 99
4013C-10/	22540A Directional Coupler 2:to 4 GHz 10db Type SMA	90.00	MC14408 MC14409	Binary to Phone Pulse Converter Binary to Phone Pulse Converter	12.99
4014-10/ 4014C-6/ 4015C-10/	22538 Directional Coupler 3.85 to 8 GHz 1008 Type SMA 22876 Directional Coupler 3.85 to 8 GHz 6d8 Type SMA 22539 Directional Coupler 7.4 to 12 GHz 10d8 Type SMA	90.00	MC1488L MC1489L MC1405L	RS232 Driver RS232 Receiver	1.00
4015C-30/ 3044-20	23105 Directional Coupler 7 to 12.4 GHz 30dB Type SMA Directional Coupler 4 to 8 GHz 20dB Type N	95.00	MC1405L MC1406L MC1408/6/7/8	6 Bit D/A Converter	9.00 7.50
3040-20	Direcitonal Coupler 240 to 500 MC 20dB Type N	125.00	MC1330P MC1349/50	Low Level Video Detector Video IF Amplifier	4.50 1.50 1.17
3003-10/ 3003-30/	22006 Directional Coupler 1.7 to 4 GHz 20dB Type N 22011 Directional Coupler 2 to 4 GHz 10dB Type N 22012 Directional Coupler 2 to 4 GHz 30dB Type N	75.00 75.00 75.00	MC1733L LM565	LM733 OP Amplifier Phase Lock Loop	2.40 2.50
3043-30/	22007 Directional Coupler 1.7 to 3.5 GHz 30dB Type N Directional Coupler 2 to 4 GHz 10dB Type N	125.00			
3033 3032	Coaxial Hybrid 2 to 4 GHz 3dB Type N Coaxial Hybrid 950 to 2 GHz 3 dB Type N	125.00	0		
784/ 22377	22380 Variable Attenuator 1 to 90dB 2 to 2.5 GHz Type SMA Waveguide to Type N Adapter	550.00 35.00	an		
720-6 3503	Fixed Attenuator 8.2 to 14.4 GHz 6 dB Waveguide	50.00 25.00	0		
PRD				- elec	etronics
U101	12.4 to 18 GHz Variable Attenuator 0 to 60dB	300.00	Toll Fr	ee Number	
X101 C101	8.2 to 12.4 GHz Variable Attenuator 0 to 60dB Variable Attenuator 0 to 60dB	200.00	800-52	8-0180	
205A/367 195B 185BS1	8.2 to 12.4 GHz Variable Attenuator 0 to 50dB	100.00	(For or	ders only) (602)) 242-8916
196C 170B	8.2 to 12.4 GHz Variable Attenuator 0 to 45dB 3.95 to 5.85 GHz Variable Attenuator 0 to 45dB	100.00		2111 W C	amelhack
588A 140A,C,D,E	Frequency Meter 5.3 to 6.7 GHz Fixed Attenuators	100.00 25.00		2111 W.C	ameruack
WEINSCHEL ENG.	2692 Variable Attenuator +30 to 60dB	100.00		Phoenix, Ariz	ona 85015

a annu

SATELLITE RECEIVER SYSTEM The entertainment opportunity of a lifetime!

Look what KLM,s SKY EYE 1 offers:Nearly 100 channles of the latest movies, sports, news, comedy, classic films, specials, religious programs and much more....all in clear, sharp <u>studio quality</u> picture and sound. Forget about "fringe" or no-reception areas, ghosts, fading, imaging and all the other problems of TV reception. KLM,s SKI EYE 1 is your direct link to the 11 TV satellites now orbiting above the U.S. You,ll experience great shows and the greatest picture quality you,ve ever seen.

KLM,s SKY EYE 1 is a <u>complete</u> system, featuring performance-proven "state of the art" electronics design and materials. All you need is a modest amount of space for the special parabolic antenna(it,s screened surface blends with the landscaping to become a discrete addition to your yard). Inside your home, all those channels are accessible through the compact SKY EYE 1 Control Center.

With KLM,s SKY EYE 1 your TV becomes a true enterainment center, bringing you an amazing variety of great shows-something to please every member of your family.

KLM, S SKY EYE 1 SYSTEM

Control Center

- * CONTINUOUS CHANNEL TUNING
- * CONTINUOUS AUDIO TUNING 5.8 TO 7.4 MHZ
- * POLARITY CONTROL CAPACITY, MOMENTARY AND LIMIT MODELS
- * SEPARATE REGULATED POWER SUPPLIES FOR LNA AND RECEIVER
- * STANDARD RG-59 COAX TO RECEIVER UNIT

Receiver Unit

- * SINGLE CONVERSION IMAGE REJECTION MIXER(greater linearity and video reponse than any PLL)
- * BUILT IN DC BLOCK
- * MODULAR CONSTRUCTION
- * WEATHER-PROOF ENCLOSURE

CONTROL CENTER and RECEIVER UNIT

\$1500.00

\$ 800.00

Antenna: KLM Parabolic Dish

- * SCREENED FOR LIGHT WEIGHT AND LOW WINDLOAD
- * EASY AZIMUTH AND ELEVATION CHANGES
- * MODEST BASEMOUNT REQUIREMENTS
- * HIGH GAIN LNA (AVANTEK)
- * MOTOR DRIVEN POLARITY CHANGES
- * 12 FOOT OR 16 FOOT PARABOLIC DISHES

12 Foot \$3000.00 16 Foot \$3500.00

TEST EQUIPMENT SPECIALS

HEWLETT PACKARD

180A Oscilloscope with a 1801A Dual Channel Vertical Amplifier Plug-in 50MHz and with a 1821A Time Base and Delay Generator Plug-in.

\$1250.00 <u>180A Oscilloscope</u> with a 1802A Dual Channel Vertical Amplifier Plug-in 100MHz and with a 1822A Time Base and Delay Generator Plug-in. \$1350.00

<u>181A Oscilloscope</u> with a 1803A Differential DC Offset Amplifier plug-in and with a 1825A Time Base and Delay Generator Plug-in. \$1950.00

181A Oscilloscopewith a 1807A Dual Channel Vertical Amplifier Plug-in35MHz and with a 1822A Time Base and Delay Generator Plug-in.\$1550.00(We will be glad to mix the above systems any way you would like them.)

141A Oscilloscopewith a 1402A Dual Channel Vertical Amplifier Plug-in20MHz and a 1421A Time Base and Delay Generator Plug-in.\$1690.00

<u>140A Oscilloscope</u> with a 1410A Dual Trace Sampling Plug-in DC to 1GHz and with a 1425A Sampling Time Base. (Built in probes.) \$2200.00

<u>141A Oscilloscope</u> with a 1411A Dual Trace Sampling Plug-in DC to 12.4 GHz. and with a 1424A Sampling Time Base. \$2000.00

<u>140A Oscilloscope</u> with a 1411A Dual Trace Sampling Plug-in DC to 12.4 GHz. and with a 1424A Sampling Time Base. \$1500.00

1430A Feed Thru Sampling Head DC to 12.4GHz, 28picosecond risetime. \$1250.00

302A Wave Analyzer High selectivity and sensitivity with frequency resolution of 10Hz. 20Hz to 50KHz range +-1%. 30mv to 300v full scale range. Built in AFC. 75dB dynamic range. \$ 975.00

<u>431C Power Meter</u> Measures RF Power 10uw to 10mw. 10MHz to 40GHz. with 478A Mount and cable. \$580.00

73 Magazine • December, 1980 203

TEST EQUIPMENT SPECIALS

HEWLETT PACKARD

805A Slotted Line 500MC to 4GHz , 1.04 residual SWR. \$ 250.00

<u>809B Carriage</u> with 806B Coaxial Slotted Section(.3 to 12GHz) a X810B Slotted Section(8.2 to 12.4GHz) a H810B Slotted Section (7.05 to 10GHz) a X281A X to N adapter a H281A H to N adapter a HX292B H to X adapter a 444A Probe(2.6 to 18GHz) a PRD250 Probe (2.4 to 12.4GHz) \$ 650.00

<u>340A Noise Figure Meter</u> Automatically Measures and Displays IF and RF Amplifier Noise At 30 or 60MHz. Bandwith of 1MHz. \$ 200.00

74A Automatic Noise Figure Meter with a type 70 Diode Noise Generator 10 to 250MHz a type 71 Power Supply a 07049 Noise Generator 3.95 to 5.85GHz a 07010 Noise Generator .20 to 2.6 GHz a 0752 Noise Generator.

\$ 650.00

661 90Picosecond Risetime Sampling Oscilloscope with a 4S1 350Picosecond Dual Trace Sampling Plug-In DC to 1GHz.,4S2 90Picosecond Dual Trace Plug-In DC to 3.5GHz., 4S3 350Picosecond Dual Trace Plug-In DC to 1GHz.(all above Plug-In,s are 2mv/cm to 200mv/cm. and with a 5T1 Plug-In Sampling System Timing . 1ns/cm to 100us/cm, (usefull beyond 5GHz.) \$1000.00

SPECTRUM ANALYZER PLUG-IN, S

1L5 50Hz to 1MHz , Center Frequency 50Hz to 990KHz, Dispersion -10Hz/cm to 100KHz/cm , Deflection Factor 10uv/cm to 2v/cm. \$1000.00

1L10 1MHz to 36MHz , Bandwidth resolution of 10Hz to 1KHz,Calibrated Dispersion from 10Hz to 2KHz , Sensitivity of -100dBm. \$ 900.00

1L30 925MHz to 10.5GHz , Bandwidth resolution of 1KHz to 100KHz, Dispersion of 1KHz to 10MHz/cm , Sensitivity of -75dBm to -105dBm. \$1100.00

1L40 1.5GHz to 40GHz. about same specifications as above. \$1500.00

3L10 1MHz to 36MHz same as 1L10 But For 560,561 Mainframe Oscilloscopes.

\$1000.00

HEWLETT PACKARD

TYPE	DESCRIPTION	PRICE EACH
UG-273	Female BNC to PL-259	\$ 3.00
116 - 146/11	50-239 to N Male	10.00
116 - 83a/11	N Female to PL-259	10.00
116 - 318/11	PI-259 to N Male	10.00
874	N Female to General Radio	15.00
UG-394b/u	BNC Male to N Female	10.00
116 - 255/11	BNC Male to S0-239	5.00
UG-21e/u	N Cable Connector Male	4.00
$UG = 58a/\mu \text{ or } UG = 58b/\mu$	N Female Pannel	4.50
S0-239	UHF Female Pannel	1.00
UG-1094a/u or UG-625b/u	BNC Female Bulkhead	1.35
UG-290a/u or UG-185/u	BNC Female	2.50
PL-259	UHF Cable Connector	1.00
UG-175 or UG-176	Adapter for RG58 or RG59 Cable For PL-259	.50
UG-88/u or UG-260/u	BNC Male 50 or 75 ohm	1.50
S0-239BM	SO-239 to PL-259 Quick Disconnect	3.00
UG-57b/u	N Male to Male	4.50
UG-27d/u	N 90 ⁰ Male to Female	6.50
UG-274a/u	BNC T Male Female Male	5.00
UG-636a/u	BNC Female to "C" Male	10.00
UG-564/u	"C" Female to N Male	10.00
UG-635/u	BNC Male to "C" Female	10.00
UG-565a/u	N Female to "C" Male	10.00
UG-201a/u	BNC Female to N Male	5.00
UG-306/u	BNC 90° Male to Female	3.00
M-358	UHF T Female Male Female	3.25
UG-491b/u	BNC Male to Male	5.00
UG-914/u	BNC Female to Female	3.00
PE9090	INC Female to N Male	10.00
PE9089	INC Male to N Female	10.00
PE9088	INC Female to INC Female	12.00
PE9087	INC 90° Male to remale	12 00
PE9086	TNC Female to Female	20.00
PE9085	TNC Papel and Bulkhead	3 00
PE9004,9003,9002	BNC Malo to E Eomalo	5.00
PE9001	BNC Male to TNC Female	10.00
PE9000	N Female to SMA Female Panel	30.00
PE9079	BNC Female to SMA Female Panel	30.00
PE9077	"C" Female to SMC Female Bulkhead	30.00
PE9076	SMA Male for .141 semi-ridg	3.00
PE9075	SMA Male for .085 semi-ridg	3.00
PF9074	SMA Flange Female	5.00
PE9073	SMA Flange Male	5.00
PE9072	SMA Female Short	7.50
PE9071	SMA Male 50 ohm load	10.00
PE9070	SMA Female to Female	10.00
Tektronix 011-0049-01	50 ohm 2 watt term. BNC Female to Male	15.00
FXR AH-A92	0.5dB SMA Male Female Att.	15.00
FXR AH-A93	1.0dB SMA Male Female Att.	15.00
FXR AH-A94	1.5dB SMA Male Female Att.	15.00

R F CONNECTORS COAX

COAX CABLE SPECIAL SALE

Microdot RG-174 miniature 50 ohm coax cable for small jobs.This cable was made to meet military spec.(PRICE PER FOOT)

1 to 25 foot .15 ¢ / 26 to 50 foot .12 ¢ / 51 to 100 foot .11 ¢ / 101 up .10 ¢

Microdot RG-402U

.141 miniature 50 ohm hard line / semi-ridg coax for use with SMA/SMC ect. miniature coax connectors. This cable is very low loss and is used for High Frequency projects. (PRICE PER FOOT)

1 to 10 foot \$5.00 / 11 to 25 foot \$4.00 / 26 to 50 foot \$3.00 /

Microdot RG-402U with two Male SMA Connectors Assembled. Aprox. 10 to 15" . \$ 5.00

Microdot RG-402U with two Male N Connectors Assembled. Aprox. 10 to 20".

\$15.00

KC/KHZ MC/MHZ MC/MIZ Lisson Gaisson Gaisson	
	IZ
1.982 2.3968/5 2.894 3.273625 5.7105 7.25 1.985 2.42 2.92545 2.33 5.733333 7.25 1.9942 2.4375 2.931 3.4045 5.74815 7.27 1.995975 2.44275 2.94375 3.4115 5.80741 7.34 1.96475 2.4495 2.945 3.4325 5.00741 7.34	Z 416 833 041 291 2916 2917 2916 2917 2916 2917 2918 2018 2
1.982 2.396875 2.894 3.273625 5.7037 7.22 1.985 2.42 2.92545 2.33 5.733333 7.25 1.9942 2.4375 2.931 3.4045 5.74815 7.27 1.995975 2.44275 2.94375 3.4115 5.80741 7.34 1.96475 2.4495 2.945 3.4325 5.00741 7.34	3333 296 5
1.9996592.452.946753.45355.837047.352.2.4822.9523.46755.89687.36	5555 5 35 296
$\begin{array}{cccccccccccccccccccccccccccccccccccc$	222 3 85 15 85 15
2.133275 2.633125 3.001 3.805 6.25185 7.47 2.13505 2.63575 3.0235 3.860 6.28146 7.48 2.1425 2.639 3.049 3.908 6.31111 7.49 2.144625 2.64325 3.053 3.9168 6.321458 7.62 2.14675 2.647 3.062 4. 6.37037 7.65	85 15 85 963 926

.....

The Startes		<u>CRYSTALS</u> <u>\$4.99</u>	-	
MC/MI	1Z MC/MHZ	MC/MHZ	MC/MHZ	
MC/MI 7.674 7.688 7.718 7.798 7.801 7.81 7.99 7.928 8.003 8.003 8.003 8.003 8.003 8.003 8.003 8.003 8.125 8.125 8.126 8.284 8.284 8.284 8.284 8.284 8.284 8.284 8.284 8.284	MC/MHZ 107 10.8864 889 10.962 852 11.005 15 11.13 11.1805 11.228 11.228 11.299 11.3565 11.5087 11.5337 11.5534 11.5537 11.5534 11.5537 11.5534 11.5537 11.5534 11.5537 11.5534 11.5537 11.5534 1333 11.705 11.905 11.905 11.905 11.905 11.905 11.9612 12.93 13.102 13.102 13.2155 14 13.2455 13.2845 13.3045 13.3045 13.3045 13.3045 13.3045	\$4.99 MC/MHZ 23.575 26.375 26.62 26.64 26.667 26.67 26.965 26.965 26.965 27.005 25 27.005 25 27.005 27.126 27.126 27.125 27.205 27.225 27.5 27.79 28. 28.615 28.728 28.728 28.805 28.805 28.835 28.835	MC/MHZ 35.14 35.18 35.19 35.2 35.3 35.36 35.55555 35.90125 35.97625 36.04 36.04 36.08 36.16 36.2 36.2675 36.3525 36.3875 36.4275 36.66667 37. 37.2175 37.46 37.77777 37.845 38. 38.33333 38.77777 38.88888 38.33333 38.77777 39.16	40.62963 40.66666 40.703704 40.740741 40.77777 40.814815 40.85185 40.88888 40.96296 42.59259 45. 46.2 48.98333 <u>MC/MHZ</u> 48.92777 49.21389 49.692 49.95 53.45 53.3 56.9 58.794 60.45 61.25 61.95 66.66667 67.52
8.526 8.625 8.82 8.827 8.828 8.837 8.845 8.854 8.862 8.871 8.879 8.888 8.905 8.913 8.930 8.930 8.930 8.930 8.930 8.930 8.930 8.930 8.930 8.930 8.930 8.930 8.930 8.930 8.930 8.930 8.930 8.935 9.026 9.327 9.367 9.555 9.565 9.565 9.657	13.3249 13.3349 13.3349 13.3449 14.315 15.02 15.016 15.02 17.009 17.009 17.009 17.115 17.165 17.926 17.936 17.946 17.926 17.926 17.926 17.926	$\begin{array}{cccccccccccccccccccccccccccccccccccc$	39. 39.16 39.51851 39.55555 39.592593 39.629630 39.6666667 39.703704 39.74071 39.777778 39.81481 39.851852 39.88888 39.92592 39.962963 40. 40.037037 40.074074 40.111111 40.14814 40.222222 40.225925 40.225925 40.29629 40.33333 40.37037 40.407407 40.407407 40.444444 40.48148 40.51851	$\begin{array}{c} 66.66667\\ 67.52\\ 67.82\\ 67.94\\ 68.1\\ 68.12\\ 68.18\\ 68.375\\ 68.48\\ 68.60\\ 71.015625\\ 72.855\\ 73.50\\ 75.185\\ 76.66667\\ 82.75\\ 83.\\ 84.\\ 90.833\\ 93.1346\\ 93.535\\ 93.9353\\ 94.3\\ 102.2\\ 106.85\\ 115.83\\ 121.5\\ 126.4\\ 128.\\ \end{array}$
$\begin{array}{c} 9.7\\ 9.75\\ 9.8\\ 9.85\\ 9.9\\ 9.934\\ 9.95\\ 10\\ 10.01\\ 10.02\\ 10.02\\ 10.20\\ 10.20\\ 10.35\\ 10.80\end{array}$	$ \begin{array}{r} 19.006\\ 19.1\\ 19.1003\\ 19.1003\\ 19.1033\\ 19.3483\\ 19.3484\\ 19.4312\\ 19.4526\\ 19.5385\\ 19.5385\\ 19.6608\\ 20.1\\ 22\\ 5\\ 22.22\\ 375\\ 23.25\\ \end{array} $	34.605 34.625 34.655 34.685 34.695 34.705 34.705 34.725 35.02 35.02 35.03 35.04 35.07 35.08 35.11 35.12	40.555556 40.59259 TOLL FREE # (800) 528-0180 (for orders only) Pho	146.64 147.09 CZ -48 electronics (602) 242-8916 2111 W. Camelback cenix, Arizona 85015



- * NO C.O.D.
- * SEND CHECK, M.O., OR CREDIT CARD #
- PHONE ORDERS ACCEPTED ON VISA/MASTER CHARGE ONLY (214) 278-3553
- * ADD 5% FOR SHIPPING

0

S

- * ORDERS UNDER \$10 ADD .75 HANDLING
- * TEX. RES. ADD 5% TAX
- FOREIGN ORDERS (EXCEPT CANADA) ADD 10% (20% FOR AIRMAIL).

Chorus * Star Spangled Banner * Yankee Doodle * America, America * Deutschland Leid * Wedding March * Beethoven's 5th and 9th * Hell's Bells * La Vien En Rose * Star Wars Theme * Clementine * Augustine * Jingle Bells * God Save The Queen * Colonel Bogey * Marseillaise * O Sole Mio * Santa Lucia * The End * Blue Danube * Brahms Lullaby * Westminister Chime * Simple Chime * Descending Octave Chime.

The Greatest Breakthrough in Electronic Music! Introducing.... The New SUPER MUSIC MAKER KIT

Commercial Displays

Doorbells



Less Speaker

Music Boxes

Car Horns

Super Music Machine Kit \$23.50 PC board only for Super Music Machine \$5.00 Basic Kit less IC's \$11.50 DIP Switches for PC Board (2) \$2.00 Blank 2708 EPROMS (Not programmed) \$9.60

AT LAST: An affordable kit that **can be programmed to play any song** or group of songs you desire. Instead of a nightmare of numerous IC's and special expensive bi-polar ROM's, the Super Music Maker uses a **special mask programmed computer chip**, one CMOS gate and the most popular erasable EPROM, the 2708/2716 series. The basic kit includes drilled, plated and screened PC Board. All components are provided **except** the EPROM and 12V transformer. The basic kit will play short renditions of 25 tunes through its' **7 watt amplifier section**. With the addition of an optional ROM any tune that is programmed can be played! If you have the equipment to program 2708 EPROMS we supply full information on programming your own music. If you wish to buy ROMS with tunes pre-programmed, we have arranged with another company to provide this service. MASTER MUSIC in Mt. Vernon, Missouri is **stocking a large inventory of preprogrammed ROMS**. If a Super Music Machine Kit is ordered, a listing of available ROMS and ordering information will be included with the shipment.

FEATURES:

- * The basic kit contains 25 "short" tunes, in the main IC.
- * Will address external ROM for up to 1,000 more notes per ROM. (ROM IS NOT INCLUDED!)

Toys

- * Operates on 12 volts AC or 12 volts DC*, @ 500 ma.
- * 7 watts of audio power will drive 8 or 16 ohm speakers or horn speakers. (Not Included!)
- * "Next Tune" provision steps sequencially through all tunes.
- * Tune address can be wire jumper selected or board is designed to take DIP switches, (available seperately).
- * Pitch, Volume and Tempo are all adjustable.
- * Special "chime" sequences can be activated regardless of tune address to provide for multiple doorbell applications.
- * All tunes consist of electronic musical notes played one at a time. There are no chords or harmony sound to the music.
- * Step-by-step assembly instructions provided. 90 day parts warranty, complete repair service.

*Using unit on 12 volts DC and with option ROM requires 9V bias battery, (not included).

BULLET ELECTRONICS -12 P.O. BOX 401244-E GARLAND, TX. 75040 THIS KIT IS IN STOCK. YOU WILL LOVE OUR FAST SERVICEI SEE OPPOSITE PAGE FOR ORDERING INFORMATION & POLICIES.



These Low Cost SSB TRANSMITTING CONVERTERS

Let you use inexpensive recycled 10M or 2M SSB exciters on UHF & VHF!

- Linear Converters for SSB, CW, FM, etc.
- A fraction of the price of other units; no need to spend \$300 - \$400!
- Use with any exciter; works with input levels as low as 1 mW.
- Use low power tap on exciter or simple resistor attenuator pad (instructions included).
- Link osc with RX converter for transceive.



XV4 UHF KIT — ONLY \$99.95

28-30 MHz in, 435-437 MHz out; 1W p.e.p. on ssb, up to 11/2W on CW or FM. Has second oscillator for other ranges. Atten, supplied for 1 to 500 mW input, use external attenuator for higher levels.

Extra crystal for 432-434 MHz range	\$5.95
XV4 Wired and tested\$	149.95

XV2 VHF KIT - ONLY \$69.95

2W p.e.p. output with as little as 1mW input. Use simple external attenuator. Many freq. ranges available.

MODEL	INPUT (MHz)	OUTPUT (MHz)
XV2-1	28-30	50-52
XV2-2	28-30	220-222
XV2-4	28-30	144-146
XV2-5	28-29 (27-27.4 0	CB)145-146 (144-144.4)
10.00		

Easy to Build FET RECEIVING CONVERTERS

Let you receive OSCAR and other exciting VHF and UHF signals on your present HF or 2M receiver



NEW LOW-NOISE DESIGN

ATTRACTIVE WOODGRAIN CASE

Less than 2dB noise figure, 20dB gain

MODEL	RF RANGE	OUTPUT RANGE	
CA28	28-32 MHz	144-148 MHz	
CA50	50-52	28-30	
CA50-2	50-54	144-148	
CA144	144-146	28-30	
CA145	145-147-or-	28-30	
	144-144.4	27-27.4 (CB)	
CA146	146-148	28-30	
CA220	220-222	28-30	
CA220-2	220-224	144-148	
CA110	Any 2MHz of	26-28	
Aller Aller and	Aircraft Band	or 28-30	
CA432-2	432-434	28-30	
CA432-5	435-437	28-30	
CA432-4	432-436 144-148		
Easily	modified for other	f and if ranges.	

STYLE	VHF	UHF	
Kit less case	\$34.95	\$49.95	
Kit with case	\$39.95	\$54.95	
Wired/Tested in case	\$54.95	\$64.95	

FAMOUS HAMTRONICS PREAMPS

Let you hear the weak ones too! Great for OSCAR, SSB, FM, ATV. Over 14,000 in use throughout the world on all types of receivers.



NEW LOW-NOISE DESIGN

- Less than 2 dB noise figure, 20 dB gain
- Case only 2 inches square
- Specify operating frequency when ordering

MODEL P-30 VHF PREAMP, available in many versions to cover bands 18-300 MHz.

MODEL P432 UHF PREAMP, available in versions to cover bands 300-650 MHz.

STYLE	VHF	UHF	
Kit less case	\$12.95	\$18.95	
Kit with case	\$18.95	\$26.95	
Wired/Tested in Case	\$27.95	\$32.95	

NEW VHF/UHF FM RCVRS **Offer Unprecedented Range of Selectivity Options**



XV2-7	144-146	50-52
XV2 Wired a	nd tested	\$109.9

XV28 2M ADAPTER KIT - \$24.95

Converts any 2M exciter to provide the 10M signal required to drive above 220 or 435 MHz units.



NEW! COMPLETE TRANSMITTING CONVERTER AND PA IN ATTRACTIVE CABINET

Far less than the cost of many 10W units!

Now, the popular Hamtronics® Transmitting Converters and heavy duty Linear Power Amplifiers are available as complete units in attractive, shielded cabinets with BNC receptacles for exciter and antenna connections. Perfect setup for versatile terrestial and OSCAR operations! Just right for phase 3! You save \$30 when you buy complete unit with cabinet under cost of individual items. Run 40-45 Watts on VHF or 30-40 Watts on UHF with one integrated unit! Call for more details.

MODEL	KIT	WIRED and TESTED	
XV2/LPA2-45/Cabt (6M or 2M)	\$199.95	\$299.95	
XV4/LPA4-30/Cabt (for UHF)	\$229.95	\$349.95	

IT'S EASY TO ORDER! ~33 Write or phone 716-392-9430

(Electronic answering service evenings & weekends) Use Credit Card, UPS COD, Check, Money Order

Add \$2.00 shipping & handling per order

when/rested in case

Professional Quality VHF/UHF FM/CW EXCITERS

- Fully shielded designs
- Double tuned circuits for spurious suppression
- Easy to align with built-in test aids



T50-50	6-chan, 6M, 2W Kit\$44.95
T50-150	6-chan, 2M, 2W Kit \$44.95
T50-220	6-chan, 220 MHz, 2W Kit \$44.95
T450	1-chan, 450 MHz, ¾W Kit \$44.95

See our Complete Line of VHF & UHF Linear PA's

Use as linear or class C PA

For use with SSB Xmtg Converters, FM Exciters, etc.

PA2-15	6M, 2M, 220; 15 to 20W\$59.9	5
PA2-30	6M, 2m; 25 to 30W \$89.9	5
PA2-40	220 MHz; 30 to 40W\$119.9	15
PA2-45	6M, 2M; 40 to 45W \$119.9	5
PA4-10	430MHz; 10 to 14W \$79.9	15
PA4-30	430MHz; 30-40W\$119.9	95
Se	e catalog for complete specifications	

Call or Write to get FREE CATALOG With Complete Details (Send 4 IRC's for overseas mailing)

HAMTRONICS° IS A REGISTERED TRADEMARK



R75A* VHF Kit for monitor or weather sattelite service. Uses wide L-C filter. -60dB at ± 30 kHz..... \$69.95

R75B* VHF Kit for normal nbfm service. Equivalent to most transceivers.-60dBat±17kHz,-80dBat±25kHz...\$74.95

R75C* VHF Kit for repeater service or high rf density area. -60dBat±14kHz,-80dB±22kHz,-100dB±30kHz....\$84.95

R75D* VHF Kit for split channel operation or repeater in high density area. Uses 8-pole crystal filter. -60dB at ±9 kHz, -100dB at ± 15 kHz. The ultimate receiver1... \$99.95

* Specify band: 10M, 6M, 2M, or 220 MHz. May also be used for adjacent commercial bands. Use 2M version for 137 MHz WX satellites.

R450() UHF FM Receiver Kits, similar to R75, but for UHF band. New low-noise front end. Add \$10 to above prices. (Add selectivity letter to model number as on R75.)

A14 5 Channel Adapter for Receivers......\$9.95

NEW R110 VHF AM RCVR

AM monitor receiver kit similar to R75A, but AM. Available for 10-11M, 6M, 2M, 220 MHz, and 110-130 MHz aircraft band \$74.95. (Also available in UHF version.)



2822 North 32nd Street, #1 • Phoenix, Arizona 85008 • Phone 602-956-9423

MRF472

SEVICENTULINING SURPLUS

MEMORY

2708 2716/2516	Description	Price	12.5 VDC, 27 MHz
	IK x 8 Eprom	\$ 5.00	4 Watts output, 10 dB gain
	2K x 8 5V single supply	9.99	\$1.69 each
2114/9114 4027 2117/4116 2732-6	1K x 4 Static 4K x 1 Dynamic Ram 16K x 1 Dynamic Ram 32K Eprom	5.00 2.99 5.00 39.95	CARBIDE CIRCUIT BOARD DRILL BITS for PCB Boards 5 mix for \$5.00
C.P.U.'s, Etc.			MURATA CERAMIC FILTERS
MC6800P	Microprocessor	9.99	SFB 455D 455 KHz 1.60
MC68B21P	PIA		CFM 455E 455 KHz 5.50
MC6845P MC6850P	CRT Controller ACIA	25.00 4.99	SFE 10.7 MA 10.7 MHz 2.99
MC6852P	SSDA	5.00	ATLAS CRYSTAL FILTERS FOR ATLAS
8008-1	Microprocessor		HAM GEAR
8080A	Microprocessor	5.00	5.52 - 2.7/8
Z80A	Microprocessor		5.595 - 2.7/8/U
Z80	Microprocessor	8.99	5.645 - 2.7/8
Z80A	PIO	9.99	5.595500/4/CW YOUR CHOICE
Z80 Z80	S10/0 S10/1	22.50	5.595 - 2.7 USB \$12.99 each

Z80	S10/1	22.50	5.595 - 2.7/8/L
8212	8 Bit input/output part	3.99	5.595 - 2.7 LSB
8251	Communication Interface	6.99	9.0 - USB/CW
TR1602/AY5-1013	UART	6.99	
TMS 1000NL	Four Bit Microprocessor	4.99	J310 N-CHANNEL J-FET 450 MHz
PT1482B	PSAT	5.99	Good for VHF/UHF Amplifier,
8257	DMA Controller	8.99	Oscillator and Mixers 3/\$1.00
3341	64 x 4 FIF0	3.00	
MM5316/F3817	Clock with alarm	5.99	AMPHENOL COAX RELAY
8741		60.00	26 VDC Coil SPDT #360-11892-13
8748	8 Bit Microcomputer with		100 Watts Good up to 18 GHz
-/	programmable/ erasable EPROM	60.00	\$19,99 each
MC14081/6	6 Bit D/A	3.25	Tipting
COM2502		9,99	78M05 Same as 7805 but only 1 Amp @
COM2601		9,99	5 VDC 49¢ each or 10/\$3.00
TYCO 001-19880 10.7 MHz narrow 3 dB bandwidth 1 20 dB bandwidth 40 dB bandwidth Ultimate 50 dB i Ripple 1 dB max. \$3.99 each MRF454, same as	Same as 2194F band 5 KHz min. 60 KHz min. 150 KHz min. nsertion loss 1 dB max. Ct. 0+/-5 pf 3600 Ohms MRF458 12.5 VDC, 3-30 MHz		F-18x 6.3 VCT @ 6 Amps \$6.99 ea. F-46x 24 V @ 1 Amp 5.99 ea. F-46x 24 V @ 1 Amp 5.99 ea. F-41x 25.2 VCT @ 2 Amps 6.99 ea. P-8380 10 VCT @ 3 Amps 7.99 ea. P-8604 20 VCT @ 1 Amp 4.99 ea. P-8130 12.6 VCT @ 2 Amps 4.99 ea. K-32B 28 VCT @ 100 MA 4.99 ea. E30554 Dual 17V @ 1Amp ea. 6.99 ea. EIMAC FINGER STOCK #Y-302
80 Watts output,	12 dB gain \$17.95 each NO ORDERS U	JNDER \$10	36 in. long x ½ in. \$4.99 each



MRF 203	\$P.O.R.	BFW92A	\$ 1.00	UHF/VHF RF POWER TRANSISTORS
MRF216	19.47	BFW92	.79	CD2867/2N6439
MRF 221	8.73	MMCM913	14.30	60 Watts output
MRF 226	10.20	MMCM2222	15.65	Reg. Price \$45.77
MRF 227	2.13	MMCM2369	15.00	SALE PRICE \$19.99
MRF238	10.00	MMCM2484	15.25	
MRF240	14.62	MMCM3960A	24.30	1900 MHz to 2500 MHz DOWNCONVERTERS
MRE 245	28.87	MWA110	6 92	Intended for amateur radio use
MRE247	28 87	MWA120	7 38	Tunable from channel 2 thru 6
MRE 262	6 25	MUA 120	8 08	3/4 dB gain 2 5 = 3 dB noise
MDE21/	12 20	MUADIO	7.16	Varranty for 6 months
MAR JI4	11.22	MWAZIO	7.40	Warranty for o months
MRF 400	11.35	MWAZZO	0.00	Model HMK II with dish antenna
MRF412	20.05	MWA230	0.02	complete Receiver and Power Supply
MRF 421	27.45	MWA310	8.08	\$225.00 (does not include coax)
MRF422A	38.25	MWA320	8.62	4 foot Yagi antenna only
MRF 422	38.25	MWA330	9.23	\$39.99
MRF 428	38.25			Downconverter Kit - PCB and parts
MRF 428A	38.25	TUBES		\$69.95
MRF 426	8.87	6кр6	\$ 5.00	Power Supply Kit - Box, PCB and parts
MRF426A	8.87	6LQ6/6JE6	6.00	\$49.99
MRF449	10.61	6MJ6/6LQ6/6JE6C	6.00	Downconverter assembled
MRF449A	10.61	6LF6/6MH6	5.00	\$79.99
MRF450	11.00	12BY7A	4.00	Power Supply assembled
MRF450A	11.77	2E26	4.69	\$59.99
MRE 452	15.00	4×150A	29.99	Complete Kit with Yagi antenna
MRE453	13 72	4CY 250B	45 00	\$109.99
MRE454	21 83	4CX2508	69.00	REPLACEMENT PARTS
MRELISLA	21 83	4072000	100.00	MREQUI CALLAR C 3 99
MDELEE	1/1.08	40A 300A	109.99	MPD101 1 20
MOELEEA	1/1 08	46x 350A/0521	100.00	001 Chip Cape 1.00
MRF 455A	14.00	4LX 350F / J/0904	100.00	Bours supply DCP / 00
MRF4/2	2.50	46215008/0000	300.00	Power supply PCB 4.99
MRF 4/4	3.00	811A	20.00	Downconverter PLB 19.99
MRF 4/5	2.90	6360	4.69	
MRF476	2.25	6939	7.99	NEW ASCII ENCODED KEYBOARDS
MRF 477	10.00	6146	5.00	110 Keys Numeric and Cursor Pad
MRF485	3.00	6146A	5.69	No data available \$19.99
MRF 492	20.40	6146B/8298	7.95	
MRF502	.93	6146W	12.00	86 PIN MOTOROLA BUS EDGE CONNECTORS
MRF604	2.00	6550A	8.00	Gold plated contacts
MRF629	3.00	8908	9.00	Dual 43/86 pin .156 spacing
MRF648	26.87	8950	9.00	Solder tail for PCB \$3.00 each
MRF 901	3.99	4-400A	71.00	
MRE 902	9.41	4-4000	80.00	CONTINUOUS TONE BUZZERS
MRE 904	3.00	572B/T1601	44.00	12 VDC \$2.00 each
MREQII	4 29	7280	9 95	12 100 92100 00011
MRE5176	11 73	2-10007	229 00	110 VAC MUEEIN FANS
MPESOOL	1 20	3-10002	120.00	Now \$11 05 llead \$5 05
MRF 0004	1.00	3-5002	129.99	New 311.95 Used 32.55
DERGU	1.00		OCHETC	DI 200 TERMINATION 52 Ober 5 Hatte
BERGI	1.25	10-3 TRANSISTOR S	UCKETS	PL-259 TERMINATION 52 UNM 5 Watts
BFR96	1.50	Phenolic type 6	5/\$1.00	\$1.50 each
				A10
NO ORDERS UNDER \$10				

the first name in Counters! ramseu 9 DIGITS 600 MHz \$129 %

PRICES	
CT-90 wired, I year warranty	\$129.9
CT-90 Kit. 90 day parts war-	
ranty	109.9
AC I AC adapter	3.9
BP-1 Nicad pack + AC	
Adapter/Charger	12.9
OV-1, Micro-power Oven	
time base	49.9
External time base input	14.9

The CT-90 is the most versatile, feature packed counter available for less than \$300.00! Advanced design features include: three selectable gate times, nine digits, gate indicator and a unique display hold function which holds the displayed count after the input signal is removed! Also, a 10mHz TCXO time base is used which enables easy zero beat calibration checks against WWV. Optionally; an internal nicad battery pack, external time base input and Micropower high stability crystal oven time base are available. The CT-90, performance you can count on!

WIKED
0 MHz
MV to 150 MHz
MV to 500 MHz
MHz range)
MHz range)
0 MHz range)
LED
.000 mHz, 1.0 ppm 20-40°C.
cro-power oven-0.1 ppm 20-40°C
250 ma

7 DIGITS 525 MHz \$9995

SPECIFICATIONS:

Range:	20 Hz to 525 MHz
Sensitivity:	Less than 50 MV to 150 MHz
	Less than 150 MV to 500 MHz
Resolution:	1.0 Hz (5 MHz range)
	10.0 Hz (50 MHz range)
	100.0 Hz (500 MHz range)
Display:	7 digits 0.4" LED
Time base:	1.0 ppm TCXO 20-40°C
Power.	12 VAC @ 250 ma

The CT-70 breaks the price barrier on lab quality frequency counters. Deluxe features such as; three frequency ranges - each with pre-amplification, dual selectable gate times, and gate activity indication make measurements a snap. The wide frequency range enables you to accurately measure signals from audio thru UHF with 1.0 ppm accuracy - that's .0001%! The CT-70 is the answer to all your measurement needs, in the field, lab or ham shack.

111	

PRICES:

CT-70 wired, 1 year warranty	\$99.95
CT-70 Kit, 90 day parts war-	
ranty	84.95
AC-1 AC adapter	3.95
BP-1 Nicad pack + AC	
adapter/charger	12.95



7 DIGITS 500 MHz \$79 95

PRICES:

MINI-100 wired, 1 year	
warranty	\$79.95
MINI-100 Kit, 90 day part	
warranty	59.95
AC-Z Ac adapter for MINI-	
100	3.95
BP-Z Nicad pack and AC	
adapter/charger	12.95

Here's a handy, general purpose counter that provides most counter functions at an unbelievable price. The MINI-100 doesn't have the full frequency range or input impedance qualities found in higher price units, but for basic RF signal measurements, it can't be beat' Accurate measurements can be made from 1 MHz all the way up to 500 MHz with excellent sensitivity throughout the range, and the two gate times let you select the resolution desired. Add the nicad pack option and the MINI-100 makes an ideal addition to your tool box for "in-the-field" frequency checks and repairs.

WIRED

SPECIFICATIONS:

1 MHz to 500 MHz
Less than 25 MV
100 Hz (slow gate)
1.0 KHz (fast gate)
7 digits, 0.4" LED
2.0 ppm 20-40°C
5 VDC @ 200 ma

8 DIGITS 600 MHz \$159% WIRED



SPECIFICATIONS:

Range: 20 Hz to 600 MHz Less than 25 mv to 150 MHz Sensitivity: Less than 150 my to 600 MHz Resolution: 1.0 Hz (60 MHz range) 10.0 Hz (600 MHz range) 8 digits 0.4" LED Display: Time base: 2.0 ppm 20-40°C 110 VAC or 12 VDC Power.

The CT-50 is a versatile lab bench counter that will measure up to 600 MHz with 8 digit precision. And, one of its best features is the Receive Frequency Adapter, which turns the CT-50 into a digital readout for any receiver. The adapter is easily programmed for any receiver and a simple connection to the receiver's VFO is all that is required for use. Adding the receiver adapter in no way limits the operation of the CT-50, the adapter can be conveniently switched on or off. The CT-50, a counter that can work double-duty!

PRICES:	125	T	-	-	m
T TFT C TO TO T	м	ы 1	£13	Þ.	200
		1.77	~	n.	hare:

T-50 wired, 1 year warranty	\$159.95
T-50 Kit, 90 day parts	
arranty	119.95
A-1, receiver adapter kit	14.95
A-1 wired and pre-program-	
ned (send copy of receiver	
chematic)	29.95



ECEIVER

DIGITAL MULTIMETER \$99%

PRICES:	
DM-700 wired, 1 year warranty DM-700 Kit, 90 day parts	\$99.95
warranty	79.95
AC-1, AC adaptor	3.95
BP-3, Nicad pack +AC	
adapter/charger	19.95
MP-1, Probe kit	2.95

The DM-700 offers professional quality performance at a hobbyist price. Features include; 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 31/2 digit, 1/2 inch LED readout with automatic decimal placement, automatic polarity, overrange indication and overload protection up to 1250 volts on all ranges, making it virtually goof-proof! The DM-700 looks great, a handsome. jet black, rugged ABS case with convenient retractable tilt bail makes it an ideal addition to any shop.

SPECIFICATIONS:

DC/AC volts	100uV to 1 KV, 5 ranges
DC/AC	
current	0.1 uA to 2.0 Amps, 5 ranges
Resistance:	0.1 ohms to 20 Megohms, 6 ranges
Input	
impedance:	10 Megohms, DC/AC volts
Accuracy:	10.1% basic DC volts
Power.	4 'C' cells

AUDIO SCALER

For high resolution audio measurements, multiplies UP in frequency.

- Great for PL tones
- Multiplies by 10 or 100
- 0.01 Hz resolution!
 - \$29.95 Kit \$39.95 Wired

ramsey electronic's, inc.

2575 Baird Rd. Penfield, NY 14526



Telescopic whip antenna - BNC plug	7.9
High impedance probe, light loading	15.9
Low pass probe, for audio measurements	15.9
Direct probe, general purpose usage	12.9
Tilt bail, for CT 70, 90, MINI-100	3.9
Color burst calibration unit, calibrates counter	
against color TV signal	14.9



COUNTER PREAMP

7.95	
5.95	For measuring extremely weak signals from 10 to 1,000
5.95	MHz. Small size, powered by plug transformer-included.
2.95	Flat 25 db gain
3.95	BNC Connectors
4.95	 Great for sniffing RF with pick-up loop \$34.95 Kit \$44.95 Wired

HRMS

Satisfaction guaranteed examine for 10 days if not pleased return in original form for retund. Add 5% for shipping insurance to a maximum of \$10. Overseas add 15% COD add \$2 Orders under \$10 add \$1.50 NY residents add 7 tax

INTRODUCING SONY'S NEW DIGITAL DIRECT ACCESS RECEIVER!

A Whole New Breed Of Radio

Innovative design. Advanced technology. Digital key-touch tuning. The ICF-2001. It's a whole new breed of radio. A receiver that supplants the conventional multi-band concept, receiving a wide amplitude-modulated frequency rangeshortwave, mediumwave and most longwave broadcasts. Plus FM, SSB and CW. Even more important, the 2001 replaces the ordinary tuning knob and dial with a direct-access tuning keyboard and a Liquid Crystal Display (LCD) for digital frequency readout. Which make the unit as easy to use as a pocket calculator. Instant, direct-access tuning modes and six memory-station presets assure maximum ease of use. And the quartz-crystal, frequency-synthesized circuitry behind them assures outstanding reception. Reception of local broadcasts and exciting news, music, sports, entertainment and information from around the world. You'll get the inside, local news stories from foreign countries ... exclusive coverage of world sports events ... plus everything from informal "ham" to marine communications. All at your fingertips.

Key-Touch Tuning

To tune a station manually, you simply punch in the station frequency numerals on the direct-access, digital tuning keyboard. Press the "Execute" key and the command is entered, the station is received and LCD readout confirms tuning. If you punch in an incorrect frequency by mistake, the ICF-2001 tells you to "Try Again" by flashing those words on the display. The instant, fingertip tuning provides total accuracy and convenience. And the LCD digital frequency display confirms the exact, drift-free signal reception.

Automatic Scanning

In auto-scan mode, the tuner can be set for continuous



Frequency Synthesis

The 2001's direct-access tuning and outstanding reception quality are made possible by the unit's all-band quartz-crystal. PLL frequency synthesis. Instead of the conventional analog tuning system, with its variable tuning capacitor, the 2001 incorporates an LSI and a quartz-crystal reference oscillator. Which means that the local-oscillator frequencies used in superheterodyning are locked to the "synthesized" quartz reference frequencies. The result is the utmost in tuning stability, without a trace of tuning drift. In addition, dualconversion superheterodyning for AM assures exceptionally clean, clear reception across the entire 150-to-29,999kHz spectrum.

Features

FM/AM/SSB/CW/wide spectrum coverage

Dual-conversion superheterodyne circuitry of AM assures high sensitivity and interference rejection

scanning of a given frequency range, which you set by means of upper and lower limit keys designated "L," and "L₂." You may want to scan an entire frequency range. For instance, the 76 to 108 MHz FM spectrum. If you want scanning to stop at any strong signal—one that reads "4" or "5" on the LED signalstrength indicator— switch on "Scan Auto Stop." For continuous scanning, leave the switch off, and just press the "Start/Stop" key to listen to a station or resume scanning.

Manual Tuning

Like the auto-scanning mode, manual tuning is useful for quick signal searching when you don't know particular station frequencies within a given range. You simply press the "Up" or "Down" key, and the tuner does the searching for you. And if you press the "Fast" key at the same time, the scanning rate increases for especially rapid station location. When you hear a broadcast you want to receive, just release the keys for instant reception, presssing the "Up" or "Down" key again if necessary for exact tuning.

Memory Presets

After you've tuned a station using punch-in, key-touch tuning or either scanning mode, you can enter it in the 2001's memory for instant, one-touch preset reception. Which means no retuning hard-to-find foreign broadcasts. Plus instant access to your favorite local stations for music and news. Six preset buttons allow up to six stations—in any wave range—to be memorized. And there's LCD digital readout of the memory buttons being used on each band. What's more, the upper and lower limit keys can be used as memory presets when they're not being used for scanning, allowing a total of eight frequencies to be memorized for instant, one-touch reception. Quartz-crystal, phase-locked-loop frequency synthesis for all bands assures the utmost tuning stability, without a trace of tuning drift

Direct-access, digital tuning keyboard and LCD digital frequency readout for quick, key-touch station selection-maximum accuracy and ease of use

Manual tuning and automatic scanning for effortless signal searching, easy DXing

6-station presets, plus 2 auxiliary presets, for instant reception of memorized stations on any band-plus LCD memory indication.

5-step LED signal-strength indicator

Local/Normal/DX sensitivity selector for AM

SSB/CW compensator for low-distortion reception

Telescopic antenna, plus external antenna included

4" speaker for full, rich sound

Slide-bar bass and treble controls

Sleep timer-with LCD readout-can be set in 10-minute increments for up to 90 minutes of play before automatic radio shut-off





Plus \$5.00 S&H (Cont'l U.S.A. Only)

PHONE: (312) 848-6777 **SPECTRONICS,** INC. – 1009 GARFIELD ST., OAK PARK, ILL.-60304

AZDEN * NEW! * AZDEN * NEW! * AZDEN * NEW! * AZDEN THE GIANT A ZDEN COMPANY **REVOLUTIONIZES THE STATE OF THE ART** AWE AND AZDEN. INTRODUCE THE BRILLIANT NEW PCS-2800 MICROCOMPUTER CONTROLLED SUPERIOR COMMERCIAL GRADE **10 METER** FM TRANSCEIVER FALL SALE

AZDEN		f took	TOK	Anne	SCANME
2 4 5/RF 1 10 0 0 0 0 0			NOK		v./ -
UL MAIN	MM MEMORY ADDRESS	DOWN	Pown		-
POWER/VOL R	ATT/SOL HIGH/LOW VOLASOL	MAIN	ADRS	-	







ster charg

COMPARE THESE FEATURES WITH <u>ANY</u> UNIT AT <u>ANY</u> PRICE

- FREQUENCY RANGE: Receive and transmit: 28.000 to 29.995 MHz, 10KHz steps with built-in + 100 KHz repeater offset.
- ALL SOLID STATE-CMOS PL DIGITAL SYNTHESIZED.
- SIZE: UNBELIEVABLE! ONLY 63/4" x 23/8" x 93/4".COMPARE!
- MICROCOMPUTER CONTROLLED: All scanning and frequencycontrol functions are performed by microcomputer.
- DETACHABLE HEAD: The control head may be separated from the radio for use in limited spaces and for security purposes.
- SIX-CHANNEL MEMORY: Each memory is re-programmable. Memory is retained even when the unit is turned off.
- MEMORY SCAN: The six channels may be scanned in either the "busy" or "vacant" modes for quick, easy location of an occupied or unoccupied frequency. AUTO RESUME. <u>COMPARE!</u>
- FULL-BAND SCAN: All channels may be scanned in either "busy" or "vacant" mode. This is especially useful for locating repeater frequencies in an unfamiliar area. AUTO RESUME. COMPARE!
- INSTANT MEMORY-1 RECALL: By pressing a button on the microphone or front panel, memory channel 1 may be recalled for immediate use.
- MIC-CONTROLLED VOLUME AND SQUELCH: Volume and squelch can be adjusted from the microphone for convenience in mobile operation.
- DIRECT FREQUENCY READOUT: LED display shows operating frequency, NOT channel number. COMPARE!

- distance communications. LED readout displays power selection when transmitting.
- DIGITAL S/RF METER: LEDs indicate signal strength and power output. No more mechanical meter movements to fall apart!
- LARGE ½-INCH LED DISPLAY: Easy-to-read frequency display minimizes "eyes-off-the-road" time.
- PUSHBUTTON FREQUENCY CONTROL FROM MIC OR FRONT PANEL: Any frequency may be selected by pressing a microphone or front-panel switch.
- SUPERIOR RECEIVER SENSITIVITY: 0.28 uV for 20-dB quieting. The squelch sensitivity is superb, requiring less than 0.1 uV to open. The receiver audio circuits are designed and built to exacting specifications, resulting in unsurpassed received-signal intelligibility.
- TRUE FM, NOT PHASE MODULATION: Transmitted audio quality is optimized by the same high standard of design and construction as is found in the receiver. The microphone amplifier and compression circuits offer intelligibility second to none.
- OTHER FEATURES: Dynamic Microphone, built in speaker, mobile mounting bracket, external remote speaker jack (head and radio) and much, much more. All cords, plugs, fuses, microphone hanger, etc. included. Weight 6 lbs.
- ACCESSORIES: 15' REMOTE CABLE.... 35.00 FMPS-4R A/C POWER SUPPLY....\$39.95. TOUCHTONE MIC. KIT....\$39.95. EXTERNAL SPEAKER....\$18.00.

• TEN (10) WATTS OUTPUT: Also 1 watt low power for shorter

AMATEUR-WHOLESALE ELECTRONICS ORDER NOW TOLL FREE 8817 S.W. 129th Terrace, Miami, Florida 33176 Telephone (305) 233-3631 • Telex: 80-3356 Hours: 9-5 Mon.-Fri. U.S. DISTRIBUTOR U.S. DISTRIBUTOR

DEALER INQUIRIES INVITED

CREDIT CARD HOLDERS MAY USE OUR TOLL FREE ORDERING NUMBER.
RAMSEY ELECTRONIC'S

162

301

324

380 555 556

565

566

567

741

1458

3900

3914

8038

4011

4013

4046

4049

4059

4511

4518

5639

2N6028 C+F

2N3055

2N2646 UJT

Inc.

PARTS WAREHOUSE

We now have available a bunch of goodies too good to bypass. Items are limited so order today

MINI KITS - YOU HAVE SEEN THESE BEFORE NOW HERE ARE OLD FAVORITE AND NEW ONES TOO. **GREAT FOR THAT AFTERNOON HOBBY.**



2575 Baird Rd. Penfield, NY 14526 716-586-3950

Call Your Phone Order in Today

TERMS: Satisfaction guaranteed or money refunded, C.O.D. add \$2.00. Minimum order \$6.00. Orders under \$10.00 add \$1.50. Add 5% for postage, insurance, handling. Overseas add 15%, N.Y. residents add 7% tax.

	Color Organ See music come	Via Converts any stable, tunab 15V, accepts the market!	teo Modulator TV to video m le over ch 4-6 std video signa Complete kit. V	Kit onitor Super Runs on 5- Il Bestuniton /D-1 \$7.95		CLOCK KITS Your old favorites are here again. Over 7,000 Sold to Date. Be one of the gang and order yours today!			
A super high performance FM wire- less mike kit! Transmits a stable signal up to 300 yards with excep- tional audio quality by means of its built in electret mike. Kit includes case, mike, on-off switch, antenna, battery and super instructions. This is the finest unit available.	alive! 3 different lights flicker with music. One light each for, high, mid-range and lows. Each indi- vidually adjust- able and drives up to 300 W runs on 110 VAC. Complete kit.	Led Blinky Kit A great attention get- ter which alternately flashes 2 jumbo LEDs. Use for name badges, buttons, warning panel lights, anything! Runs on 3 to 15 volts. Complete kit, BL-1 \$2.95		Super Sleuth A super sensitive ampli- fier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general pur- pose amplifier Full 2 W rms output, runs on 6 to 15 volts, uses 8-45 ohm speaker Complete kit, BN-9 \$5.95		Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six .4" LED digits provide a highly readable display. This is a complete kit, no extras needed, and it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, black (specify). Clock kit, 12/24 hour, DC-5 Clock with 10 min. ID timer, 12/24 hour, DC-10 Alarm clock, 12 hour only, DC-8 12V DC car clock, DC-7 S29.95			
FM-3 Kit \$14.95 FM-3 Wired and Tested 19.95	ML-1 \$8.95	CPO-1 Runs on 3-12 Alarm, Audio	Vdc 1 wall c Oscillator	out, 1 KHZ goo Complete kit	od for CPO. \$2.95	For wired and tested close SPECIFY 12 OR 2	cks add \$10.00 to kit price. 24 HOUR FORMAT		
FM Wireless Mike Kit Transmits up to 300' to any FM broadcast ra- tio, uses any type of mike. Runs on 3 to 9V. Type FM-2 has added sensitive mike preamp stage. FM-1 kit \$3.95 FM-2 kit \$4.95	Wireless Mike Kit Ismits up to 300' to FM broadcast ra- uses any type of Runs on 3 to 9V Type FM-2 added sensitive mike preamp e. 1 kit \$3.95 FM-2 kit \$4.95 Whisper Light Kit An interesting kit, small mike picks up sounds and converts them to light. The louder the sound, the brighter the light. Includes mike, controls up to 300 W, runs on 110 VAC. Complete kit, WL-1 \$6.95			Decoder te tone deco- a single PC eatures 400- adjustable 20 turn pot. vo 7 IC Useful st detection, be used as a s Runs on 5 to kit, TD-1	Itage regu- for touch- FSK, etc stable tone 12 volts 5.95	Car Clock The UN-KIT, only 5 solder connections Here's a super looking rugged and accurate auto clock which is a snap to build and install Clock movement is completely assembled — you only solder 3 wires and 2 switches takes about 15 minutes! Display is bright green with automatic brightness control photocell — assures you of a highly readable display day or night. Comes in a satin finish anodized aluminum case which can be attached 5 different ways using 2 sided tape. Choice of silver, black or gold case (specify) DC-3 kit 12 hour format DC-3 wired and tested \$22.95			
Universal Timer Kit Provides the basic parts and PC board required to provide a source of precision timing and pulse generation Uses 555 timer IC and includes a range of parts for most	Mad Blaster Produces LOUD ear sh attention getting siren Can supply up to 1 obnoxious audio. Runs o	Produces wail char siren. 5 W on 3-15 speaker Complete	Siren Kit upward and acteristic of peak audio of volts, uses kit, SM-3	downward a police utput, runs 3-45 ohm \$2.95	Calendar Alarm Clock The clock that's got it all: 6-5" LEDs, 12/24 hour, snooze, 24 hour alarm, 4 year calendar, battery backup, and lots more. The super 7001 chip is used. Size, 5x4x2 inches. Complete kit. less case (not available) DC-9. \$34,95 Under Dash Car Clo 12/24 hour clock in a beautiful plastic 6 jumbo RED LEDS high accuracy 3 wire hookup display blanks with super instructions. Optional dimmer adjusts display to ambient light level DC-11 clock with mtg bracket DM-1 dimmer adapter. Add \$10.00 Assy and Ter				
timing needs. UT-5 Kit \$5.95		Runs on 5-1 min/month acc TB-7 Assy	60 Hz Time Bas 5 VDC Low curre uracy TB-7 Kit	e nt (2 5ma) 1 \$5.50 \$9.95	Video Terminal A completely self-contained stand alone video terminal card. Requires only an ASCII keyboard and TV set to become a complete terminal unit. Features are: single 5V supply: XTAL controlled sync and baud rates (to 9600): complete computer and keyboard control of cursor. Parity error control and display. Accepts and generates serial ASCII plus parallel keyboard input. The 6416 is 64 char: by 16 lines with scrolling: upper and lower case (optional) and has RS-232 and 20ma loop interfaces on board. Kits include sockets and complete documentation.				

P	AR	13	PA	UC.

Lower Case option



TAKE YOUR PICK Specials these prices are NOT misprints!

Here is a chance to stock up your lab at unprecendented prices... we've got to move these out to make room for our everexpanding CompuPro[™] division. Limited quantities - first come, first served. Sorry, at these low prices we cannot include spec sheets or accept COD/telephone orders. Part numbers must include the special -S suffix or you will be charged our regular prices. Parts may be house numbered or have dual markings. This is your chance to save!

21/52 21/52

6/\$2 21/\$2

8/\$2

21/\$2 21/\$2 10/\$2

12/\$2 18/\$2

8/\$2 8/\$2 4/\$2 8/\$2 8/\$2 6/\$2

4/\$2 4/\$2 4/\$2

6/\$2

4/\$2

12/\$2

4/\$2

4/\$2 2/\$2 12/\$2

> 4/\$2 4/\$2 2/\$2

2/\$2

2/\$2

2/\$2

2/\$2

2/\$2

2/\$2

TTL	
Quad 2 input OC	
riple 3 input NAND	
to 16 line decoder/d	emi
Jund 2 input NAND (20

7403-S

7410-S

7413-S

7438-S	Quad 2 input NAND OC
7444-S	Gray to decimal decoder
7450-S	And-or-invert
7472-S	JK M-S flip flop
7493-S	4 bit binary counter
7496-S	5 bit shift register
74122-S	Retriggerable one-shot
74151-S	8 channel mux
74155-S	Dual 2/4 demux
74159-S	4 to 16 line decoder/demux OC
74161-S	Synchro 4 bit binary counter
74163-S	Synchro 4 bit binary counter
74164-S	8 bit shift register
74190-S	Up/down decade counter
74192-S	Up/down binary counter
74194-S	4 bit bidirectional shift reg
74195-S	4 bit parallel shift register
74198-S	8 bit shift register

CMOS

4012-S	Dual 4 input NAND
4020-S	14 stage counter
4023-S	Triple 3 input NAND
4044-S	Quad R-S latch
4046-S	Phase locked loop
4071-S	Quad 2 input OR
4093-S	Quad 2 in NAND Schmitt trig
4507-S	Quad EX-OR
4510-S	BCD up/down counter



SOCKET SPECIAL

Now that you've got the ICs, get some sockets at a fantastic price!

14 pin:	50/\$4.95	20 pin:	40/\$4.95
16 pin:	50/\$4.95	24 pin:	30/\$4.95
18 pin:	50/\$4.95	28 pin:	30/\$4.95
		40 pin:	20/\$4.95

74LS00	\$0.34	74LS154	2.10	
74LS01	0.34	74LS155	1.87	
74LS02	0.34	74LS157	1,57	
74LS04	0.38	74LS160	2.20	
74LS05	0.44	74LS161	2.18	
74LS08	0.34	74LS162	2.20	
74LS10	0.34	74LS163	2.18	
74LS11	0.40	74LS168	3,75	
74LS12	0.34	74LS169	3.75	
74LS14	2.20	74LS173	2.08	
74LS15	0.40	74LS174	2.05	
74LS20	0.34	74LS175	1.95	
74LS21	0.40	74LS181	3.50	
74LS22	0.40	74LS192	3.05	
74LS26	0.48	74LS195	1.87	
74LS27	0.42	74LS221	1.70	
74LS30	0.34	74LS240	2.50	
74LS32	0.46	74LS241	2.50	
74LS33	0.60	74LS244	2.50	
74LS37	0.48	74LS257	1.95	
74LS38	0.48	74LS258	2.02	
74LS42	1.56	74LS266	0.69	
74LS47	1.68	74LS273	2.91	
74LS48	1.68	74LS283	2.02	
74LS74	0.54	74LS365	0.88	
74LS75	0.82	74LS366	0.88	
74LS76	0.50	74LS367	0.88	
74LS86	0.58	74LS368	0.88	
74LS109	0.62	74LS386	0.69	
74LS123	1.70	80LS95	0.88	
74LS125	0.87	80LS96	0.88	
74LS126	0.87	80LS97	0.88	
74LS132	1.50	80LS98	0.88	
74LS136	0.69	81LS95	2.10	
74LS138	1.87	81LS96	2.10	
74LS139	1.87	81LS97	2.10	
74LS151	1.66	81LS98	2.10	



16K DYNAMIC RAMS

Lowest price ever on one of our most popular items. Expands memory in TRS-80* -I and -II, as well as machines made by Apple, Exidy, Heath H89, newer PETs, etc. Low power, speed (4 MHz). Add \$3 for dip shunts plus TRS-80* conversion instructions. Limited quantity — first come, first served. *TRS-80 is a trademark of the Tandy Corporation



Limited quantity: 32K of static memory in kit (not unkit) form. Includes all parts, sockets for all ICs, documentation, mounting bracket, etc. With solder-masked, doublesided, fully legended board for easy assembly. If you own an H8, this is your chance to obtain top-notch memory — without paying top-notch prices.

(package type: H = T099, M = minidip, D = dip, TK = T066)

201H-S	Improved 301 op amp	10/\$2
308H-S	Micropower op amp	6/\$2
703H-S	RF/IF amp	6/\$2
723D-S	Voltage regulator	6/\$2
741M-S	Compensated op amp	15/\$2
1458M-S	Dual 741	10/\$2
4558M-S	Dual 741	12/\$2
4195TK-S	Dual track 15V reg w/data	2/\$2
Charles and the second second		

TO-220 NEGATIVE VOLTAGE REGULATORS

7906-S	-6V regulator
7908-S	-8V regulator
7912-S	-12V regulator
79M15-S	-15V regulator
7918-S	-18V regulator
7924-S	-24V regulator

OTHER SEMICONDUCTORS

 General purpose silicon signal diodes 50/\$2 GT5306 NPN darlington, min gain 17000, 25V 200 mA, T092 package 100/\$8.95 100/\$7.95 NPN transistor similar 2N3904 100/\$8.95 PNP transistor similar 2N3906 4N28-S opto-coupler 6 pin minidip. MCT-2/IL-1 pinout 5/\$2 1/\$2.50 SN76477-S complex sound generator Opto-Isolator Grab Bag — 50 mixed optoisolators from a major manufacturer. Unmarked 6 and 8 lead minidips include single and dual types with diode, transistor, and darlington outputs. Test them yourself and save! Not recommended for beginners. 50/\$4



MORE TRANSISTORS AND FETS

2N2221	NPN TO-18 unmarked	7/\$1.00
2N2222	PNP TO-18 unmarked	5/\$1.00
2N2907A	PNP plastic house #	5/\$1.00
2N3055	NPN TO-3 house #	1/\$0.75
2N3904	NPN TO-105 house #	5/\$1.00
2N3906	PNP TO-105 house #	5/\$1.00
2N4124	30V/350 mW TO-92	3/\$1.00
2N4304	TO-18 plastic N-JFET gen purp	2/\$1.00
2N4400	NPN plastic house #	5/\$1.00
2N4917	PNP TO-106	5/\$1.00
2N4946	NPN TO-106	6/\$1.00
2N5227	PNP TO-92 30V	6/\$1.00
2N5306	NPN TO-92 darlington	3/\$1.00
2N5449	NPN	6/\$1.00
2N5484	RF N-JFET	3/\$1.00
D41D1	PNP TO-202 1A max	1/\$0.50
D44C4	NPN TO-220 4A/55V	1/\$0.75
D45C4	PNP TO-220 4A/55V	1/\$0.75
D45H8	PNP TO-220 10A/60V	3/\$2.00
MPS3694	NPN gen purp	4/\$1.00
FPT100	Phototransistor	1/\$0.50
FET-2	Dual N-JFET TO-18 sim 2N4416	3/\$1.00
FET-3	Dual N-JFET lo noise audio	2/\$1.00
FET-6	Gen purp dual gate MOSFET	3/\$2.00
	house #	

MA1003 CLOCK MODULE - \$14.95

Our very best clock module operates from 12V DC and includes an internal timebase accurate to 0.01%, making it ideal for mobile applications in your car, van, or boat. Blue-green flourescent readouts don't wash out during the day, and look great at night. Easy to build; just hook up power, add two time-setting switches, and you've got one of the best clock modules on the road. With application note that shows you how to get the most out of your MA1003.

Also available: clock/case combination. For \$19.95, we'll include a matching case, with mounting hardware and optical filter, along with the MA1003.

TERMS: Cal res add tax. Allow 5% for shipping; excess refunded. Orders under \$15 add \$1 handling. VISA*/ Mastercard[®] orders (\$25 min) call our 24 hour order desk at (415) 562-0636. COD OK with street address for UPS. PLEASE NOTE: TELEPHONE ORDERS AND CODS ARE NOT ALLOWED ON SPECIALS LISTED ABOVE. Sale prices good through cover month of magazine; other prices subject to change without notice.

GODBOUT ELECTRONICS Bldg. 725, Oakland Airport, CA 94614

FREE FLYER: This ad is only the tip of the iceberg; our catalog tells the rest of the story. Add 41 cents in stamps for 1st class delivery. Outside USA, include \$2 to cover postage (refundable with order). Thank you for your business!

National Semiconductor Clock Modules	MIC	ROPROCES	S	OR C	OMPONENTS	s	COMPUTER CUBET
AUTOMOTIVE/		A/BOBOA SUPPORT DEVICES -		DATA	COUISITION (CONTINUED)-		ANNE -
- INSTROMENT	DP8212	#Bit input/Output	13	ADCHICCN	8-Bit A/D Converter (SE-Ch. Multi.)	温度	Mem
APPLICATIONS:	OP(2)A	Priority Interrupt Control	5.35	DACIMUCN	30-Bit D/A Conv. Micro. Comp. (6.8%) 36-Bit D/A Conv. Micro. Comp. (6.2%)	11月 11月	798
+ In-dash autoclocks	DP\$224	Clock Generator/Driver	1.95	DACIESUCN	ID-Bit D/A Converter (0.85% LIN.)	1.0	
• After-market auto/	DPE26	Bus Driver Swittern Controller Bus Driver	149	DACINITICN	10-Bit D/A Converter (0.2% Lin.) 12-Bit D/A Converter (0.2% Lin.)	9.95	the second se
· Aircraft marine ciks	DP8238	System Controller	5.95	CD45IN	8-Channel Muttiplexer	1.19	the second se
• 12VDC oper. instru.	INSR00	1/O Expander for 48 Series	3,55	AY-5-1013	WK BAUD UART	5.25	The state of the second s
Portable/battery Powared instruments	DP8251	Prog. Comm. I/O (USART)	7.95	2101		1.49	
Easturns: Reight 0.3" green display. Internal crystal time-	DPI253 DPI255	Prog. Interval Timer Prog. Peripheral I/O (PPI)	14.95	1303	1094x1 Dynamic	.99	
hase + 0.5 sec./day accur. Auto, display brightness control	DP8257	Prog. DMA Control	15.95	2101 (8101)	10/x1 Static	1.75	
logic. Display color filterable to blue, blue-green, green &	DP8259 DP8275	Prog. CRT Controller	利润	211.02	1024x1 Static	1.95	
yellow. Complete - just add switches and lens.	DP8279	Prog. Keyboard/Disblay Interface	19,95	2111 (8111) 2112	25614 Static 25614 Static MOS	4.95	COMPLETED ODT MONITOD & ACCESSORY CASE
MA1003 Module	DP600C OP6002	Octal Bus Receiver System Timing Element	6.95	2114	1024#4 Static 450nz	5.95	COMPUTER CRT MONITOR & ACCESSORY CASE
	DP9304	8-Bit Bi-Directional Receiver	1.95	7134L 2134-3	1024x4 Static 490hs Low Power 1024x4 Static 300hs	2.49	· Painted to match Apple II & III (Lt. beige, textured finish
MA1023 .7" Low Cost Digital LED Clock Module 8.95	DP0307	BBit Bi-Directional Receiver	195	211413	1024x4 Static 30ns Low Power	7.95	 Smoke colored acrylic front cover (removable)
MA1026 .7" Dig. LED Alarm Clock/Thermometer 18.95		OVERAN SURPORT DEVICE	1000	2117 645421473	epident Crynamic Stone (house markett) epidet Fast 70ns	2.8	Built-in shell holds CH1 and allows room for 2 Apple disk drives below shelf
MA5036 .3" Low Cost Digital LED Clock/Timer 6.95	MC680	MPU	14.95	Sint	26x4 Static	7.86	. Three 2%" holes provided in bottom of case for addition
MA1002.5 LED Display Dig. Clock & Aformer 8.55	MC6803CIF	MPU with Clock and RAM	3.5	MMS82	JKAL Dynamic Pury Decides	-	· of fan it needed.
A Makanal Comissendualas	MCBBIGAPT	Peripheral Inter, Astart (MCM20)	1.45	NAM5280/2307	40641 Dynamic	4.85	 Fan hole positioned above Apple motherboard location. Hookup cables can be run through other 2 holes.
a National Semiconouctor	MORES	Priority Interrupt Controller	315	MMM528LI-224234	BK Dyn. 20ms (lower is of MMS26/)	1.5	· Case accommodates most B&W and Color uncased CRT
	MCGERLE	Asynchronous Comm. Adapter	6.15	1485	Me4 Static	1.15	· monitors made by Motorola, Ball Bros., Zenith, Sanyo,
	MCREE	Synchronous Serial Data Adapter	6.95	TMSA04445NL	AK Static	14.55	 Panasonic, Hitachi, etc. or any monitor that will fit into 10.3/P'H v 14V'W v 13V'D mane.
	14C6960	9400pts Digital MODEM	12.55	TMS406	SDRx4 Static	14.95	• Size: 15" x 15" x 15" O.D., 14%"H x 14%"W x 13%"I.D.
Ville.	MCBBBA	Quad 3-State Bus. Trans. (MC#T#)	2.25		- PROMS/EPROMS		Weight: approximately 12 lbs.
Y	M	ICROPROCESSOR CHIPS-		1702A	IK EPROM	5.95	CRT monitor fan and disk drives not included.
MM5290J-2 (MK4116/UPD416) \$6.95 each	Z80 (780C)	CPU (MHC3880N) (2MHz)	11.95	TM52716	16K EPROM (-5V, +5V, +11V)	18.95	011054 00005
16K DYNAMIC RAM (150NS)	280A (780-1)	CPU (MK3880N-4) (4MHz)	15.95	27561mtel(2536)7#	IK EPROM (Single +5V)	17.95	CUBE-1
(8 EACH \$49.95) (100 EACH \$550.00/lot)	2650	MPU	16.95	2758	BK EPROM (450ns) (Single +5V)	1,95	
MM52981-3A \$3.25 each	IDM2901ADC	CPU-4-Bit Slice (Com, Temp, Grade)	19,95	5203	294 PROM (Open Collector)	14,95	TDC-80
RK DYNAMIC RAM (LOW HALF OF MM5290J) 200NS	INS8035N-6	MPU-a-Bit (6MHz)	16.95	625115	40% Bipolar PROM	19.95	113-00
(8 EACH \$23.95) (100 EACH \$250.00/lot)	1NS8039N-6	CPU-Sel. Chip 8-Bit (128 bytes RAM) CDU UNE Bytes RAM)	19.95	825123(745288)	12x8 Tri-State Bipolar PROM	4.95	16K Conversion Kit
MM2114 2 \$5.95 each	INS8070N	CPU-64 Bytes RAM	24.95	ecates	POM'S		
AK STATIC RAM (200NS)	PROES	CPU CPU-Ik-Bit	19.55	2513(2140)	Character Generator (Upper Case)	5.95	Expand your 4K TRS-80 System to 16K.
(8 FACH \$43 95) (100 FACH \$450.00/lot)	TMS9900JL	MPU-3-Bit	49.95	2513(3021)	Character Generator (Lower Cale)	8.95	Kit comes complete with: • 9 each MME200.2 (UPDA16) (1EV Ducamic Pare)
	-	-SHIFT REGISTERS		AMM5250N	298-Bit Rass Only Memory	1.85	(250NS or less)
MM2114L-3 \$6.25 each	MMSODH	Dual 2-Bit Dynamic	-50	-NMO	READ ONLY MEMORIES		Documentation for conversion
4K STATIC HAM (LOW POWER 300NS)	MMS20H	Dual SP-Bit Dynamic	-50	MCMETUP	Liketer ASCII Shifted w/Greek	13.50	TDC 16V CAO OF
18 EACH 344.951 (100 EACH 3475.00/101)	AMMEDIH	Deal 54 Bit Accumulator	.50	MCMMETADP	Literar Math Symbol & Pictures	12.50	IN3-10N
EDDOM English Lang	MMSAE	26-64 Dynamic	15	11101	IOPROCESSOR MANUALS		
EPROM Erasing Lamp	MMSEISH	M0/513-Bit Dynamic		16-240	User Manual	2.50	JE610 ASCII
	MM504W	Octal M-Bit	3.95	M-CDPIND	User Manual	7.50	
	2504 V (1404.A)	2004 Bit Dynamic	1.35	10-254	SPECIAL EUNCTION	a	Encoded Keyboard Kit
	2518N	Here 32-Bit Static	4.95	DS005CN	Dual MOS Clock Driver (IM2)	1.50	
	2574V	SI2-Bit Dynamic	.99	DS006CN	Dual MOS Clock Driver (SM2)	1,95	m
	2525 V	1034-Bit Dynamic Dual 25-Bit State	2.95	1N52651N	Communication Chip	19.95	
	2528	Dual 20-Bit Static	4.00	MMSE167N	Microprocessor Real Time Clock	8.95	
	2529V	Dual 240-Bit Static	4.00	COP402N	Microcontroller with 64-Digit RAM	6.95	
	3MIPC	Fito (Dual 80)	6.95	00000000	and Direct LED Drive	1.44	
Erases 2708, 2716, 1702A, 5203Q, 5204Q, etc.	CALCUTOR .	-DATA ACQUISITION	10110	COMUZININ	A Direct LED Drive w/N Buss Int.	1.40	
Erases up to 4 chips within 20 minutes.	AF100-ICN	Universal Active Filter 2.5%	5.95	COP470N	12-Seg. VAC Fluor. Driver (20-pin pkg.)	2.25	
Maintains constant exposure distance of one inch.	AF23-ICJ	Touch Tone Low Pass Filter	19.95	TELE	PHONE/KEYBOARD CHIPS -	-	most any computer system. The kit comes complete
Special conductive foam liner eliminates static build-up.	LMSEAH	Super Gain Op Amp	1.00	AY-5-8100	Push Button Telephone Dialer Bapertory Dialer	34.35	with an industrial grade keyboard switch assembly
Compact - only 7.5/9" > 2.7/9" > 2"	LMEHZ	Constant Currant Source	1.30	AY-54900	CMOS Clock Generator	4.35	(62-keys), IC's, sockets, connector, electronic compo-
Complete with holding tray for 4 chins	LMIB2	JFET Input Op Amp	1.32	AY-S-ZIM	Keyboard Encoder (NE keys)	11.55	nents and a double-sided printed wiring board. The
Complete min norming way for a cript	LFIMN	Sample & Hold Amplifiers	1.95	74C522	Rayboard Encoder (15 keys)	5,45	\$ 10 mA for operation. Features 50 keys generate the
IVS-11F \$79.50	LM3991	Tarrig, Comp. Prec. Ref. (300m/C1)	4.5	74C803	Keyboard Encoder (25 keys)	5.75	126 characters, upper and lower case ASCII set. Fully



✓ Reader Service—see page 226

ASSOCIATED RADIO 913-381-5900 8012 CONSER BOX 4327

OVERLAND PARK, KANSAS 66204



CALL US WITH YOUR REQUIREMENTS AMERICA'S NO. 1 Real Amateur Radio Store



"ASSOCIATED" IS THE BEST PLACE TO BUY. *NOTE: WE BUY EQUIPMENT, AS WELL AS SELL AND TRADE.





NOTE: SEND \$1.00 FOR OUR CURRENT CATALOG OF NEW AND RECONDITIONED EQUIPMENT.

*ALSO WE PERIODICALLY PUBLISH A LIST OF UNSERV-ICED EQUIPMENT AT GREAT SAVINGS. A BONANZA FOR THE EXPERIENCED OPERATOR. TO OBTAIN THE NEXT UNSERVICED BARGAIN LIST, SEND A SELF ADDRESSED STAMPED ENVELOPE.

welcome here

Radio Bookshop

-FOR THE NOVICE-

NEW, UPDATED EDITIONS OF OUR FAMOUS NOVICE CLASS STUDY GUIDE AND NOVICE THEORY TAPES.

• NOVICE STUDY GUIDE—SG7357—Here is a completely new study guide and reference book for the potential ham. This is not a question/answer memorization course. Electronic and radio fundamentals are presented and explained in an easy-to-understand fashion, preparing the beginner for the Novice exam. Includes the latest FCC amateur regulations, as well as application forms. Easily the best path into the exciting world of ham radio! \$4.95.*

• NOVICE THEORY TAPES—CT7300—Startling Learning Breakthrough. You'll be astounded at how really simple the theory is when you hear it explained on these tapes. Three tapes of theory and one of questions and answers from the latest Novice exams give you the edge you need to breeze through your exam. 73 is interested in helping get more amateurs, so we're giving you the complete set of our tapes for the incredibly low price of ONLY \$15.95.*



Scientists have proven that you learn faster by listening than by reading because you can play a cassette tape over and over in your spare time—even while you're driving! You get more and more info each time you hear it. You can't progress without solid fundamentals. These four hour-long tapes give you all the basics you'll need to pass the Novice exam easily. You'll have an understanding of the basics which will be invaluable to you for the rest of your life! Can you afford to take your Novice exam without first listening to these tapes? Set of 4—\$15.95.*

SPECIAL OFFER! BOTH NOVICE CLASS STUDY GUIDE AND NOVICE THEORY TAPES \$20.00 ORDER NP7300.

HANDBOOKS FOR THE HAMSHACK



• WORLD REPEATER ATLAS—BK7315—Completely updated, over 230 pages of repeater listings are indexed by location and frequency. More than 50 maps pinpoint 2000 repeater locations throughout the USA. Foreign listings include Europe, the Middle East, South American and Africa. \$4.95.

• THE PRACTICAL HANDBOOK OF AMATEUR RADIO FM REPEATERS—BK1185—by Bill Pasternak WA6ITF (author of 73 Magazine's monthly column "Looking West") This is the book for the VHF/UHF FMer, compiled from material submitted by over a hundred individuals, clubs, organizations and equipment manufacturers. A "must have" for your ham shack shelf. \$9.95.

• WORLD RADIO TV HANDBOOK 1981, 35TH EDITION — BK1184 — This book is the bible of international broadcasters, providing the only authoritative source of exact information about broadcasting and TV stations world wide. This 1981 edition is completely revised, giving comprehensive coverage of short, medium and long wave, 560 pages of vital aspects of world listening. \$16.50.



OTHER STUDY GUIDES

• ADVANCED CLASS LICENSE STUDY GUIDE—SG1081—Ready to upgrade your license? To prevent retaking the FCC theory exam, you need the 73 Advanced theory guide. SSB, antenna theory, transmitters, and electronics measuring techniques are covered in detail in this easy-to-follow study guide. Special modes and techniques, such as RTTY, are also treated. An engineering degree is *not* necessary to master the Advanced theory—try this book before visiting the examiner's office! \$6.95.* (Published by TAB Books previous to recent changes in FCC exam material.)

• EXTRA CLASS LICENSE STUDY GUIDE—SG1080—Before going for your 1 × 2 call, it pays to be a master of the Extra class electronics theory. This study guide is the logical extension of the 73 theory course. All the theory necessary to pass the exam is presented. Antennas, transmission lines, swr are discussed, as well as noise, propagation, and specialized communication techniques. This book is not a classroom lecture or memorization guide, but rather a logical presentation of the material that must be *understood* before attempting the Extra exam. Save yourself a return trip to the FCC and try the 73 method first! \$5.95.*

• UNDERSTANDING AND PROGRAMMING MICROCOMPUTERS—BK7382—A valuable addition to your computing library. This two part text includes the best articles that have appeared in 73 and Kilobaud Microcomputing magazines on the hardware and software aspects of microcomputing. Well known authors and well structured text helps the reader get involved. \$10.95*

• 40 COMPUTER GAMES FROM KILOBAUD MICROCOMPUTING—BK7381—Forty games in all in nine different categories. Games for large and small systems, and even a section on calculator games. Many versions of BASIC used and a wide variety of systems represented. A must for the serious computer gamesman. \$7.95*

• SOME OF THE BEST FROM KILOBAUD/MICROCOMPUTING—BK7311—A collection of the best articles that have recently appeared in Kilobaud/MICROCOMPUTING. Included is material on the TRS-80 and PET systems, CP/M, the 8080/8085/Z80 chips, the ASR-33 terminal. Data base management, word processing, text editors and file structures are covered too. Programming techniques and hardcore hardware construction projects for modems, high speed cassette interfaces and TVTs are also included in this large format, 200 plus page edition. \$10.95.*

• HOBBY COMPUTERS ARE HERE!—BK7322—If you want to come up to speed on how computers work...hardware and software...this is an excellent book. It starts with fundamentals and explains the circuits, and the basics of programming, along with a couple of TVT construction projects, ASCII-Baudot, etc. This book has the highest recommendations as a teaching aid. \$4.95.*

• THE NEW HOBBY COMPUTERS—BK7340—This book takes it from where "HOBBY COMPUTERS ARE HERE!" leaves off, with chapters on Large Scale Integration, how to choose a microprocessor chip, an introduction to programming, low cost I/O for a computer, computer arithmetic, checking memory boards ... and much, much more! Don't miss this tremendous value! Only \$4.95.*

*Use the order card in the back of this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop • Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. *Add \$1.00 handling charge. Note: Prices subject to change on books not published by 73 Magazine. Questions regarding your order? Please write to Customer Service at the above address. Please allow 4–6 weeks for delivery.

RADIO BOOKSHOP =73 TECHNICAL LIBRARY

• BEHIND THE DIAL—BK7307—By Bob Grove. Get more fun out of shortwave listening with this interesting guide to receivers, antennas, frequencies and interference. \$4.95.*

•THE CHALLENGE OF 160—BK7309—is the newest book in the 73 technical library, dedicated to 160 meter operating. Si Dunn provides all necessary information to get started on this unique band. The all-important antenna and ground systems are described in detail. The introduction contains interesting photos of Stew Perry's (the King of 160) shack. This reference is a must for new and experienced "Top Band" operators. Price: \$4.95.*

• IC OP-AMP COOKBOOK—BK1028—by Walter G. Jung. Covers not only the basic theory of the IC op amp in great detail, but also includes over 250 practical circuit applications, liberally illustrated. 592 pages, $5\frac{1}{2} \times 8\frac{1}{2}$, softbound. \$12.95.*



• THE POWER SUPPLY HANDBOOK — BK7305 — Need a power supply for a gadget you're building? In the POWER SUPPLY HAND-BOOK there are dozens ready-to-build, plus detailed steps for designing your own. There are circuits and parts lists for all kinds of supplies, ranging from simple DC types to highly stable regulated versions. If you need a circuit to convert a DC voltage to a higher or lower voltage, turn DC into AC, or AC to DC — then this is the book you need. With more than 400 pages, you should be able to find just the circuit you need. Without a doubt one of the best power supply source books available, compiled by the editors of 73. \$9.95.*



• WEATHER SATELLITE HANDBOOK—BK7370—Simple equipment and methods for getting good pictures from the weather satellite. Antennas, receivers, monitors, facsimile you can build, tracking, automatic control (you don't even have to be home). Dr. Taggart WB8DQT.\$4.95.*

• THE NEW RTTY HANDBOOK—BK7347—is a new edition and the only up-to-date RTTY book available. The state of the art has been changing radically and has made all previous RTTY books obsolete. It has the latest circuits, great for the newcomer and expert alike. \$5.95.*

• PROPAGATION WIZARD'S HANDBOOK—BK7302—by J. H. Nelson. When sunspots riddled the worldwide communications networks of the 1940's, John Henry Nelson looked to the planets for an answer. The result was a theory of propagation forecasting based upon interplanetary alignment that made the author the most reliable forecaster in America today. The book provides an enlightened look at communications past, present, and future, as well as teaching the art of propagation forecasting. \$6.95.*

• SSB ... THE MISUNDERSTOOD MODE—BK7351—by James B. Wilson. Single Sideband Transmission ... thousands of us use it every day, yet it remains one of the least understood facets of amateur radio. J. B. Wilson presents several methods of sideband generation, amply illustrated with charts and schematics, which will enable the ambitious reader to construct his own sideband generator. A must for the technically-serious ham. \$5.50.*

• MASTER HANDBOOK OF HAM RADIO CIRCUITS – BK1033 – This is an encyclopedia of amateur radio circuits, gleaned from past issues of 73 Magazine and carefully selected according to application. You'll find many you've never seen before, some new twists on the tried and true, and several that have been long forgotten but are well worth remembering. Where your interest ranges from ragchewing to EME, from CW to slow-scan TV, from DX to county nets, this handbook will be a welcome addition to your shack. \$8.95.*





• OWNER REPAIR OF RADIO EQUIPMENT – BK7310 – Frank Glass K6RQ shares over 40 years of operating, servicing, and design experience in this book which ranges from the elementary to the highly technical written for the top engineers in the field. It is written in narrative style on the subjects of electronic servicing, how components work, and how they are combined to provide communication equipment. This book will help you understand the concepts required to service your own station equipment. \$7.95.*

•TOOLS & TECHNIQUES FOR ELECTRONICS – BK7348 – is an easy-to-understand book written for the beginning kit builder as well as the experienced hobbyist. It has numerous pictures and descriptions of the safe and correct ways to use basic and specialized tools for electronic projects as well as specialized metal working tools and the chemical aids which are used in repair shops. \$4.95*

•THE CONTEST COOKBOOK – BK7308 – reveals the secrets of the contest winners (Domestic, DX and specialty contests), complete with photos and diagrams of equipment used by the top scorers. Find out how to make 150 contacts in one hour. \$5.95*

*Use the order card in the back of this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop • Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. *Add \$1.00 handling charge. Note: Prices subject to change on books not published by 73 Magazine. Questions regarding your order? Please write to Customer Service at the above address. Please allow 4-6 weeks for delivery.

RAdio Bookshop

TEST EQUIPMENT

. RF AND DIGITAL TEST EQUIPMENT YOU CAN BUILD-BK1044-Rf burst, function, square wave generators, variable length pulse generators-100 kHz marker, i-f and rf sweep generators, audio osc, af/rf signal injector, 146 MHz synthesizer, digital readouts for counters, several counters, prescaler, microwave meter, etc. 252 pages. \$5.95.*

• VOL. I COMPONENT TESTERS-LB7359- ... how to build transistor testers (8), diode testers (3), IC testers (3), voltmeters and VTVMs (9), ohmmeters (8 different kinds), inductance (3), capacity (9), Q measurement, crystal checking (6), temperature (2), aural meters for the blind (3) and all sorts of miscellaneous data on meters . . . using them, making them more versatile, making standards. Invaluable book. \$4.95.*

• VOL. II AUDIO FREQUENCY TESTERS-LB7360-... jam packed with all kinds of audio frequency test equipment. If you're into SSB, RTTY, SSTV, etc., this book is a must for you . . . a good book for hi-fi addicts and experimenters, too! \$4.95.*



• VOL. III RADIO FREQUENCY TESTERS-LB7361-Radio frequency waves, the common denominator of Amateur Radio. Such items as SWR, antenna impedance, line impedance, rf output and field strength; detailed instructions on testing these items includes sections on signal generators, crystal calibrators, grid dip oscillators, noise generators, dummy loads and much more. \$4.95.*

• VOL. IV IC TEST EQUIPMENT-LB7362-Become a troubleshooting wizard! In this fourth volume of the 73 TEST EQUIP-MENT LIBRARY are 42 home construction projects for building test equipment to work with your ham station and in servicing digital equipment. Plus a cumulative index for all four volumes of the 73 TEST EQUIPMENT LIBRARY. \$4.95.*

THE WELL-EQUIPPED HAM SHACK=



NDERS

• THE MAGIC OF HAM RADIO - BK7312 - by Jerrold Swank, W8HXR begins with a brief history of amateur radio and of Jerry's involvement in it. Part 2 details many of ham radio's heroic moments. Hamdom's close ties with the continent of Antarctica are the subject of Part 3. In Part 4 the strange and humorous sides of ham life get their due. And what of the future? Part 5 peers into the crystal ball. \$4.95.*

• A GUIDE TO HAM RADIO - BK7321 - by Larry Kahaner WB2NEL. What's Amateur Radio all about? You can learn the basics of this fascinating hobby with this excellent beginner's guide. It answers the most frequently asked questions in an easy-going manner, and it shows the best way to go about getting an FCC license. A Guide to Ham Radio is an ideal introduction to a hobby enjoyed by people around the world. \$4.95.*



. HOW TO BUILD A MICROCOMPUTER - AND REALLY **UNDERSTAND IT** – BK7325 – by Sam Creason. The electronics hobbyist who wants to build his own microcomputer system now has a practical "How-To" guidebook. This book is a combination technical manual and programming guide that takes the hobbyist step-by-step through the design, construction, testing and debugging of a complete microcomputer system. Must reading for anyone desiring a true understanding of small computer systems. \$9.95.*

• LIBRARY SHELF BOXES - These sturdy white, corrugated, dirt-resistant boxes each hold a full year of 73, Kilobaud Microcomputing or 80 Microcomputing. With your order, request self-sticking labels for any of the following: 73, Kilobaud Microcomputing, 80 Microcomputing, CQ, QST, Ham Radio, Personal Computing, Radio Electronics, Interface Age, and Byte. Order 1-BX1000 - for \$2.00*; order 2-7 - BX2002 - for \$1.50 each*; order 8 or more - BX1002 - for \$1.25 each*.



Preserve and protect your collection for a lifetime! Order these handsome red binders MACAZINE with gold lettering. \$7.50 for 1, 3 for \$21.75, 6 for \$42.00. (Postpaid within USA, please add \$2.50 per order outside USA.) Check or money orders only, no phone or C.O.D. orders. 73 Binders, P.O. Box 5120, Philadelphia, PA 19141.

*Use the order card in the back of this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop • Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. *Add \$1.00 handling charge. Note: Prices subject to change on books not published by 73 Magazine. Questions regarding your order? Please write to Customer Service at the above address. Please allow 4-6 weeks for delivery.

Radio Bookshop

 73 DIPOLE AND LONG-WIRE ANTENNAS—BK1016—by Edward M. Noll W3FQJ. This is the first collection of virtually every type of wire antenna used by amateurs. Includes dimensions, configurations, and detailed construction data for 73 different antenna types. Appendices describe the construction of noise bridges, line tuners, and data on measuring resonant frequency, velocity factor, and swr. \$5.50.*



PRACTICAL ANTENNAS FOR THE RADIO AMATEUR – BK1015

 A manual describing how to equip a ham station with a suitable antenna. A wide range of antenna topics, systems, and accessories are presented giving the reader some food for thought and practical data for construction. Designed to aid the experienced ham and novice as well. Only \$9.95.*

•TTL COOKBOOK – BK1063 – by Donald Lancaster. Explains what TTL is, how it works, and how to use it. Discusses practical applications, such as a digital counter and display system, events counter, electronic stopwatch, digital voltmeter and a digital tachometer. \$9.50.

• CMOS COOKBOOK – BK1011 – by Don Lancaster. Details the application of CMOS, the low power logic family suitable for most applications presently dominated by TTL. Required reading for every serious digital experimenter! \$10.50.*

• THE GIANT BOOK OF AMATEUR RADIO ANTENNAS—With the GIANT Book of Amateur Radio Antennas—BK1104—by your side, antennas will become the least of your worries. Over 450 pages of design ideas, theory and reference data make this book live up to its title. The 7 chapters cover everything from basic antenna theory through designs for DIY accessories, as well as dozens of antenna designs. Whether planning to build or buy, design or admire, test or enjoy a ham antenna—this is the book for you. From the editors of 73; published by Tab Books. Hardcover \$12.95.*

•73 VERTICAL, BEAM AND TRIANGLE ANTENNAS—BK1069 by Edward M. Noll W3FQJ. Describes 73 different antennas for amateurs. Each design is the result of the author's own experiments covering the construction of noise bridges and antenna line tuners, as well as methods for measuring resonant frequency, velocity factor, and standing-wave ratios. 160 pages. \$5.50.*

 VHF ANTENNA HANDBOOK—BK7368—The NEW VHF Antenna Handbook details the theory, design and construction of hundreds of different VHF and UHF antennas ... A practical book written for the average amateur who takes joy in building, not full of complex formulas for the design engineer. Packed with fabulous antenna projects you can build. \$5.95.*



• TVT COOKBOOK—BK1064—by Don Lancaster. Describes the use of a standard television receiver as a microprocessor CRT terminal. Explains and describes character generation, cursor control and interface information in typical, easy-to-understand Lancaster style. \$9.95.*

• RTL COOKBOOK—BK1059—by Donald Lancaster. Explains the how and why of RTL (Resistor-Transistor Logic) and gives design information that can be put to practical use. Gives a multitude of digital applications ranging from the basic switch to the sophisticated counter. 240 pages; \$6.50.*



•SLOW SCAN TELEVISION TAPE—CT7350—Prize-winning programs from the 73 SSTV contest. Excellent for Demo! \$5.95.*





"GENESIS"

5 WPM—CT7305—This is the beginning tape for people who do not know the code at all. It takes them through the 26 letters, 10 numbers and necessary punctuation, complete with practice every step of the way using the newest blitz teaching techniques. It is almost miraculous! In one hour many people—including kids of ten —are able to master the code. The ease of learning gives confidence to beginners who might otherwise drop out.

"THE STICKLER"

6+ WPM—CT7306—This is the practice tape for the Novice and Technician licenses. It is made up of one solid hour of code, sent at the official FCC standard (no other tape we've heard uses these standards, so many people flunk the code when they are suddenly—under pressure —faced with characters sent at 13 wpm and spaced for 5 wpm). This tape is not memorizable, unlike the zany 5 wpm tape, since the code groups are entirely random characters sent in groups of five.



"BACK BREAKER"

13 + WPM—CT7313—Code groups again, at a brisk 13 per so you will be at ease when you sit down in front of the steely-eyed government inspector and he starts sending you plain language at only 13 per. You need this extra margin to overcome the panic which is universal in the test situations. When you've spent your money and time to take the test, you'll thank heavens you had this back-breaking tape.

"COURAGEOUS"

20 + WPM—CT7320—Code is what gets you when you go for the Extra class license. It is so embarrassing to panic out just because you didn't prepare yourself with this tape. Though this is only one word faster, the code groups are so difficult that you'll almost fall asleep copying the FCC stuff by comparison. Users report that they can't believe how easy 20 per really is with this fantastic one hour tape.

"OUTRAGEOUS"

25 + WPM—CT7325—This is the tape for that small group of overachieving hams who wouldn't be content to simply satisfy the code requirements of the Extra Class license. It's the toughest tape we've got and we keep a permanent file of hams who have mastered it. Let us know when you're up to speed and we'll inscribe your name in 73's CW "Hall of Fame."



*Use the order card in the back of this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop
Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. *Add \$1.00 handling charge. Note: Prices subject to change on books not published by 73 Magazine. Questions regarding your order? Please write to Customer Service at the above address. Please allow 4–6 weeks for delivery.

DIRECTORY

San Jose CA

Bay area's newest Amateur Radio store. New & used Amateur Radio sales & service. We feature Kenwood, ICOM, KDK, Yaesu, Ten-Tec, VHF Engineering & many more. Shaver Radio, Inc., 1378 So. Bascom Ave., San Jose CA 95128, 998-1103.

San Leandro CA

Specializing in Amateur Radio Test Guides. We publish the most accurate F.C.C. exam preparation material in the country according to letters on file from hams nationwide. General, Advanced, and Extra Class manuals available. Bash Educational Services, 519 Estudillo Avenue, P.O. Box 2115, San Leandro, CA 94577, 352-5420.

Denver CO

Experimenter's paradise! Electronic and mechanical components for computer people, audio people, hams, robot builders, experimenters. Open six days a week. Gateway Electronics Corp., 2839 W. 44th Ave., Denver CO 80211, 458-5444.

Uncasville CT

Cushcraft, Bencher, Hy-Gain, Telex, Barker & Williamson, Nye-Viking, Hustler, MFJ, Callbook, Murch, Unadilla, OK, Saxton, ARRL Books, Used equipment, Electronic parts and accessories, free catalog. Donovan Electronics, Inc., 2510 Norwich, New London Tpke, Uncasville CT 06382, 848-3434.

St. Louis MO

Experimenter's paradise! Electronic and mechanical components for computer people, audio people, hams, robot builders, experimenters. Open six days a week. Gateway Electronics Corp., 8123-25 Page Blvd., St. Louis MO 63130, 427-6116.

Svracuse-Rome-Utica NY

Featuring: Kenwood, Yaesu, ICOM, Drake, Ten-Tec, Swan, DenTron, Alpha, Robot, MFJ, Tempo, Astron, KLM, Hy Gain, Mosley, Larsen, Cushcraft, Hustler, Mini Products. You won't be disappointed with equipment/service. Radio World, Oneida County Airport-Terminal Building, Oriskany NY 13424, 337 - 0203.

Phila. PA/Camden NJ

Waveguide & coaxial microwave components & equipment. Laboratory grade test instruments, power supplies. Buy, sell & trade all popular makes, HP, GR, FXR, ESI, Sorensen, Singer, etc. Lectronic Research Labs., 1423 Ferry Ave., Camden NJ 08104, 541-4200.

Columbus OH

All major brands featured in the biggest and best ham store for miles around. Come in and twist the knobs before you buy. Universal Amateur Radio, Inc., 1280 Aida Dr., Reynoldsburg (Columbus) OH 43068, 866-4267.

PROPAGATION

J. H. Nelson 4 Plymouth Dr. Whiting NJ 08759

EASTERN UNITED STATES TO:

GMT	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14A	34	7	7	7	7	7	7	14	14A	21A	21A
ARGENTINA	14	7A	7	78	78	7	14A	21	21A	21A	21A	21A
AUSTRALIA	21	14	78	78	78	78	78	148	21	21	21A	21A
CANAL ZONE	14	7	7	7	7	7	14	21A	21A	21A	21A	21
ENGLAND	7	7	7	7	7	7	14	21A	21A	14A	54	7
HAWAII	21A	14	78	7	7	7	7	78	34	21A	21A	21A
INDIA	7	7	78	78	78	7B	14	14A	14	78	78	7
JAPAN	14A	148	78	78	7	7	7	78	78	78	14B	14
MEXICO	14A	7A	7	7	7	7	7	14A	21A	21A	21A	21
PHILIPPINES	14A	148	78	78	78	78	78	148	148	148	148	14
PUERTO RICO	54	7	7	7	7	2	14	21A	21A	21A	21	21
SOUTH AFRICA	14	78	7	78	78	14	21A	21A	21A	21A	21A	14A
U. S. S. R.	7	7	7	7	7	78	14	21A	21	78	78	7
WEST COAST	21	14	7	7	7	7	7	14	21A	21A	21A	21A
CENTR	A	L	UN	III	E	D	ST	A	TE	S	т):
ALASKA	21	14	7	7	7	7	7	7	14	14A	21A	21A
ARGENTINA	21	-14	7	78	7日	7	14	21	21A	21A	21A	21A
AUSTRALIA	21A	34	78	78	78	78	78	78	14	21	21A	21A
CANAL ZONE	14	7A	7	7	7	7	7A	21A	21A	21A	21A	21A
ENGLAND	7	7	7	7	7	7	78	14A	21A	14A	14	78
HAWAII	21A	14	7	7	7	7	7	7	14	21A	21A	21A
INDIA	78	78	78	78	78	78	78	78	14	78	78	78
JAPAN	21A	14	78	78	7	7	7	7	78	78	148	21
MEXICO	14	7	7	7	7	7	7	14	21	21A	21A	21
PHILIPPINES	21A	14	78	78	7B	78	78	7	148	14B	148	14
PUERTO RICO	14	7	7	7	7	7	7A	21	21A	21A	21	21
SOUTH AFRICA	14	78	7	78	7B	78	14	21A	21A	21A	21A	14A
U. S. S. R.	78	7	7	7	7	76	78	14A	14A	78	78	78
WESTE	RN	J	UN	JIT	E)	ST	A	TE:	S	тс):
ALASKA	21A	14	7	7	7	7	7	3A	7A	14	21	21A
ARGENTINA	21A.	14	7A	78	7B	7	78	14A	21A	21A	21A	21A
AUSTRALIA	21A	21	14	7	78	78	7B	78	14	21	21A	21A
CANAL ZONE	21	14	7	7	7	7	7	14A	21A	21A	21A	21A
ENGLAND	78	7	7	7	7	7	78	14B	21A	14A	148	7B
HAWAII	21A	21	14	7A	7	7	7	7	14	21A	21A	21A
INDIA	78	14	78	7B	79	78	78	7B	148	7B	78	78
JAPAN	21A	14A	148	78	7	7	7	7	7	7B	14B	21A
MEXICO	21	14	7	7	7	7	7	7A	21	21A	21A	21A
PHILIPPINES	21A	14A	148	7B	78	7B	78	7	148	14B	148	14
PUERTO RICO	21	14	7	7	7	7	7	14A	21A	21A	21A	21
SOUTH AFRICA	21	14	7	78	7B	78	78	14	21A	21A	21A	144
U. S. S. R.	78	7	7	7	7B	78	78	78	14	78	78	78
EAST COAST	21	14	7	7	7	7	7	14	21A	21A	21A	21A
and the second se		_	_		-					and the second division of the second divisio		Statement Street

Columbus GA KENWOOD-YAESU-DRAKE

The world's most fantastic amateur showroom! You gotta see it to believe it! Radio Wholesale, 2012 Auburn Avenue, Columbus GA 31906, 561-7000.

Boise ID

Adzen, Amidon, Ameco, ARRL, B&W, Callbook, Collins, CushCraft, Dentron, Hustler, ICOM, Jim-Pak, KDK, MFJ, NPC, Nye, Sams, SST, Swan, Ten-Tec, Wanzer, Wilson. Custom Electronics, 1209 Broadway, Boise ID 83706, Bob W7SC 344-5084.

Preston ID

Ross WB7BYZ, has the Largest Stock of Amateur Gear in the Intermountain West and the Best Prices. Call me for all your ham needs. Ross Distributing, 78 So. State, Preston ID 83263, 852-0830.

Terre Haute IN

Your ham headquarters located in the heart of the midwest. Hoosier Electronics, Inc., 43B Meadows Shopping Center, P.O. Box 2001, Terre Haute IN 47802, 238-1456.

Littleton MA

The ham store of N.E. you can rely on. Kenwood, ICOM, Wilson, Yaesu, DenTron, KLM amps, B&W switches & wattmeters, Whistler radar detectors, Bearcat, Regency, antennas by Larsen, Wilson, Hustler, GAM. TEL-COM Inc. Communications & Electronics, 675 Great Rd., Rt. 119, Littleton MA 01460, 486-3040.

Laurel MD

Kenwood, Drake, ICOM, Ten-Tec, Swan, Dentron, Tempo and many ham accessories. Also computers by Apple and Exidy. The Comm Center, Inc., Laurel Plaza-Rt. 198, Laurel MD 20810, 792-0600.

Houston TX

Experimenter's paradise! Electronic and mechanical components for computer people, audio people, hams, robot builders, experimenters. Open six days a week. Gateway Electronics Inc., 8932 Clarkcrest, Houston TX 77063, 978-6575.

San Antonio TX

Complete 2 way service shop. Call Dee, W5FSP. Selling Antenna Specialists, Avanti, Azden, Bird, Hy-gain, Standard communications, Genave, Henry, CushCraft, Dielectric, Hustler, ICOM, MFJ, Nye, Shure, Swan, Tem-po, Ten-Tec and others. Appliance & Equipment Co., Inc., 2317 Vance Jackson Road, San Antonio TX 78213, 734-7793.

DEALERS

Your company name and message can contain up to 25 words for as little as \$150 yearly (prepaid), or \$15 per month (prepaid quarterly). No mention of mail-order business or area code permitted. Directory text and payment must reach us 60 days in advance of publication. For example, advertising for the February issue must be in our hands by December 1st. Mail to 73 Magazine, Peterborough NH 03458. ATTN: Nancy Ciampa.

- = Next higher frequency may also be useful
- = Difficult circuit this period В

= Fair G = Good = Poor

SF = Chance of solar flares

december



List of Advertisers

*Please contact these advertisers directly.

To receive full information from our advertisers please complete the following postage-paid card.

R.S. No.	Page	R.S. No.	Page R.S	No. Page	R.S.	No. Page
* AEA/Advanced Elect. Appl	lica., Inc.	386 Electro-Compone	nts Div 173 385	MELCO Enterprises	367	Slep Electronics
		323 Fox-Tando Corp.		Macrotronics	484	Sony
3 AED Electronics		27 G.I.S.M.O		Madison Electronics	360	Soundpower 163
362 A.P. Systems		25 Germantown Am	at. Supply 136 46	Maggiore Electronic Lab 104	317	Space Electronics 104
1 Adirondack Radio Supply.	Inc 169	478 Gilfer Associates		Magnetic Call Sign	309	Spacecoast Research 173
314 Alliance Mfg. Co		28 Godbout Electron	nics	Micro Control Specialties78, 136	67	Spectronics
5 Amateur-Wholesale Electr	onics	352 Grove Enterprise	s	Micro Management Systems 28	68	Spectrum Comm
	23, 216	378 HVB		Microcraft Corp	73	TET, USA
7 American Crystal Supply.	173	345 Hal Comm		Micro-80, Inc		Ten-Tec, Inc
334 Amidon Associates	171	31 Hal-Tronix		Microlog Corp	76	Trac Electronics25
301 Appli, & Equip, Co., Inc		30 The Ham-Key Co		MidCom Electronics, Inc	77	Tufts Radio Electronics 150-161
8 Aptron Laboratories	163	32 Ham Radio Cente	er	Mor-Gain 51	361	UHF Sales & Service 104
* Associated Radio		33 Hamtronics, NY.		National Comm. Group Co	37	UPI Comm. Systems, Inc 111
358 Astron Corporation		476 Hamtronics, NY.		OK Machine & Tool		Universal Communications 173
10 Avanti Research & Develor	0 109	481 Heath Co		Optoelectronics, Inc	387	Urban Engineering51
11 Barker & Williamson	165	34 Henry Radio		Orbit Magazine	311	Vanguard Labs
483 Barker & Williamson	188	305 Hustler, Inc		P. C. Electronics	373	Van Gorden Engineering77
12 Bullet Electronics	. 208, 209	363 I-Can Company		Pagel Electronics146	90	VoCom Products Corp 131
477 Centurion International.	186	• IRL		Palomar Engineers25	79	Wacom Products 163
13 Cleag	101	* ICOM		Panasonic	80	Western Electronics171
89 Clutterfree Modular Conso	les 89	35 Info-Tech, Inc		Poly Paks		Wilson Systems, Inc 90, 116-119
14 Comm. Center, NE	87, 147	36 International Cry	stal Mfg90 60	Quest Electronics 197	82	Xitex Corp
382 Comm. Concepts, Inc	171	38 Jameco Electror	nics	Radio Amateur Callbook, Inc 91	83	Yaesu Electronics Corp.
377 Communications Electron	ics 196	479 Jameco Electroni	cs	Radio Systems Tech., Inc 171		Cov III, 67, 93
15 Comm. Specialists	10, 11	39 Jan Crystals		Radio World	336	Z Associates
16 Crown Micro Products		384 Jim-Pak Electron	ic Comp 80, 81 62	Ramsey Electronics 214, 217		
70 Cubic Communications, Ir	nc83	 Kantronics 		Rochester Hamfest		
20 DSI Instruments		482 Karetron Engine	ering 188 65	S-F Amateur Radio Services 105		
330 Debco Electronics	111	* KB Microcompu	ting	SK Electronics 104		
* Paul Davis Electronics	104	* Kenwood	Cov IV, 7 376	SMP79		
346 Data Service	173	375 Herb Kreckman	Co 104 64	Semiconductors Surplus		
365 Larry Dennison	146	* LaRue Electronic	s 169			
* Digital Research Parts		43 Lunar Electronics		Sentry Mfg. Co 165		
19 R. L. Drake Co	30, 31	47 MFJ Enterprises.		73 Magazine		
* 80 Microcomputing	149	48 MHz Electronics				
* Erickson Comm.	105	56 Macaw Electron	ics	Signalcrafters		





Bool	KS.	FT	C
	m p		U •

Catalog #	Item	Price
BK1016	73 DIPOLE & LONG WIRE ANTENN	AS
		.\$ 5.50
ST0000	73 BACK ISSUE	.\$ 3.00
ST2500	73 BACK ISSUES-25 OUR CHOICE.	.\$12.00
ST0500	73 BACK ISSUES-5 YOUR CHOICE	.\$ 8.75
ST1000	73 BACK ISSUES-10 YOUR CHOIC	E
		.\$14.00
ST2501	73 BACK ISSUES-25 YOUR CHOIC	E
		.\$25.00
BK7307	BEHIND THE DIAL	.\$ 4.95
BK7309	CHALLENGE OF 160	.\$ 4.95
CT7305	CODE TAPE-5 WPM	.\$ 4.95
CT7306	CODE TAPE-6 + WPM	.\$ 4.95
CT7313	CODE TAPE-13 + WPM	.\$ 4.95
CT7320	CODE TAPE-20 + WPM	.\$ 4.95
CT7325	CODE TAPE-25 + WPM	.\$ 4.95
CT7394	CODE TAPES (ANY FOUR ABOVE)	.\$15.95
BK7308	THE CONTEST COOKBOOK	.\$ 5.95
BK7381	40 COMPUTER GAMES	.\$ 7.95
BK7304	GIANT BOOK OF AMATEUR RADIO)
	ANTENNAS	.\$12.95
BK7322	HOBBY COMPUTERS ARE HERE	.\$ 4.95
BK7325	HOW TO BUILD A MICROCOMPUTI	ER &
	REALLY UNDERSTAND IT	.\$ 9.95
BK1028	IC OP AMP COOKBOOK	.\$12.95
BK7312	MAGIC OF HAM RADIO	.\$ 4.95

To order, complete the following postage-paid card, or itemize your order including detailed credit card information or check and mail to: 73 Magazine/Mail Order Dept./Peterborough NH 03458.

Catalog #	Item Price	
BK1033	MASTER HANDBOOK OF HAM RADIO CIR-	
	CUITS\$ 8.95	
BK7340	THE NEW HOBBY COMPUTERS\$ 4.95	
CT7300	NOVICE THEORY TAPES\$15.95	
BK7310	OWNER REPAIR OF RADIO EQUIPMENT	
	\$ 7.95	
BK7305	POWER SUPPLY HANDBOOK	
BK1015	PRACTICAL ANTENNAS FOR THE RADIO	
	AMATEUR\$ 9.95	
BK7302	PROPAGATION WIZARD'S HANDBOOK	
	\$ 6.95	
QW0250	QSL CARDS-STYLE W-250 \$ 8.95	
QW0500	QSL CARDS-STYLE W-500\$13.95	
QX0250	QSL CARDS-STYLE X-250\$ 8.95	
QX0500	QSL CARDS-STYLE X-500\$13.95	
QY0250	QSL CARDS-STYLE Y-250\$ 8.95	
QY0500	QSL CARDS-STYLE Y-500\$13.95	
BK1044	RF & DIGITAL TEST EQUIPMENT\$ 5.95	
BK7347	RTTY HANDBOOK\$ 5.95	
BK1059	RTL COOKBOOK\$ 6.50	
BX1000	SHELF BOX-1\$ 2.00	
BX1001	SHELF BOXES-2-7\$1.50 each	
BX1002	SHELF BOXES-8 AND UP\$1.25 each	
BK7351	SSB THE MISUNDERSTOOD MODE \$ 5.50	
CT7350	SSTV TAPE\$ 5.95	
SG1081	STUDY GUIDE-ADV. CLASS\$ 6.95	

Catalog #	Item Pric	e
SG1080	STUDY GUIDE-EXTRA CLASS\$ 5.	95
SG7358	STUDY GUIDE-GENERAL CLASS \$ 5.	95
SG7357	STUDY GUIDE-NOVICE CLASS\$ 4.	95
LB7359	TEST EQUIP LIB V1-COMPONENT	
	TESTERS\$ 4.	.95
LB7360	TEST EQUIP LIB V2-AUDIO TESTERS	
	\$ 4.	.95
LB7361	TEST EQUIP LIB V3-RADIO EQUIP \$ 4.	.95
LB7362	TEST EQUIP LIB V4-IC TEST EQ\$ 4.	95
BK7348	TOOLS & TECHNIQUES \$ 4.	95
BK1063	TTL COOKBOOK \$ 9.	.50
BK1064	TVT COOKBOOK \$ 9	.95
BK7382	UNDERSTANDING & PROGRAMMING	
	MICROCOMPUTERS\$10	.95
BK1069	VERTICAL BEAM & TRIANGLE ANTNS	
	\$ 5	.50
BK7368	VHF ANTENNA HANDBOOK	.95
BK7370	WEATHER SATELLITE HANDBOOK.\$ 4	.95



peterborough, n.h. 03458

With the Yaesu FT-480R . . . **TWO METERS COMES ALIVE!**

1420000

ET-480R

SSB activity is flourishing, repeater activity is at an all-time high, and OSCAR users are breaking records every day. Let the FT-480R step you up to space-age performance on SSB, CW, and FM.

Features

Coverage of 143.5 - 148.5 MHz (good news for

Built-in tone burst generator

- you MARS operators)
- USB, LSB, CW and FM operation are all built-in
- Four channels of memory, with priority channel
- Two VFOs for unusual repeater splits
- Convenient synthesizer steps: 10 Hz, 100 Hz, or 1 kHz per step on SSB/CW, 1 kHz, 20 kHz, or 100 kHz per step on FM
- Scanning control from microphone
- Highly effective noise blanker
- Receiver offset tuning for following Dopplershifted signals
- SAT switch allows shifting of transmit frequency during OSCAR operation (many rigs cannot QSY on TX)
- 30 watts DC input on FM/CW, 30 watts PEP input on SSB, HI/LOW power selection on FM and CW



- Bright LED signal strength/relative power output level meter
- Easy-to-read fluorescent display of operating frequency and memory channel
- Front panel switch for zeroing synthesizer to convenient step when changing modes from SSB/CW to FM
- Requires 13.8 VDC, negative ground

Available Options:

FP-80 AC Power Supply FTS-64E Synthesized CTCSS/Burst Encoder

> Price and specifications subject to change without notice or obligation

> > ×83

Did You Know . . . Yaesu now has a crystal-controlled 220 MHz FM rig - The FT-127

The radio. 1080

YAESU ELECTRONICS CORP., 6851 Waithall Way, Paramount, CA 90723 (213) 633-4007 YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246

New 2-meter direction.



PS-20

TR-9000

A compact transceiver with FM/SSB/CW plus...

TR-9000

Kenwood's done it again! Now, bet! Because of its compactness, the TR-9000 is ideal for it's the exciting TR-9000 2meter all-mode transceiver... mobile installation. Add on its fixed station accessories and complete with a host of new it becomes the obvious choice features. Combining the confor your ham shack! venience of FM with long distance SSB and CW in a very See your Authorized Kenwood compact, very affordable **Dealer now for details on the** package, the TR-9000 is the TR-9000...the new direction answer for any serious Amain 2-meter all-mode transteur Operator! Versatile? You ceivers!

Note: Price, specifications subject to change without notice and obligation.

B0-9

SP-120

UP/DOWN microphone (standard) ..."beep" sounds with each frequency step.



1111 WEST WALNUT/COMPTON, CALIFORNIA 90220